

EE451 HW #2

Q1, Implement the following Boolean equations using transistor level and gate level implementations, and compare the Cons and Pros of them.

1. $F=(AB+C(D+XY))'$

2. $F=(A+B)(C+XY)$