

### ECE451 Homework #3

1. Draw the schematics for the following functions using NOR gates and inverters only
  - a.  $\overline{X} + (\overline{Y + Z})$
  - b.  $\overline{(\overline{X + Y}) + (\overline{X + Z})}$
  
2. Draw the schematics for the following functions using NAND gate and inverters only
  - a.  $\overline{X(\overline{Y} \overline{Z})}$
  - b.  $XY + XZ$
  
3. Prove the following simplification theorems using the first eight laws of Boolean algebra
  - a.  $(X + Y)(X + \overline{Y}) = X$
  - b.  $X(X + Y) = X$
  - c.  $(X + \overline{Y})Y = XY$
  - d.  $(X + Y)(\overline{X} + Z) = XZ + \overline{X}Y$