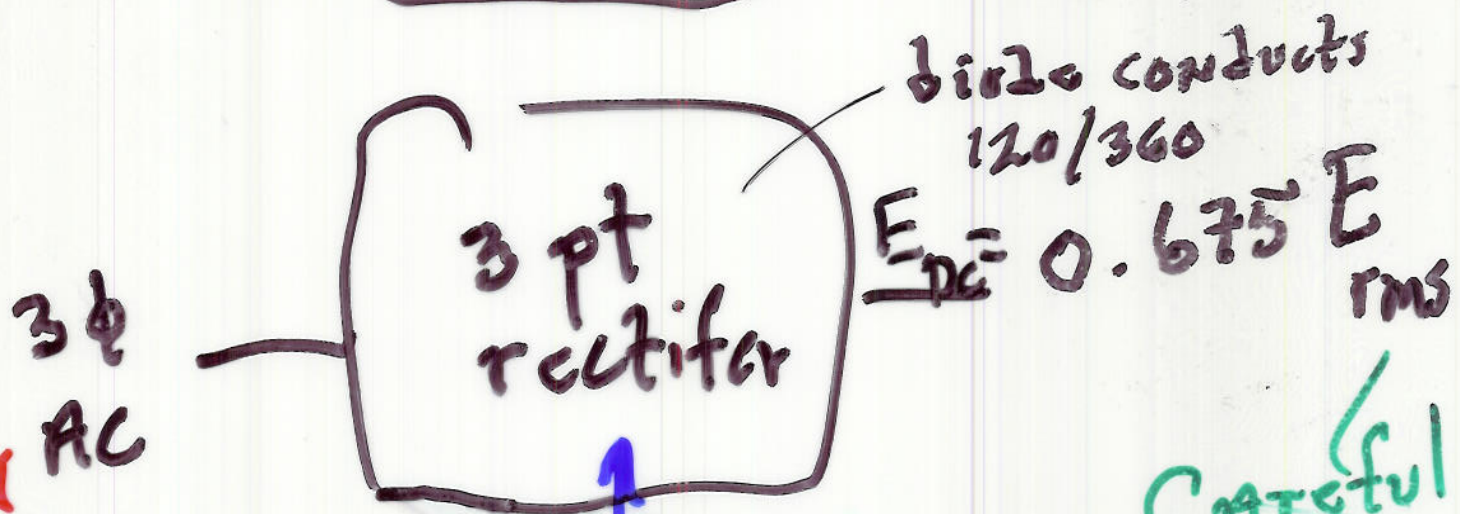


3 diodes only  
3 pt / 3  $\phi$  rectifier  
is analagous to  
1 pt / 1  $\phi$  rectifier

full wave  
1  $\phi$   
 $0.9 E_s$




3 Phases  
are fed  
line to neutral

later 6 point  
rectifiers

Careful

60mV 345mV - 130KV 55


Figure 21-16 Three-phase, 3-pulse rectifier with inductive filter fed by a 3-phase transformer.

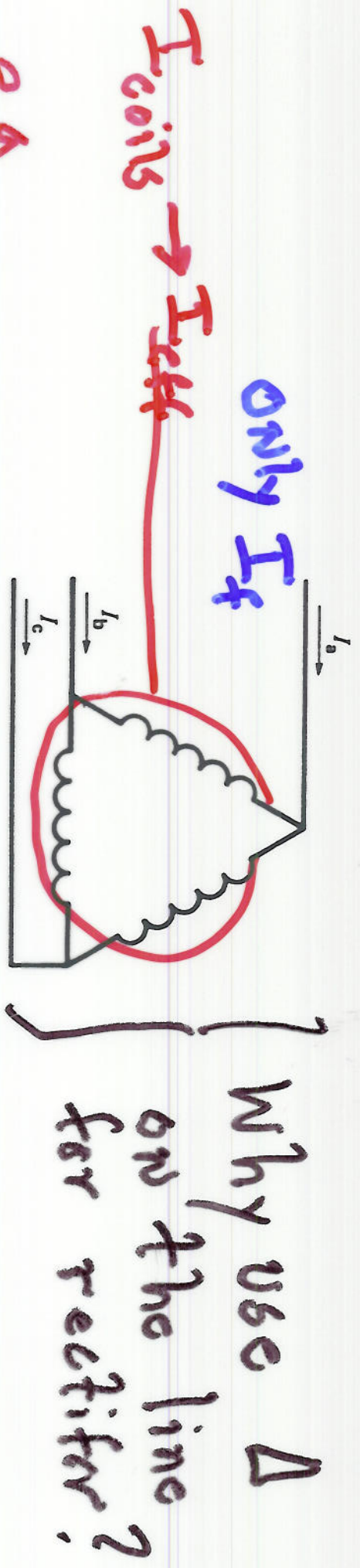

e.g

$E_{LN} = 2400 \text{ rms}$

load across  $\sqrt{3} E_{LN}$

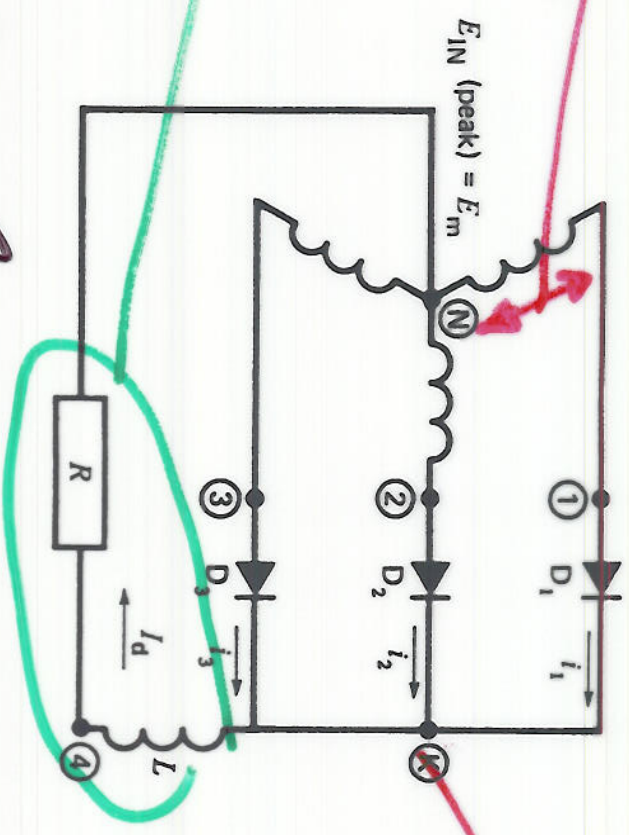


$E_{out} \text{ is } \sqrt{3} E_{LN}$

$E_{DC} = ?$   
 $I_{diode} = ? \text{ if } I_R = 660 \text{ A}$




Load is between LINE & NEUTRAL

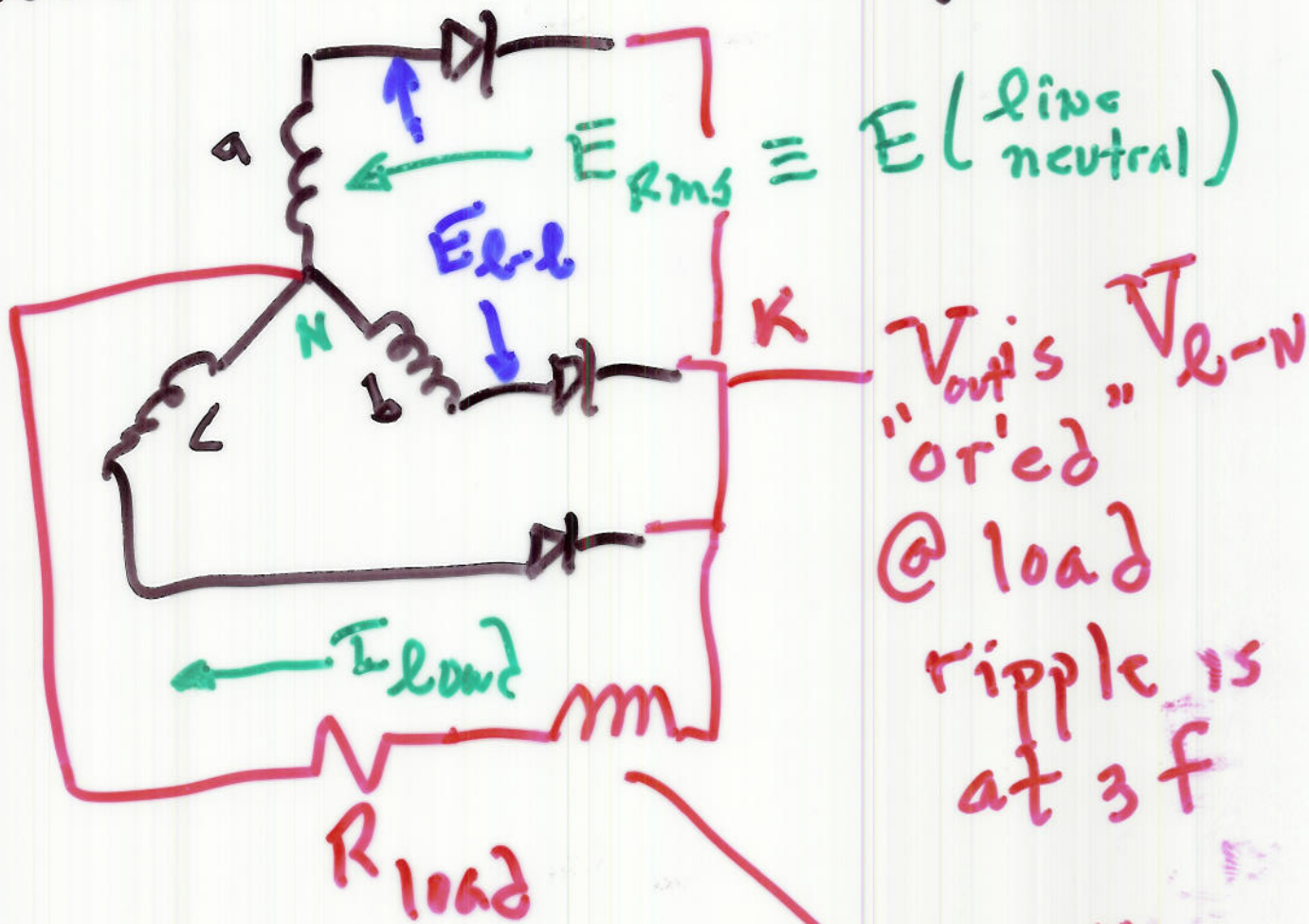

$$E_{LL} = \sqrt{3} E_{L-N}$$

use for

Diode P.I.N. = ?

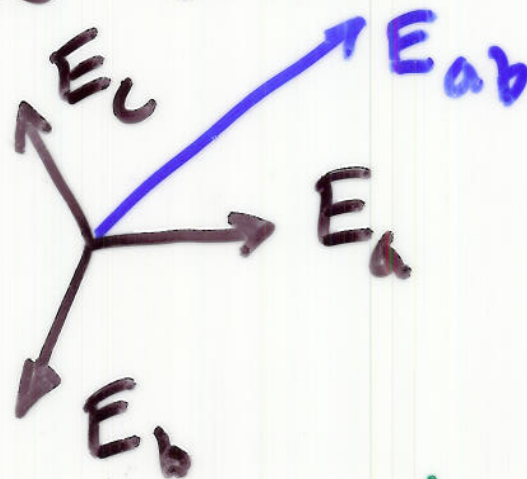


"Key" "Large"  $L$

$\Rightarrow$

$L$  is a  $\square$ -wave

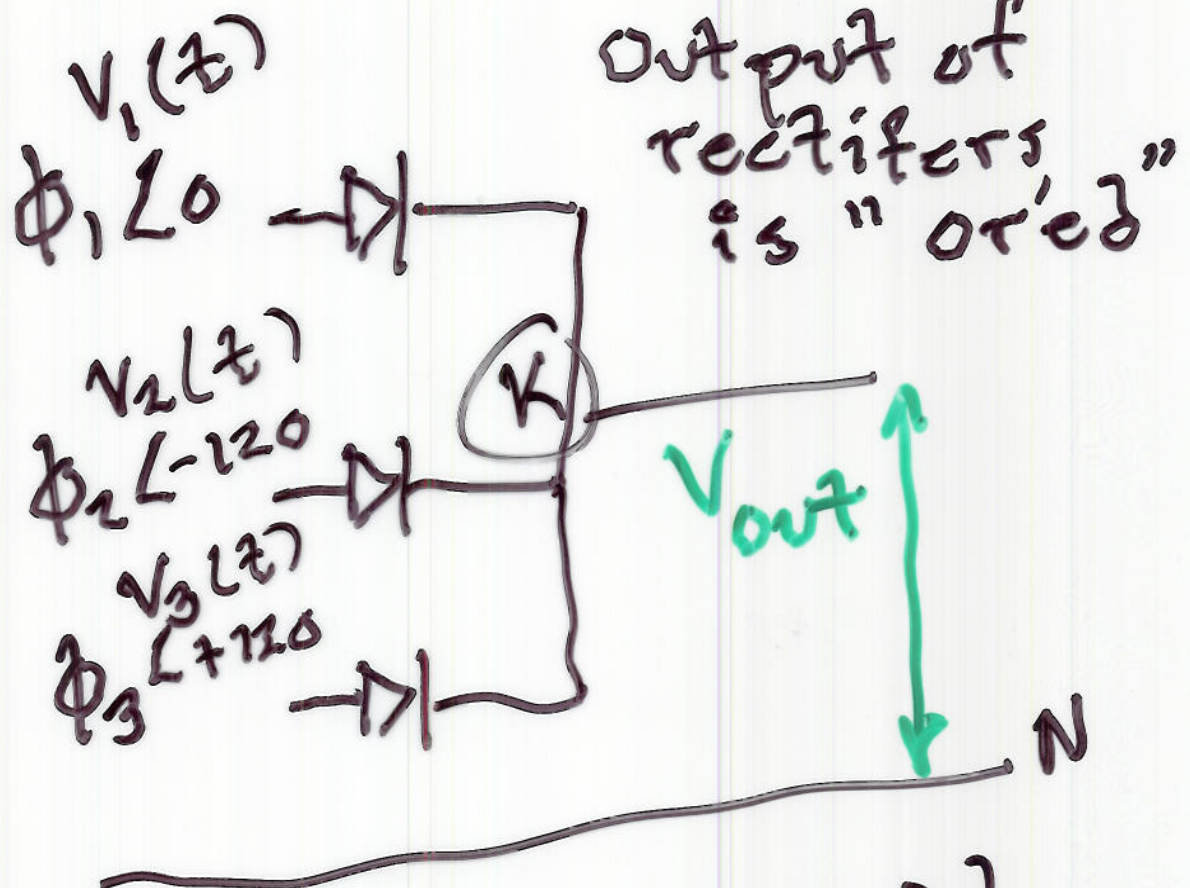Each diode peak  $i = I_{load}$  } But  $I_{AV} = I_L/3$



$V(60^\circ)$  →  $\frac{V(\text{sinusoid})_{\max}}{2}$   
 Recall

With 3 phases the "OR"  
 One phase dominates for only 120°  
 circuit changes

$-60 \rightarrow 60^\circ$

$60 \rightarrow 180$

$180 \rightarrow 300$

$V_o = V_1(t)$  largest  
 $V_o = V_2(t)$  "  
 $V_o = V_3(t)$  "



## Summary 3 Point

① Every 120° diode conduction changes due to

Phase 1 largest  $|V_{in}| - 60^\circ \rightarrow +120^\circ$

$\Rightarrow$  Diode 1 ON  $D_2$  off  
 $D_3$

Phase 2 largest  $|V_{2n}| + 60^\circ \rightarrow +120^\circ$

$\Rightarrow$  Diode 2 ON  $D_1$  off  
 $D_3$

②  $i_{diode}^{AV}$  ON  $\left(\frac{120}{360}\right) = \frac{1}{3}$  time on  
 $\frac{2}{3}$  off

③  $\Rightarrow i_{(transformer)} \approx$   
 $\frac{1}{3}$  ON  $\frac{2}{3}$  off



$$E_{DC} (eff) = 0.675 E_{rms}$$

Minimum voltage:

$$\Delta E_{L-R} = \frac{E_{pk}}{2}$$

3 half waves of

$$E_m - \frac{E_m}{2} = \frac{E_m}{2}$$

$$E_{pk} - \frac{E_{pk}}{2} = \frac{E_{pk}}{2}$$

$$E_{av} = \frac{3 \left( \frac{E_{pk}}{2} \right)}{\pi} = \frac{3 E_{pk}}{2\pi} = \frac{3 \sqrt{2} E_{rms}}{2\pi}$$


$$E_{av}^{3\phi} = \frac{3}{\sqrt{2}} \left( \frac{1}{\pi} \right) E_{rms}^{L-R} \text{ or } (0.675)$$

$$E_{av}^{6\phi} (\text{full wave rectifier}) = ? \text{ guess}$$



Longer term

Figure 21-17 Voltage and current waveforms in a 3-phase, 3-pulse rectifier.

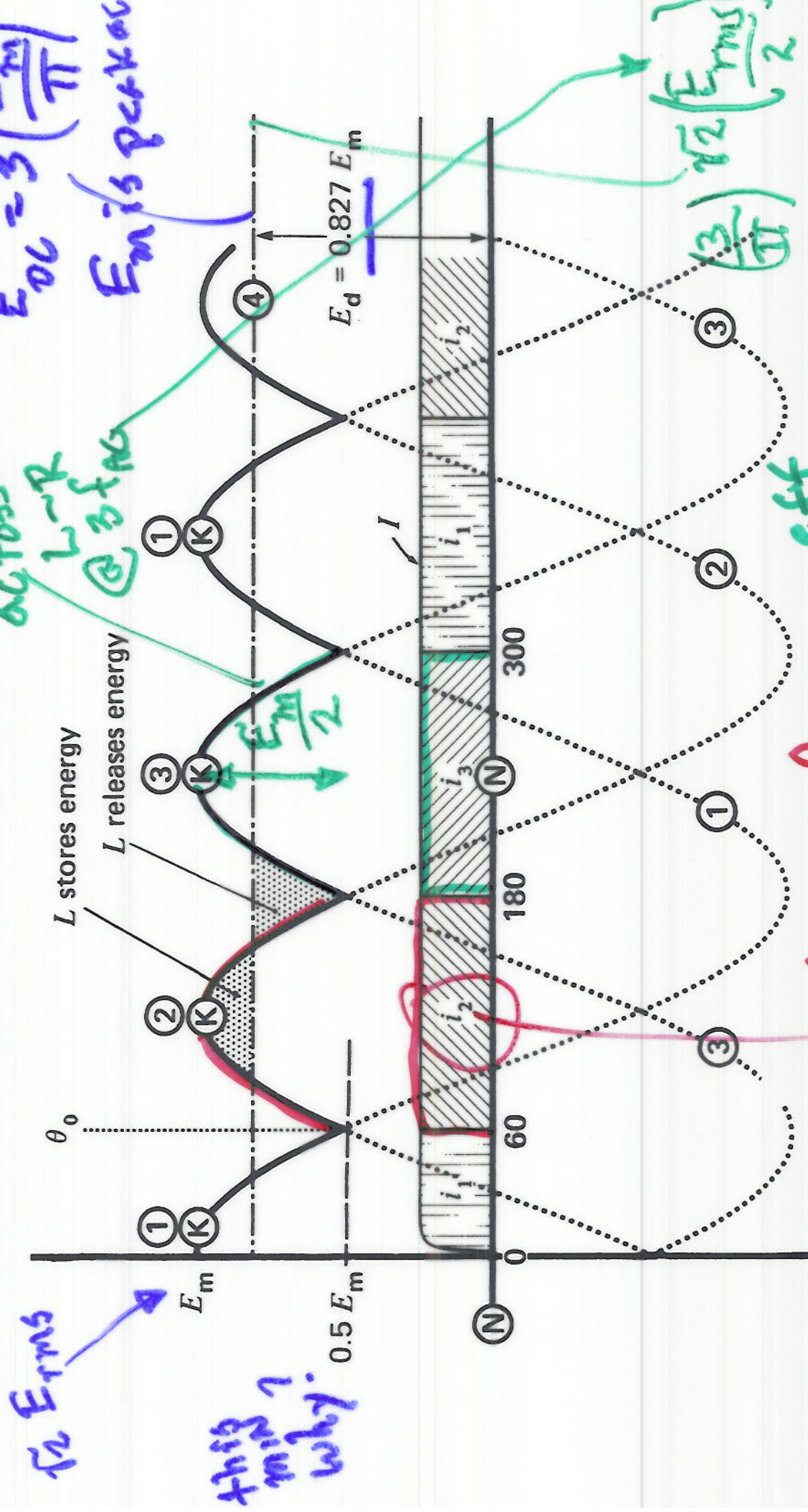

$E_{dc} = 3 \left( \frac{E_m}{\pi} \right)$   
 $E_m$  is peak ac  
 $V_{dc}$  across  $L-R$  @ 3 f ac  
 $E_d = 0.827 E_m$   
 $\sqrt{2} E_{rms}$   
 $\frac{E_m}{2}$   
 $\left( \frac{3}{\pi} \right) \sqrt{2} E_{rms}$   
 $E_{dc} \approx 0.675 E_{rms}$   
 $E_{dc}^{eff} = 0.675 \sqrt{2}$

ON for 120°


Reality check:  $0.827 =$



1) Peak

1) Ripple is 3% mains

2)  $E_{eff}(dc)$

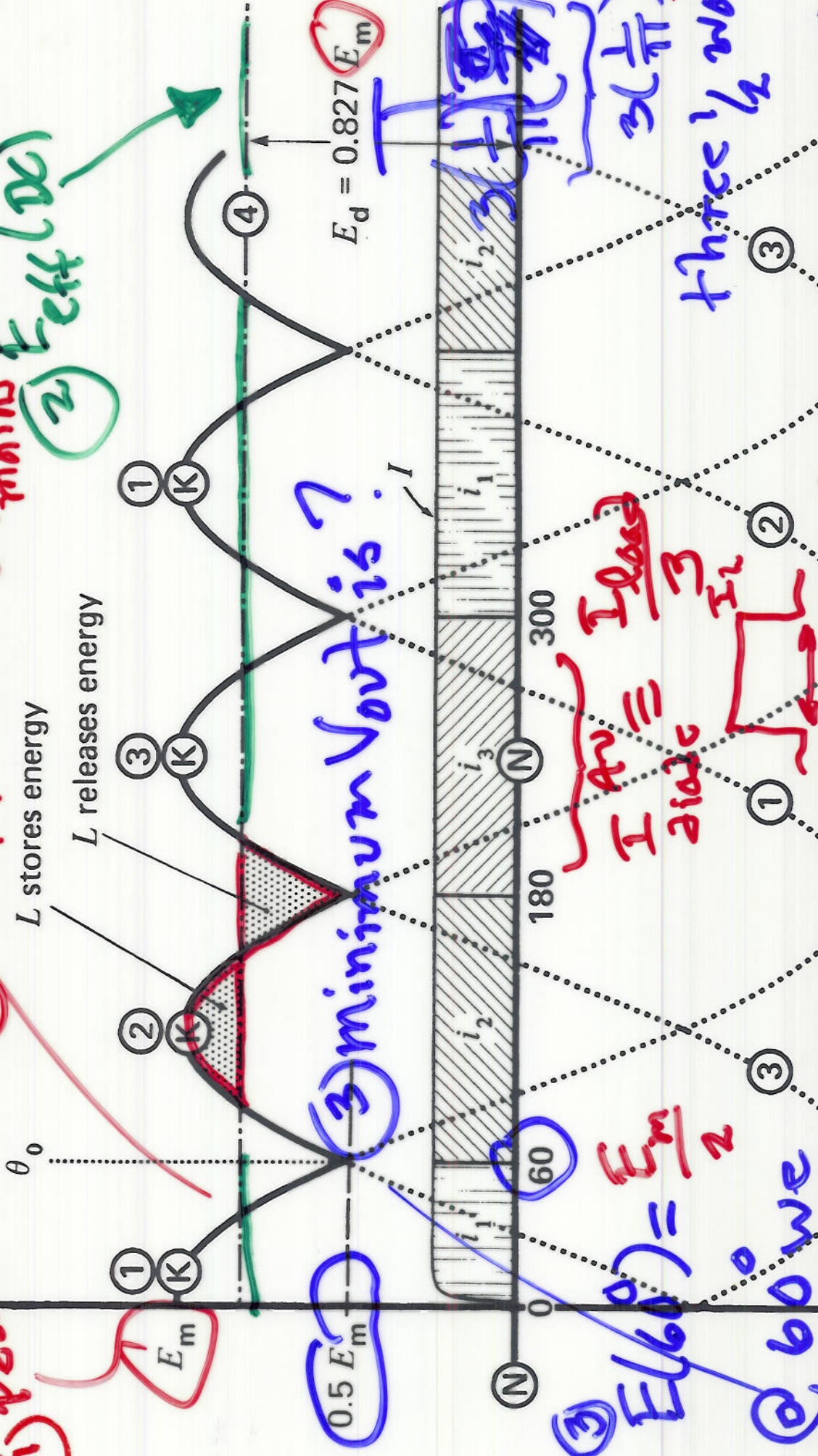

3) minimum Vout is?

3)  $E(60^\circ) = \frac{E_m}{2}$

@ 60° we have  $E_{out}$  taken over by phase 2

$I_{avg} = \frac{I_{dc}}{3}$   
 $I_{avg} = \frac{I_{dc}}{3}$

three 1/2 waves  
 $E_{dc}(eff) = \frac{3}{\pi} \frac{12 E_{rms}}{2} = 0.675 E_{rms}$