


$I$  (fundamental)  
AC



$I_o(DC)$

$$V_{DC} = 0.9 V_{rms}$$
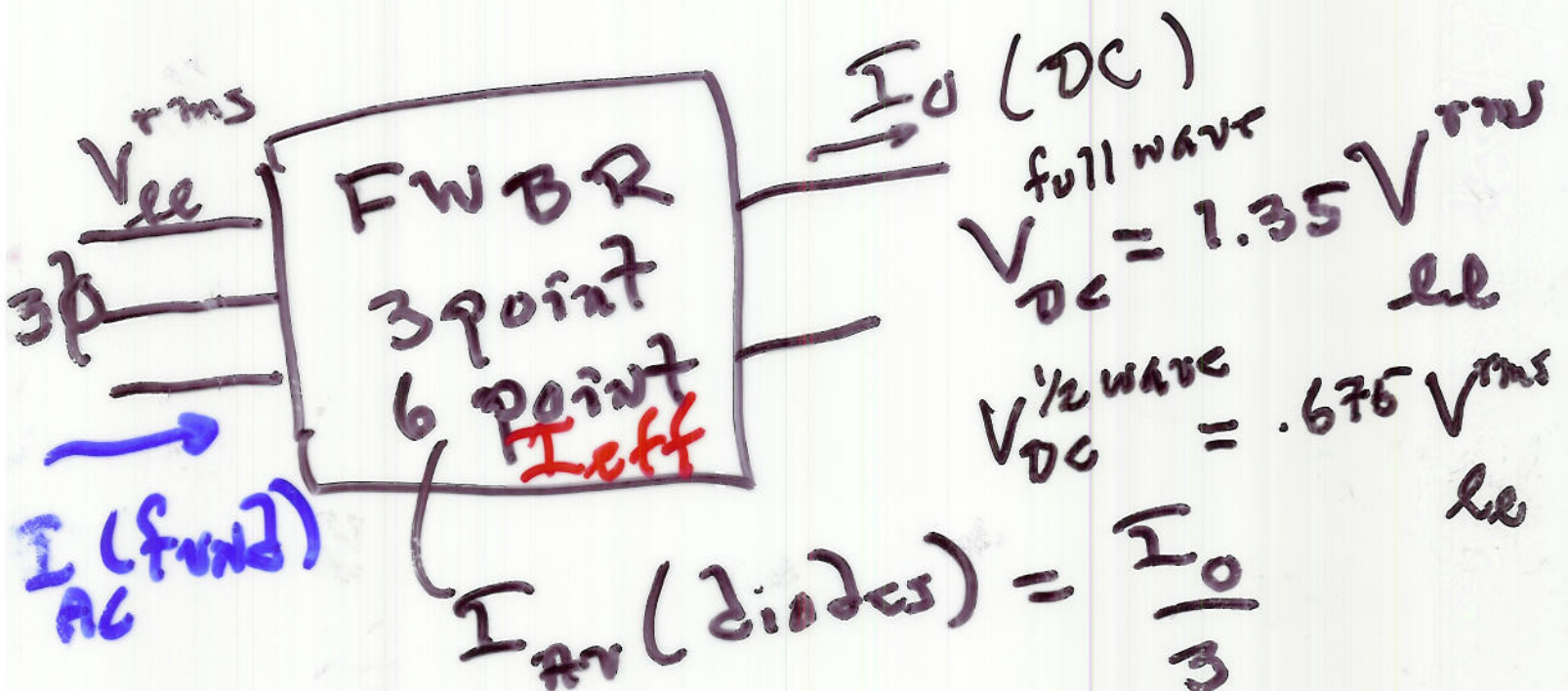
$$I_{Av}(2\text{ diodes}) = \frac{I_o(DC)}{2}$$



$$V_{DC} = 1.35 V_{LL}$$

$$V_{DC}^{1/2 \text{ wave}} = .675 V_{rms \text{ LL}}$$


$$I_{Av}(2\text{ diodes}) = \frac{I_o}{3}$$

$R_{load}$




R-L Load

big

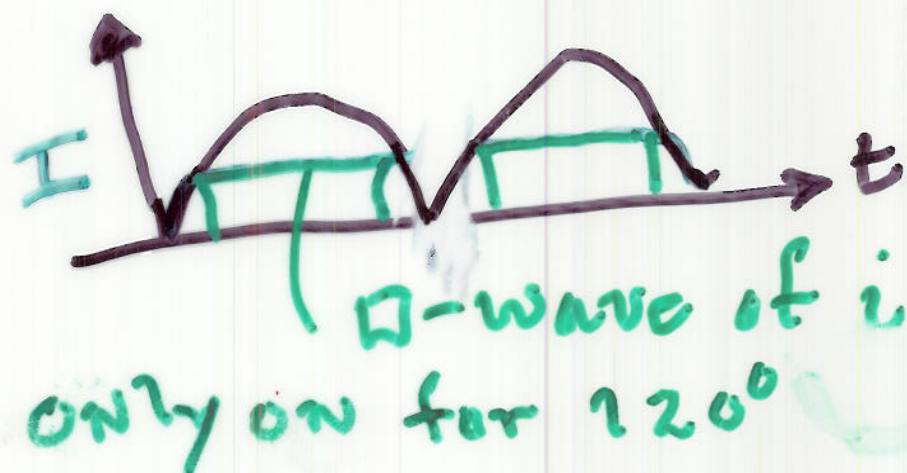


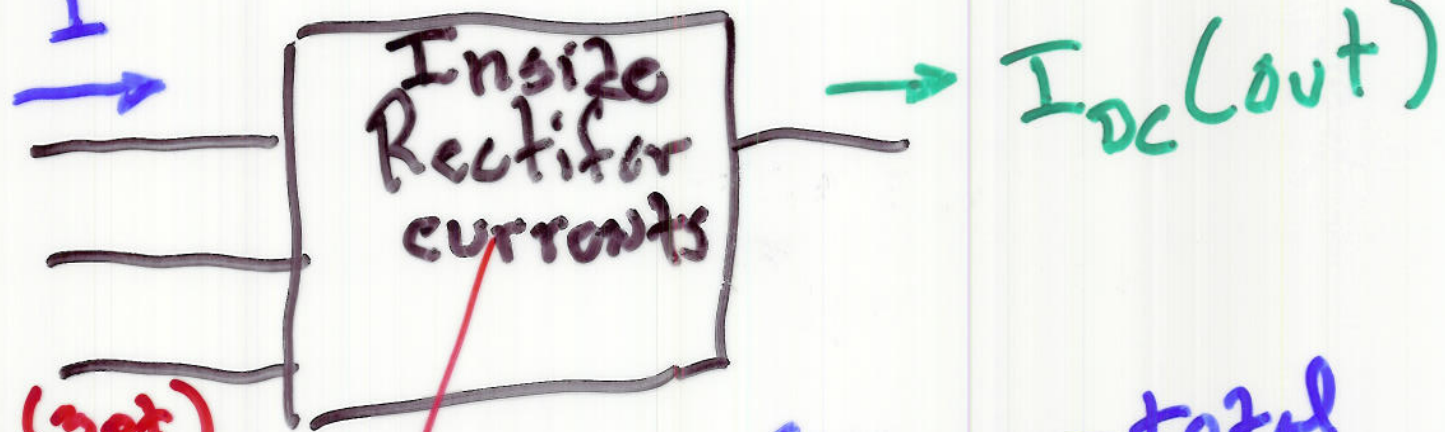
Mains can only supply  $I_{Ac}$  fundamental  
 If Load is DC



$i(t)$  on the transformer coils  
 =  $i(t)$  diodes


$$I_{ac}^{eff} = I_f^2 + I_{H}^{total}$$

diode  $i(t)$

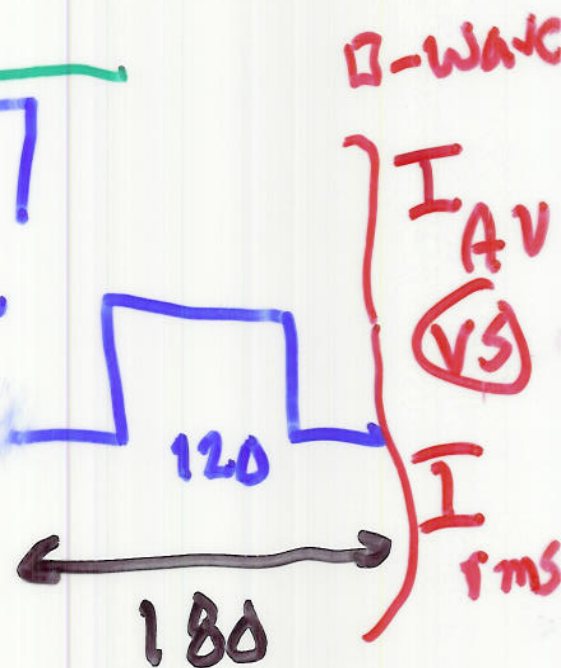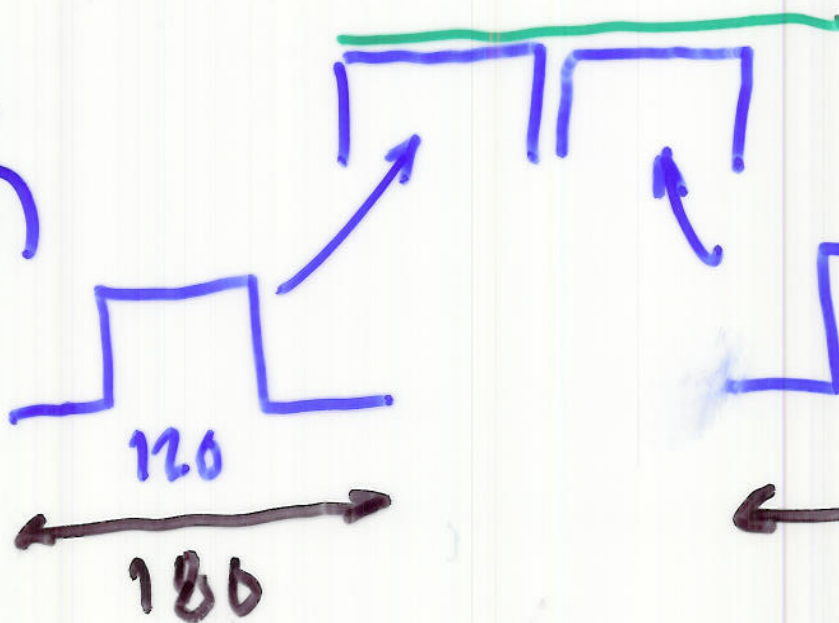



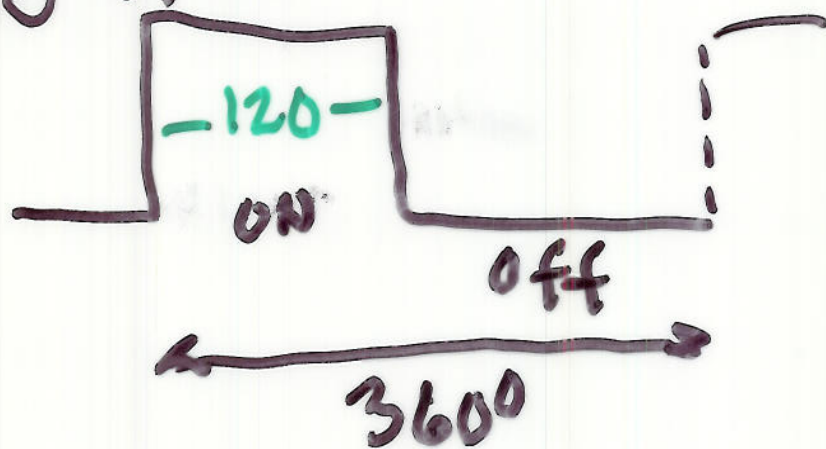□ - Waves :  $I_{Av}$  vs  $I_{Rms}$   
diode  $i(t)$



←  $I_{peak} = I_{DC}$

$$I_{Av}^{diode} = \frac{120}{360} I_{DC} = \frac{I_{DC}}{3}$$

$$I_{Rms} = \sqrt{\frac{120}{360}} I_{DC} = 0.816 I_{DC}$$

$I_{eff}$




later lectures

$$I_{eff}^2 = I_F^2 + I_H^2$$

Now only find relation  $I_{eff} \leftrightarrow I_F$   
See Pbm 21.29

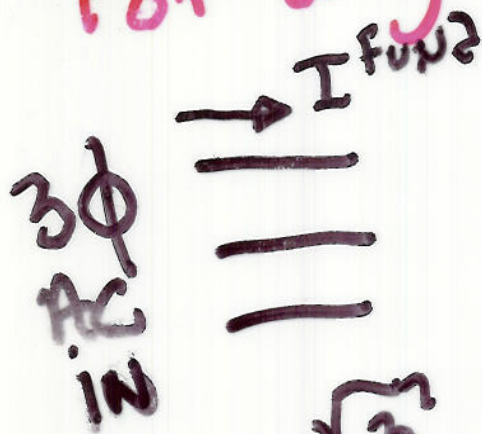For a given DC load:  $P = E_{dc} I_{dc}$



$$P_{AC} = \sqrt{3} E_{AC} I_{AC}$$

$$\sqrt{3} E_{AC}^{ll} I_{AC}^{fund} = E_{dc} I_{dc}$$

Mains only sources  $I_{fund}$

$$I_{AC}^{fund} = \underbrace{\frac{1.35}{0.816} \frac{1}{\sqrt{3}}}_{.955} I_{AC}^{eff}$$



Due to harmonics

$$|I(\text{fundamental})| < I_{Ac}^{\text{eff}}$$

$$\text{Distortion Power Factor} \equiv \frac{\text{Active Mains Power}}{\text{Effective Power}}$$

$$= \frac{\sqrt{3} V_{LL} I(\text{fund})}{\sqrt{3} V_{LL} I_{Ac}^{\text{eff}}}$$


$$\text{distortion p.f.} = \frac{I_F}{I_{\text{eff}}} = 0.955$$

$$I_{\text{eff}}^2 = I_F^2 + I_H^2$$


$$\text{Total Harmonic Distortion} = \frac{I_H}{I_F}$$

Coming

Displacement P.F.

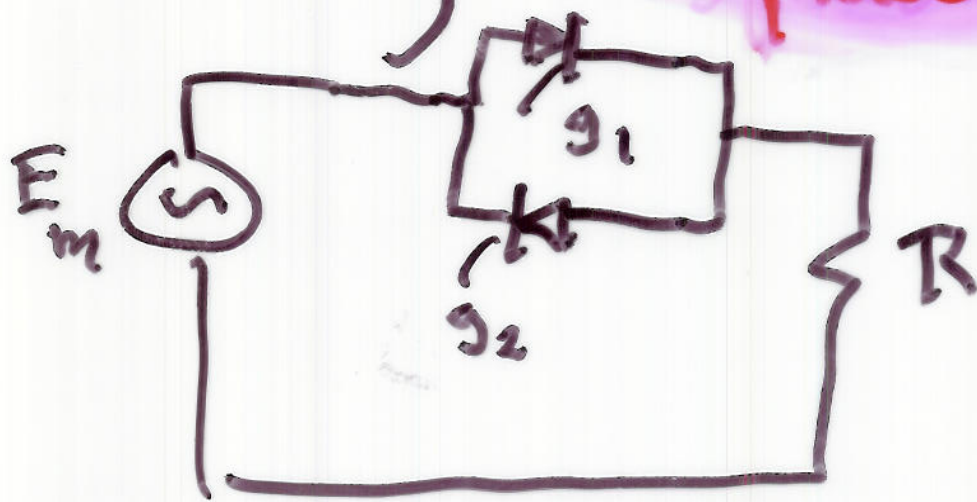

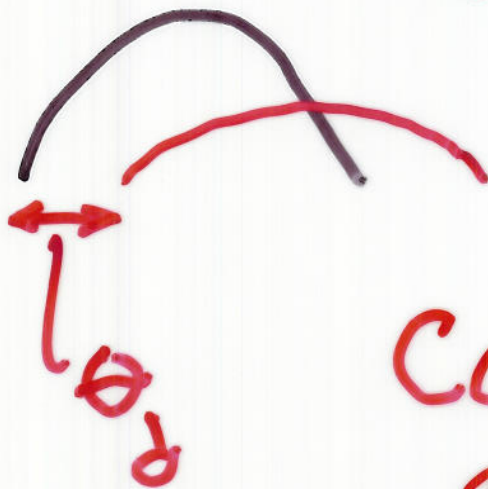express periodic  $i_R(t)$   
terms of fundamental @  $f_m$   
harmonics @  $nf_m$



$\cos \theta_d \equiv$   
Displacement  
Power factor