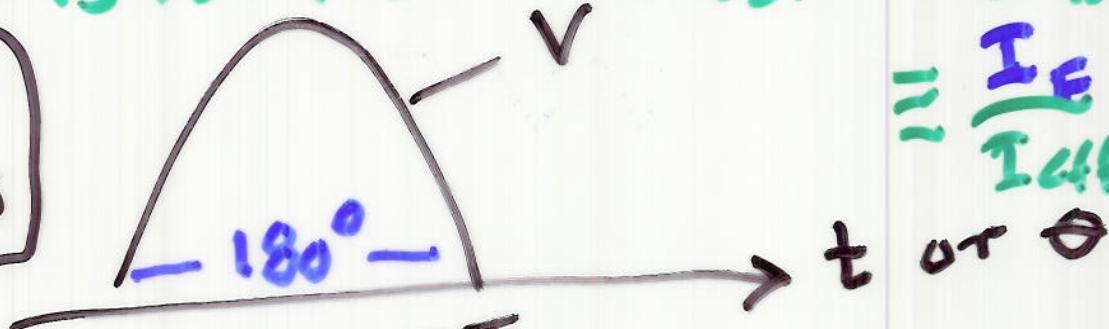



Distortion Power Factor

1 ϕ
Case



$$\equiv \frac{I_E}{I_{CH}} = 0.955$$

FWR

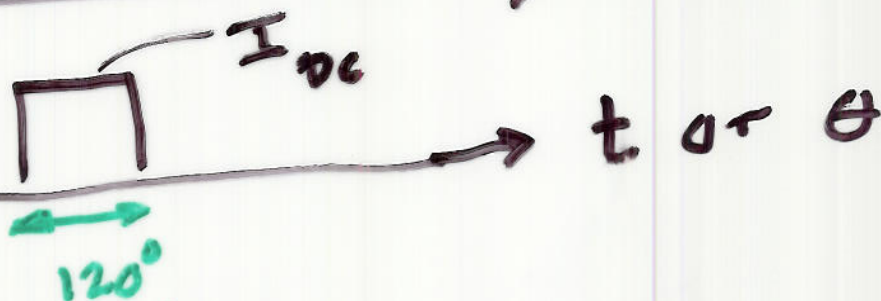

$I_{eff}^{in AC}$ (is sinewave
fundamental
plus
harmonics)

Use

$$\equiv I_{DC} \sqrt{\frac{120}{180}}$$

$I_{eff}^{in AC}$

$$= \left(\frac{120}{180} \right)^{1/2} I_{DC}$$

0.816

$\neq I_{rms}^{fund} (line)$

$\frac{I_{AC}^{eff}}{0.816}$


For the fundamental line

$$\sqrt{3} E_{rms} I_{rms}^{fund} \equiv E_{DC} I_{DC}$$

$$I_{rms}^{fund} = \left(\frac{1.35}{\sqrt{3}} \right) \frac{1.35 E_{rms}}{0.816} = 0.955 I_{CH}$$

Fig 21.18
pg 485

Get just
Add two 3 points together?

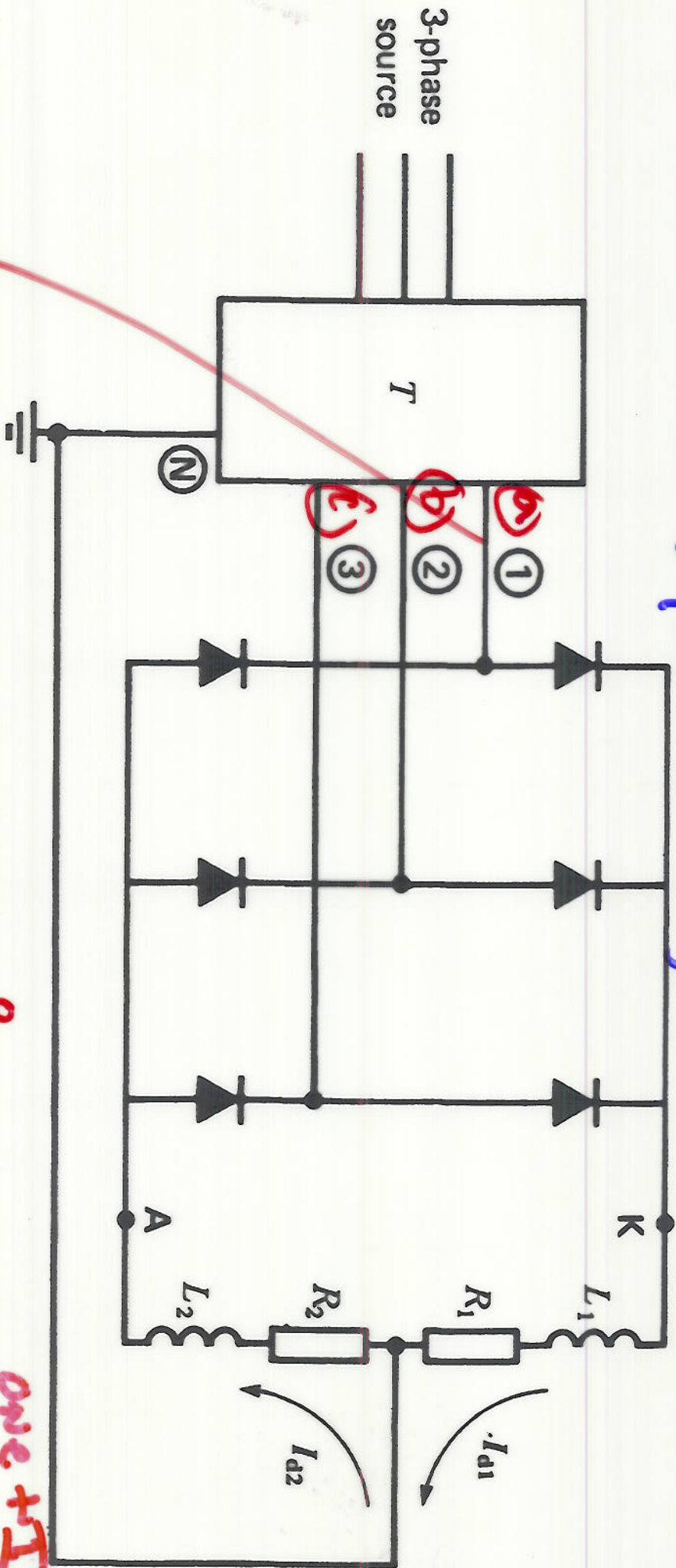


I will flow for $\frac{240^\circ}{360^\circ} \approx \frac{2}{3}$ time one - I

I_{d2} will flow $120/360 \approx \frac{1}{3}$ time

one + I

1/4

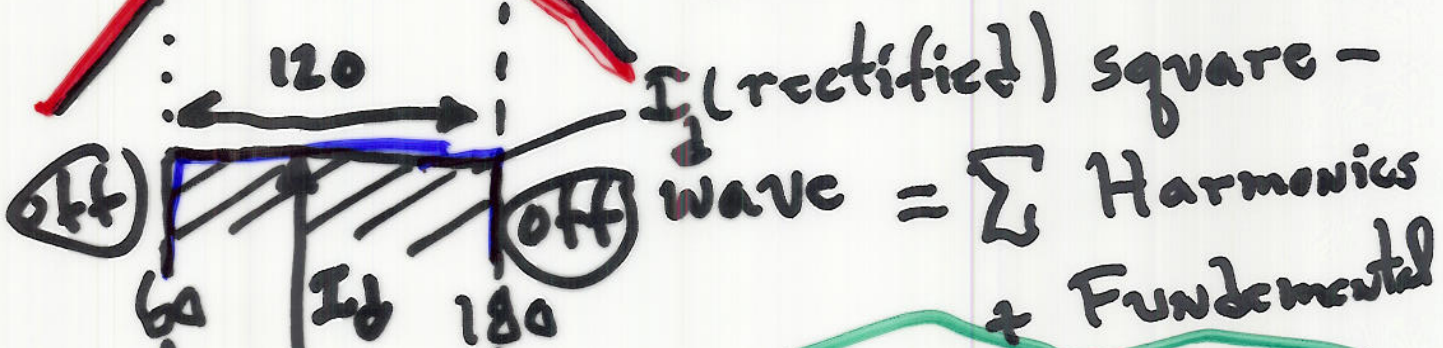V (rectified) 6 pt 1-42
rectifier
With "L Filter"



Consider case
 I (120 square)
 I_{eff} wave
all frequencies

$\Rightarrow I_{eff} \neq$ funde-
mental
Not yet!

$$I_{180} = I_D \quad 120 \quad I_D (\text{peak})$$

i from
mains
fundamentals

$$I_{eff} = .816$$

I_D (peak of \square -
wave)


fundamental i

all harmonics of i

effective
means

$$1.35 E_{rms}$$

Consider AC to DC Converter

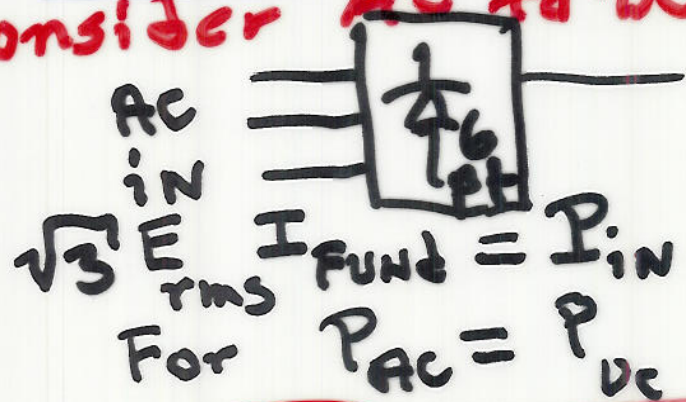

$$P_{DC} = E_{DC} I_{DC}$$

$$I_{DC} = I_{eff} / .816$$

$$I_{Fund} = .78 I_{DC}$$

$$.78 = \frac{1.35}{\sqrt{3}}$$


$$= \frac{1.3}{1.7}$$

$$I_{Fund} = 0.955 I_{eff} \text{ (due to all harmonics)}$$

$V_{out}(DC) \text{ vs } E_{rms} \text{ (per pulse)}$

ripple is
~~6.75~~ remains

Fig 21.21
 pg 1188

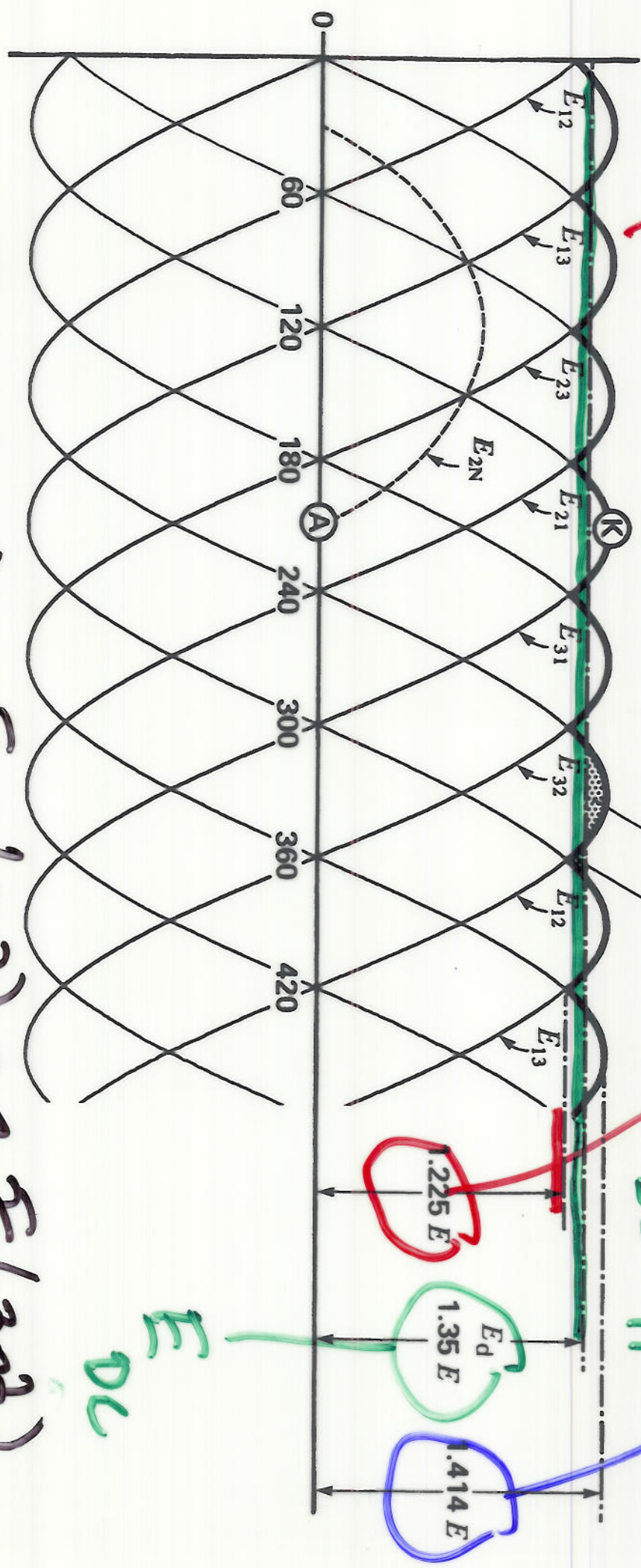

E_{min}
 E_{DC}
 E_{peak}
 $> E$

Intuitively $E_{DC}(6pf) = 2 E(3pf)$


$E_{DC}(6pf) = 1.35 E_{rms}$
 not 1-2
 $\cdot 675 E_{rms}$

Point Ripple on $E_{DC} (V_{avg}) \approx 20\% E_{RMS}$

$E = 1.414 E_n$ Use E_{AC} neutral for E_{DC}

$E_{DC} = 1.35 E_{RMS}$ L stores energy L releases energy

$E_{max} = \sqrt{2} E_{RMS}$

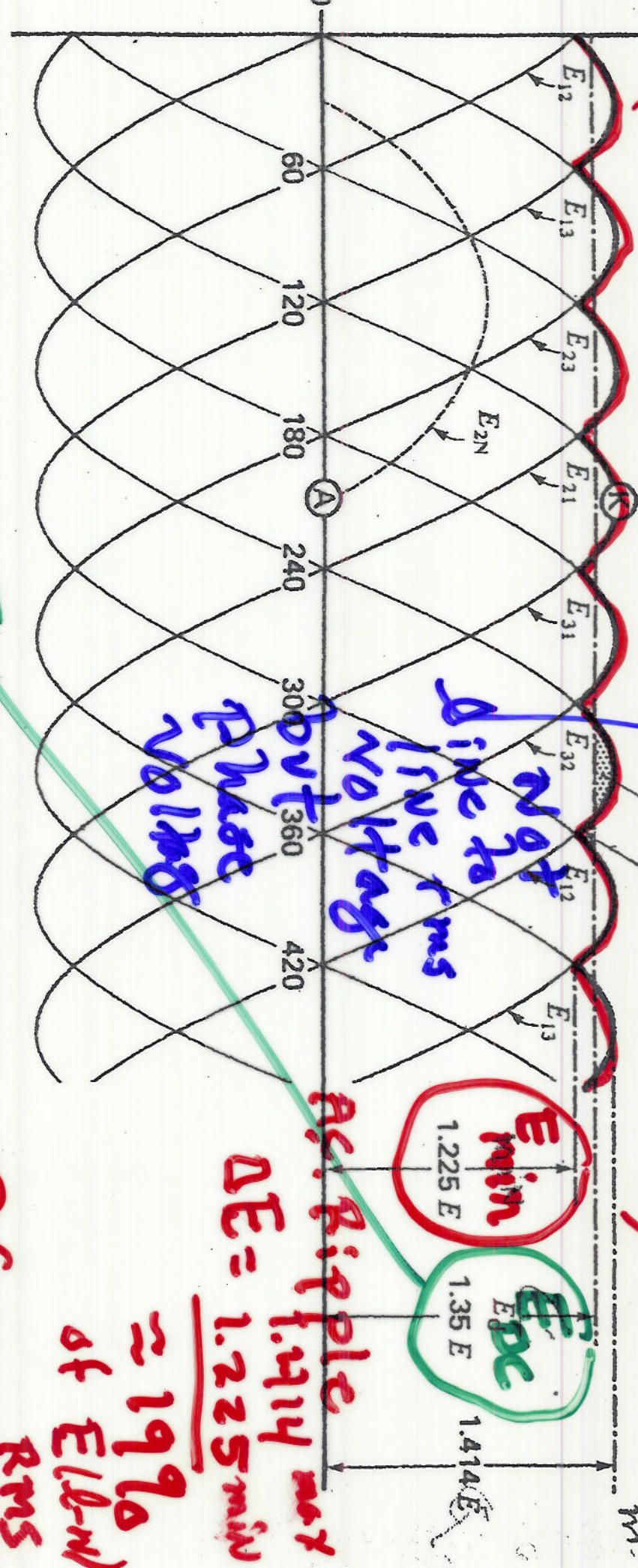

Line to
line rms
phase
voltage

$E_{DC} = 1.35$

675

familiar?

@ f

$\approx 6f_{RMS}$

≈ 1990

$\Delta E = 1.225 E_{min}$


300-360 Hz

way of showing E_{KA} using line voltage potentials. Note also the position of E_n with respect to the

1-28

Consider two stacked
3 point rectifiers. Each
 stack operates separately.
 If balanced $I_N = 0$

$$V_{L-N} = \frac{V_{L-L}}{\sqrt{3}}$$

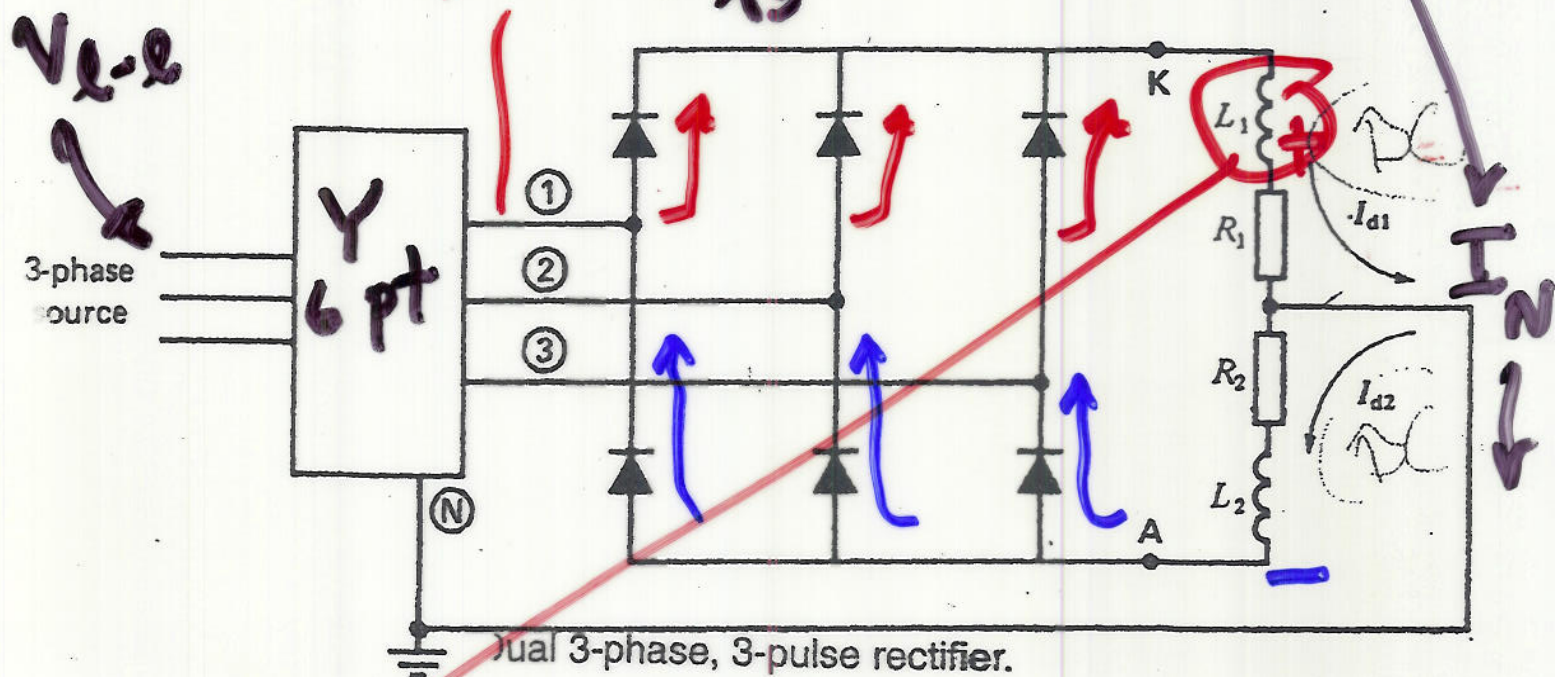


Additional role of "L" is short
 circuit protection as well as $\frac{di}{dt}$
 If $E_{out} = 250V$ and we
 suddenly short out R

$$I(\text{initial}) = 1KA$$

$$\text{limit } I_{max} = 3KA \text{ in } 5ms \} L = ?$$

¹¹ 3 ϕ 6 Pulse Rectifier ¹¹ Fullwave ₁₋₂₇

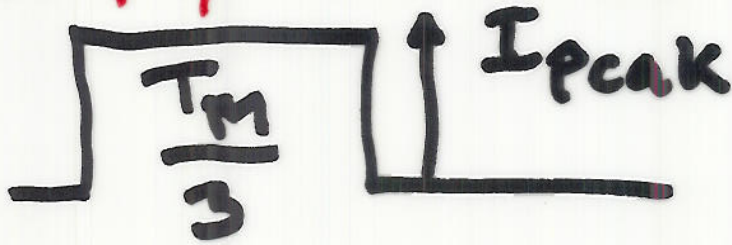employs Twice as many diodes and often $V_{ac}(in) = L-L$ Not phase



How to increase on duty cycle above $\left(\frac{120}{360}\right)$?

We cannot! But we can overlap more current pulses than 3. The duration $\left(\frac{120}{360}\right)$ is fixed but more

\square -waves of i is possible

Overlapping intervals will reduce each diode peak current also. 😊

$(I_{peak} \downarrow \Rightarrow \text{Cheaper diode})$
CAN be used


1
30

Six ~~total~~ line currents feed two diodes


$$\begin{aligned} I_a &= i_1 - i_4 \\ I_b &= i_2 - i_5 \\ I_c &= i_3 - i_6 \end{aligned}$$

Diode currents flow for 120 only when 360
 $V_o(\text{lin}) - V_K > 0$

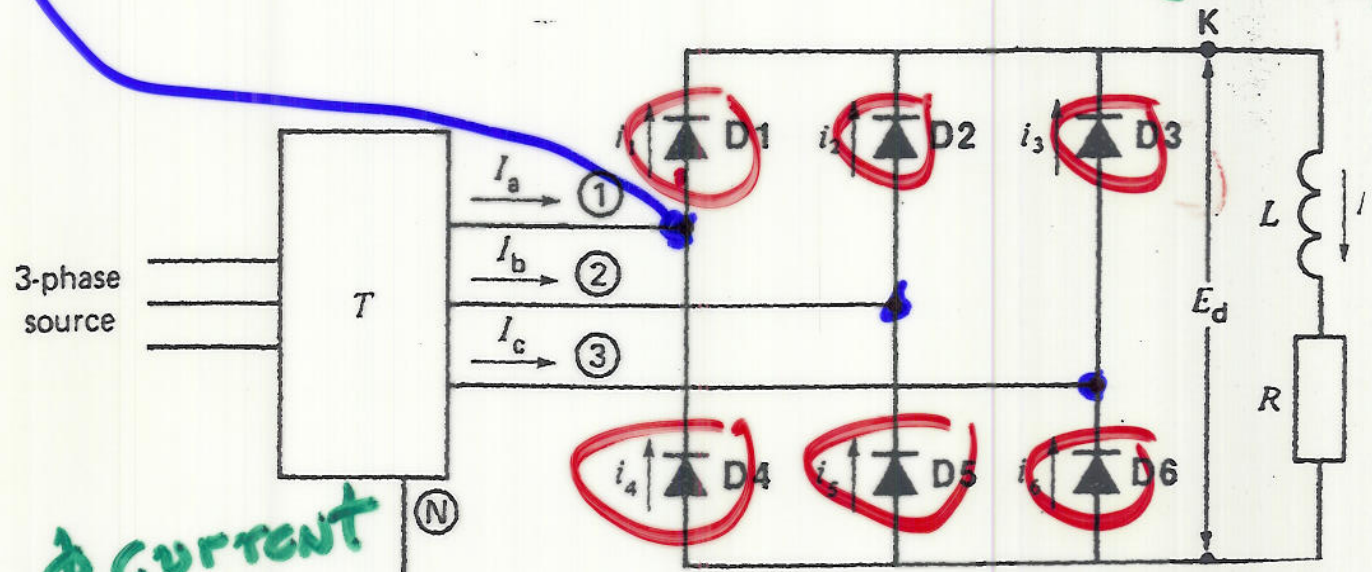Phase currents flow $\left(\frac{240}{360}\right)$



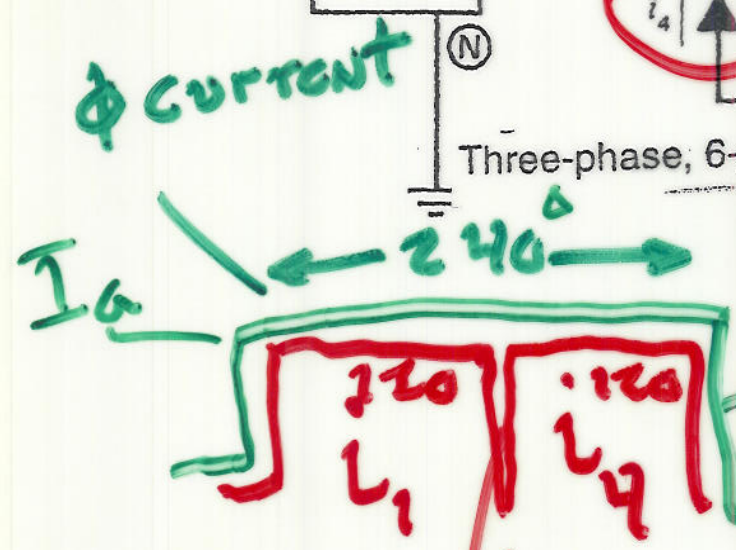Three-phase, 6-pulse rectifier with inductive filter.



Still Chopped, I_a but less
 (EMC) due to 240/360
 (EMI) 240/360

i_1 and i_4 are opposite

with 6 point rectifier I_ϕ

see directions: add 240/360