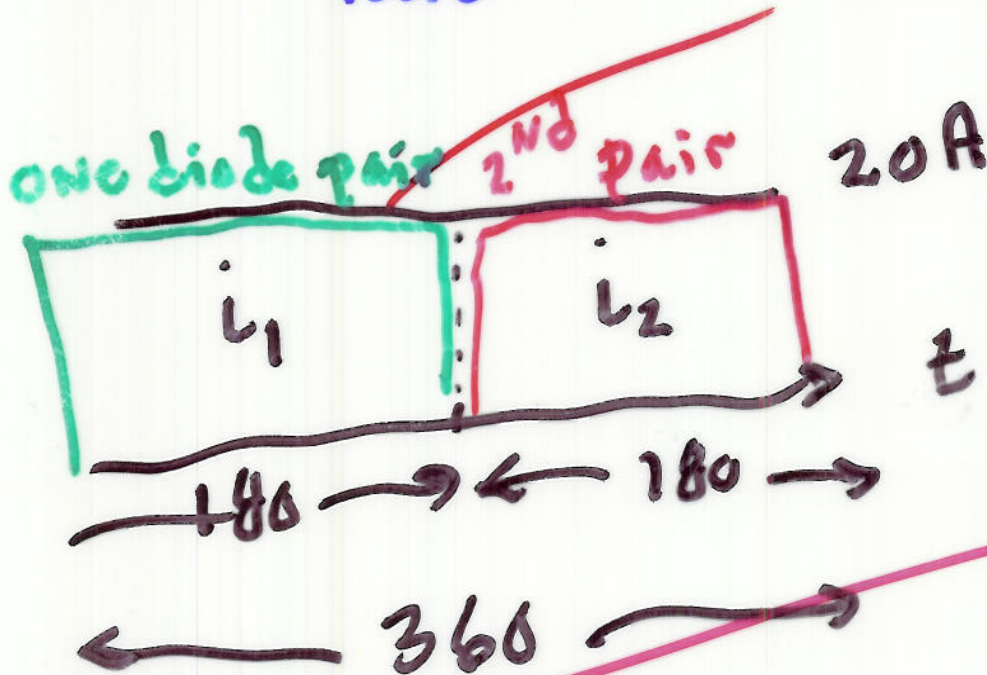


if  $I_{load}^{DC} = 20\text{ A}$  each diode is  $i_p(t)$



~~Diode~~

$$I_{AV} = \left( \frac{180}{360} \right) 20 = 10\text{ A}$$

$$I_{peak} = 20\text{ A}$$

$$I_{RMS} = ?$$

Diode  $i_{AV}$  specs

P1V = ?

1 $\phi$  Rectifier:

$$\text{Ripple in \%} = \frac{5.5 I_{\text{load}}}{f_{AC} W_L (J)}$$


Look ahead

① 3 $\phi$  Rectifier:

$$\text{Ripple in \%} = \frac{0.17 I_{\text{load}}}{f_{AC} W_L (J)}$$

WOW!  
25% less ripple!  
3 $\phi$  rectifier!

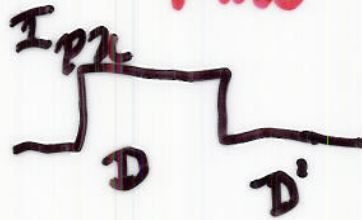② Imagine the case  $I_{\text{rms}}$  (effective) = ?



$$\frac{I}{I_{\text{rms}}} = \sqrt{D} \quad I_{\text{pk}}$$


$$I_{\text{rms}}^{\text{eff}} = \sqrt{\frac{120}{180}}$$

$$I_{\text{pk}} = \sqrt{3/2} I_{\text{pk}}$$

$$0.816 I_{\text{pk}}$$




# 1 $\phi$ Power Factor: Passive Loads

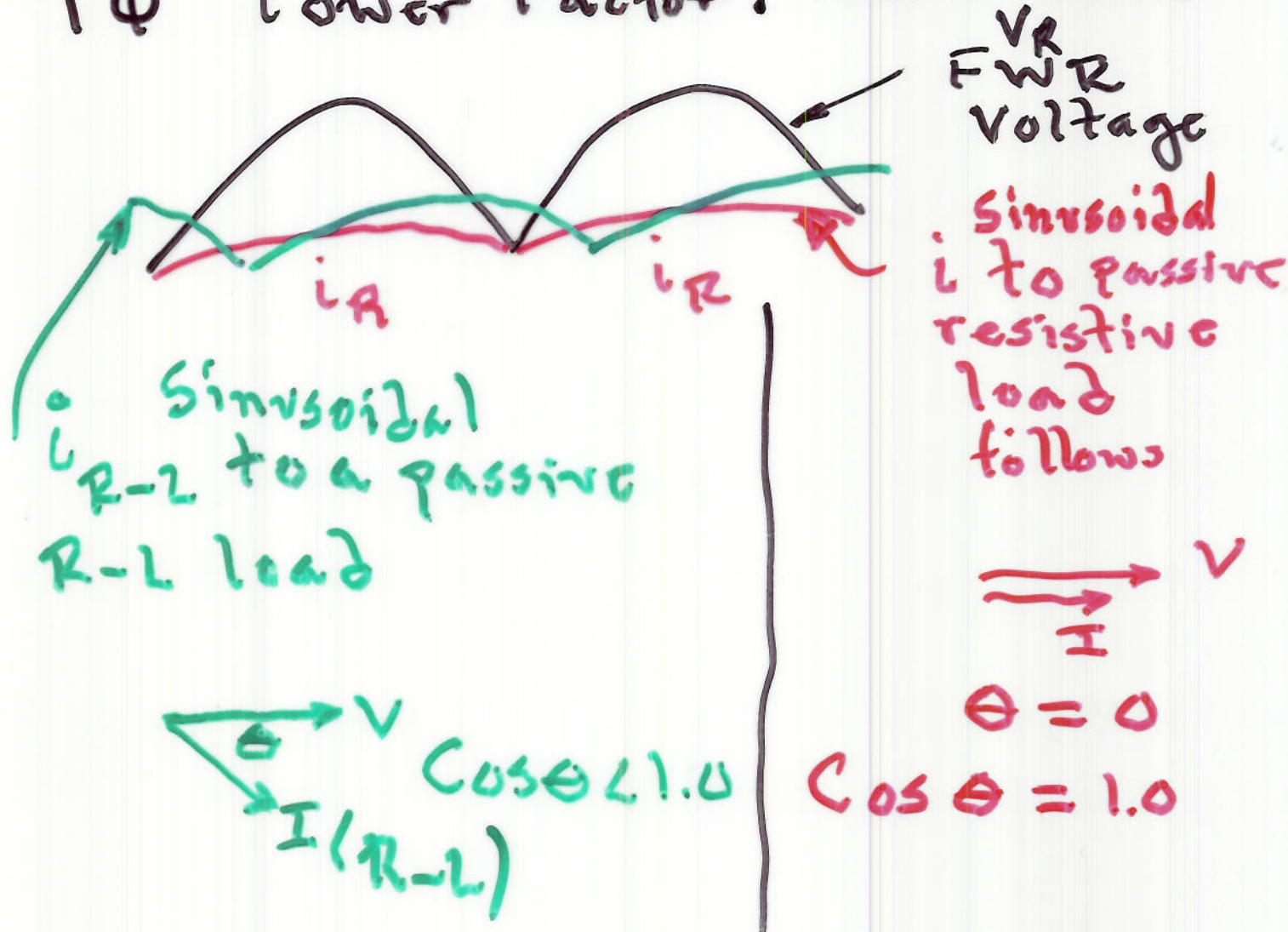
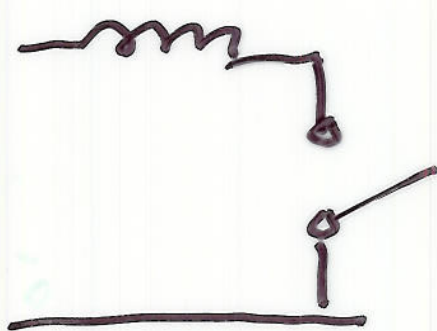
## 1 $\phi$ Power Factor: Active Loads

Control  $Z(\text{load})$  to force  $i_{\text{load}}$  to follow  $V_R$



force  $i_L(t)$  to be sinusoidal  
 }  $\mu s$  switch duration  
 $\Rightarrow$  small  $L$  OK

# Energy Conservation

> 500 million  
yr


AC  $\rightarrow$  DC  
rectifiers

PC's

200 million/yr

LCD/LPT

300 million/yr

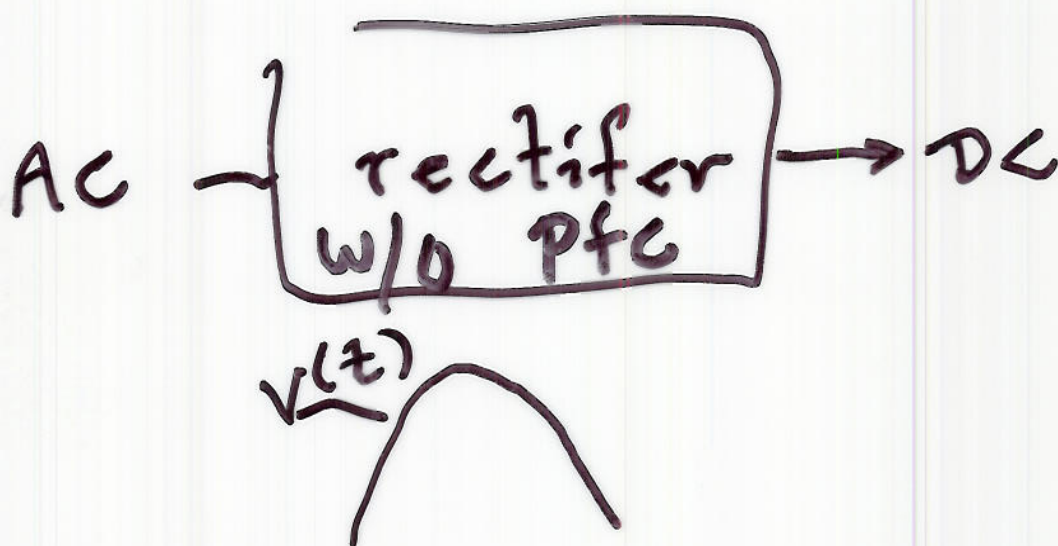

$i(t)$  does not follow  $v(t)$

CAUSES "pollution" of the mains

- harmonics

- Poor power factors

New PFC regulation EN-61000-3-2



Power Electronic Switches  
enable

PF  $\rightarrow$  1.0 saves Grid

## PFC DESIGN

boost  
topology  
allows large at  
low  $V_{in}$

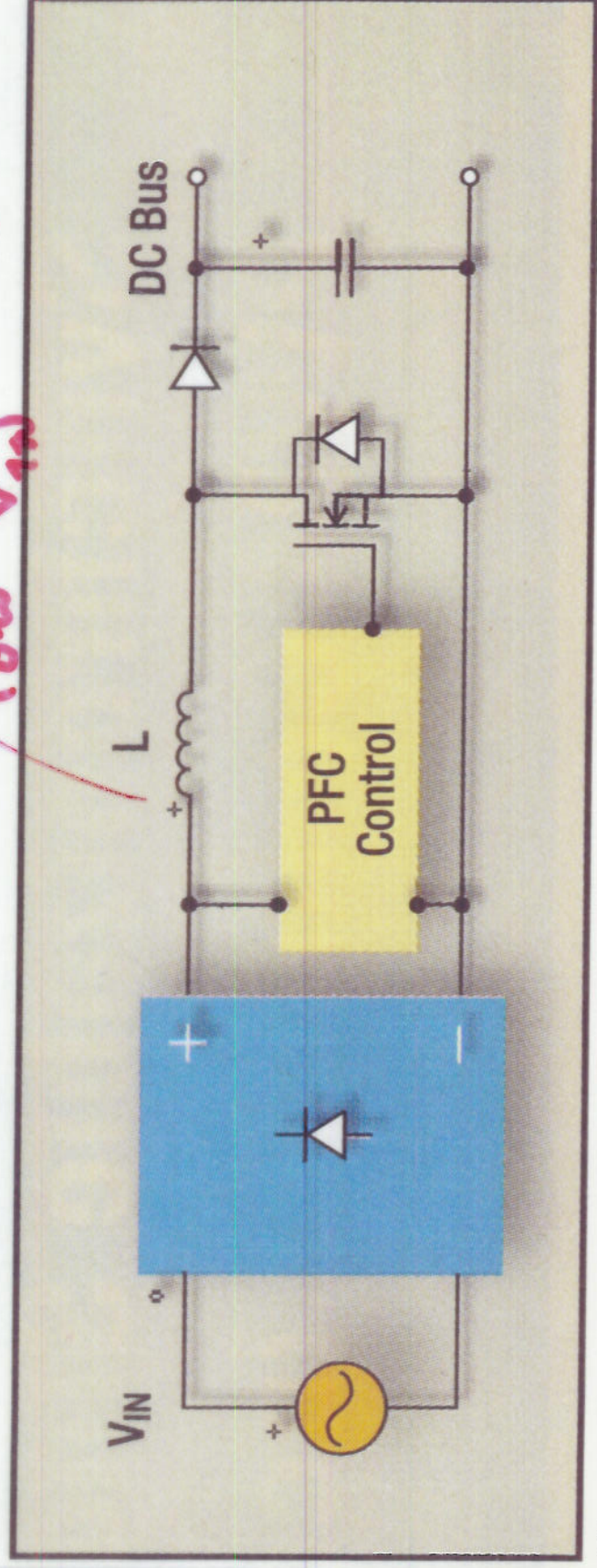


Fig. 2. An active PFC circuit produces low THD and uses relatively small passives, but degrades power-supply efficiency because of the losses



components, but these components are large  
**Fig. 1. A passive BFC circuit requires only a few**

