


$$E_{\text{du}} \text{ FWR } \cap \Phi \approx .9 \text{ E}_{\text{TMS}}$$

2542125

$$E_{\text{eff}}(\omega) = \frac{2}{\pi} E_{\text{pk}}(\omega)$$

$$= \frac{2\sqrt{2}}{\pi} E(2\pi)$$

$$E_{\text{eff}} = 0.9 E_{\text{rms}}$$

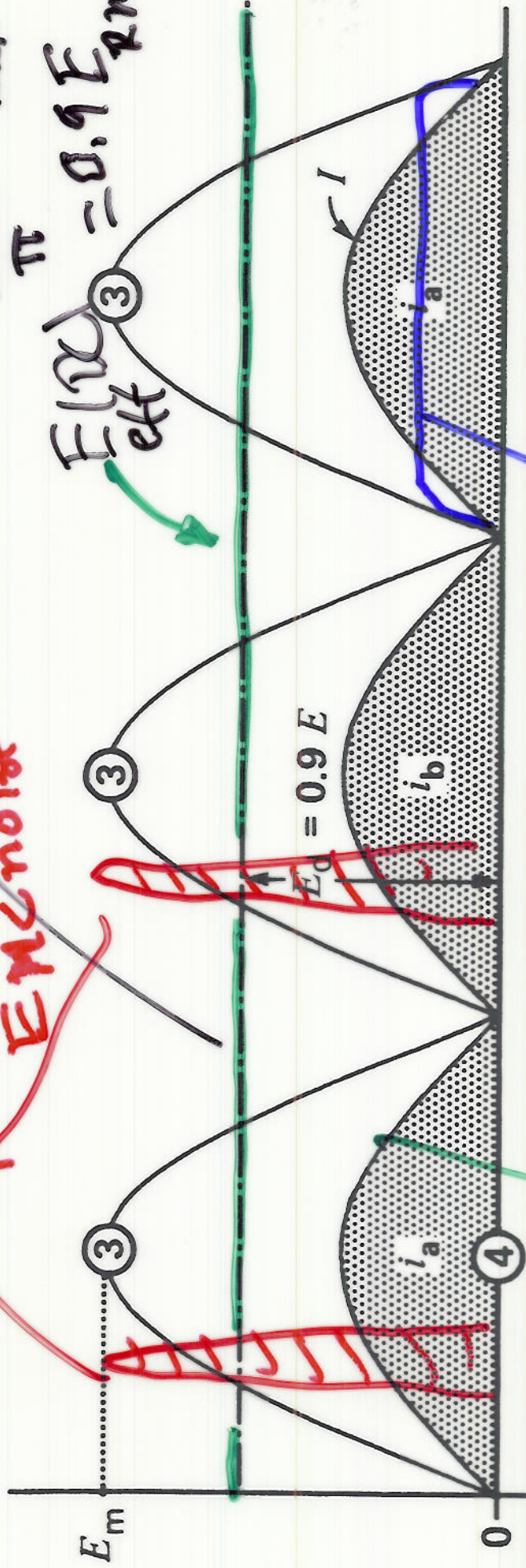

12-67

Spikes (noise)


EMC noise

[i for small L
or pure R


$$i(2-k) \text{ for large } L$$

$E_{\text{eff}}(\frac{1}{2} \text{ Wave}) = ?$ same for all?

$$V_0^{DC} (R-L)$$

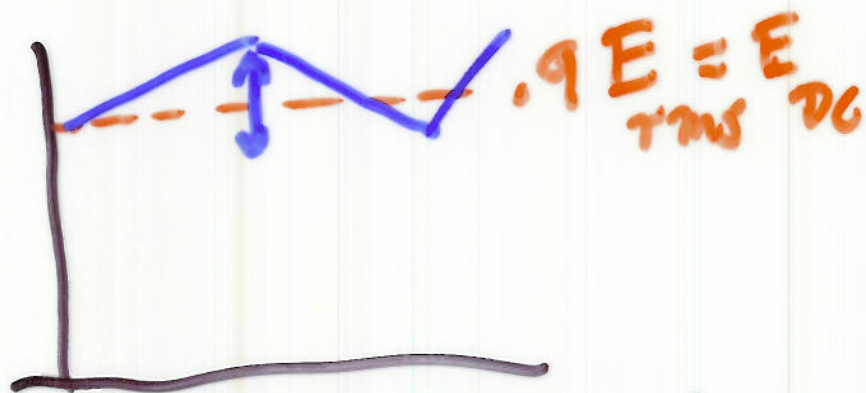

$$V_0^{DC} (R-C)$$

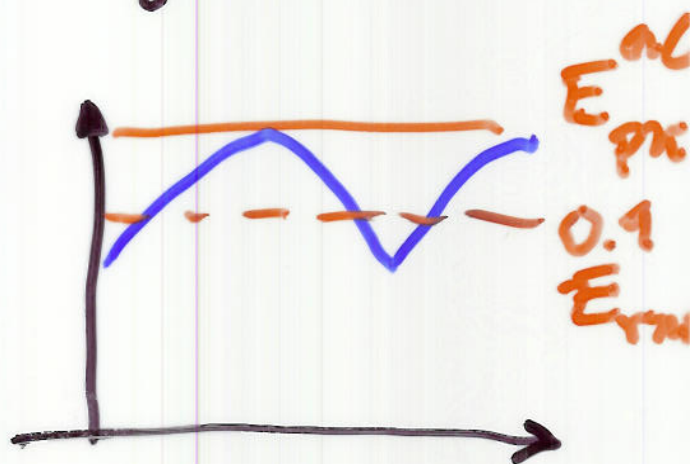

$$\Delta \phi_L = \left(\frac{E_L}{L} \right) \Delta t \quad \left. \vphantom{\Delta \phi_L} \right\} \text{for short time}$$

more like $E > .9 E_{rms}$


AC Sinusoidal

a Δ -wave
yet we have
 $E_L^{DC} = 0$


$$E_R^{DC} = .9 E_{rms}$$

DC $E_L =$ ① E_{pk} for large R

② 

③  for R small

Given \square -wave of V_{IN}

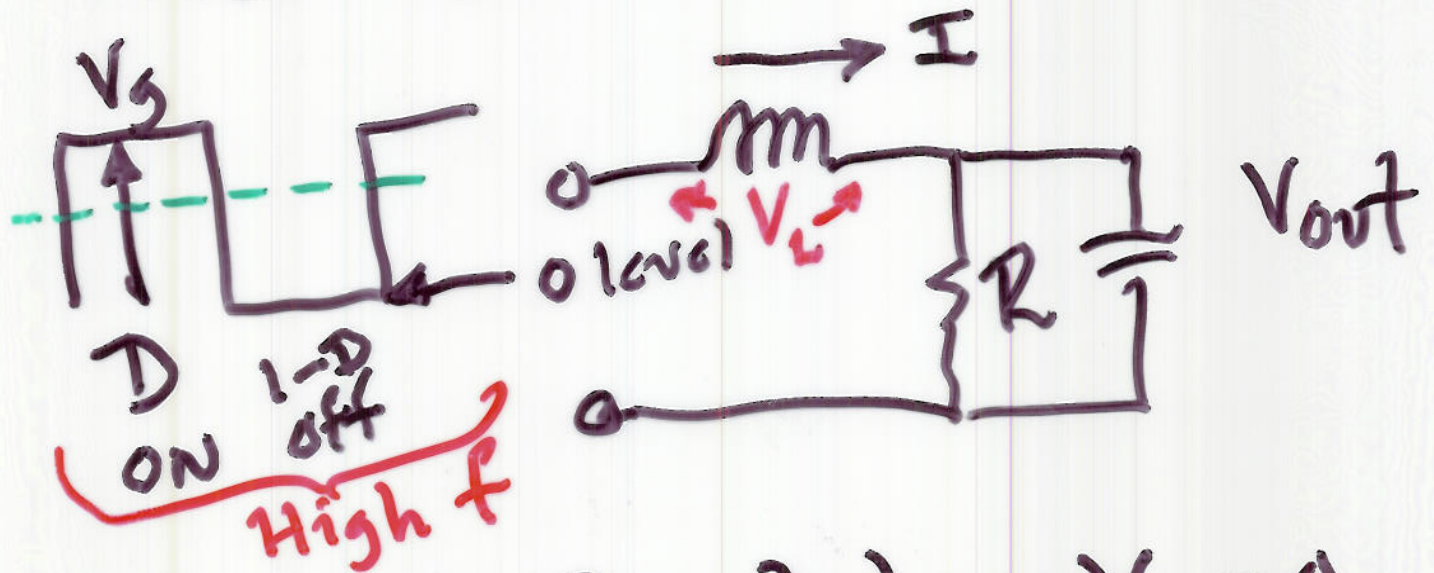


In steady state $V_L = 0$

$$V_{IN}^{AV} \equiv DV_g + \Delta V$$

$$I_{out}^{AV} = \frac{DV_g}{R}$$

$$V_{out}^{DC} = DV_g$$

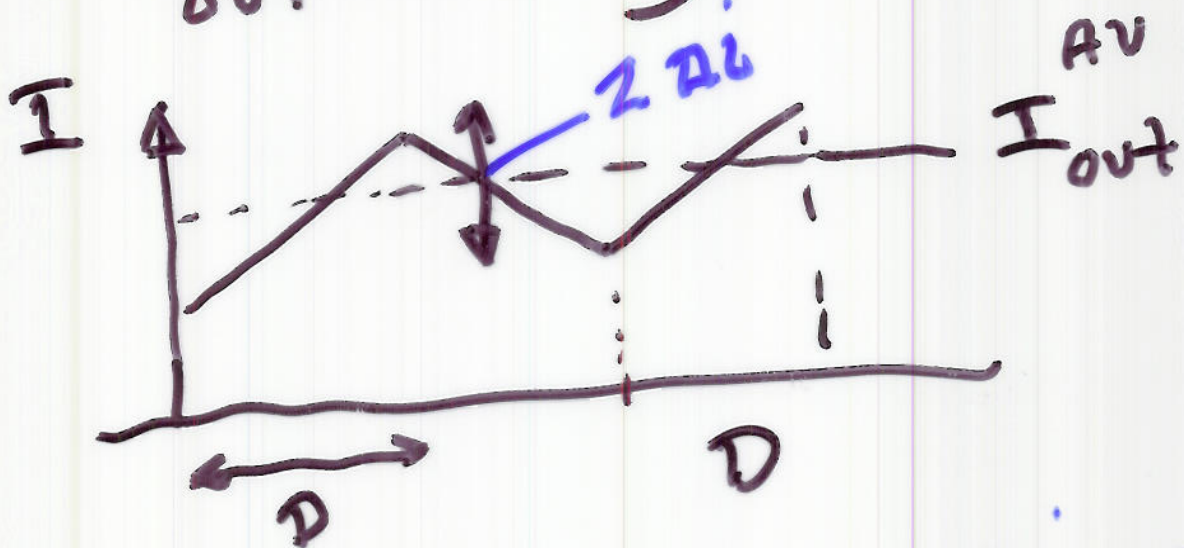

Want to know $\frac{\Delta i}{I}$ factor

Chapter 21 Fundamental Elements of Power Electronics

This chapter covers such a broad range that it is impossible to sum it up in a few words. Rather, we suggest a quick glance through the Section headings to become familiar with the contents. The user-friendly presentation is arranged so that even the non-initiated will be able to understand the meaning and thrust of power electronics. No complicated mathematics, no nitty-gritty detail to mask the basic principles.

① Distortion power factor, displacement power factor and total harmonic distortion are introduced in Sections 21.12 to 21.14. These terms have become important in today's power electronic environment.

② The application of thyristors has been grouped into six fundamental circuits that describe the majority of all industrial applications (Sections 21.20 to 21.25). They give the student a broad understanding of how line-commutated converters are used in industry. (The term *naturally-commutated* is sometimes used instead of line-commutated).

old switch of
pe only
turns
off
@ I_a
or
 I_L

③ The development of GTOs and IGBTs has permitted the development of self-commutated converters that can initiate and terminate conduction at will. (The term *force-commutated*

New switches
CAN turn
off
any
time


1 ϕ F.W. Bridge (4 diodes)

Fig 21.13

pg 481

Consider Loads: ① R ② R-L

peak voltage = E_m

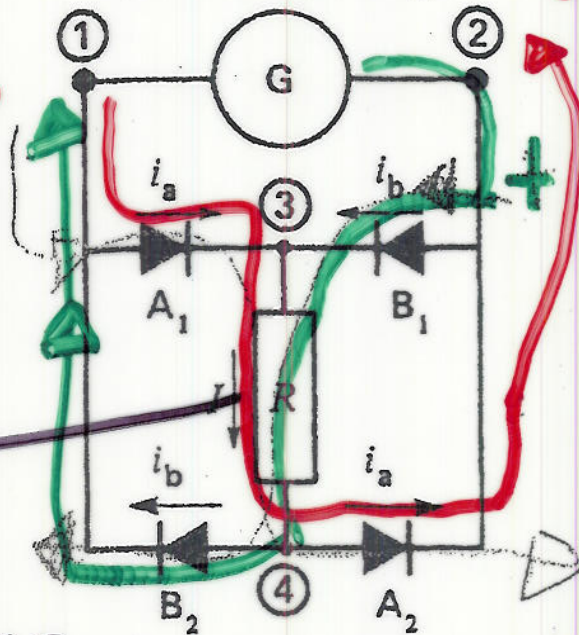

Ex Cr.
Voltage
Doubler
Circuit

① R_{load} only
Flow of
 i_R is
full-wave
rectified



a. Single-phase bridge rectifier.
b. Voltage levels.

V_L for I_{DC}
=?

② With load

$i_{load} \rightarrow$ \square -wave

Why?

Our
Key
Approx


\Rightarrow
 $V_0 =$
 $9V_m$

Gate Signals control i angle:

① No g_1, g_2 fully open switch

Fig 21.33
Pg 500

AC source

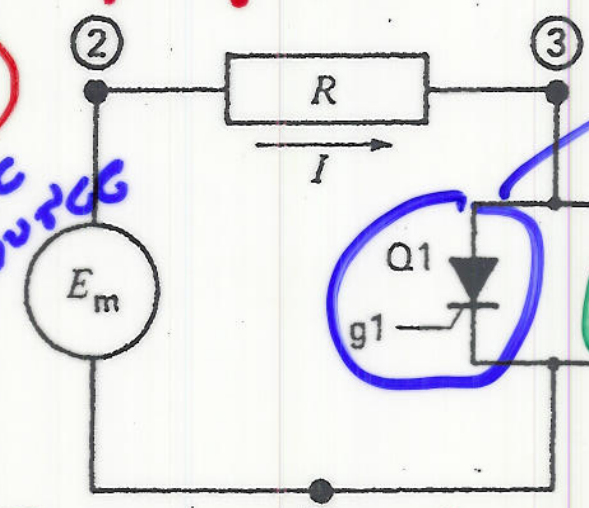

+ V_{in} control + i angle


- V_{in} control - i angle set.

For timing at gates

② $g_1 @ 0$
 $g_2 @ 180$

Fully closed switch for all times

Other
③ g_1, g_2 timing is more useful

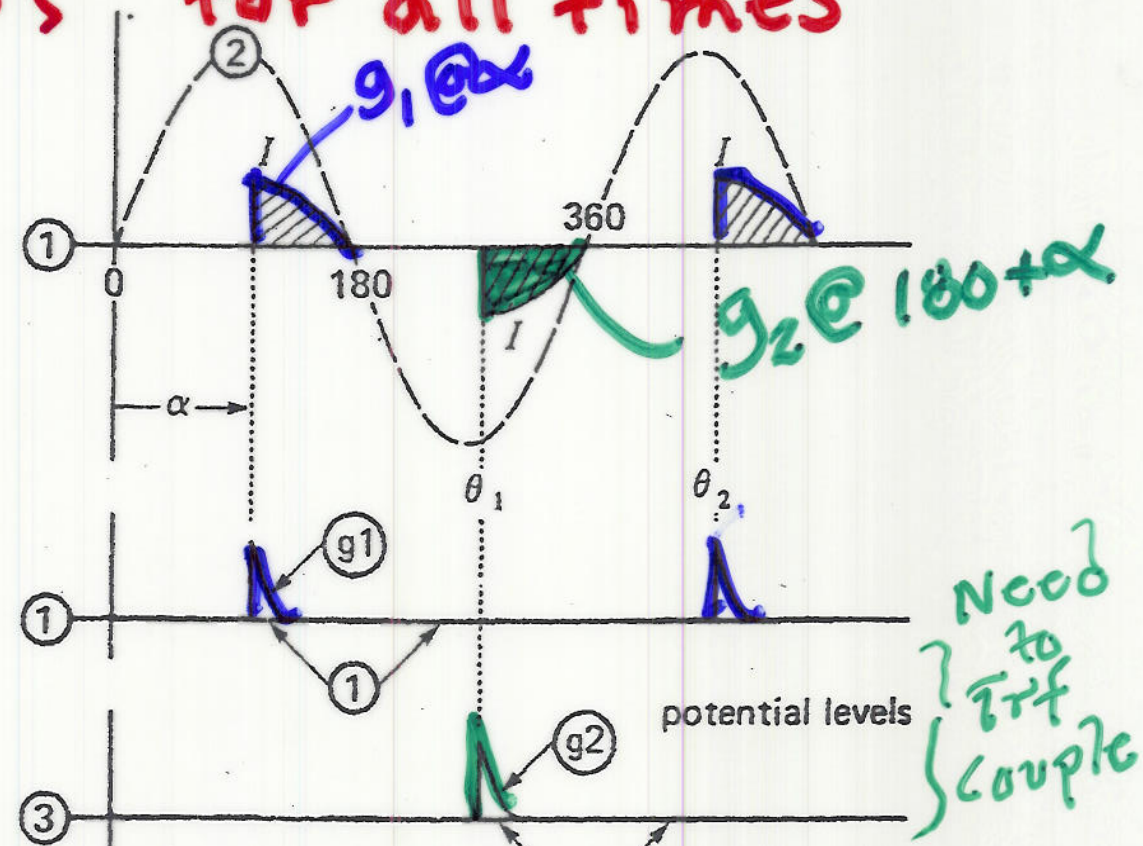


Need to π f couple

$$I_{ON} [R_{ON} + V_{ON}] = \text{Contactor Power loss}$$

- a. Electronic contactor.
- b. Waveforms with a resistive load.

Fortunately $I_{surge} \text{ of SCR } \approx 10 * I_{AC}$

now

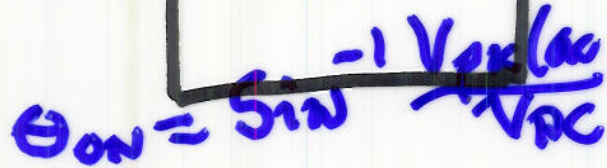

easy fix
 $R \rightarrow L$



PF \uparrow due to "L" longer Duration
 $I_L(\text{peak}) \sim$ Positive V_{sec} across "L"