

Power System Components

1-3

① R, L, C elements

② Transformers

③ Solid State Switches:

Ideal Switch?



ON: $R_{ON}, V_{ON}?$

Max $I_{ON}?$ through Sw

Real switch values?

off: R_{off}, I_{off}

Max V_{off} across Sw

Switch Time: Ideal $\Delta t = 0$

$\Delta t(\text{off-on}) \neq \Delta t(\text{on-off})$


Why?

Stored Charge diodes
bipolar

Parasitic C and L

↑ How? eg transformer line

Change to L-R load

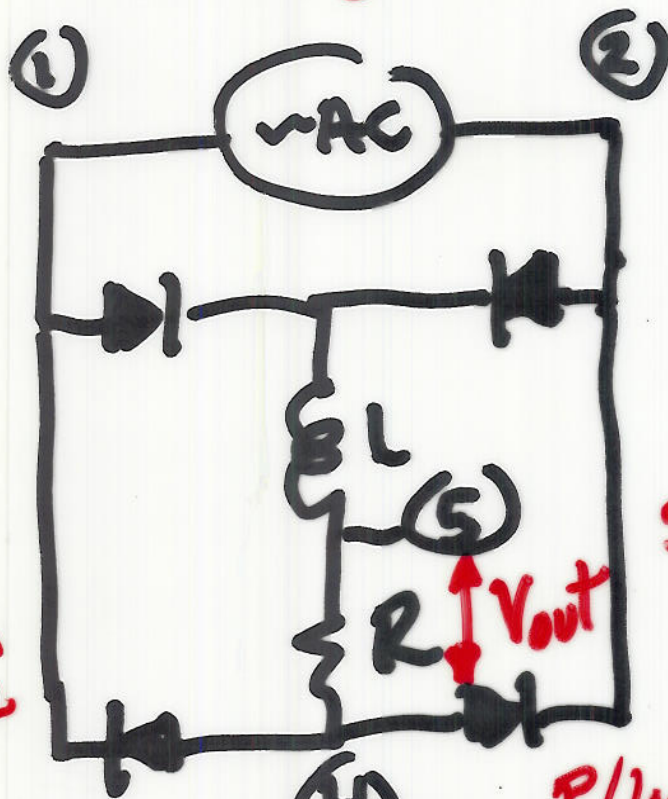

L-R load

L acts for:

1. i limiter if R is shorted
2. Keeps rectified i a D-wave

Short CKT Protect

EA 21.2

? $\frac{\Delta I_{AC}}{I_{DC}} \equiv 5.5 \frac{I_{(load)}}{f W_L (stored)}$ Limits ripple i? Ex Cr. derive? next?

If 'L' achieves V-sec

balance over an ac cycle

then $V_L (DC) = ? \Rightarrow V_{DC} = ?$

We will see that

$E_{DC} (\text{out across } R) \approx 0.9 E_{rms}$

for a full wave rectifier



PROPERTIES OF SOME TYPICAL DIODES

Relative power	I_0 [A]	E_0 [V]	I_{cr} [A]	E_2 [V]	I_2 [mA]	T_J [°C]
low	1	0.8	30	1000	0.05	175
medium	12	0.6	240	1000	0.6	200
high	100	0.6	1 600	1000	4.5	200
very high	1000 kA	1.1	10 000	2000	50	200

I_0 – average dc current

E_0 – voltage drop corresponding to I_0

I_{cr} – peak value of surge current for one cycle

E_2 – peak inverse voltage

I_2 – reverse leakage current corresponding to E_2

T_J – maximum junction temperature (inside the diode)

d – diameter

l – length

T_{MAX}