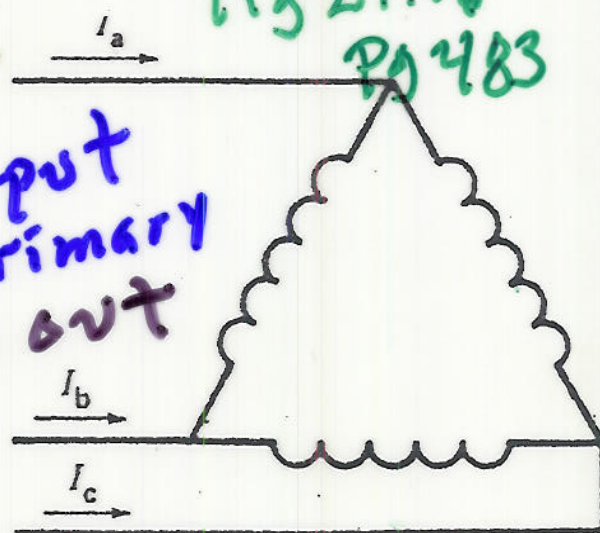


[3 ϕ] Rectifier Driving L-R load

L-R

Fig 21.16 Pg 483

input primary
No 3 w out



3 Phase
Has 120°
Phasing
abc


$$E_K - E_N = E_{out}$$

Only 3 point
rectifier
each diode
sees

$$E_{IN} (\text{peak}) = E_m$$

$$\frac{V_{el}}{T_0} = V_\phi$$

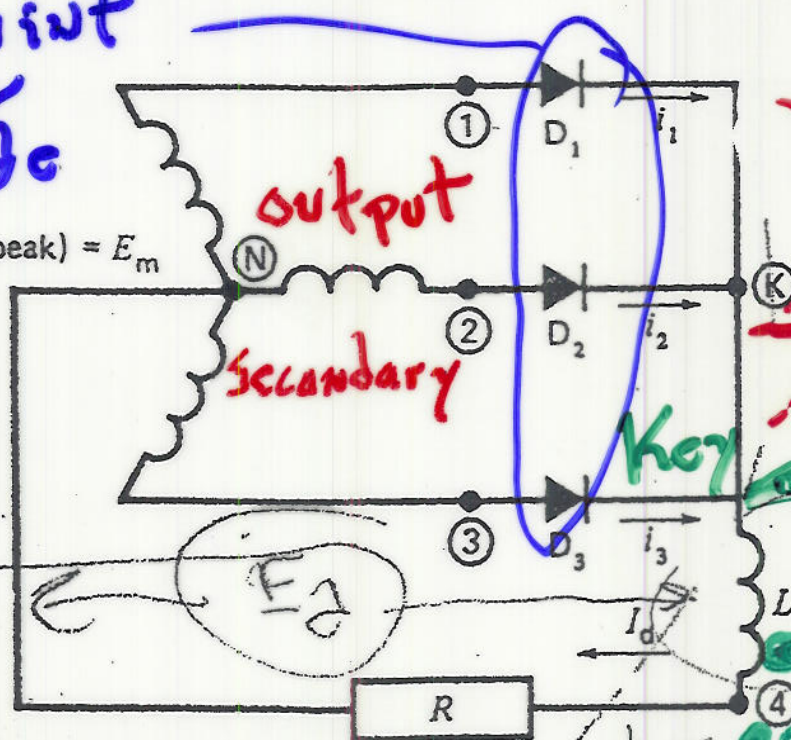$E_{ac} = .67 \text{ rms or } .92 \text{ peak}$



$E(3\phi)$
DC
does
Not
ever go to
zero

3 ϕ Half-wave rectifier


Three-phase, 3-pulse rectifier with inductive filter fed by a 3-phase transformer.

L-R load makes $i_L \approx \text{constant}$

Phase 1: @ 60° $E_0 = E_m \cos 60 = \frac{E_m}{2}$
 3 $\frac{1}{2}$ waves / cycle and \rightarrow Minimum Voltage = $\frac{E_m}{2}$

Phase 2 @ $60^\circ = E_m$ and \rightarrow Voltage rising = $\frac{E_m}{2}$

Max $E_m \cos[-120 + 60] = \cos 60$

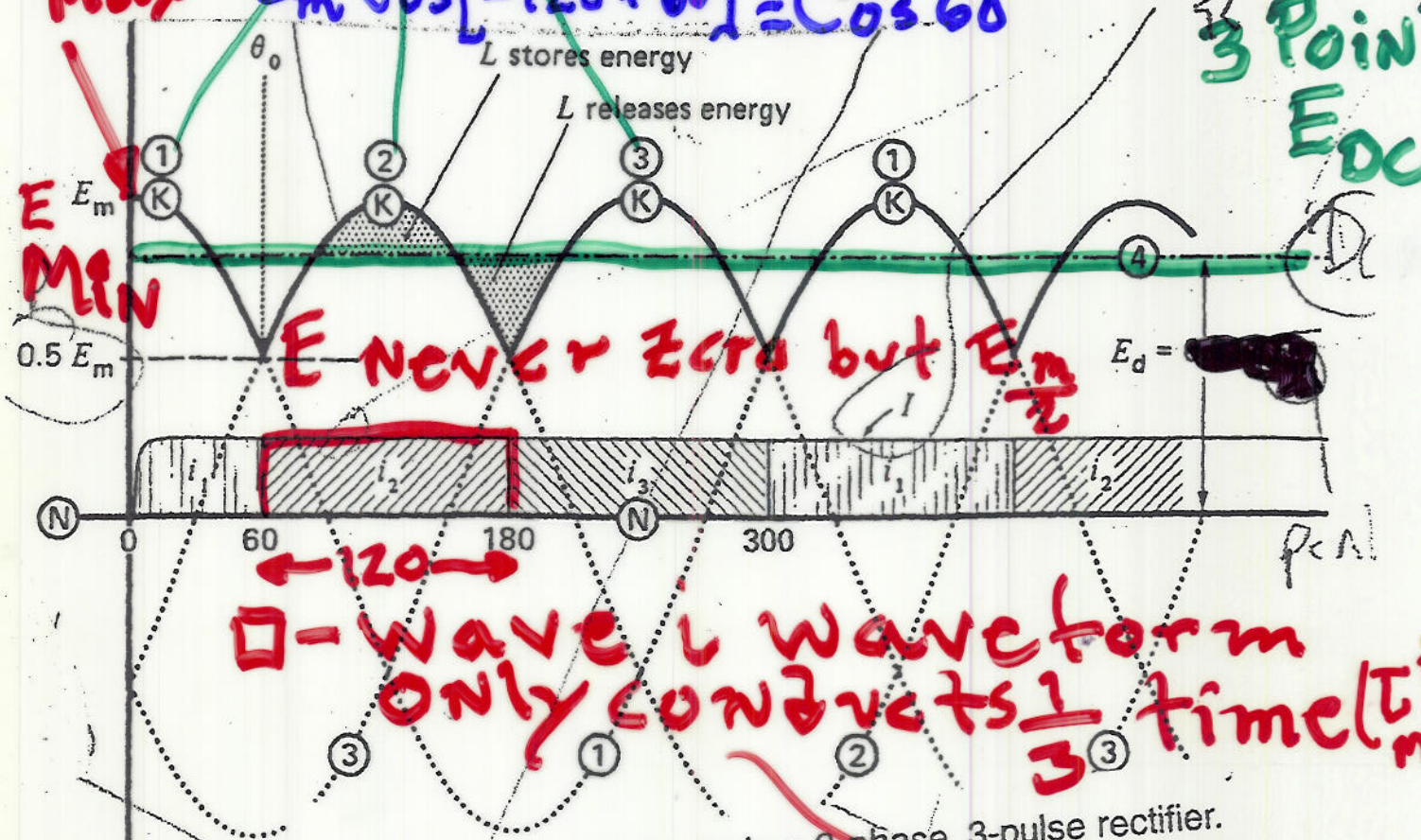

□-wave i waveform ONLY conducts $\frac{1}{3}$ time ($\frac{T_m}{3}$)

Voltage and current waveforms in a 3-phase, 3-pulse rectifier.


3 point 3 Half-waves CAUSES EMC EMI
 $E_{DC} = \left(\frac{1}{\pi} \right) \left(\frac{3}{2} \right) E_{peak}$
 $\frac{3}{\pi} \left(\frac{1}{\sqrt{2}} \right) E_{RMS} (1-n)$

$FW = .675 E_{RMS}$? believable?
 $E_{DC} (1\phi)$ is ? 1 or .827 E_{peak}

.9 E_{RMS}

Fig 27.76 Q 2405

Fig 27.76
Q 2403

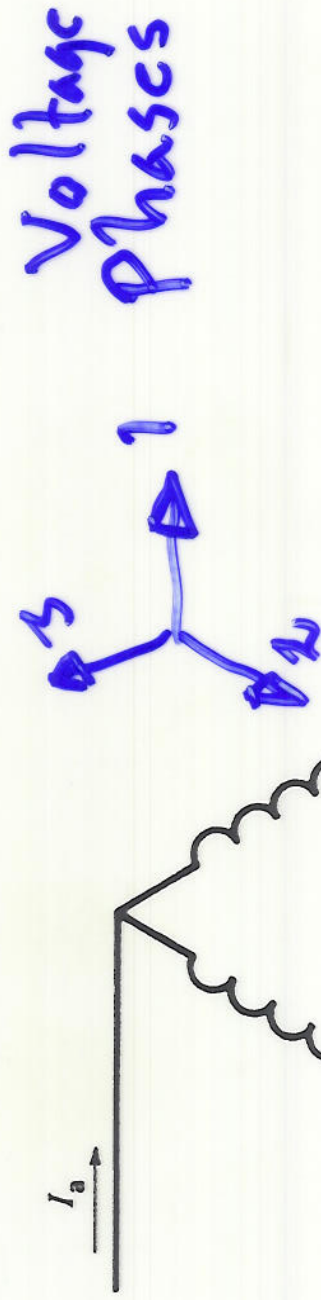


Voltage Phases

- ① 3 diode "3 phase rectifier"
- ② $V_{\text{reverse}} = \frac{V_{\text{ph}}}{\sqrt{3}}$


Isolated 3 ϕ Rectifier

E_{rms} is a voltage V_{RMS} not $L-L$

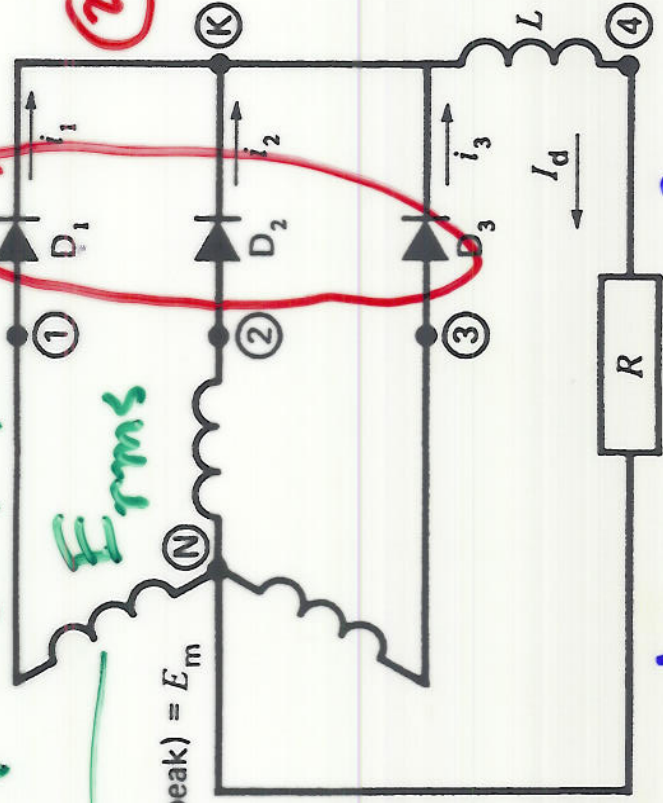


Big L
R-L load means?

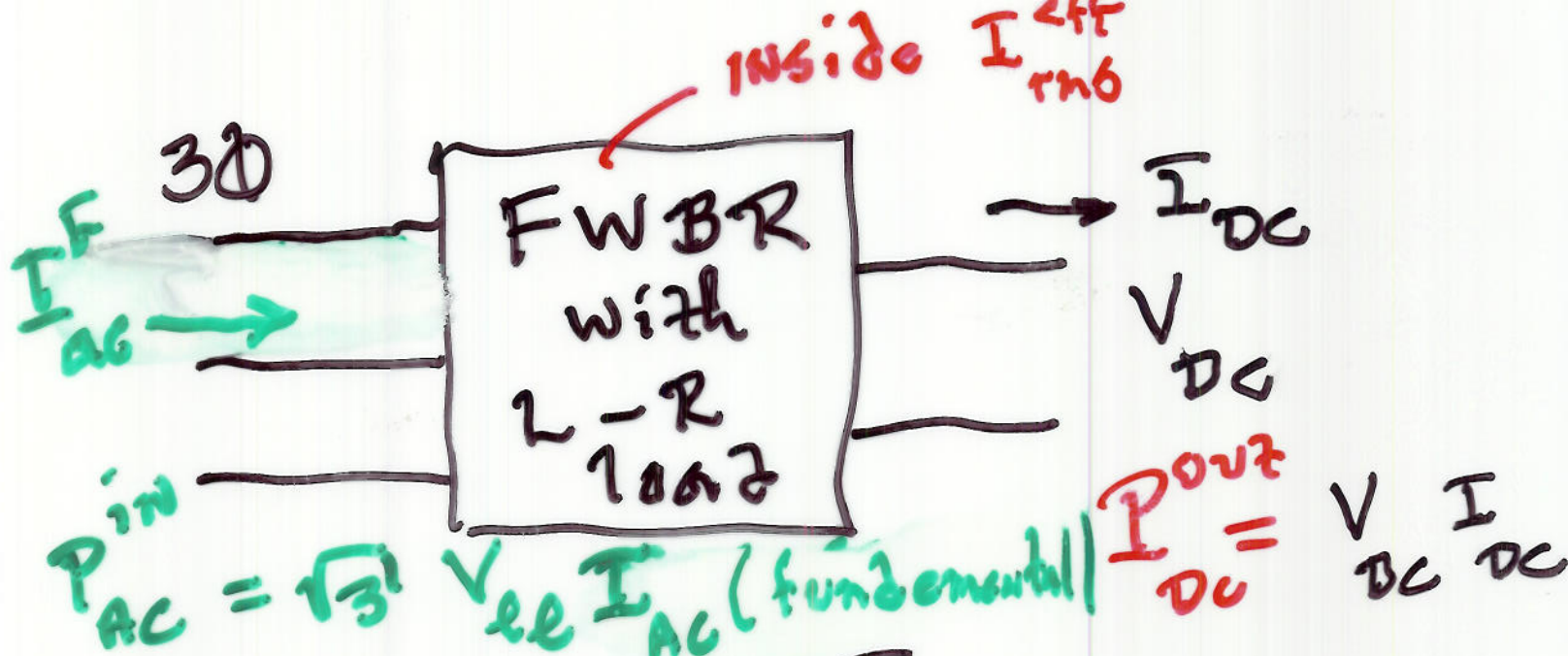? $E_{\text{DC}} (3\phi) \text{ vs } E_{\text{2L}} (1\phi) = 0.9 E_{\text{rms}}$



$$I_{diodes} (AV) = \frac{I_{DC}}{3} \quad \text{because}$$

diodes are only on $\frac{120}{360}$

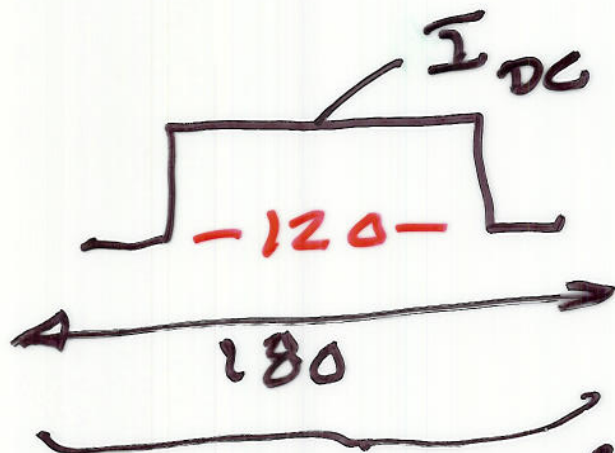

$$I_{rms}^{eff} = \sqrt{\frac{120}{360}} I_{DC}$$

$$I_{rms}^{eff} = 0.816 I_{DC}$$

Rectified @ $2f_{sw}$
 so duration of rectified V is 180°
 Mains is only able to source

I (fundamental)

Whats the relation to I_{rms}^{eff}