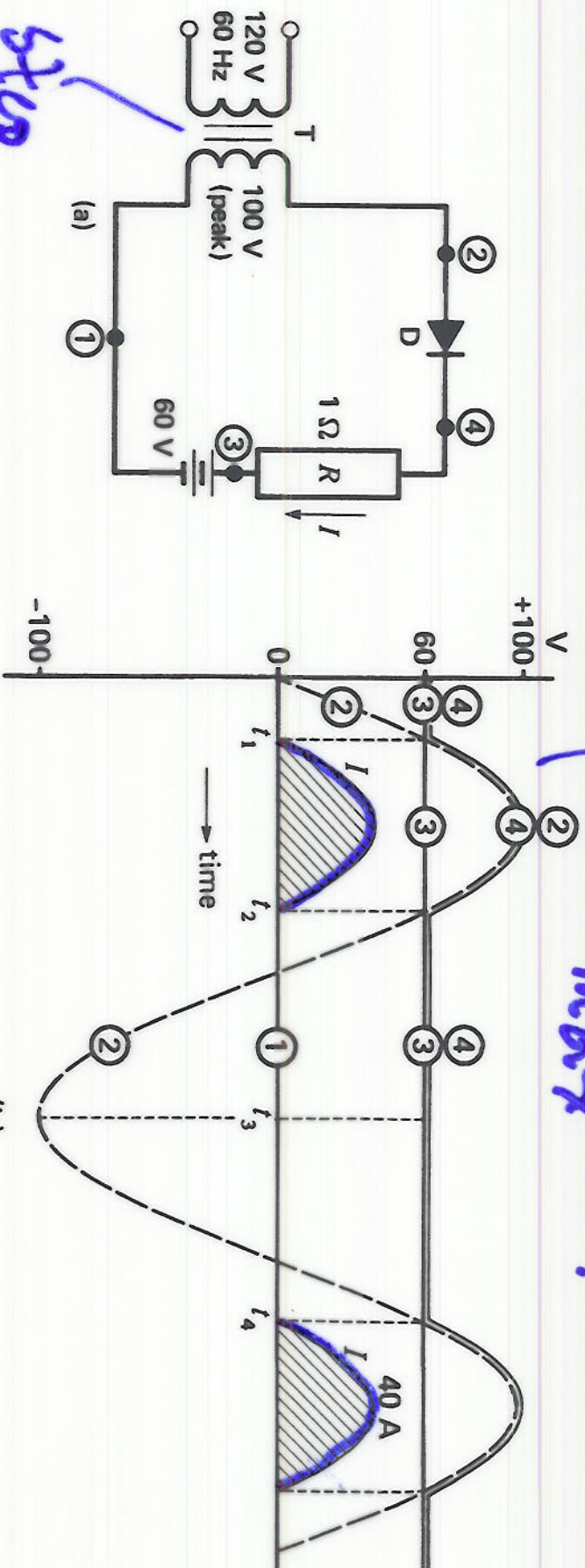


Figure 21-11 a. Simple battery charger circuit. b. Corresponding voltage and current waveforms.





step  
down

diode limits  $V_R$   
 $I_{max} = ?$

Any losses to charge  
battery?  $I_{rms} R$

① Fig 21.1)  
Pg 478

① What is the P.F. below high or low

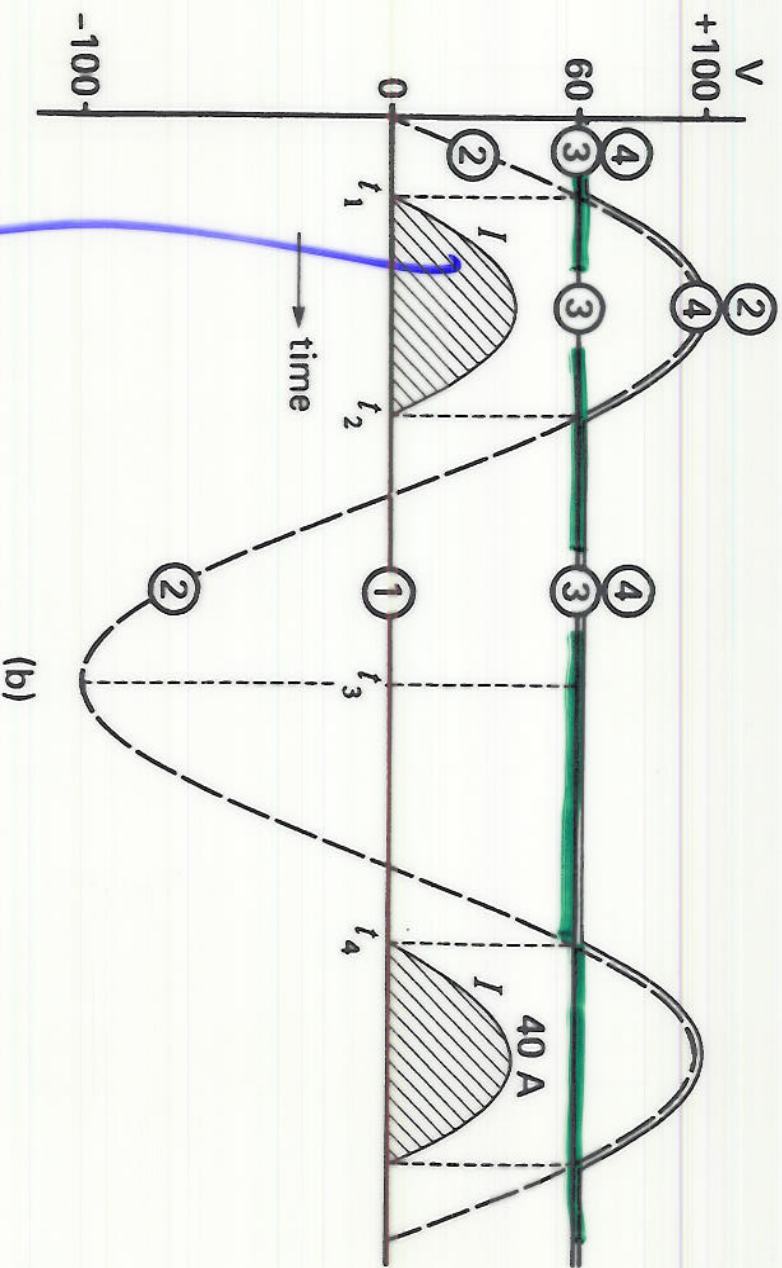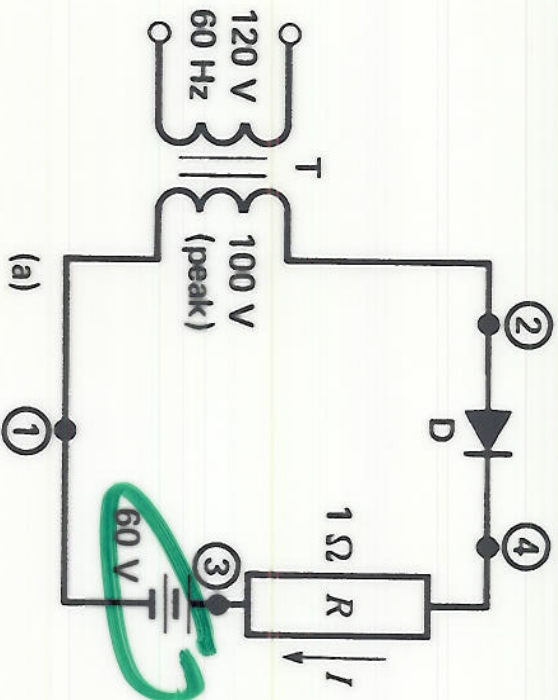

I follows V

if?

② What can we add to increase P.F. that has no real power loss?





When  $V_{AC} > V_{DC}$

$\nearrow di/dt$  up

When  $V_{AC} < V_{DC}$

$\searrow di/dt$  down

$$i_L(t) = \frac{\int V_L(t) dt}{L} \quad \text{Volt-sec}$$

Assumes  $L \neq f(i_L)$  No saturation

$\int V_L(t) dt$  just area

$i_L(t)$  will be stretched out compared to  $i_R(t)$


Replace D-R (lossy)

with

D-L (ideal lossless)

ideally L has no losses

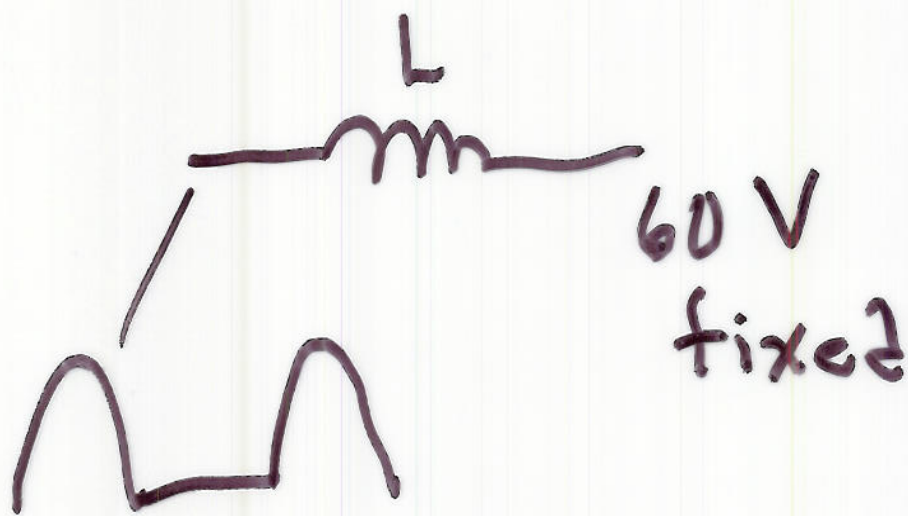
$\frac{e_L}{L} dt \Rightarrow$   $i(\text{charge})$  changes are slow



$$\Delta V_L(t) = ?$$

$$i_L(t) = ?$$

# Qualitative

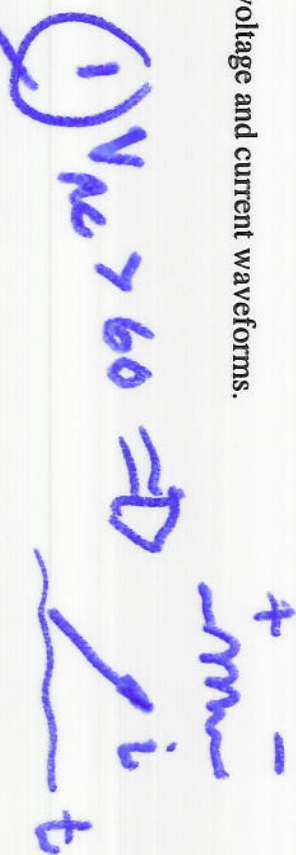

Q Why i speak  
here

Why  $i_L = 0$

$$m +$$



✓ Vac 60  
✓ 75



PER when it overlaps  $v(t)$

① Fig 27.12

479

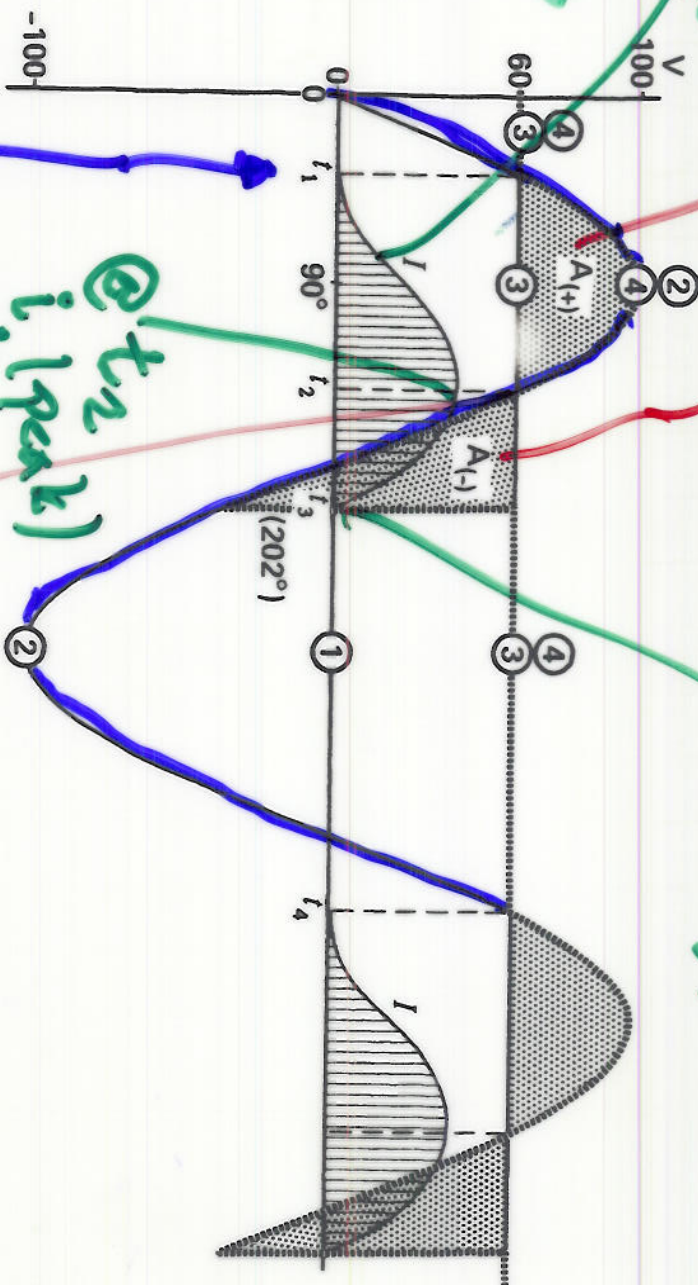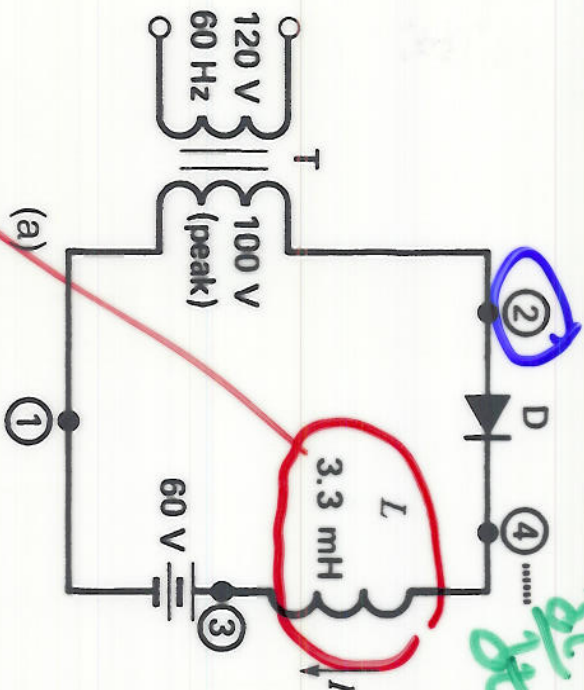

$I^+$  increases

$I^-$  decreases

Note  
big change in  
left time

Lossless?

no change  
on i on  
time

How to calculate  $i(\text{peak})$ ?


For steady state

$$I^+ + I^- = ?$$

Positive  $\gamma$ -sec region

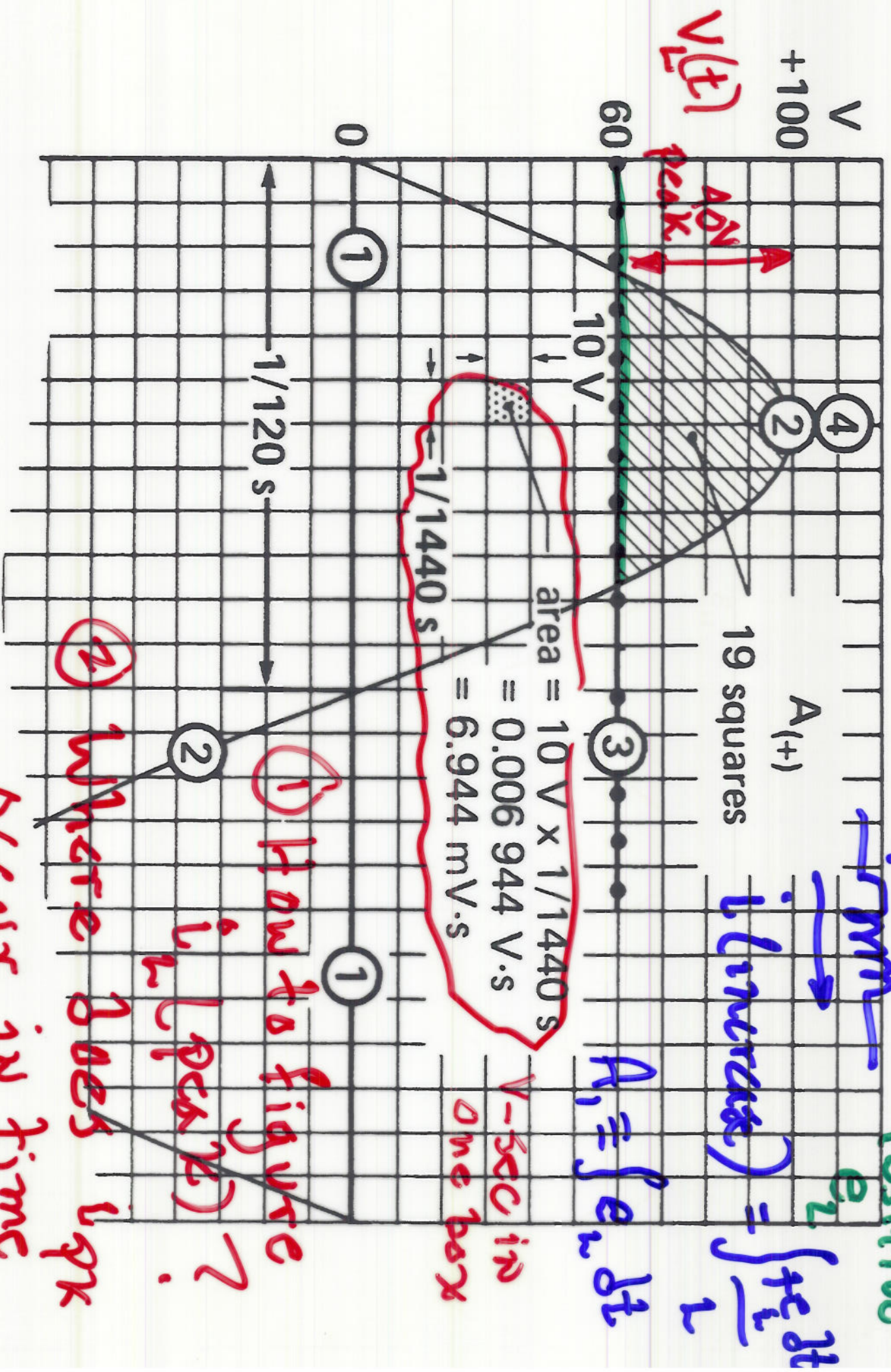$V$   
 +100  
 60  
 0  
 1 2 3 4  
 $A(+)$   
 19 squares  
 area =  $10 \text{ V} \times 1/1440 \text{ s}$   
 $= 0.006\,944 \text{ V.s}$   
 $= 6.944 \text{ mV.s}$   
 $1/120 \text{ s}$   
 $1/1440 \text{ s}$





1 How to figure  $L_p$  (peak)?

2 Where does  $L_{pk}$

BLUR in time



Specific Case (with L load)



$$i_{pk} \sim \frac{\int dt (V - V_L)}{L}$$


or do graphically

If  $L = 3.3 \mu H$

and area of  $\pm V$ -sec as shown below  $\Rightarrow \Delta i$

+V-sec interval area

$t_{ON}$   
 $V_{ac} > 60$

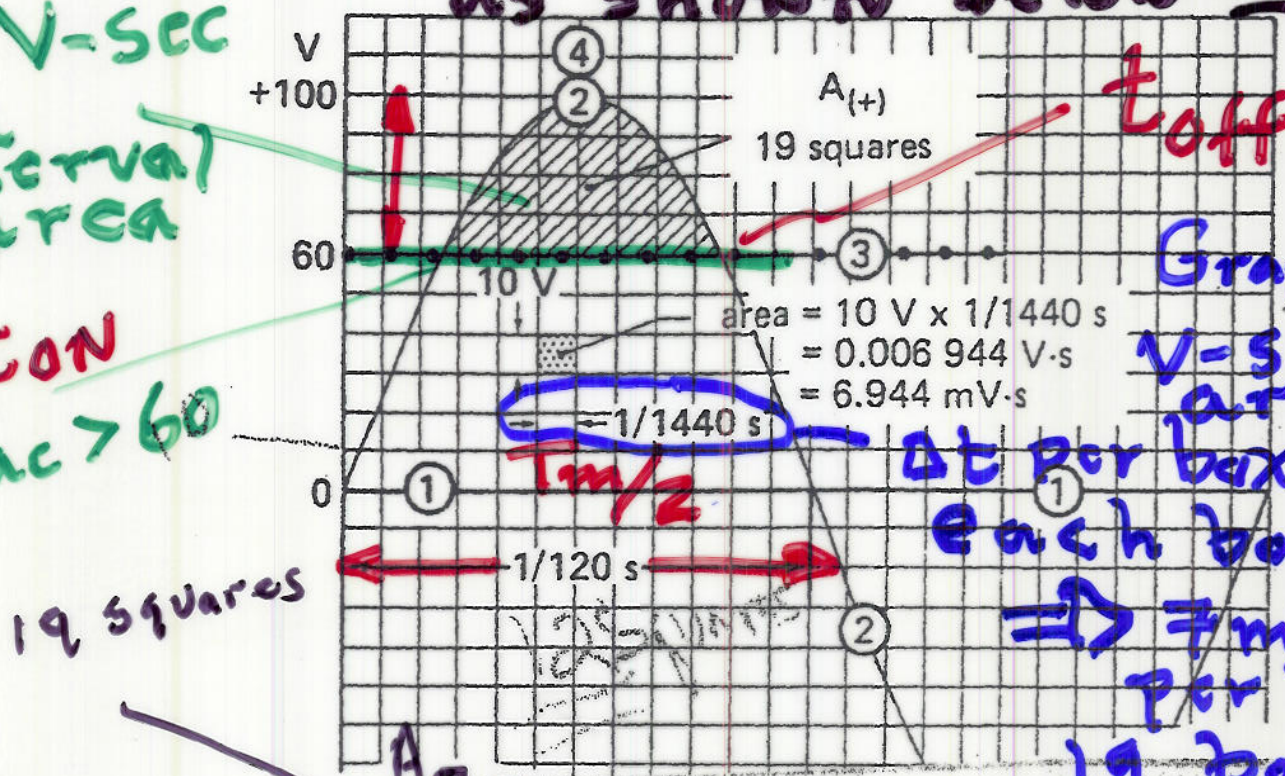

Graphical  
V-sec area:

$\Delta t$  per box  
Each box  $20V$   
 $\Rightarrow 7mV$ -sec per box  
19 boxes

$$i_{pk} = \frac{(19)(7) \frac{mV \cdot sec}{10}}{3.3 \mu H} = 40 A = \frac{\int V dt}{L}$$

Since  $\Delta V_{max}^L = 40 V \Rightarrow$  replace "L" by  $R = 1 \Omega$  for same  $i$ .

"L" has  
1. bigger P.F.  $\cos \frac{40}{1} = 40$   
2. "No" losses