

Equivalent circuits corresponding to
ideal dc-dc converter equations

Figs 3.2 / 3.3

$$P_{in} = P_{out} \quad V_g I_g = V I \quad V = M(D) V_g \quad I_g = M(D) I$$


$V_o \downarrow I_o \uparrow$

Power balance

So that


Dc transformer

$\equiv V_g I_g$

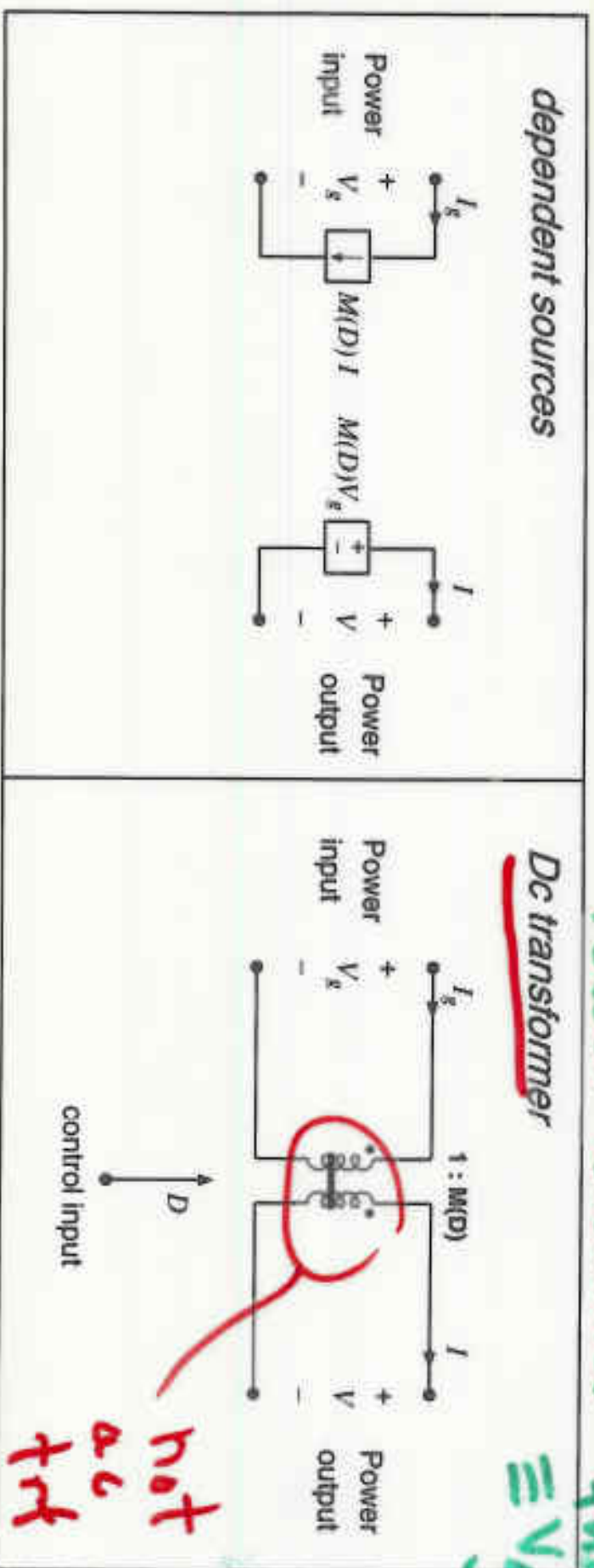

The dc transformer model

Fig 3.3

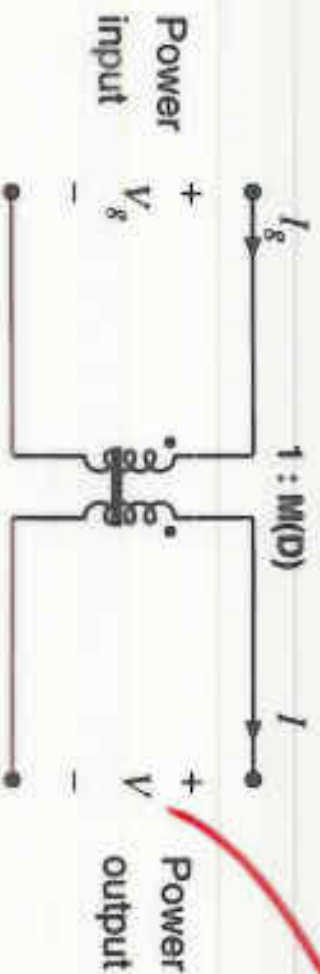

Ch 2 $V_{out} = f(D)$ only

Models basic properties of ideal dc-dc converter:

- conversion of dc voltages and currents, ideally with 100% efficiency
- conversion ratio M controllable via duty cycle

Why is $V_{out} \neq f(D)$ only?

$V_{out} = f(I_{load})?$




- Solid line denotes ideal transformer model, capable of passing dc voltages and currents
- Time-invariant model (no switching) which can be solved to find dc components of converter waveforms

$$\text{Ch 3 } \eta = f(D)!$$

Part I. Converters in equilibrium

Overview of Loss & Efficiency


Inductor waveforms

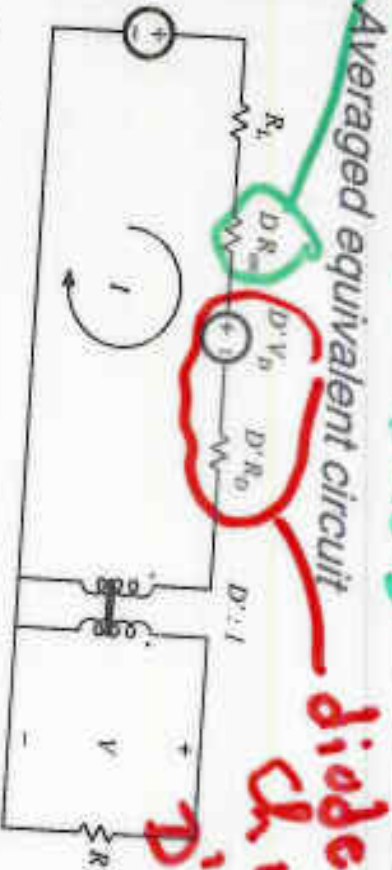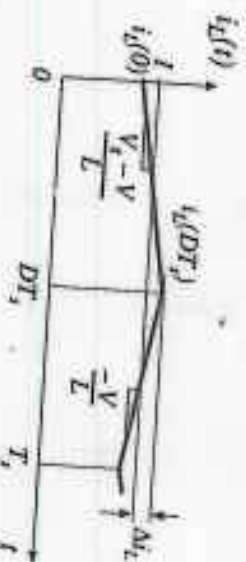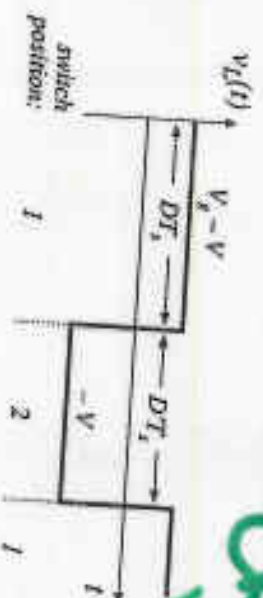

Averaged equivalent circuit

diode loss
Ch 4 via
D why?

Predicted efficiency

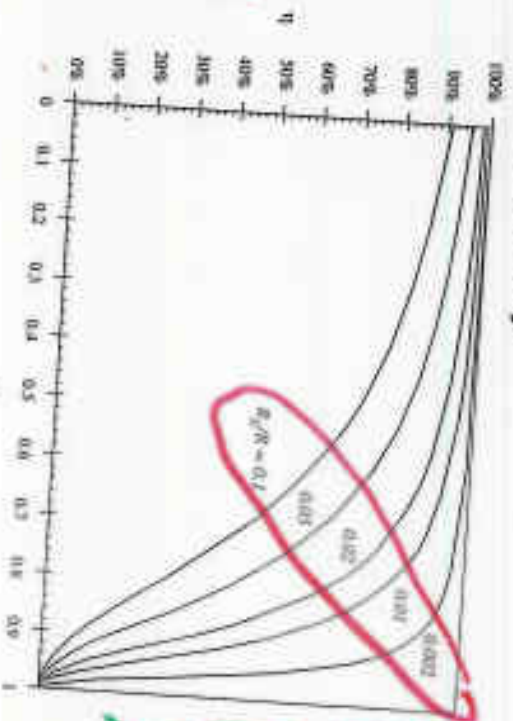


Now
(η(D))

Discontinuous conduction mode - Ch 5
Transformer isolation - Ch 6


$$m(D) = V_o/V_g = V_o/V_i$$

Example: use of the dc transformer model


1. Original system

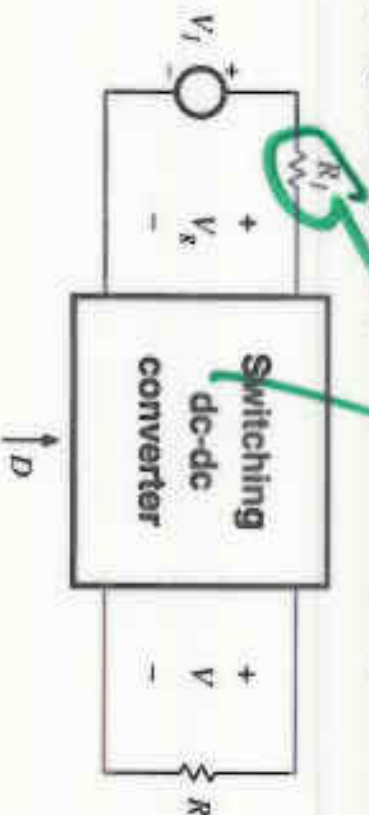

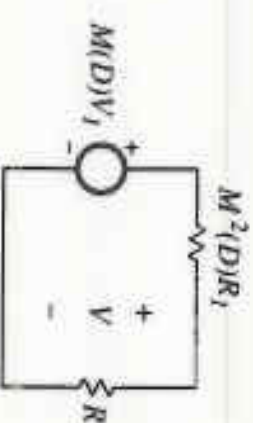Source R_i } 1st reality check
wire R } 3. Push source through transformer



2. Insert dc transformer model

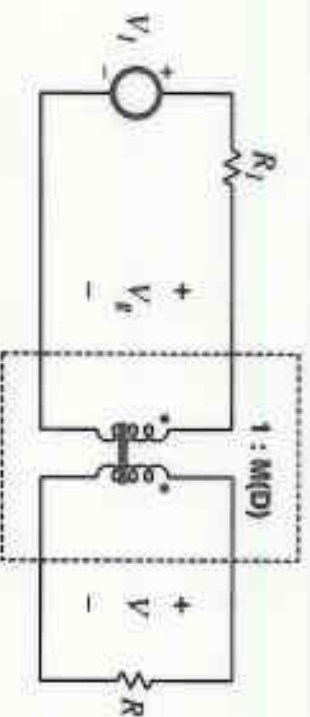

4. Solve circuit

$$V = m(D) V_i$$

$$\frac{R}{R + m^2(D) R_i}$$



still V_g only ideal

Loss Effects due to R_{source} with

V_{out}

25th

2nd reality

Limited Q

3.2. Inclusion of inductor copper loss

Follow $mL/D/R = mD(4\pi)E5R$ cases

Dc transformer model can be extended, to include converter nonidealities.


Example: inductor copper loss (resistance of winding):



Also core loss can be modeled

Insert this inductor model into boost converter circuit:

Fig 3.6

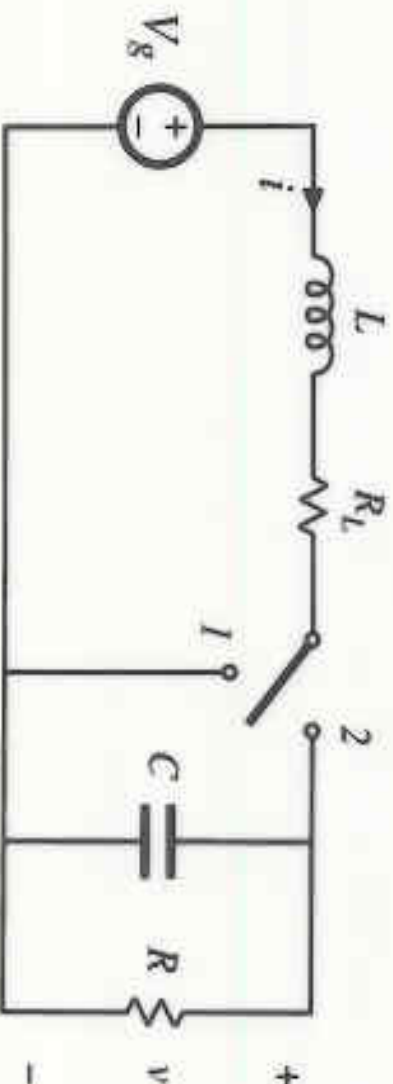

Boost

Why?