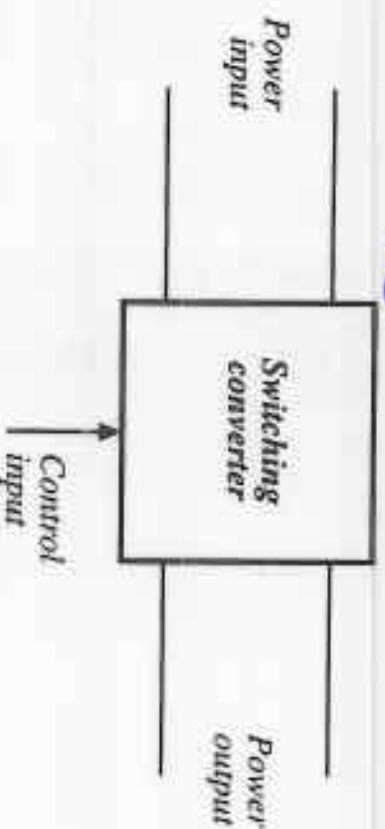


1.1 Introduction to Power Processing

10-20kW Conversion @ 95% efficiency



Dc-dc conversion:

Change and control voltage magnitude

Ac-dc rectification:

Possibly control dc voltage, ac current

Dc-ac inversion:

Produce sinusoid of controllable


magnitude and frequency

Ac-ac cycloconversion: Change and control voltage magnitude

and frequency

A simple dc-dc converter example

DC Transformer
≡ "D"

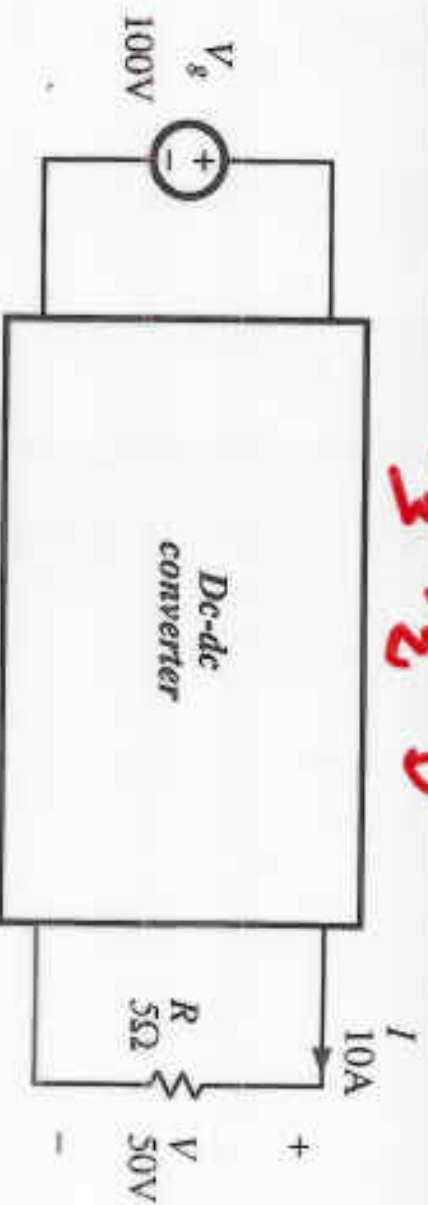


Input source: 100V


Output load: 50V, 10A, 500W

How can this converter be realized?

Use of a SPDT switch

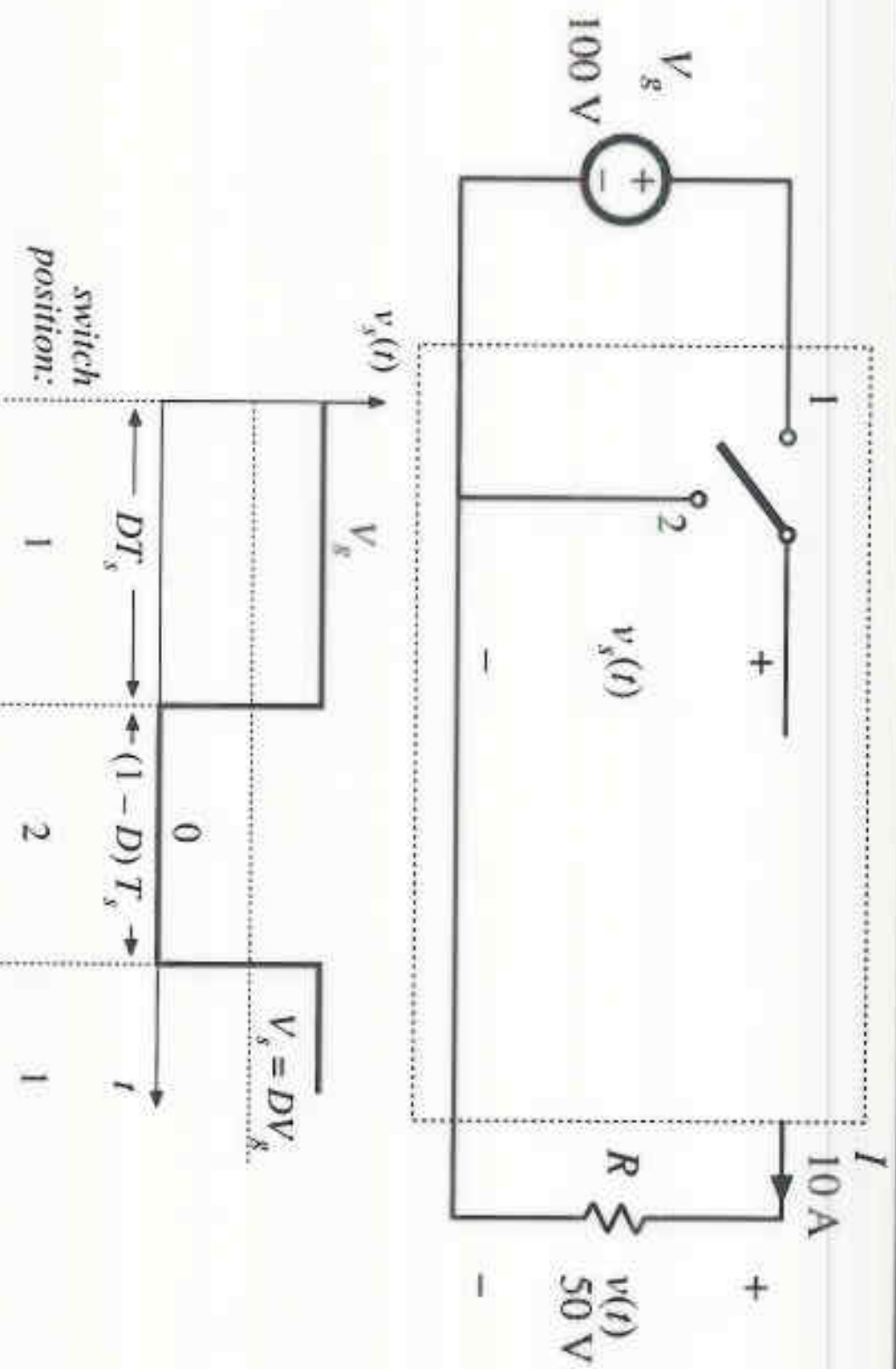

The switch changes the dc voltage level

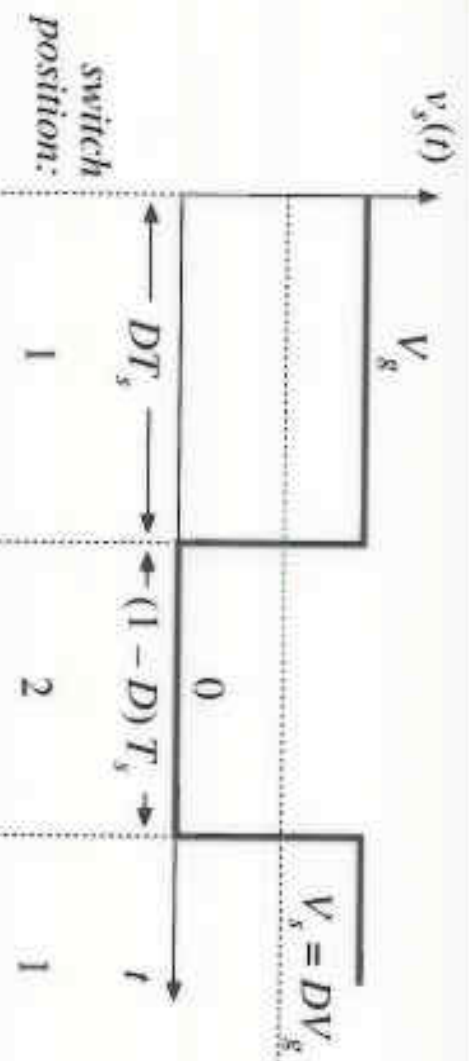

D = switch duty cycle

$$0 \leq D \leq 1$$


T_s = switching period

f_s = switching frequency
 $= 1 / T_s$

DC component of $v_s(t)$ = average value:


$$V_s = \frac{1}{T_s} \int_0^{T_s} v_s(t) dt = DV_g$$

Control is invariably required

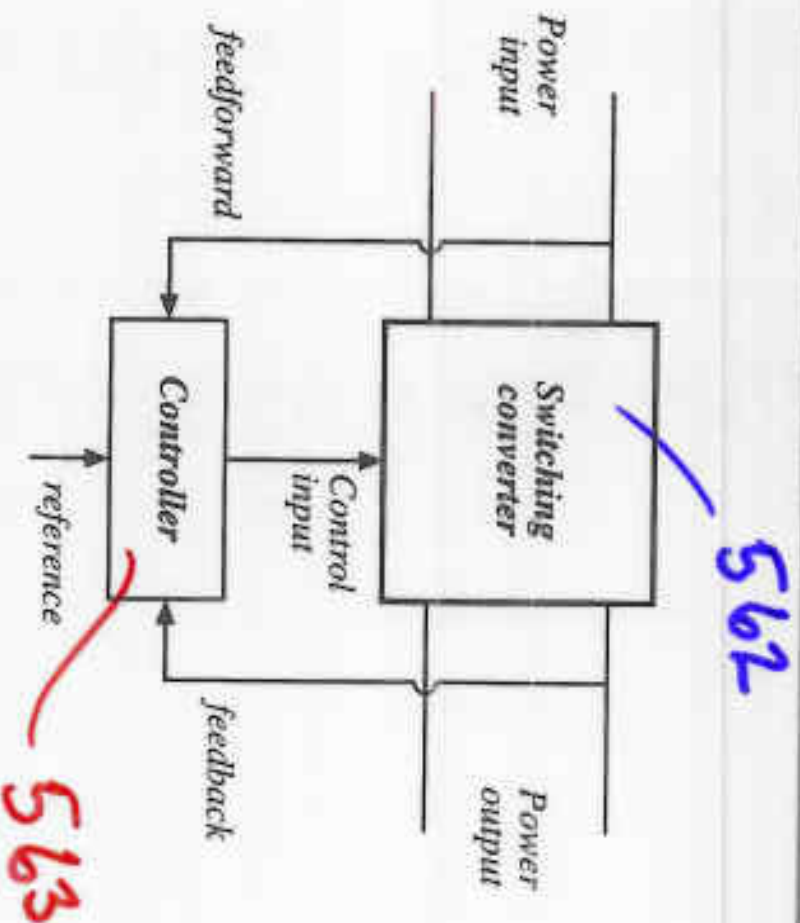


Part II. Converter dynamics and control

Closed-loop converter system

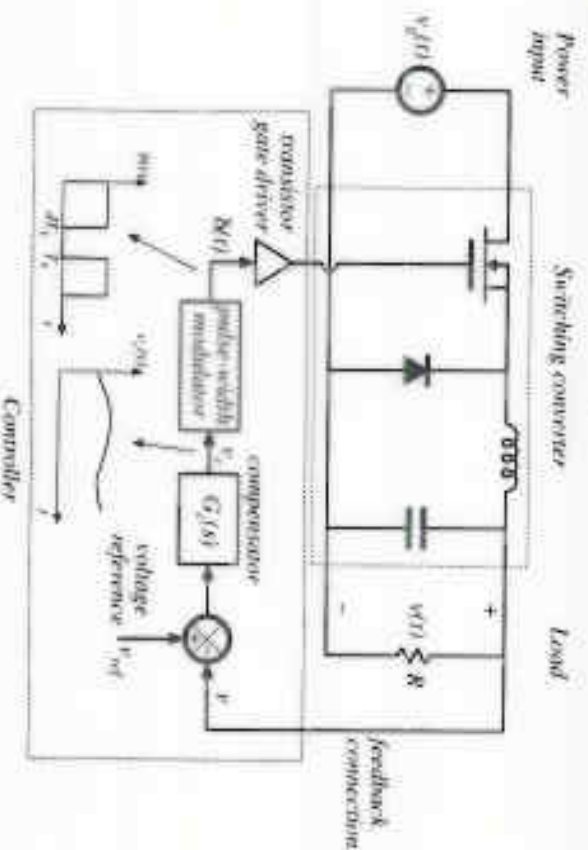

Averaging the waveforms

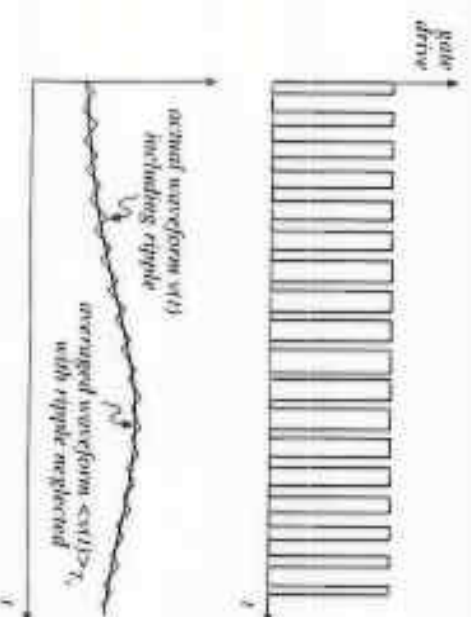

Small-signal averaged equivalent circuit

