


Power Electronics 3

564 Lecture 3 $Z(s)$

1/5

Up

Page 1

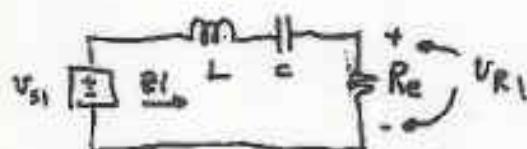

$$H(s) = \frac{v_{R1}(s)}{v_{s1}(s)}$$

Plot $\|H\|$

$$H(s) = \frac{R}{Z_i(s)}$$

$$Z_i(s) = sL + \frac{1}{sC} + R$$

20dB/decade



20dB/decade

$$|Z_C| = \frac{1}{\omega C}$$

$$|Z_L| = \omega L$$


$$Z_C = Z_L @$$

$$\omega_R = \frac{1}{\sqrt{LC}}$$

$$|Z_C| = |Z_L| @ \omega_R$$

$$= Z_0 = \sqrt{\frac{L}{C}}$$

Page 2

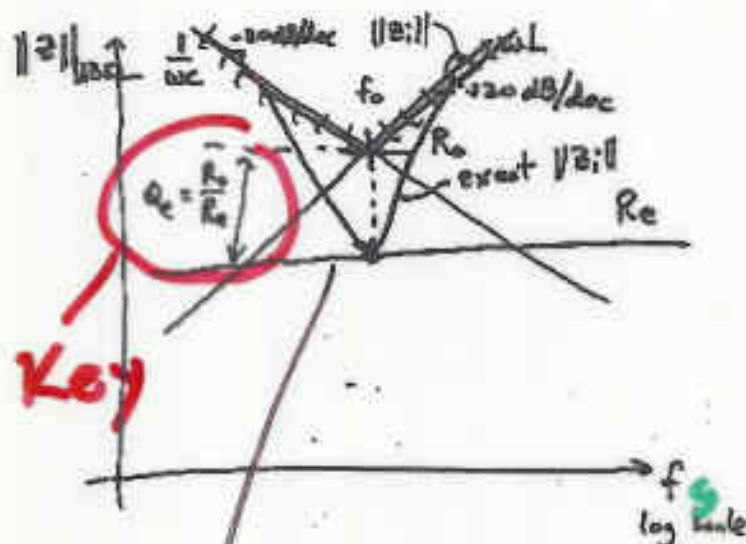

Page 3

Case: $R_0 < Z_0$

$$Z_i(\omega_R) = ?$$

at f_0 :

$$\omega_0 = 2\pi f_0$$

$$R_0 = \frac{1}{\omega_0 C} = \omega_0 L \Rightarrow \omega_0^2 = \frac{1}{LC}$$

$$= \sqrt{\frac{1}{LC}} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

Exact $\|Z_i\|$ at $\omega = \omega_0$

$$Z_i(j\omega) = j\omega L + \frac{1}{j\omega C} + R_e = jR_0 + \frac{R_0}{j} + R_e$$


$$= R_e$$

$\frac{1}{\omega_0 C} = R_0$


 Z_C cancels Z_L

$$V_R/V_{IN} = \frac{R_e}{Z_i} = M = \frac{V_{out}}{V_{sig}}$$

Page 4

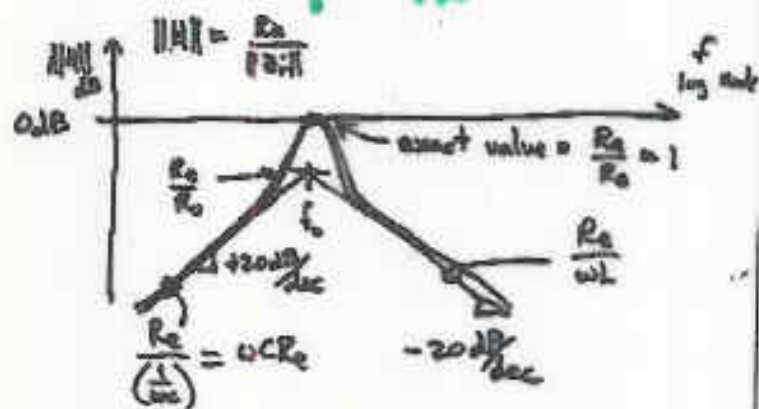

Page 5

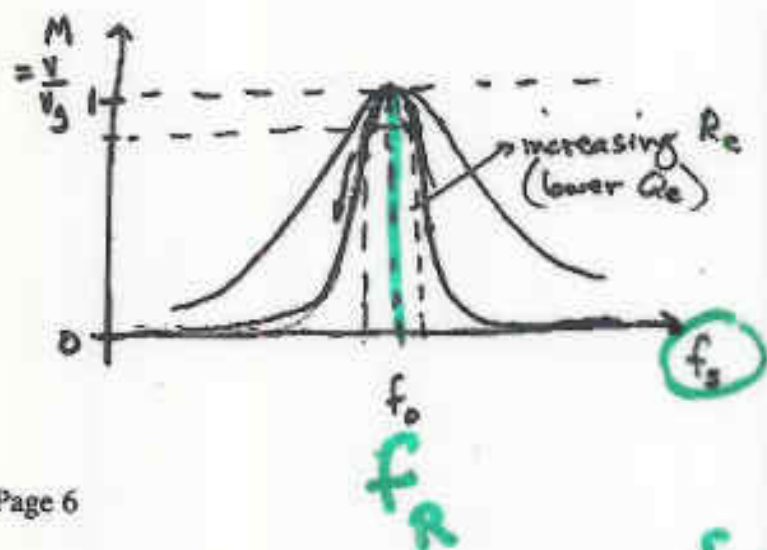

$$Q = \frac{Z_0}{R} = \frac{\sqrt{L/C}}{R}$$

$$Q = \frac{1}{\omega R} \sqrt{\frac{L}{C}}$$

$$= \frac{1}{\omega_R C R}$$

Page 6

Define

$$\frac{f_s}{f_R} = F$$

Equation of M vs F

$$M = \frac{V}{V_g} \quad F = \frac{f_s \cdot \pi}{f_0 \cdot \pi} = \frac{\omega_s}{\omega_0}$$

$$M = \|H(j\omega_s)\| \quad \omega_s = 2\pi f_s$$

$$H(j\omega_s) = \frac{R_e}{j\omega_s L + \frac{1}{j\omega_s C} + R_e} = \frac{V_0}{V_{\text{signal}}}$$

Page 7

$$= \frac{j\omega_s C R_e}{(j\omega_s L)(j\omega_s C) + 1 + j\omega_s C R_e}$$

$$= \frac{j\omega_s C R_e}{1 + j\omega_s C R_e - \omega_s^2 L C}$$

$\underbrace{j\omega_s C R_e}_{= j \frac{F}{Q_e}} \quad \underbrace{\omega_s^2 L C}_{\frac{\omega_s^2}{\omega_0^2} = F^2}$

Page 8

$$Q_e = \frac{R_0}{R_e} = \frac{1}{\omega_0 C R_e}$$

$$\Rightarrow C = \frac{1}{\omega_0 R_e Q_e}$$

$$\text{so } j\omega_s C R_e = \frac{j\omega_s R_e}{\omega_0 R_e Q_e} = j \frac{\omega_s}{\omega_0} \frac{1}{Q_e} = j \frac{F}{Q_e}$$

Page 9

3/5

$$\frac{V_0}{V_g} = f(F, Q)$$

$$\omega_0 = \omega_R \quad \omega_R = \frac{1}{\sqrt{LC}}$$

$$R_0 = \sqrt{L/C} \quad Q = \omega_R R = \frac{1}{\omega_R C R}$$

4/5

$$H(j\omega) = \frac{j \frac{F}{Q_e}}{1 - F^2 + j \frac{F}{Q_e}}$$

$$M = \|H(j\omega)\| = \frac{\|j \frac{F}{Q_e}\|}{\|1 - F^2 + j \frac{F}{Q_e}\|}$$

$$= \frac{\left(\frac{F}{Q_e}\right)}{\sqrt{(1 - F^2)^2 + \left(\frac{F}{Q_e}\right)^2}}$$

$$\left. \begin{array}{l} \frac{V_{out}}{V_{in}} \end{array} \right\}$$

Page 10

$$M = \frac{1}{\sqrt{1 + \frac{Q_e^2}{F^2} (1 - F^2)^2}}$$

$$M = \frac{1}{\sqrt{1 + Q_e^2 \left(\frac{1}{F} - F\right)^2}}$$

Page 11