


Choices for high Q circuits

- #1 $Z_L > R$ Series $R < Z_L$
- #2 $Z_L < R$ (Both Mixed Parallel) $R > Z_L$

Topology of Resonance

① Pure Series

$R < Z_L$

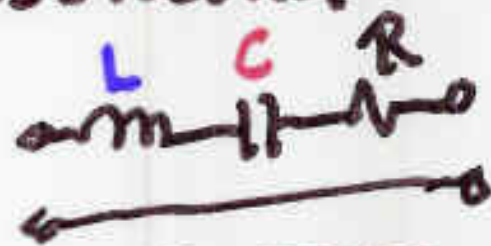

② Pure Parallel

$R > Z_L$



③ Mixed:




④ Special Purpose



$R = 0$ (vs) $R = \infty$





013 Simple Series

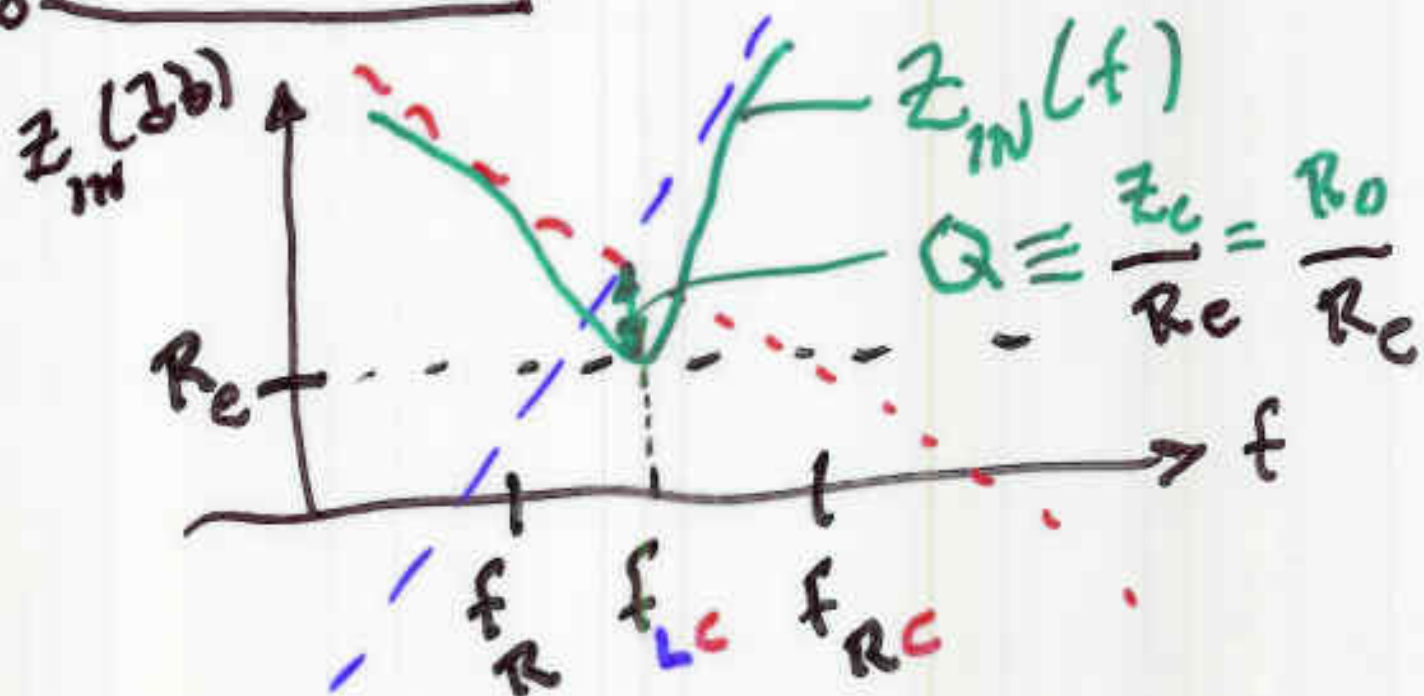

Pure Parallel


$$z_L \equiv \sqrt{\frac{L}{C}}$$

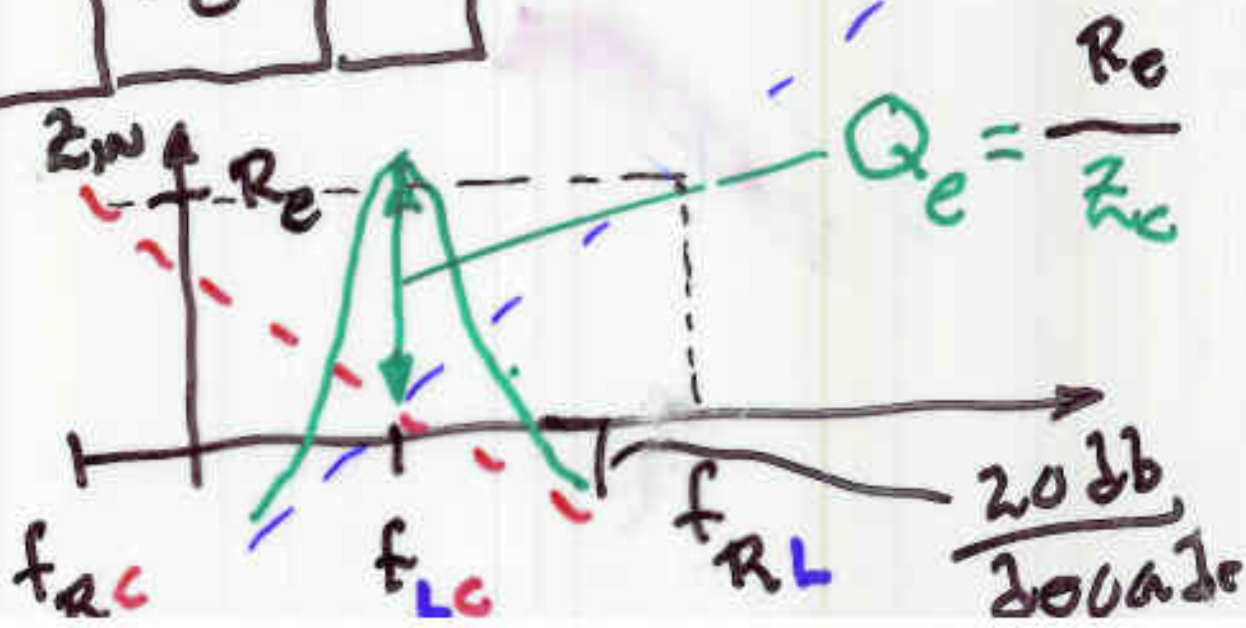

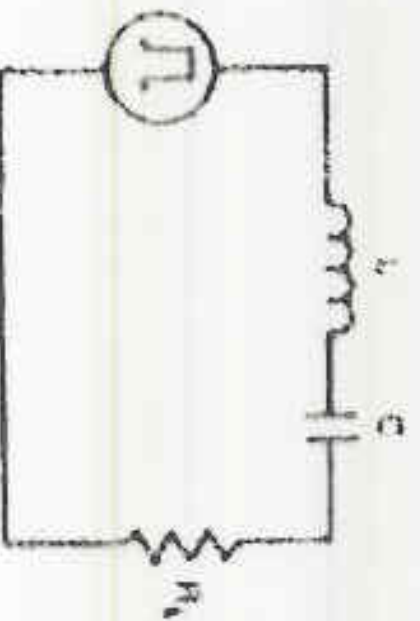

A. SERIES LOADING
(current output)

why $R_L < \sqrt{\frac{L}{C}}$

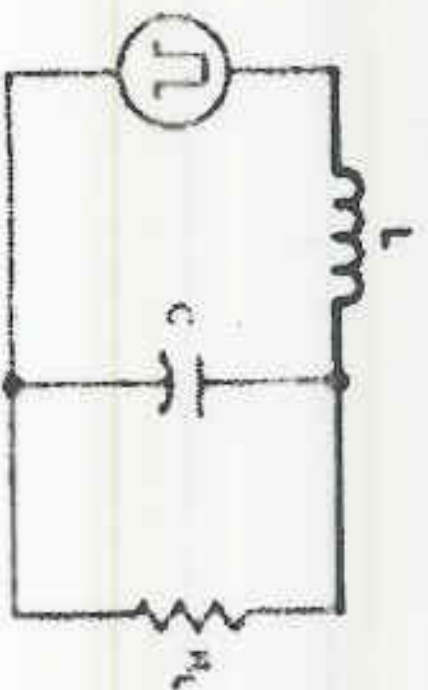

B. PARALLEL LOADING
(voltage output)

why $R_L > \sqrt{\frac{L}{C}}$


Fig. 9 - Resonant Mode Loading

Flourescent Light: - () -



How to get V_{off} large
 V_{on} small

"naturally" via resonant circuit

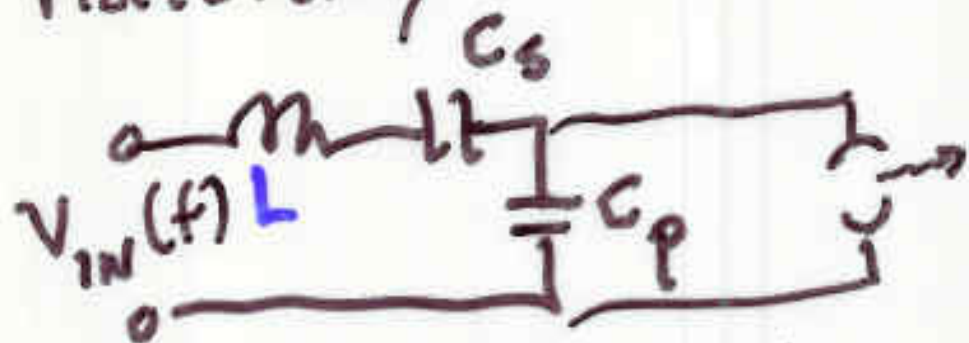

$$f_R (\text{light off}) = \frac{1}{\sqrt{L C_{eff}}} = f_{High}$$


smaller
than C_p

$$f_R (\text{light on}) = \frac{1}{\sqrt{L C_s}} = f_{Low}$$

$$V_{IN}(f)$$

Near resonance

$$V_L \approx Q V_{IN}$$

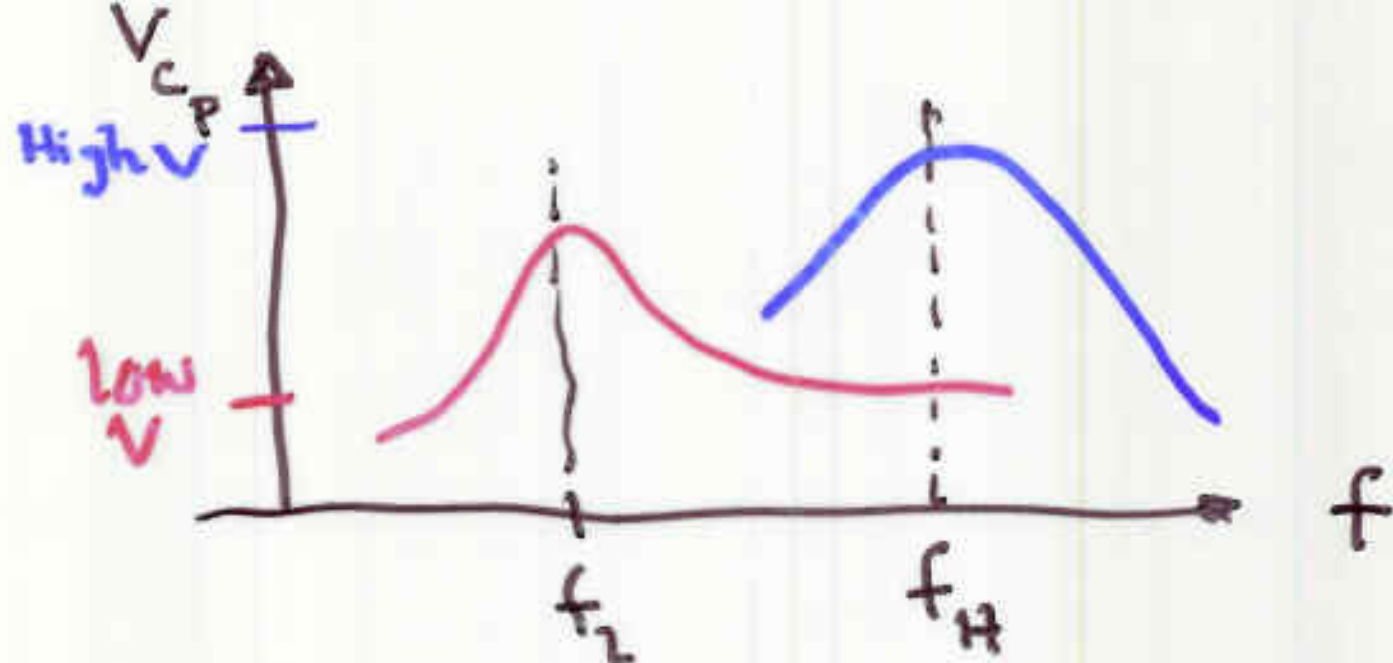

Sweep f starting $f > f_H$



$f = f_H$ V_{CP} is max

CFR breakdown shorts


C_p : circuit moves to red

f_L curve $V_{CP} \downarrow$



LCC Resonant Supply

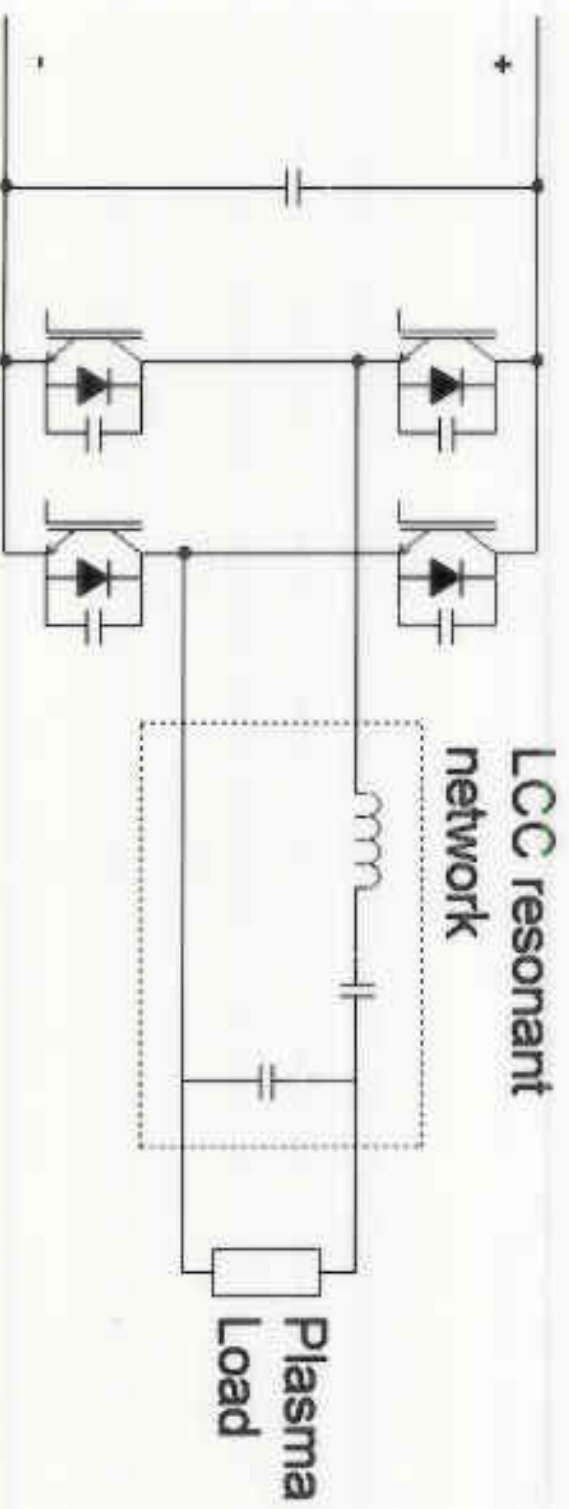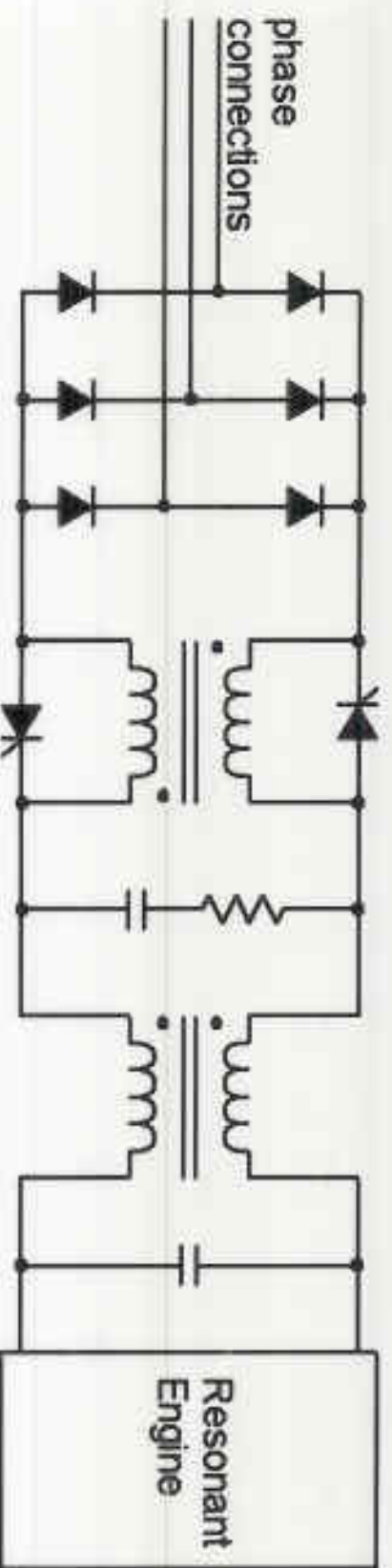

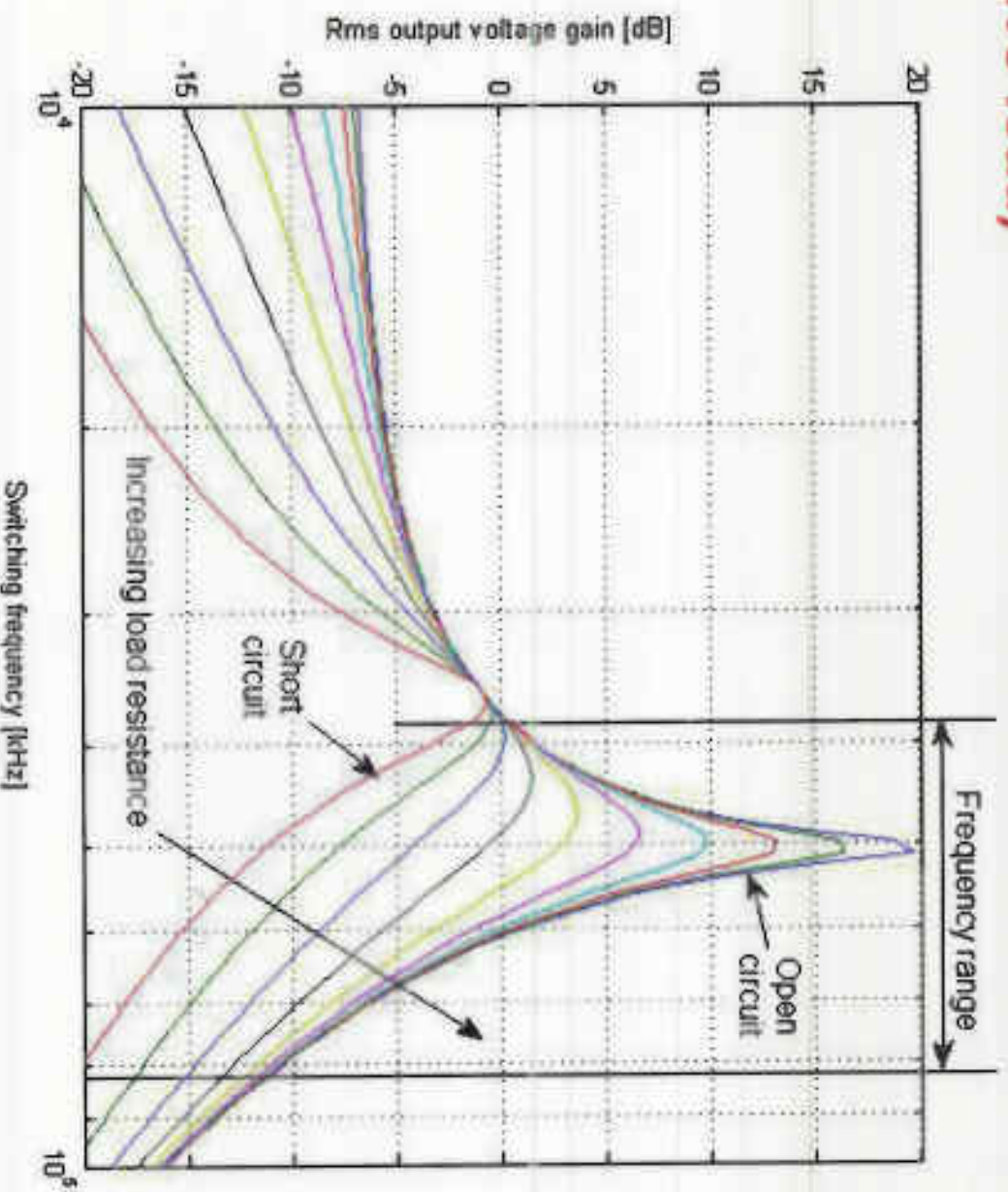Voltage Gain – Resonant supply with LCC tank (Resistive load)



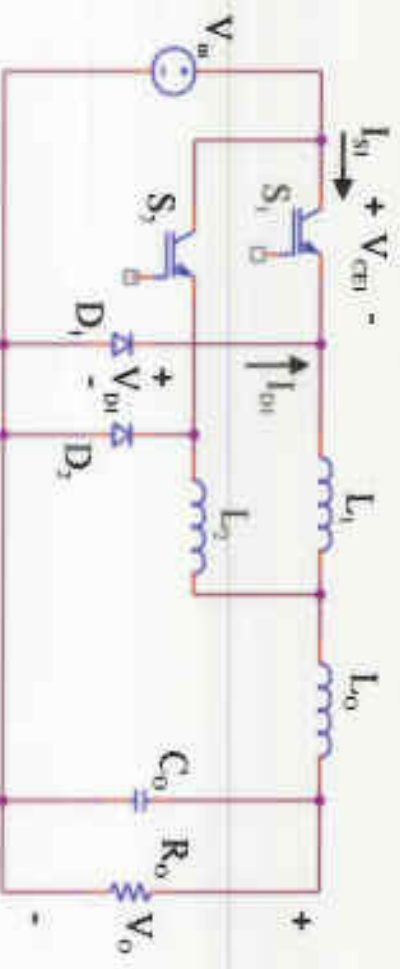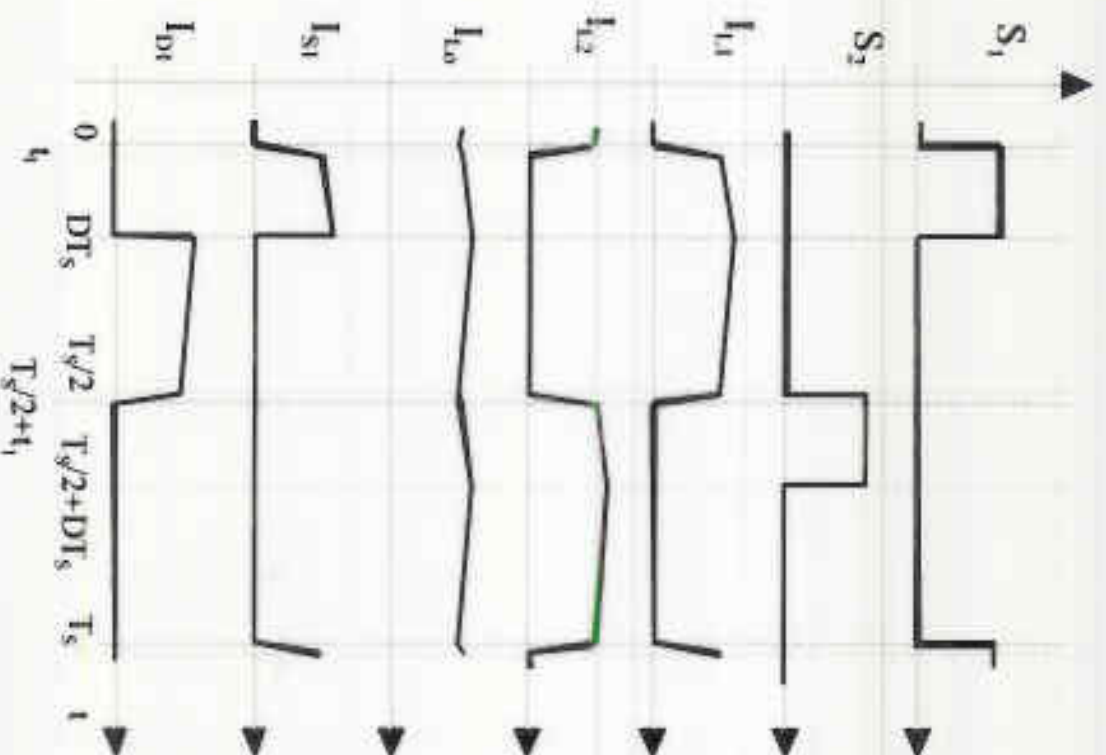Interleaved ZCT converter operation (ideal waveforms)



Diode recovery slope:

$$V_{in} / (L_1 + L_2)$$

Transition interval:

$$t_1 = \frac{I_{Lo}(L_1 + L_2)}{V_{in}}$$