

You said  $f_{sw} \uparrow$  better but ...

#### 4.3.4. Efficiency vs. switching frequency

Don't  $W_{off}$  often Choose diode

Add up all of the energies lost during the switching transitions of one switching period:  $f_{type}$  to get  $Q_{rr}$

DC loss

$$W_{tot} = W_{on} + W_{off} + W_D + W_C + W_L + \dots + \underbrace{W_{par}}_{\text{parasitics}}$$

Average switching power loss is

AC loss

$$P_{sw} = W_{tot} f_{sw}$$

Total converter loss can be expressed as

$$P_{loss} = P_{cond} + P_{fixed} + \underbrace{W_{tot} f_{sw}}_{\text{largest loss term}}$$

where

$P_{fixed}$  = fixed losses (independent of load and  $f_{sw}$ )

$P_{cond}$  = conduction losses

564 to 7hr rescue

$$P_{\text{DYNAMIC}} = \frac{1}{2} (t_r + t_f) I_{\text{LOAD}} V_{\text{IN}} f_s + V_{\text{DRIVE}} Q_G f_s$$

$$P_{\text{CONDUCTION}} = I_{\text{LOAD}}^2 R_{\text{DS(ON)}} \Delta P_{\text{PWM}}$$

$$P_{\text{DISSIPATION}} = P_{\text{DYNAMIC}} + P_{\text{CONDUCTION}}$$

depend on  $Q_G$

Want small

Gate Drive losses  $Q_G$  small Lower losses

$R_{\text{DS(ON)}} \propto Q_G$

Product should be small!

nC

# SOP Advance MOSFET Ron-Qg Comparison

● = Competing Products

Lower Switching Loss

Qg (typ) @ Vds=24V, Vgs=5V [nC]

0 10 20 30 40 50 60 70

Higher Efficiency

TPCA8004H

TPCA8003H

Ron (max) @ 4.5V [mOhm]

Lower Conduction Loss

mA

$R_{DS(on)} \propto Q_g$  want's to be small

Exam

n-channel

which type of FET



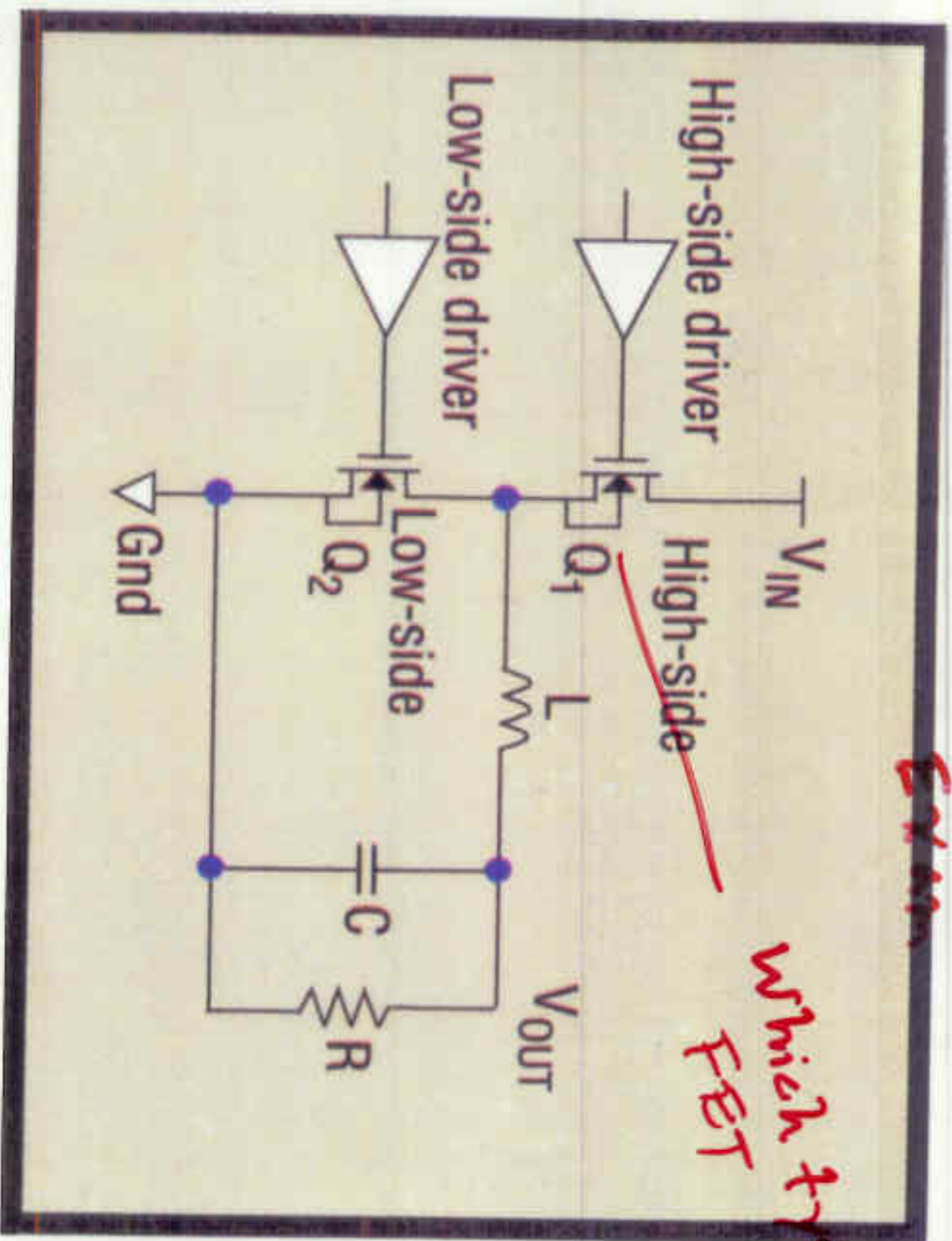


Fig. 1. Circuit diagram of dc-to-dc synchronous buck converter.

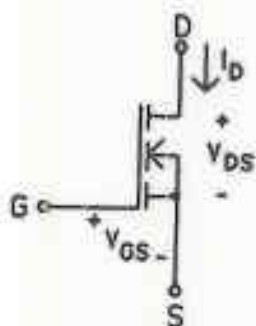


Symbol

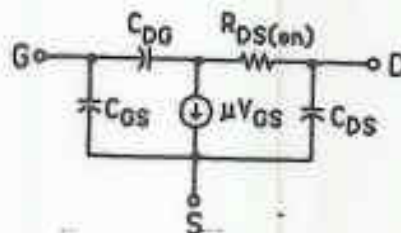

Approximate Equivalent Circuit


Gate Drive

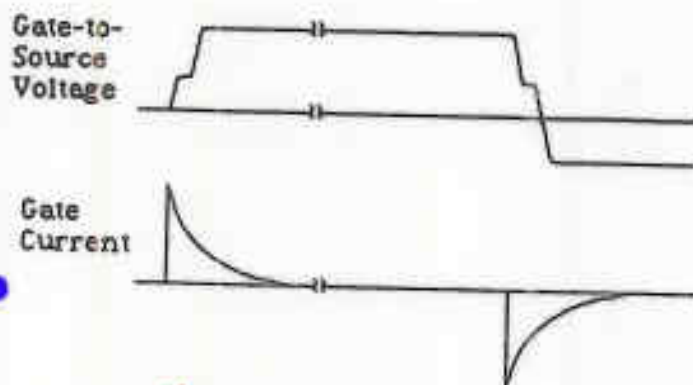

Gate Drive Power  

$$P = f_{sw} [E_{on} + E_{off}]$$
  
 neglect as  $V_G, I_G$  are low

$E(off \rightarrow on)$

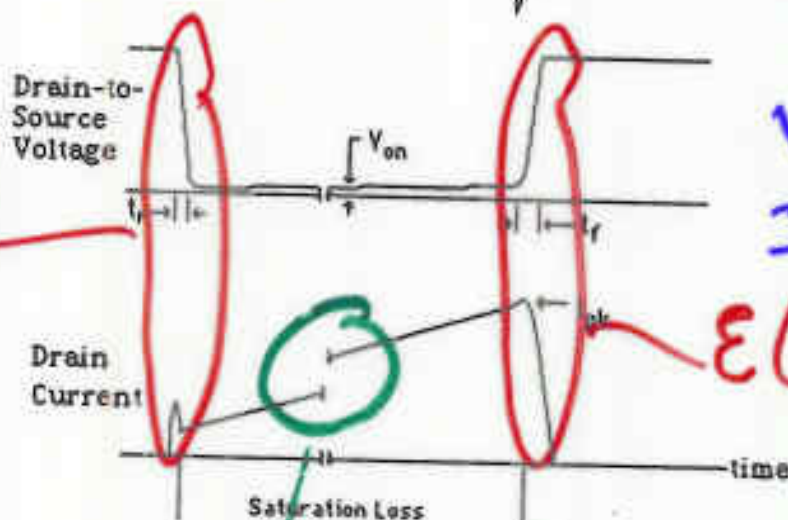

$V_{ON}$  rises as  $I_{ON}$  ramps up

$E(on \rightarrow off)$

Waveforms for a power MOSFET in a PWM switching power supply.


$$P(switching) = f_{sw} [E(off \rightarrow on) + E(on \rightarrow off)]$$

These  $I_D$  and  $V_{DS}$  waveforms will allow us to calculate switch loss for each switching cycle. The cycle includes two parts as each switch alternates on and off alternatively. We neglect switch driver losses for now.

$$\frac{di}{dt} \text{ limited by } \frac{V}{L}$$

Not in Erickson

## A simple MOSFET equivalent circuit

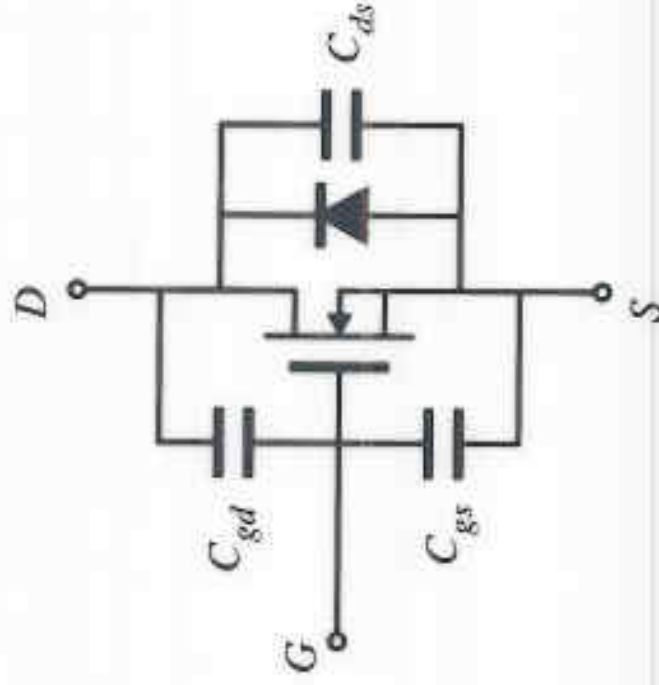

- $C_{gs}$  : large, essentially constant
- $C_{gd}$  : small, highly nonlinear
- $C_{ds}$  : intermediate in value, highly nonlinear
- switching times determined by rate at which gate driver charges/discharges  $C_{gs}$  and  $C_{gd}$

$$C_{ds}(v_{ds}) = \frac{C_0}{\sqrt{1 + \frac{v_{ds}}{V_0}}}$$


$$C_{ds}(v_{ds}) \approx C_0 \sqrt{\frac{V_0}{v_{ds}}} = \frac{C_0}{\sqrt{v_{ds}}}$$

$C_V = Q$   $C_{DS} \uparrow$  when  $V_{GS} \uparrow$  is good !! for fast off time or 11 slow on time

Fig 4.29 Pg 80

A simple MOSFET equivalent circuit

More free parasitic elements: C

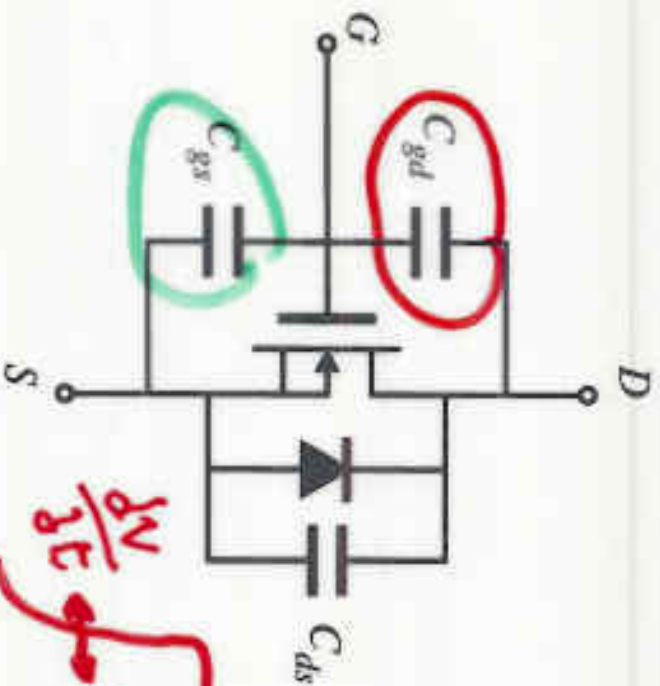

$$\frac{dV}{dt} \propto \frac{I}{C}$$

- $C_{gs}$ : large, essentially constant
- $C_{gd}$ : small, highly nonlinear
- $C_{ds}$ : intermediate in value, highly nonlinear
- switching times determined by rate at which gate driver charges/ discharges  $C_{gs}$  and  $C_{gd}$

100nF  
10nF  
Miller C

$$C_{ds}(V_{ds}) = \frac{C_0}{\sqrt{1 + \frac{V_{ds}}{V_0}}}$$

$$C_{ds}(V_{ds}) \approx C_0 \sqrt{\frac{V_0}{V_{ds}}} = \frac{C_0}{\sqrt{V_{ds}}}$$



# Can we justify $W_C \sim \frac{1}{2} C V^2$ ?

MOSFET nonlinear  $C_{ds}(V_{DS})$

Approximate dependence of incremental  $C_{ds}$  on  $V_{DS}$ :

$$\underline{C_{ds}(V_{DS})} \approx C_0 \sqrt{\frac{V_0}{V_{DS}}} = \frac{C_0}{\sqrt{V_{DS}}}$$

$$C = f(V)$$

Energy stored in  $C_{ds}$  at  $V_{DS} = V_{DS}$ :

$$i_C = C \frac{dV_{DS}}{dt}$$

$$W_{C_{ds}} = \int_{V_{DS}} V_{DS} i_C dt = \int_0^{V_{DS}} V_{DS} C_{ds}(V_{DS}) dV_{DS}$$

$$W_{C_{ds}} = \int_0^{V_{DS}} C_0(V_{DS}) \sqrt{V_{DS}} dV_{DS} = \frac{2}{3} C_{ds}(V_{DS}) V_{DS}^2$$

$$\approx \frac{1}{2} C V^2$$

$$C_{DS} = \frac{C_0}{\sqrt{V_{DS}}}$$

— same energy loss as linear capacitor having value

$$\frac{4}{3} C_{ds}(V_{DS})$$

Appears 33% larger

due to  $C(V)$


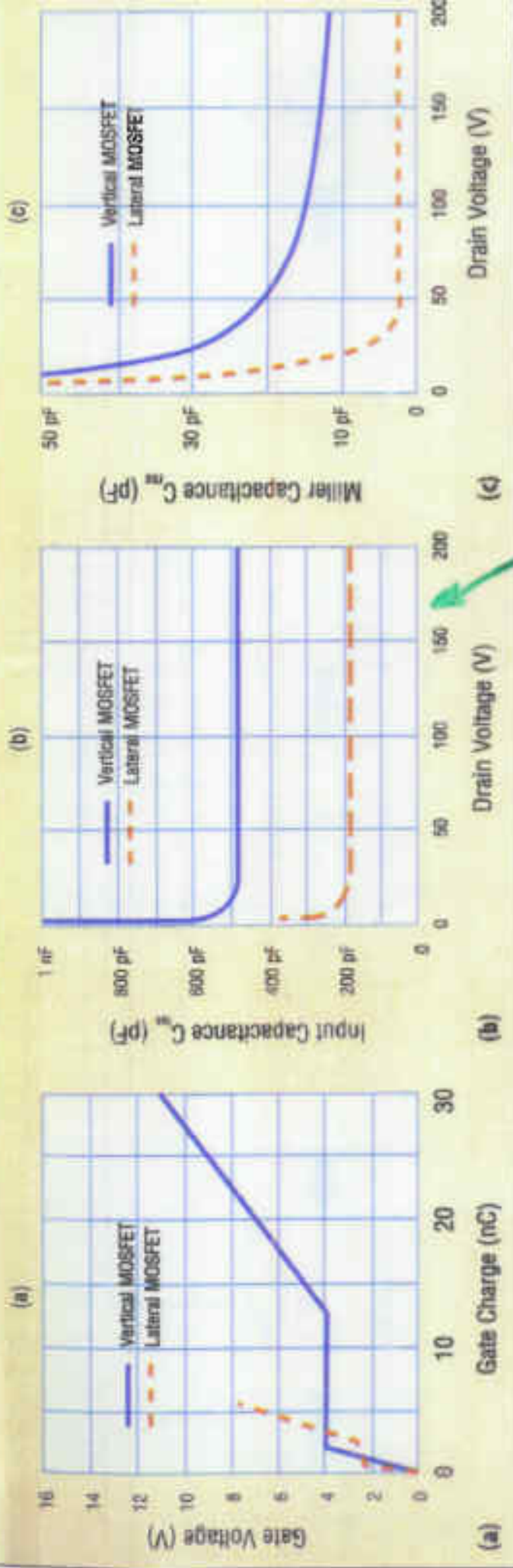


Fig. 3. Standard vertical MOSFET versus an integrated lateral MOSFET: (a) gate charge, (b) input capacitance and (c) Miller capacitance.

## Switching loss caused by semiconductor output capacitances

### *Buck converter example*

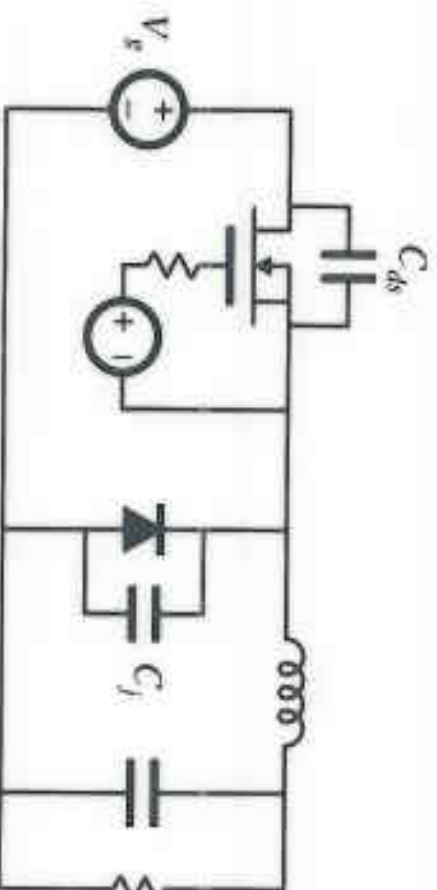

Energy lost during MOSFET turn-on transition  
(assuming linear capacitances):


$$W_C = \frac{1}{2} (C_{ds} + C_f) V_s^2$$

Fig 4.52 pg 98

$C_{DS} = \text{min} \Rightarrow 10 \mu\text{F}$

Example: semiconductor output capacitances

Buck converter example

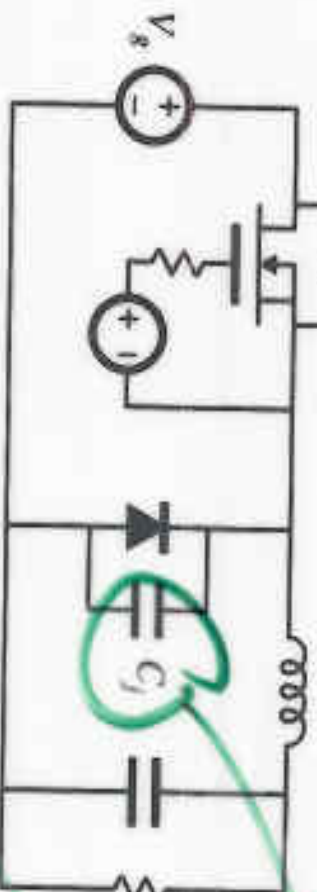

drawn to source  
 $C_{DS} \sim \frac{C_{DS}}{\sqrt{V_{DS}}}$

Typical?  
sec spec  
sheet

Energy lost during MOSFET turn-on transition  
(assuming linear capacitances):

$$W_C = \frac{1}{2} (C_{DS} + C_j) V_g^2$$

↑  
Tr was off is  $C_{DS}$  max or min?

68  
Tr was storing charge  
IR must eat this during turn-on

## Some other sources of this type of switching loss

### Schottky diode

- Essentially no stored charge  $I_{rr} \rightarrow 0$
- Significant reverse-biased junction capacitance

### Transformer leakage inductance

- Effective inductances in series with windings
- A significant loss when windings are not tightly coupled

### Interconnection and package inductances

- Diodes
- Transistors
- A significant loss in high current applications

wiring  
PCB



# Inside a failed Power MOSFET

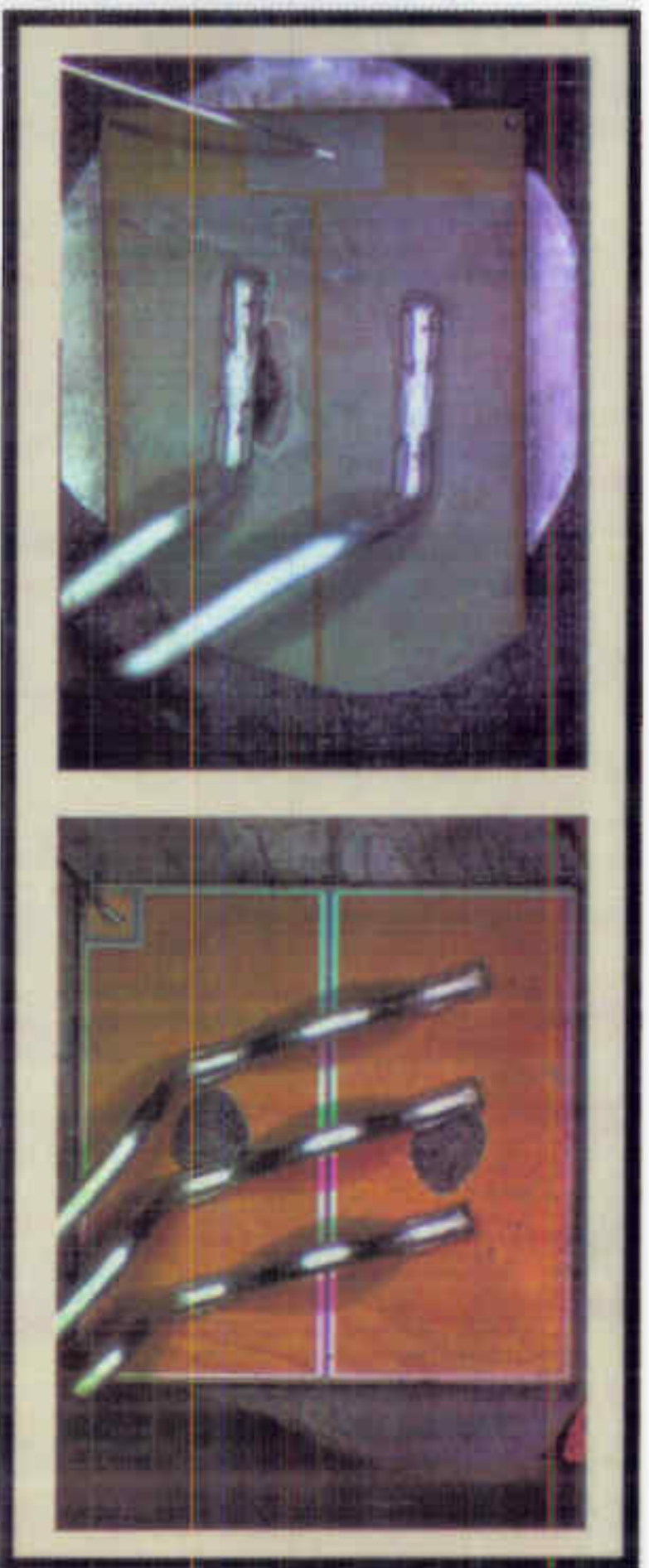


Fig. 6. FETs destroyed by the capacitor-dump test. Planar is on the left; Trench is on the right. Note the dual damage sites on the trench part.

## MOSFET: conclusions

- A majority-carrier device: fast switching speed **to 3 MHz**
- Typical switching frequencies: tens and hundreds of kHz **600 kHz**
- On-resistance increases rapidly with rated blocking voltage
- Easy to drive
- The device of choice for blocking voltages less than 500V  **$V_{DS} = 600$ ,  $R_{DS} = 14 \Omega$**
- **1200** 1000V devices are available, but are useful only at low power levels **(100W)**
- Part number is selected on the basis of on-resistance rather than current rating

## Summary of chapter 4

---

1. How an SPST ideal switch can be realized using semiconductor devices depends on the polarity of the voltage which the devices must block in the off-state, and on the polarity of the current which the devices must conduct in the on-state.
2. Single-quadrant SPST switches can be realized using a single transistor or a single diode, depending on the relative polarities of the off-state voltage and on-state current.
3. Two-quadrant SPST switches can be realized using a transistor and diode, connected in series (bidirectional-voltage) or in anti-parallel (bidirectional-current). Several four-quadrant schemes are also listed here.
4. A “synchronous rectifier” is a MOSFET connected to conduct reverse current, with gate drive control as necessary. This device can be used where a diode would otherwise be required. If a MOSFET with sufficiently low  $R_{on}$  is used, reduced conduction loss is obtained.

## Summary of chapter 4

---

5. Majority carrier devices, including the MOSFET and Schottky diode, exhibit very fast switching times, controlled essentially by the charging of the device capacitances. However, the forward voltage drops of these devices increases quickly with increasing breakdown voltage.
6. Minority carrier devices, including the BJT, IGBT, and thyristor family, can exhibit high breakdown voltages with relatively low forward voltage drop. However, the switching times of these devices are longer, and are controlled by the times needed to insert or remove stored minority charge.
7. Energy is lost during switching transitions, due to a variety of mechanisms. The resulting average power loss, or switching loss, is equal to this energy loss multiplied by the switching frequency. Switching loss imposes an upper limit on the switching frequencies of practical converters.

## Summary of chapter 4

---

8. The diode and inductor present a “clamped inductive load” to the transistor. When a transistor drives such a load, it experiences high instantaneous power loss during the switching transitions. An example where this leads to significant switching loss is the IGBT and the “current tail” observed during its turn-off transition.
9. Other significant sources of switching loss include diode stored charge and energy stored in certain parasitic capacitances and inductances. Parasitic ringing also indicates the presence of switching loss.