

Chapter 4. Switch Realization

slow 4 quadr
wire switch
VS



Semiconductor
fast 1-2 quads

4.1. Switch applications

Single-, two-, and four-quadrant switches. Synchronous rectifiers

4.2. A brief survey of power semiconductor devices

Power diodes, MOSFETs, BJTs, IGBTs, and thyristors

4.3. Switching loss

Two parts are?

Transistor switching with clamped inductive load. Diode recovered charge. Stray capacitances and inductances, and ringing. Efficiency vs. switching frequency.

4.4. Summary of key points

Total Loss = $S_w \text{ Loss} + \text{Core Losses} + i^2 R$

Chapter 4. Switch Realization

Not yet in solid state

Mechanical Switch: $R_{off} = \infty$

bipolar $R_{on} = 0$

Back to the Future: μ Mechanical Switches @ 100 kHz

4.1. Switch applications

Single-, two-, and four-quadrant switches. Synchronous rectifiers

fast but limited quadrants

4.2. A brief survey of power semiconductor devices

Power diodes, MOSFETs, BJTs, IGBTs, and thyristors

4.3. Switching loss

Total = $P_{DC} + \text{Switch Loss}$

Transistor switching with clamped inductive load. Diode



recovered charge. Stray capacitances and inductances, and ringing. Efficiency vs. switching frequency.

4.4. Summary of key points


$f_{sw} \left[\frac{1}{2} C V^2 + \frac{1}{2} i_c^2 \right]$

3 I_{rr} V_{off} meaning

Some basic switch applications

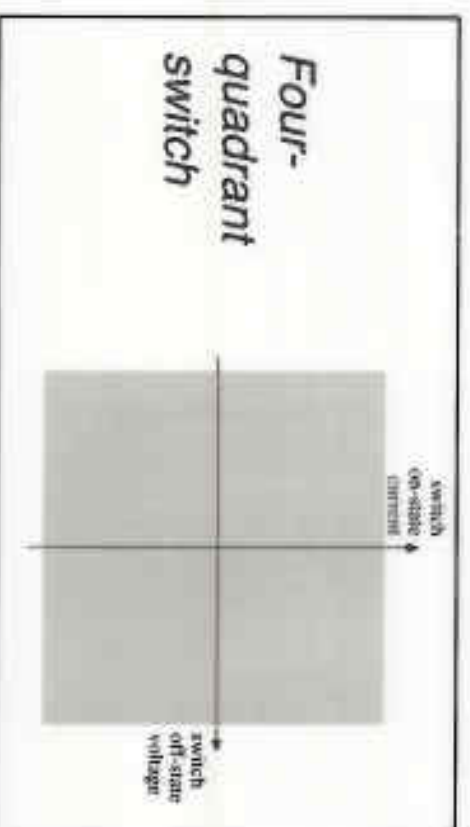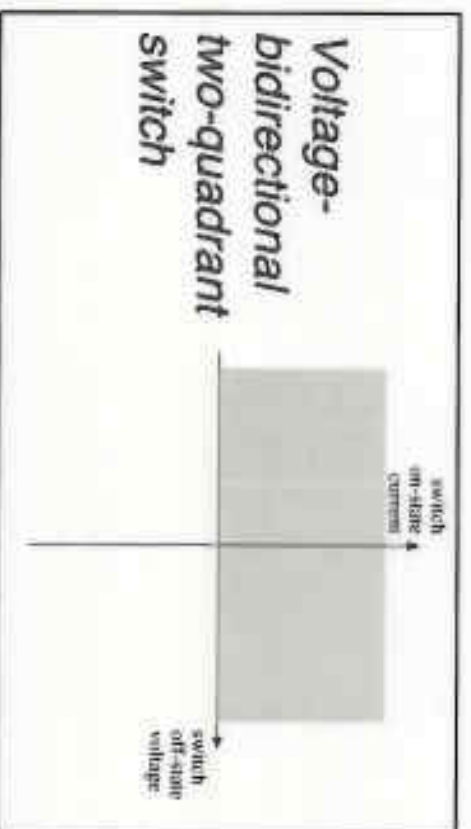

Quadrants of SPST switch operation

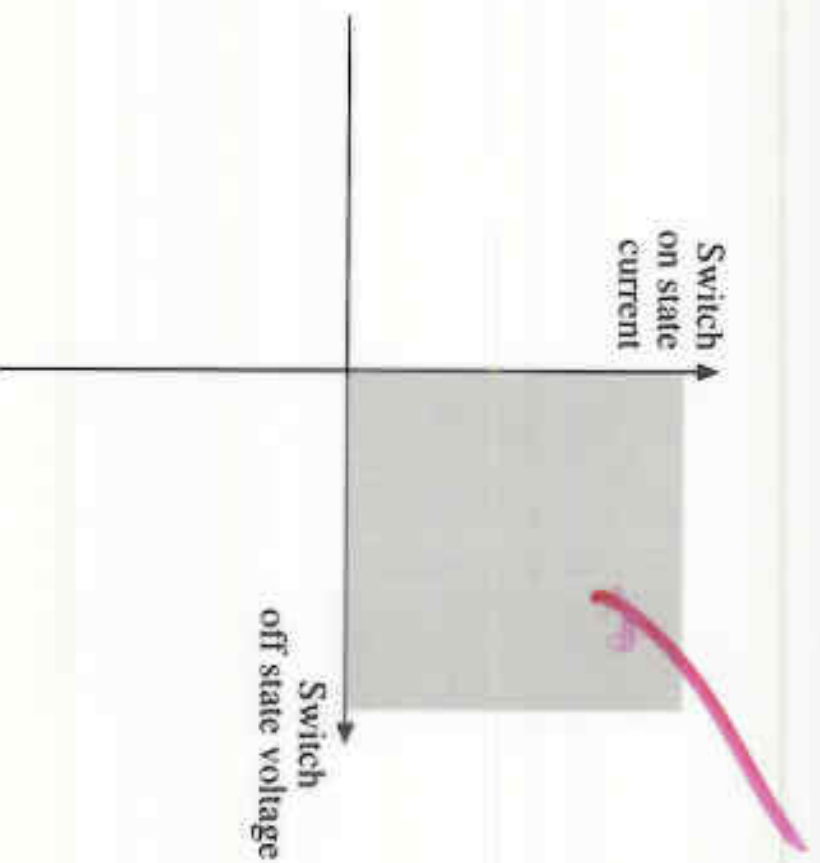

Solid state has limits


A single-quadrant switch example:

ON-state: $i > 0$

OFF-state: $v > 0$

Fig 4.3

Quadrants of SPST switch operation

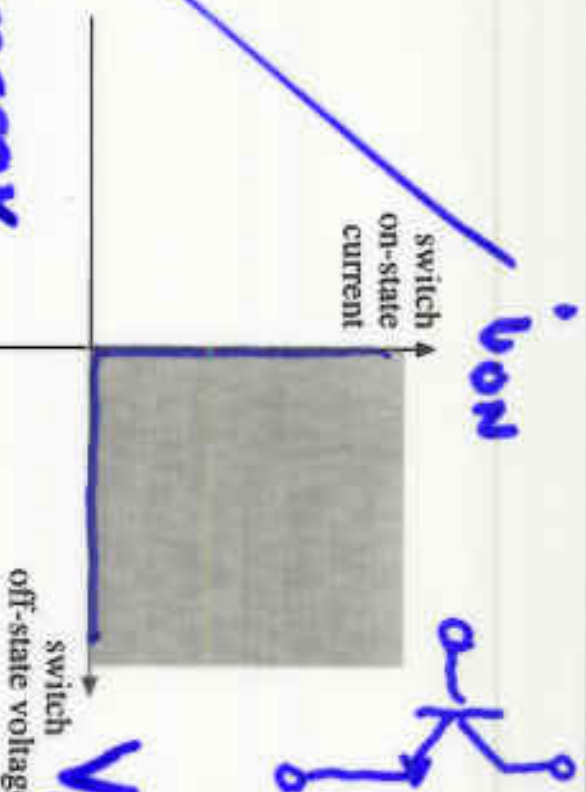

BST

A single-quadrant
switch example:

ON-state: $i > 0$

OFF-state: $v > 0$

"ON" stored energy
 $\frac{1}{2} L(i_{on})^2$

"OFF" stored energy
 $\frac{1}{2} C(\text{device}) V_{off}^2$

causes ON \rightarrow off only

1055cs
Go for it?




compare

causes off \rightarrow ON
105505 only

Go for it?

Some basic switch applications

MOSFET
 $\pm i_{OK}$

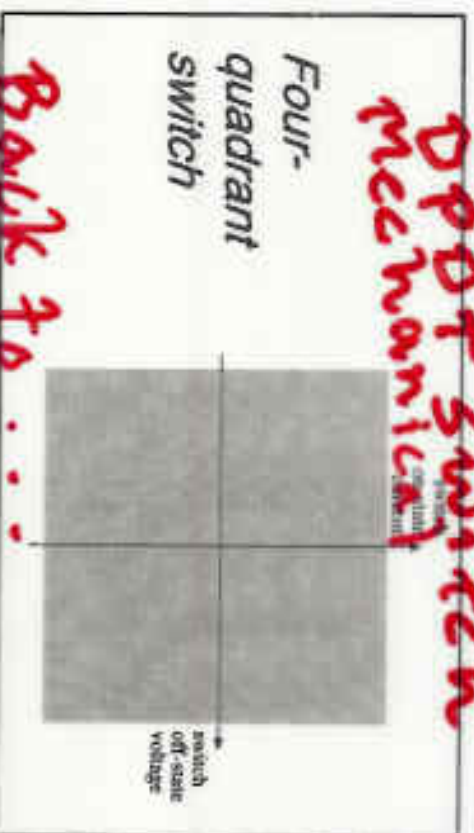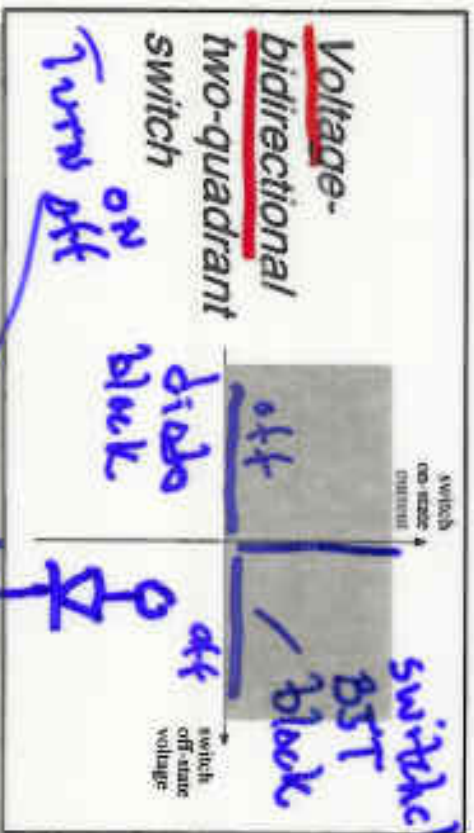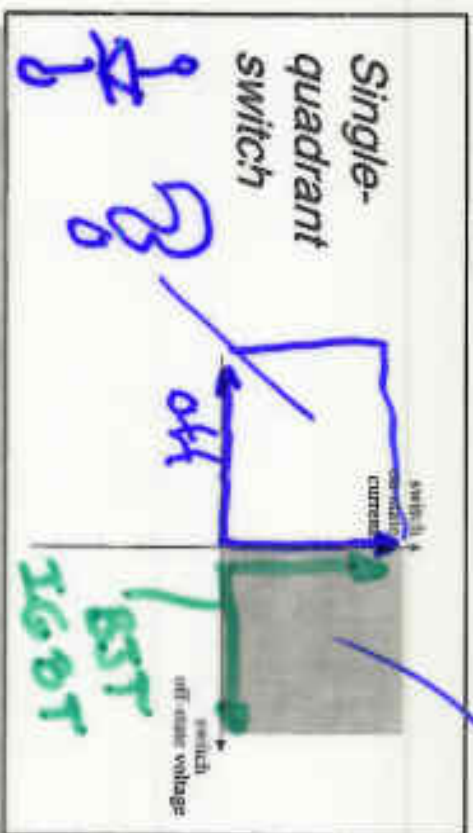

DPDT switch
mechanical

Back to ...


SPST (single-pole single-throw) switches

SPST switch, with voltage and current polarities defined




All power semiconductor devices function as SPST switches.

Buck converter with SPDT switch:

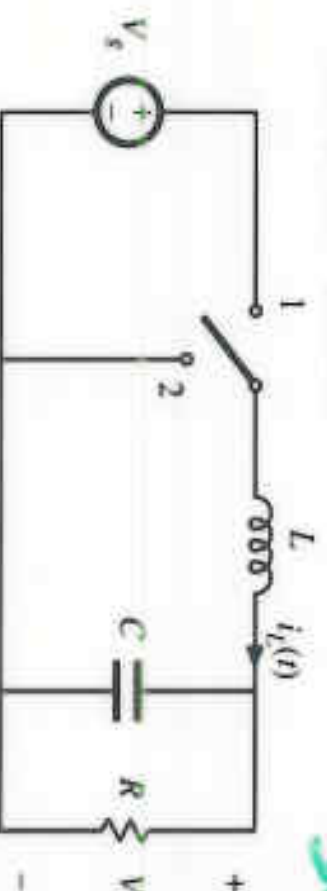

with two SPST switches:

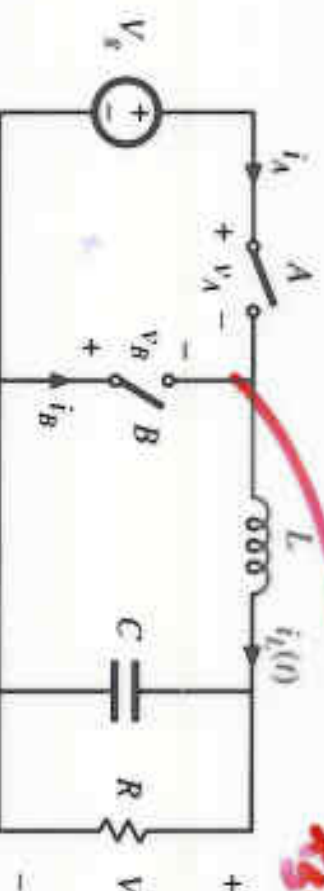


Semiconductors
100ns → MHz

New MEMS
500 10kHz

SPST (single-pole single-throw) switches

stand Fig 4.2 p 64

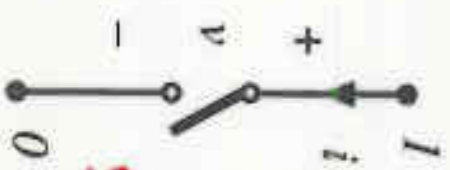SPST switch, with voltage and current polarities defined



Voff
air
arc
30kV
Cm

All power semiconductor devices function as SPST switches.

wire fully bipolar
semiconductor?


Buck converter

with SPDT switch:



same is simpler before make

with two SPST switches:

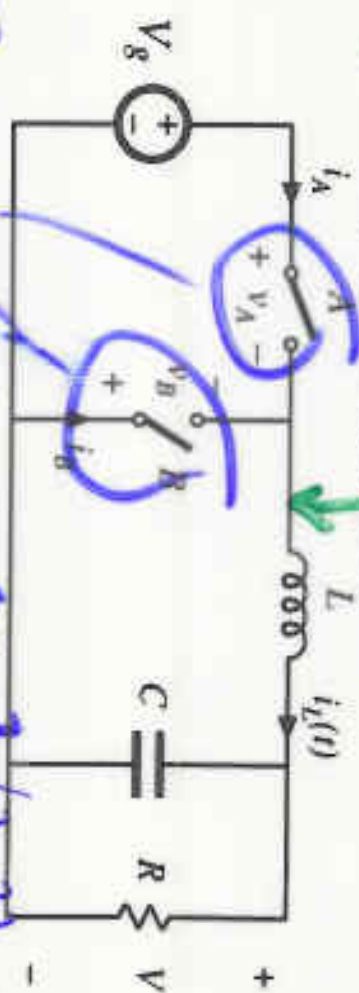

Two synchronized (both on?)
S.S. switches

Realization of SPDT switch using two SPST switches

- A nontrivial step: two SPST switches are not exactly equivalent to one SPDT switch
- It is possible for both SPST switches to be simultaneously ON or OFF
- Behavior of converter is then significantly modified
 - discontinuous conduction modes (chapter 5)
- Conducting state of SPST switch may depend on applied voltage or current — for example: diode

Converter



Realization of SPDT switch using two SPST switches

Limited $V-I$ quadrants causes

- A nontrivial step: two SPST switches are not exactly equivalent to one SPDT switch
- It is possible for both SPST switches to be simultaneously ON or OFF
- Behavior of converter is then significantly modified
—discontinuous conduction modes (ch. 5)
- Conducting state of SPST switch may depend on applied voltage or current—for example: diode

Sw. drive
synch
cause
 $I_n = 0$

"Break before make"
requires a deadtime interval, Δt
with both off

OR ?

4.1.1. Single-quadrant switches



Active switch: Switch state is controlled exclusively by a third terminal (control terminal).

Passive switch: Switch state is controlled by the applied current and/or voltage at terminals 1 and 2.

SCR: A special case — turn-on transition is active, while turn-off transition is passive.

Single-quadrant switch: on-state $i(t)$ and off-state $v(t)$ are unipolar.

i zero crossing $\rightarrow 0$

4.1.1. Single-quadrant switches



Active switch: Switch state is controlled exclusively by a third terminal (control terminal).

Passive switch: Switch state is controlled by the applied current and/or voltage at terminals 1 and 2


SCR: A special case — turn-on transition is active, while turn-off transition is passive.

Single-quadrant switch: on-state $i(t)$ and off-state $v(t)$ are unipolar.

FET
Bipolar
ON Thyristor
Diode
off thyristor

When Thyristor off?

The diode

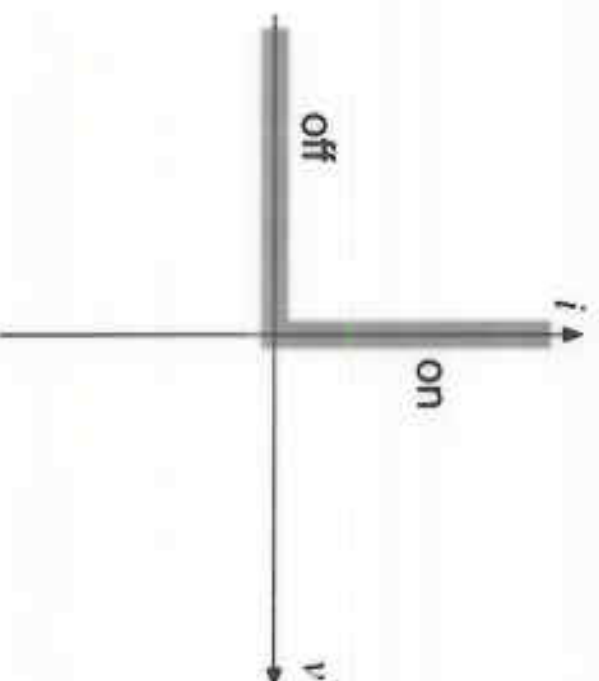


Symbol

instantaneous i - v characteristic

- A passive switch
- Single-quadrant switch:
- can conduct positive on-state current
- can block negative off-state voltage
- provided that the intended on-state and off-state operating points lie on the diode i - v characteristic, then switch can be realized using a diode

Figure 4.4 p 65

The diode



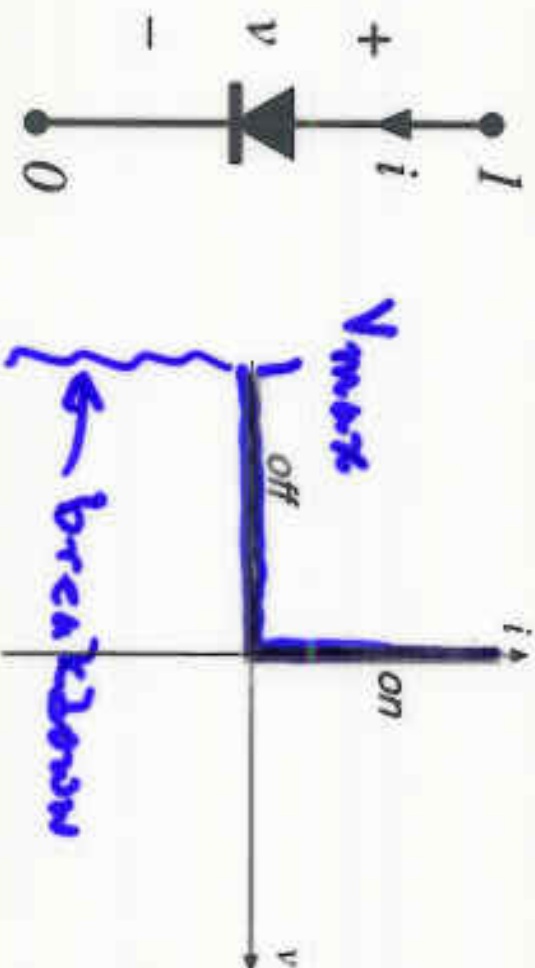


Symbol

instantaneous i - v characteristic

- A passive switch
- Single-quadrant switch:
- can conduct positive on-state current
- can block negative off-state voltage
- provided that the intended on-state and off-state operating points lie on the diode i - v characteristic, then switch can be realized using a diode

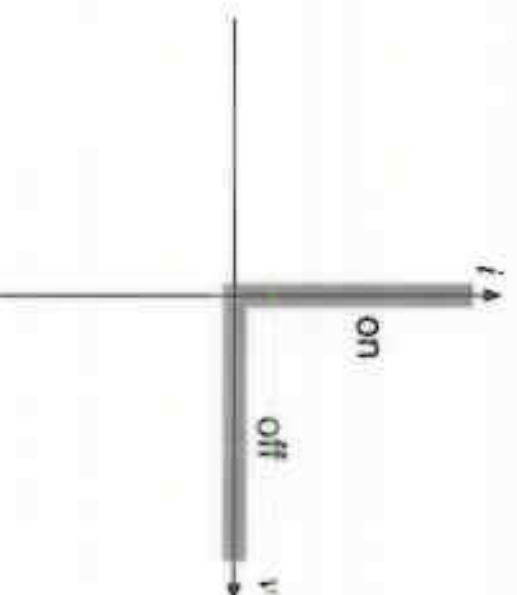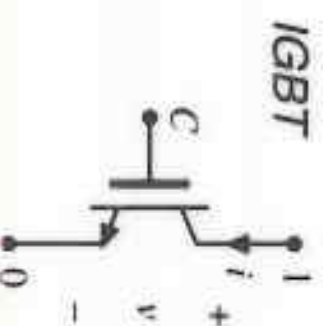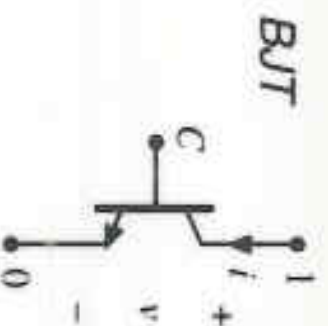The Bipolar Junction Transistor (BJT) and the Insulated Gate Bipolar Transistor (IGBT)



instantaneous i-v characteristic


- An active switch, controlled by terminal C
- Single-quadrant switch:
- can conduct positive on-state current
- can block positive off-state voltage
- provided that the intended on-state and off-state operating points lie on the transistor i-v characteristic, then switch can be realized using a BJT or IGBT

The Bipolar Junction Transistor (BJT) and the Insulated Gate Bipolar Transistor (IGBT)



Nonbipolar) very low 0.2V "tailed"

it) for is 10ns tailed

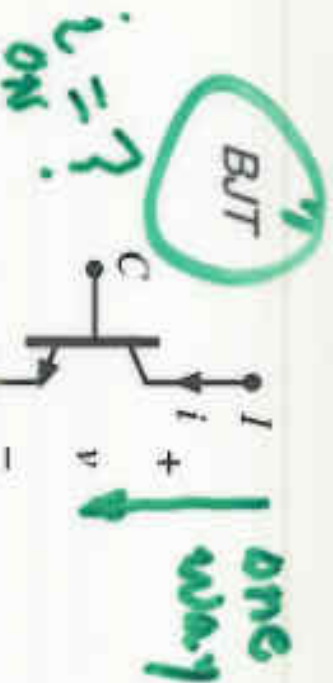- An active switch, controlled by terminal C



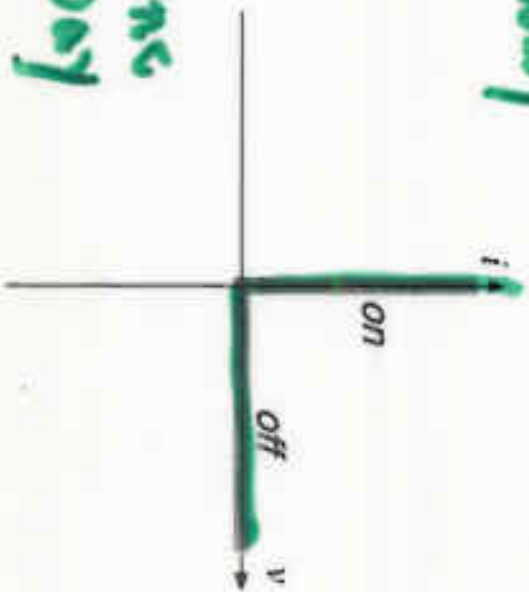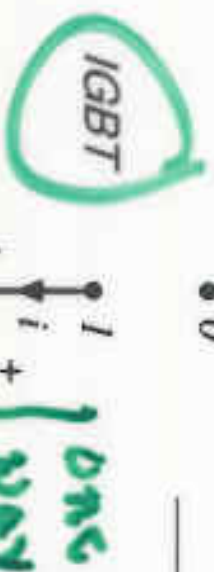- Single-quadrant switch: I_{max}
- can conduct positive on-state current



- can block positive off-state voltage V_{max}

- provided that the intended on-state and off-state operating points lie on the transistor i-v characteristic,

then switch can be realized using a BJT or IGBT

any problem is) 23




instantaneous i-v characteristic



The Metal-Oxide Semiconductor Field Effect Transistor (MOSFET)

~~Exam~~
Yes Polarities

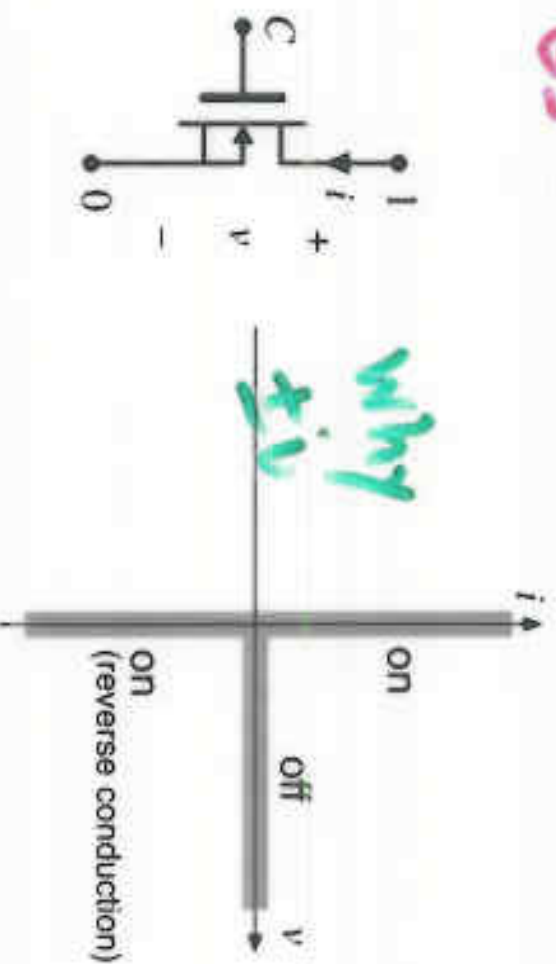


Symbol instantaneous i - v characteristic

- An active switch, controlled by terminal C
- Normally operated as single-quadrant switch:
- can conduct positive on-state current (can also conduct negative current in some circumstances)
- can block positive off-state voltage
- provided that the intended on-state and off-state operating points lie on the MOSFET i - v characteristic, then switch can be realized using a MOSFET

Figure 4.10 pg 28

The Metal-Oxide Semiconductor Field Effect

Transistor (MOSFET)

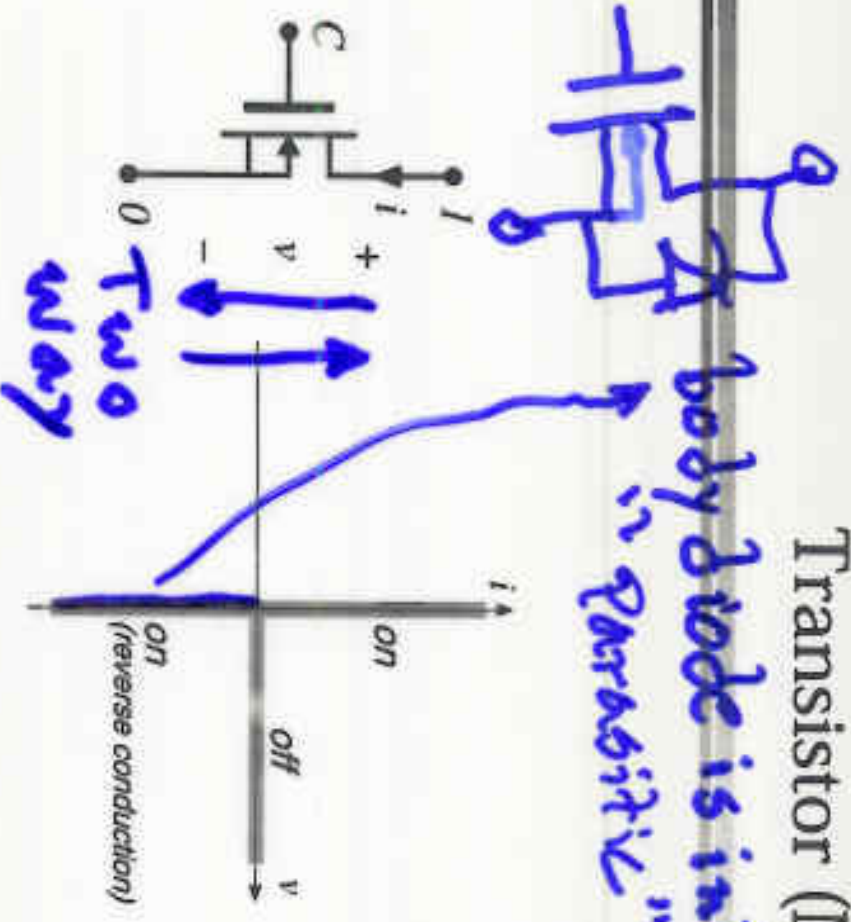

- An active switch, controlled by terminal C
- Normally operated as single-quadrant switch:
- can conduct positive on-state current (can also conduct negative current in some circumstances)
- can block positive off-state voltage

- provided that the intended on-state and off-state operating points lie on the MOSFET $i-v$ characteristic, then switch can be realized using a MOSFET

Symbol instantaneous $i-v$ characteristic

