

Figs 4.38
4.39

pg 287

The IGBT




Symbol

NO S.S.
V_{ON} needed
to keep SW
ON




Equivalent
circuit

low
V_{ON}
of
bipolar

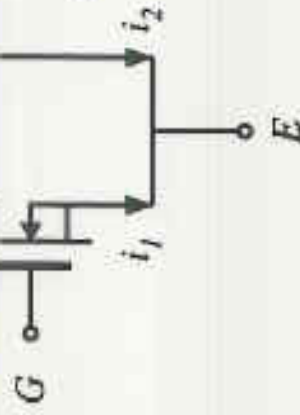

new in place is
6000 V IGBT
for power system
BVC

Location of equivalent devices

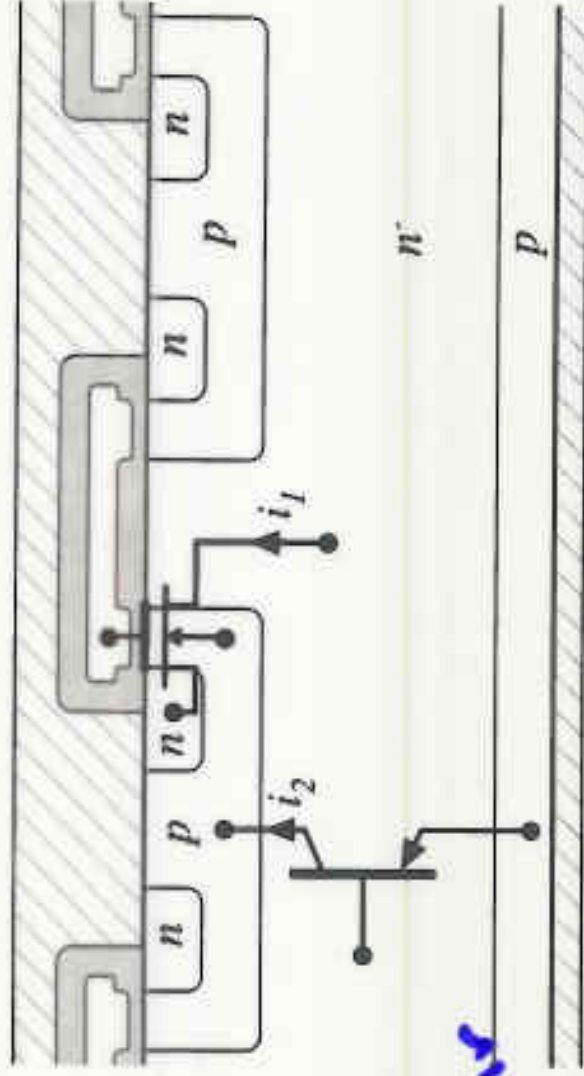

Conclusions: IGBT

Wide use

12V
Motors
low cost
sw
Von

- Becoming the device of choice in 500-1700V applications, at power levels of 1-1000kW
- Positive temperature coefficient at high current —easy to parallel and construct modules
- Forward voltage drop: diode in series with on-resistance. 2-4V
- Easy to drive —similar to MOSFET
- Slower than MOSFET, but faster than Darlington, GTO, SCR
- Typical switching frequencies: 3-30kHz
- IGBT technology is rapidly advancing —next generation: 2500V —

10kV
12kV
power system



6000V!

ON to off Transition R load

$$\left[\frac{1}{6} V_{off} I_{on} \right] = P_{loss}$$

$$P_{loss} \cdot \Delta t = W_{loss}$$

Fig 3a: Ideal Voltage and Current Waveforms with Resistive Loading } other

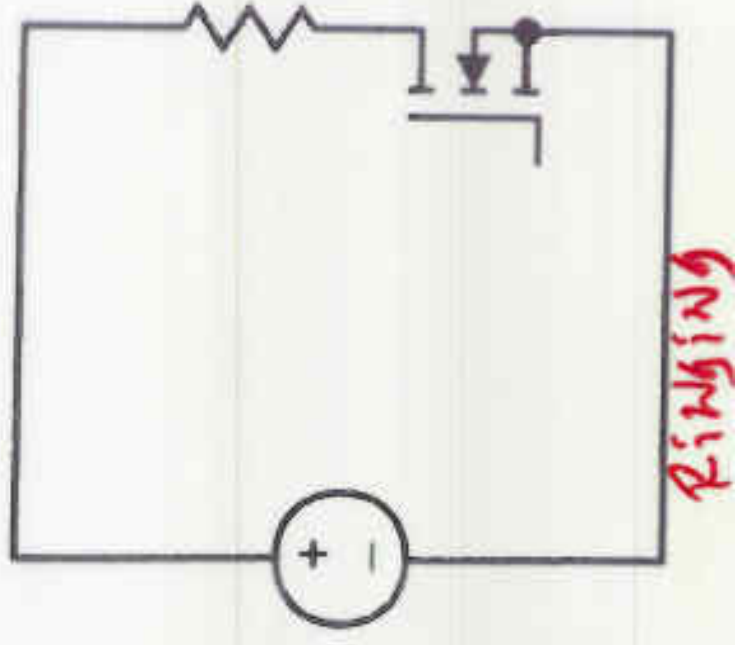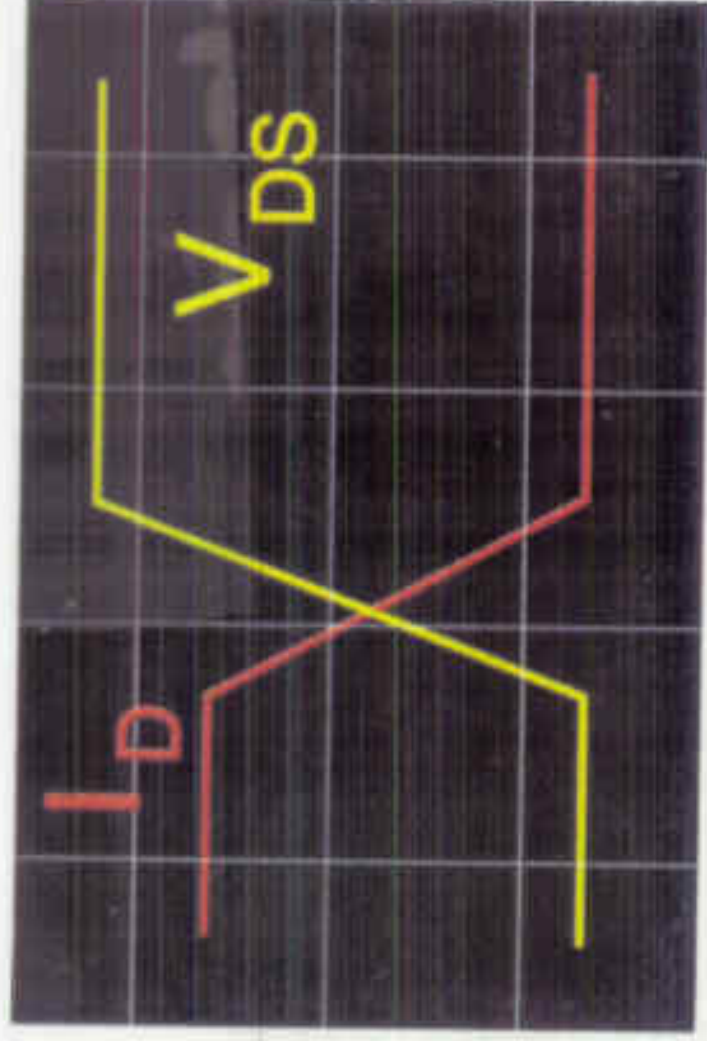



ON to off transition "L" load

$$P_{loss} = \frac{1}{2} V_{off} I_{on}$$

$$W_{loss} = P_{loss} \times \Delta t$$

Brithley assumes I_L hangs till $V_{DS} \rightarrow \text{Max}$

Fig 3b: Ideal Voltage and Current Waveforms with Inductive Loading

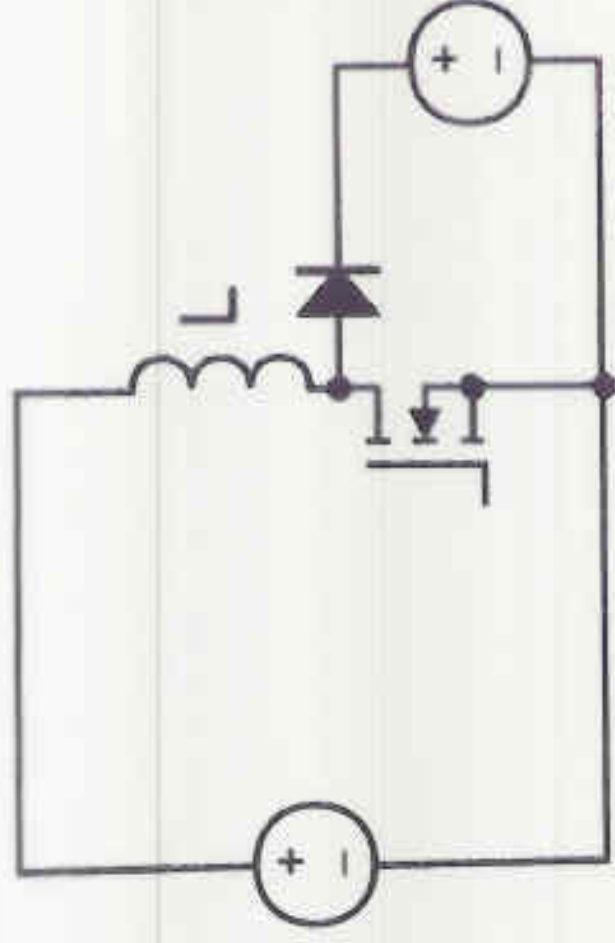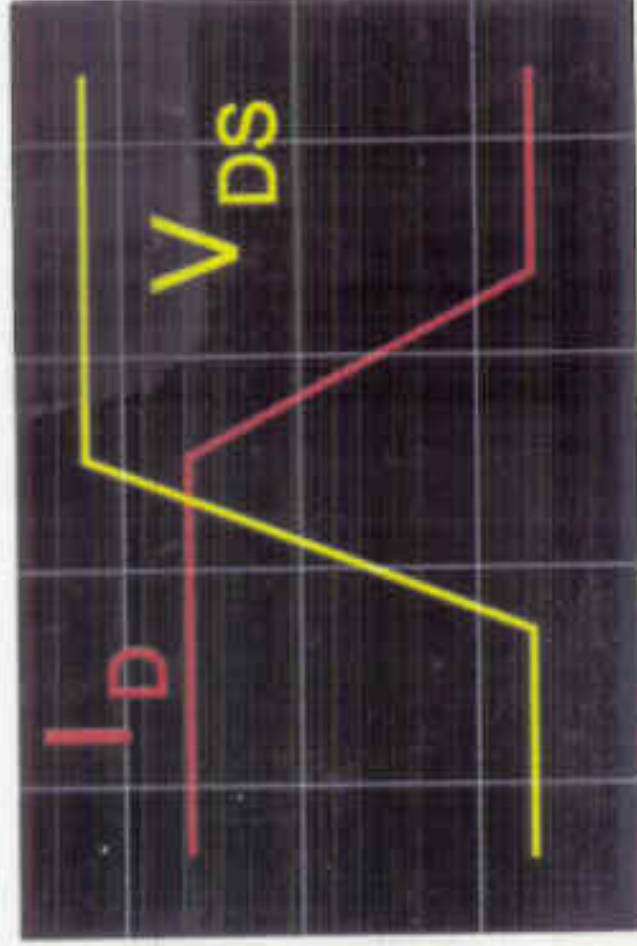


new

Current tailing in IGBTs


The V_{CE} has a tail - a long one

sw loss
 $I_{ON} V_{CE, off}$

too long
high loss

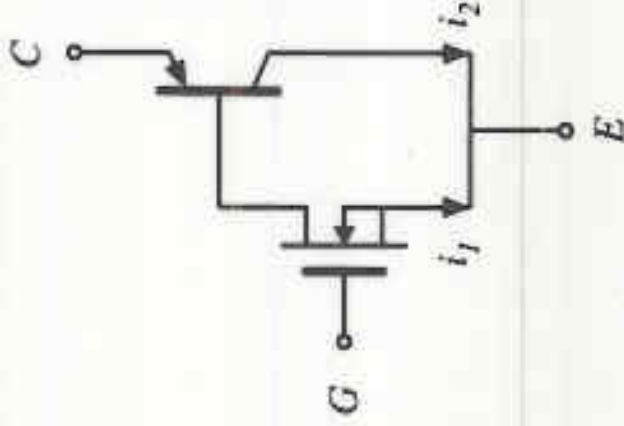


Wow
 I_{ON}
of
1-2 V A
 V_{ON} 2-3V

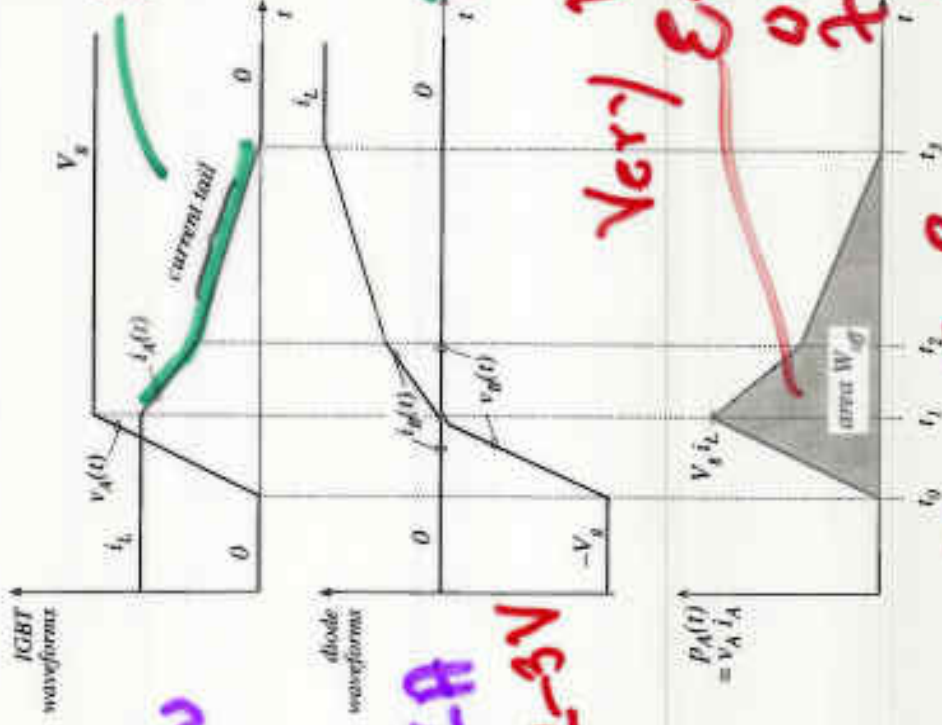

Very High Energy per ON-off transition due to long

$$P = E_{on} f_{sw} + E_{off}$$

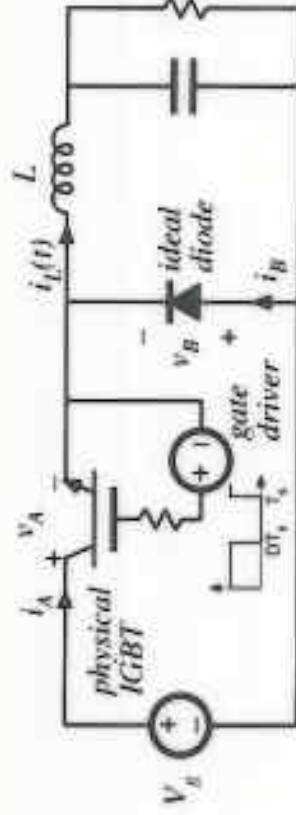Switching loss due to current-tailing in IGBT




Example: buck converter with IGBT

f_{sw} each cycle

transistor turn-off transition

$$P_{sw} = \frac{1}{T} \int p_A(t) dt = (W_{on} + W_{off}) f_s$$

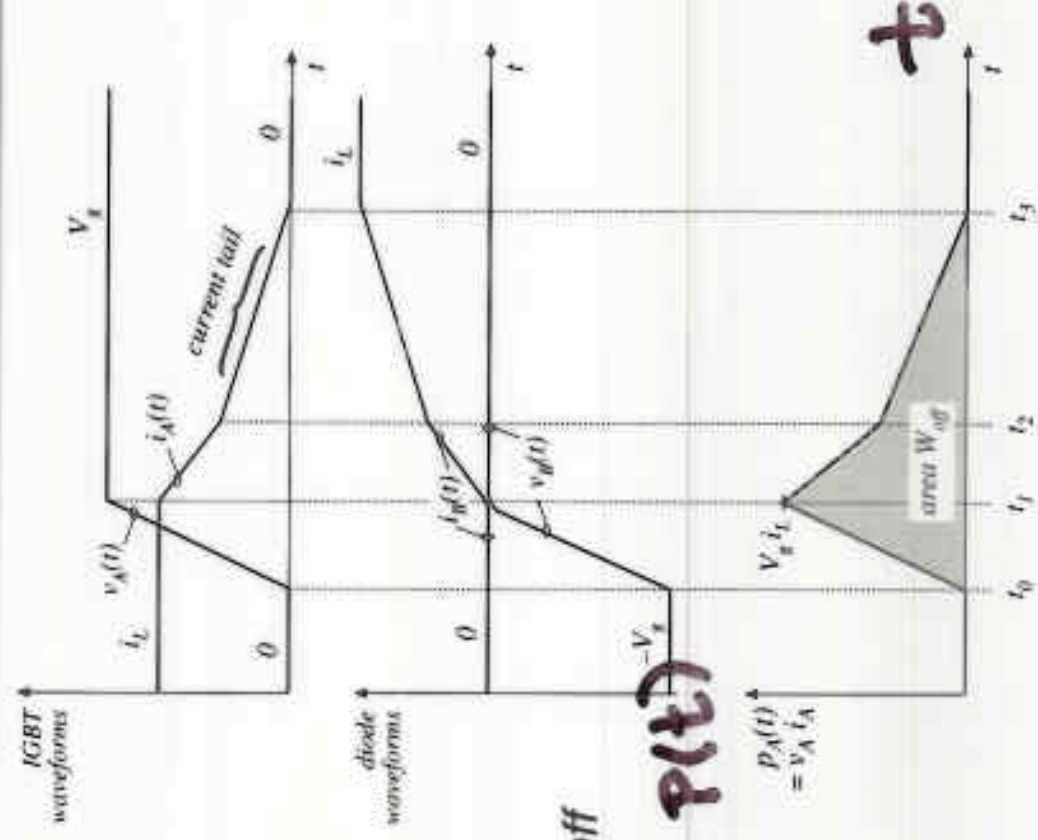


Problem 4.7

Multiply $v_{CE}(t) i_c(t) = p(t)$

Estimate energy under $p(t)$ waveform by graphical integration

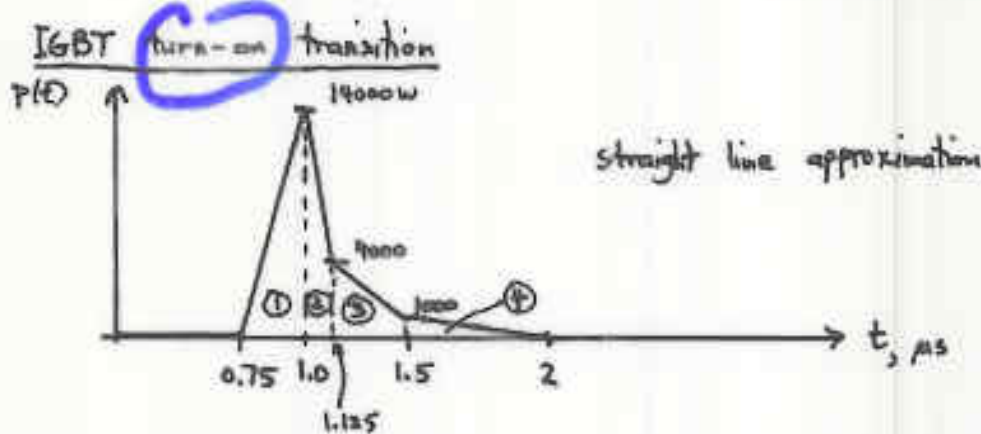Modern Scope $\rightarrow E_{total}$ for transition



Sum areas ① - ④:


$$\textcircled{1} \quad \frac{1}{2} (14000) (0.25 \cdot 10^{-6}) = 1.75 \text{ mJ}$$

$$\textcircled{2} \quad \frac{1}{2} (14000 + 4000) (0.125 \cdot 10^{-6}) = 1.125 \text{ mJ}$$

$$\textcircled{3} \quad \frac{1}{2} (4000 + 1000) (0.375 \cdot 10^{-6}) = 0.9375 \text{ mJ}$$

$$\textcircled{4} \quad \frac{1}{2} (1000) (0.5 \cdot 10^{-6}) = 0.25 \text{ mJ}$$
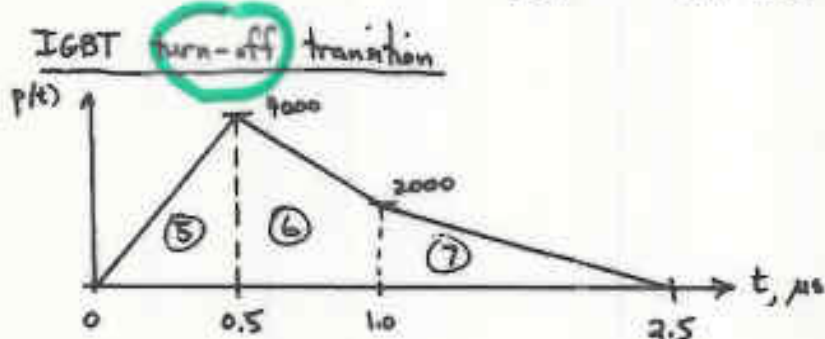
$$\text{total} \quad 4.1 \text{ mJ} = E_{on}$$



$$\textcircled{5} \quad \frac{1}{2} (4000) (0.5 \mu s) = 1.0 \text{ mJ}$$

$$\textcircled{6} \quad \frac{1}{2} (4000 + 2000) (0.5 \mu s) = 1.5 \text{ mJ}$$

$$\textcircled{7} \quad \frac{1}{2} (2000) (1.5 \mu s) = 1.5 \text{ mJ}$$

$$\text{total} \quad 4.0 \text{ mJ} = E_{off}$$

each cycle at f_{sw}

Total $E_{on} + E_{off}$


$$E_{sw} = 8.1 \text{ mJ}$$

(any estimate near this value is OK)

Diol: DC losses Buck are f1D)

b) IGBT

Buck converter model: conduction loss

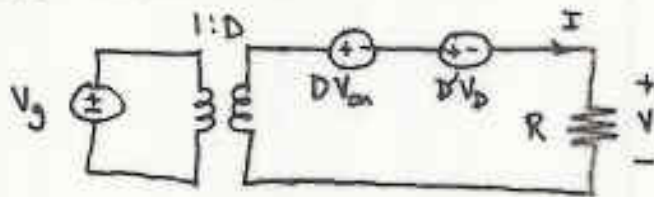

$$V_g = 400 \text{ V}$$

$$V = 200 \text{ V}$$

$$I = 10 \text{ A}$$

$$R = 20 \Omega$$

$$V_{on} = 2.5 \text{ V}$$

$$V_d = 1.5 \text{ V}$$

$$V = DV_g - DV_{on} - D'V_d$$

$$\Rightarrow V + V_d = D(V_g - V_{on} + V_d)$$

$$\text{so } D = \frac{V + V_d}{V_g - V_{on} + V_d} = 0.505$$

Element

power loss

IGBT

$$IDV_{on} = 12.6 \text{ W}$$

diode

$$ID'V_d = 7.4 \text{ W}$$

$$\text{total } 20 \text{ W} = P_{cond}$$

DC loss both switches

$$c) \text{ converter efficiency} = \frac{P_{out}}{P_{in}} \quad \text{with } P_{out} = (200 \text{ V})(10 \text{ A}) = 2 \text{ kW}$$


$$P_{in} = P_{out} + P_{loss} = P_{out} + P_{cond} + E_{sw}f_{sw}$$

$$\text{so } \eta = \frac{P_{out}}{P_{out} + P_{cond} + E_{sw}f_{sw}} = \frac{2000}{2000 + 20 + (8.1 \cdot 10^{-3})f_{sw}}$$

Plot on next page

$$\text{From Eq. (4.23): } f_{crit} = \frac{20 \text{ W}}{8.1 \text{ mJ}} = 2.5 \text{ kHz}$$

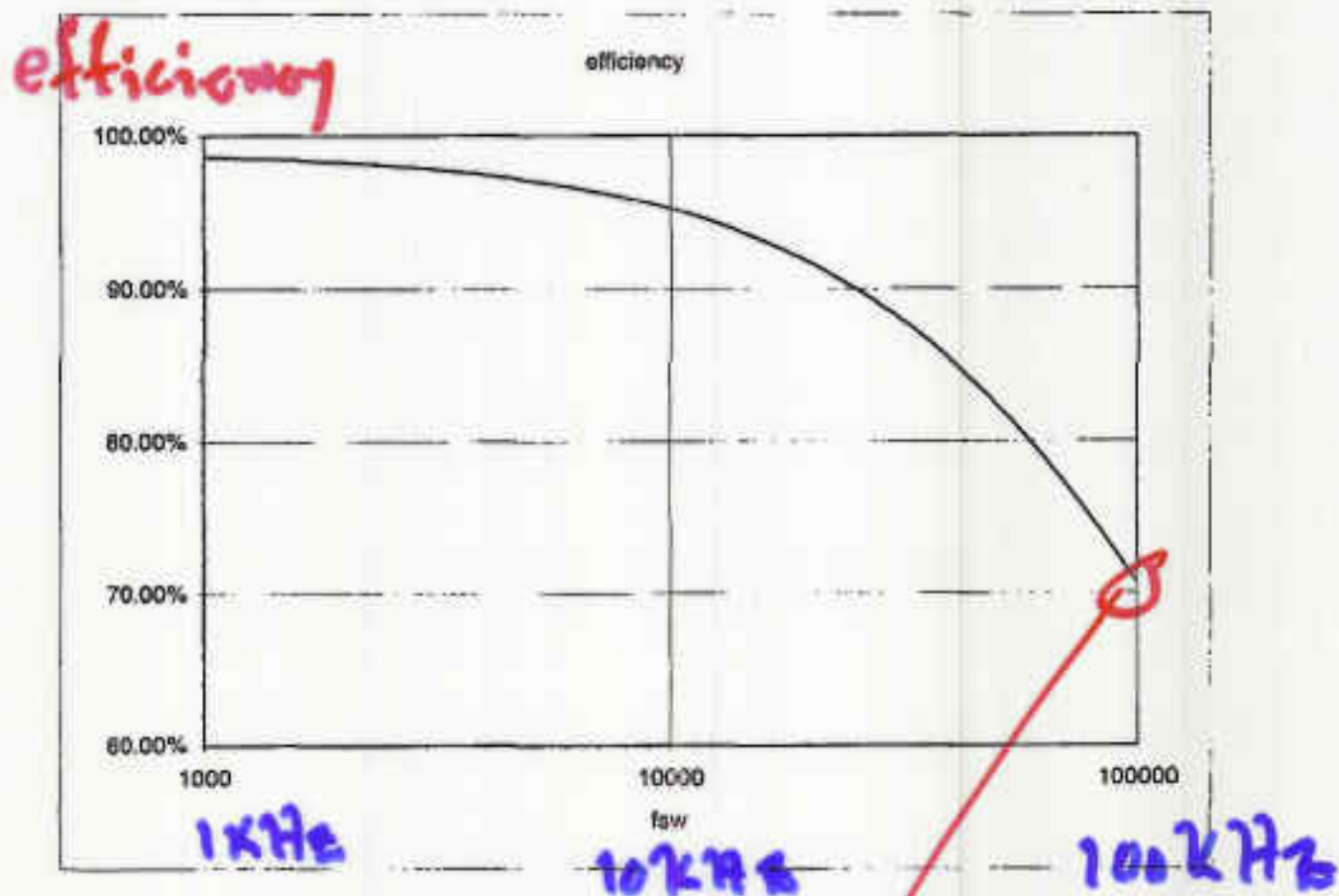Problem 4.7, part (c)
Efficiency vs. switching frequency



30% heat loss

Current tailing in IGBTs

Causes E_{sw} (off-on)

