
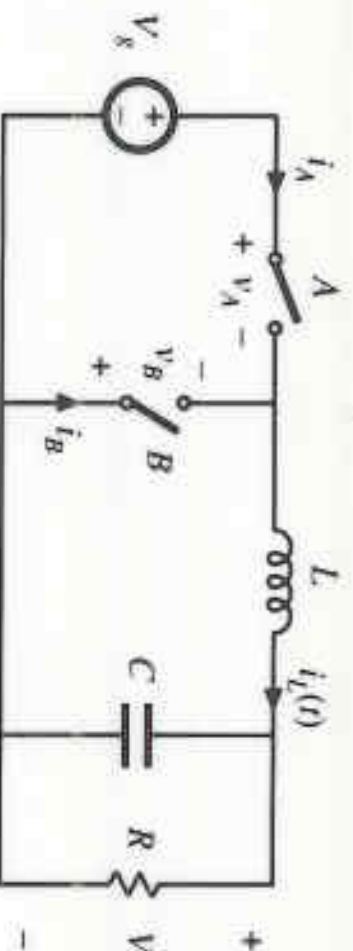


Realization of switch using transistors and diodes


Buck converter example

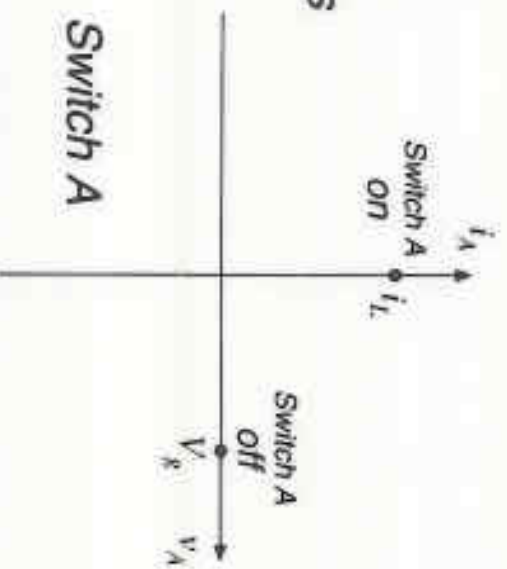

SPST switch
operating points



Switch A: transistor
Switch B: diode

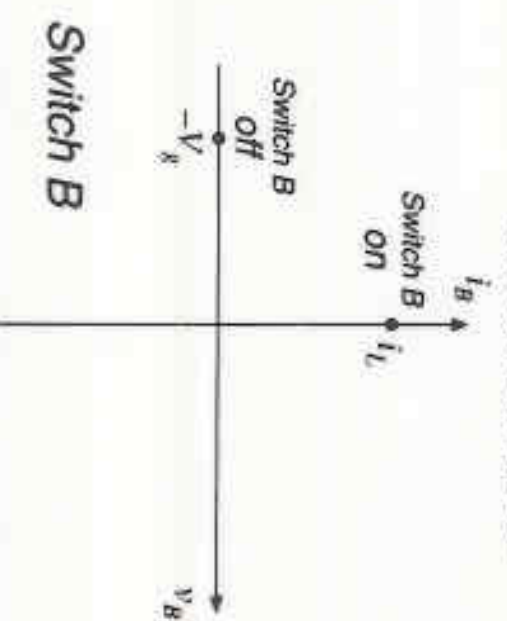

Realization of switch using


transistors and diodes

circuit driven


"gated" ↑

BST, IGBT, MOSFET, more;

Buck converter example

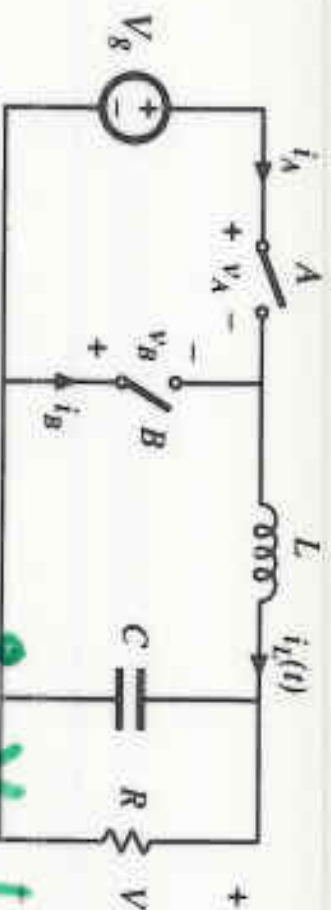

SPST switch
operating points

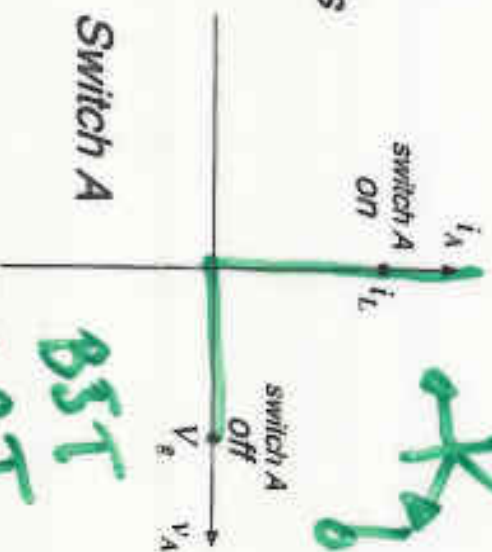


Switch A

BST

IGBT

Switch B

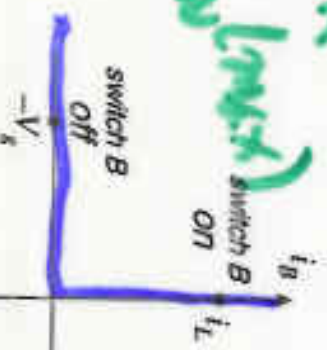

Switch A: transistor

Switch B: diode







Switching occurs naturally
No external control

Requires central driver
each device: different driver

Realization of buck converter using single-quadrant switches

When Flow
Shoot through

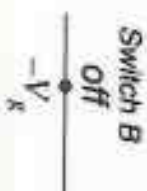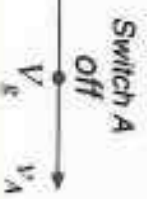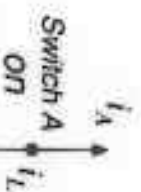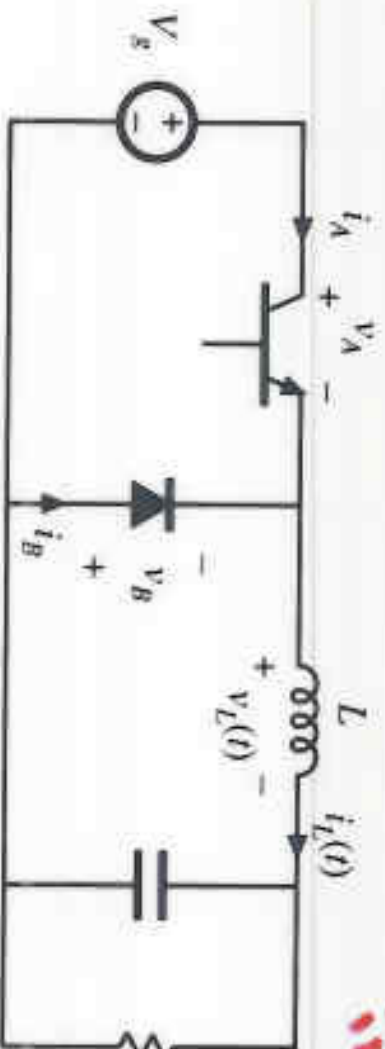

Realization of buck converter using single-quadrant switches


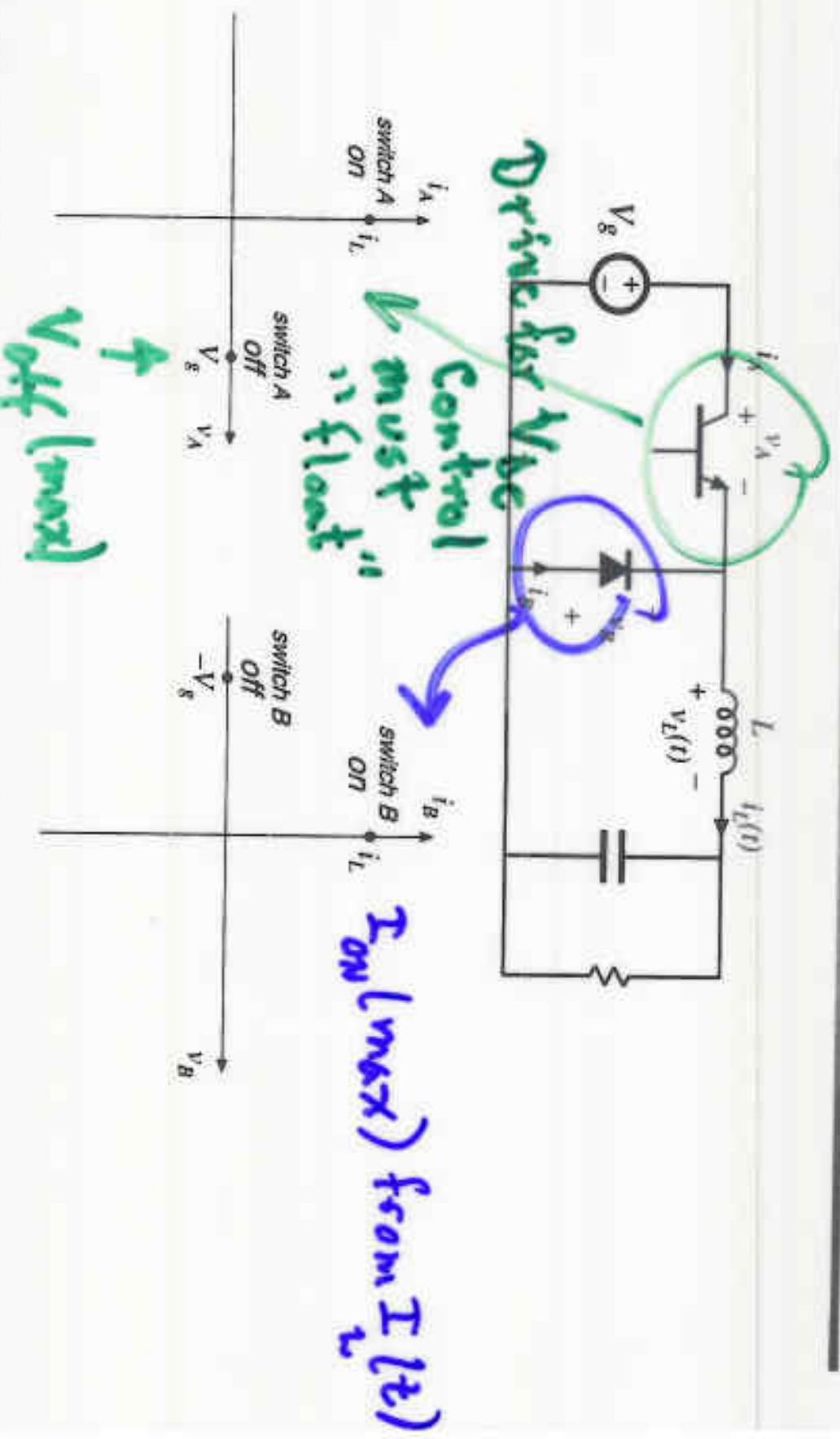



Fig 9.18 968

MOSFET body diode
For i_D flow parasitic diode


blocks internal diode use

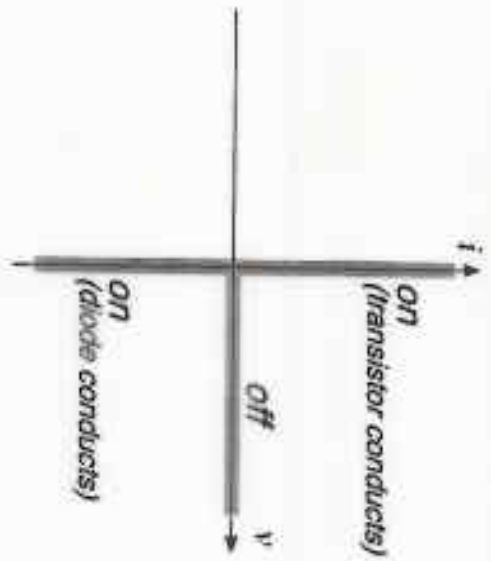

Power MOSFET characteristics

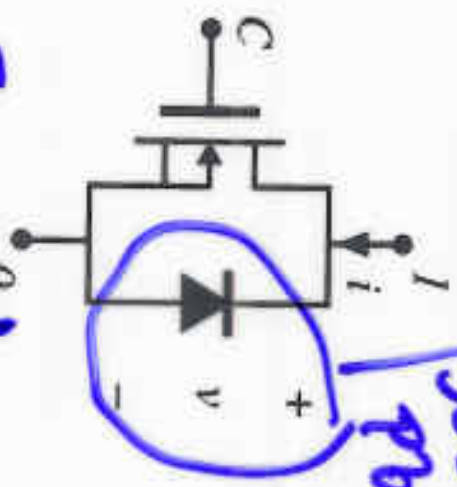

turn-off 300ns? pbsms?

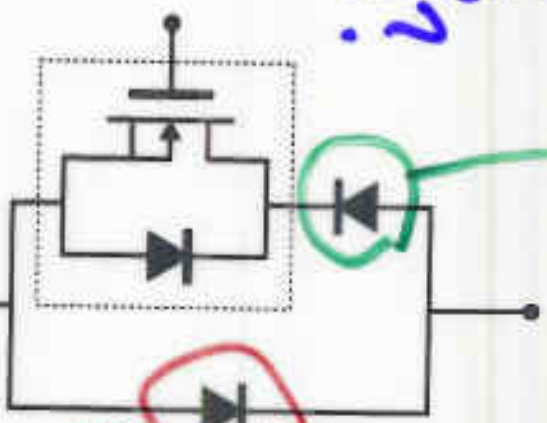

Turn-off first i_D ext. switchy 10ms

Forces i_D into FET drain

i_D flow very high $\Rightarrow$ loss

Power MOSFET, and its integral

Use of external diodes to prevent conduction of body diode

before $V_{GS} \rightarrow 0$

$\Rightarrow V_{GS} = V_{GS} i_D \Delta t_{off}$



Figure 4.9 P 68

4.1.2. Current-bidirectional

two-quadrant switches

$MOS \pm v$ or $5x$

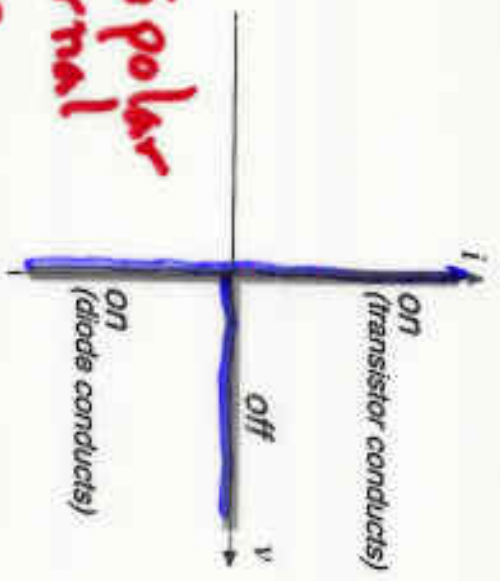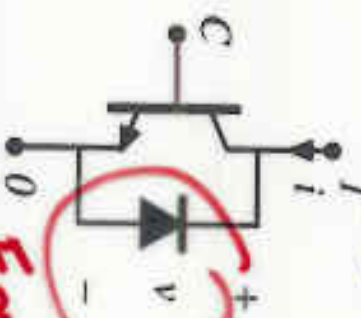G $\frac{1}{\mu F}$ ds body diode (internal) Control is Yes






BJT / anti-parallel diode realization

instantaneous $i-v$ characteristic

Bipolar External Diode added

- Usually an active switch, controlled by terminal C
- Normally operated as two-quadrant switch:
- can conduct positive or negative on-state current
- can block positive off-state voltage
- provided that the intended on-state and off-state operating points lie on the composite $i-v$ characteristic, then switch can be realized as shown

MOSFET body diode

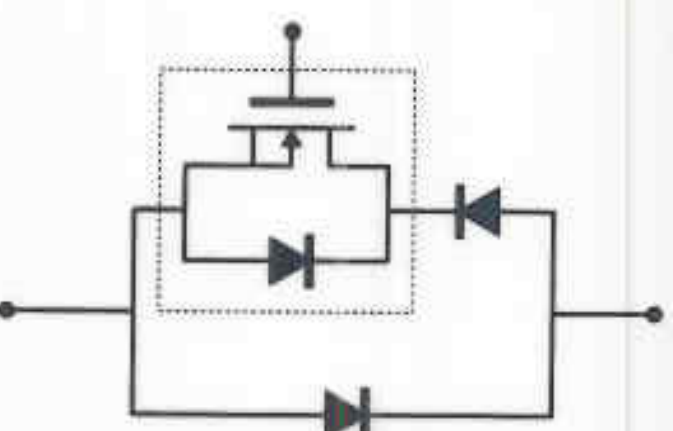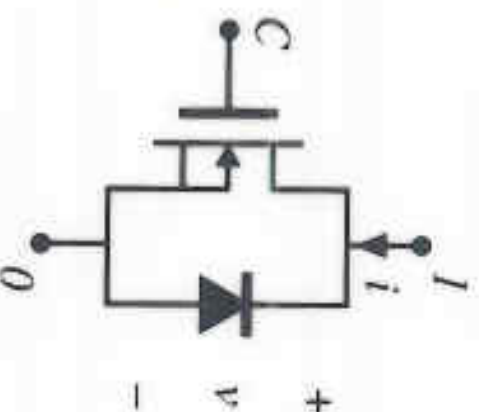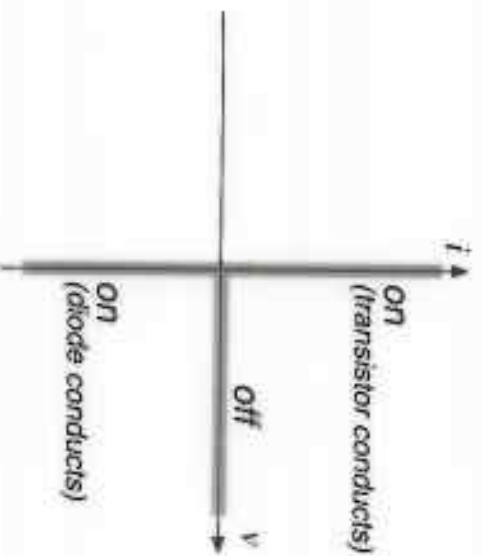

Power MOSFET characteristics

Power MOSFET, and its integral body diode

Use of external diodes to prevent conduction of body diode

Two quadrant switches



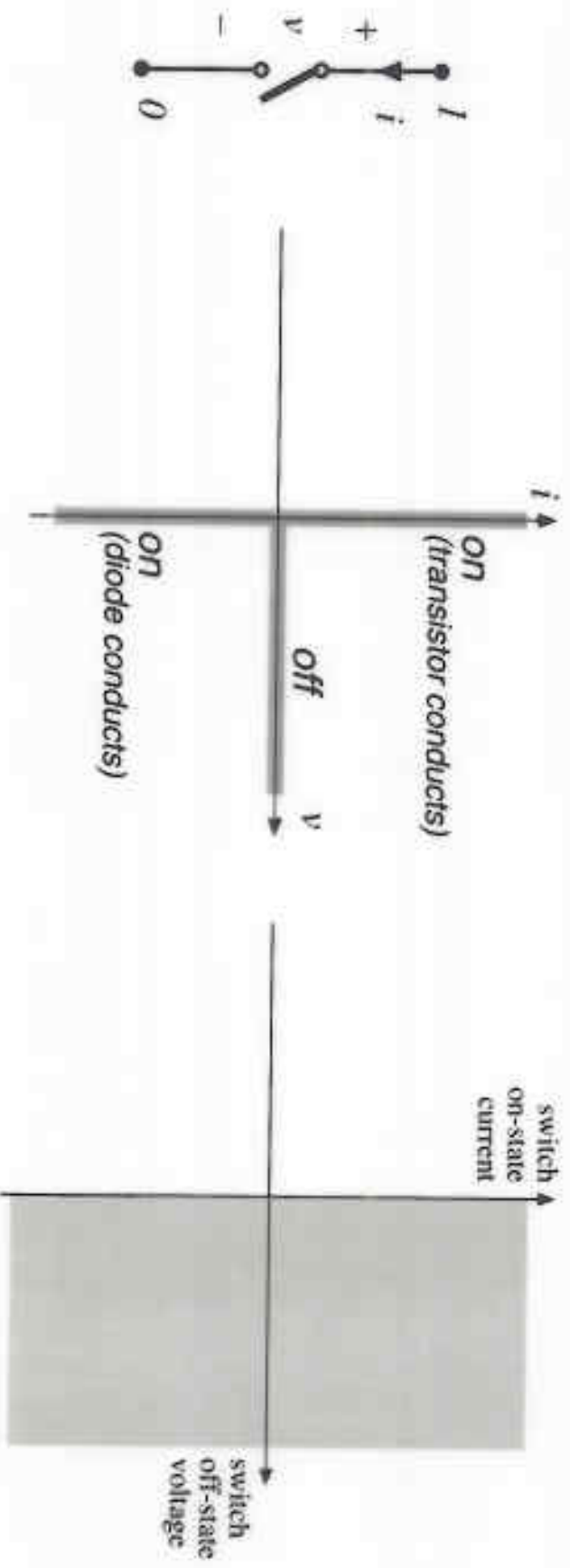
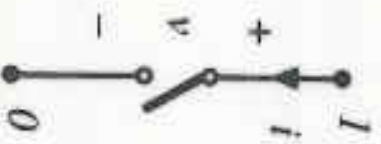
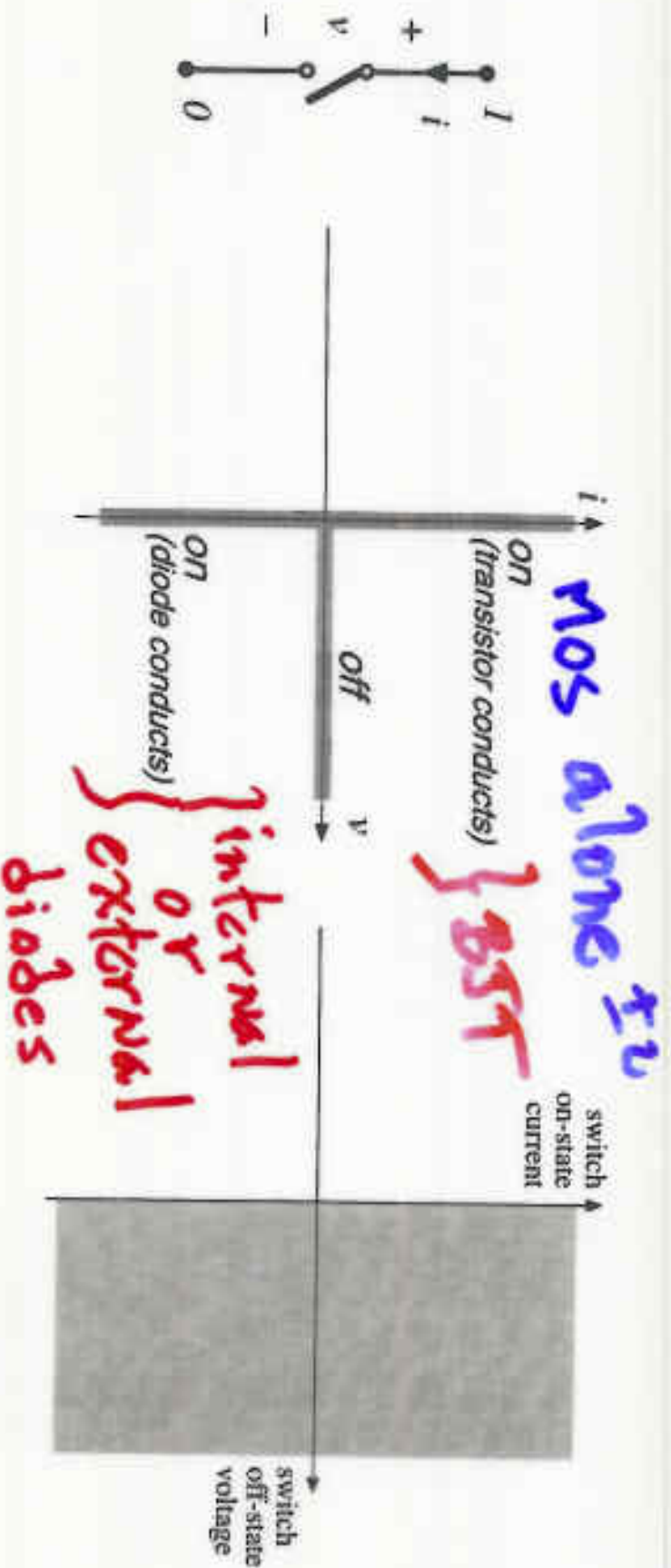


Fig 4.22 pg 73

Two quadrant switches

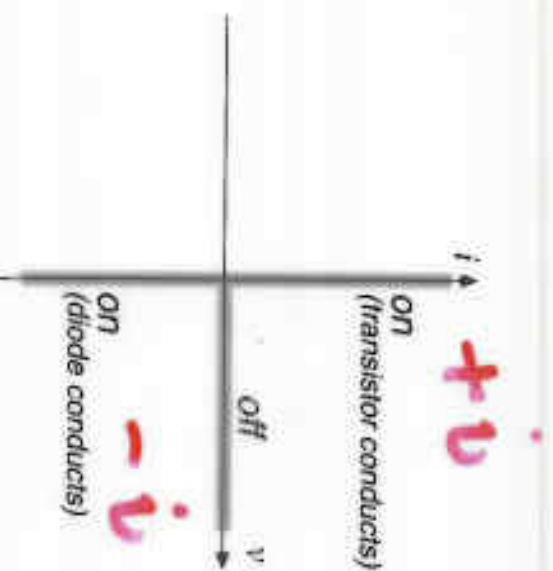

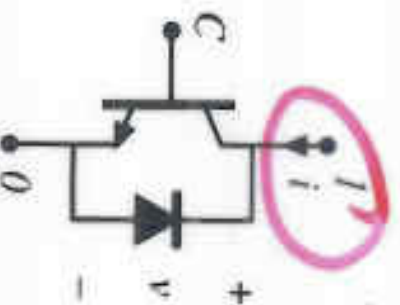4.1.2. Current-bidirectional two-quadrant switches




BJT / anti-parallel
diode realization

instantaneous i - v
characteristic

- Usually an active switch, controlled by terminal C
- Normally operated as two-quadrant switch:
- can conduct positive or negative on-state current
- can block positive off-state voltage
- provided that the intended on-state and off-state operating points lie on the composite i - v characteristic, then switch can be realized as shown

A simple inverter

DC $\rightarrow$?

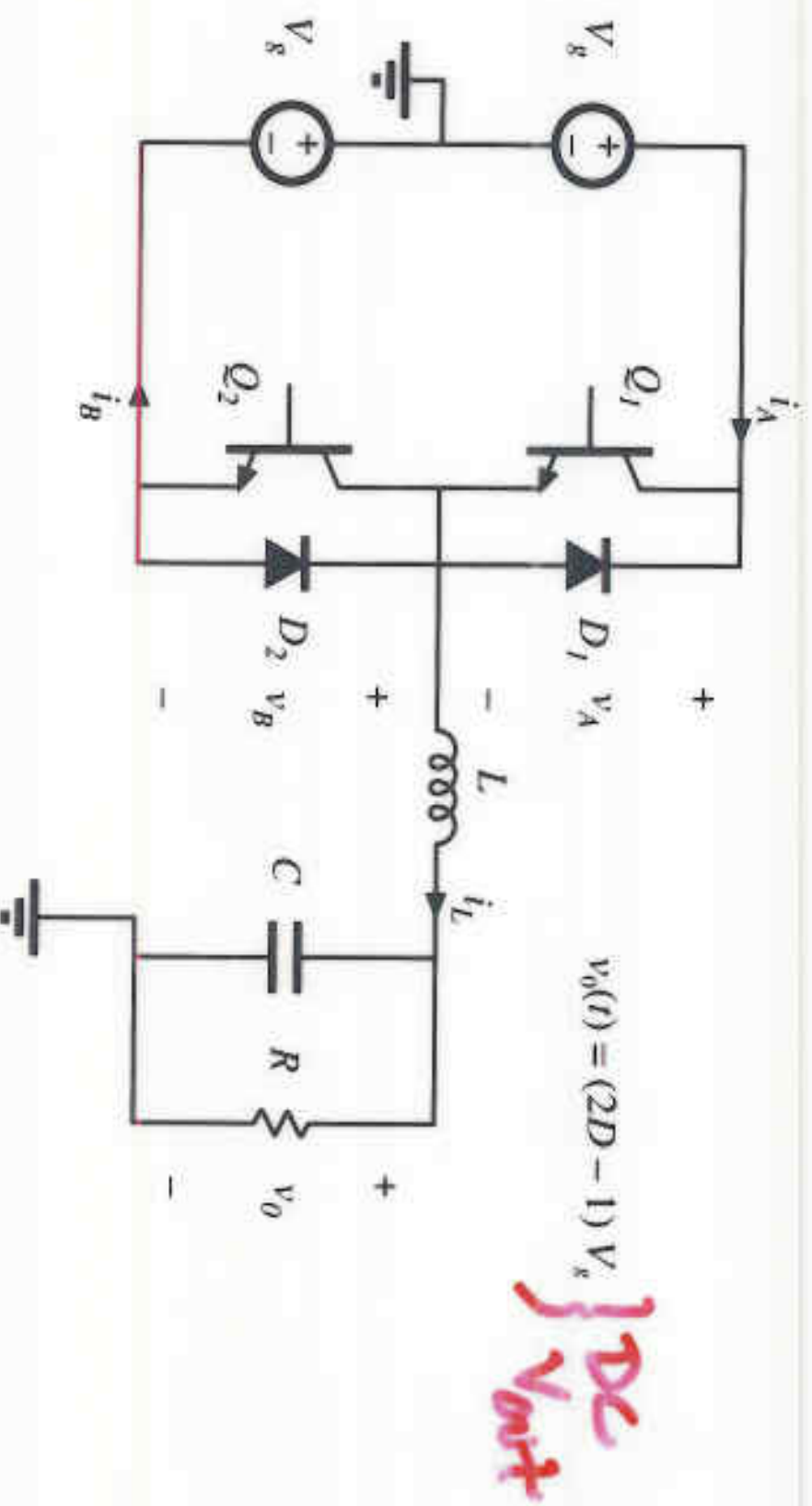

H₂O₁ Solar → AC or DC → AC (any frequency)

A simple inverter

Fig 4.11 Pg 69

External diodes

Why $\pm i$ required?

D_1 and D_2 can handle reverse "currents" before Q on


$$v_o(t) = (2D - 1) V_g$$

Symmetric drive on Q_1 & Q_2

$$D = \frac{1}{2} + D \sin \omega_s t$$

Key

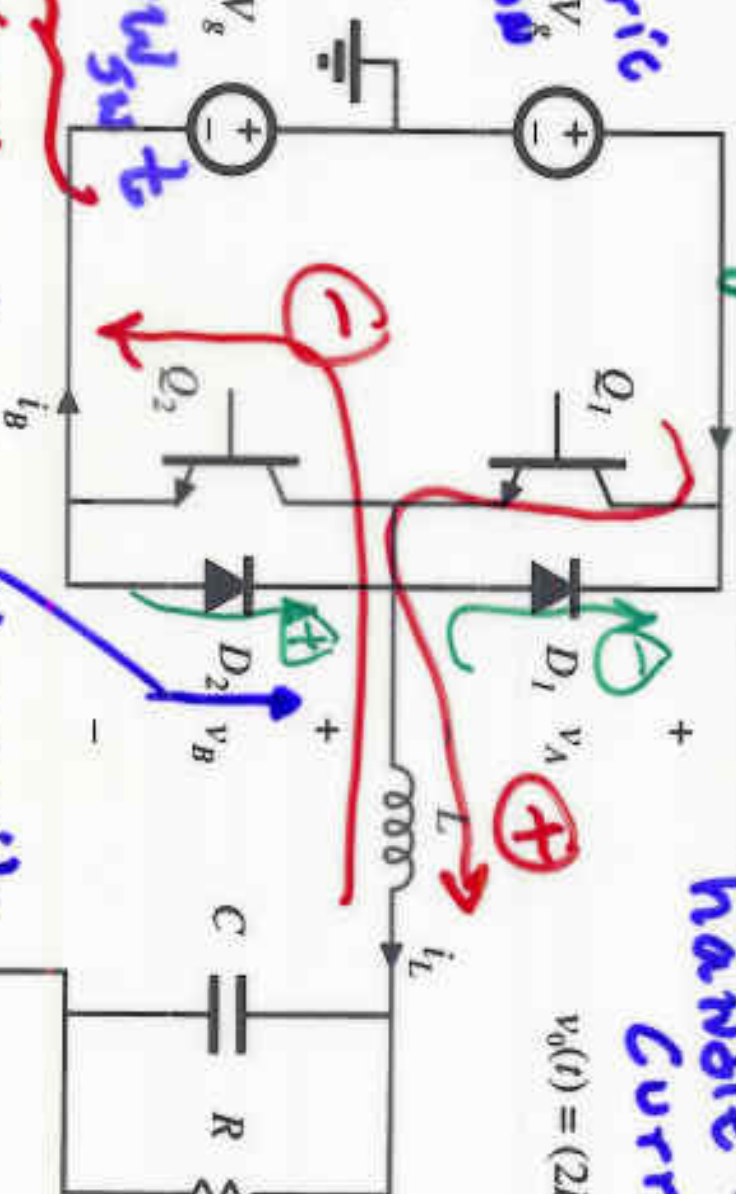
i_{D2} could provide i_{D1} before D_1 is on



DC level $(2D-1)V_g$

Inverter: sinusoidal modulation of D

$$V_o(t) = (2D - 1) V_g$$

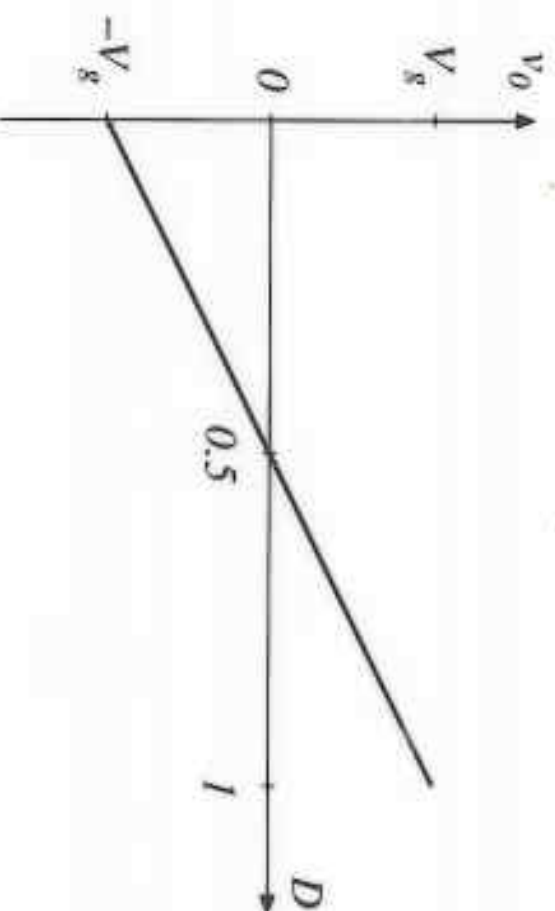

Sinusoidal modulation to produce ac output:

$m = 1$

$$D(t) = 0.5 + D_m \sin(\omega t)$$

The resulting inductor current variation is also sinusoidal:

$$i_L(t) = \frac{V_o(t)}{R} = (2D - 1) \frac{V_g}{R}$$

Hence, current-bidirectional two-quadrant switches are required.


(key +ve)
inverter!

2.4 2.6

Fig 9.12 Pg 69

Inverter: sinusoidal modulation of D

$$v_o(t) = (2D - 1) V_g$$

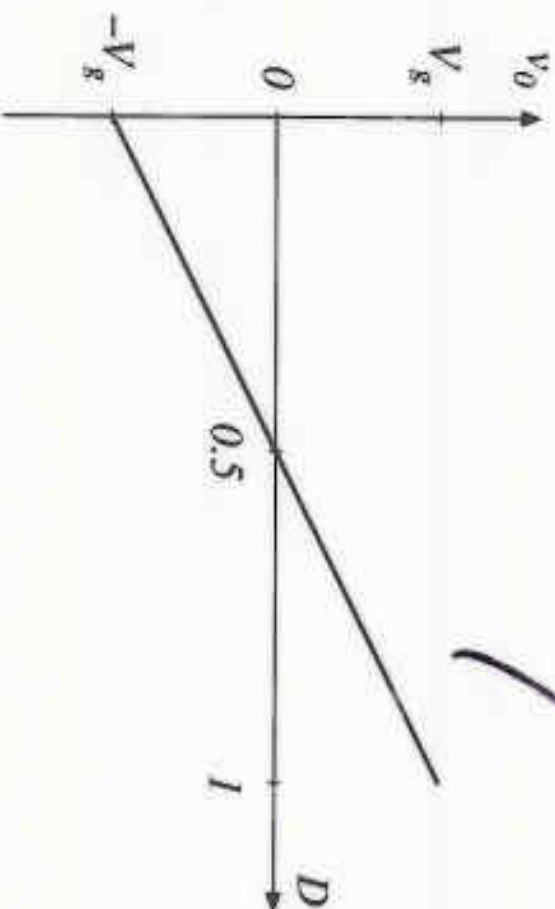

Recognize
Pg 69 Ch 2

Sinusoidal modulation to produce ac output:


$$D(t) = 0.5 + D_m \sin(\omega t)$$

The resulting inductor current variation is also sinusoidal:

$$i_L(t) = \frac{v_o(t)}{R} = (2D - 1) \frac{V_g}{R}$$

Hence, current-bidirectional two-quadrant switches are required.

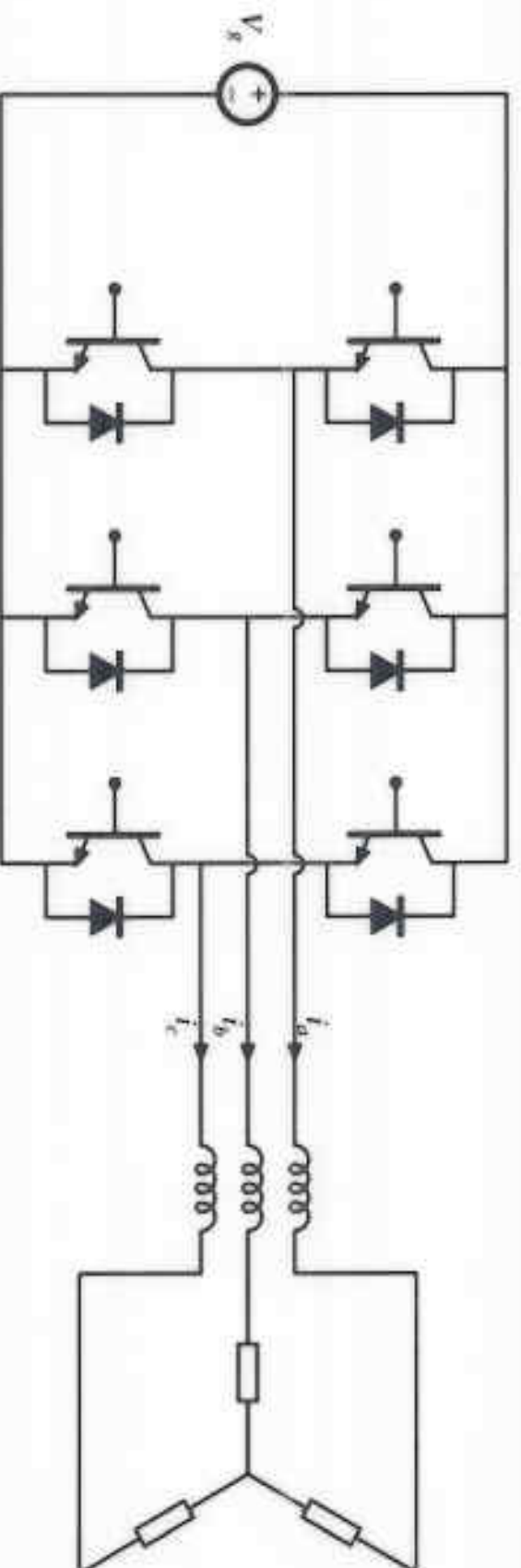The dc-3 ϕ ac voltage source inverter (VSI)



Switches must block dc input voltage, and conduct ac load current.