
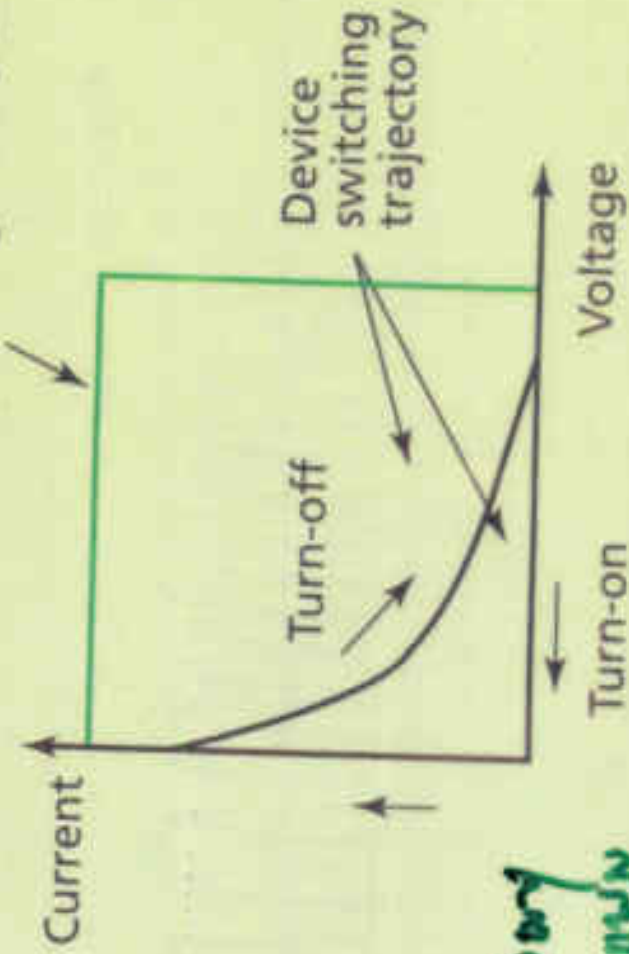
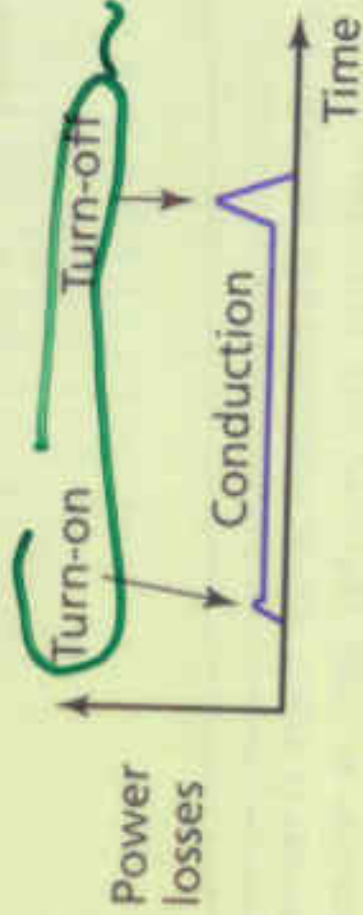


EE 564 Soft Switching

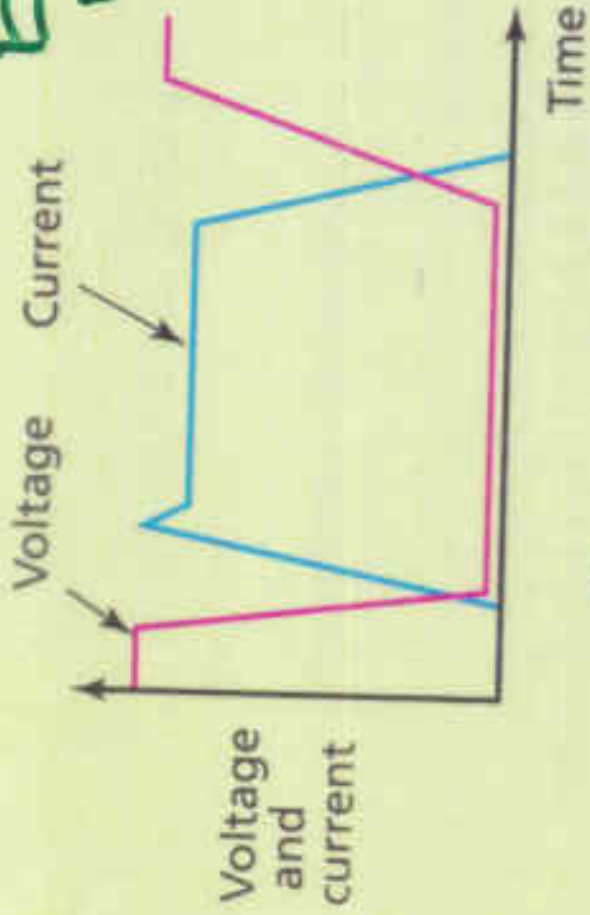V_{CE} body diodes, control gate timing
Safe operating area (SOA)



V_{CE} body diode


Soft switching

- Zero voltage across the device at both turn-on and turn-off keeps switching losses low.
- Neither diode recovery nor device capacitance causes undesirable effects during operation.
- Switching trajectory is well within the safe operating area.
- Electromagnetic interference is low because switching speeds approach at most 0.1–0.5 GV/s.
- Operation at high frequency is made possible by the low losses.

A hard look at hard and soft switching

Ch 4

which type?

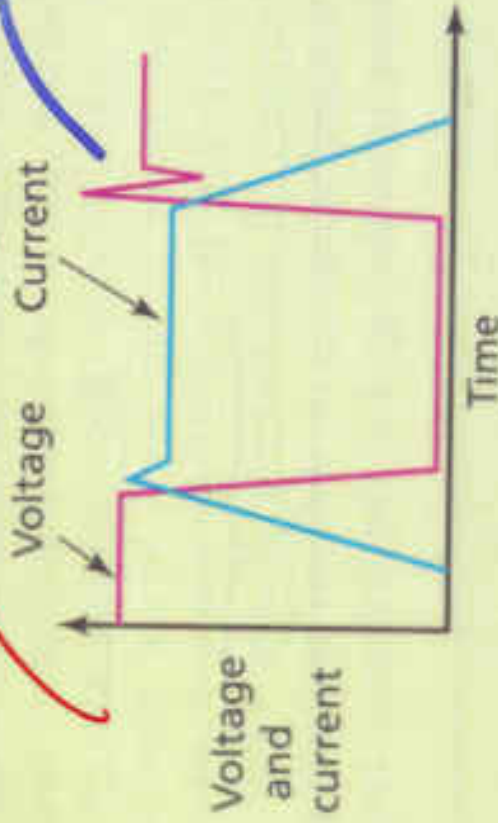

Voltage

Current


Time

Safe operating area (SOA)

Switch

Current


Device switching trajectory

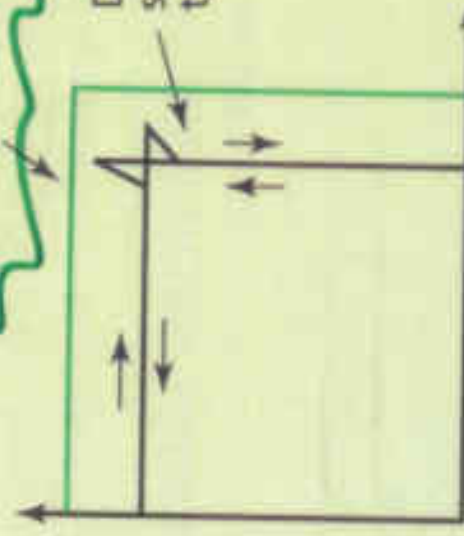

Power losses

Turn-on

Turn-off

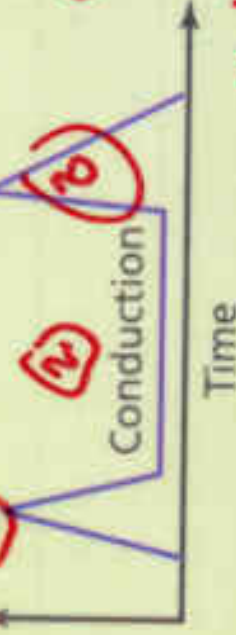

Hard switching

- Device carries a full load current and sustains full voltage at both turn-on and turn-off.
- Diode recovery effects and stray inductance increase stresses and device losses.
- Switching trajectory must be within the safe operating area.
- Electromagnetic interference is high because switching speeds are high, approaching 5-10 GV/s.
- Operation at high frequencies requires derating of the device to curb switching losses.

SOA curves


① ② ③ dominate f_{sw}?
562 - any cure?
① ② ③ High limits what?

Time 1/2 Volt I_{rr}

f_{max} limit

"ON" goes to "off"

$L(\text{stray})$

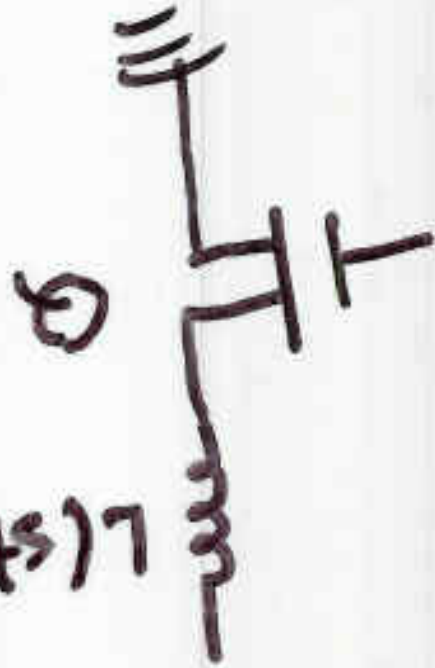

$\frac{dV_G}{dt}$ is -

V_G spikes



Causes Avalanche!

Solution:
 Slow $\frac{dV}{dt}$,
 Reduce $\frac{\partial V}{\partial t}$,
 reduce $L(\text{stray})$

more stable Ch 7/8/9 2nd semester

Introduction to

Discontinuous Conduction Mode (DCM)

3 current
biode only one way

if
diodes
used
 $i_L \rightarrow 0$
new circuit

- Occurs because switching ripple in inductor current or capacitor voltage causes polarity of applied switch current or voltage to reverse, such that the current- or voltage-unidirectional assumptions made in realizing the switch are violated.

- Commonly occurs in dc-dc converters and rectifiers, having single-quadrant switches. May also occur in converters having two-quadrant switches.

- Typical example: dc-dc converter operating at light load (small load current). Sometimes, dc-dc converters and rectifiers are purposely designed to operate in DCM at all loads.

why? →

- Properties of converters change radically when DCM is entered:

M becomes load-dependent

Output impedance is increased

Dynamics are altered

Control of output voltage may be lost when load is removed

Good!

OPEN
load
always
DCM

More!
Personalities!

GOOD for stability - Ch 7/8/9

↑

↑ Pspice simulations

Subinterval 1


$$v_L(t) = V_g - v(t)$$

$$i_C(t) = i_L(t) - v(t) / R$$

Small ripple approximation
for $v(t)$ (but not for $i(t)$):

$$v_L(t) \approx V_g - V$$

$$i_C(t) \approx i_L(t) - V / R$$

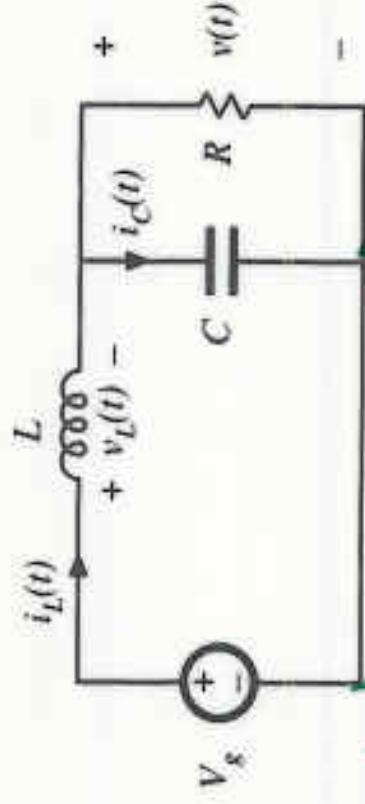


Careful "small ripple" i varies from i_{max} to 0 as i is DCM

Subinterval 2

$$v_L(t) = -v(t)$$
$$i_C(t) = i_L(t) - v(t) / R$$

Useful
Small ripple approximation
for $v(t)$ but not for $i(t)$:

$$v_L(t) \approx -V$$
$$i_C(t) \approx i_L(t) - V / R$$

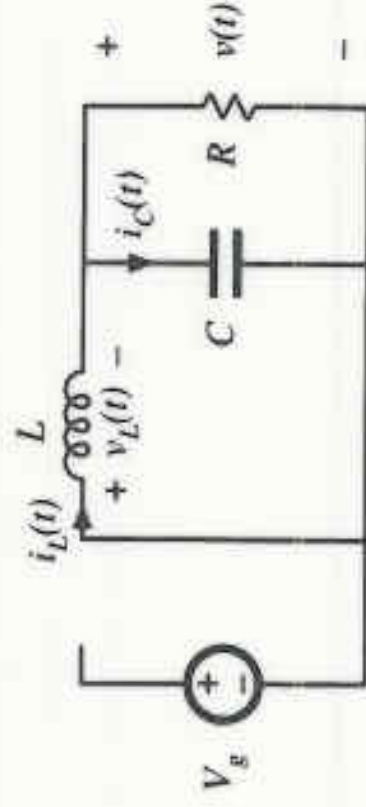

Subinterval 3

$$v_L = 0, \quad i_L = 0$$
$$i_C(t) = i_L(t) - v(t) / R$$

Small ripple approximation:

$$v_L(t) = 0$$
$$i_C(t) = -V / R$$

