

only M(0) for CCM, but for DCM

5.2. Analysis of the conversion ratio $M(D, K)$

$K = \frac{2L}{RT_{sw}}$ defined by choices of components & f_{sw}

Analysis techniques for the discontinuous conduction mode:

Inductor volt-second balance

$$\langle v_L \rangle = \frac{1}{T_s} \int_0^{T_s} v_L(t) dt = 0$$

Capacitor charge balance

$$\langle i_C \rangle = \frac{1}{T_s} \int_0^{T_s} i_C(t) dt = 0$$

Small ripple approximation sometimes applies:

$v(t) \approx V$ because $\Delta v \ll V$ (due to feedback)

$i(t) \approx I$ is a poor approximation when $\Delta i > I$

Converter steady-state equations obtained via charge balance on each capacitor and volt-second balance on each inductor. Use care in applying small ripple approximation.

small ripple approx. INVARIANT


Whoa! DCM $\Delta i > I$

Three unknowns: D_1, D_2, D_3

Example: Analysis of

DCM buck converter $M(D, K)$


Fig 5.9
p.113

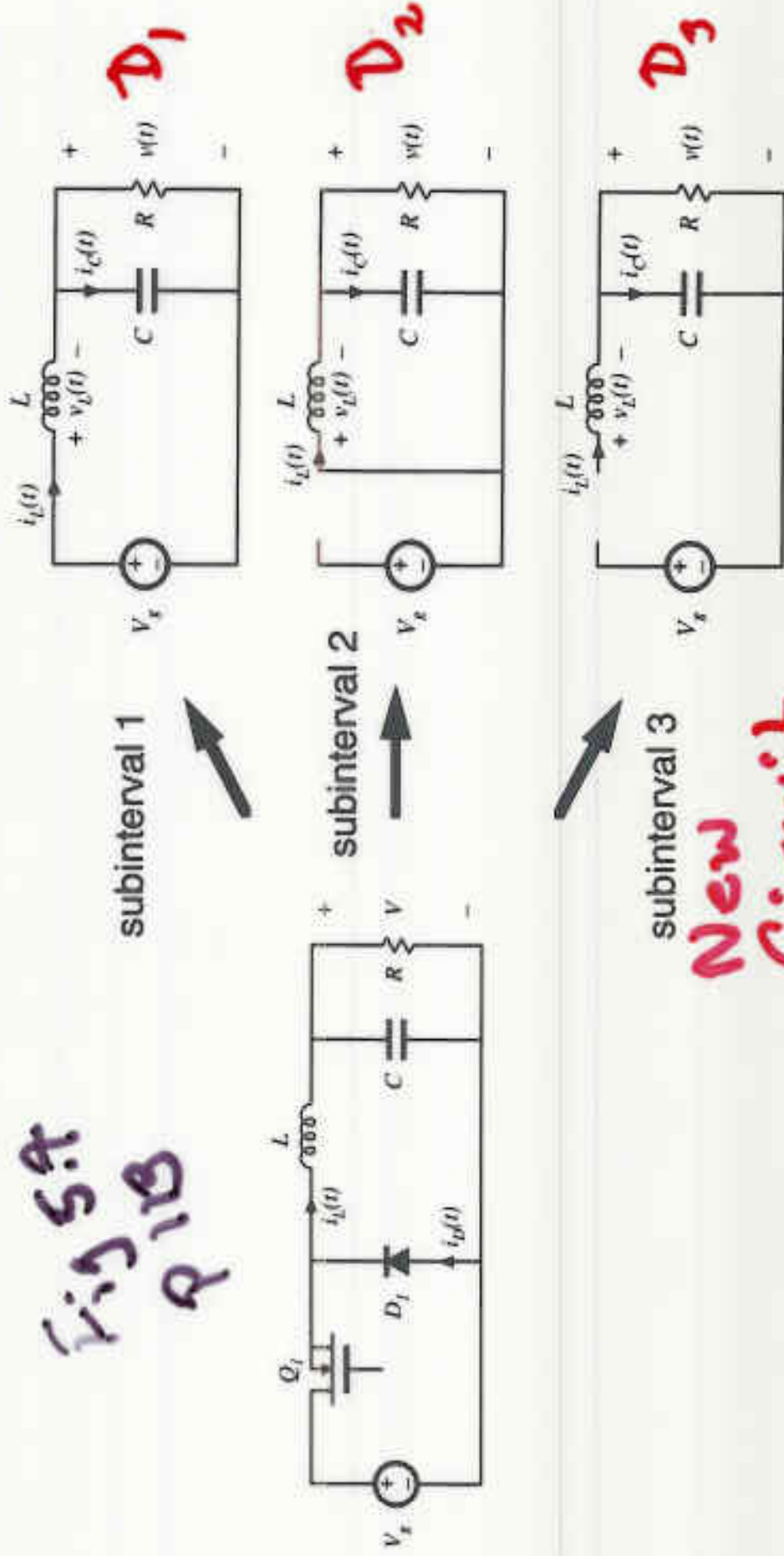

New Circuit
for D_3
diode opens for reverse

Inductor volt-second balance

Fig 5.8 p115

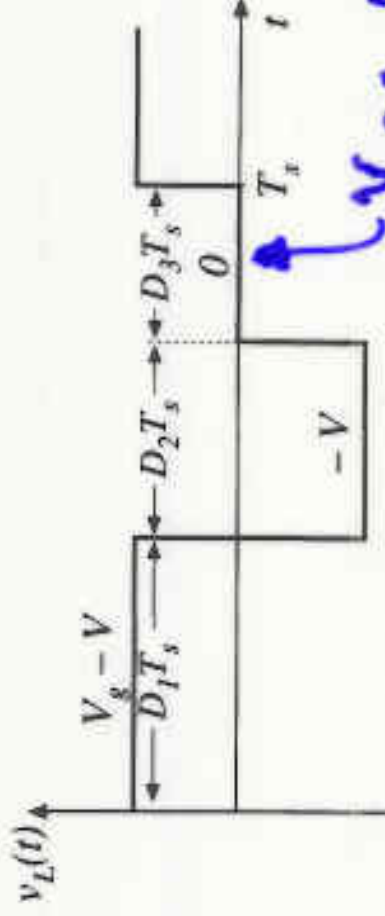

Key to understanding

$V_L = 0$ when $i_L = 0$

Volt-second balance:

$$\langle v_L(t) \rangle = D_1(V_g - V) + D_2(-V) + D_3(0) = 0$$

Solve for V :

$$V = V_g \frac{D_1}{D_1 + D_2}$$

Usually D_1 set by designer

note that D_2 is unknown

Capacitor charge balance

node equation:

$$i_L(t) = i_C(t) + V/R$$



capacitor charge balance:

$$\langle i_C \rangle = 0$$

hence

$$\langle i_L \rangle = V/R$$

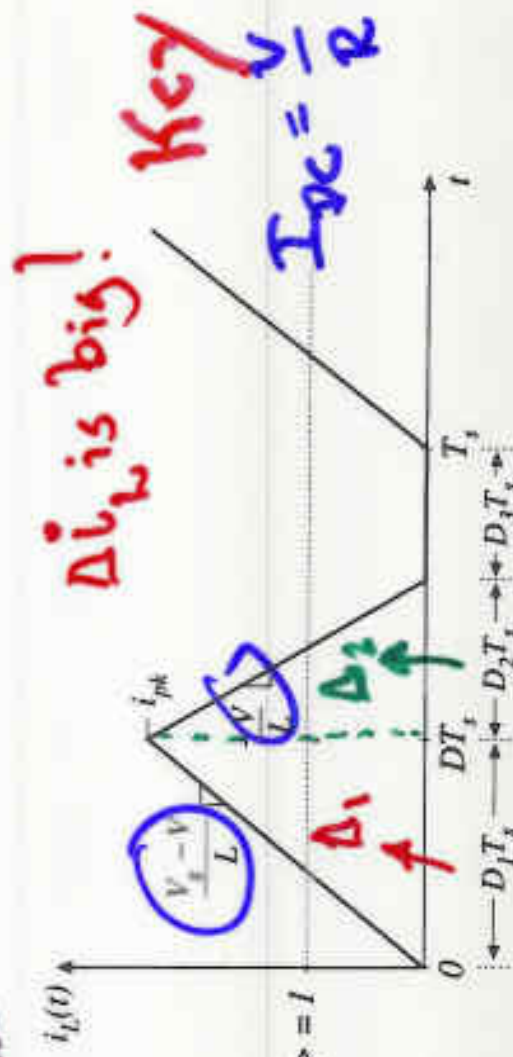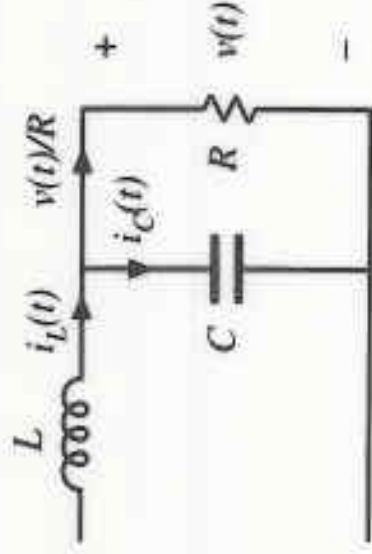must compute dc component of inductor current and equate to load current (for this buck converter example)



Inductor current waveform

peak current:

$$① \quad i_L(D_1 T_s) = i_{pk} = \frac{V_g - V}{L} D_1 T_s$$


② average current:

$$\langle i_L \rangle = \frac{1}{T_s} \int_0^{T_s} i_L(t) dt$$

triangle area formula:

$$\int_0^{T_s} i_L(t) dt = \frac{1}{2} i_{pk} (D_1 + D_2) T_s$$
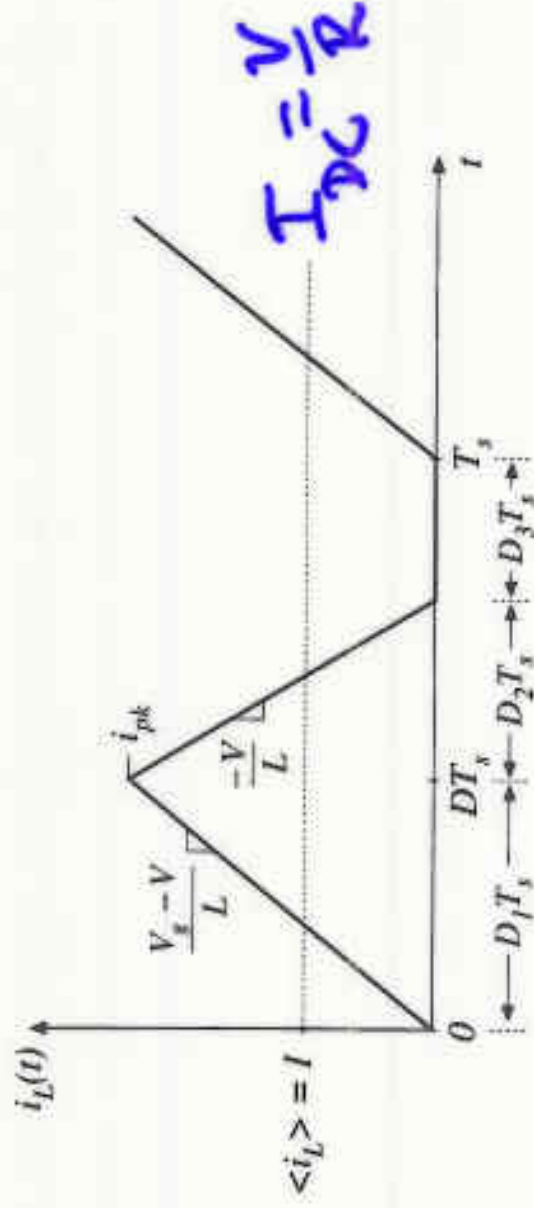
$$③ \quad \langle i_L \rangle = (V_g - V) \frac{D_1 T_s}{2L} (D_1 + D_2)$$



equate dc component to dc load current:

$$③ \quad \frac{V}{R} = \frac{D_1 T_s}{2L} (D_1 + D_2) (V_g - V)$$

$$M(D)_{CCM} = 1$$

Solution for V

Know $D_1, D_2 \Rightarrow D, B_s$ known

Two equations and two unknowns (V and D_2):

$$1. \quad V = V_s \frac{D_1}{D_1 + D_2}$$

(from inductor volt-second balance)

$$2. \quad \frac{V}{R} = \frac{D_1 T_s}{2L} (D_1 + D_2) (V_s - V)$$

(from capacitor charge balance)

Eliminate D_2 , solve for V :

For DCM
Buck

$$\frac{V}{V_s} = \frac{2}{1 + \sqrt{1 + 4K / D_1^2}}$$

where $K = 2L / RT_s$
valid for $K < K_{crit}$

K Methodology

Buck
CCM = ?


As $K \gg K_c$

$m(D) = \eta(D, K)$

Solve a quadratic for
DC Transfer Function
for DCM

Buck converter $M(D,K)$

Fig 5.11
p.117

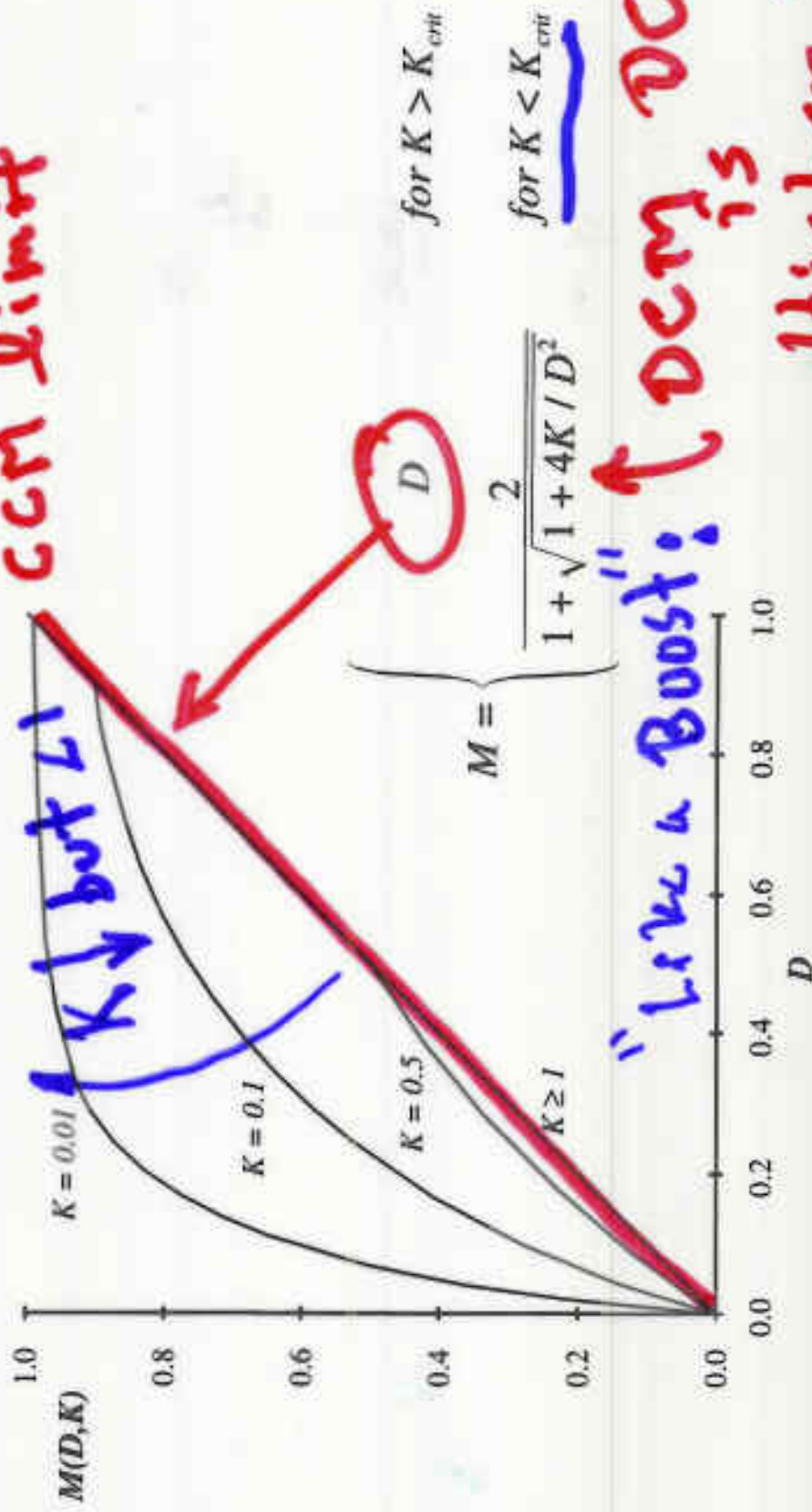

for $K > K_{crit}$

for $K < K_{crit}$