

6.4. Converter evaluation and design

For a given application, which converter topology is best?

There is no ultimate converter, perfectly suited for all possible applications

Trade studies

- Rough designs of several converter topologies to meet the given specifications
- An unbiased quantitative comparison of worst-case transistor currents and voltages, transformer size, etc.

Comparison via switch stress, switch utilization, and semiconductor cost

Spreadsheet design

6.4.2. Converter design using computer spreadsheet

Given ranges of V_g and P_{load} , as well as desired value of V and other quantities such as switching frequency, ripple, etc., there are two basic engineering design tasks:

- Compare converter topologies and select the best for the given specifications
- Optimize the design of a given converter

A computer spreadsheet is a very useful tool for this job. The results of the steady-state converter analyses of Chapters 1-6 can be entered, and detailed design investigations can be quickly performed:

- Evaluation of worst-case stresses over a range of operating points
- Evaluation of design tradeoffs

Spreadsheet design example

Choices

Specifications

Maximum input voltage V_g
Minimum input voltage V_g
Output voltage V
Maximum load power P_{load}
Minimum load power P_{load}
Switching frequency f_s
Maximum output ripple Δv


390 V
260 V
15 V
200 W
20 W
100 kHz
0.1 V

- Input voltage: rectified 230 Vrms $\pm 20\%$
- Regulated output of 15 V
- Rated load power 200 W
- Must operate at 10% load
- Select switching frequency of 100 kHz
- Output voltage ripple $\leq 0.1V$

Compare single-transistor forward and flyback converters in this application

Specifications are entered at top of spreadsheet

Forward converter design, CCM

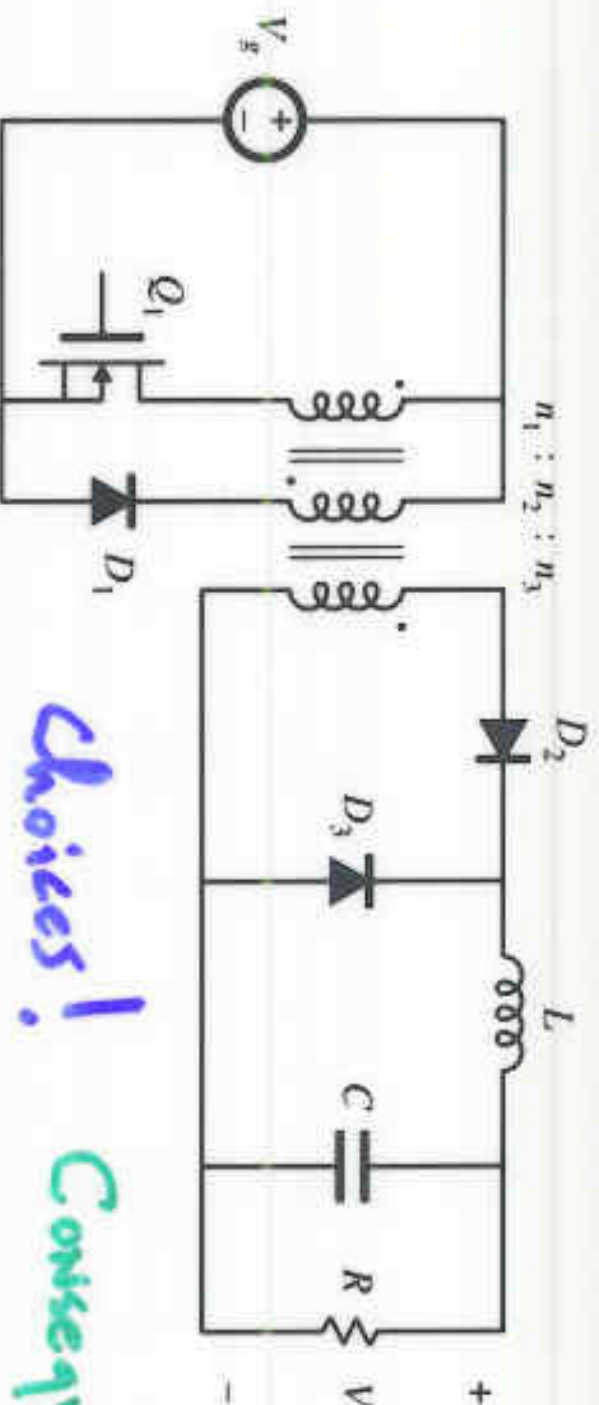

Choices! Consequences?

Design variables

Reset winding turns ratio n_2/n_1

Turns ratio n_3/n_1

Inductor current ripple Δi

1
0.125
2A ref to sec

- Design for CCM at full load; may operate in DCM at light load

Enter results of converter analysis into spreadsheet (Forward converter example)

Maximum duty cycle occurs at minimum V_g and maximum P_{load} .
Converter then operates in CCM, with

$$D = \frac{n_1}{n_3} \frac{V_g}{V_g}$$

Inductor current ripple is

$$\Delta i = \frac{D V T_s}{2L}$$

Solve for L :

$$L = \frac{D V T_s}{2\Delta i}$$

Consequence #1

Δi is a design variable. For a given Δi , the equation above can be used to determine L . To ensure CCM operation at full load, Δi should be less than the full-load output current. C can be found in a similar manner.

Forward converter example, continued

Check for DCM at light load. The solution of the buck converter operating in DCM is

$$V = \frac{n_3}{n_1} V_g \frac{2}{\sqrt{1 + \frac{4K}{D^2}}}$$

with $K = 2L / RT_s$, and $R = V^2 / P_{load}$

These equations apply equally well to the forward converter, provided that all quantities are referred to the transformer secondary side.

Solve for D :

$$D = \frac{2\sqrt{K}}{\sqrt{\left(\frac{2n_3 V_g}{n_1 V} - 1\right)^2 - 1}} \quad \text{in DCM} \qquad D = \frac{n_1}{n_3} \frac{V}{V_g} \quad \text{in CCM}$$

at a given operating point, the actual duty cycle is the small of the values calculated by the CCM and DCM equations above. Minimum D occurs at minimum P_{load} and maximum V_g .

More regarding forward converter example

Worst-case component stresses can now be evaluated.

Peak transistor voltage is

$$\max(V_{Q1}) = V_g \left(1 + \frac{n_1}{n_2} \right) \quad \text{transformer}$$

RMS transistor current is

$$I_{Q1,rms} = \frac{n_3}{n_1} \sqrt{D} \sqrt{I^2 + \frac{(\Delta i)^2}{3}} \approx \frac{n_3}{n_1} \sqrt{D} I \quad \text{D-wave}$$

(this neglects transformer magnetizing current)

Other component stresses can be found in a similar manner.
Magnetics design is left for a later chapter.


How to force $V_{prim} = 0$? $V_p = 0 \Rightarrow V_g = \frac{1}{2} V_g = \frac{1}{2} V_g$

Transformer reset mechanism

Equal & opposite

boost inductor

publishing
Trent

 

$V_{out} = V_{in}$
Sets $V_{primary}$ during D

Switch #1 T


Switch #2 T

- As in full-bridge buck topology, transformer volt-second balance is obtained over two switching periods.
- During first switching period: transistors Q_1 and Q_4 conduct for time DT_1 , applying volt-seconds VDT_1 to secondary winding.
- During next switching period: transistors Q_2 and Q_3 conduct for time DT_2 , applying volt-seconds $-VDT_2$ to secondary winding.

TYPE OF CONVERTER

CIRCUIT CONFIGURATION

$$\frac{V_{IN}}{N_1} = \frac{V_0}{N_2}$$

 

Full Bridge

IDEAL TRANSFER FUNCTION

$$\frac{V_0}{V_{IN}} = 2 \frac{N_2}{N_1} \left(\frac{1}{1+S} \right) = 2 \frac{N_2}{N_1} (D)$$

PEAK DRAIN CURRENT

$$I_{DMAX} = \frac{N_2}{2 N_1} \left(I_{RL} + \frac{\Delta I_L}{2} \right) + I_{MAG}$$

(I_{MAG} = Peak magnetizing current.)

PEAK DRAIN VOLTAGE

$$V_{DS} = V_{IN}$$

AVERAGE DIODE CURRENTS

$$I_{CR5} = I_{RL}$$

$$I_{CR6} = I_{RL}$$

$$I_{diode} = I_{AV}$$


$$I_{AV} = I_{ON} D + D' I_{OFF}$$

5% increase
max = I_{AV}

DIODE VOLTAGES (V_{RM})

$$V_{RM} \begin{cases} V_{CR5} = 2V_{IN} \left(\frac{N_2}{N_1} \right) V_{CR1} = V_{IN} \\ V_{CR6} = 2V_{IN} \left(\frac{N_2}{N_1} \right) V_{CR2} = V_{IN} \end{cases}$$

VOLTAGE AND CURRENT WAVEFORMS

 

ADVANTAGES

DISADVANTAGES

TYPICAL APPLICATIONS

APPLICABLE HARRIS PRODUCTS

Good transformer utilization, transistors rated at V_{DS} , isolation, multiple outputs. ID is reduced as a ratio of N_2/N_1 . Zero voltage switching possible. Low output ripple.

High parts count. C1 has high ripple current. Requires high side switch drive. Cross conduction of Q1 and Q2 or Q3 and Q4 possible. High input current ripple.

High power, high input voltage

HIP4080B1 HIP2500 HV400

Le

Missing

Summary of key points

Lehm

3. The steady-state behavior of transformer-isolated converters may be understood by first replacing the transformer with the magnetizing-inductance-plus-ideal-transformer equivalent circuit. The techniques developed in the previous chapters can then be applied, including use of inductor volt-second balance and capacitor charge balance to find dc currents and voltages, use of equivalent circuits to model losses and efficiency, and analysis of the discontinuous conduction mode.


4. In the full-bridge, half-bridge, and push-pull isolated versions of the buck and/or boost converters, the transformer frequency is twice the output ripple frequency. The transformer is reset while it transfers energy: the applied voltage polarity alternates on successive switching periods.

buck L

$2f_{\text{eff}}$

$\frac{1}{2}$


Differential Output

 

Case $M_1(D)$ buck driven by D ,
 $M_2(D)$ buck driven by D'

$$V_{out} = DV_g - D'V_g = (2D - 1)V_g$$

Flyback converter design, CCM

 

Design variables

Turns ratio n_2/n_1

Inductor current ripple Δi

0.125

3 A ref to sec

- Design for CCM at full load; may operate in DCM at light load