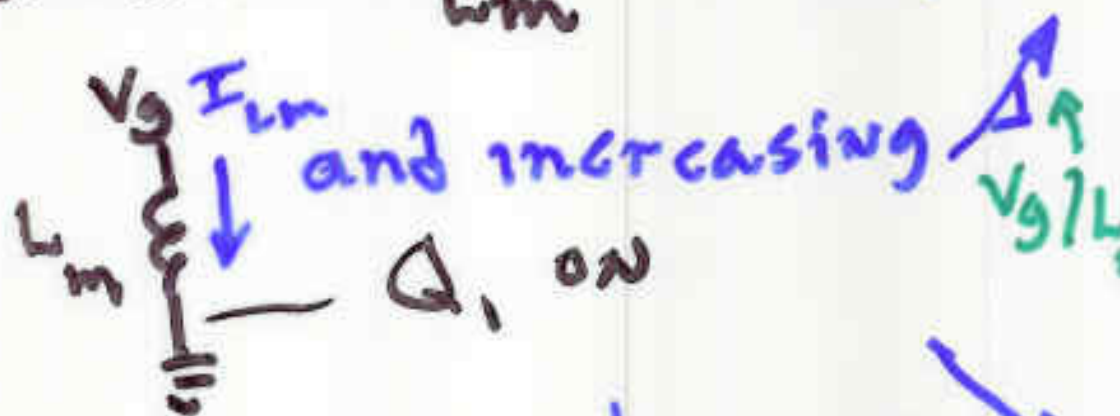


Summarize $V(t)_{Lm}$ $I(t)_{Lm}$

$D_1 T_{sw}$



$D_2 T_{sw}$



D_1 on

$$\frac{-V_g}{N_2} = \frac{V_{Lm}}{N_1}$$

N_2 coil N_1 coil

$$-\frac{N_1}{N_2} \frac{V_g}{L_m}$$


$$\frac{N_1}{N_2} > 1$$

forces

DCM



DCM Forward converter: waveforms

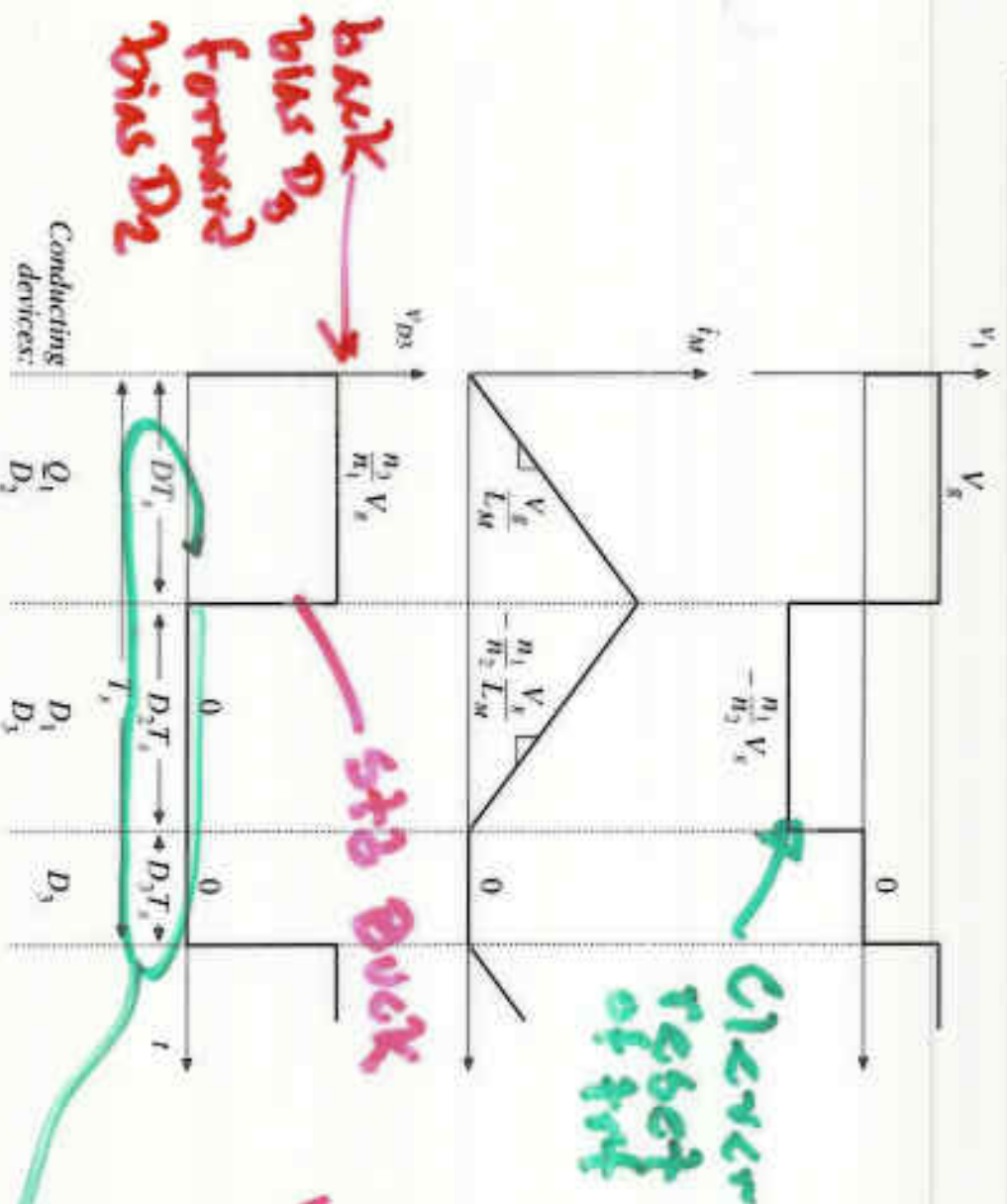

- Magnetizing current, in conjunction with diode D_1 , operates in discontinuous conduction mode
- Output filter inductor, in conjunction with diode D_3 , may operate in either CCM or DCM

$$V_o = D \frac{n_3}{n_1} V_g$$

Next Details!

Quantitative

Conditions for

Transformer reset

→ D₁ choice

$$\frac{n_2}{n_1} \text{ ratio} \geq 1.7$$

From magnetizing current volt-second balance:

$$\langle v_1 \rangle = D(V_g) + D_2(-V_g n_1/n_2) + D_3(0) = 0$$

Solve for D₂:

$$D_2 = \frac{n_2}{n_1} D$$

D₃ cannot be negative. But D₃ = 1 - D - D₂. Hence

$$D_3 = 1 - D - D_2 \geq 0$$

$$D_3 = 1 - D \left(1 + \frac{n_2}{n_1} \right) \geq 0$$

Solve for D

$$D \leq \frac{1}{1 + \frac{n_2}{n_1}}$$

To insure No L_m saturation

① Reset for CCM Forward

② To achieve DCM

Limited DCM

Forward


for $n_1 = n_2$: $D \leq \frac{1}{2}$
 $\pm V_g$ on V_g

$D_3 T_{sw}$

Subinterval 3

DCM condition
 $L_{Lm} \rightarrow 0$
if proper conditions

$\ominus I_{Lm}$

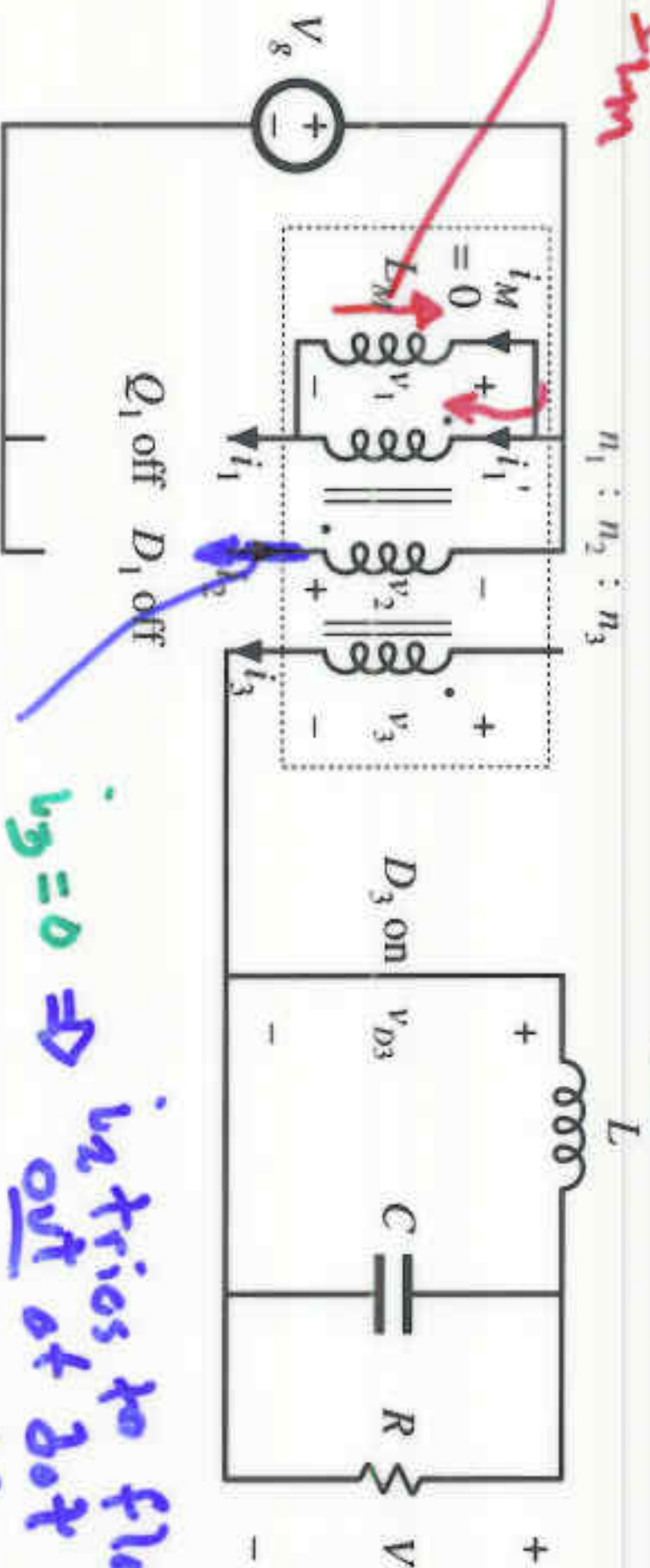

$i_3 = 0 \Rightarrow i_2$ tries to flow
out at D_1
 D_1 off

↙ interval

If D_1 short enough $i_{Lm}(\max)$ is low


Subinterval 3

② Interval 3 Caused by i_{Lm} going $\rightarrow 0$

All coils $i_{coil} = ?$

$i_{Lm} \rightarrow 0, D_1 \text{ off}$

fix 6.25C
96 156

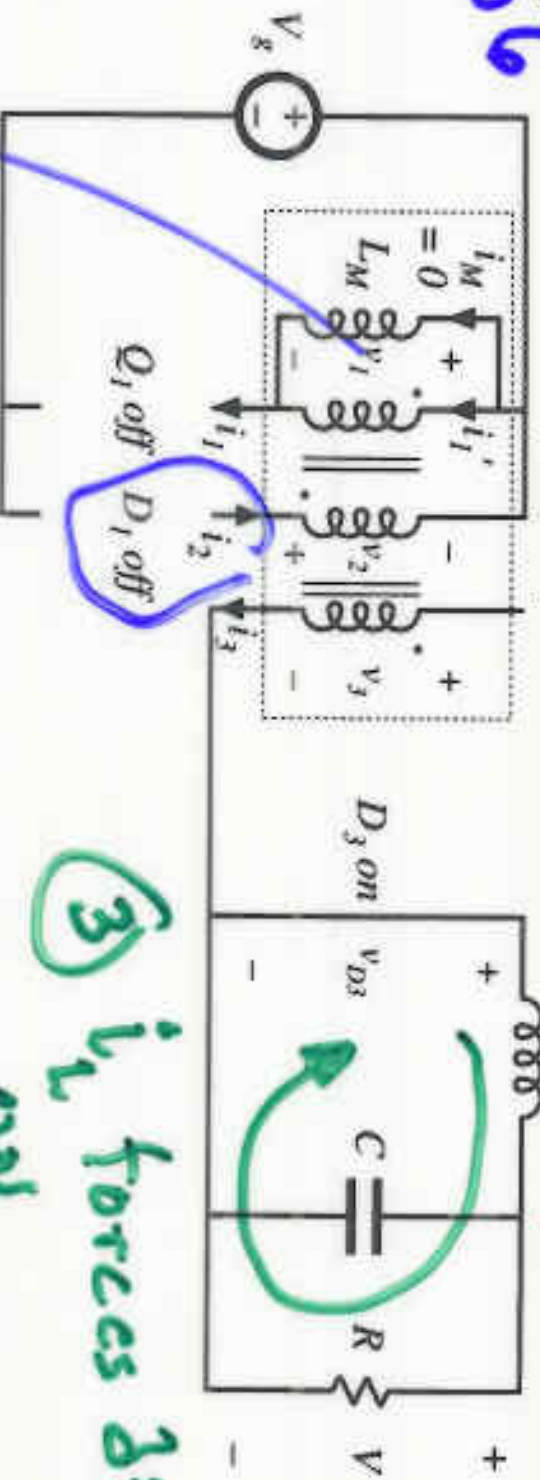


③ i_L forces diode 3 on

Is $v_{D3} = 0$ for both D_2 & D_3 intervals?

① $i_L = 0 \Rightarrow v_{D1} = 0$

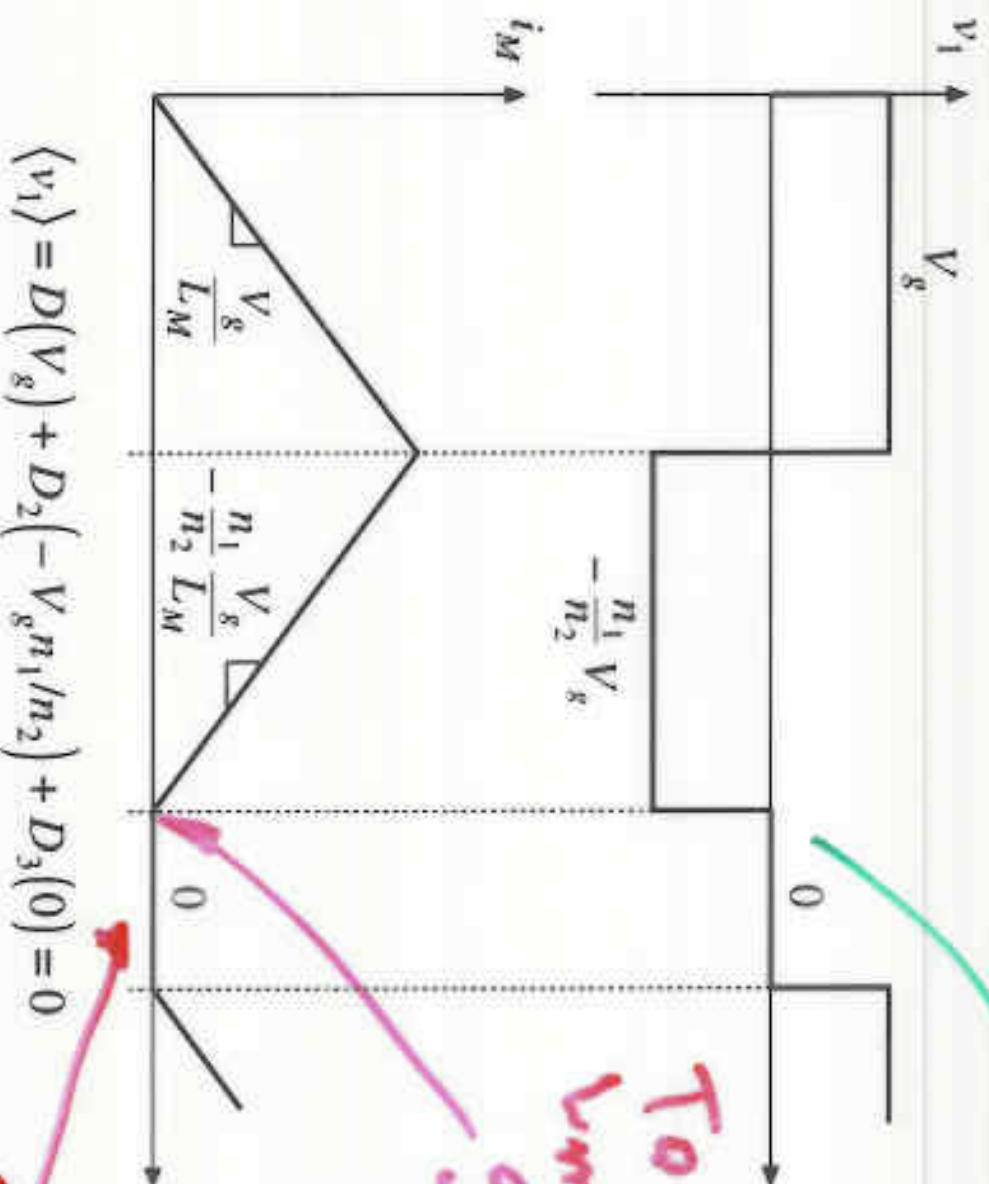Magnetizing inductance volt-second balance



$$\langle v_1 \rangle = D(V_g) + D_2(-V_g n_1/n_2) + D_3(0) = 0$$

$$i_L = 0 \text{ at } t_{off} \Rightarrow D V_L = 0$$

No saturation
To insure
 L_m sat
goal $V_{Lm} = \Delta$
each sm
cycle


Force a
D₃ interval

Quantifying Trf. Reset Condition

Magnetizing inductance volt-second balance

ON COIL #1 (L_M)

Fig 6.24
pg 155

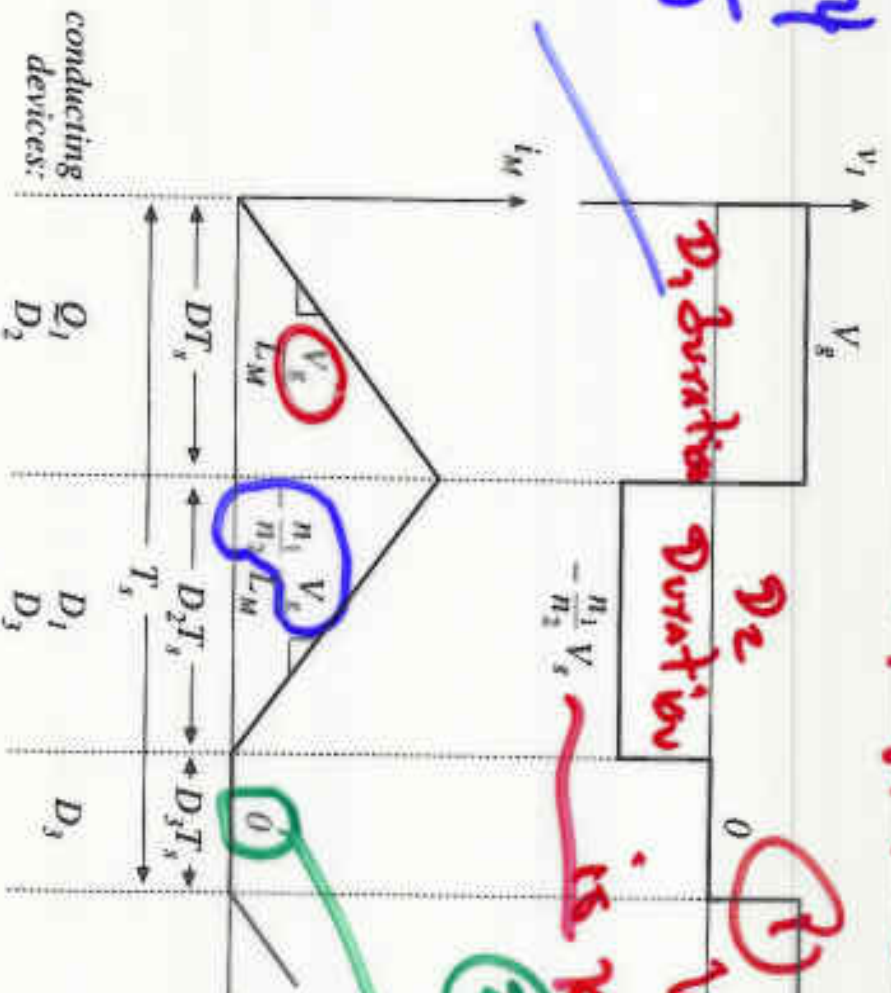

① ON coil #1
V-sec balance!
D₁ is time!

② is key! D₁ is time!

must for reset of L_M
hence why
DCM best
for doing so
② solve for D_2
as D_1 is set
by Q control

③
Times: D_1, D_2, D_3 : $\langle V_t \rangle = D(V_g) + D_2(-V_g n_1/n_2) + D_3(0) = 0$