

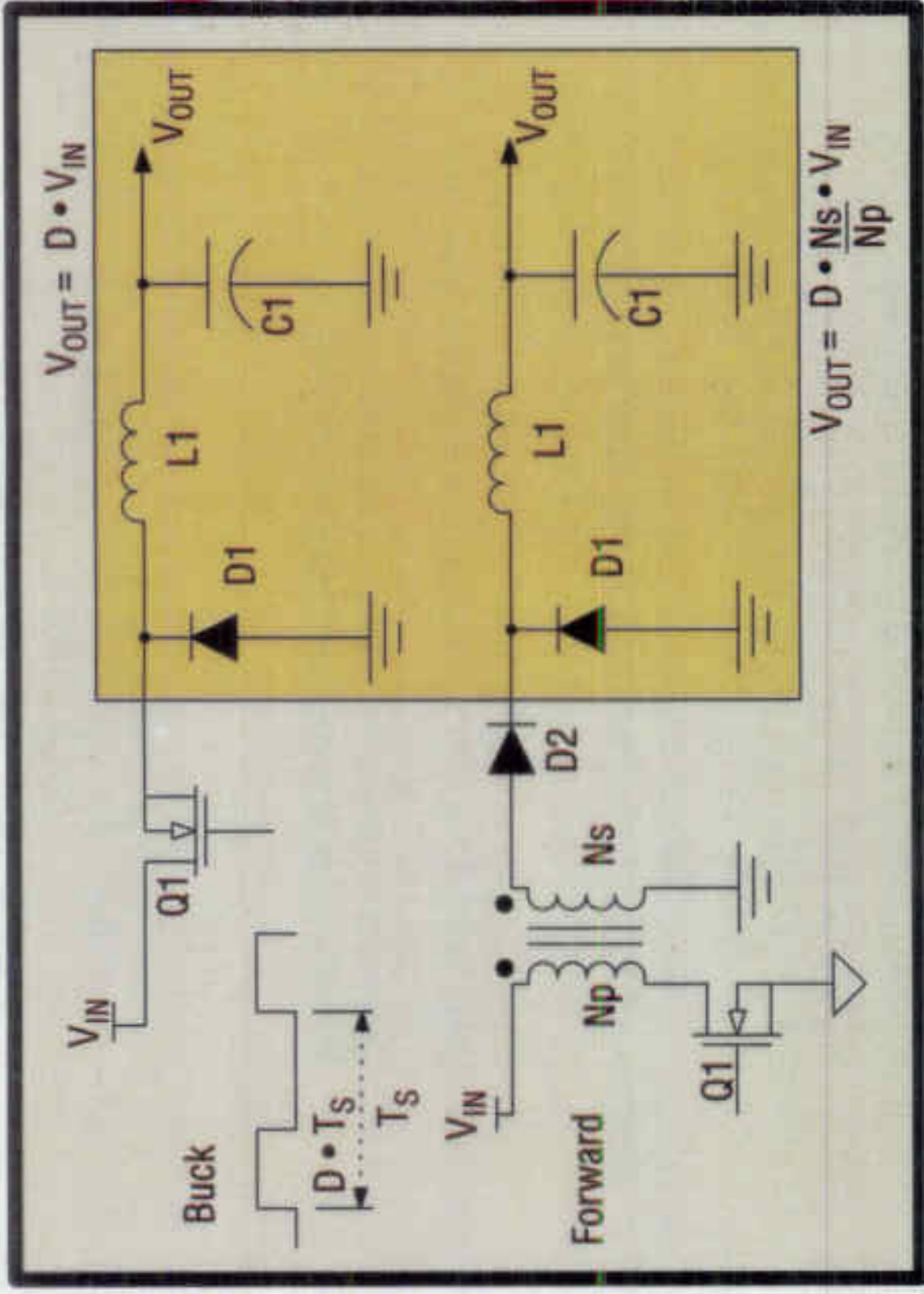


Fig.1. Buck and forward topology.

tive cost, complexity and efficiency tradeoffs. The forward converter is derived from the buck topology family,

Buck $\rightarrow$ Forward

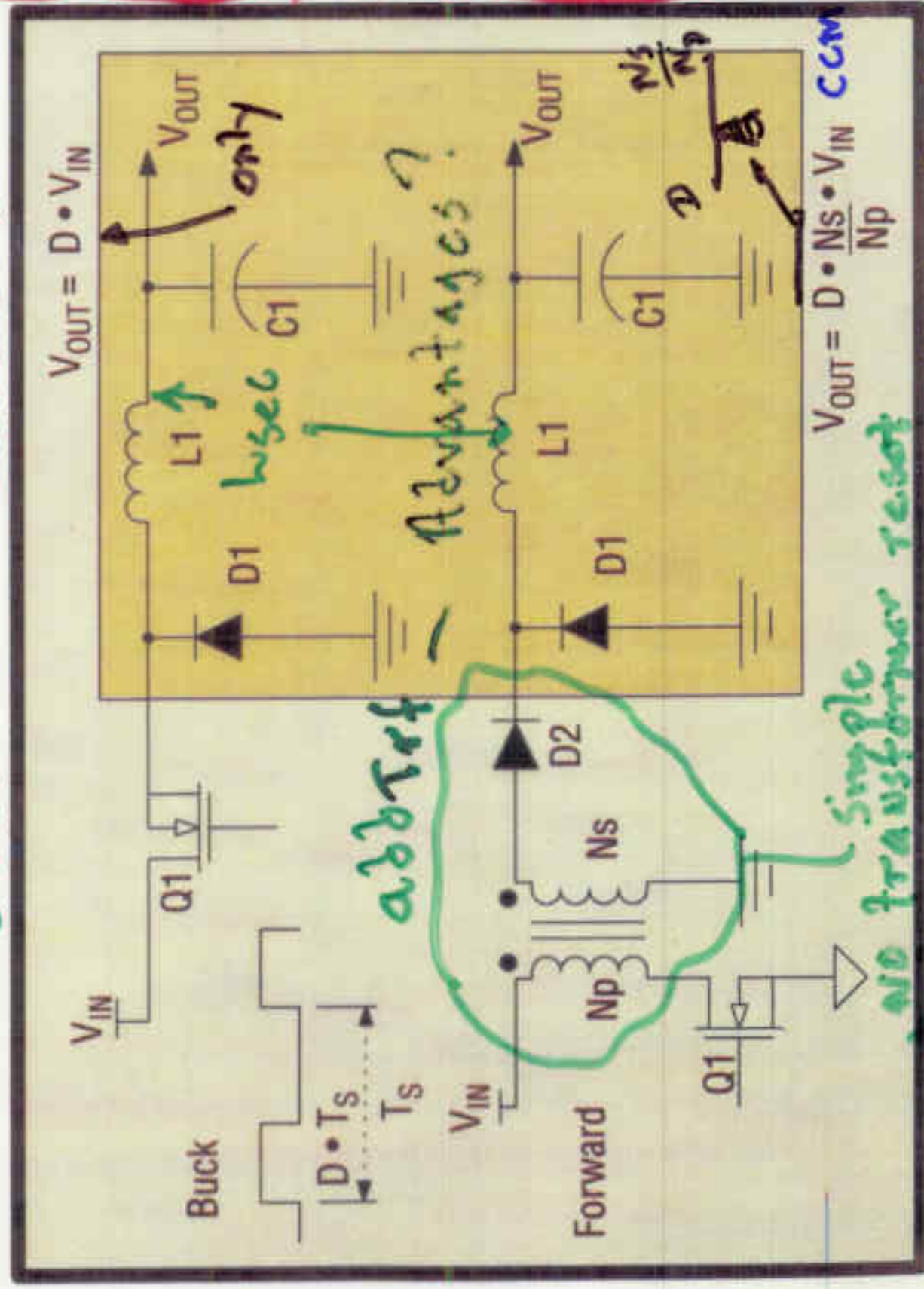


Fig.1. Buck and forward topology.

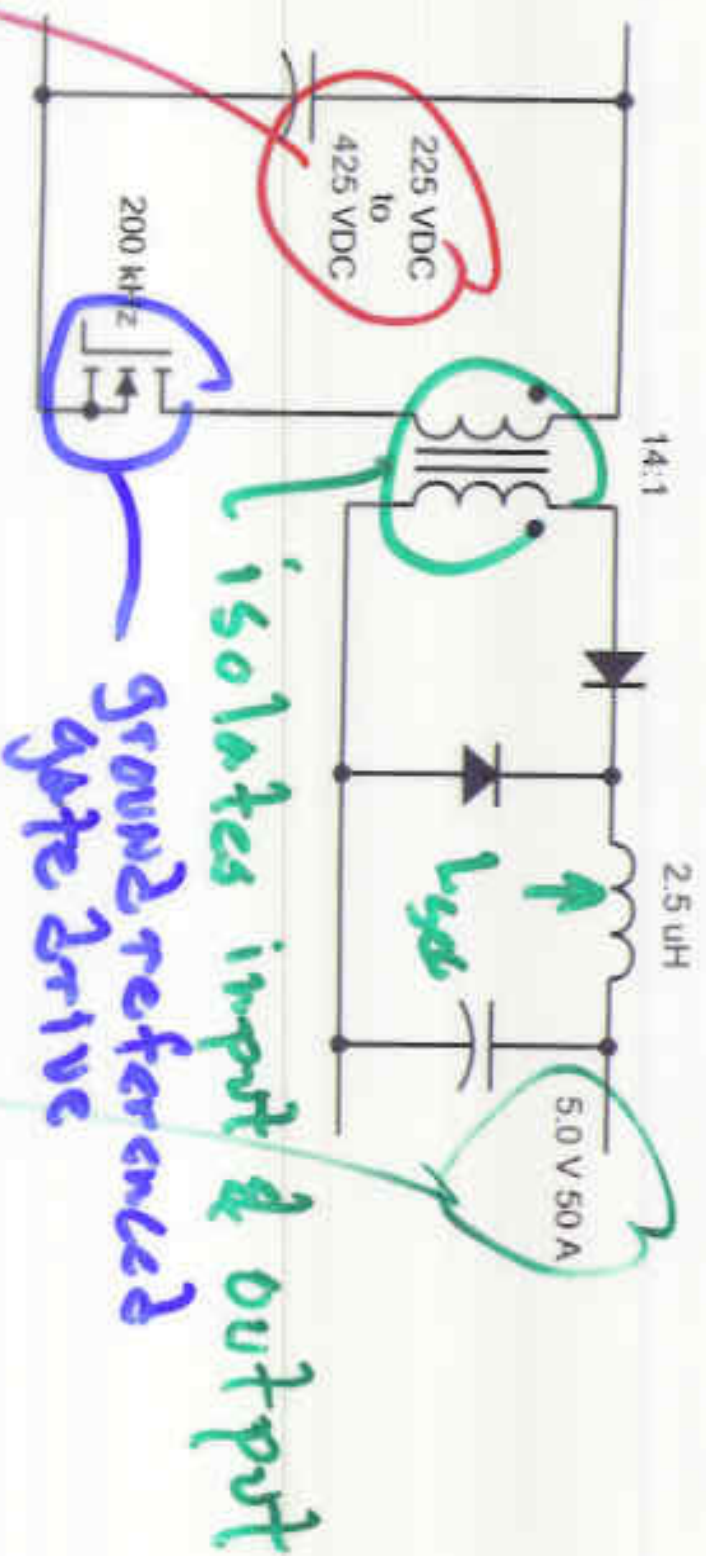


Figure 1 : Forward converter designed for rugged operation.

V_s (train) very high far?
 Server with $10^3 \mu F$

V_{out} low
 eg 2.10 V

① → Buck
No Trf

$$V_o = D V_{in}$$

② → big V_{max} on D_1
Buck
With Trf
is

$$V_o = \left(\frac{N_s}{N_p} \right) V_{in}$$

D
↑
fine
tune


Forward
Floating gate drive
eliminated

$\frac{N_s}{N_p}$
big
step down

Small V_{max} on L_1 by $\frac{N_s}{N_p}$

Need extra diode D_2

Both cases

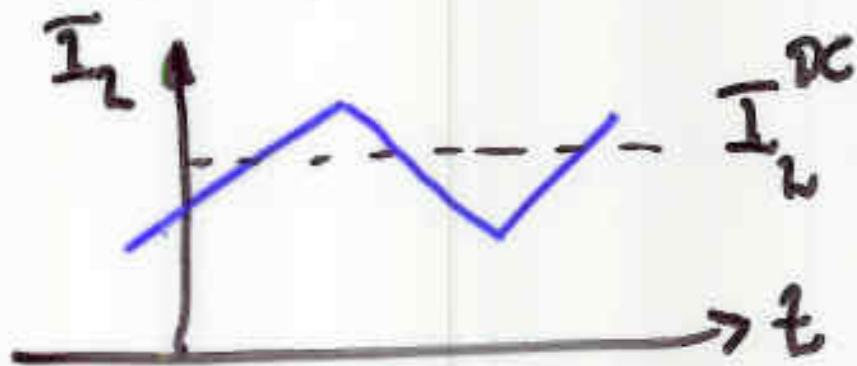

$$\frac{V_{in} - V_o}{L}$$

Buck
switches



$$V_o/2$$

?

Forward
switches



?



?

Adv of Trf

① Isolation: separate grounds
 V_p & V_{sec} and multiple
 N_s coils for multiple V_{out}

② Q_1 will have lower I_{max}
 in primary of a step down
 trf

V_{GS} w.r.t ground! $\frac{V_s}{V_p}$ step down

③ $V_o = D V_{IN} \left(\frac{N_s}{N_p} \right)$ D $\frac{N_s}{N_p}$

 Buck $\frac{N_s}{N_p}$
 step down Trf

④ L_m for Forward
 which and why

⑤ CCM vs DCM

Effect choice of
 I_{IN} secondary

big ?

small.

goals

L_{buck}

in sec

reset
 circuits

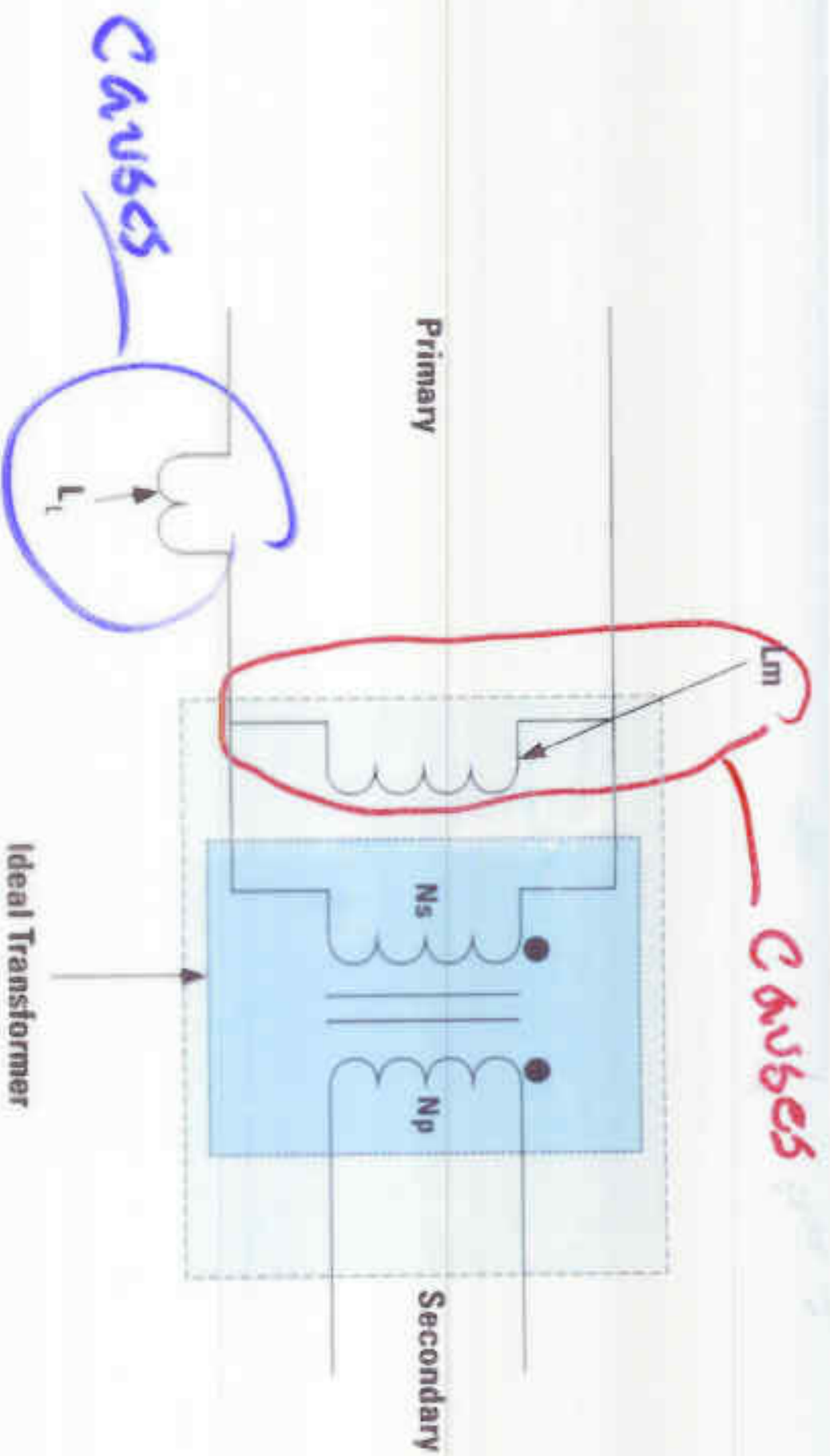


Figure 2. Transformer Model

Disadvantage of Trf

Worst case

- ① Saturation of L_m by V_{sec} from big V_{in}
 $\Rightarrow$ ① desire large L_m value to avoid

② Will need active trf reset as well - how achieved?

- ② No residual V_{DC} on input to Trf allowed } ☹️



- ③ Extra losses $\hookleftarrow$ R windings

avg duty cycle
is small loss

1.00

Forward Transformer Dissipation at 25°C
100-W output

$$P_{tot} \text{ loss} = P_{core} + P_{winding}$$

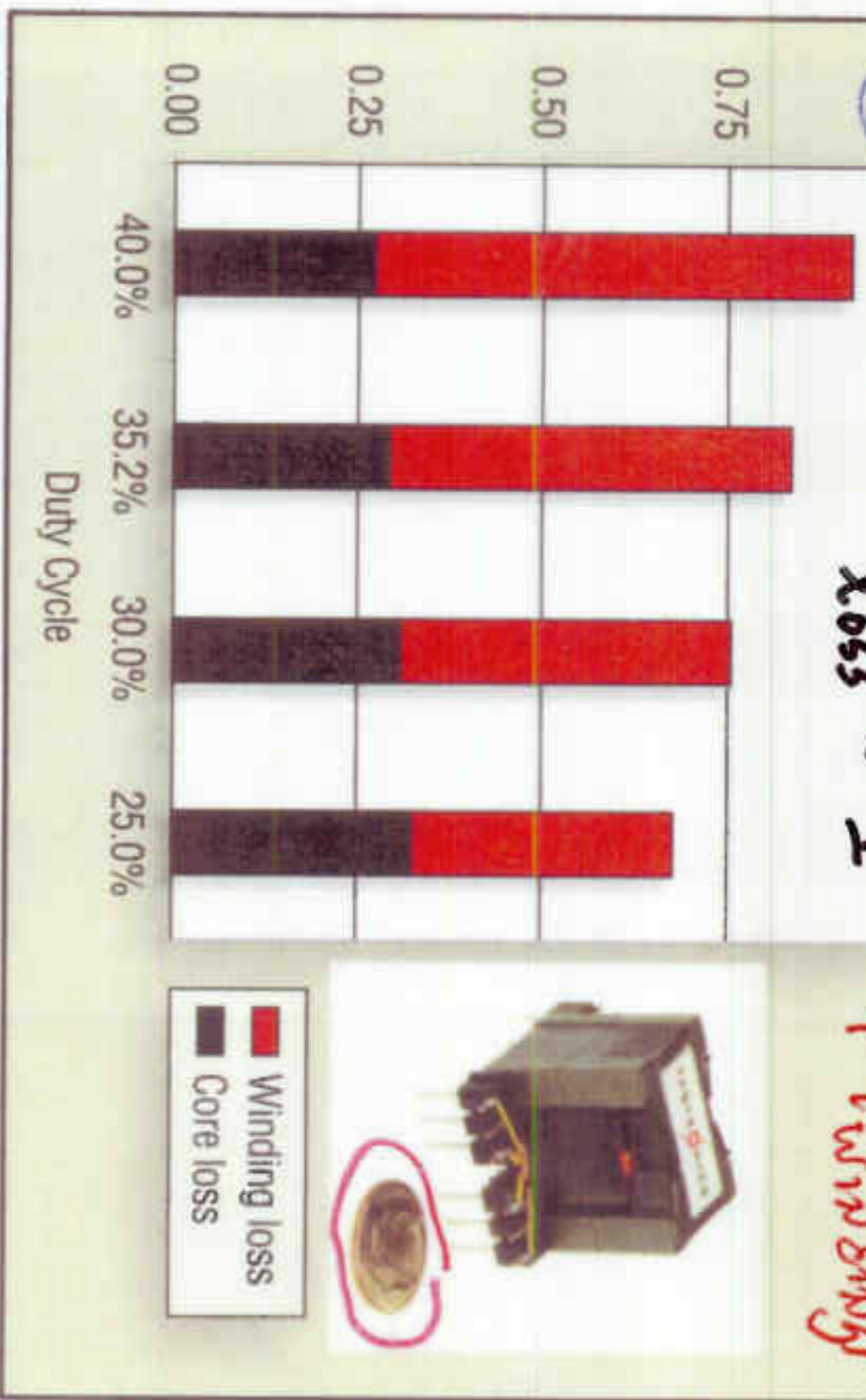


Fig. 11. Measured total loss of 100-kHz forward transformer providing 20 V at 5 A.

Ways to insure L_m does not
saturate

- ① Make sure i_{L_m} always
returns to "0" over a
switch cycle — operate
ONLY DCM
 $\Rightarrow$ small L (sec)
will cause $i_{L_m} > I_{oc}$
Buck
- ② Insure equal & opposite
V-sec on L_m over a
CCM switch cycle — add a
third winding and a
clamp diode