

Series RLC


$$f_{RC} = \frac{1}{2\pi RC}$$

Z_C series with R




$$f_{RL} = \frac{R}{2\pi L}$$


Z_L series with R

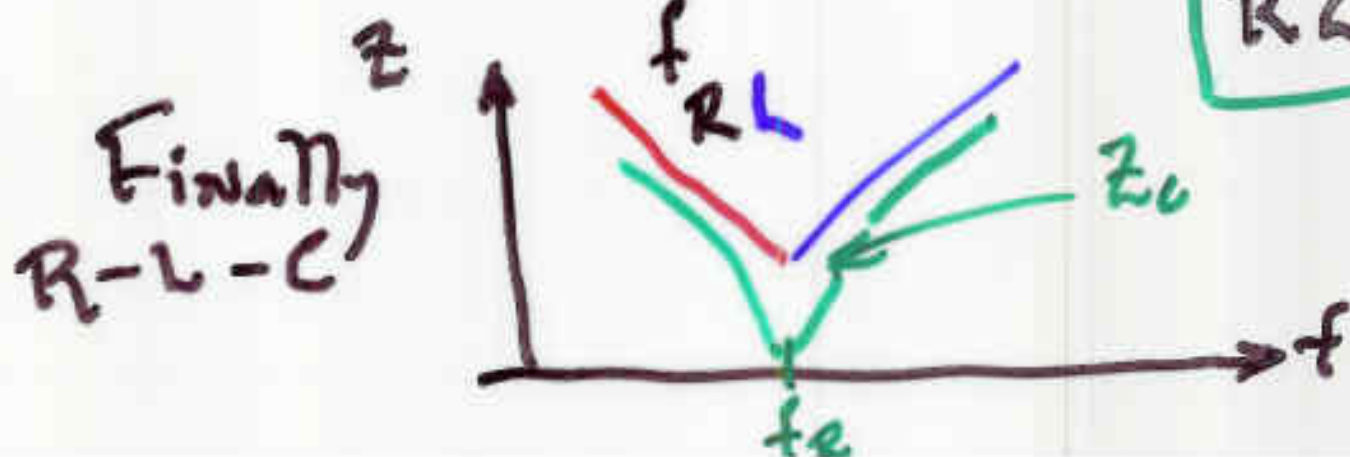

Series RLC

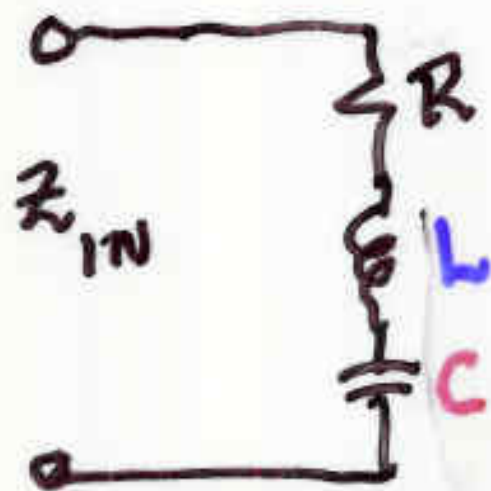

log Z_{in}

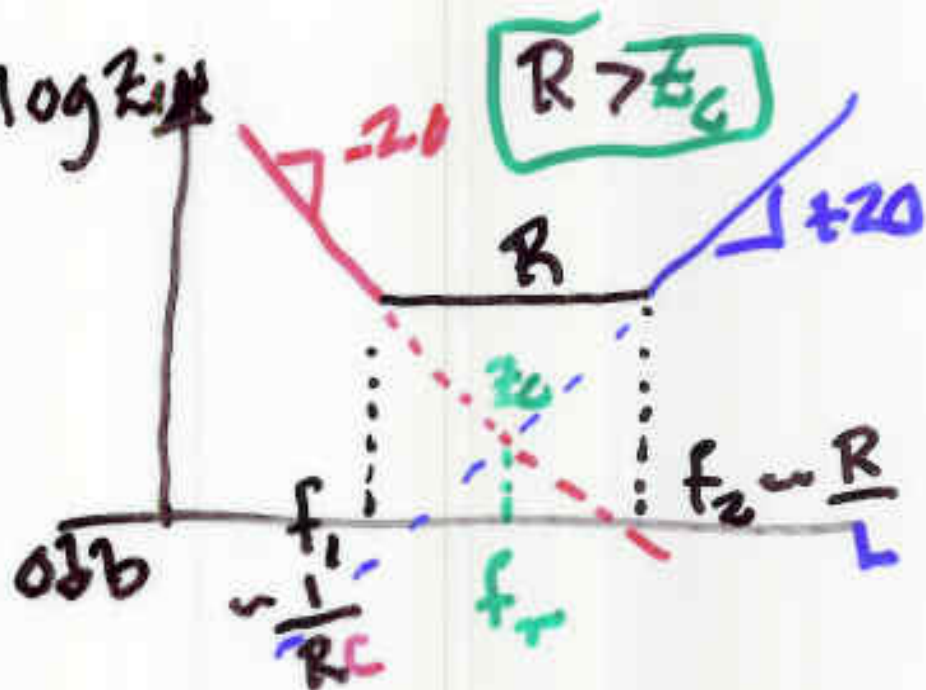

$$f_1 = \frac{1}{2\pi RC}$$

$$f_2 = \frac{R}{2\pi L}$$

$$f_r = ? \quad \left| \frac{1}{wC} \right| = |wL| @ w_r$$


$$w_r = \frac{1}{\sqrt{LC}}$$

$$f_r = \frac{1}{2\pi \sqrt{LC}}$$

$$Z_c = Z_r @ w_r = \sqrt{\frac{L}{C}} \equiv Z_c$$

Above case for $R > Z_c$

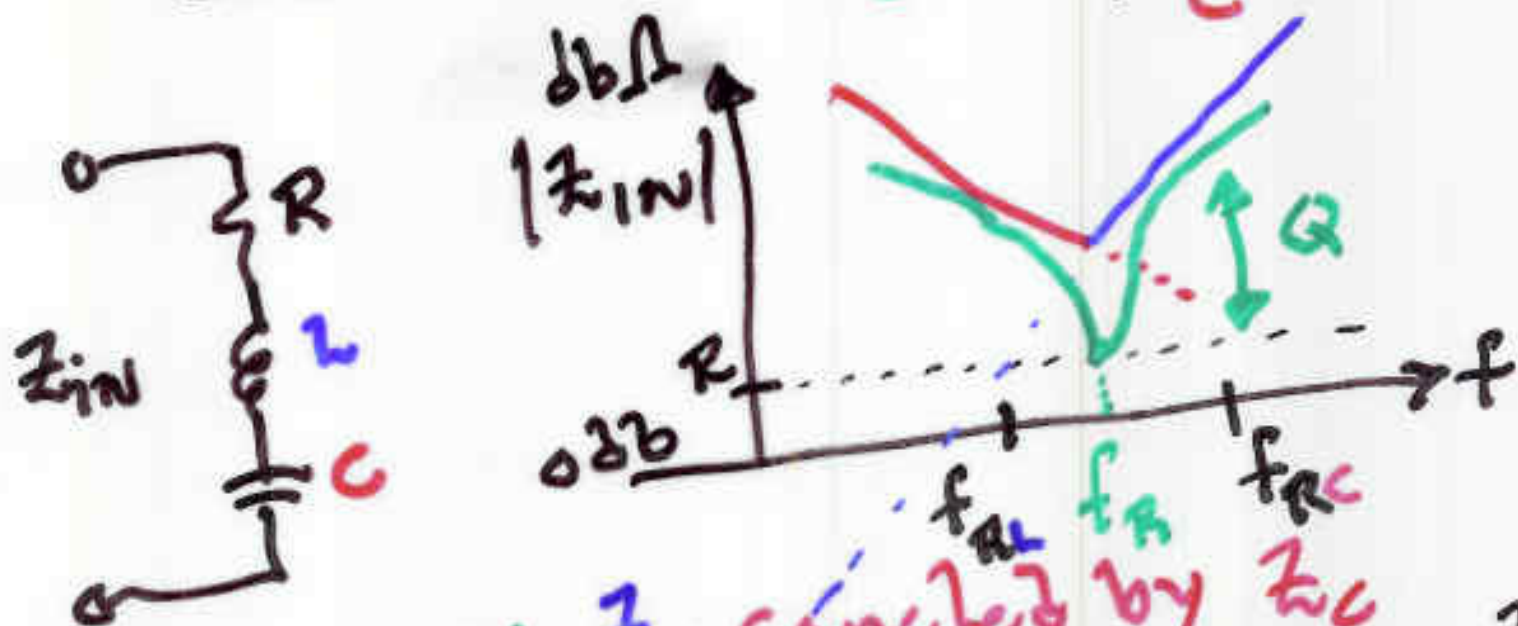Case: $R \ L \ Z_c \equiv \sqrt{\frac{L}{C}}$



Resonance: Z_L canceled by Z_C

$Q = \text{Deviation from asymptote @ } f_r$


$$Q = \frac{Z_c}{R}$$

$$Q(\omega) = Z_c(\omega) - R(\omega)$$

If Z_{in} "Q's" down $\downarrow$ then $i_{in}(t)$?



Resonant Buck

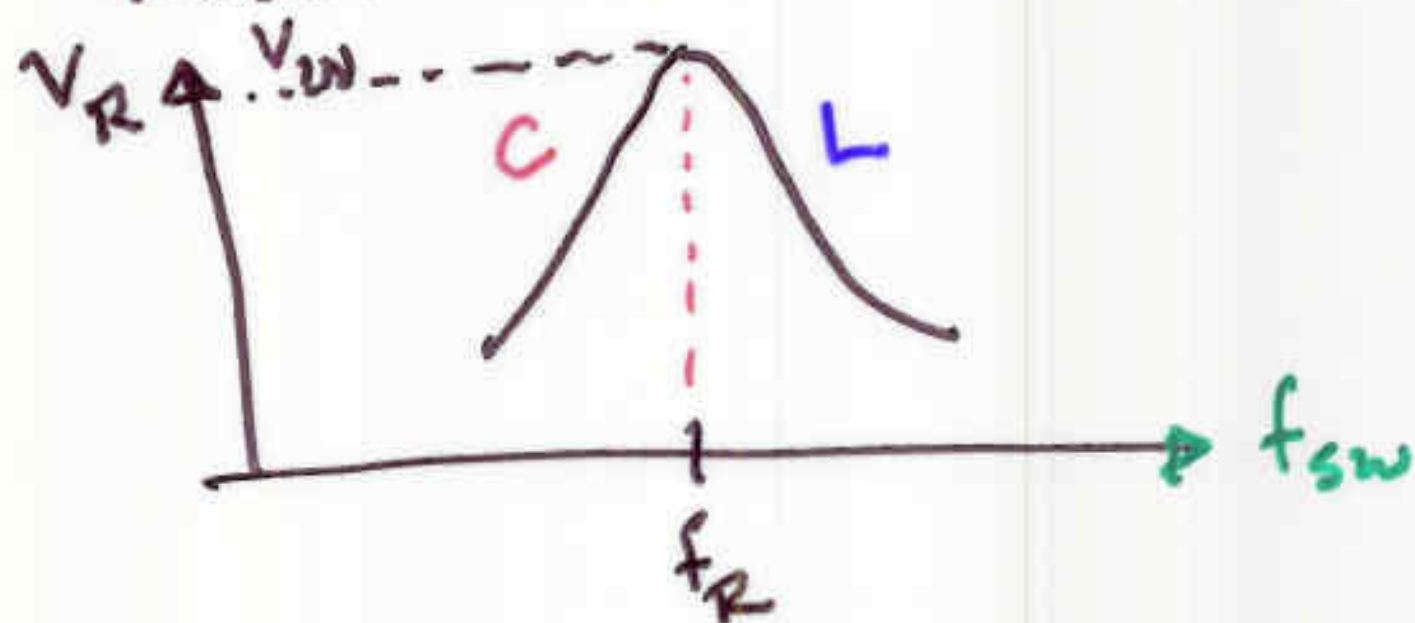

$$f_{sw} = f_R \quad V_R = V_{IN}$$

$$f_{sw} \neq f_R \quad V_R < V_{IN}$$

$f < f_R$: Capacitive BUCK



ZVS for FET

$f > f_R$: Inductive



ZCS for FET

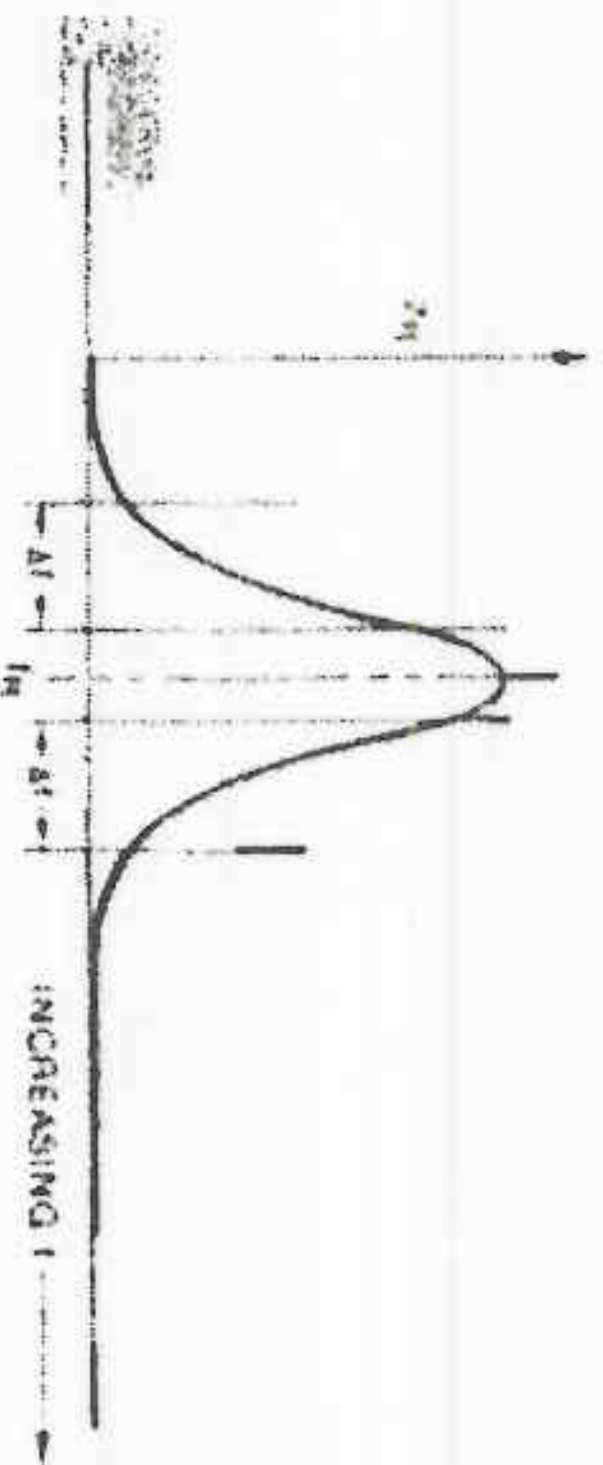
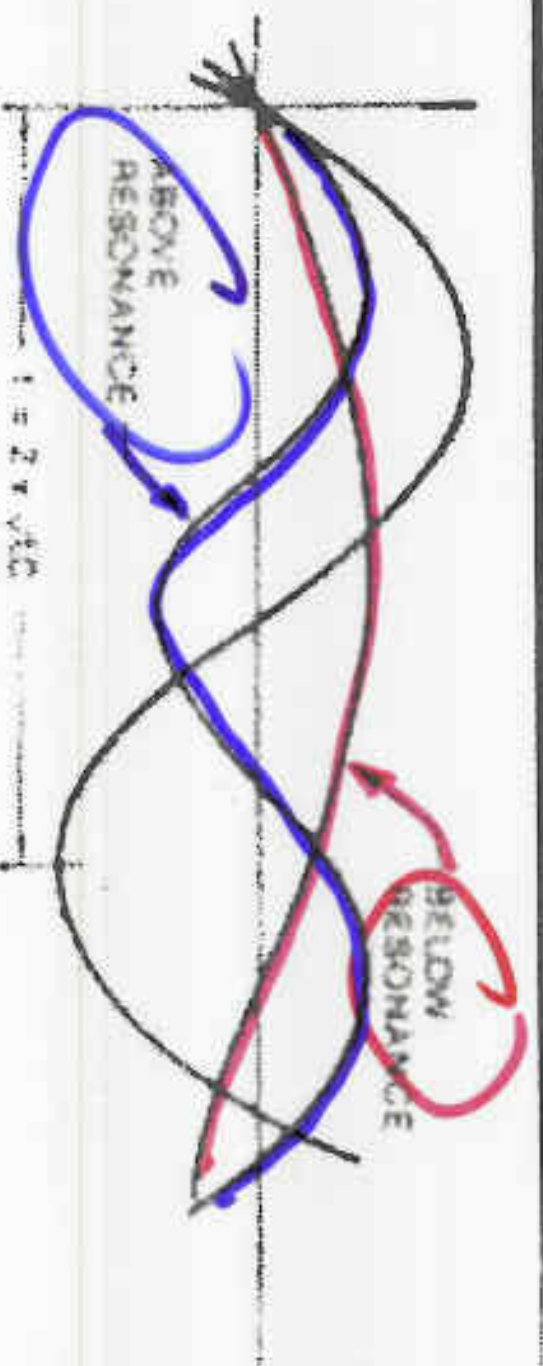


Fig. 11 - Variable Frequency Continuous Resonance

1. SERIES OR PARALLEL LOADED?
2. FIXED OR VARIABLE FREQUENCY?
3. CONTINUOUS / DISCONTINUOUS RESONANCE?
4. ZERO CURRENT OR VOLTAGE SWITCHING?
5. HALF OR FULL CYCLE CONDUCTION?

Fig. 8 - Classifying Resonant Converters

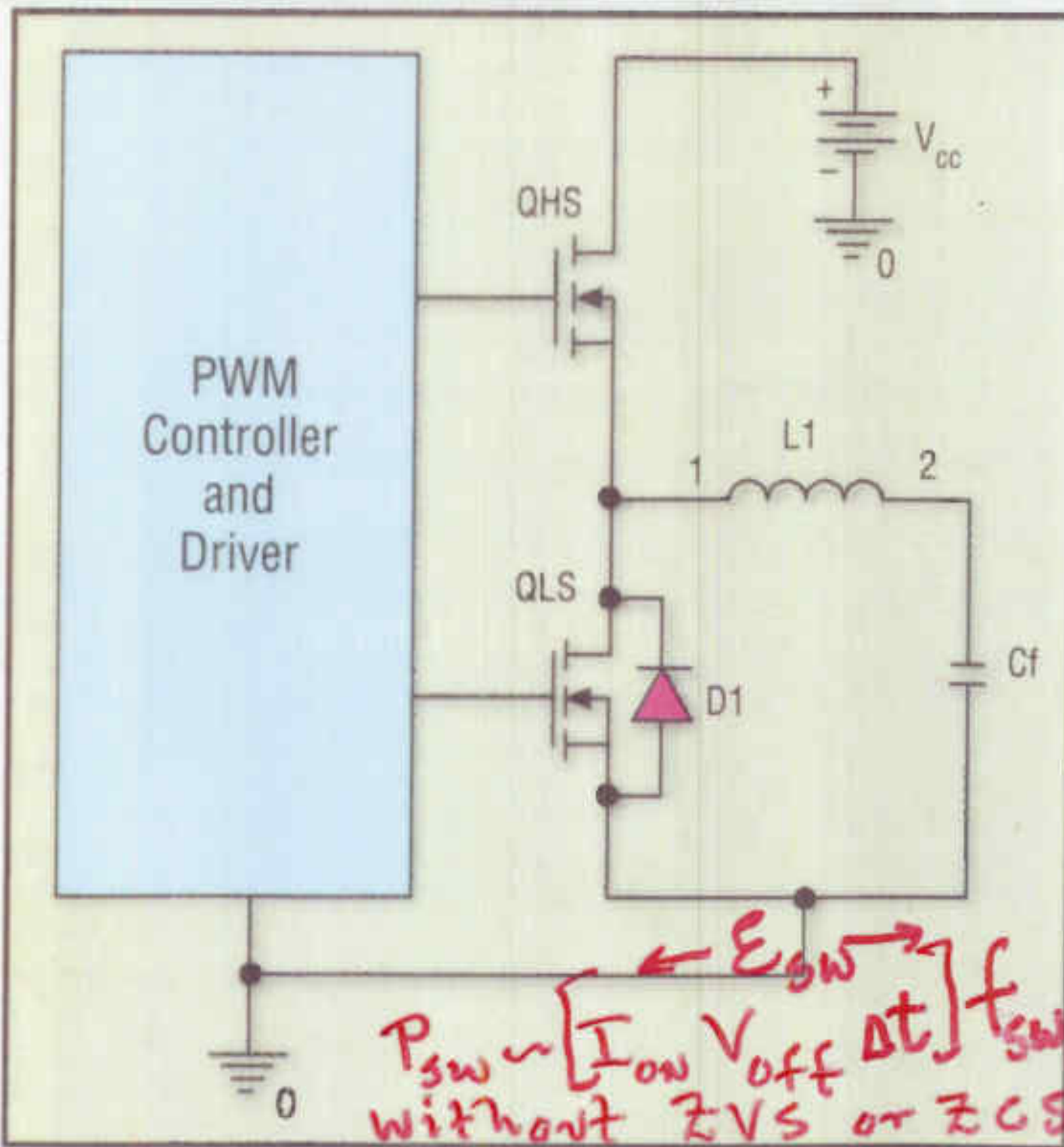


Fig. 1. The classical synchronous buck converter uses two switching MOSFETs: the high-side (control) device, QHS, and the low-side synchronous rectifier, QLS.

5 to 20 kHz	-AUDIBLE NOISE -SLOW BIPOLAR SWITCHES -LARGE L's AND C's
20 to 100 kHz	-ABOVE AUDIBLE RANGE -FAST BIPOLAR TRANSISTOR -MAGNETICS BECOME IMPORTANT -SMALL SIZES
100 to 500 kHz	-POWER MOSFET SWITCHES -LOSSES IN L's AND C's -DIODE RECOVERY TIME -RFI AND EMI -PACKAGING PROBLEMS

Fig. 2 - Power Supply Switching Frequencies

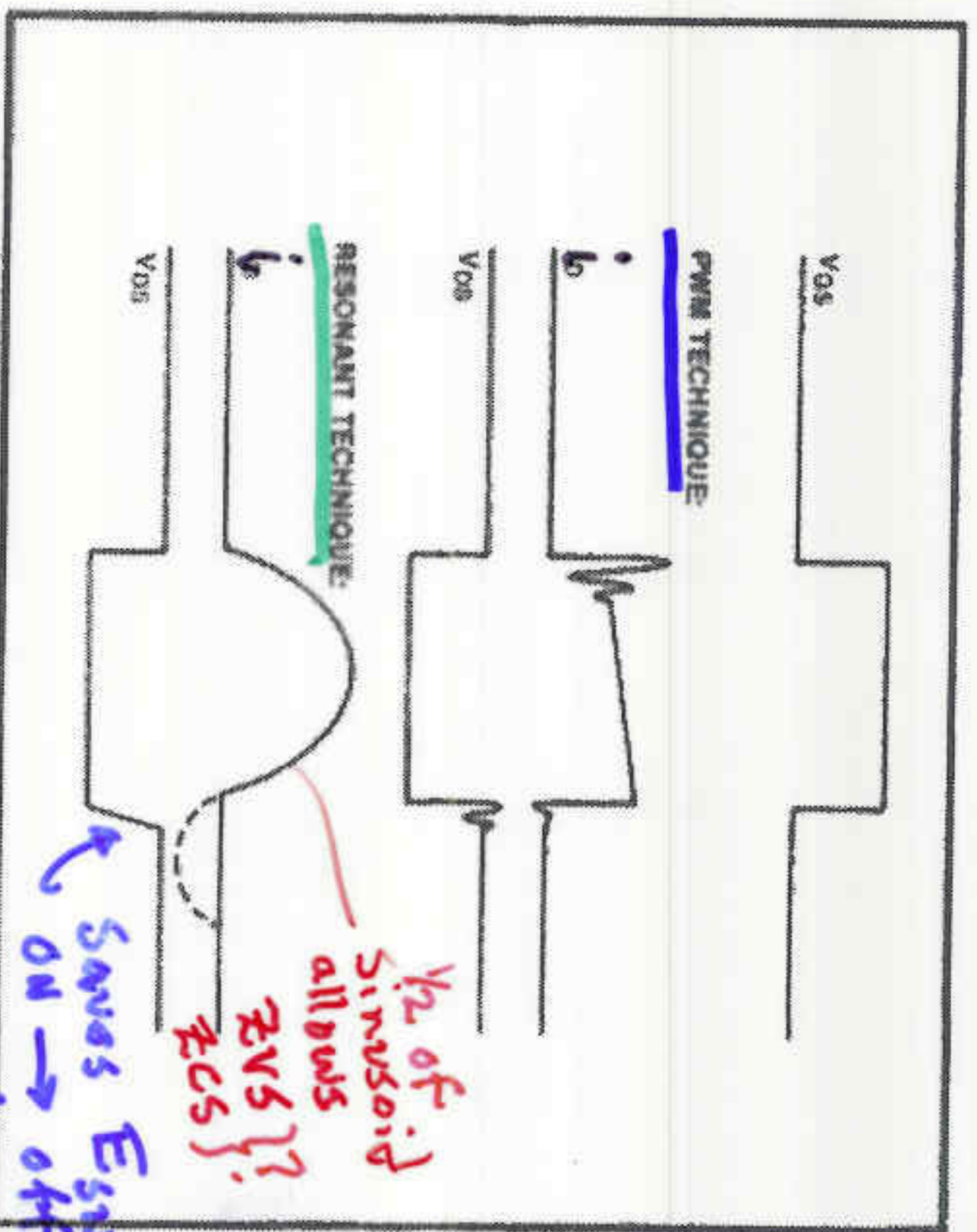


Fig. 5 - PWM vs. Resonant Switching