

R_L Q dependence varies with each circuit

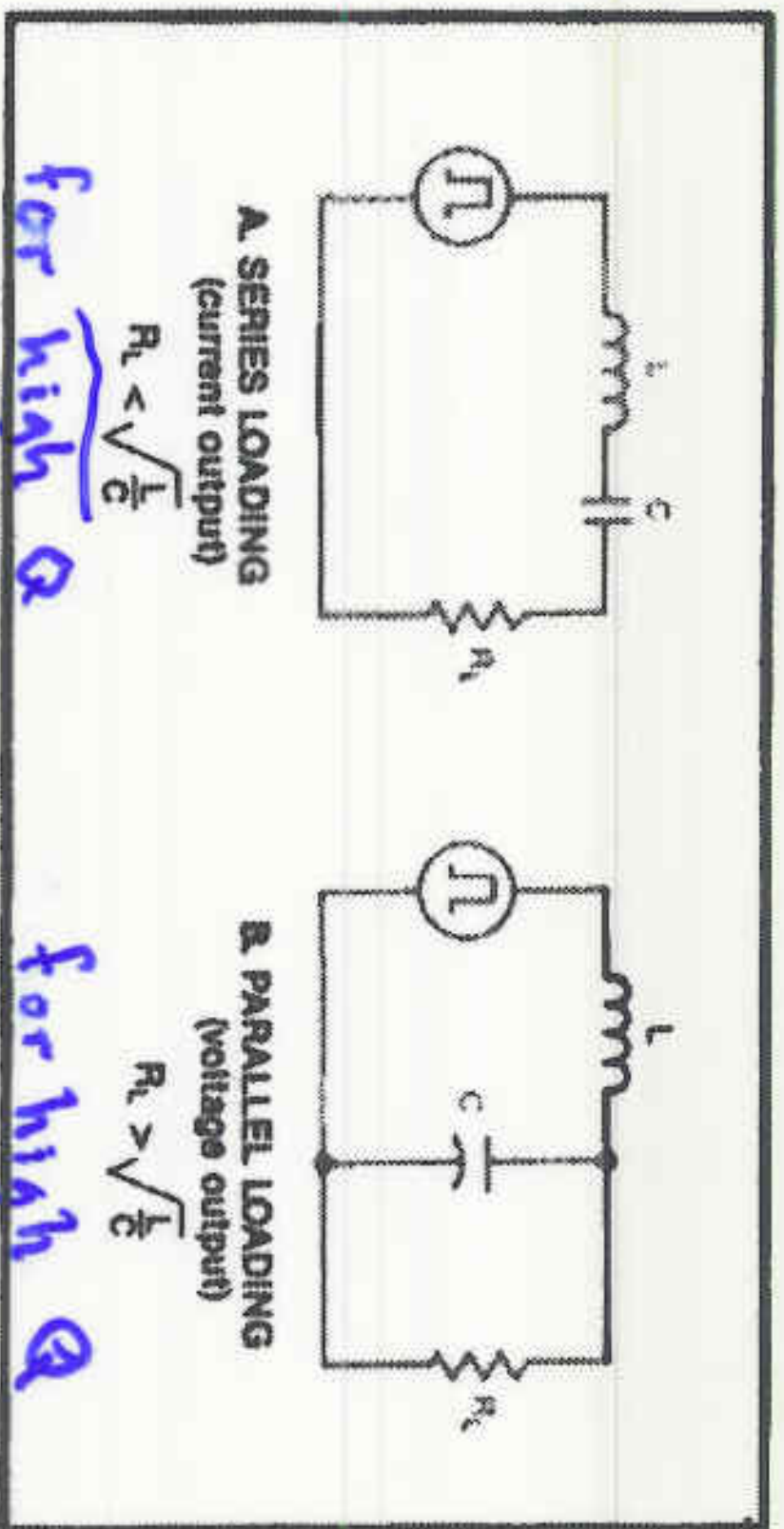


Fig. 9 - Resonant Mode Loading


$Q(\text{series}) = \frac{Z_0}{R}$

$R \downarrow \Rightarrow Q \uparrow$

$Q(\text{parallel}) = \frac{R}{Z_0}$

$R \uparrow \Rightarrow Q \uparrow$

Superior
P.P.M.
19.1

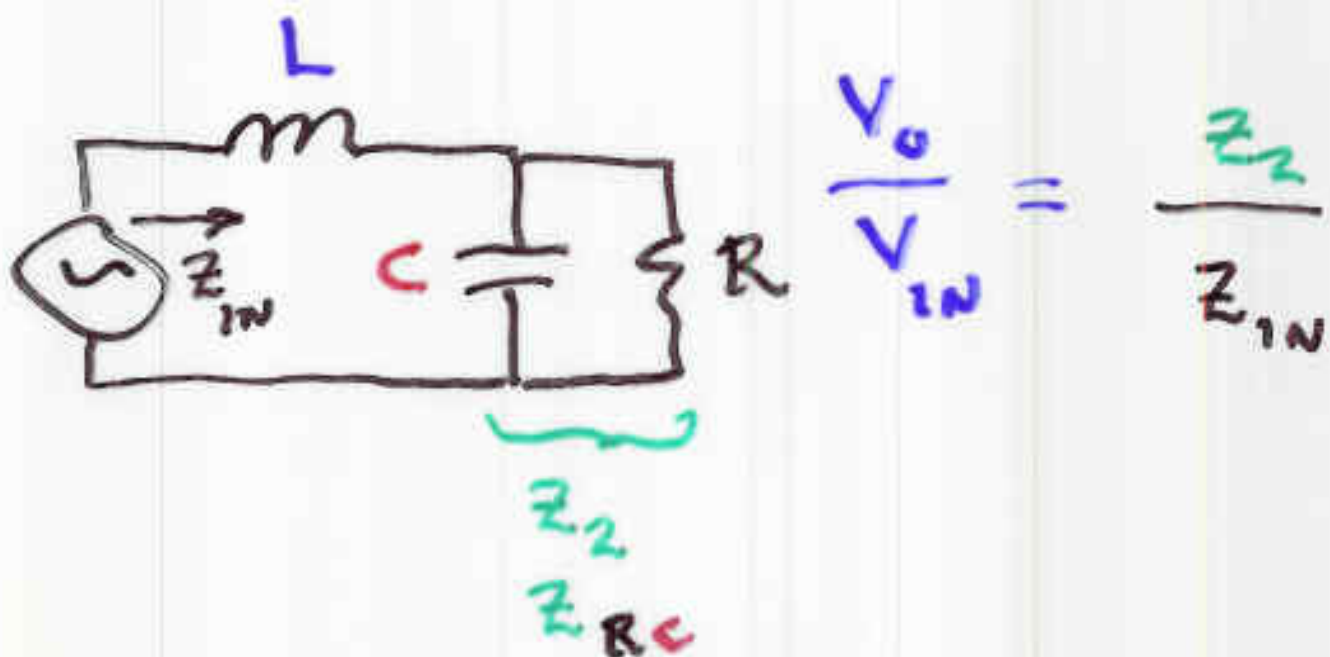

Do the $\frac{V_O}{V_i}$ again with
Same $R > Z_c = \sqrt{\frac{L}{C}}$


Same $f_{RC} < f_{LC} < f_{RL}$

1st plot $R || Z_c$ vs f

plot $Z_{IN}(f)$

Divide $\frac{Z_2}{Z_{IN}}$

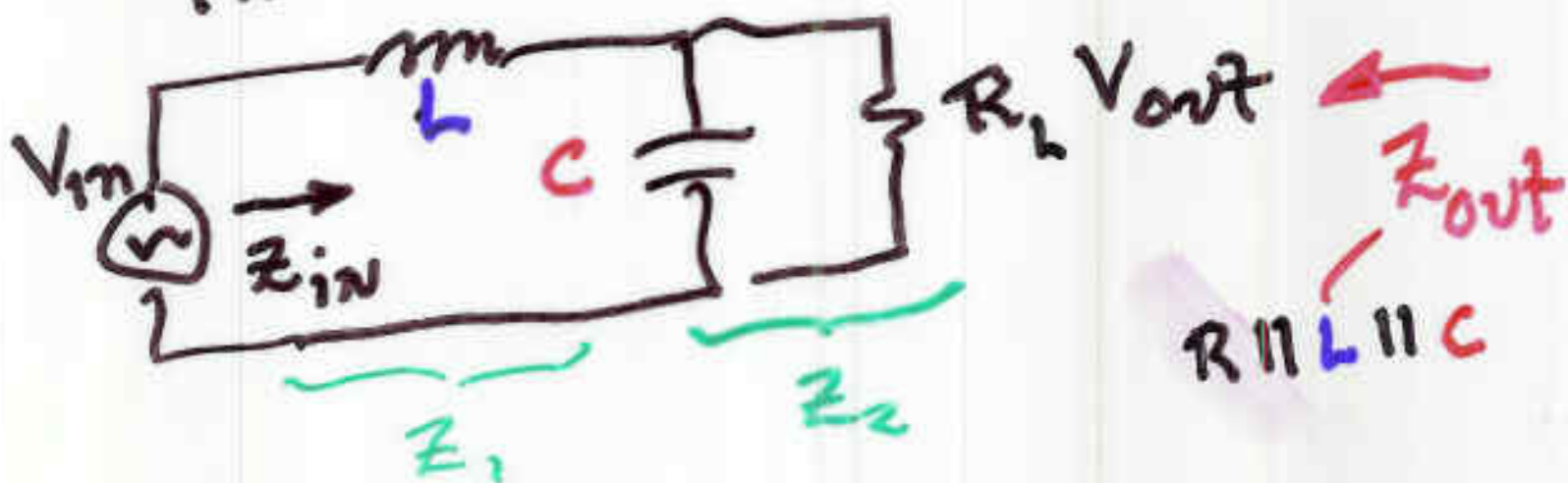Voltage Divider for Load across C } Call it a parallel res
in a series resonant circuit




$$\frac{V_o}{V_i} = \frac{Z_2}{Z_1 + Z_2} = \frac{Z_2}{Z_{in}}$$

$$= Z_1 \frac{Z_2}{Z_1 + Z_2} \quad \frac{1}{Z_1} = \frac{Z_{out}}{Z_1}$$

Recognize Z_{out} is 

Take the case $R > Z_C$


$\Rightarrow$ hierarchy of frequencies

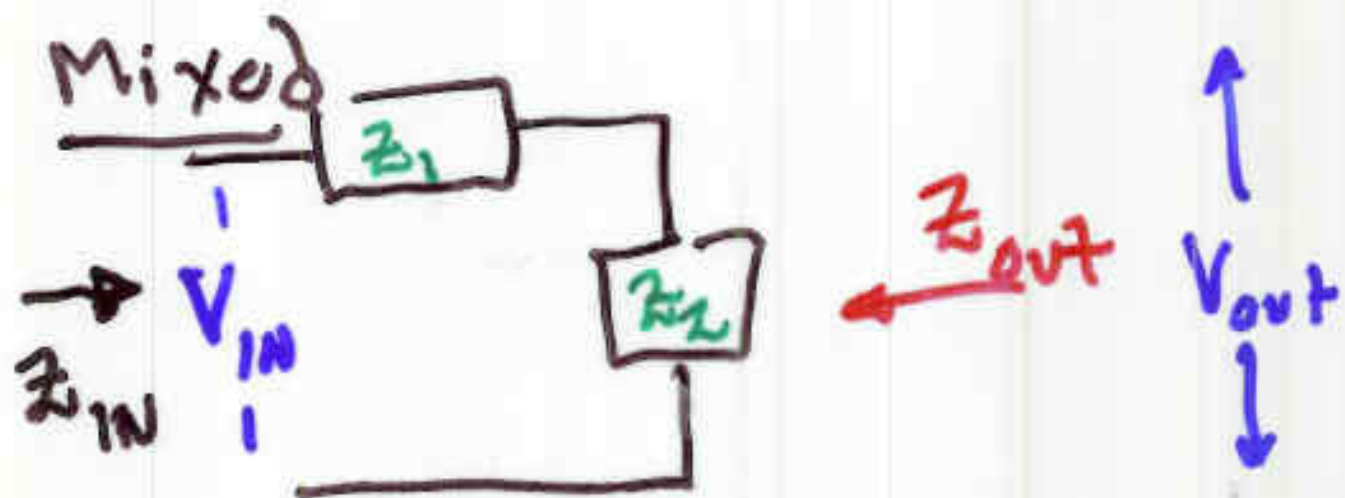

$$Z_{IN} = Z_1 + Z_2, \quad Z_{OUT} = Z_1 \parallel Z_2 = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$\frac{V_O}{V_{IN}} = \frac{Z_2}{Z_1 + Z_2} = \frac{Z_2}{Z_{IN}} = \frac{Z_{OUT}}{Z_1}$$

Choose easier one Z_{OUT}

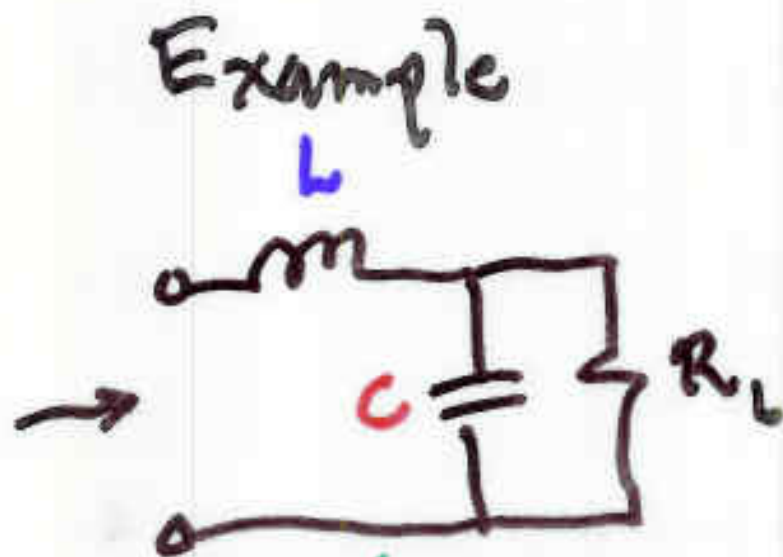

$$\frac{V_o}{V_i} = \frac{L \parallel C \parallel R}{\omega L}$$

$$Z_1 = \omega L, \quad Z_{OUT} = R \parallel L \parallel C$$

Consider the cases in Z_{out}


$$f_1 = \frac{1}{2\pi RC} \text{ is lowest} = f_{RC}$$

$$f_2 = \frac{1}{2\pi\sqrt{LC}} \text{ middle} = f_{LC}$$

$$f_3 = \frac{R}{2\pi L} \text{ highest} = f_{RL}$$


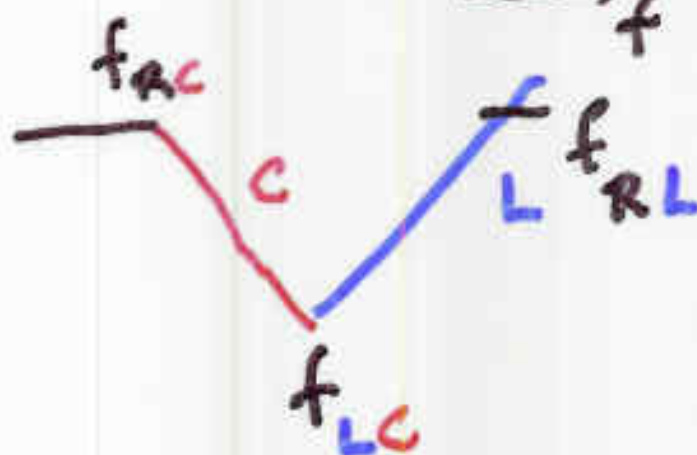
$$\frac{V_o}{V_{in}} = \frac{Z_{out}}{Z_1} = \frac{R \parallel Z_2 \parallel Z_C}{Z_L}$$



Compare $z_i(f)$



$$f < f_{LC} \quad z_i(R \text{ large}) > z_i(R=0)$$

$$i_{IN}(R=0) > i_{IN}(R=\infty)$$


$$f > f_{RL}$$

z_{IN} same for
 $R=0$ or R large

$$f < f_{LC} < f_{RL} ?$$

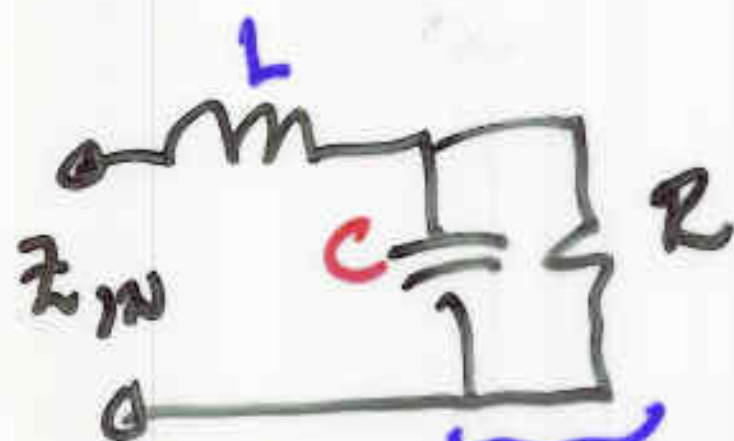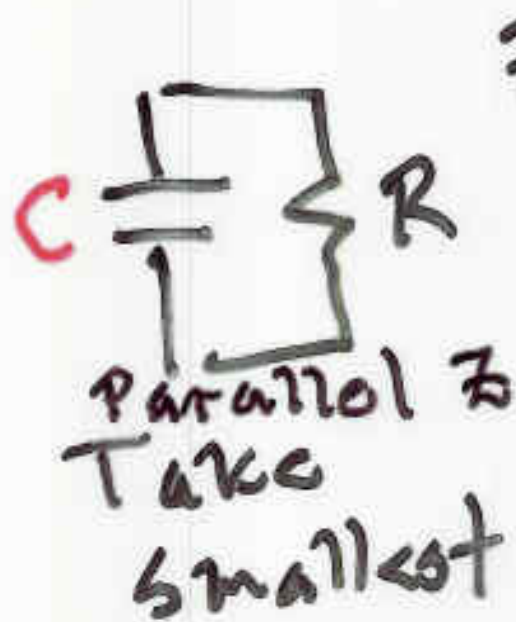


Add L in
Series
take largest

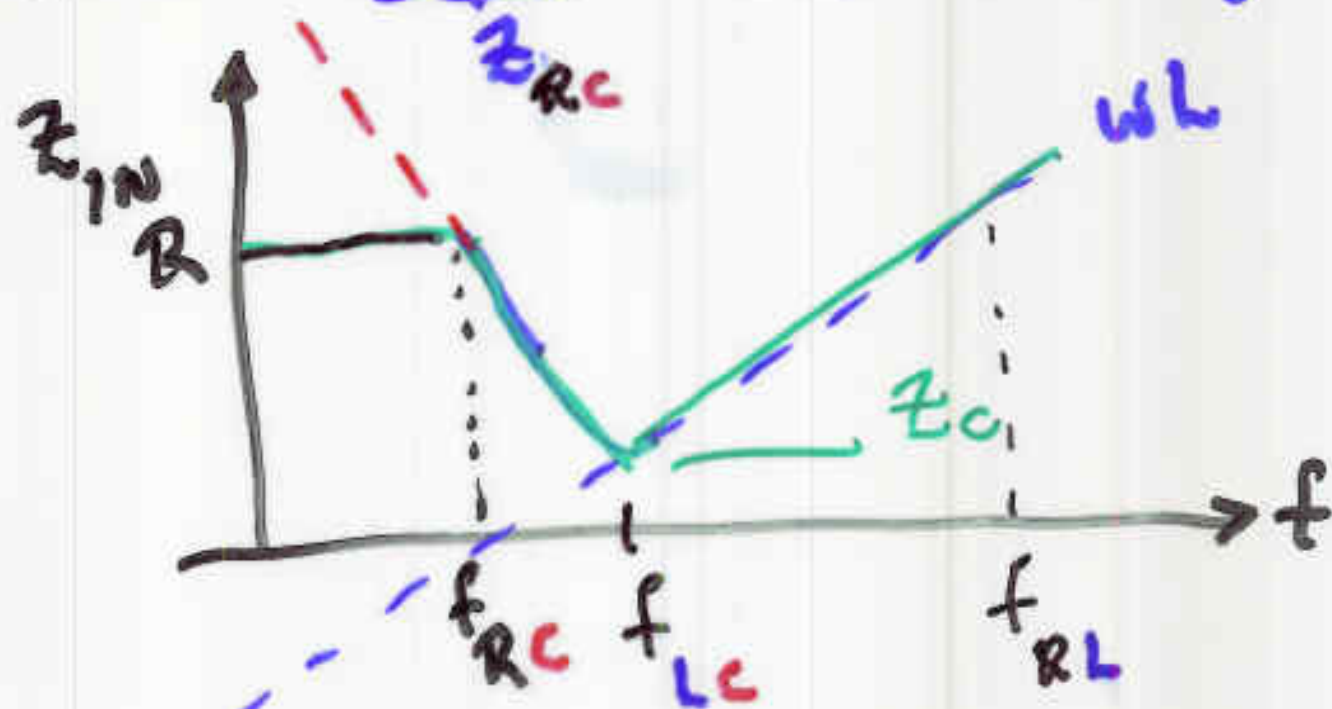

$$\frac{V_o}{V_{in}} = \frac{Z_L}{Z_{in}}$$



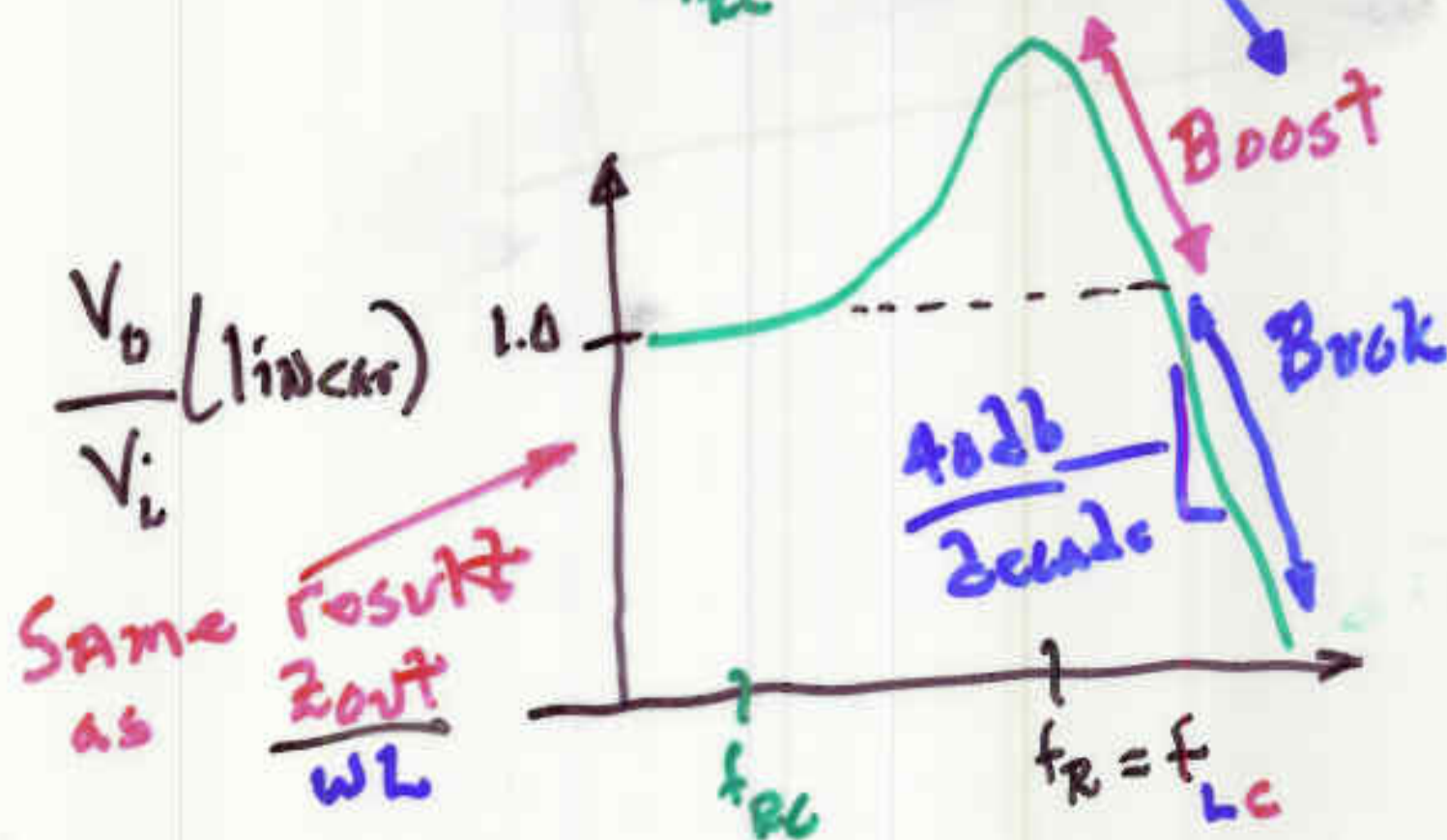
$$\frac{V_o}{V_i} = \frac{\frac{1}{\omega C} \parallel R}{\omega L + \frac{1}{\omega C} \parallel R}$$




For boost action: $\frac{R}{Z_0} \gg 1$
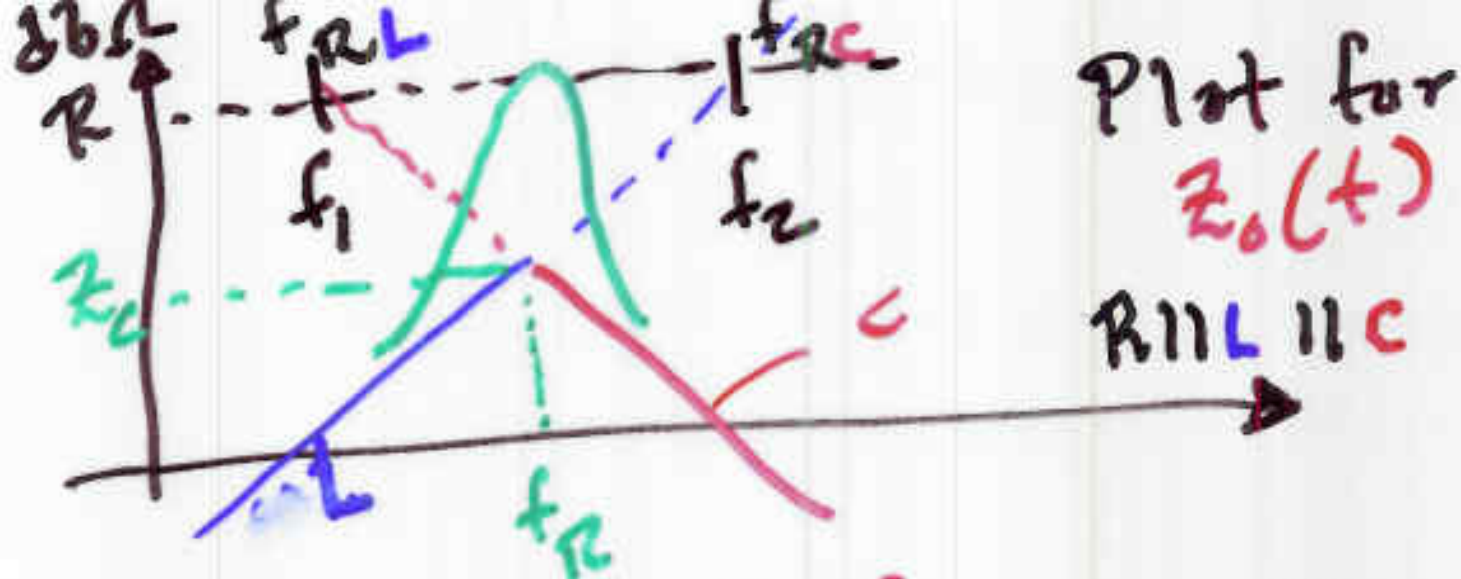
$$Z_0 = \sqrt{\frac{L}{C}} \text{ Choices } \dots \omega_R = \frac{1}{\sqrt{LC}}$$





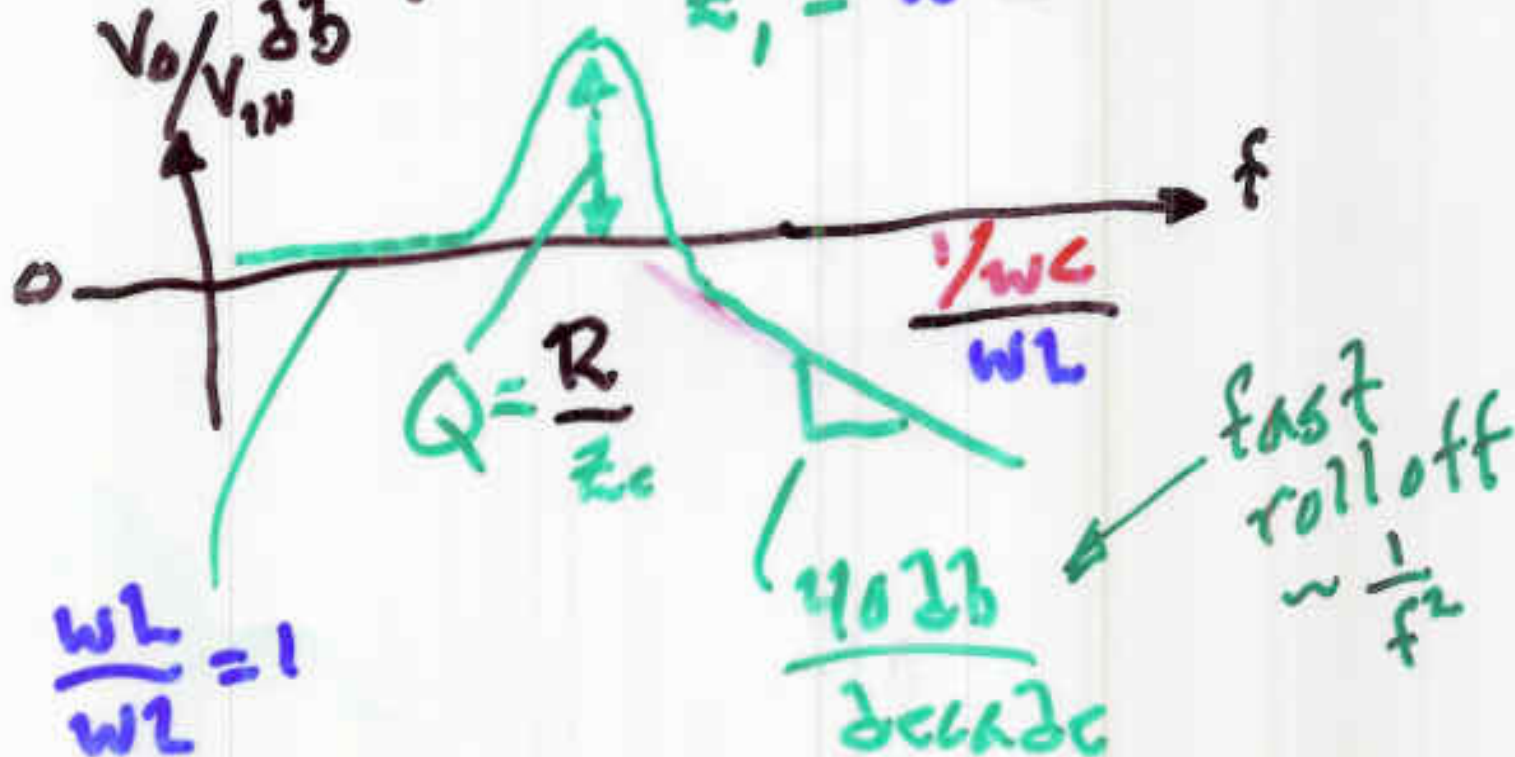
Next plot: $\frac{V_{out}}{V_{in}}$ unitless in dB




Note: V_{out} "Q's up" @ f_R
 V_{R-C} has peak vs f
 Use ? lighting other

$$Z(R||L||C) = Z_{out} \text{ for } Z_0 < R$$

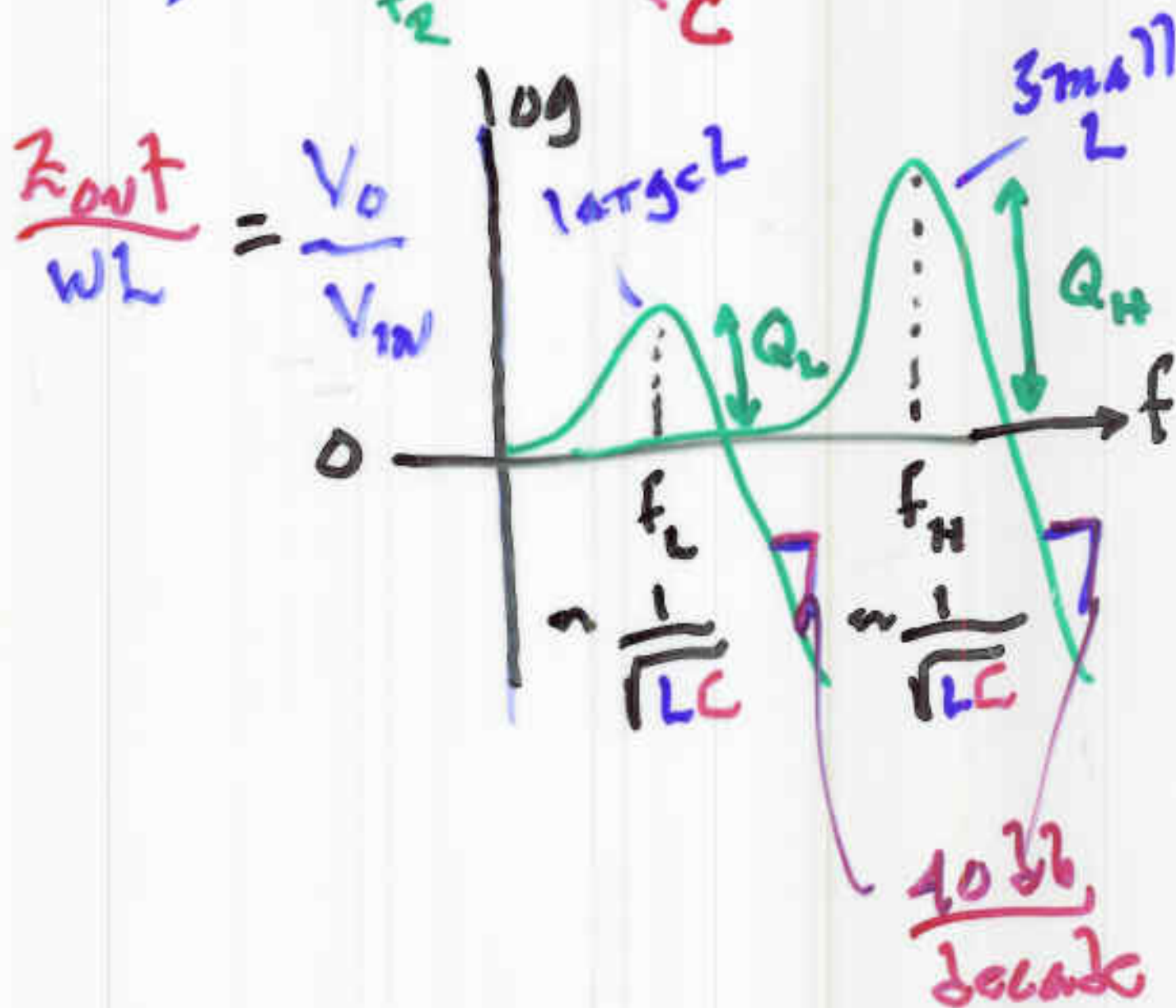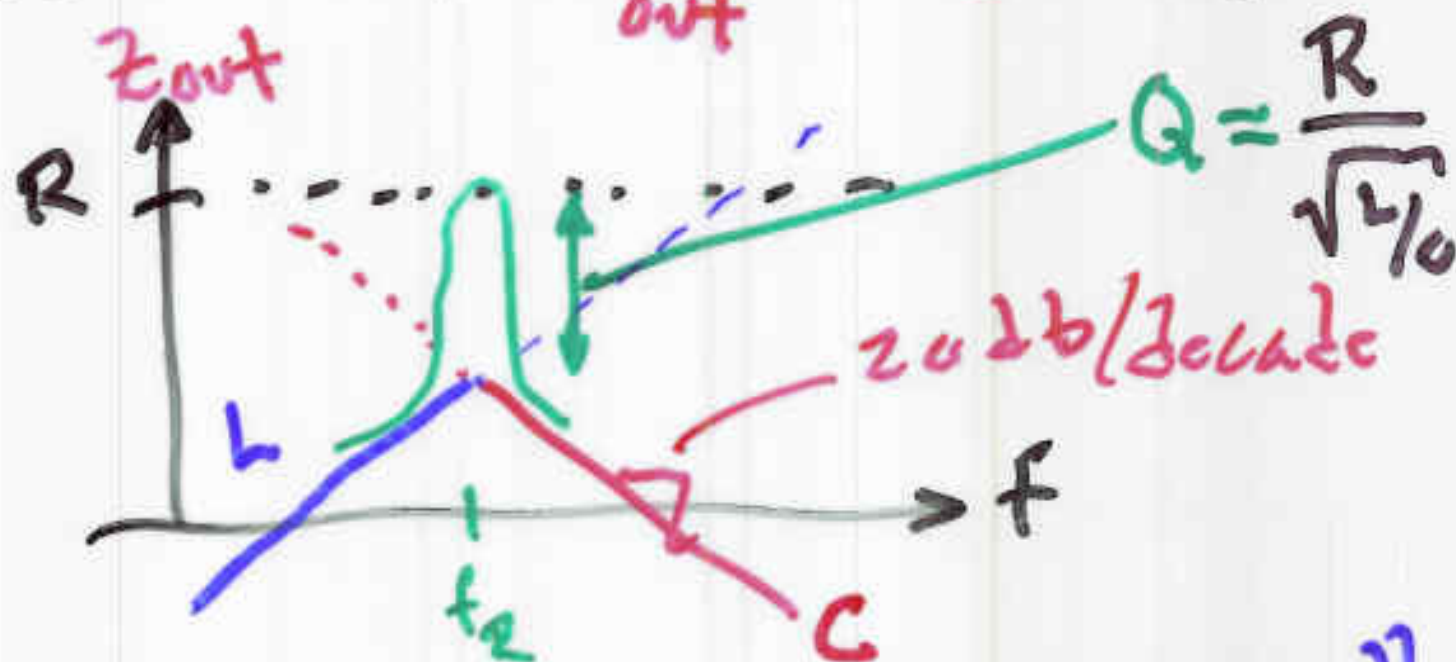

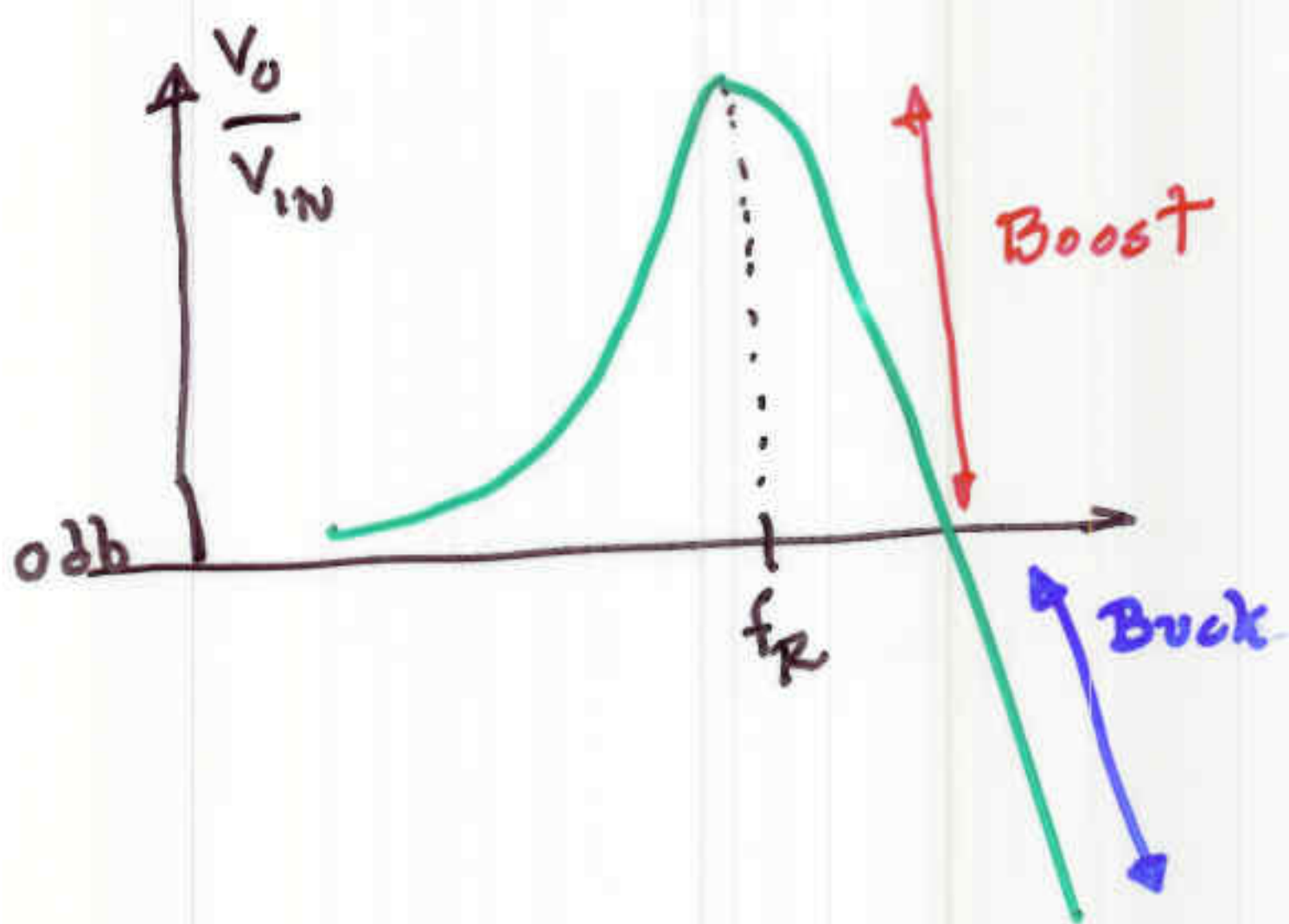

Add a transformer

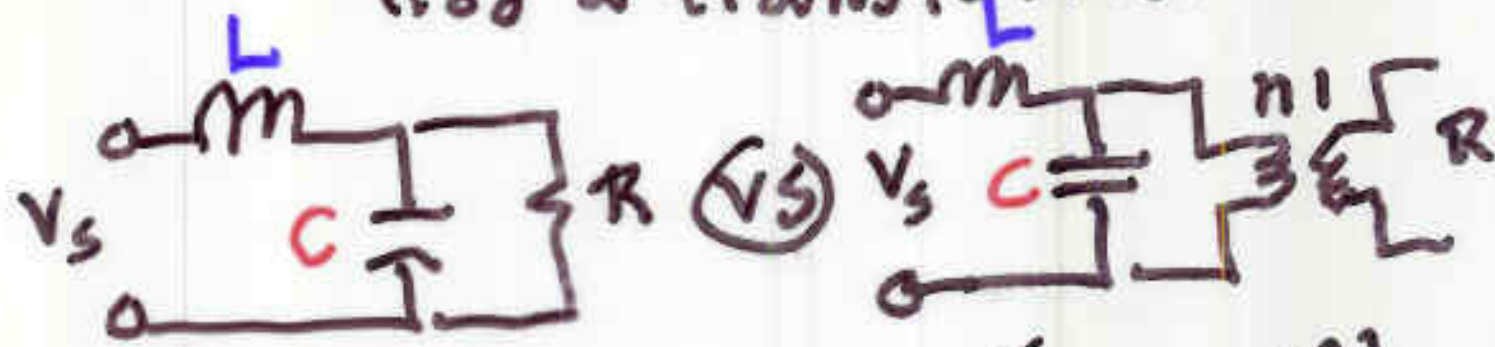

move all
to
secondary




$$f_{LC} = \frac{1}{\sqrt{LC}} \quad n^2 \text{ cancels}$$

BUT

Q is enhanced!

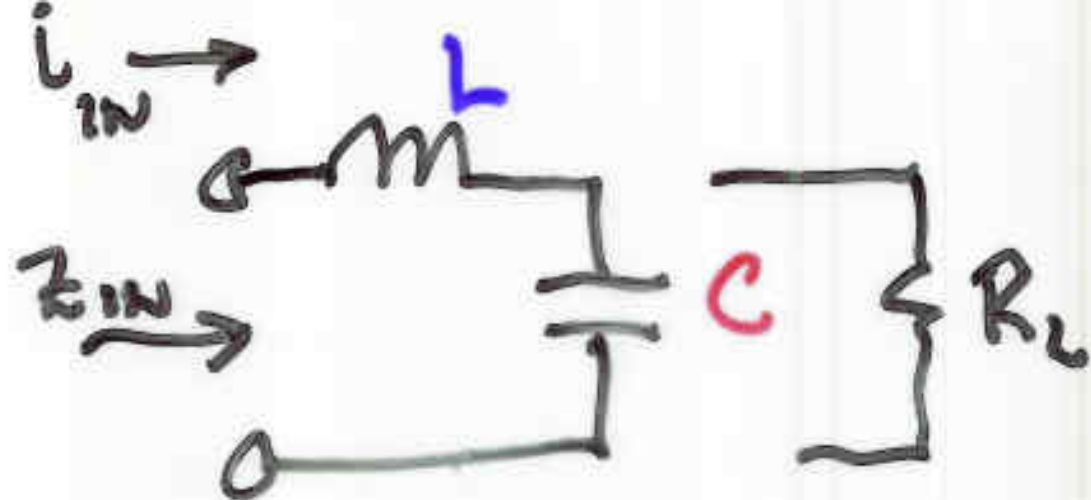
$$Q = \frac{R}{\sqrt{\frac{L_{\text{eff}}}{C_{\text{eff}}}}} = n^2 \frac{R}{\sqrt{\frac{L}{C}}}$$



When is i_{IN} a maximum?
 for sinusoidal V_{IN} ?
 $i_L(\max) R_L = ?$

Consider extremes: $R_L = 0$
 $R_L = \infty$


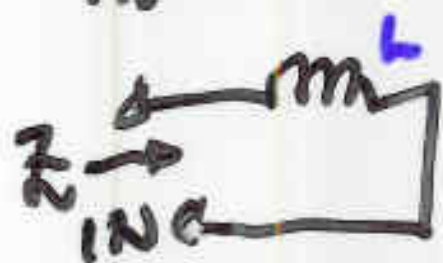
$Z_{IN}(R_L = \infty)$ vs $Z_{IN}(R_L = 0)$



$Z_{IN}(f = f_R)$

$Z_{IN}(f = f_R)$

Which is smaller?

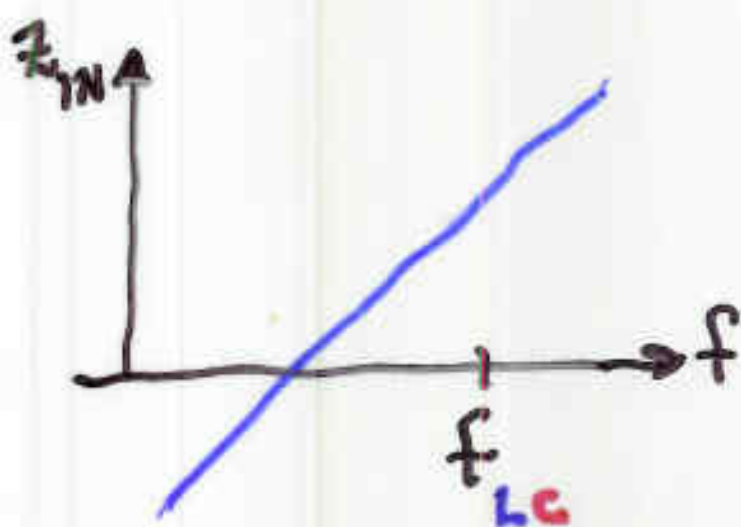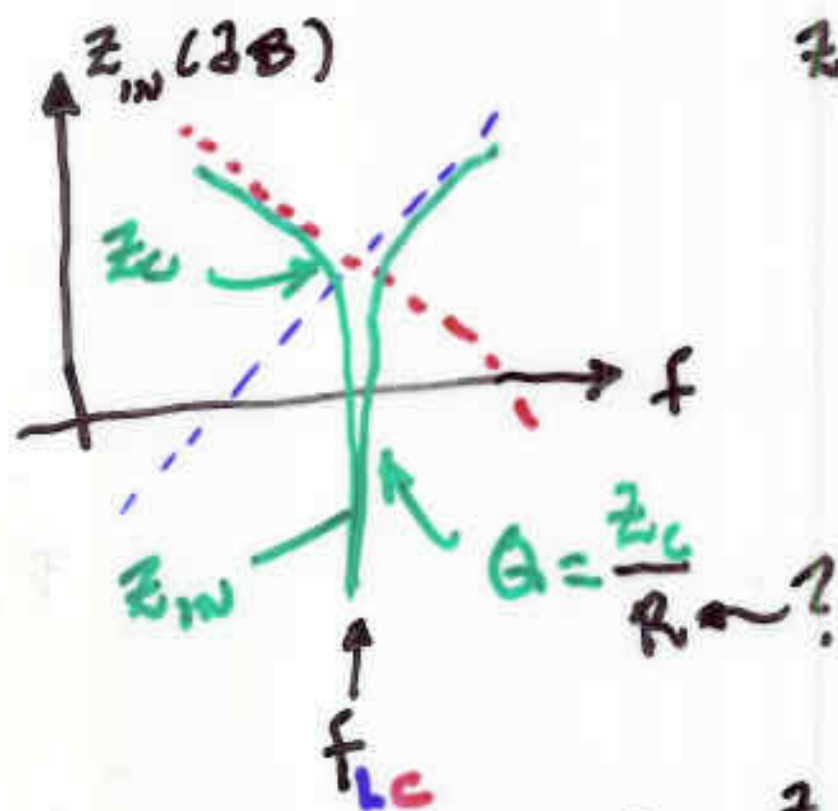


For below resonance: $f < f_{LC}$: $Z_{IN}(R=0) \leq Z_{IN}(R=\infty) \Rightarrow I_{IN}(R=0) > I_{IN}(R=\infty)$

above f_R : $f > f_{LC}$: $Z_{IN}(R=0) \approx Z_{IN}(R=\infty)$ same I_{IN}

$f = f_{LC}$ which is lower Z_{IN} higher I_{IN}

Doing data ERC

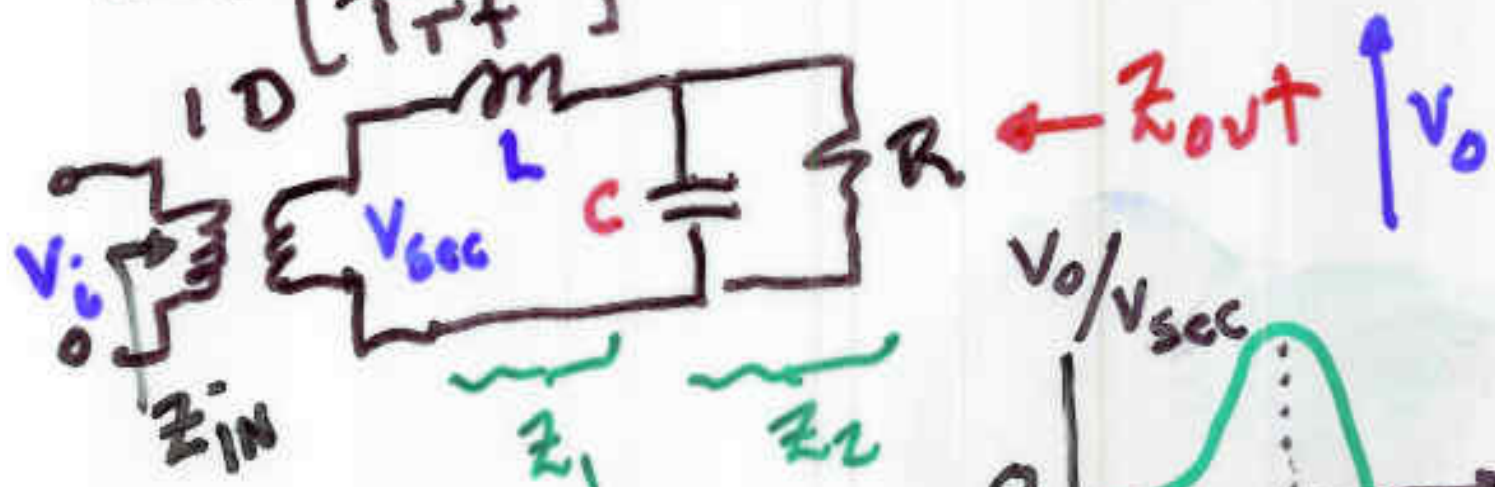Add $\left[\frac{P, W, M}{1, r, f}\right]$ effects $V_{sec} = D V_i$



$$\frac{V_o}{V_i} = \left[\frac{Z_{out}}{Z_1} \right] D$$

$\frac{V_o}{V_{sec}}$



But what are D effects

Careful:

@ V_i $Z_{in} = \frac{1}{D^2} [Z_1 + Z_2]$

@ V_o $Z_{out} = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{Z_1 Z_2}{D^2 Z_{in}}$

$$Z_{in} = \frac{1}{D^2} \frac{Z_1 Z_2}{Z_{out}}$$

D^2 effects
cancel

Evaluate $Z_{in}(f) @ v_i$


① $f = f_R$

$Z_{out} = R$


Z_1 and Z_2 both are
 $Z_0 = \sqrt{L/C}$


$Z_{in}(f_R) = \frac{Z_0^2}{D^2 R}$
 @ v_i

② $f \ll f_R$

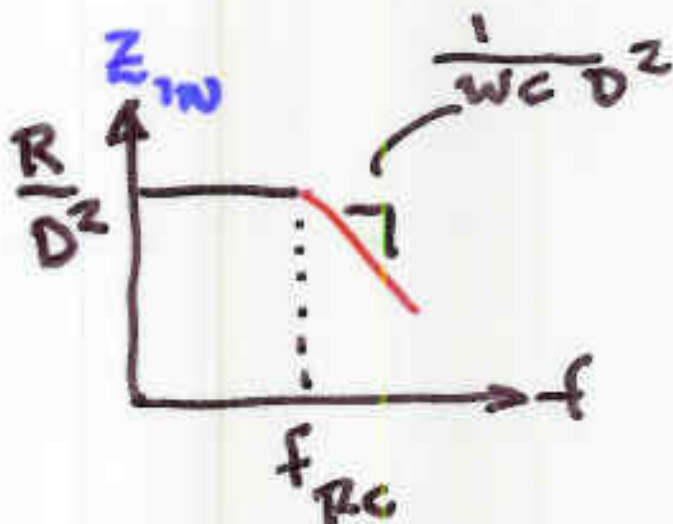


③ $f \gg f_R$

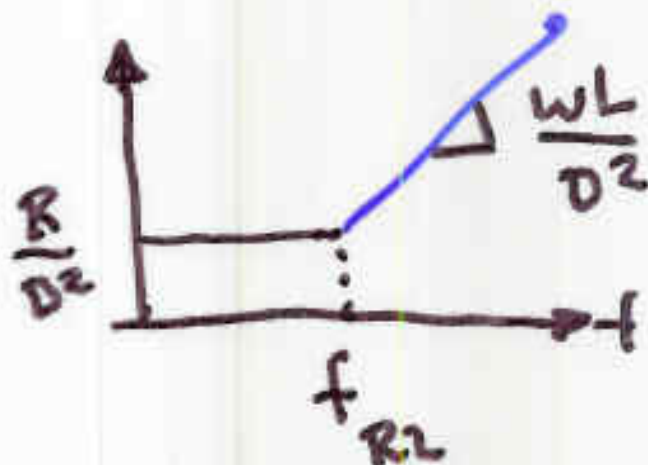

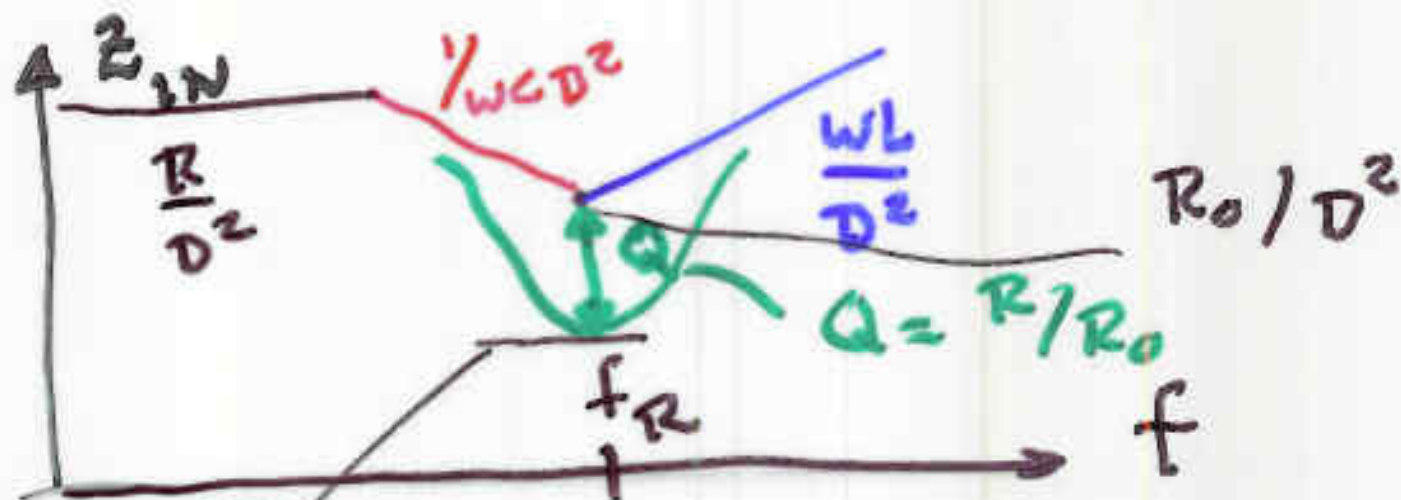

$$\left(\frac{R_0^2}{D^2 R} \right)$$

Z_{IN} has D^2 effects
for $f \neq f_R$

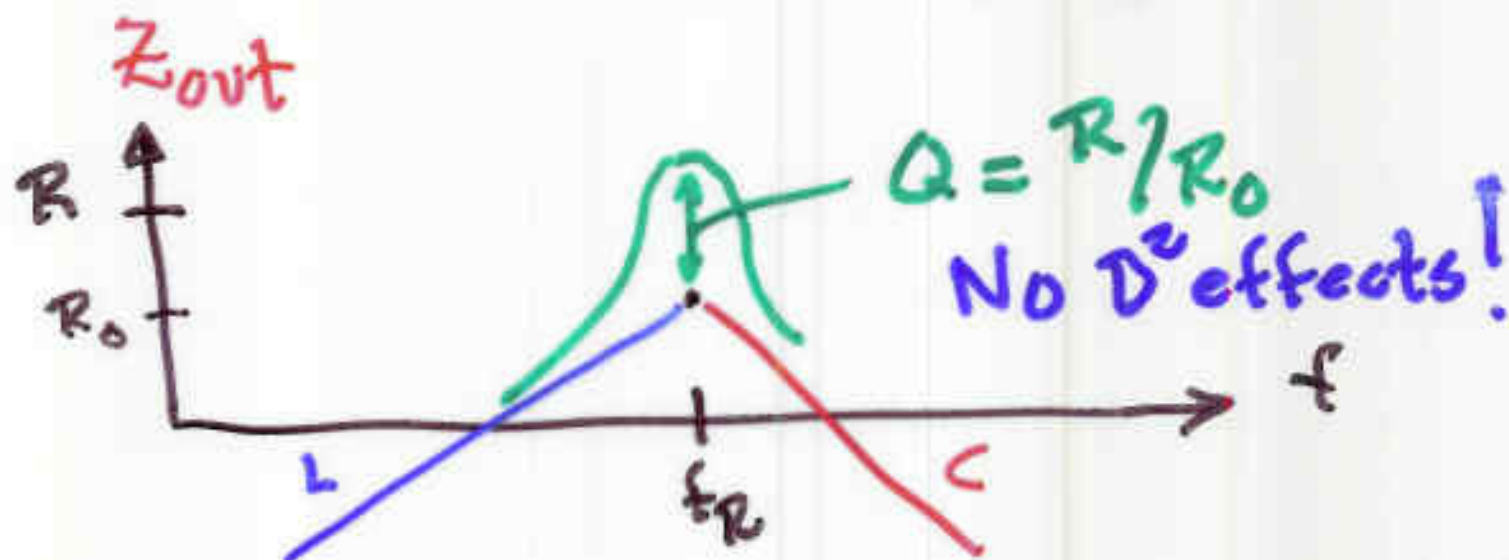

$$\frac{V_{out}}{V_{in}} = \frac{Z_{out}}{wL}$$

