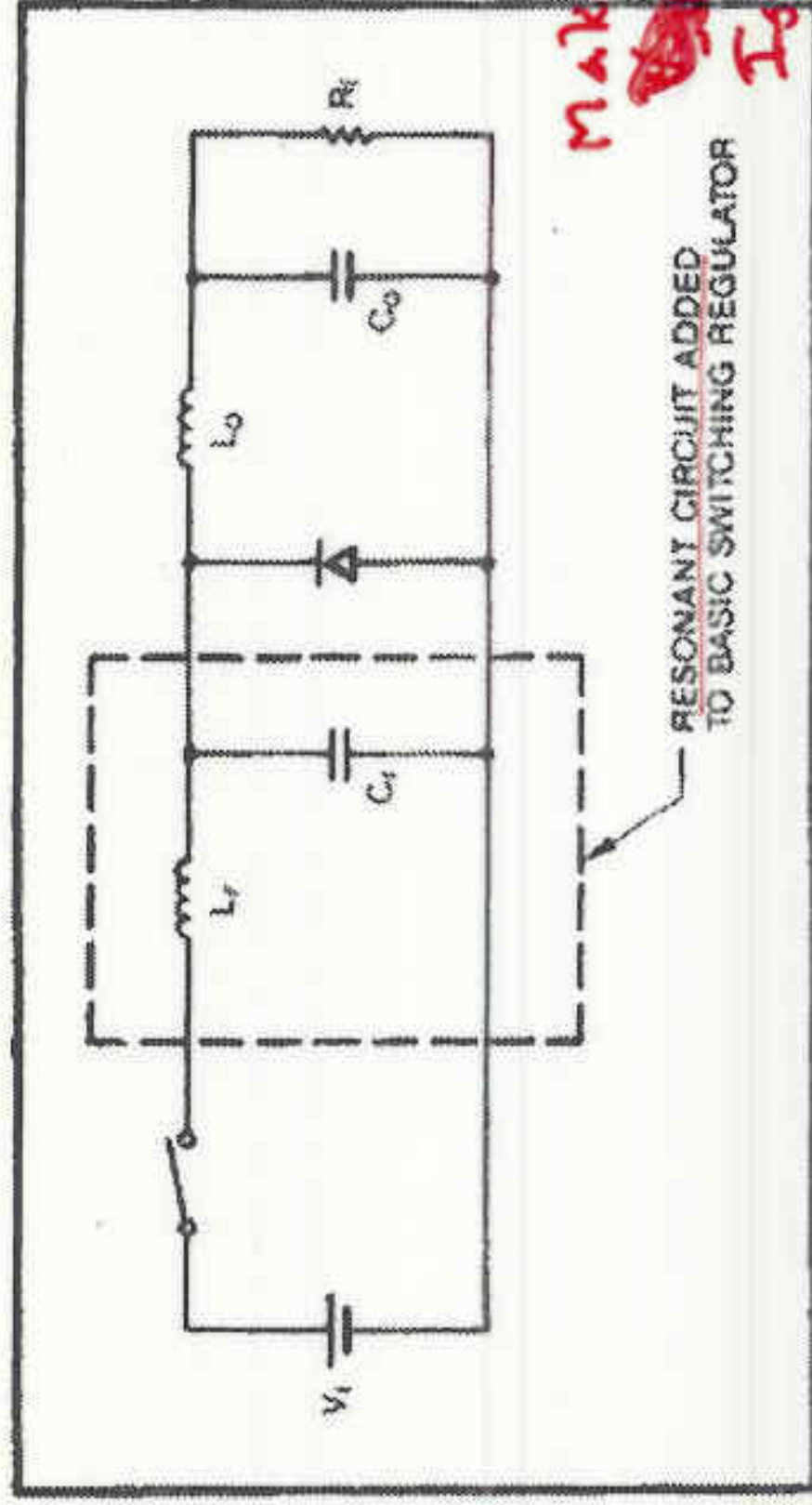




Makes ~~only~~ only

I_{sw}

Fig. 3 - Basic Resonant Converter

sinusoidal

vs

V_{sw} still $\rightarrow$ square-wave

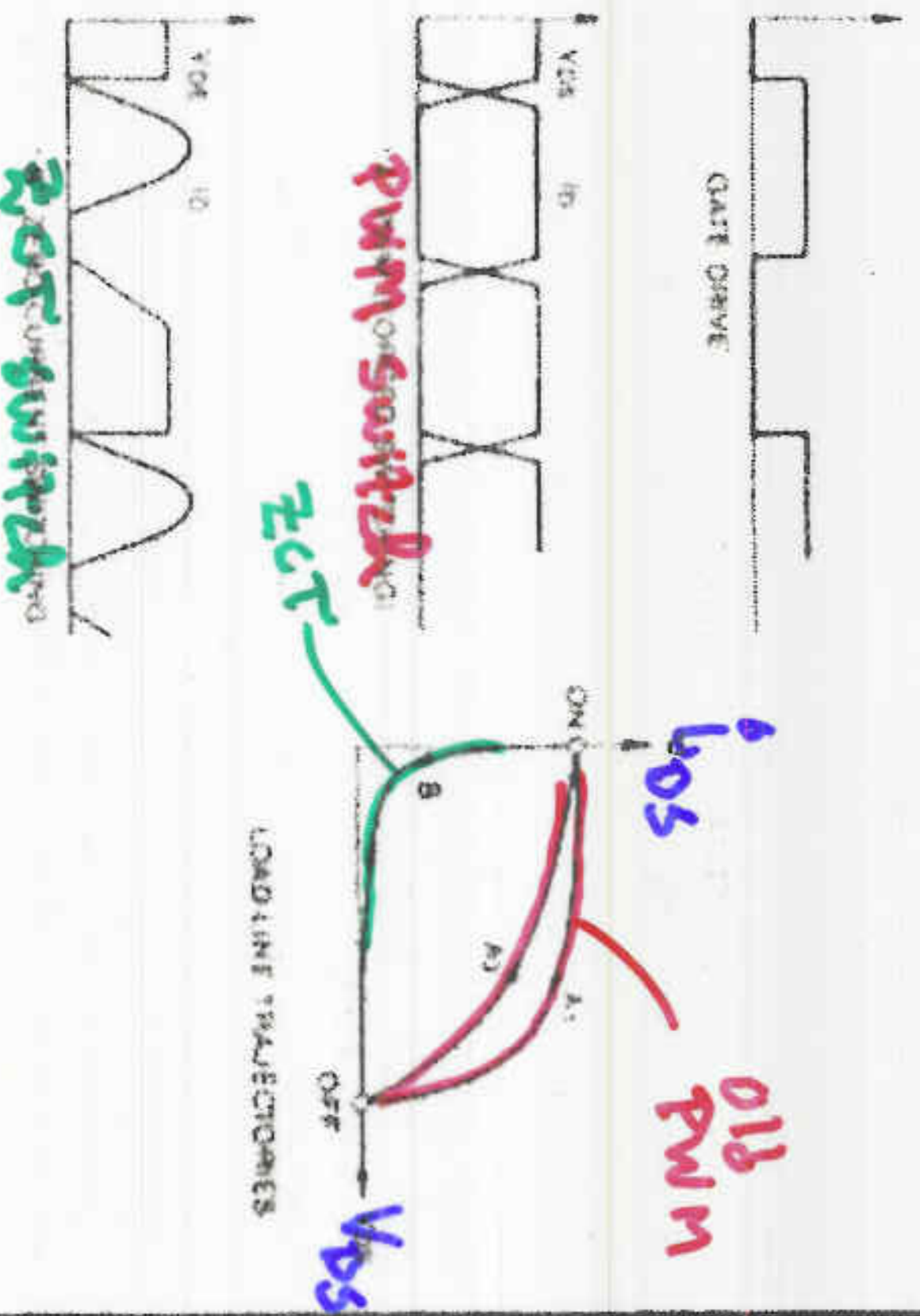


Fig. 6 - Switching Stress and Switching Loss



ZERO CURRENT

for when the
filling / emptying
limits Δu loss



ZERO VOLTAGE

for when C_{ds}
charging / discharging
limits Δu loss

Fig. 7 - Resonant Switches

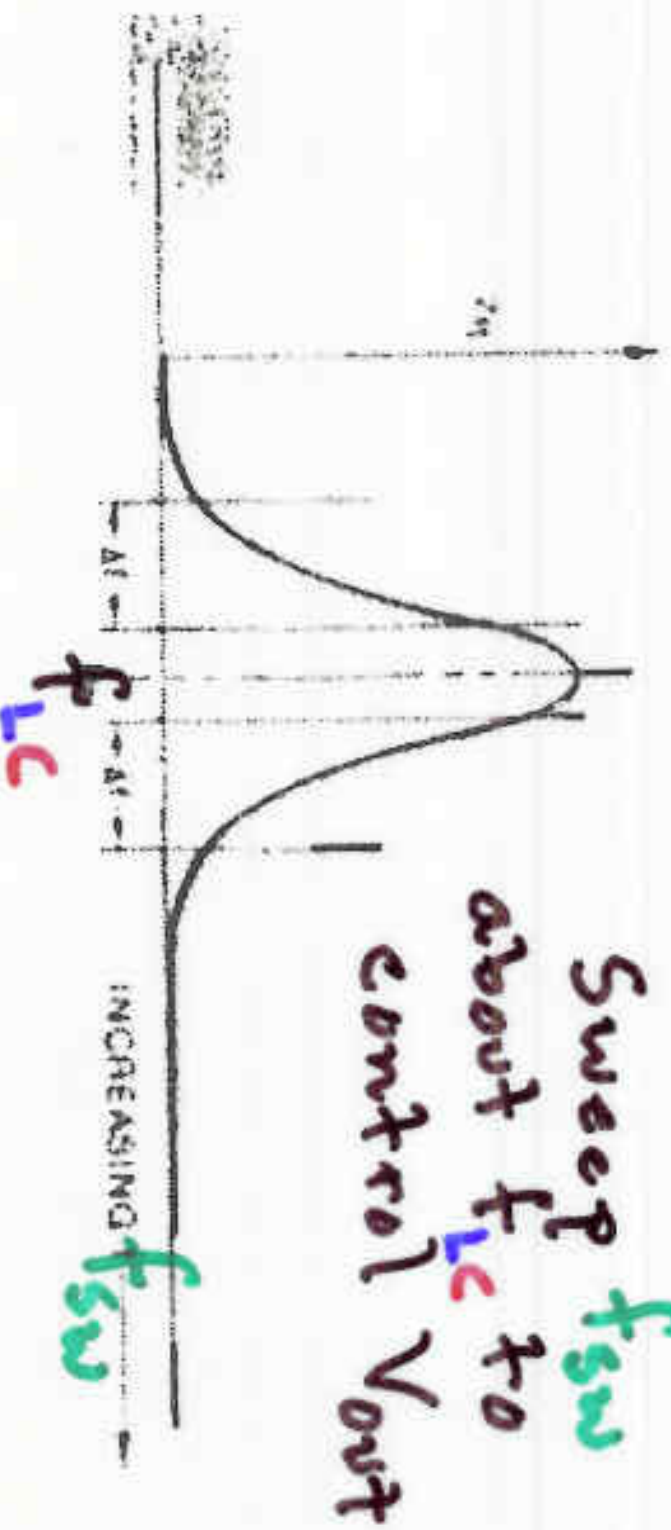


Fig. 11 - Variable Frequency Continuous Resonance

ADVANTAGES:

1. ZERO CURRENT SWITCHING
2. LOW COMPONENT STRESS
3. LOW EMI
4. USEFUL PARASITIC ELEMENTS
5. IMPROVED DIODE RECOVERY

non-linear
control loops

DISADVANTAGES:

1. GREATER COMPLEXITY
2. HIGHER PEAK CURRENTS
3. NEW TECHNOLOGY LEARNING CURVE

$a_s f_{sw} \rightarrow f_{lc}$

Fig. 4 - Resonant Converter Advantages

form of DCM
where $i \rightarrow 0$ each
cycle


QUASI-RESONANCE =

NOT TRUE SINUSOIDAL WAVESHAPE

VARIABLE FREQUENCY,

DISCONTINUOUS RESONANCE

Sinusoidal
portion

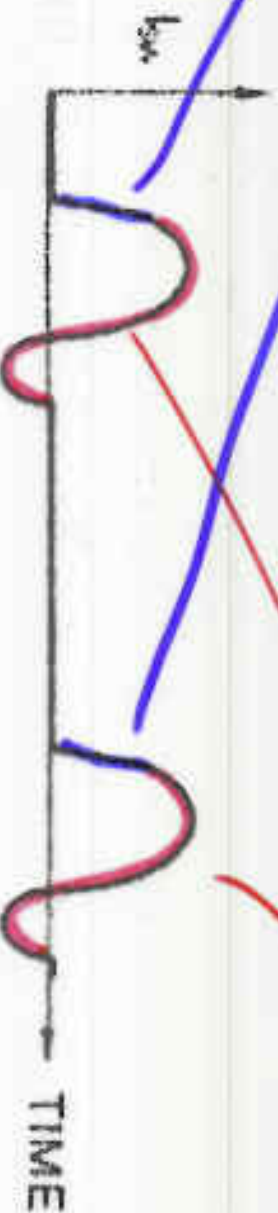

QUASI-RESONANCE CAN BE:

PARALLEL OR SERIES LOADED

HALF OR FULL CYCLE CONDUCTION

SWITCHED AT ZERO CURRENT OR VOLTAGE

CAN APPROACH CONTINUOUS RESONANCE

AS A LIMIT AT MAXIMUM LOAD.

Fig. 12 - Quasi-Resonance Definition

Control Loop for DCM Quasi-resonance

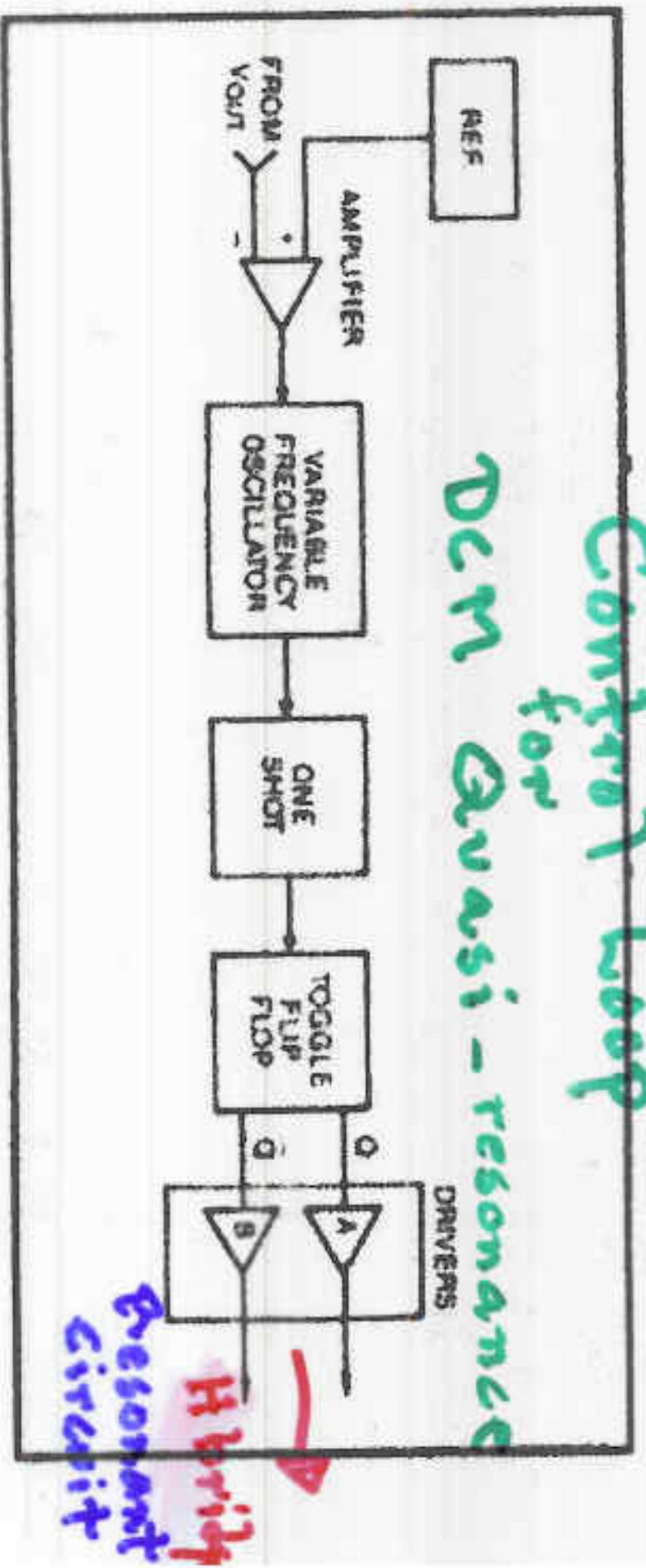


Fig. 13 - Quasi-Resonant Control

H Bridge: Sense for zero crossing of I or V to switch

~~trigger~~ trigger for H-bridge transition

L_g is an issue

C_g of Q is an issue

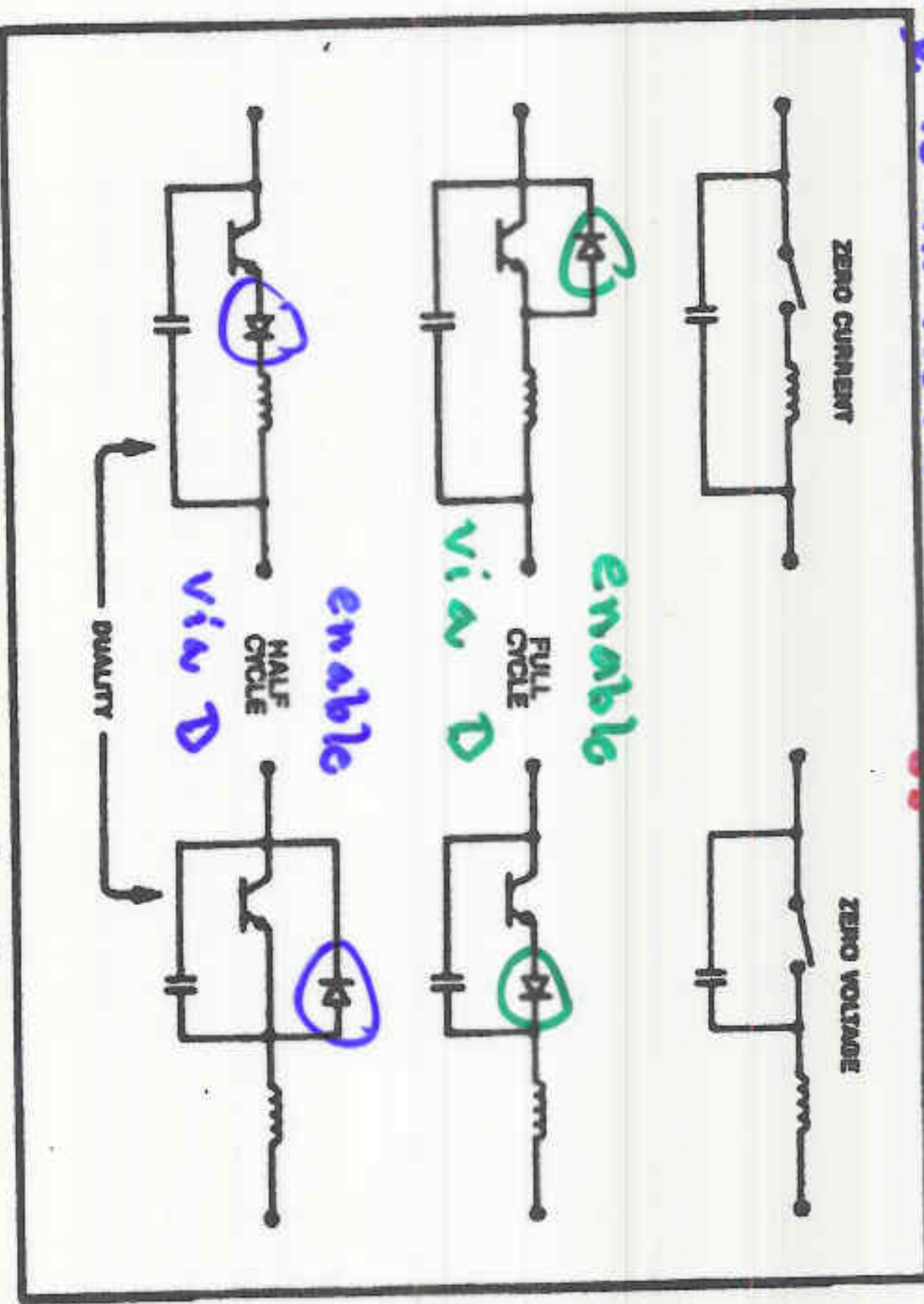


Fig. 14 - Switch Activation

CHARACTERISTIC	ZERO-CURRENT SWITCH	ZERO-VOLTAGE SWITCH
CONTROL	CONSTANT ON-TIME	CONSTANT OFF-TIME
SWITCH VOLTAGE WAVEFORM	$\approx$ SQUARE	$\approx$ SINUSOIDAL
SWITCH CURRENT WAVEFORM	$\approx$ SINUSOIDAL	$\approx$ SQUARE
LOAD RANGE	$R_{min} \rightarrow \infty$	$0 \rightarrow R_{max}$
SWITCH LIMITATIONS	PEAK ON CURRENT	PEAK OFF VOLTAGE

ZERO-VOLTAGE USAGE:

1. VERY HIGH FREQUENCIES WHERE SWITCH PARASITIC CAPACITANCE WOULD CAUSE EXCESSIVE POWER LOSS AT SWITCHING


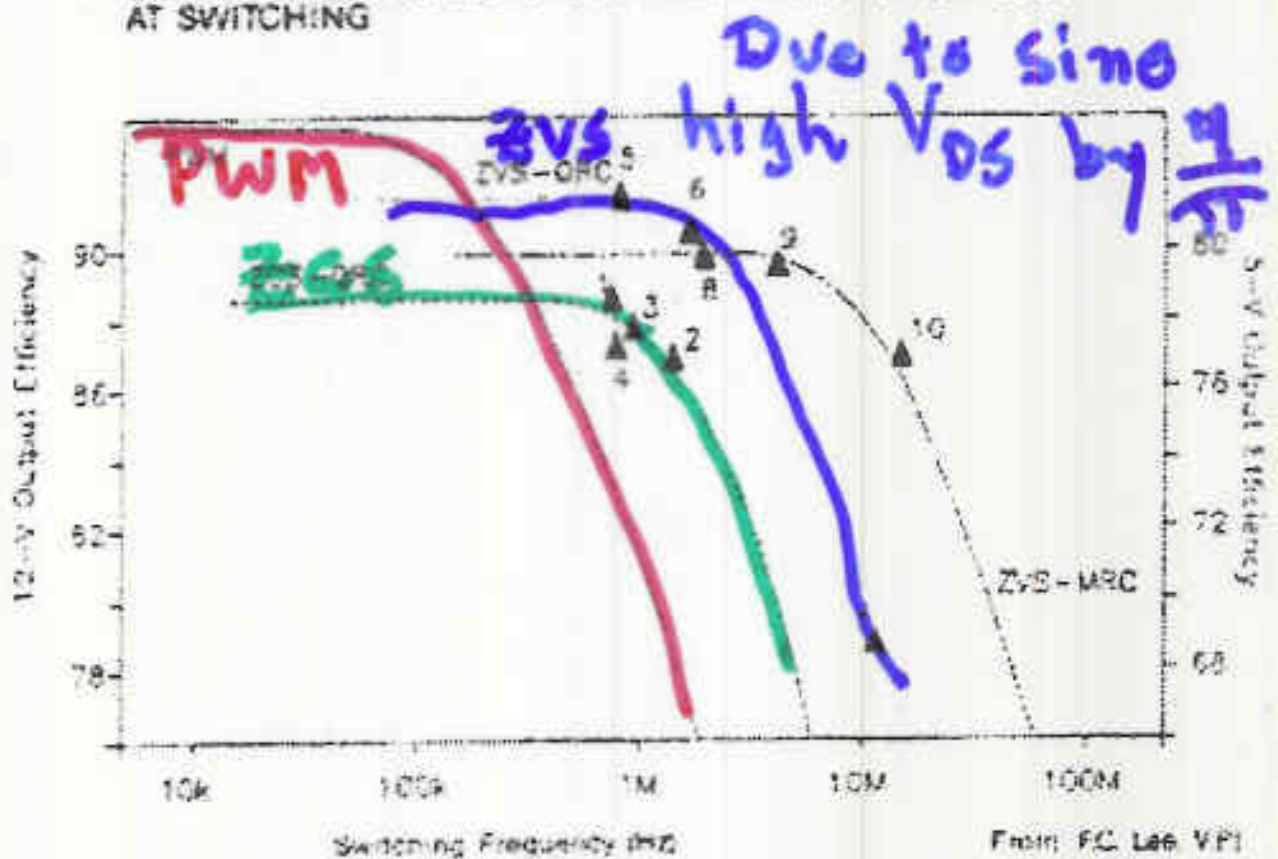


Fig. 15 - Switching Techniques Compared

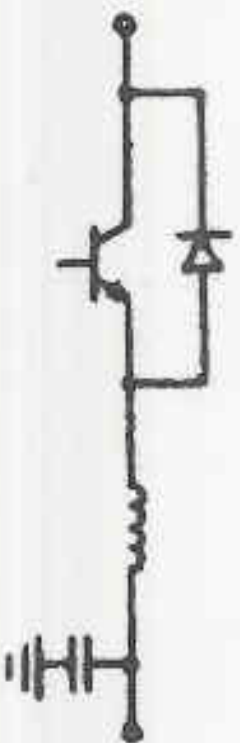

FULL CYCLE



HALF CYCLE


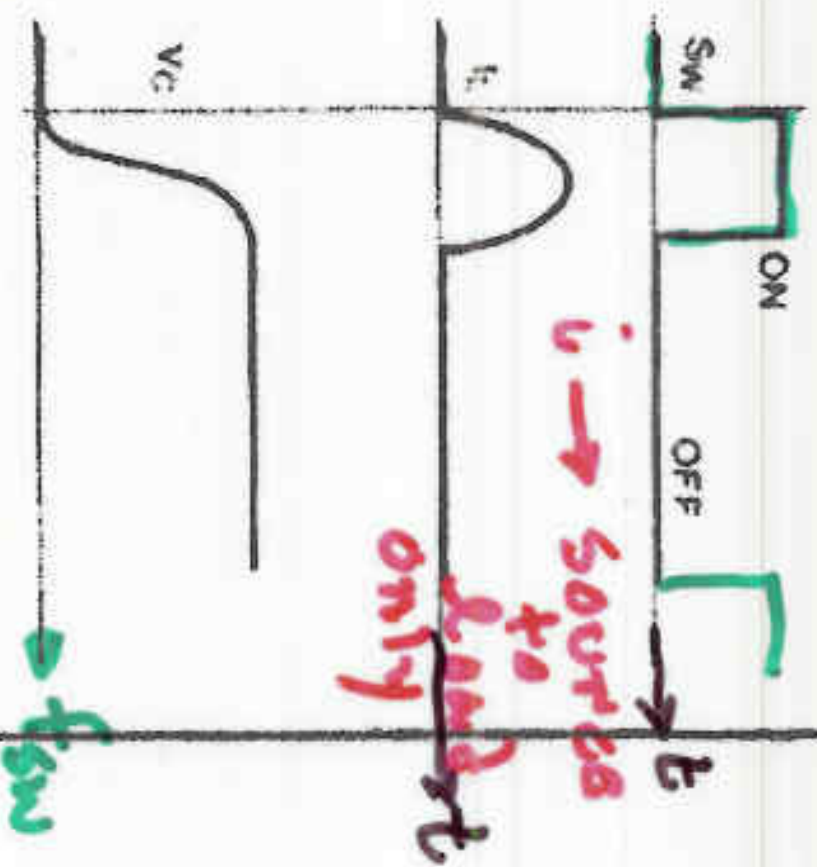


Fig. 16 - Half and Full Cycle Waveforms with Unloaded Resonant Switch

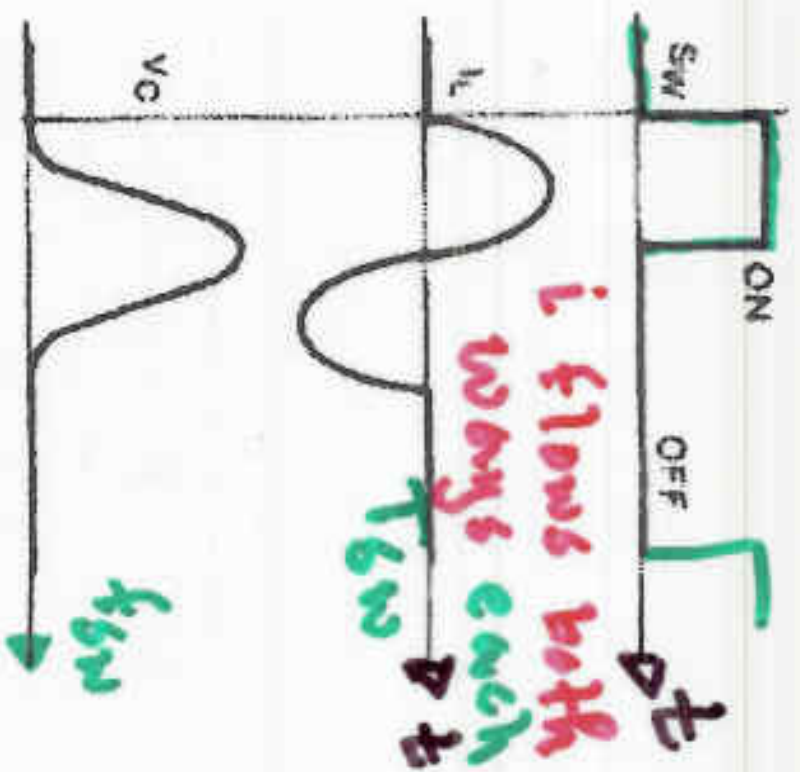

$$f_0 = \frac{1}{\sqrt{L_0 C_0}}$$

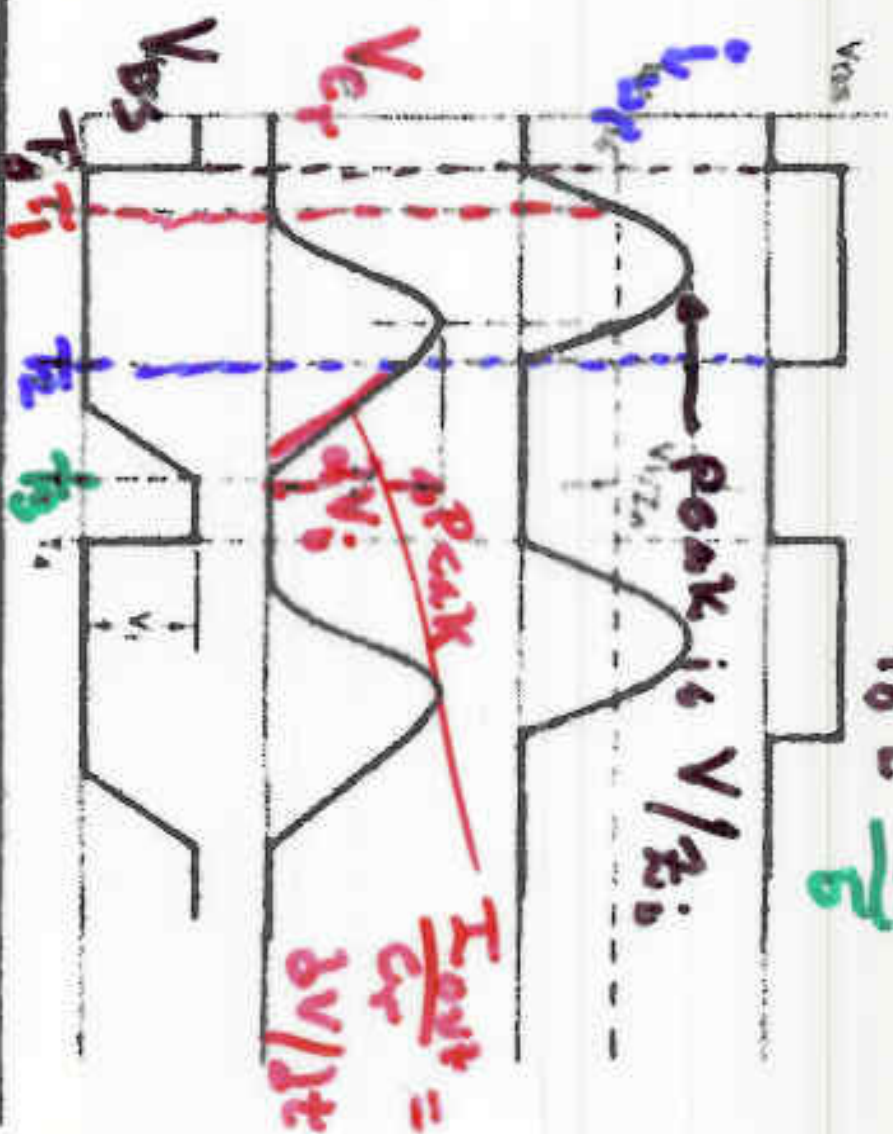


Fig. 17 - Quasi-Resonant Switching Operation

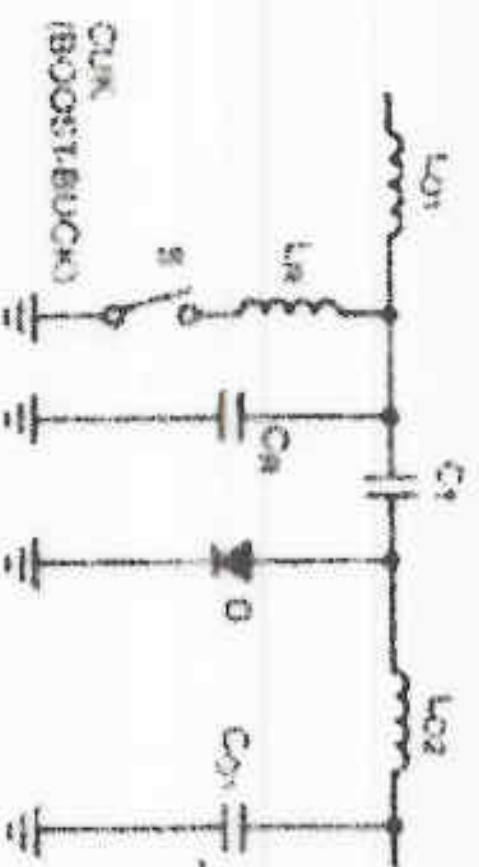
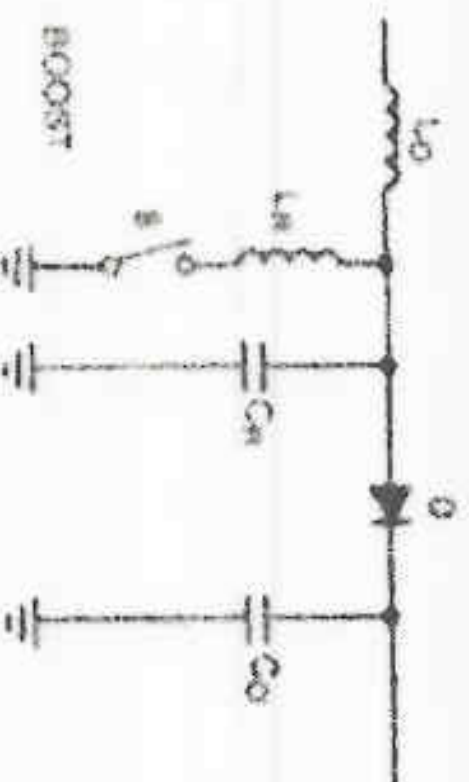
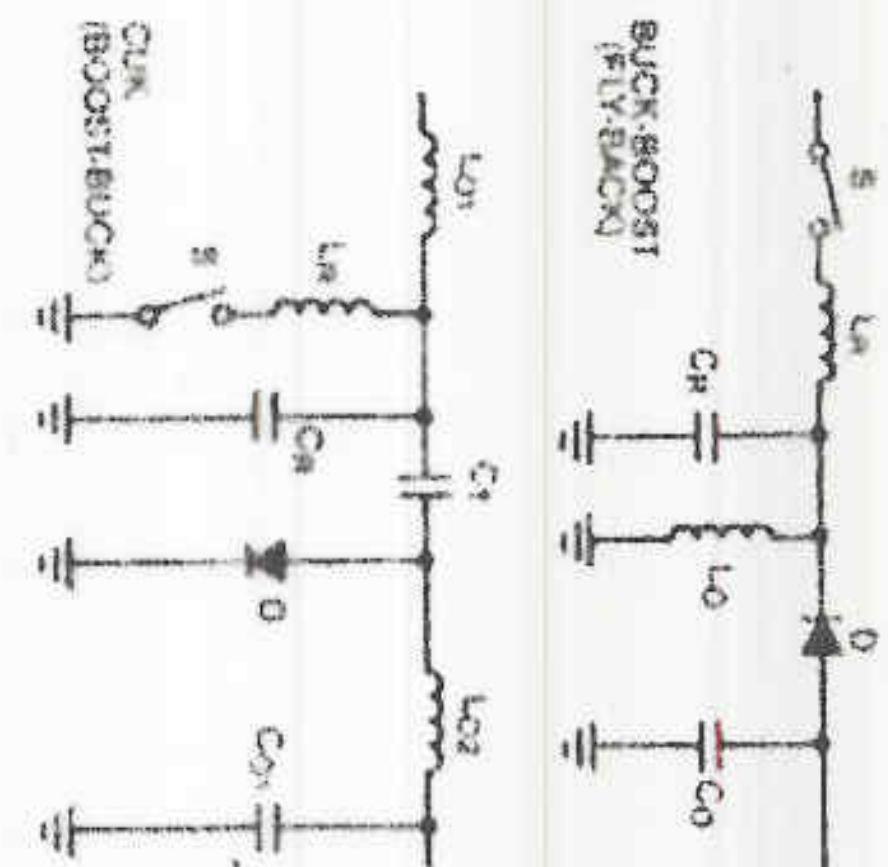
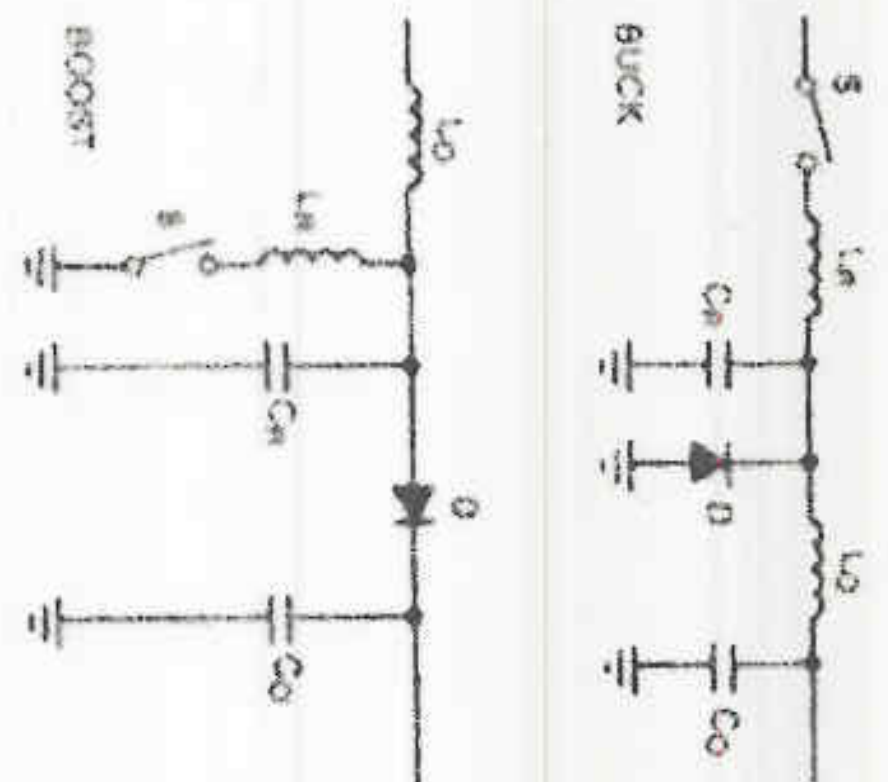


Fig. 18 - Parallel-Loaded Resonant Converter Versions of Square-Wave Power Conversion Topologies



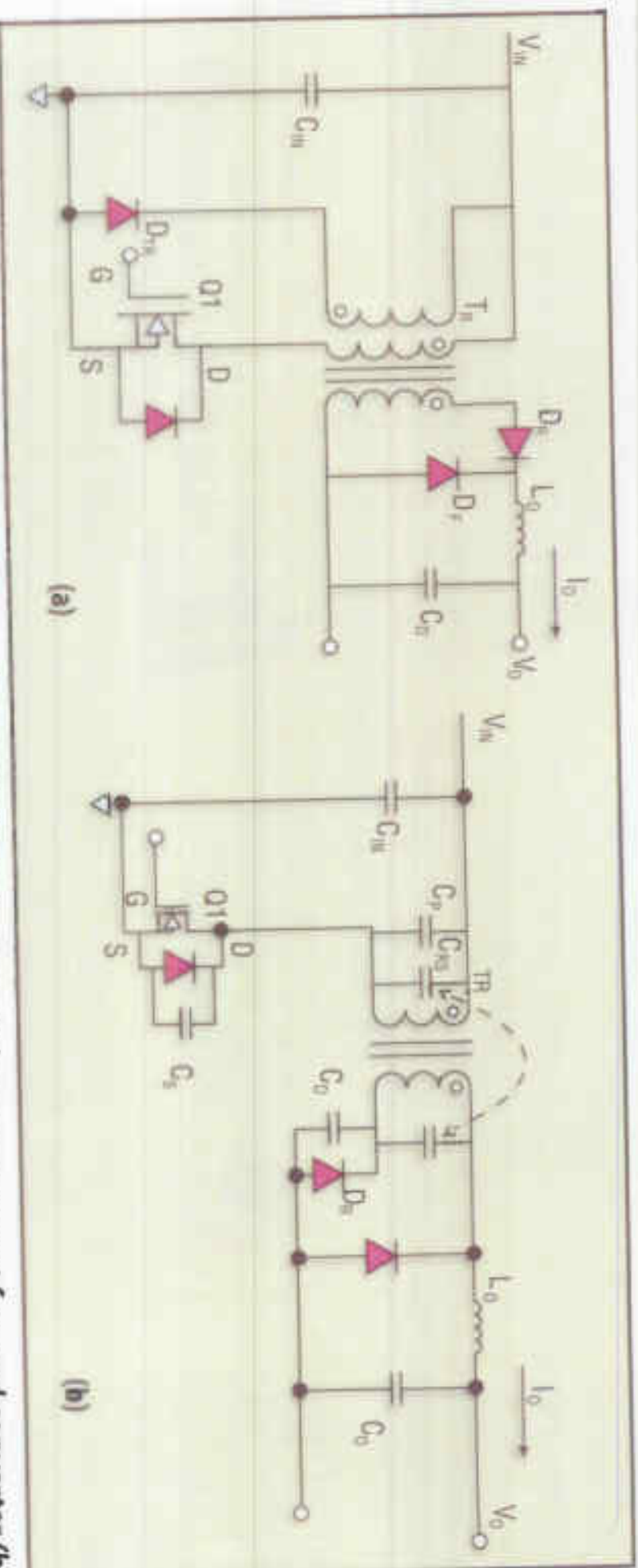


Fig. 1. A conventional single-transistor forward converter (a). A single-switch, resonant-reset forward converter (b).

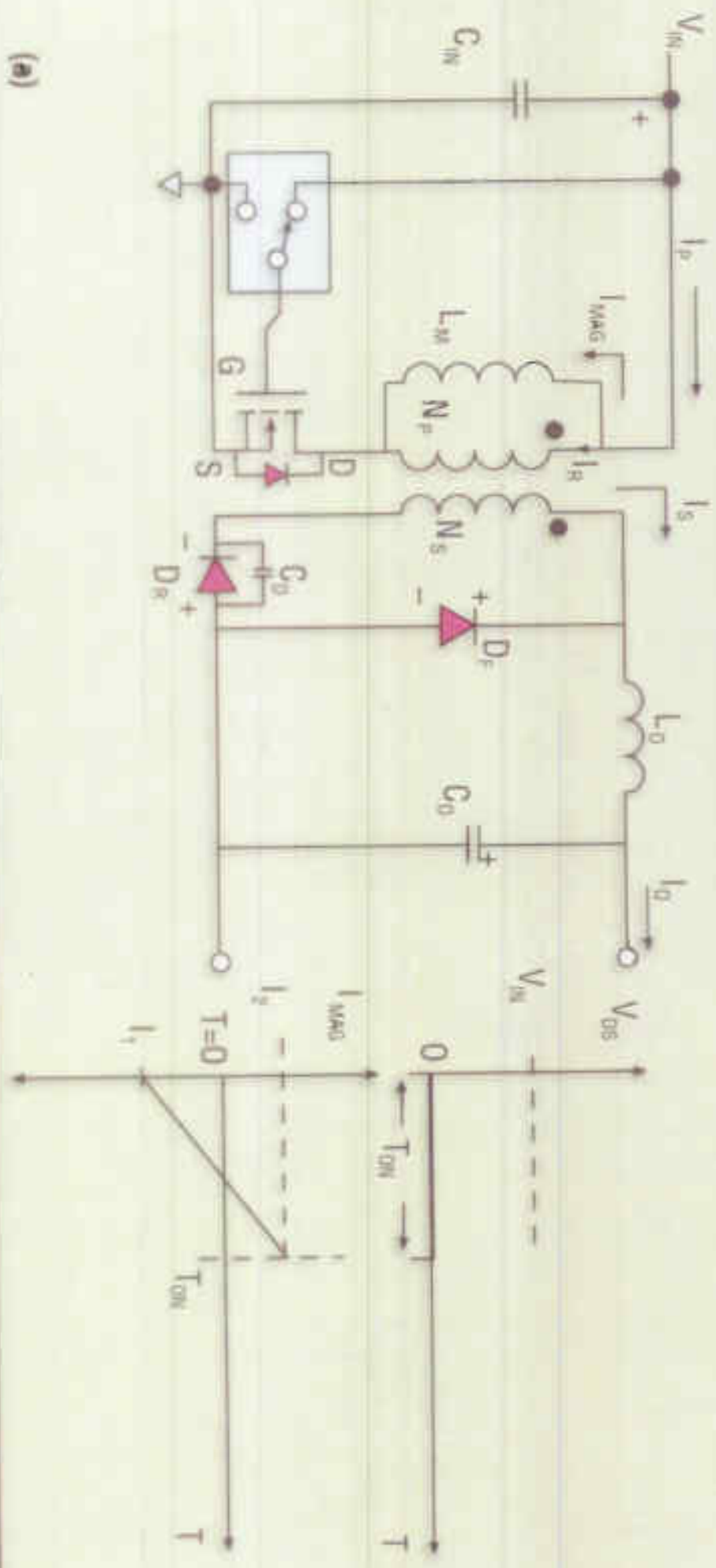

(a)

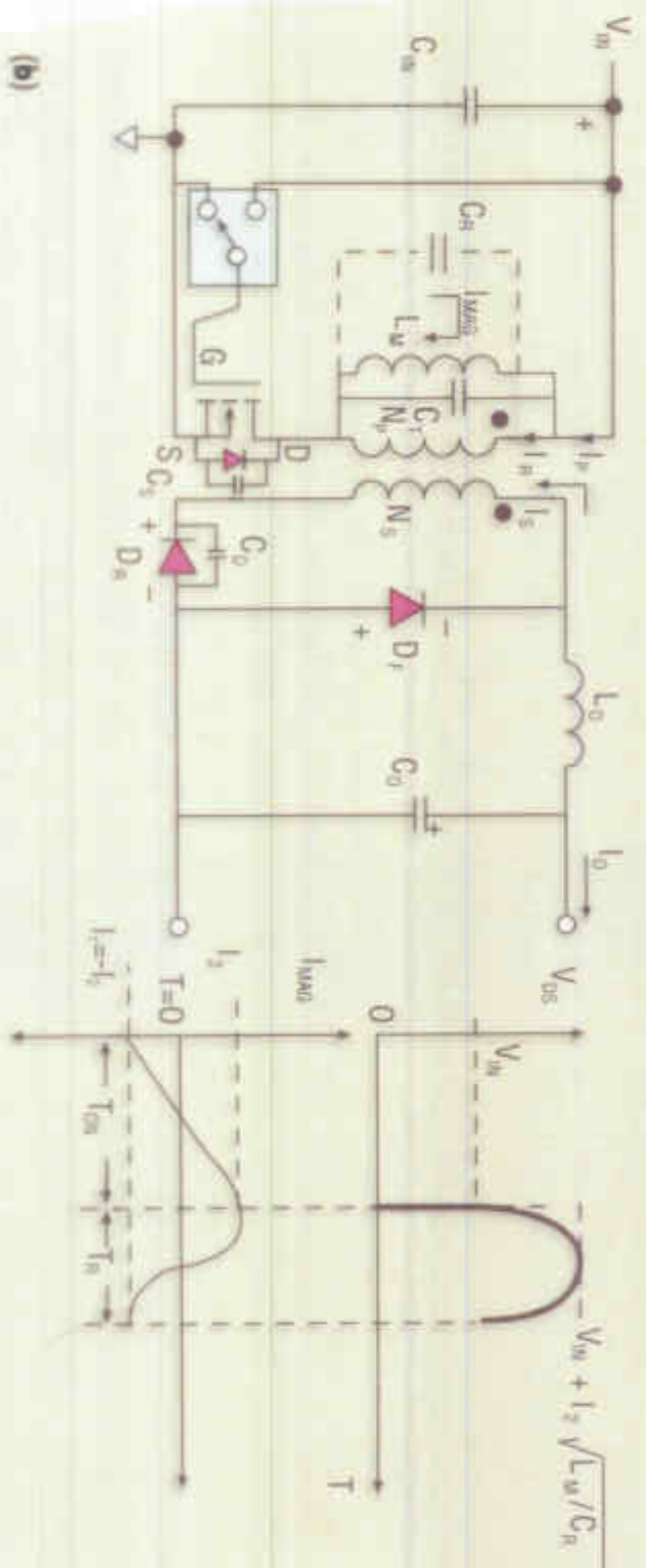

(b)

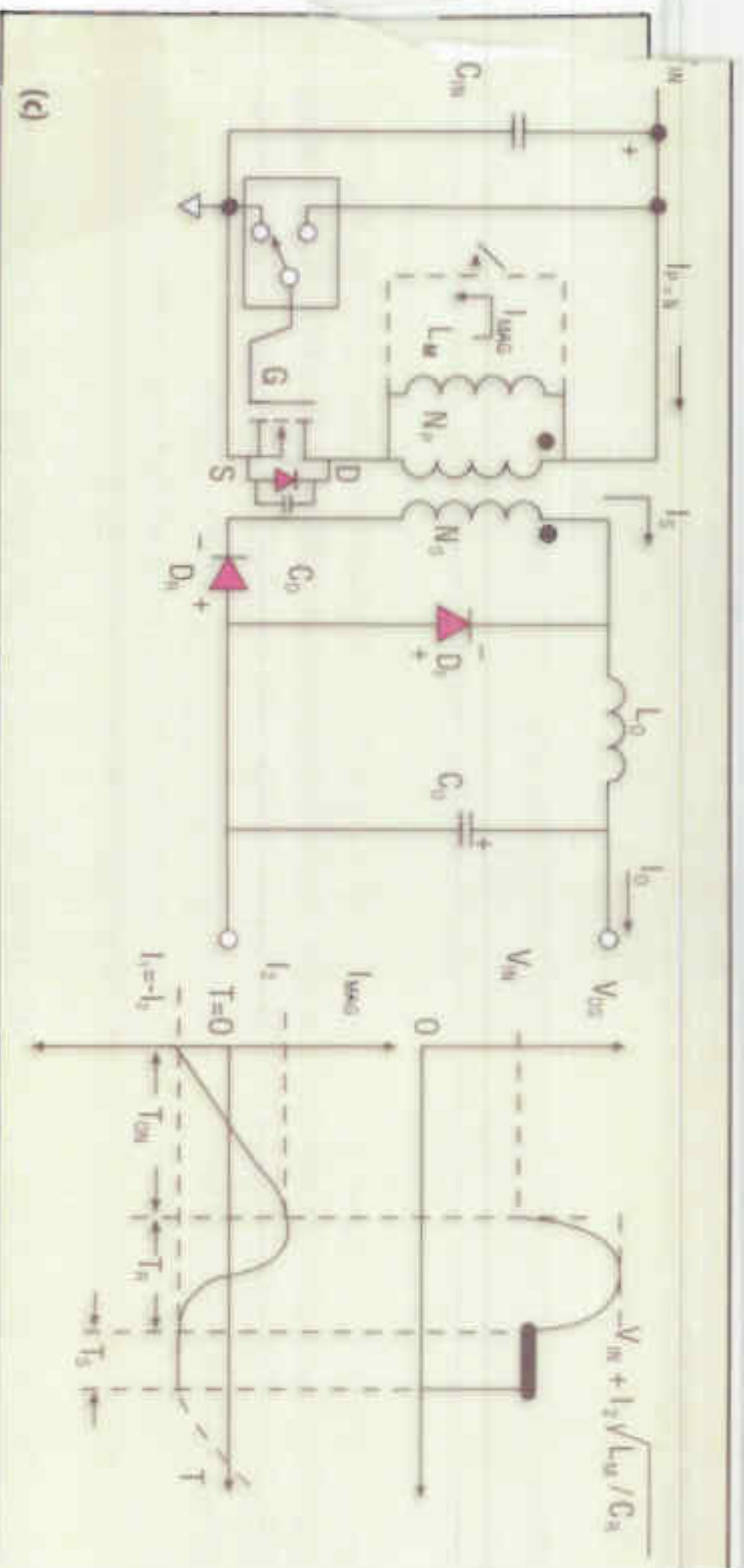


Fig. 2: From Fig. 1b, an equivalent circuit for the voltage on Q1 and the primary magnetizing-current waveform during Interval 1—not to scale (a). From Fig. 1b, an equivalent circuit for the voltage on Q1 and the primary magnetizing-current waveform during Interval 2—not to scale (b). From Fig. 1b, an equivalent circuit for the voltage on Q1 and the primary magnetizing-current waveform during Interval 3—not to scale (c).

Fig. 3 - Basic Resonant Converter



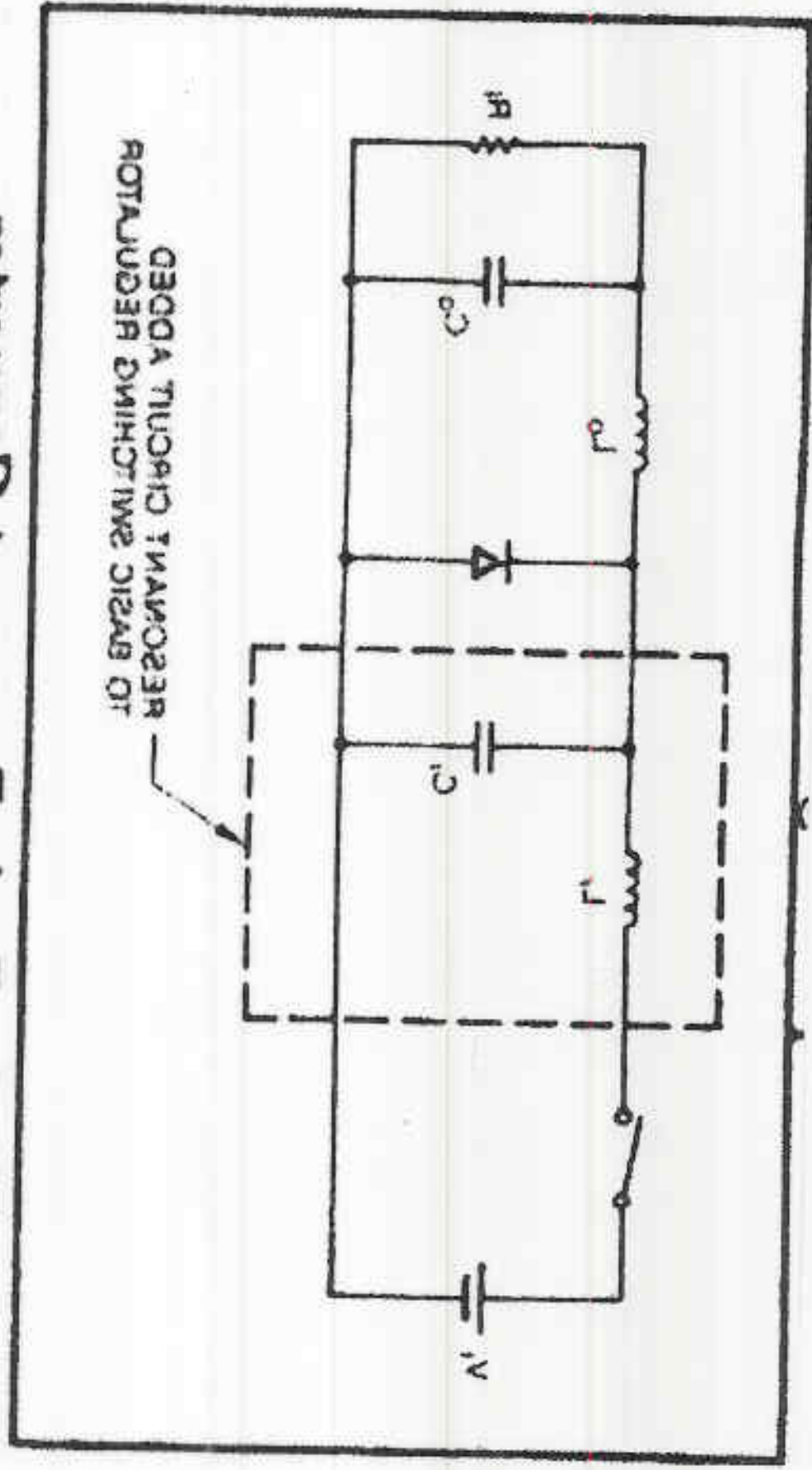
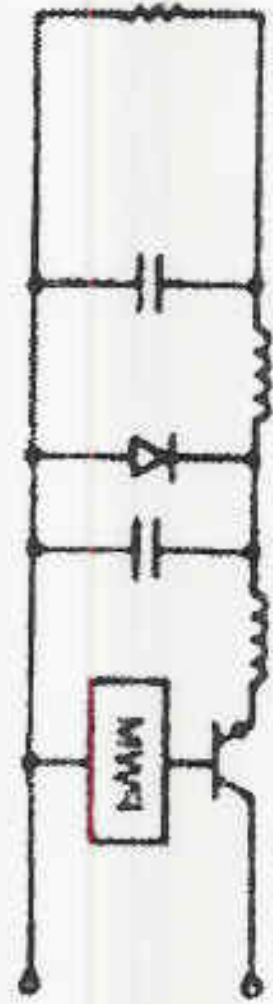


Fig. 10 - Fixed Frequency Resonance

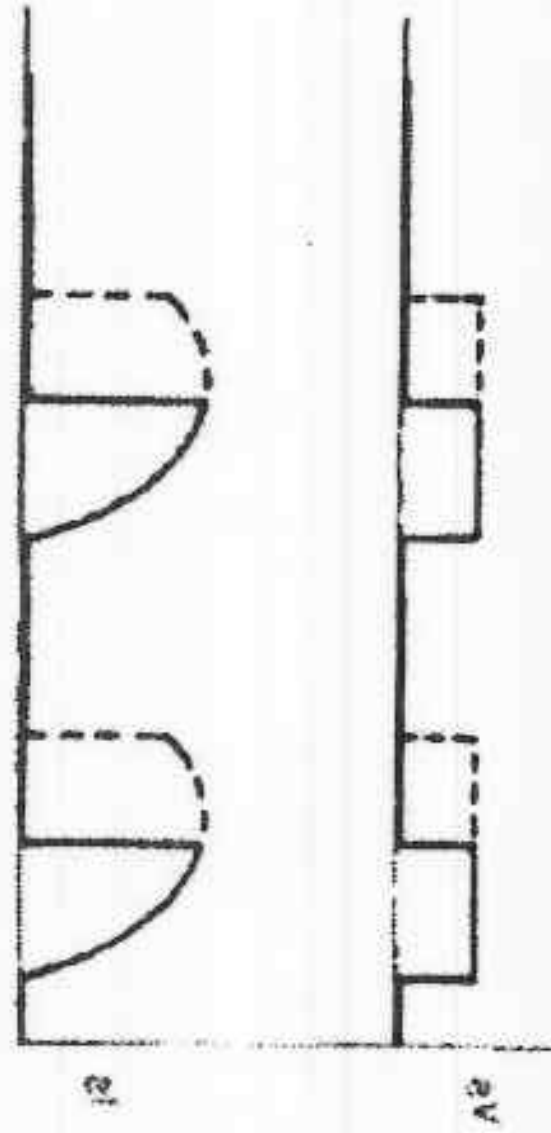

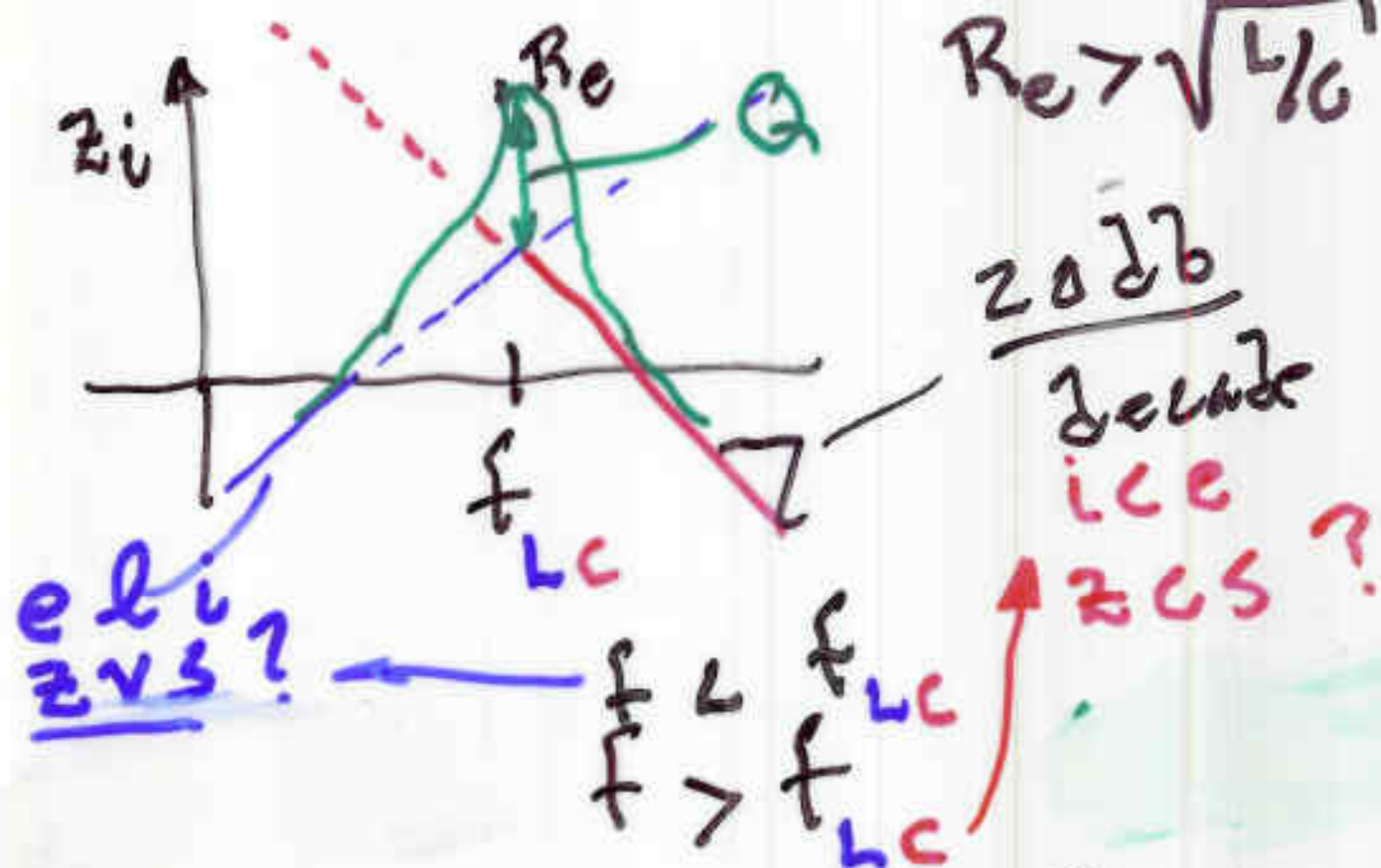

Q1 and make $f_{sw} \approx f_{LC}$

Then for our analysis

With these conditions met

1. I_H^{total} is negligible only f_{LC}

2. $i_s(t) \approx \sin f_{LC} t$

DC - AC - DC Converter

$$\frac{V_{s1}}{V_g} \cdot \frac{V_{out}^{DC}}{V_{s1}} = \frac{V_{out}^{DC}}{V_g^{DC}}$$