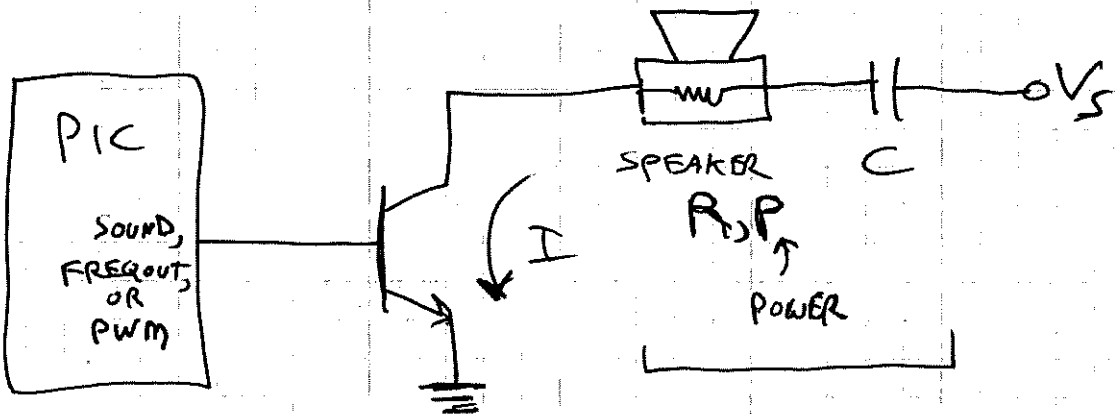


CHEAP/EASY WAY TO GET LOUDER AUDIO FROM MICROCONTROLLER



HIGH-PASS
FILTER w/:

$$\omega_c = \frac{1}{RC}$$

$$f_c = \frac{\omega_c}{2\pi} = \frac{1}{2\pi RC}$$

CHOOSE $f_c < f_{\text{AUDIO}}$

LOWEST
FREQUENCY
SENT TO SPEAKER

$$\Rightarrow C > \frac{1}{2\pi R f_{\text{AUDIO}}}$$

CHOOSE V_s
BASED ON SPEAKER
POWER RATING:

$$P_{\text{MAX}} = \frac{V_s^2}{R}$$

$$\Rightarrow V_s < \sqrt{R \cdot P_{\text{MAX}}}$$

SELECT TRANSISTOR

w/ ADEQUATE CURRENT
CAPACITY:

$$I_{\text{MAX}} = \frac{V_s}{R}$$