

■ **CLASS DISCUSSION ITEM 6.5**

***JK Flip-Flop Timing Diagram***

Construct a timing diagram for the negative edge-triggered JK flip-flop illustrating its complete functionality.