
 



Homework 11 Due 11/14/17

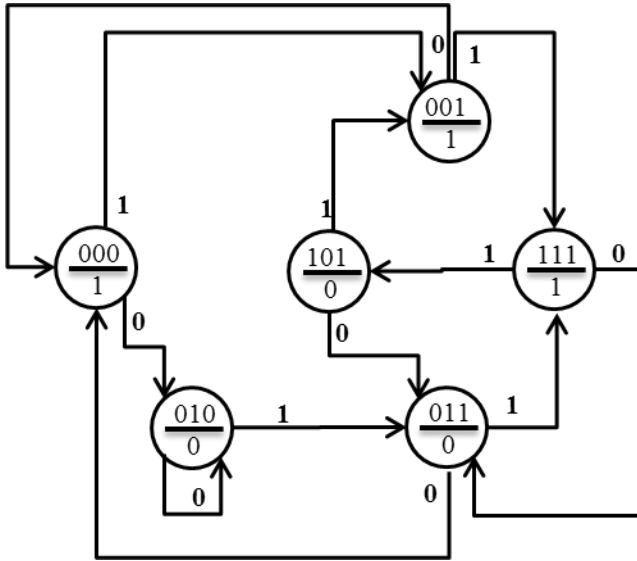1. The state diagram shown below is implemented using three negative edge-triggered flip-flops with outputs labeled A, B, C. The output of the circuit is Z. Complete the timing diagram, assuming that the initial state is 101.



 
2. A sequential circuit is given below. The states in the transition diagrams are labeled AB, e.g., the state

corresponding to $A=0, B=1$ is denoted as 01. The inputs to the sequential circuit are X and Y , and its output is Z . Draw a complete state transition diagram for the circuit.



 3. Design a circuit to implement the following state diagram. All the K-maps and circuit diagrams should be complete and clearly labeled.

- using T type positive edge triggered flip-flops and
- using D-type positive edge triggered flip-flops



4. Design Moore and Mealy state diagrams for the following: A circuit has a two-bit binary number (X_1, X_0) as inputs and an output Z . Z is 1 iff the most recent binary number

(X_1, X_0) is greater than the previous binary number.

5. Design Moore and Mealy state diagrams for the following:
A circuit has a two-bit binary number (X_1, X_0) as inputs and three output lines Z_2, Z_1, Z_0 . The binary number (Z_2, Z_1, Z_0) is equal to the two the sum of most recent input values. For the first pair of input values, use 00 as the previous pair.
Ex.

```
X1: 0 1 0 1 0 1 0 0 0 0 . .  
X0: 1 1 1 0 1 1 0 0 1 1  
Z2: 0 1 1 0 0 1 0 0 0 0  
Z1: 0 0 0 1 1 0 1 0 0 1  
Z0: 1 0 0 1 1 0 1 0 1 0
```

