


**ECE 331: Electronics Principles
I Fall 2014**

Lab #3: MOSFETs Characterization


Pre-lab due on Thursday, Oct. 16, before noon

Pre-lab

 - A. Draw both the large and small signal models for NMOS transistors. Sketch I_D vs V_{DS} characteristics for several values of V_{GS} and graphically illustrate the Channel Length Modulation effect.
- B. List the difference between NMOS and PMOS transistors. Draw a schematic of each one, Labeling all relevant voltages and currents. What is an advantage of using a PMOS? What is a drawback? (Hint: Consider the response time)
- C. For an NMOS transistor with threshold voltage $V_t = 0.62$ V, $K_n' = 0.167 \text{ mA/V}^2$, here K_n' is defined to be equal to $\mu_n C_{ox}$, If $V_{over-drive}$ is 0.25 V, $W = 0.55 \text{ } \mu\text{m}$ and $L = 0.18 \text{ } \mu\text{m}$, answering the questions listed below:
1. What is the actual channel length for V_{ds} equal to 0.5 V, 1V and 1.5V separately? Assume $\lambda = 0.1 \text{ V}^{-1}$ for this process. What is the output impedance r_o at $V_{ds} = 1$ V?
 2. Assume $\lambda = 0$, find g_m at $I_D = 1$ mA.
- D. For the circuit below, given $V_t = 1$ V, $K_n'(W/L) = 2 \text{ mA/V}^2$ and $\lambda = 0$, Find R to make $I_D = 1$ mA and how much V_D is.



 - E. For the circuit below, given $V_t = 1$ V, $K_n'(W/L) = 0.5$ mA/V² and $\lambda = 0$, $R_{G1} = 5$ M Ω , $R_{G2} = 5$ M Ω , $R_D = 6$ K Ω AND $R_S = 6$ K Ω , Find voltages at the each terminal (V_G , V_S , V_D) and current at each node (I_G , I_S , I_1 , I_2).



- F. Design the circuit below to make Q_p working in saturation region and $I_D = 1$ mA, $V_D = 3$ V, given $V_t = -1$ V, $K_p'(W/L) = 2$ mA/V² and $\lambda = 0$, Find R_D , R_{G1} , R_{G2}

