

Chapter 11 #1

Transformers

- Special Transformers
- Three Phase
- Open Delta
- Auto Transformers
- Why Auto Transformers


At a location near you!

4 - 12 KV



} Very familiar?
Sight

120, 120
240

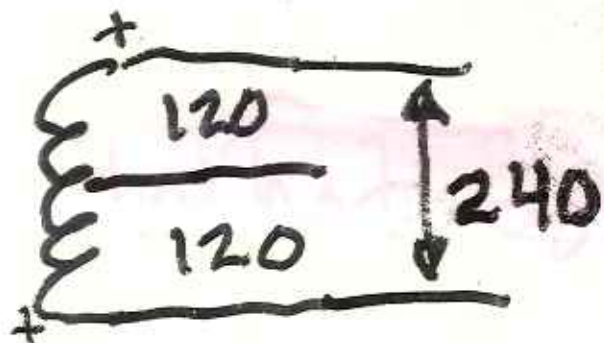


20KW/home

Careful 3 coils

Figure 11-1 a. Distribution transformer with 120 V/240 V secondary. The central conductor is the neutral. b. Same distribution transformers reconnected to give only 120 V.

Careful
of
dot
location

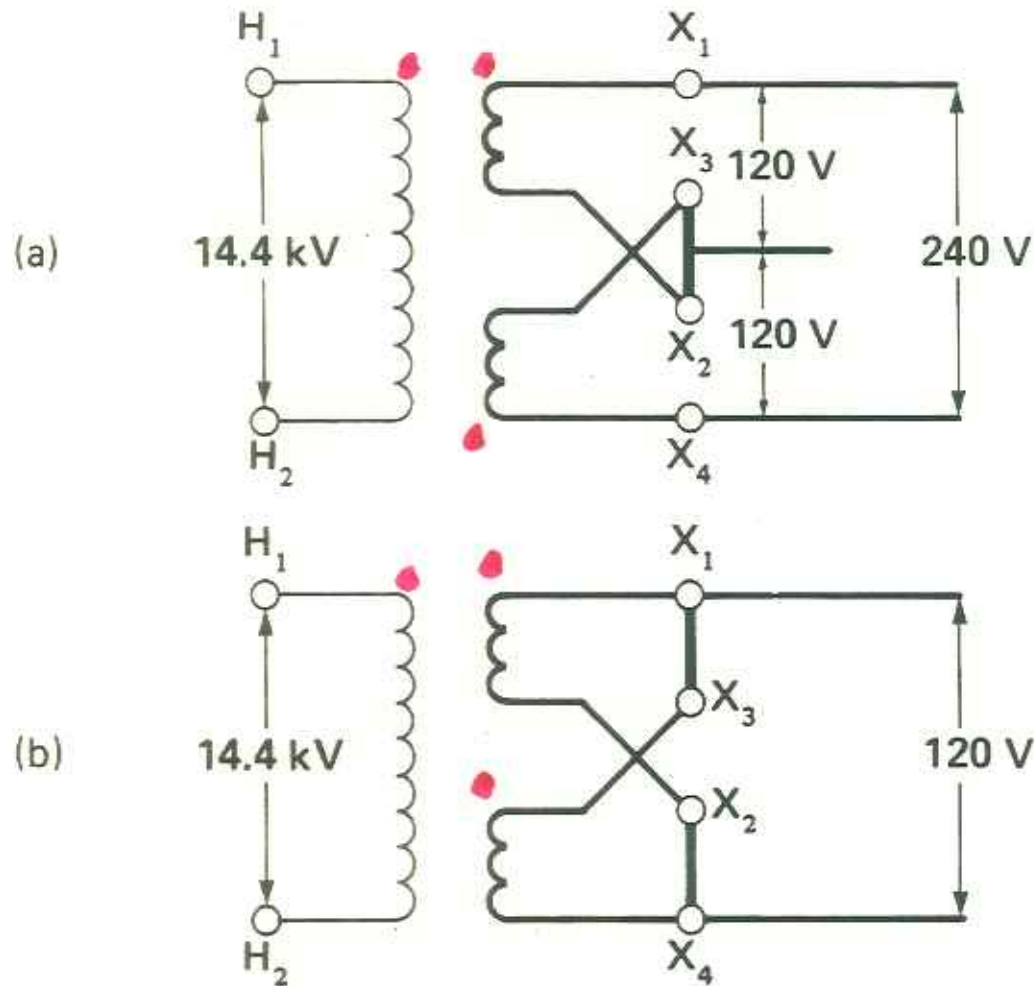

Why both
120 ?
240 .

Why only
120



Wiring on exam?

2

Fig 17.1
Pg 226



new Low loss core
to reduce low
(L=0) load core loss

HV
Primary

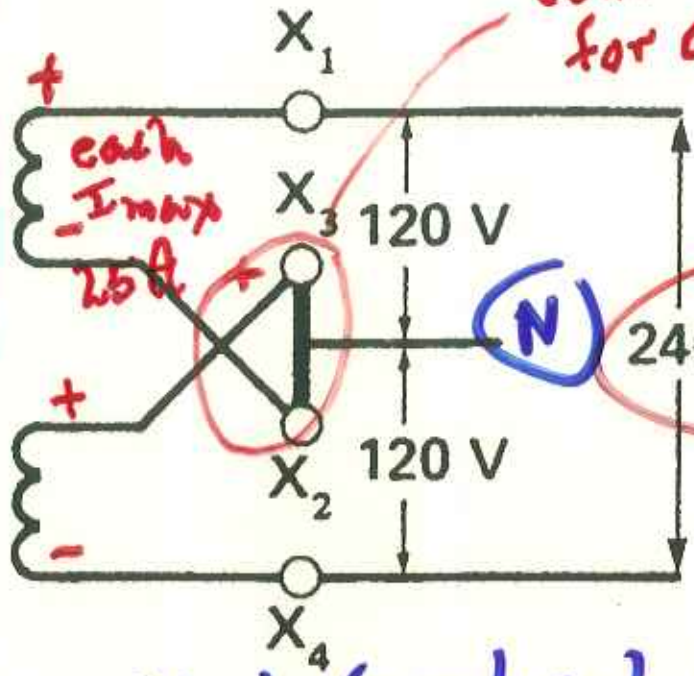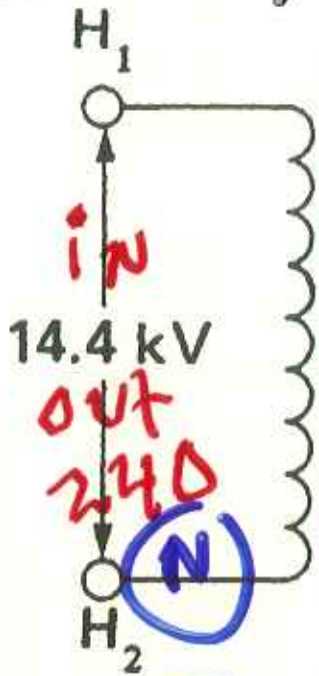

3 wire
for
dryer
home
store
for?

To parallel for high I 120

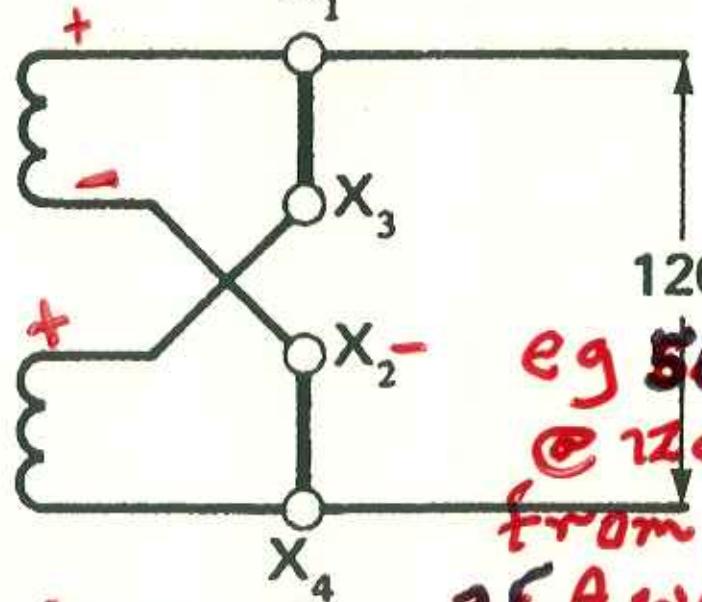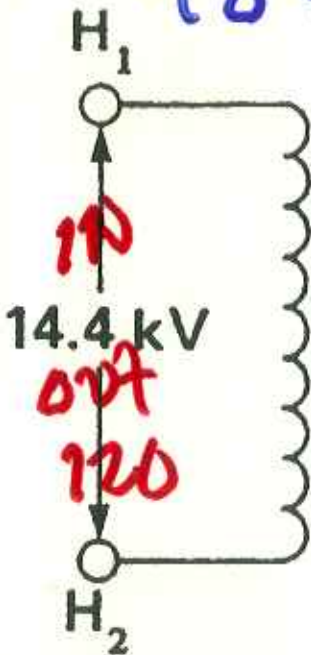


Two parallel Trf

store
dryer

INTELLIGENT POWER

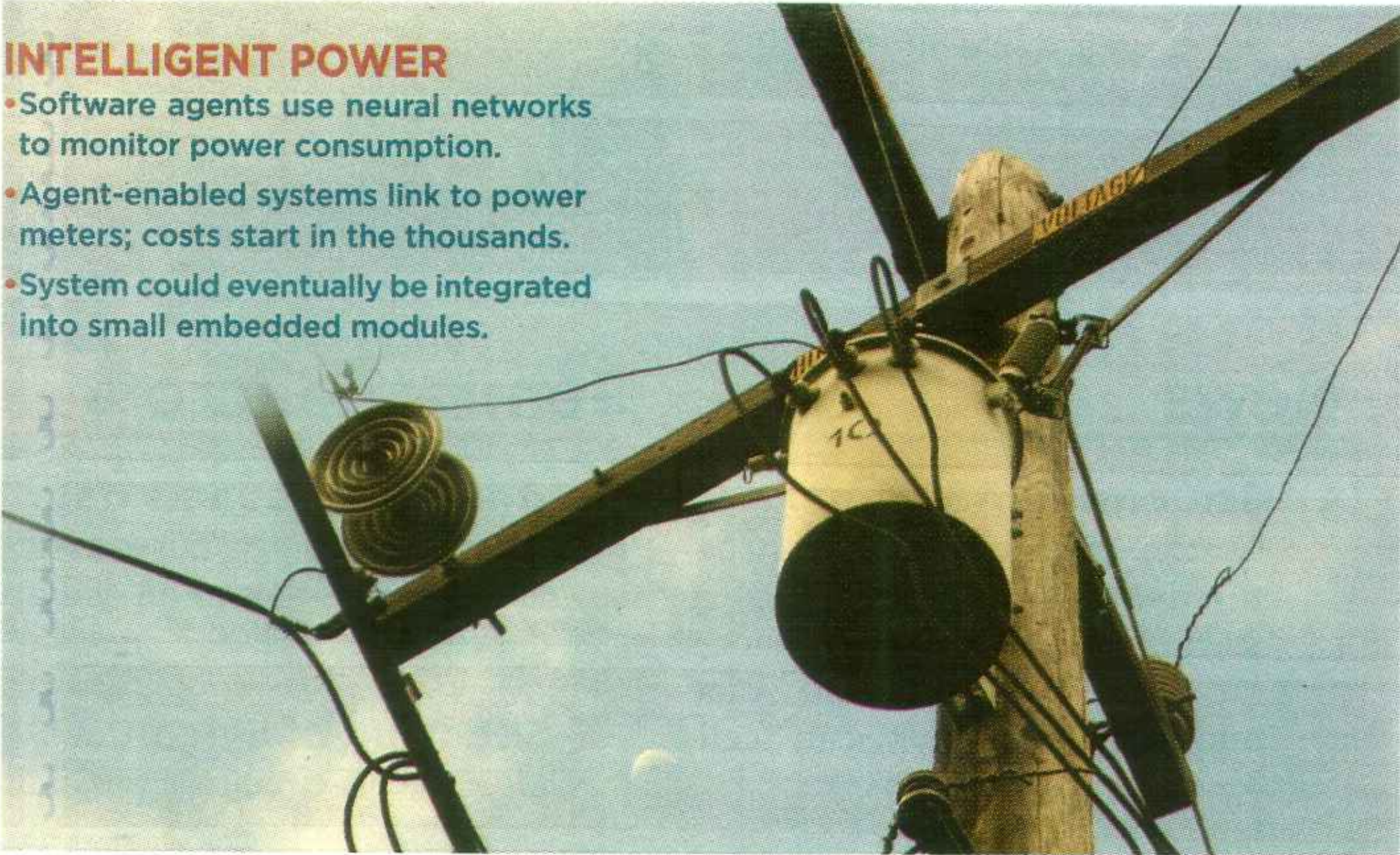- Software agents use neural networks to monitor power consumption.
- Agent-enabled systems link to power meters; costs start in the thousands.
- System could eventually be integrated into small embedded modules.



New grid:
Each house monitored / controlled

Interwinding C could be deadly. How?

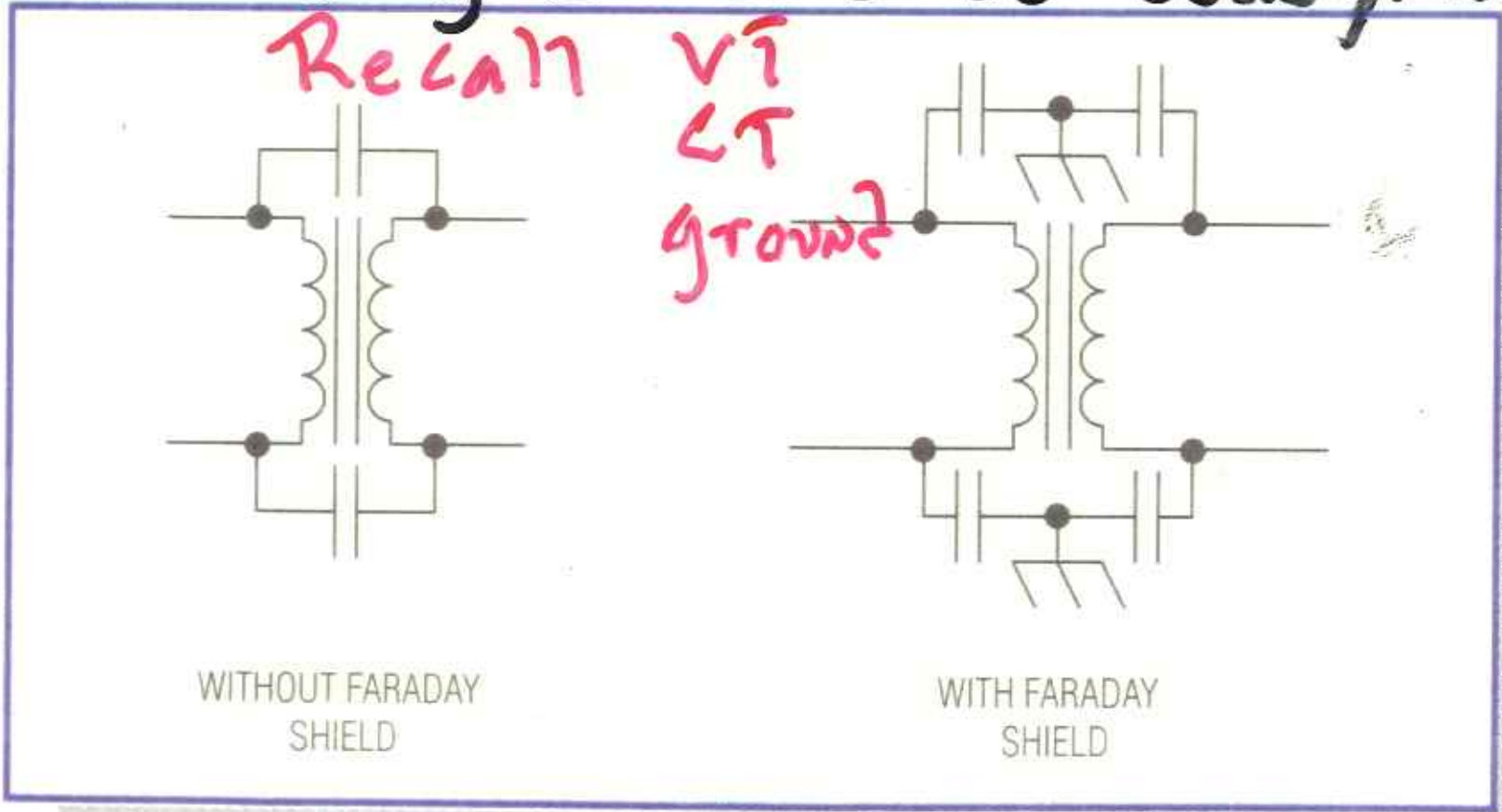


Figure 8. A Faraday shield between primary and secondary blocks common-mode noise that would otherwise pass through the transformer's parasitic interwinding capacitance.

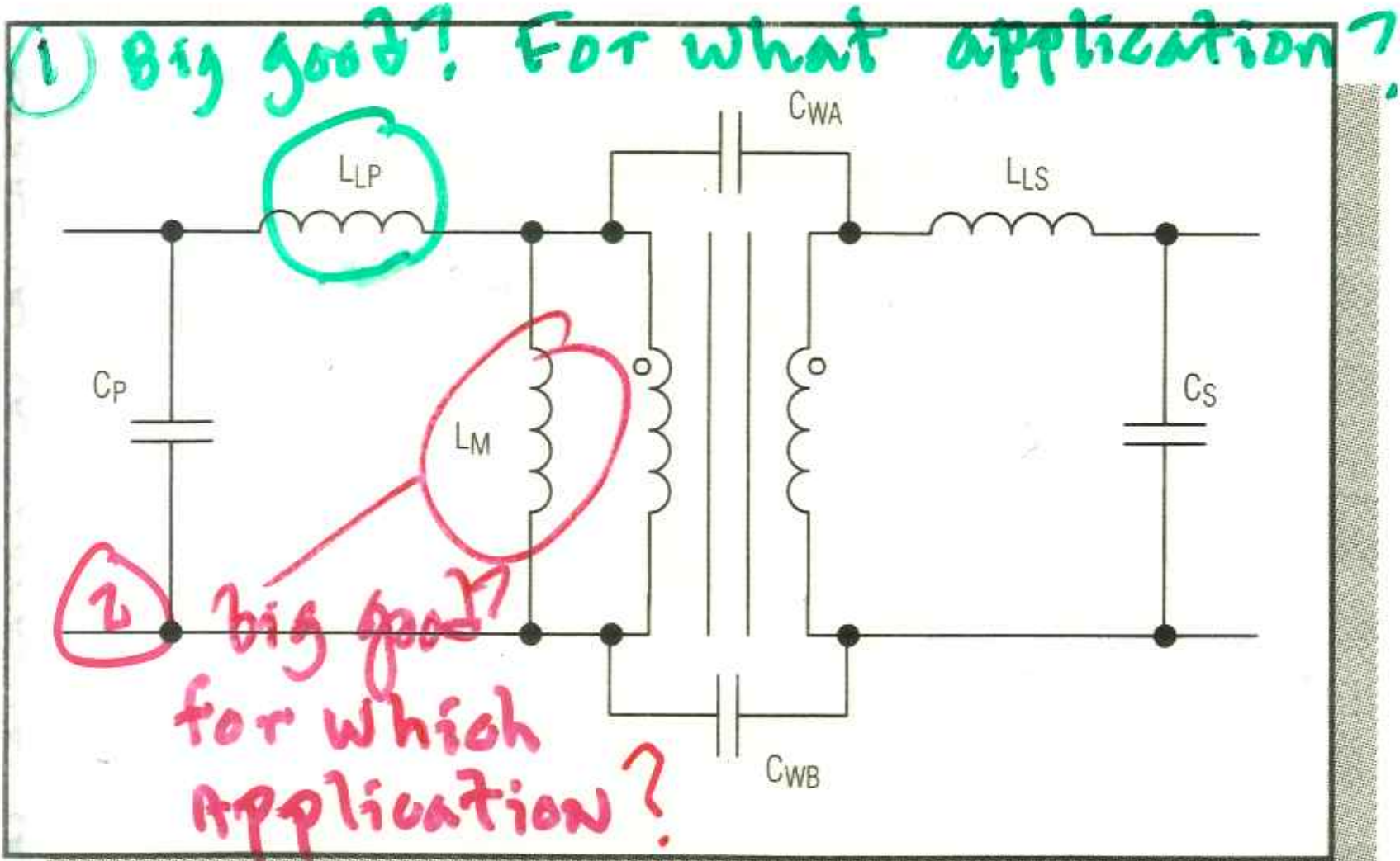


Figure 11. Parasitic elements in the equivalent model for a transformer modify its ideal behavior.


CAN you explain each C and L?
 Challenge: How to "fix" C_{WA} and C_{WB}

Why X_e large can be better



Figure 11-24 a. Schematic diagram of a neon-sign transformer. b. Construction of the transformer. c. Typical E-1 characteristic of the transformer.

in gas discharge load

Why?

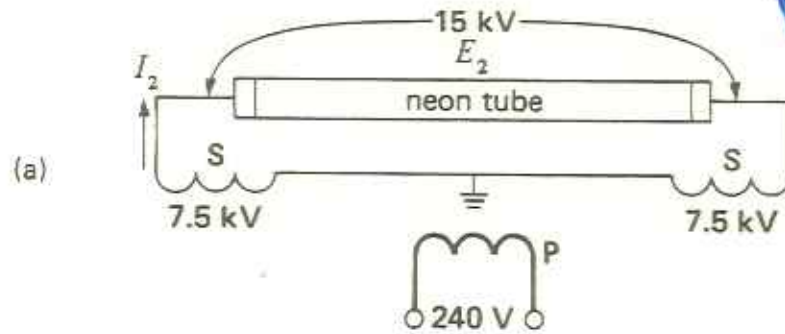

(b)

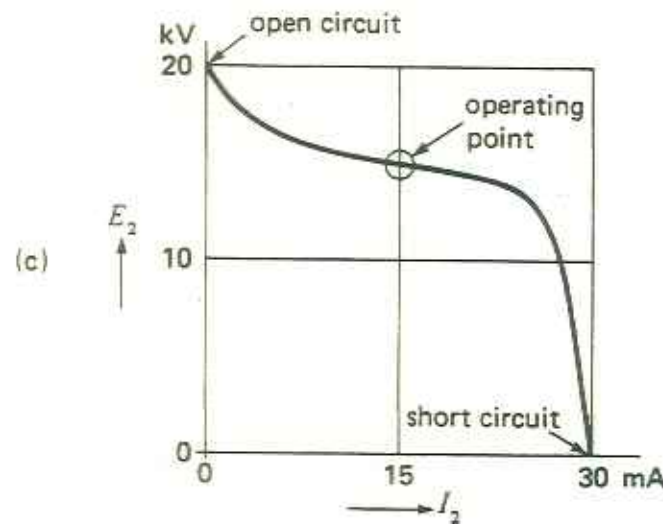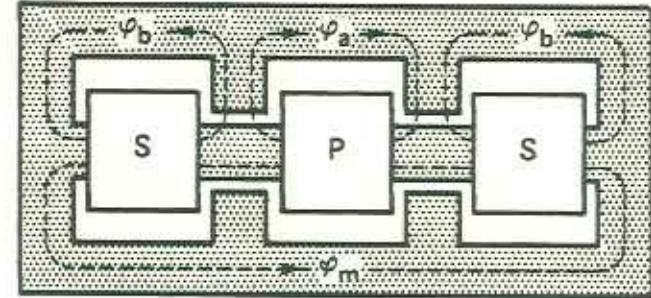


X_e best it? and why

Line variations are normal


Generally V_{swell} — V_H
AC line varies V_{sag} — V_L
(swell) occurs over 10-60 minutes
Known ΔV

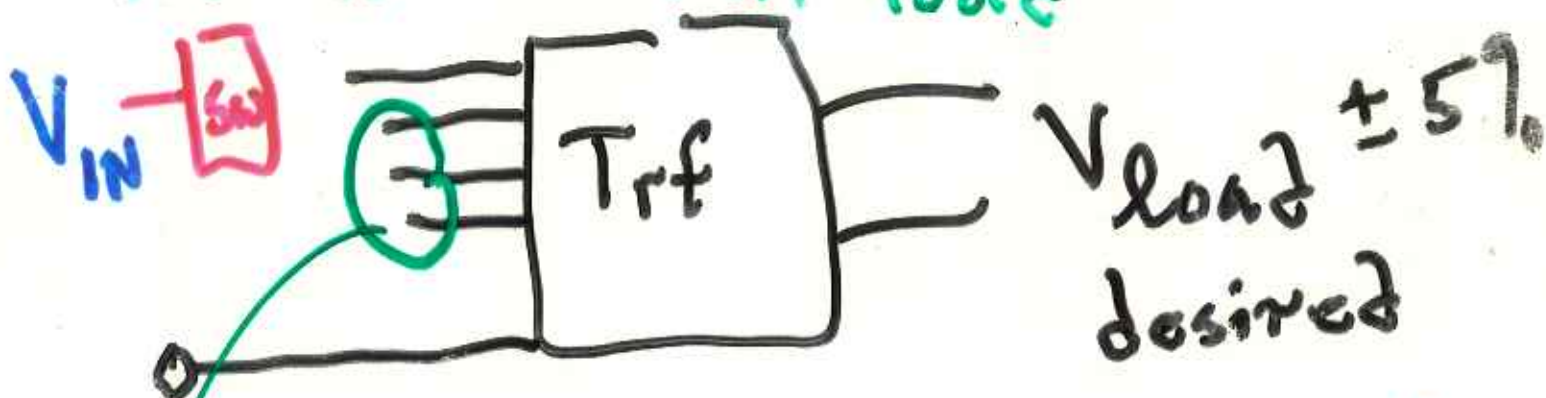How to keep V_{load} fixed
with only (transformer)
switches
for a critical load



Old SW: e-mechanical Δt ms
New SW: IGBT 1kA Δt μs
12kV

Taps at e.g. 95% V_{IN}
:
80% V_{IN}

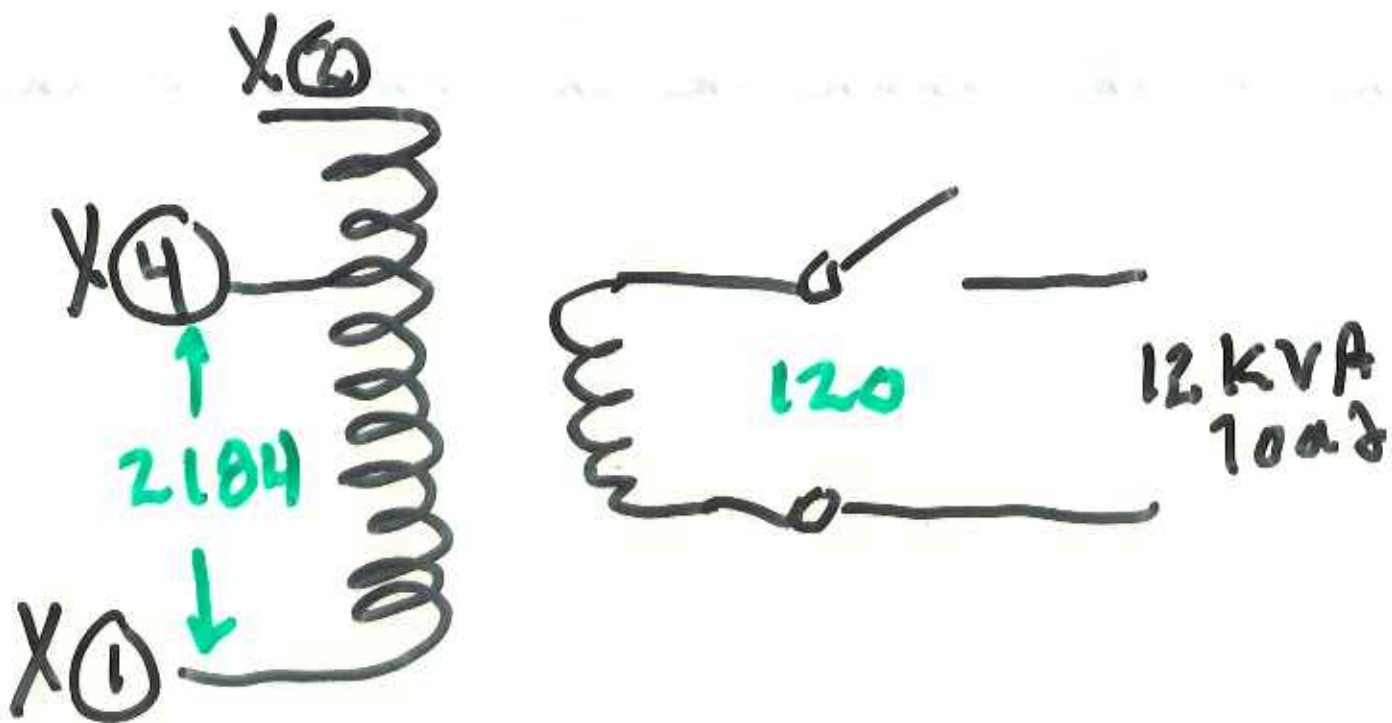

if 2184 rises to 2300

$$V_{out} = \frac{2300}{2184} 120 = 126.4$$

not 120

$$V_{12} = ? \quad \text{for } 2184 = V_{12}$$

Prior slide $V_{12} = 2400$

For 12KVA load $V_{14} = 2300$

$$I_{out} = ? = \frac{S}{V}$$

$$= \frac{12,000}{126} = 95 \text{ A}$$


$$I_{2300} = ?$$

$$= \frac{12,000}{2300}$$

$$= 5.2 \text{ A}$$

Each Trf. rated at 5

Figure 12-1 Delta-delta connection of three single-phase transformers. The incoming lines (source) are A, B, C and the outgoing lines (load) are 1, 2, 3.

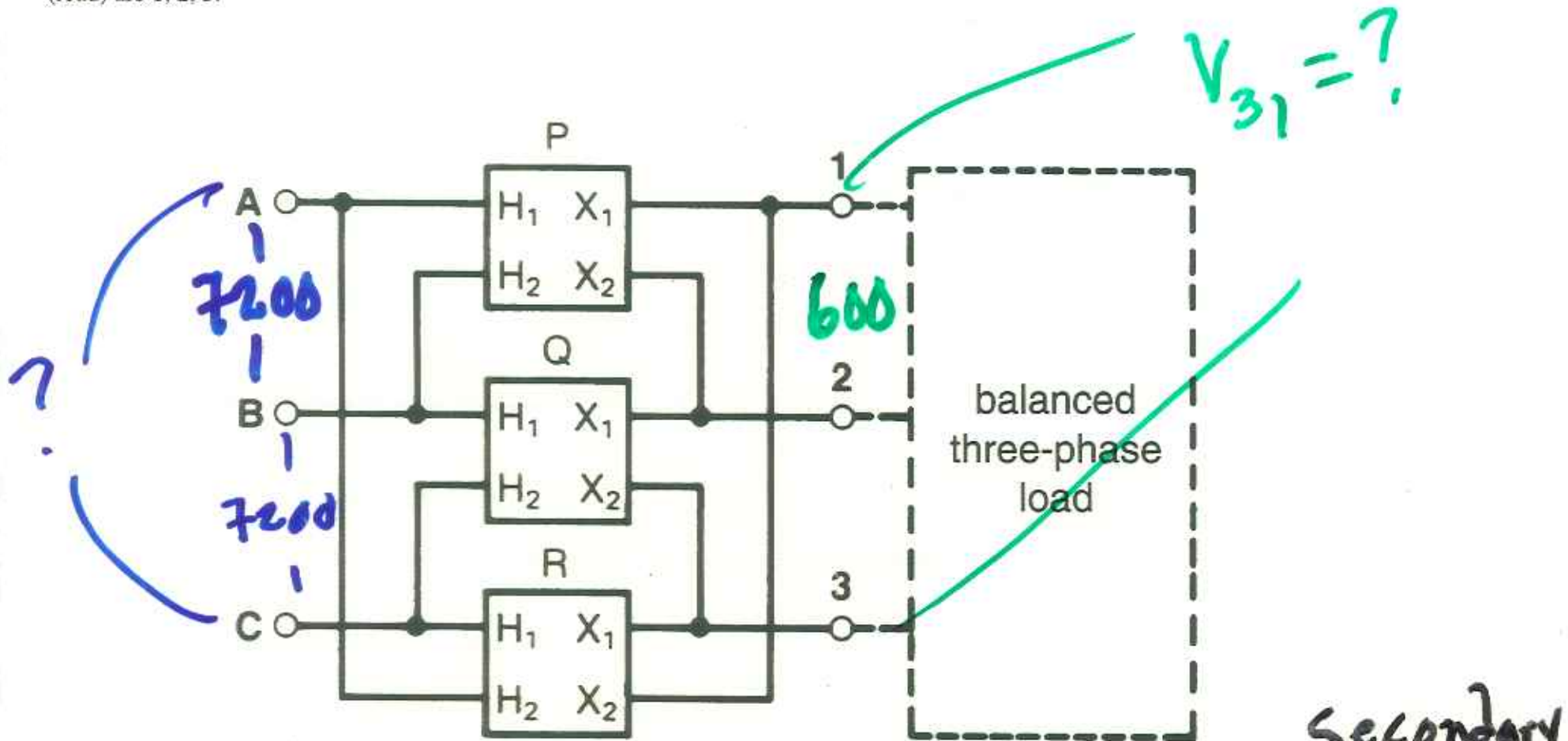

Suppose 1 Trf dies - Secondary opens
 What can a power engr do?
 Vout is 2 ϕ only?
 Sout is 2 S (trf)



Three 1 ϕ transformers: $S_{\text{max}} = 150$ KVA

$$I_{\text{max}} (600\text{V coil}) = \frac{150 \text{ KVA}}{600} = 250 \text{ A}$$

$$S_{3\phi}^{\text{max}} (600\text{V full } \Delta) = 3 (150) = 450 \text{ KVA}$$

$$I_{\text{line}} (600\text{V delta}) = \frac{450,000}{\sqrt{3} \cdot 600} = \sqrt{3} \cdot 250$$

Based on 3 ϕ relations

What if one 1 ϕ trf dies?

CAN we rewire two trf?

What do we get? 2 ϕ ? 2S?

2 Transformers each rated S


⇒ Should be able to deliver 2S to load

$$S_{load}^{3\phi} = \sqrt{3} \underbrace{I_e}_{\text{Not } \sqrt{3} I_{\phi} \text{ in open } \Delta \text{ but only } I_{max} \text{ (trf rating)}} \underbrace{V_{ll}}_{\text{normal}}$$

$$I_{max} = \frac{S}{V} = \frac{150 \text{ kVA}}{600} = 250 \text{ A}$$

NO ONLY 260 KVA

Open Δ: Each trf 150 KVA Rating

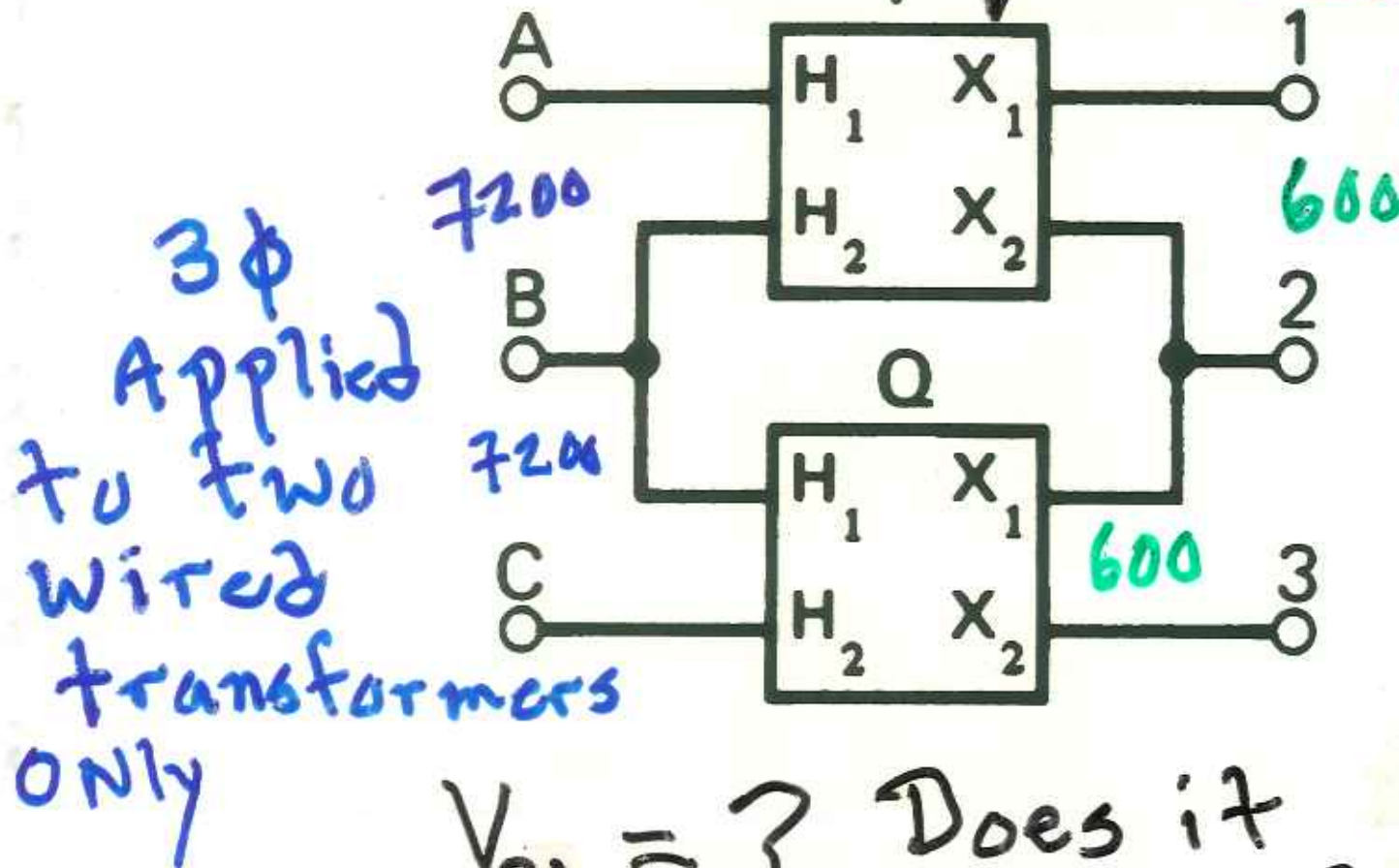

→ $I_{line\ max}^{(out)}$?
① 250 A

② $S_{max}^{(open\ \Delta)}$?
?

③ = 300kVA!
guess

$V_{31} = ?$ Does it exist?
 $V_{AC} = ?$

CAN we do better?
?


Given Each Trf 150 kV: ^{Two total}
 in Open Δ (Two cases)

Figure 12-8a Open-delta connection.

① General

Surprise: E_{out} has all 3 phases!
 V_{12}, V_{23}, V_{13}
 Can only deliver 86% of 2S w/o overheat!
 Why

3Φ in

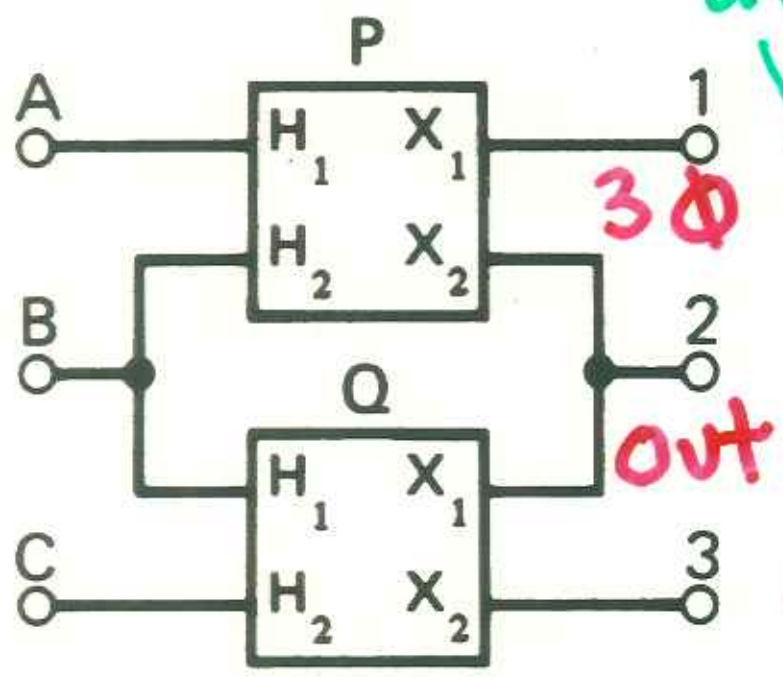


②

eg $V_{in} (l-l) = 7200$

$V_{out} (l-l) = 600$


each trf 150 MVA

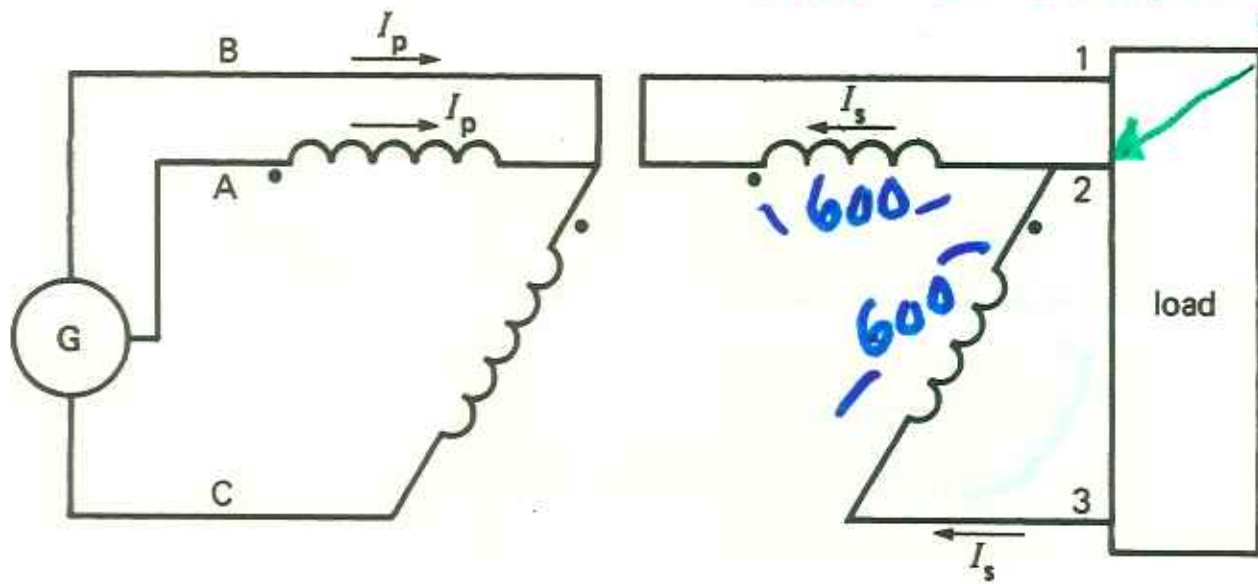$I(\text{load})$ only? \rightarrow I_{max} each coil
 $I(600) = 250\text{A}$ for
 all 3 lines of open Δ




$I_L \neq \sqrt{3} 250$
 $S_{\text{max}} (\text{open } \Delta)$
 $= \sqrt{3} V_L I_L$
 $= \sqrt{3} \cdot 600 \cdot 250$

$= 260\text{KVA}$

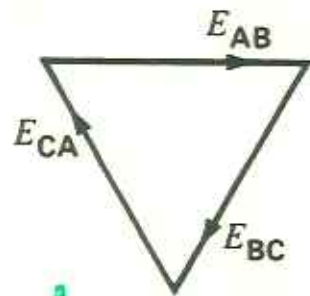

(b)

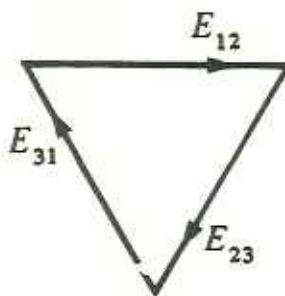


$S_{\text{max}} (\text{open } \Delta)$
 $\frac{260}{(2 S_{\text{trf}})_{\text{in}}}$

$= \frac{260}{2(150)}$

$= 86\%$
 of
 $2 S_{1\phi}$

Summary: Open Δ:

Figure 12-8b Associated schematic and phasor diagram.

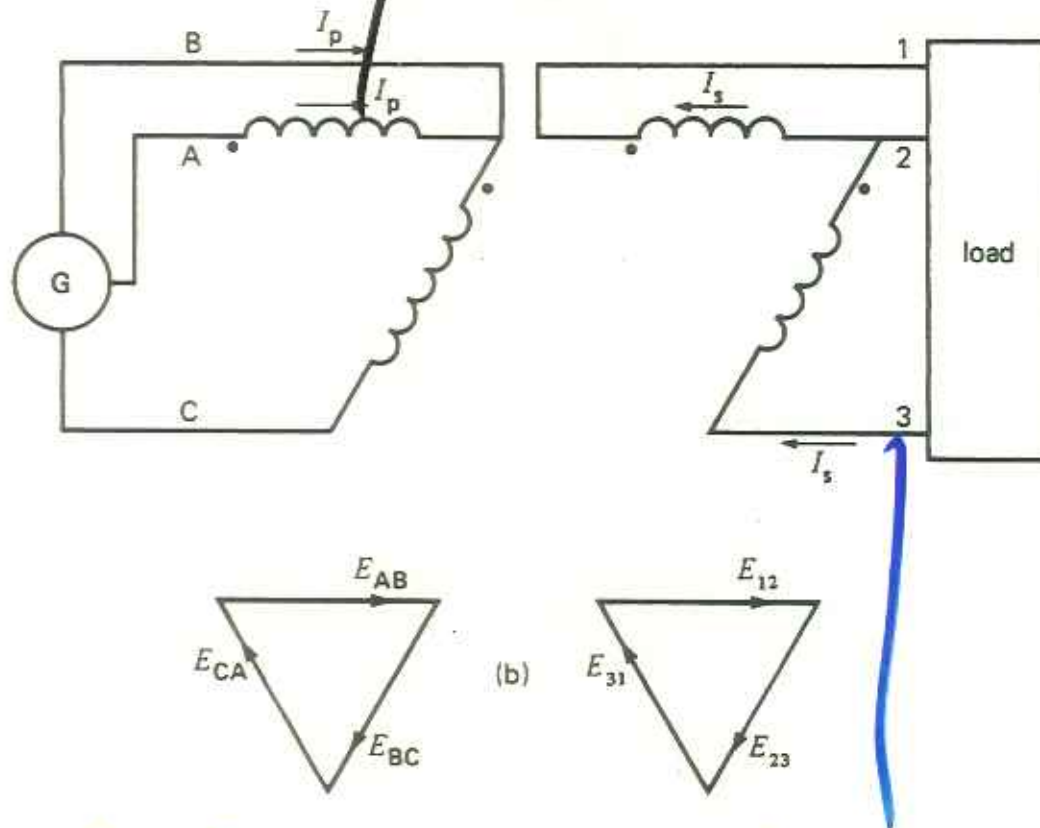

Two Trf
each
150 KVA

Delivers all $V_{3\phi}$
but
Open Δ
cannot

Deliver full
25 ϕ
Trf
only
86% of
25 ϕ
trf

$$I_L (\text{regular } 3 \text{ trf } \Delta) = \sqrt{3} I_\phi$$

$$I_{\text{line}} (\text{open } \Delta) = I_{\text{max}} \phi$$

NO $\sqrt{3}$ possible



Differ by $\sqrt{3}$

Two Trf $S = 250 \text{ kVA}$ } each
 $2.4 \text{ kV} / 600 \text{ V}$ $4:1$ } trf

Open Δ $I_{\text{line}} = I_{\text{coil}}$

$\Delta : \Delta$

12-8

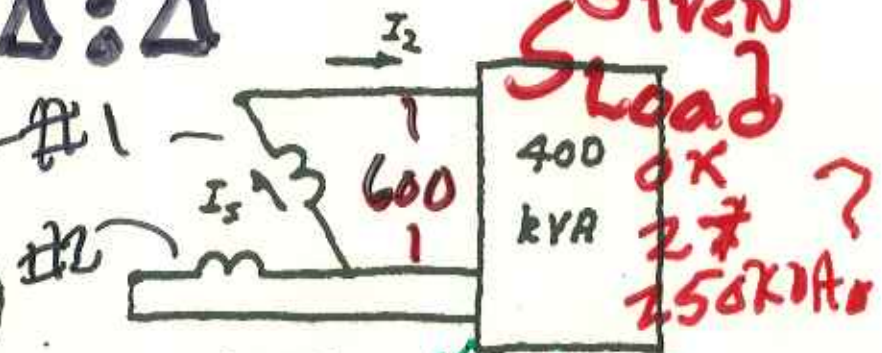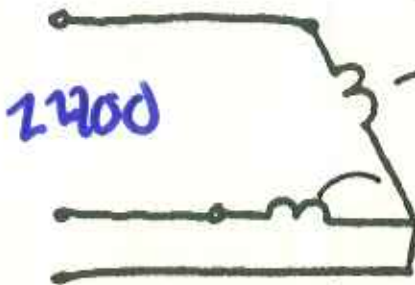

Load pulls 2.4 kV
 $I_e = I_2 = \frac{400 \times 10^3}{600 \sqrt{3}} = 385 \text{ A}$

KEY
 Open Δ trf
 $I_e = I_p$

Nominal value of $I_s = \frac{250 \text{ kVA}}{600} = 417 \text{ A}$
Rated only by single coil

a. The transformers are not overloaded

b. The max load is $417 \times 600 \times \sqrt{3} = 433 \text{ kVA}$.

in open Δ wiring
 Close to overload
 For open Δ be careful
CANNOT USE $S = 500 \text{ kVA}$

Exam!


Sum
 two
 250 kVA

Nameplate Specs or Trt rating

$S = 50VA, 120/12.8$ } low voltage

11-12

Apply

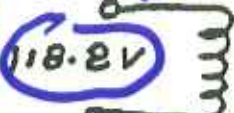

Measured at "no load"

Turns ratio = $118.8/13.74$

$\frac{N_s R_s / A_s}{N_p R_p / A_p} = R_s a = 8.646$

If 120V is applied to primary, the secondary voltage would be $120/8.646 = 13.88V$. The 13.88V

at no load is higher than the 12.8V shown on

a) the nameplate. The reason is that when the transformer is loaded, the internal voltage drop due to the resistance and leakage reactance of the windings, will cause the secondary voltage to fall to about 12.8V at full load. $I_{max} = S/V_0$

$\frac{120}{N_1} = \frac{12.8}{N_2}$



ONLY WHEN load draws i

$a = \frac{N_1}{N_2} = \frac{120}{12.8} = 9.375$

Expect 15.2 reflected into secondary is $15.2 \frac{1}{a^2} = 2.09$

ideal I^2R losses are balanced
in primary and sec

$$I_p^2 R_p = I_s^2 R_s$$

11-13 In an ideal transformer, the I^2R losses
in the primary and secondary should be
about the same. Based on the 120V winding

resistance, the calculated versus resistance of the secondary should

be $15.2 \Omega \times \left(\frac{1}{8.646}\right)^2 = 0.203 \Omega$. The actual

value is 0.306 Ω . Consequently, we are led

to the conclusion that the LV winding is wound

on top of the HV winding, because that way

the mean length per turn is greater.

Subtle but true

$$R = \frac{\rho l}{A} \text{ (for 1 turn)}$$


depends what
you wind around
core or (core
plus
coil)

Prior
Big S_{load} but limited

S_{Trf} Problem (I) Use 2


in Parallel. Assumes S_{load}
matches S_{source}

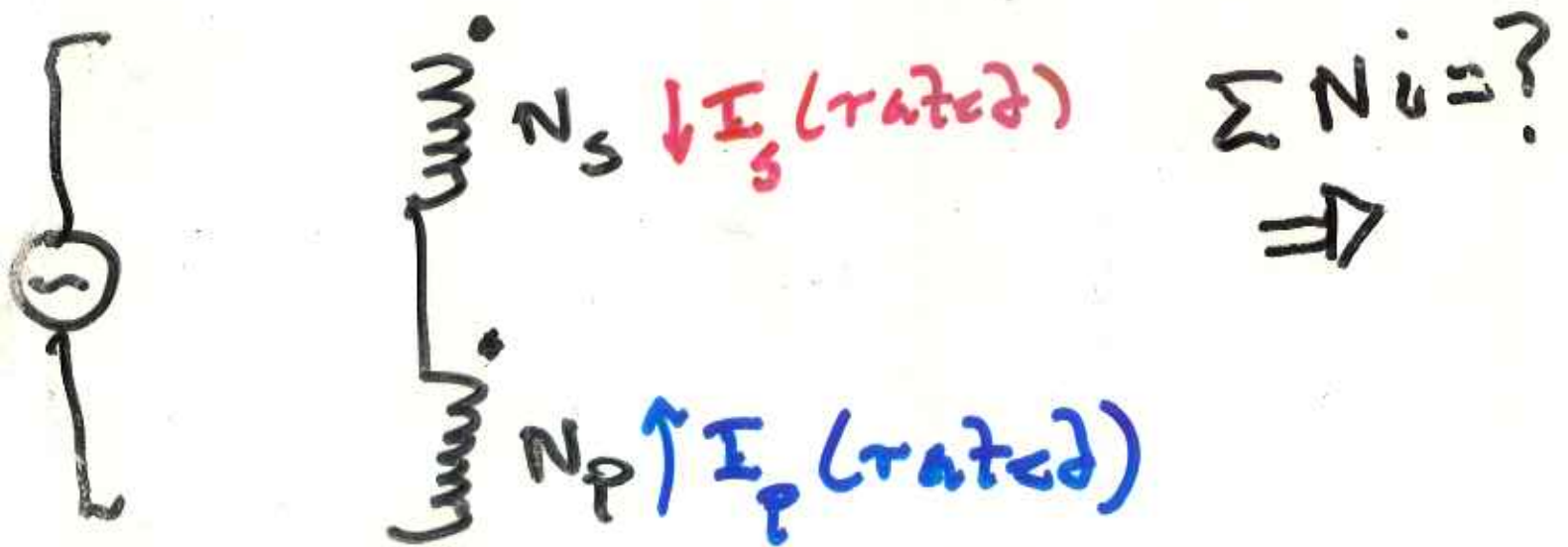(II) Stretch thinking use 1 Trf
in a clever way 😊



How to wire for
maximum S_{load} ?

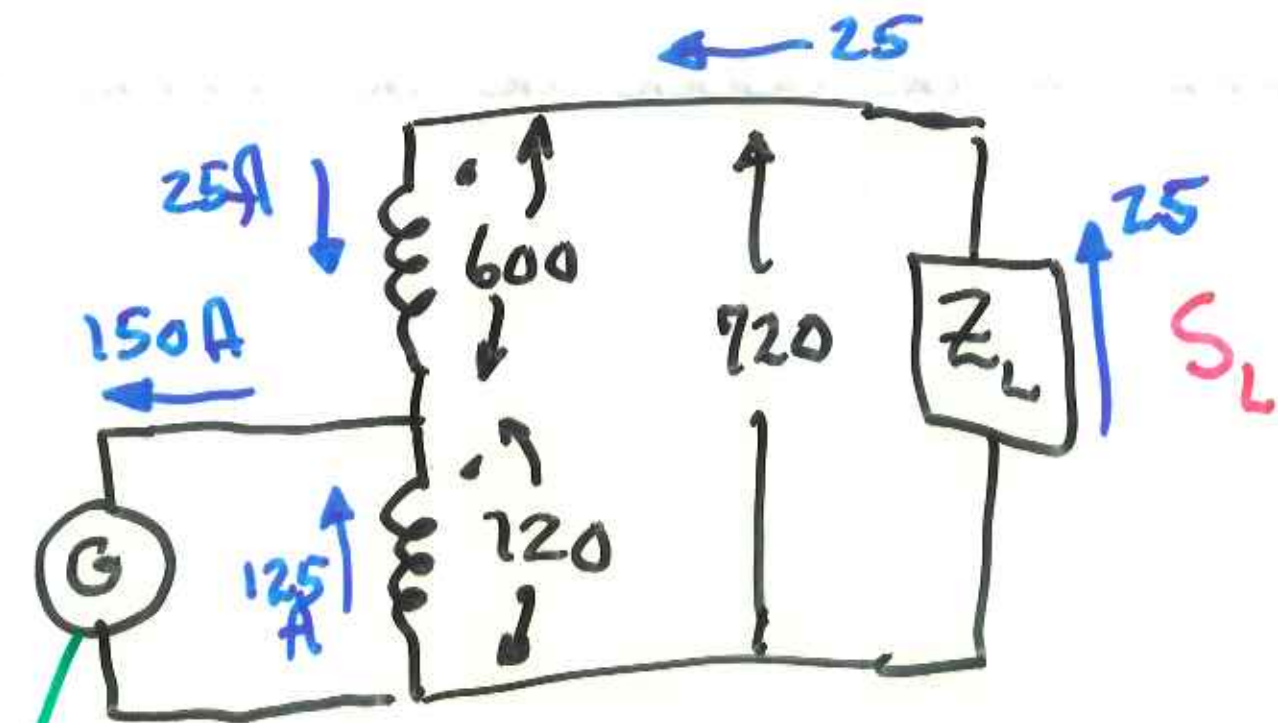Can get $S(\text{load}) > S(\text{trf})$?



$$S_o = (120)(150) = 18 \text{ kVA}$$

$$S_L = (720)(25) = 18 \text{ kVA}$$


Yet S (transformer) is only 15 kVA

Transformer $S = 15 \text{ kVA}$ sets I_{max} ONLY

Dots for both V_{load} & I_{load}

Applied source delivers 60 kVA easy eg 100 A
Trf I_{max}


125 A

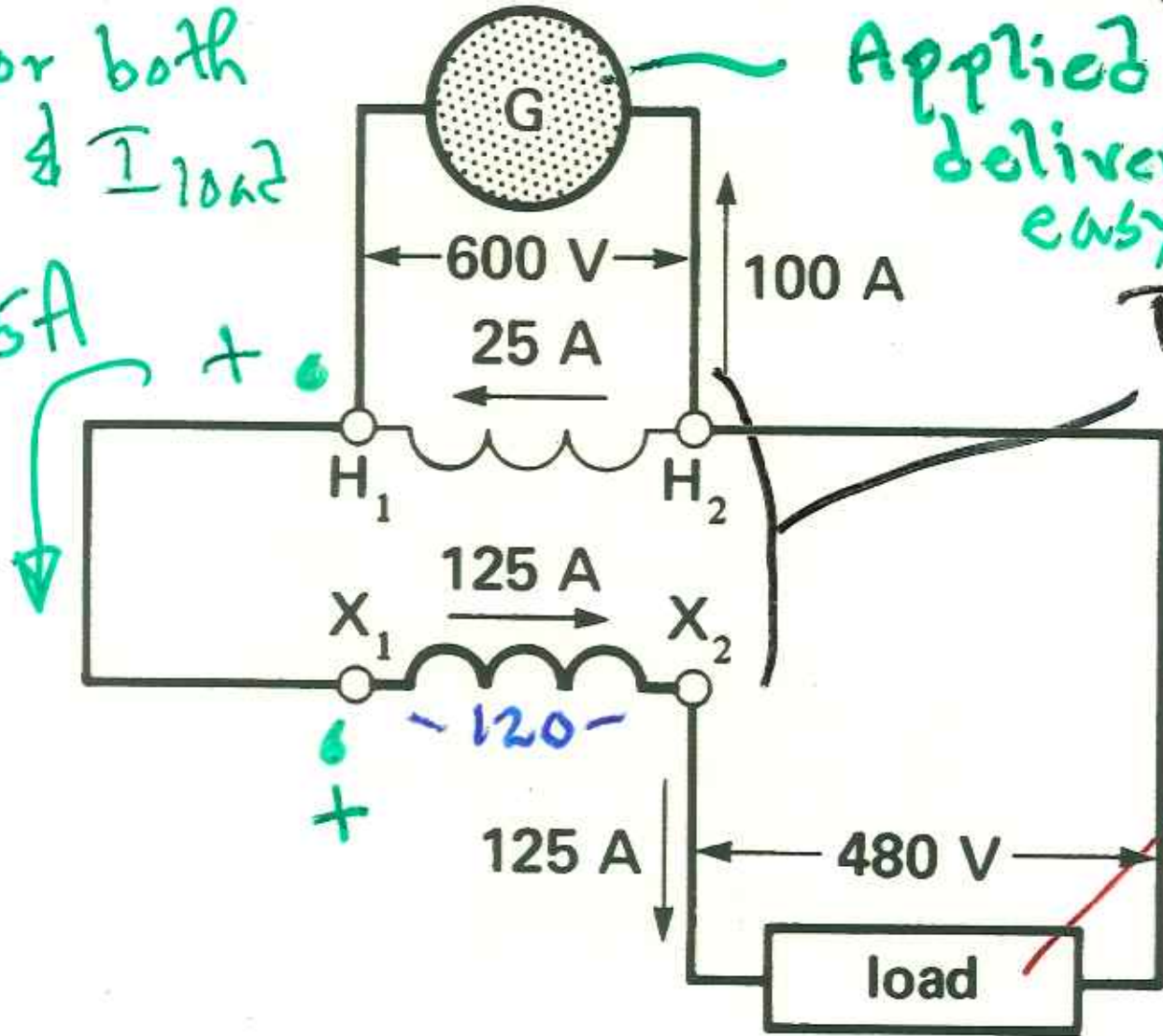


load SINKS $S = ?$
 $(125) 480$
60 kVA

S_{Trf} (VS) 15 kVA

S_G S_L
60 kVA

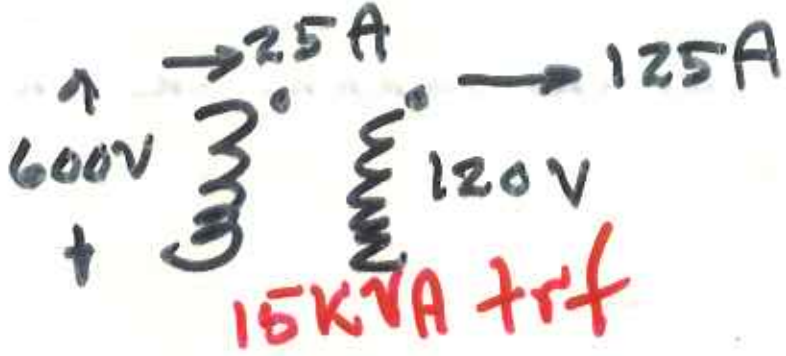

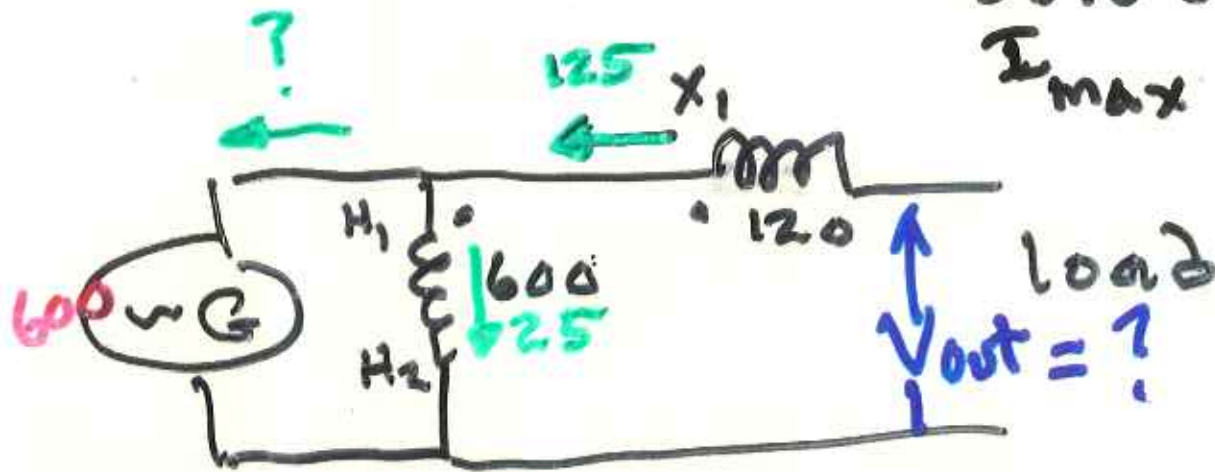$S_{max} = S_{max}$
 $P_{in} = P_{out} = 15KVA$
 for both coils
 Dots on coils for
 I_{max} directions




$P_{out} = ?$
 $I_{out} = ?$

$P_{in}^{max} = ?$
 $P_{out}^{max} = ?$
 60KVA

$P_{out}^{max} = (125)(480)$
 60KVA


Any objections to the following?

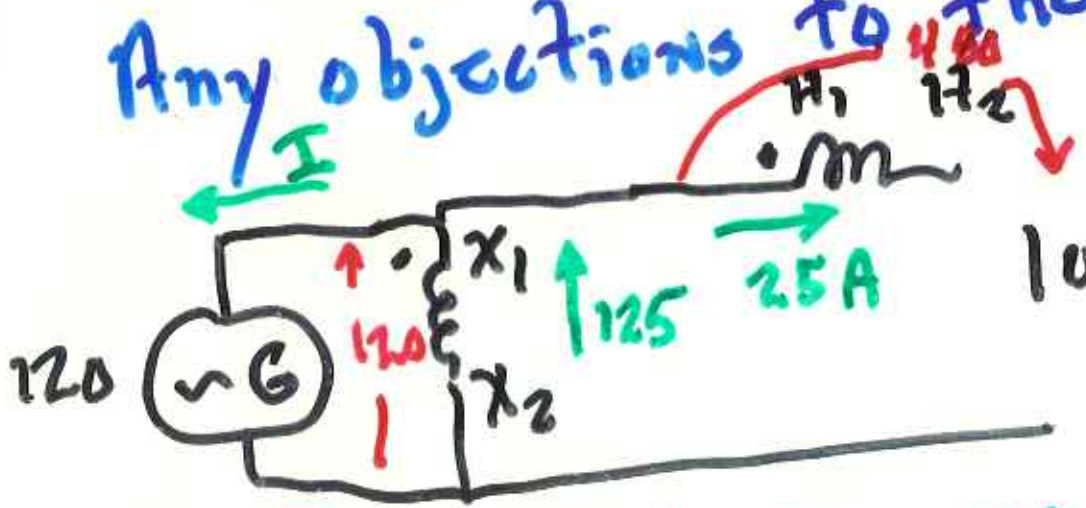

$P_{out} = (25) * 480$
 $= 12KVA$

$P_{in} = (120)(120) = 12KVA$

Third Case

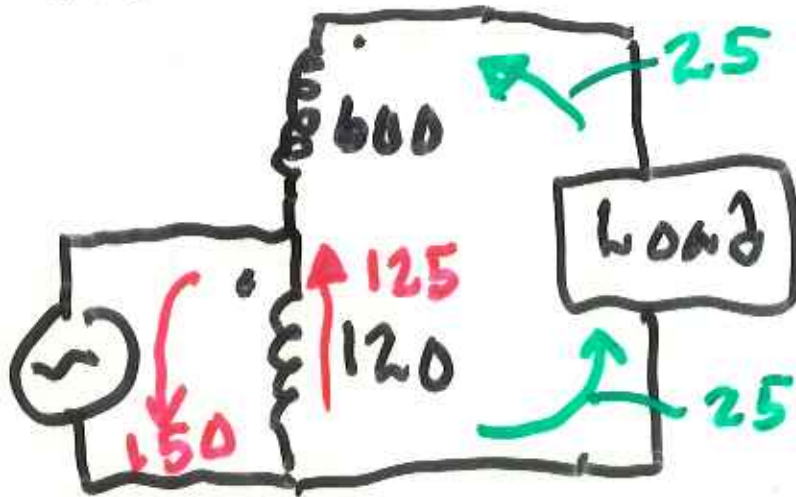


Dots on coils tell I_{max} directions

$$P_{in} = (150)(120) = 18 \text{ KVA}$$

$$P_{out} = (25)(120) = 18 \text{ KVA}$$

Fourth

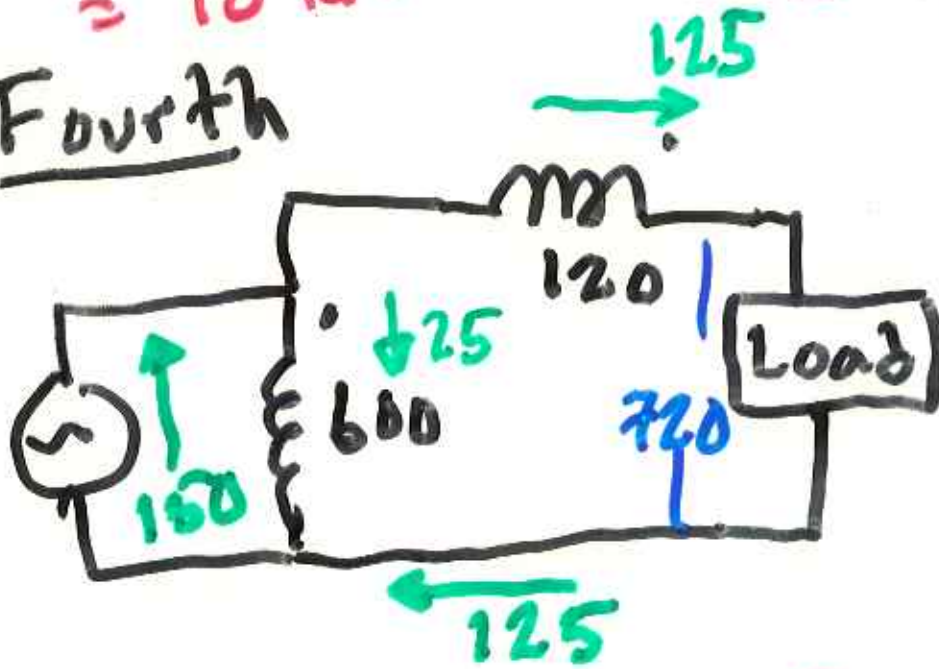


Dots on coil I_{max} directions

$$P_{in} = 150(600) = 90 \text{ KVA}$$

$$P_{out} = (125)(720) = 90 \text{ KVA}$$

$I_{IN} @ 600$; 720 sum winding / wiring

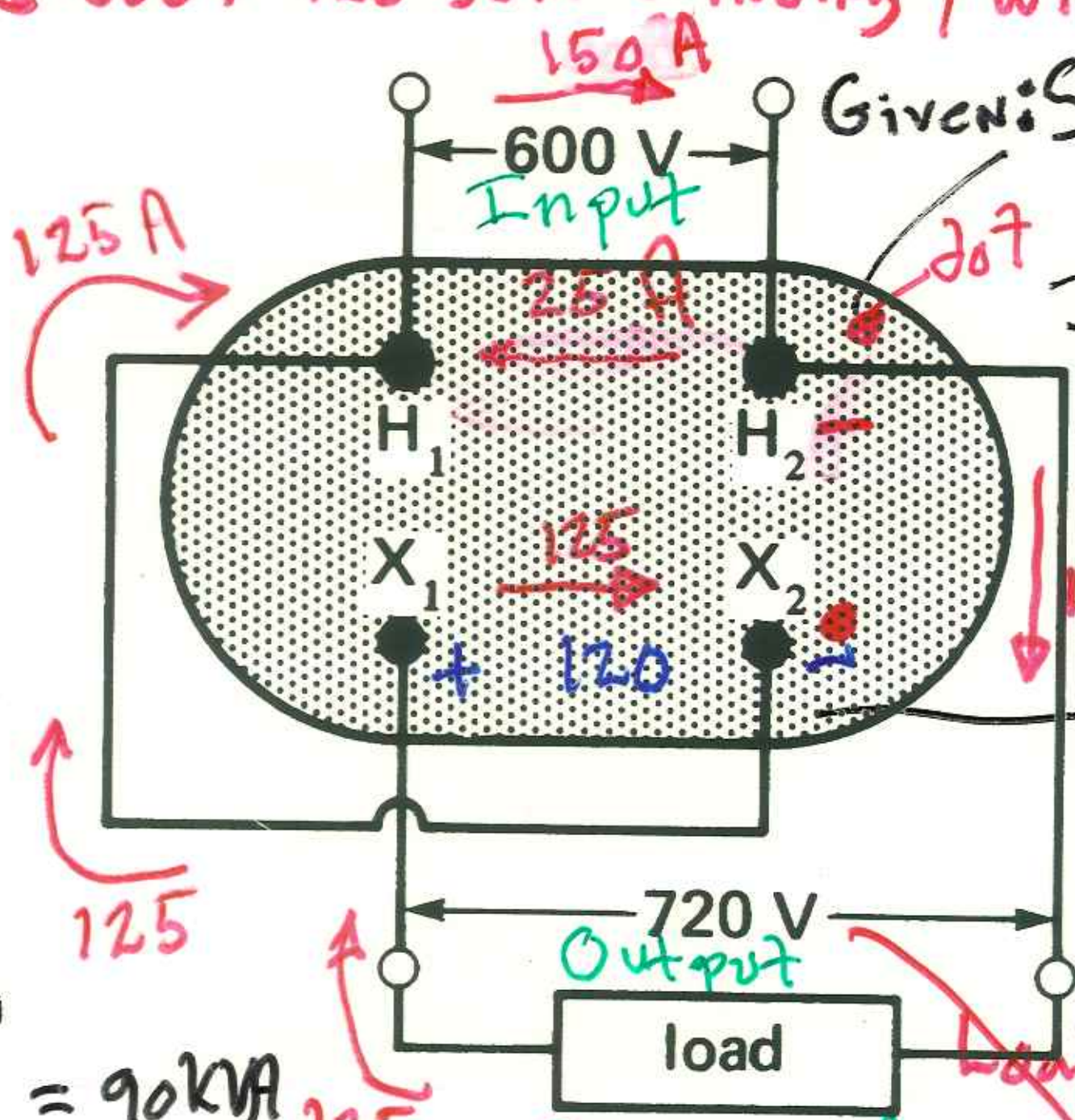

Given: $S_{Trf} = 15 \text{ kVA}$

$I_{max} = ?$
H₁-H₂
i through coil H

$I_{max} = ?$
X₁-X₂
i through coil X

Load sum of coil voltages

Again
 $S_{IN} = S_{out} = 90 \text{ kVA}$
done with 15 kVA trf

90 kVA capable

15 KVA rated transformer

600V coil \Rightarrow 25 A max

120V coil \Rightarrow 125 A max

New wiring possibilities!

Wire coils so $V_{out} = V_p + V_s$
or $V_{out} = V_p - V_s = 480$ 720V

Choose $V_{in} = 600V$

Load across 720V or 480V


$I_{out}^{max} = ?$

15KVA
of limit
of transformer

Your gran P_a did better!

90KVA! How? Δ Sources are not limited

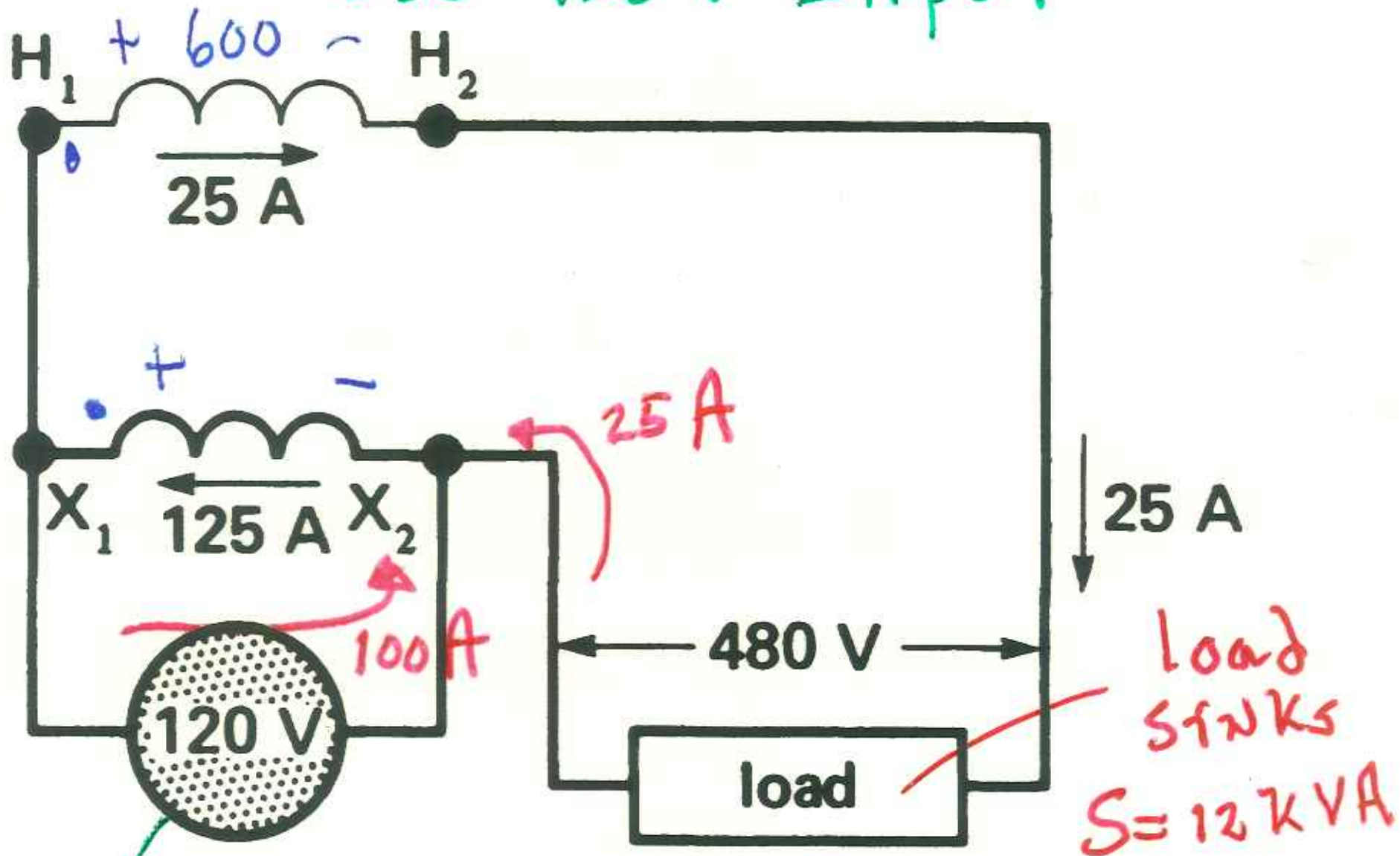$I_{IN} @ 120$: Given winding / wiring 480
 Use 120V Input




Source provides $S = ?$
 $I = ?$ vs S_{trf}

Auto Trf: Intro ①

$$E_2 = \frac{N_2}{N_1} E_1$$

Figure 11-3 Autotransformer having N_1 turns on the primary and N_2 turns on the secondary.

turns = ?

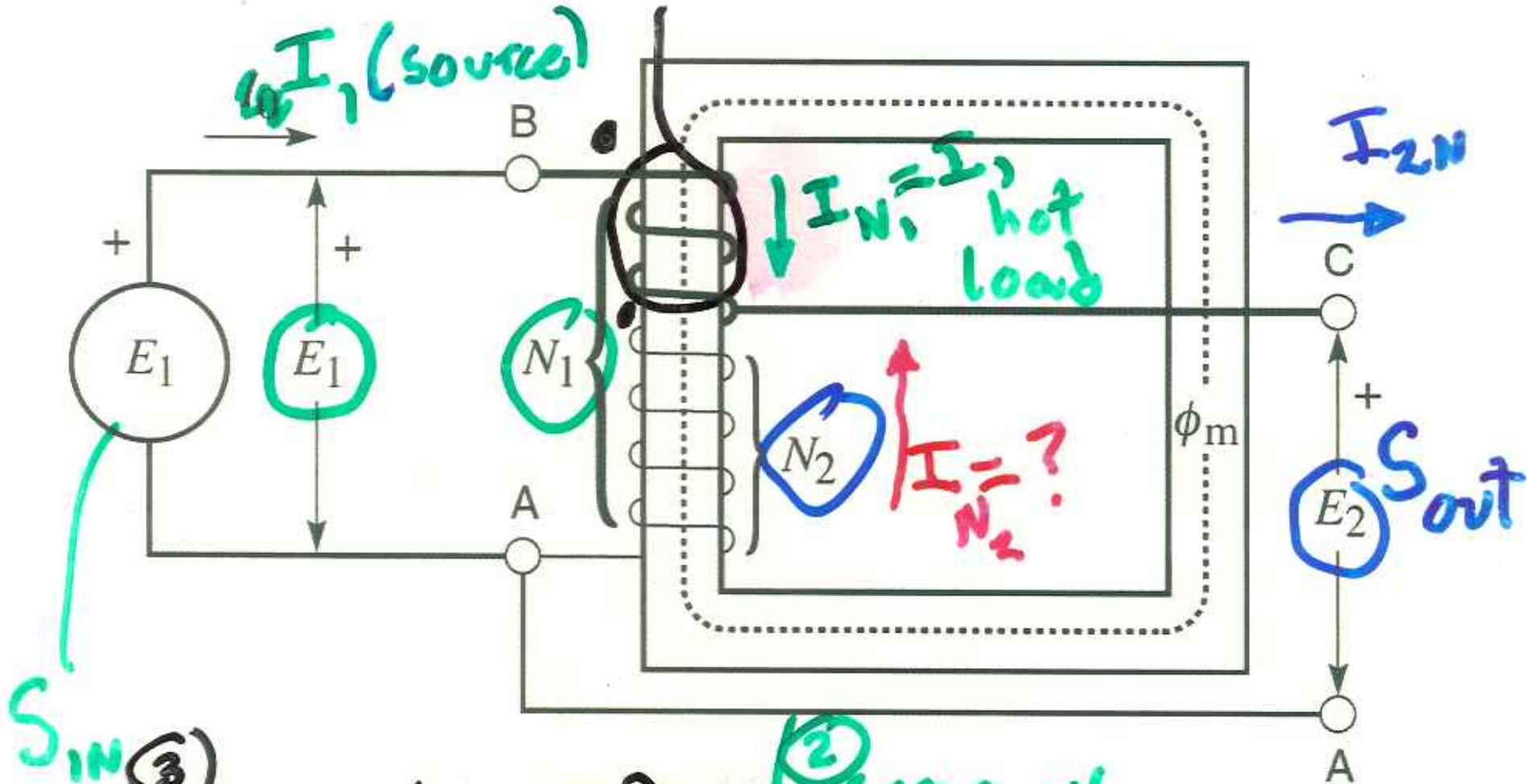


S_{IN} ③

I_1 into $(N_1 - N_2)$ coil
 I_{N_2} out of N_2 dot

② Common ground E_1 & E_2

Relation $I(N_1 - N_2) = ?$ $I(N_2) = ?$

Figure 11-4 Autotransformer under load. The currents flow in opposite directions in the upper and lower windings.

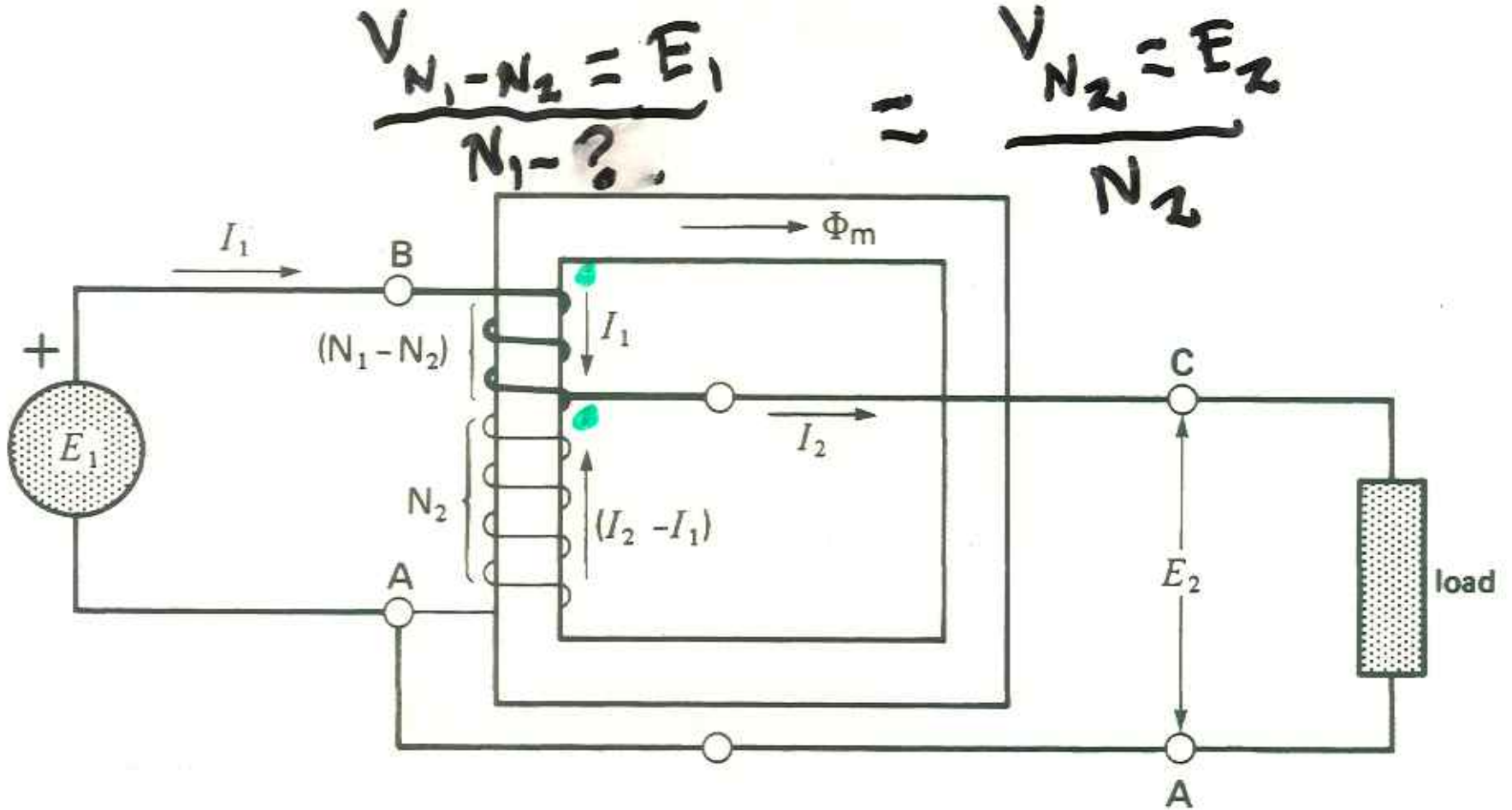

$$I_1 (N_1 - N_2) - (I_2 - I_1) N_2 = 0$$


$$E_1 / N_1$$

Another Equation

$$S_{IN} = S_{OUT}$$

$$(12)(300) = (15)(240)$$

Figure 11-5 Autotransformer of Example 11-1.

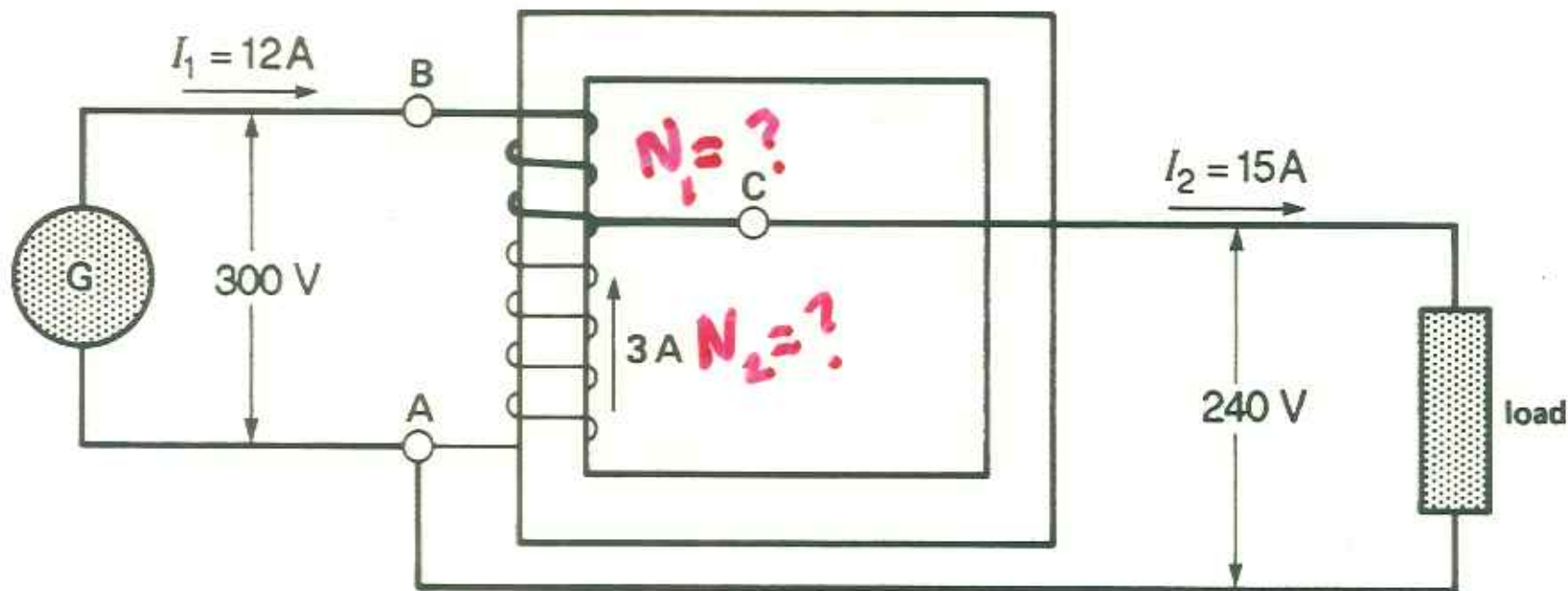

$$I_{max} = \frac{15,000}{600} = 25 \text{ A}$$

$$I_{max} = \frac{15,000}{120} = 125 \text{ A}$$



Wire additive or subtractive
 $V_{out} = V_H \pm V_L$
 720 **Add**
 or
 480 **Sub V**

Two V_o and two V_{in}
 For $V_{out} = 480$

\Rightarrow @ 600V input
 $I = ?$

V_{in} @ 600 coil
 @ 120 coil

I_{out} and S_{out} two cases

I_{out} @ 480 could be either:

$I(480) = 25 \text{ A}$ to load

$S = 1.8 \text{ KVA}$

$I(480) = \text{full } 125 \text{ A}$ to load

$S = 60 \text{ KVA}$

Consider



$S = 15 \text{ kVA}$ coils

We will show that:

(1) We can arrange "dots" on coils and wire for

$$V_{out} = \begin{matrix} 720 \\ 480 \end{matrix}$$

OK?

600

120

(2) We can wire load for

$$I_{out} = \begin{matrix} 125 \text{ A} \\ 100 \text{ A} \end{matrix}$$

OK?

150 A?


$$S_{out} = \begin{matrix} 90 \text{ kVA} \\ 60 \text{ kVA} \\ 18 \text{ kVA} \end{matrix}$$

S_{in} must match

? Use 15 kVA trf/coils for all?

Windings for

$I_{load} = 125 A$
 $S_w = 60 KVA$

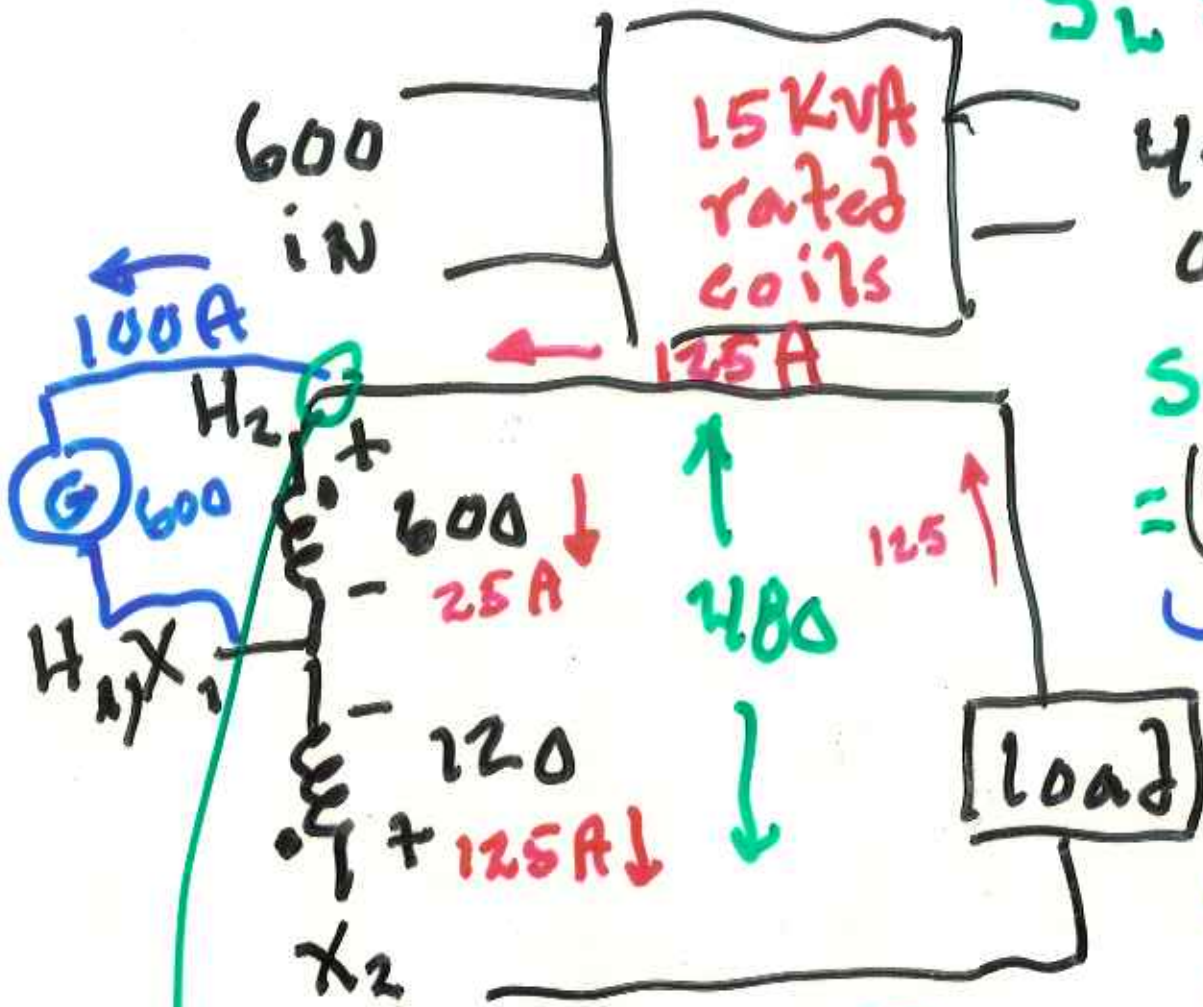

$480 \text{ out} \} V_H$

$S = 60 KVA$
 $= (480)(125)$


How avoid energy conservation?

120V coil feeds load

Σ currents balances

G provides $S_{in} = 60 KVA = S_{out}$
 through a 15 KVA trf

Figure 11-8 Schematic diagram of Fig. 11.7 showing voltages and current flows.

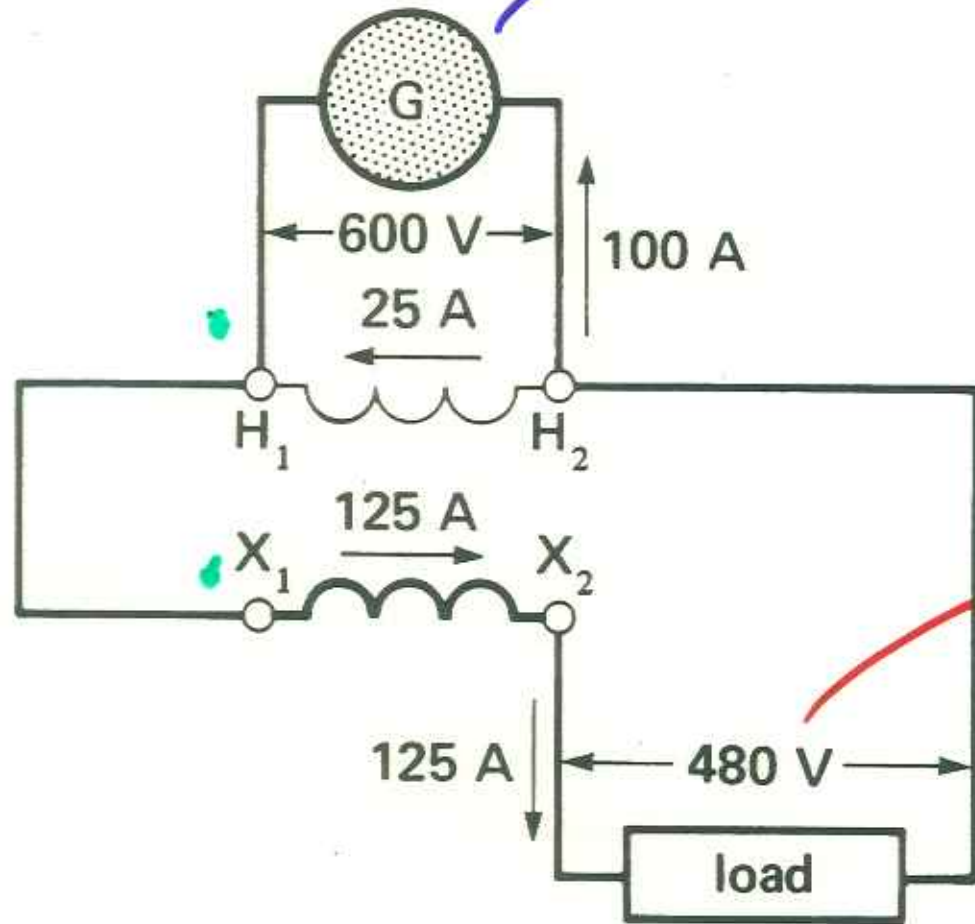


Summary Insights


480 V out

Figure 11-7 Transformer reconnected as an autotransformer to give a ratio of 600 V/480 V.
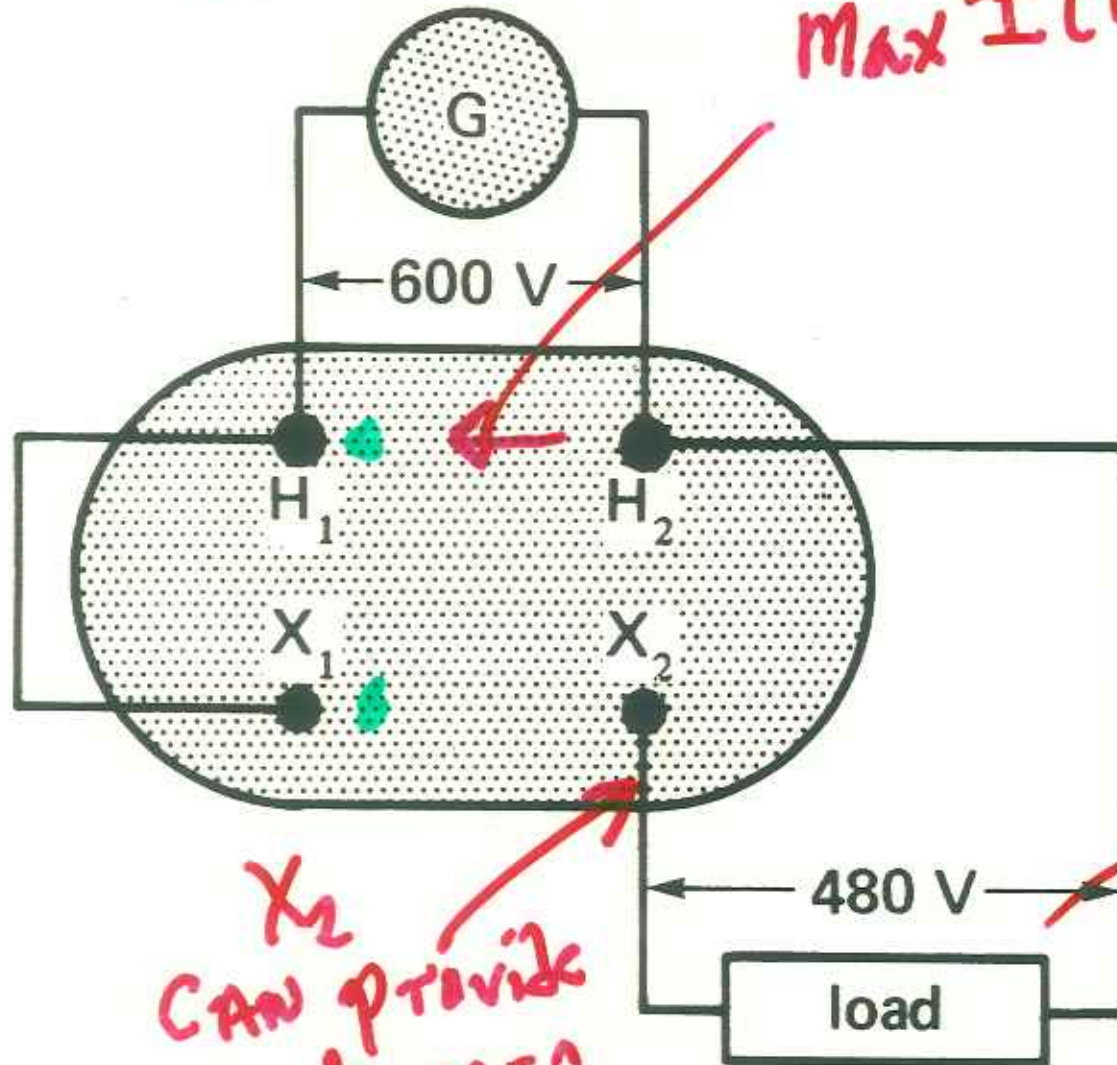
$$\text{Max } I(H_1 - H_2) = 25 \text{ A}$$




$$S_L = 90 \text{ KVA}$$

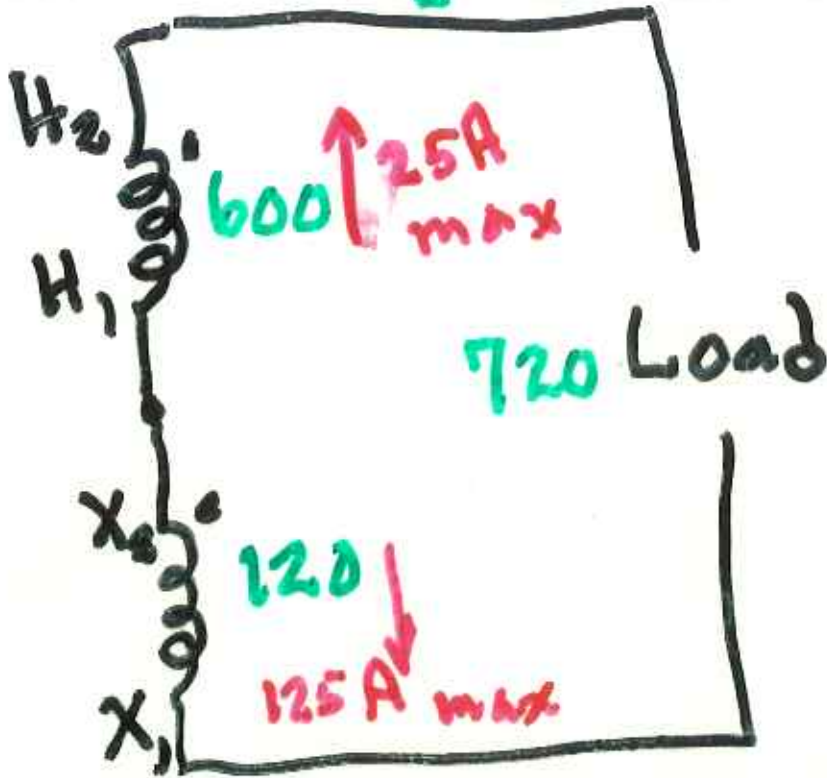

Phasing on I's

Place **G** on either H or X

H case

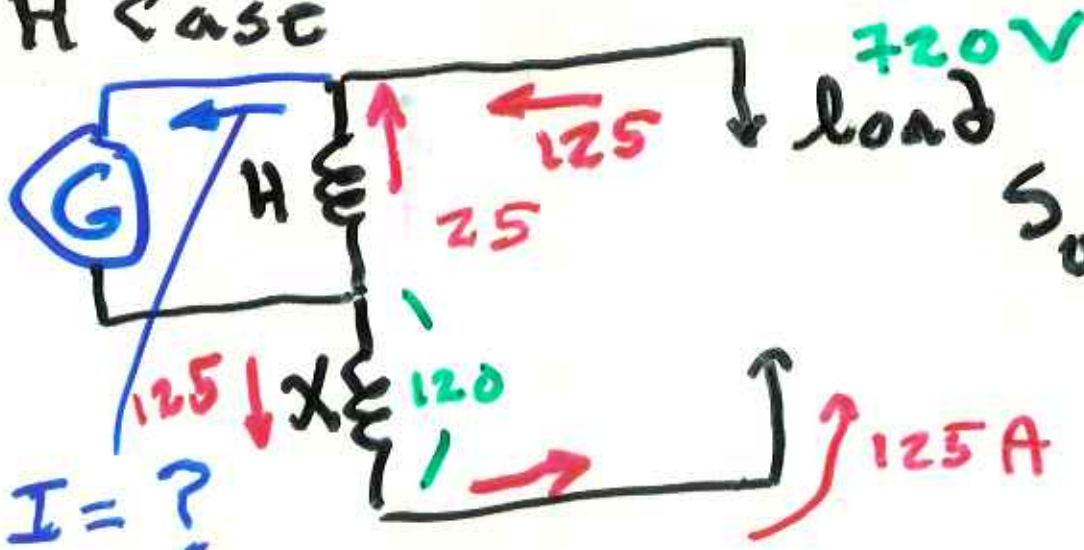

$$S_{out} = (720) 125 = 90 \text{ KVA}$$

$I = ?$

Must be }
 $\xrightarrow{150 \text{ A}}$
 from G

$$S_{in} = (600) 150 = 90 \text{ KVA}$$

Figure 11-9 Transformer reconnected to give a ratio of 600 V/720 V.


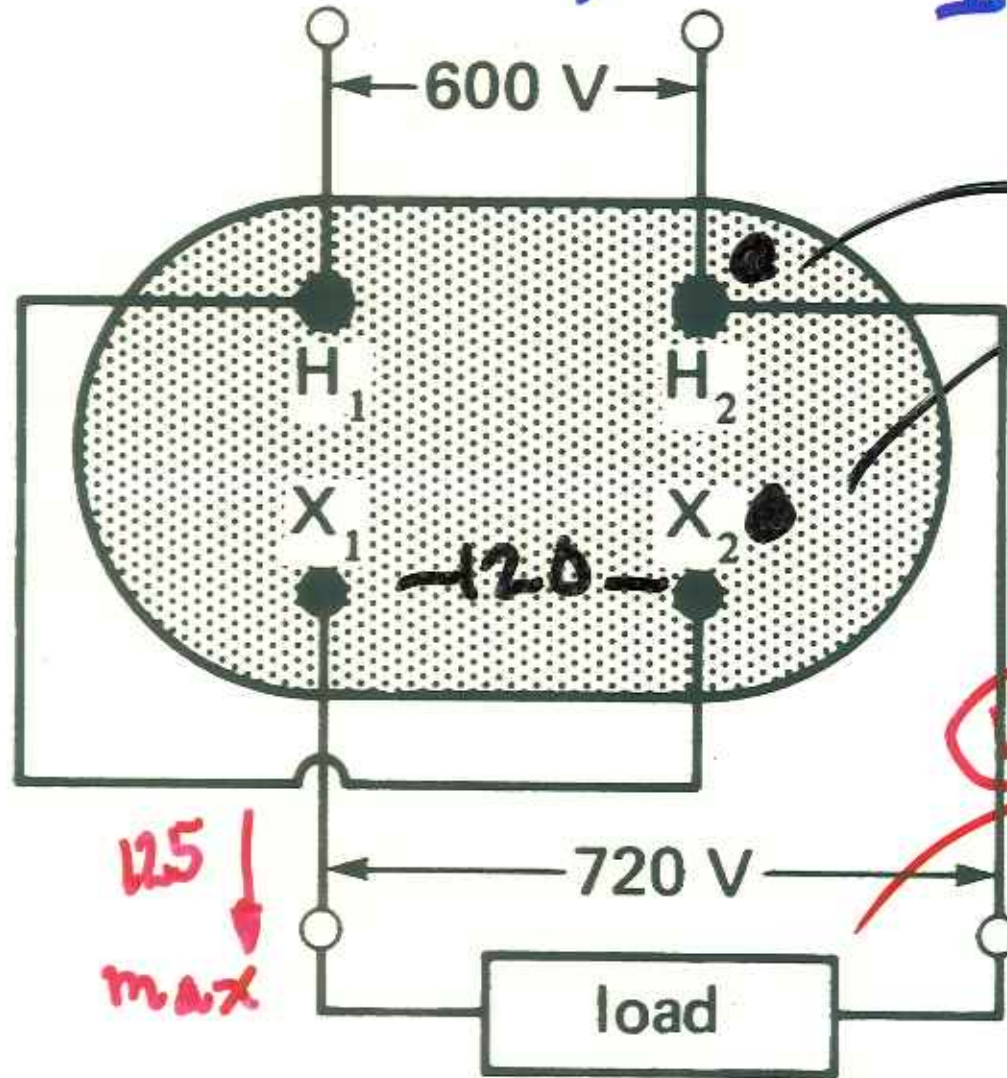


Figure 11-10 Transformer reconnected to give a ratio of 120 V/480 V.

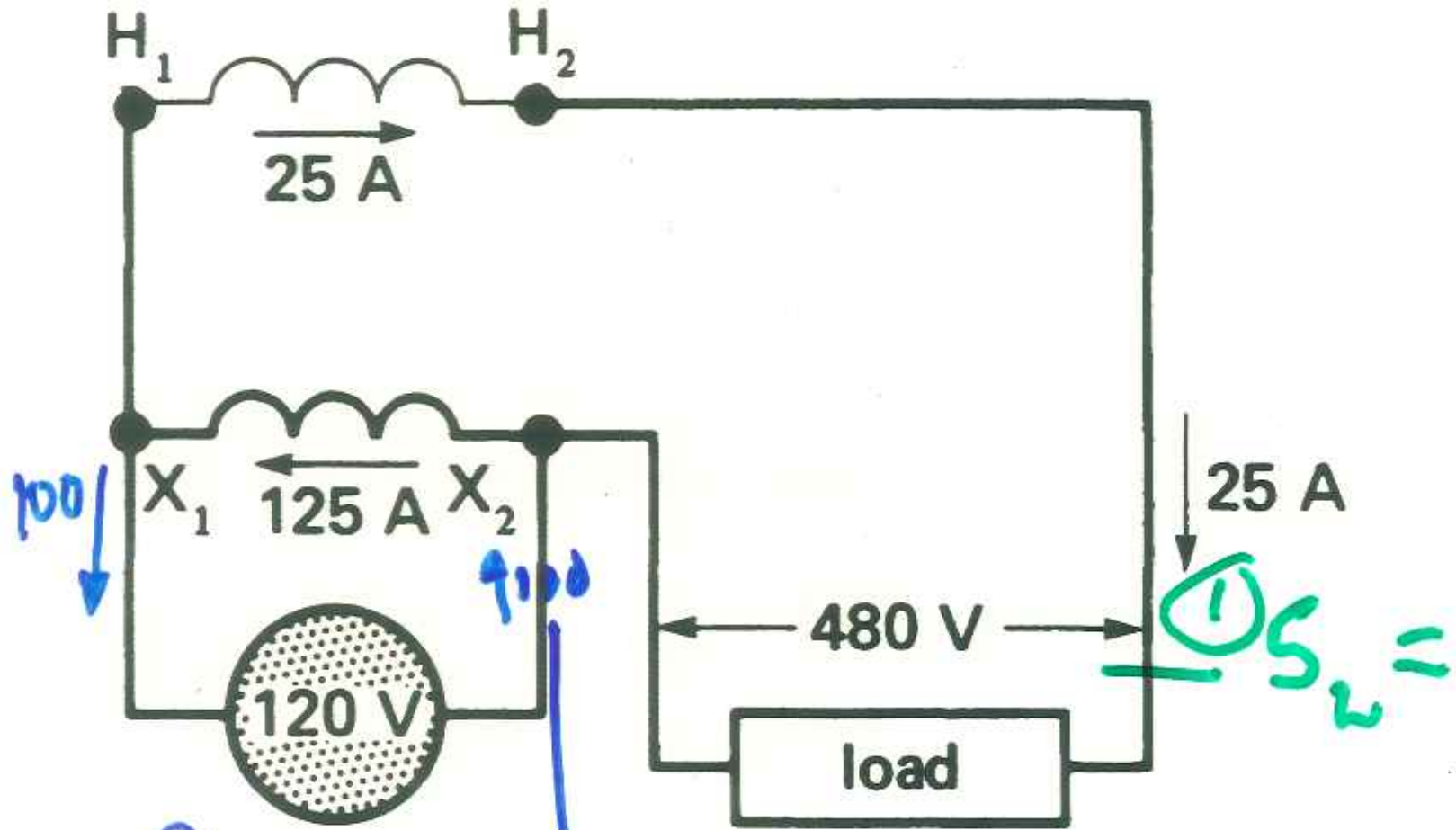

② $S_{120} = ?$, $I_{120} = ?$

$S_{120} = 12 \text{ kVA}$ $I = 100$

$S_L = 12 \text{ kVA @ 480}$