

Chapter 8b

Topics:

- Talks
- Three Phase Review
 - Wye
 - Delta
- Homework
- Unbalanced Three Phase




CALDWELL...

*"That's my favorite story. But tonight
I'd like to hear both sides."*


Nuclear vs Solar vs Coal
vs Wind




Meet Sad Socket

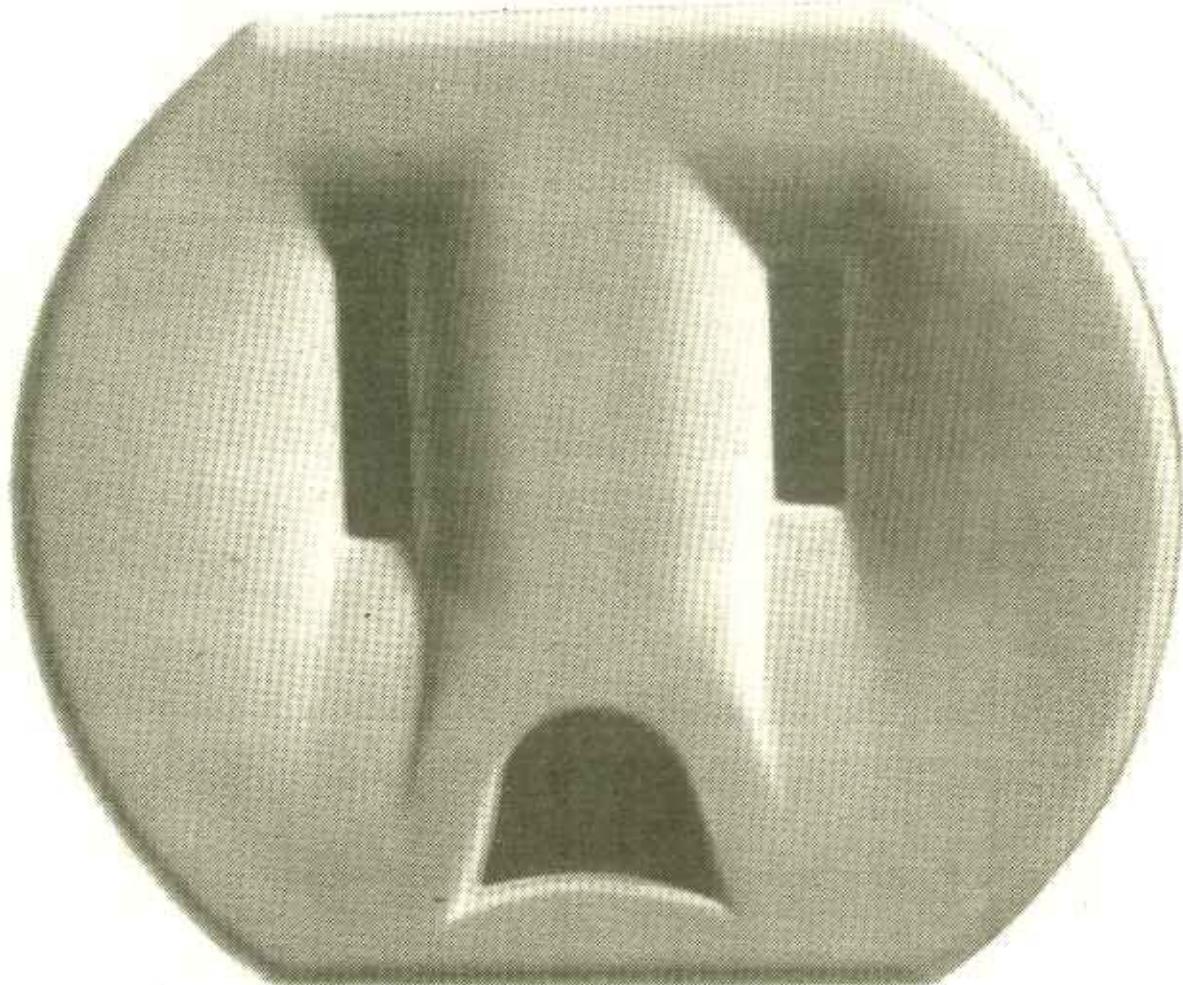


Sad Socket

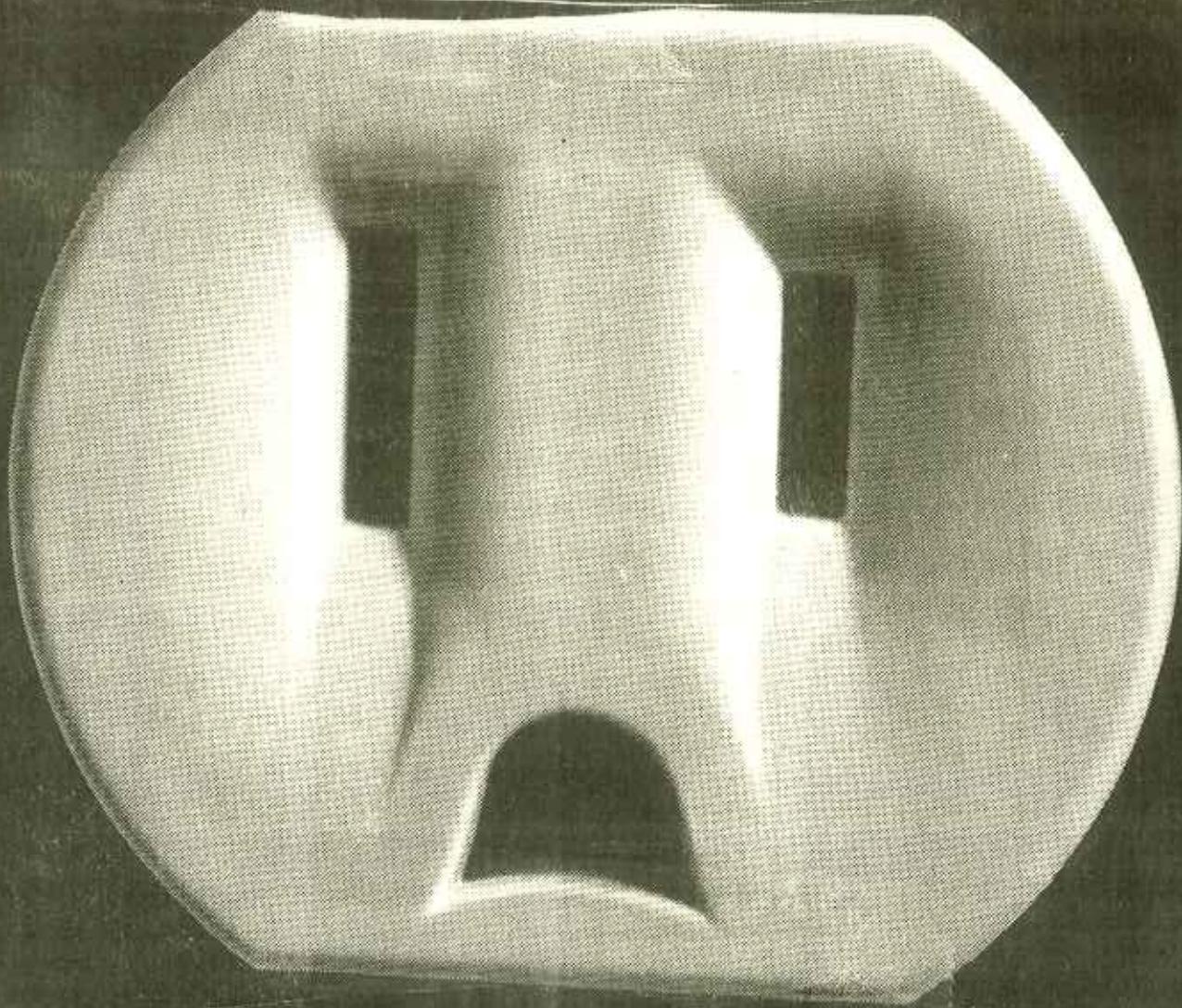


Gets Smart

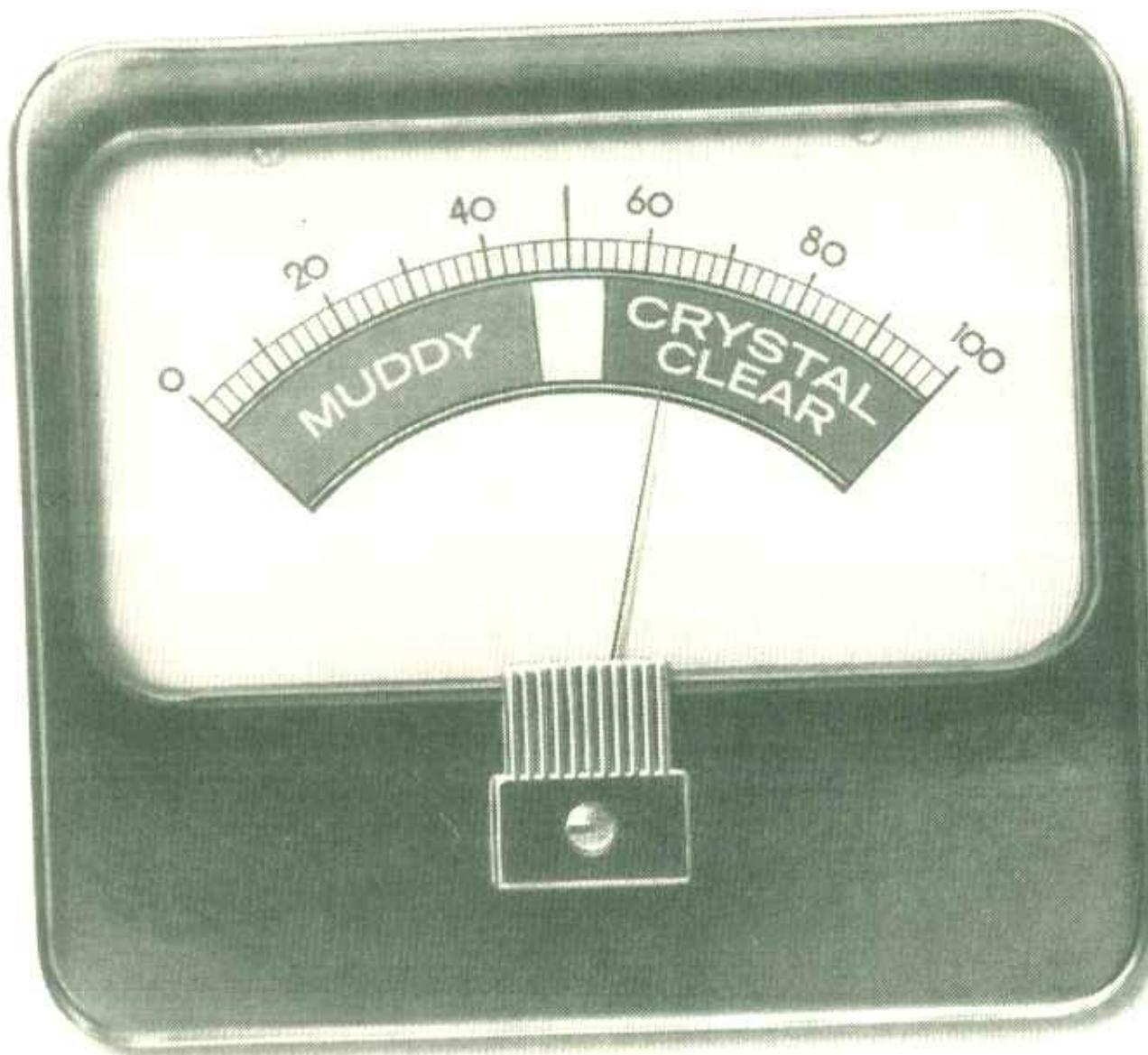


CLARITY

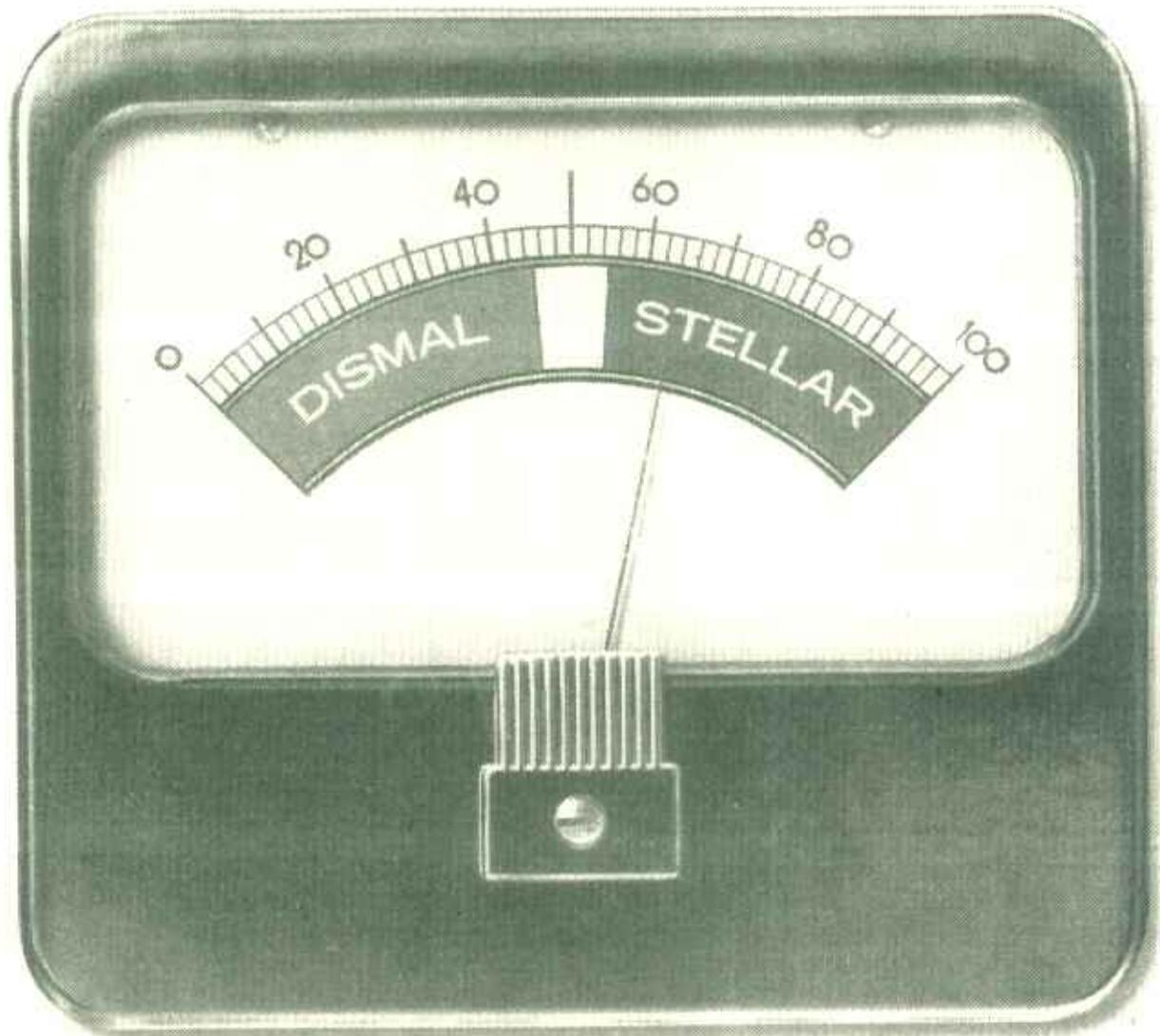

• PERFORMANCE •

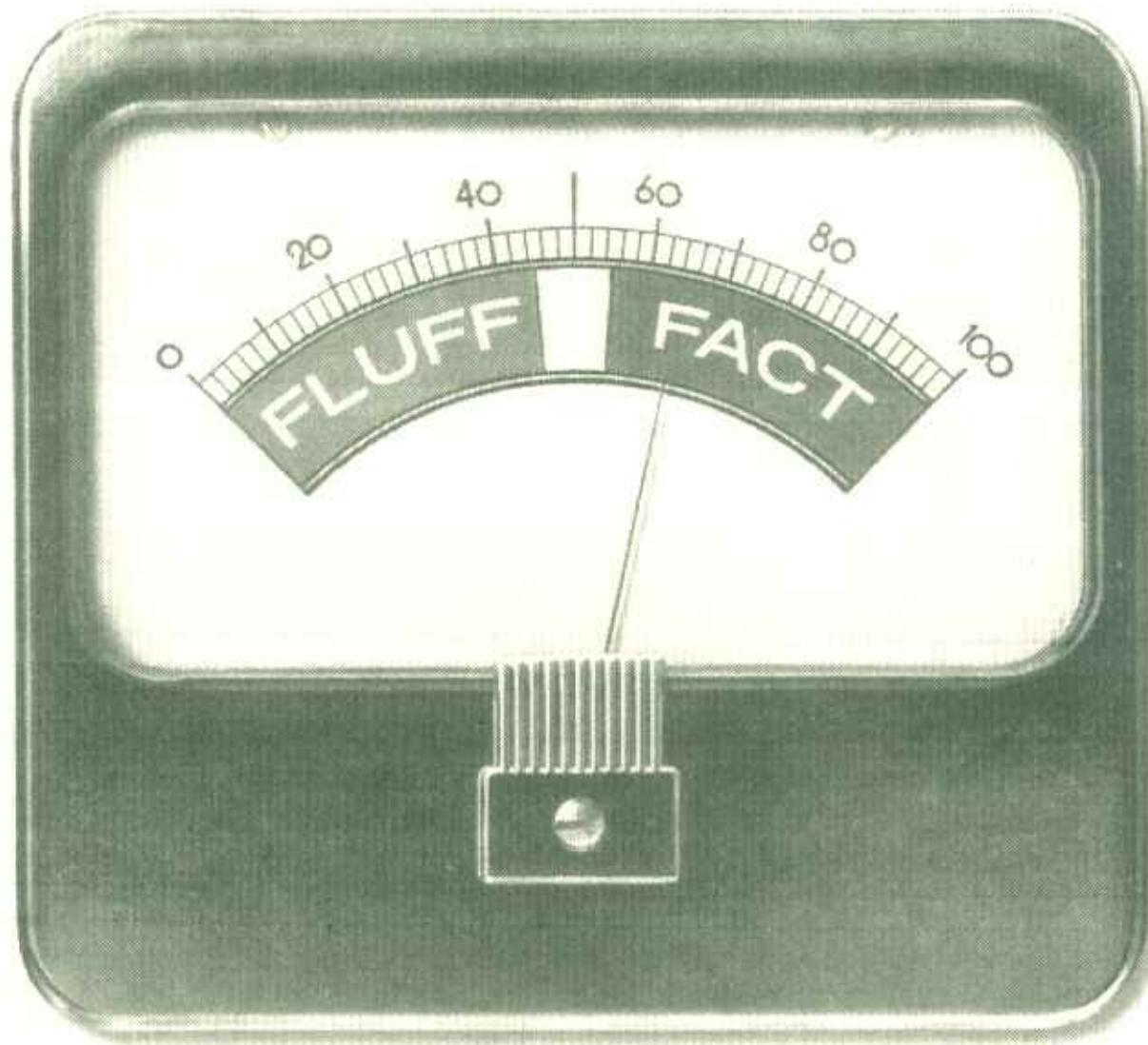


© HONESTY ©

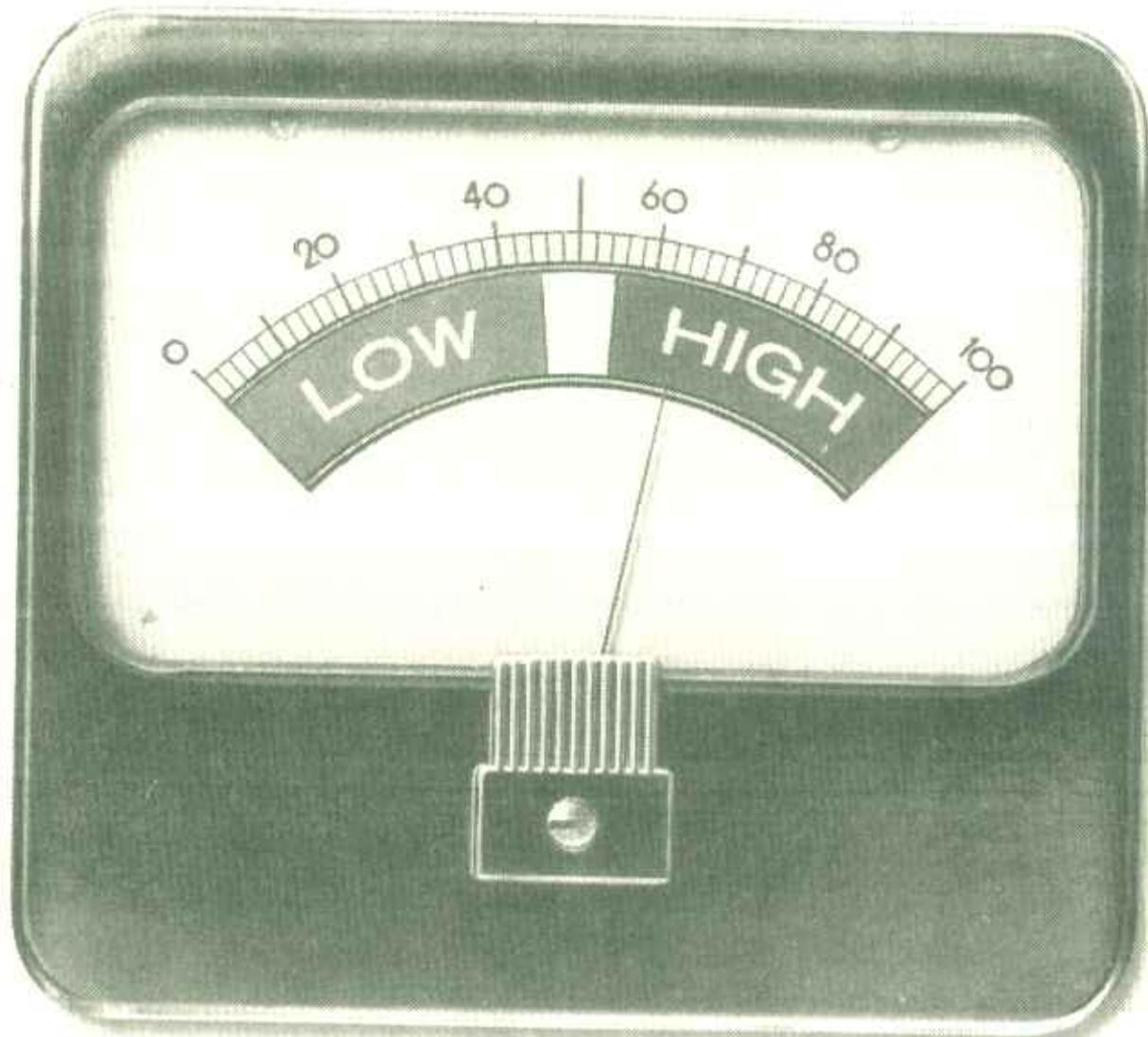

• RISK •


Watts and Miles

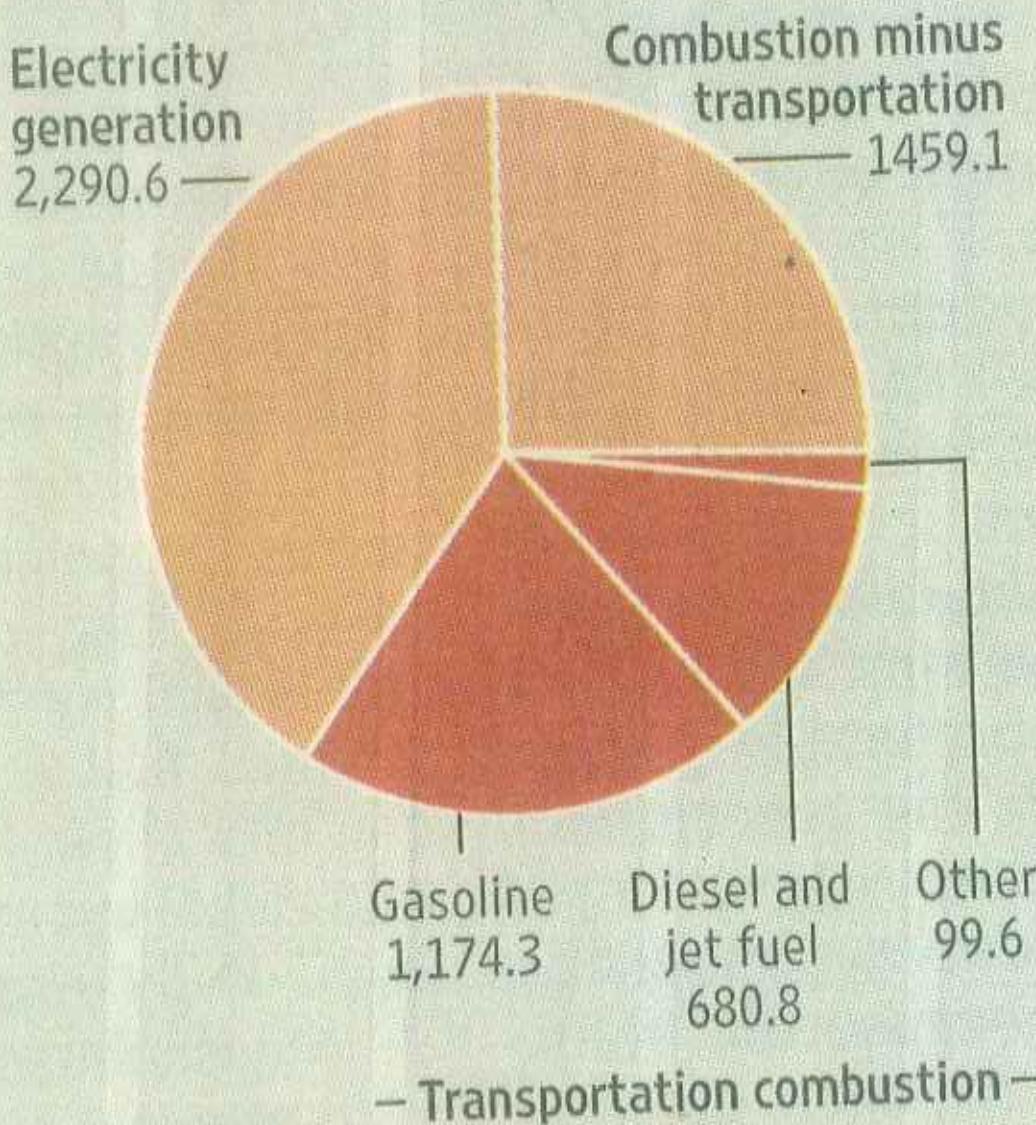U.S. carbon-dioxide emissions from fossil-fuel combustion by end-use sector, in teragrams of carbon dioxide





Note: Doesn't include U.S. territories


Source: Environmental Protection Agency

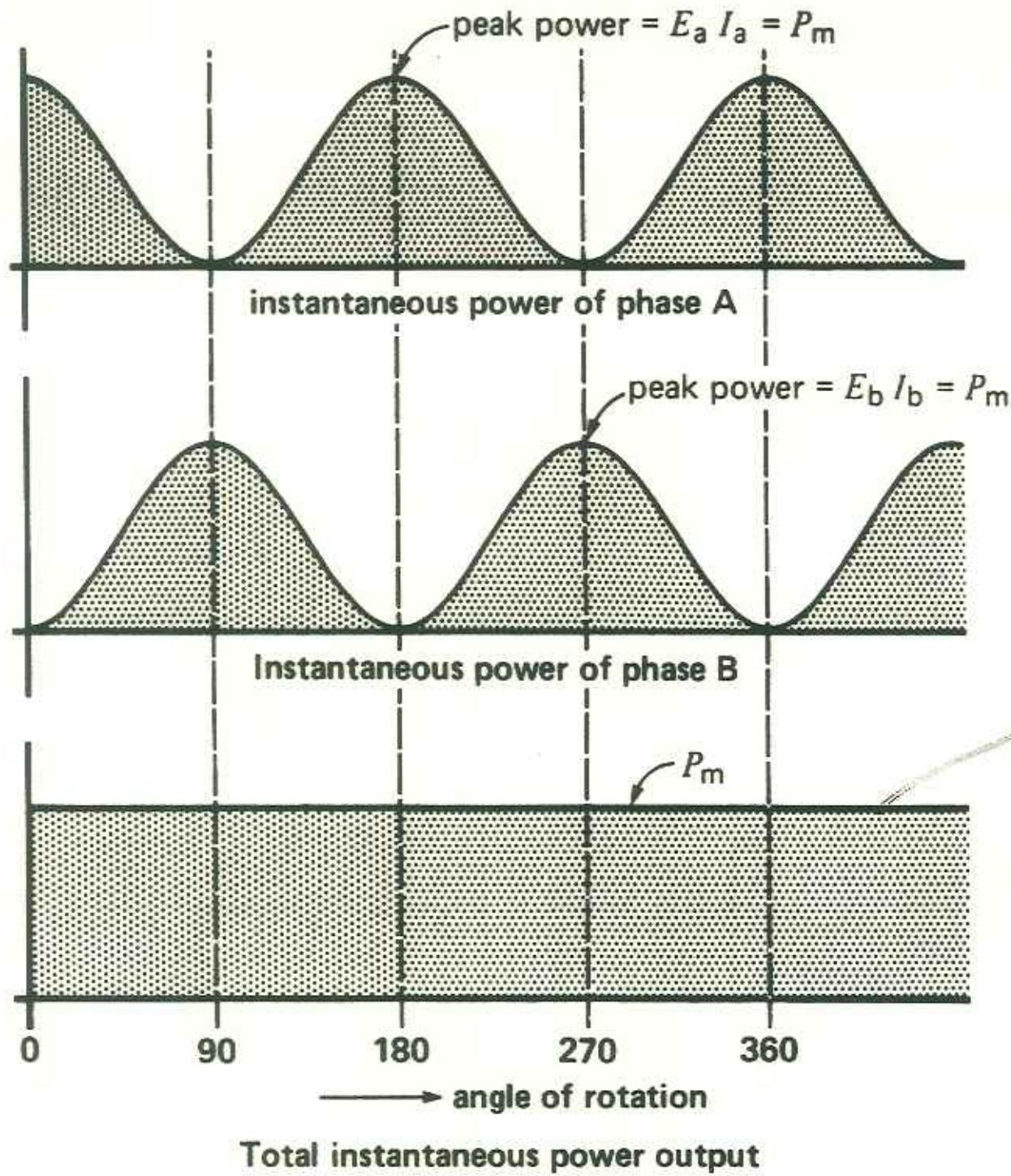

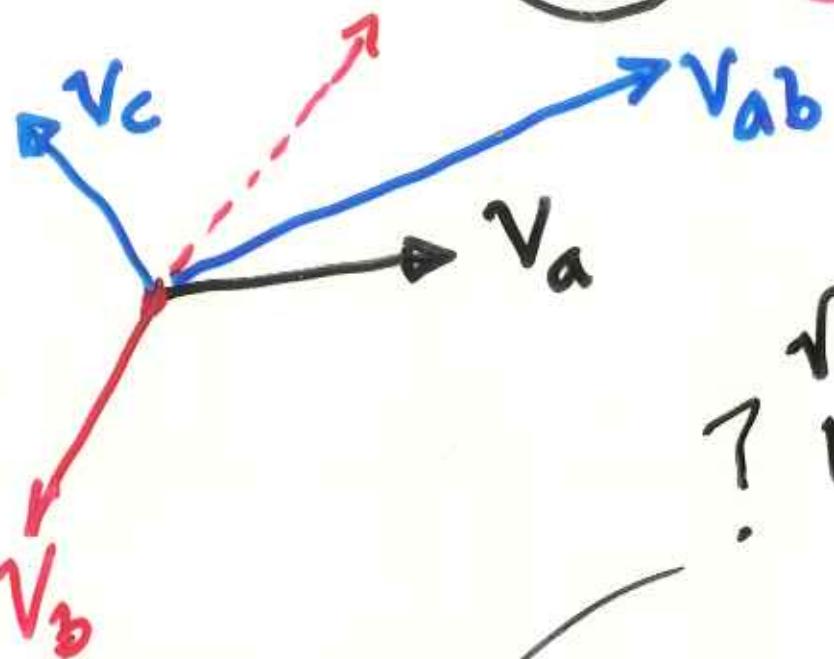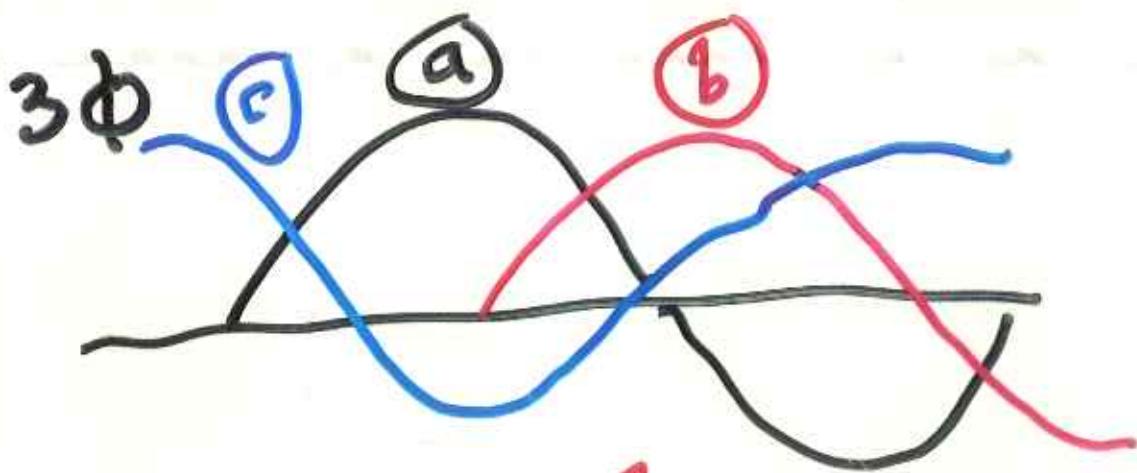$2 \quad 1\phi$
 90° apart
 easy to
 prove
 why
 $P \neq f(t)$



$\sqrt{3} \times$
? leading 30°

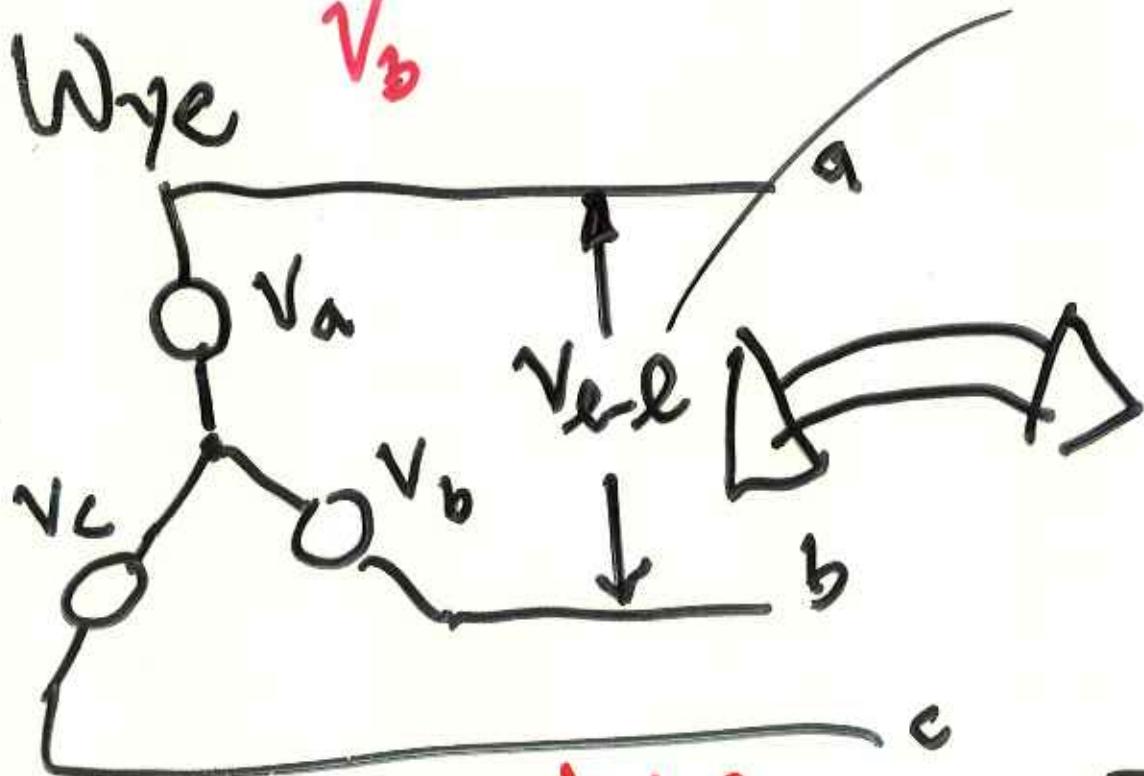

per
phase
circuit
for
balanced


$$|V_{el}| = \sqrt{3} N_\phi$$

V_{ab} vs V_a

who LAGS



15

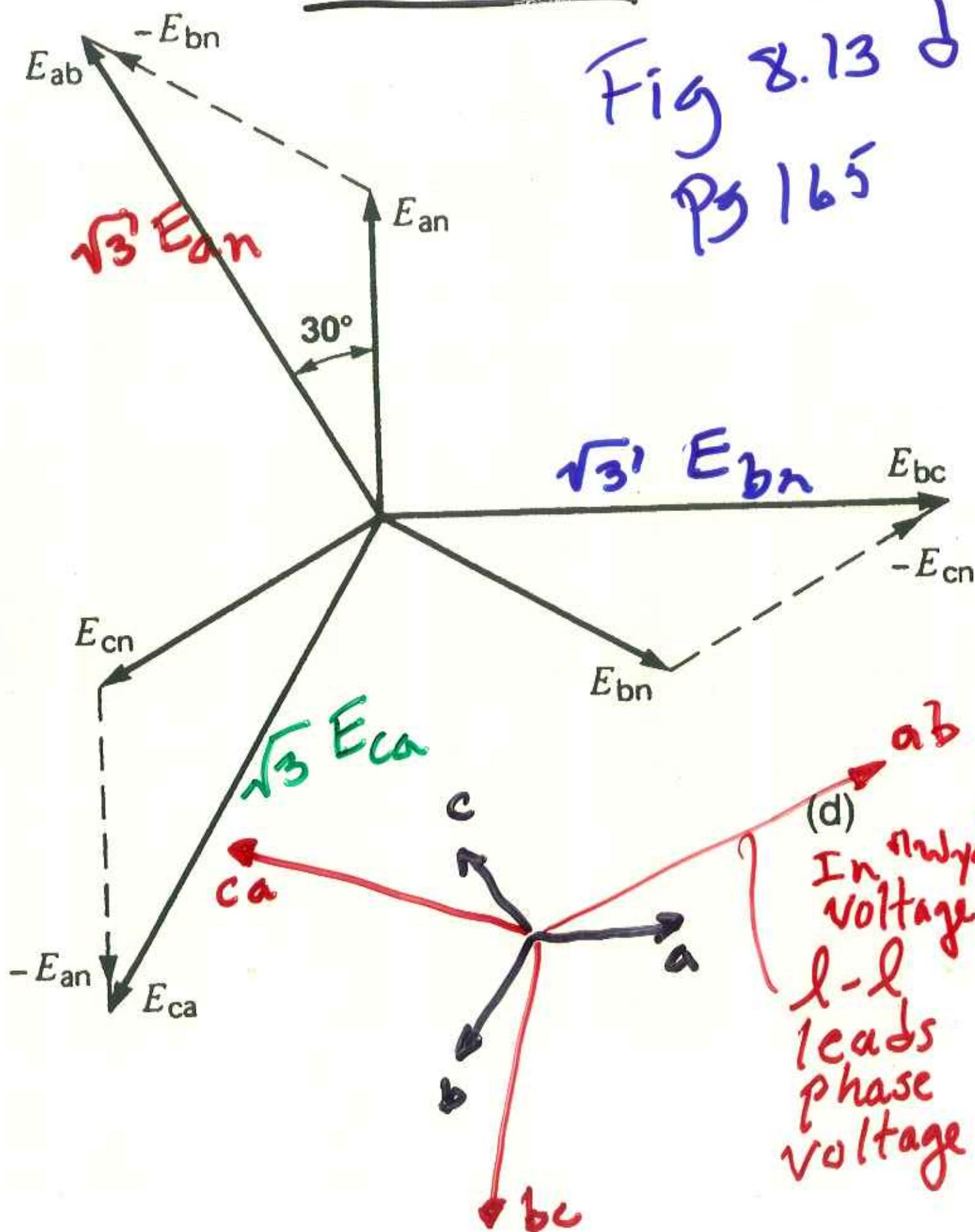
Summary $\sqrt{3}$ & 30° Fig 8.13 d
Pg 165

16

$V_{line} = 100 \text{ V}$ on each coil

Due to "Wye" wiring among coils $E_{ll} = \sqrt{3} E_{coil}$

Fig 8.14
p 166

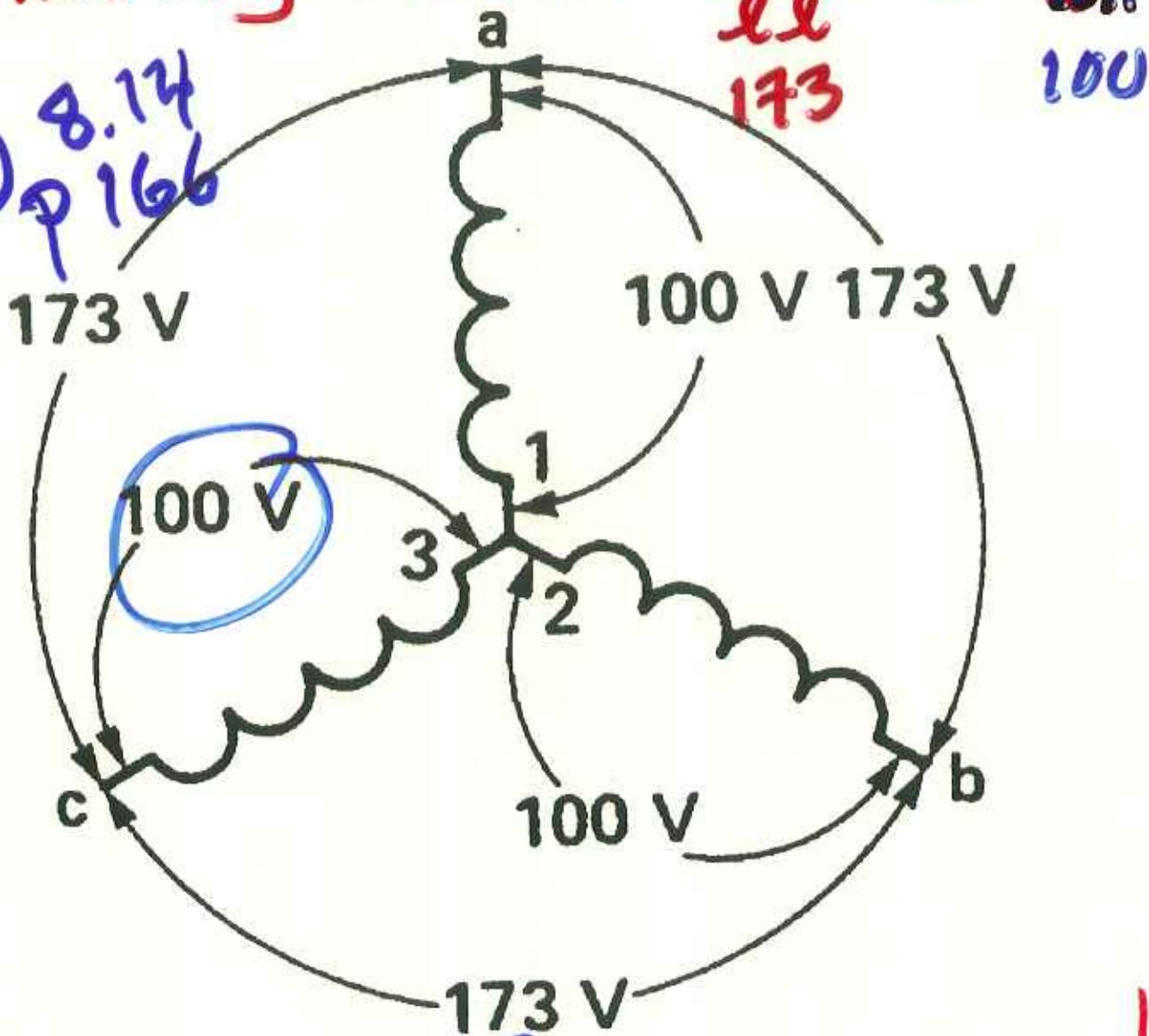

If $E_{coil} = E_{ll}/\sqrt{3}$
Common Distribution Voltages!

— $\uparrow 23.9 \text{ kV}$ $\Rightarrow l-n$
— \uparrow line-line

$$V_{peak} (l-l) = \sqrt{2} 23.9 = 33.9 \text{ kV}$$

Design for peak

$$Z = \sqrt{X^2 + R^2} = \sqrt{4^2 + 3^2} = 5$$


Wye phase voltage:

$$V_b = \frac{440}{\sqrt{3}} = 254 \text{ V}$$

Given the circuit below:

$$I_{\text{line}} = \cdot \quad I = ?$$

Fig
8.18

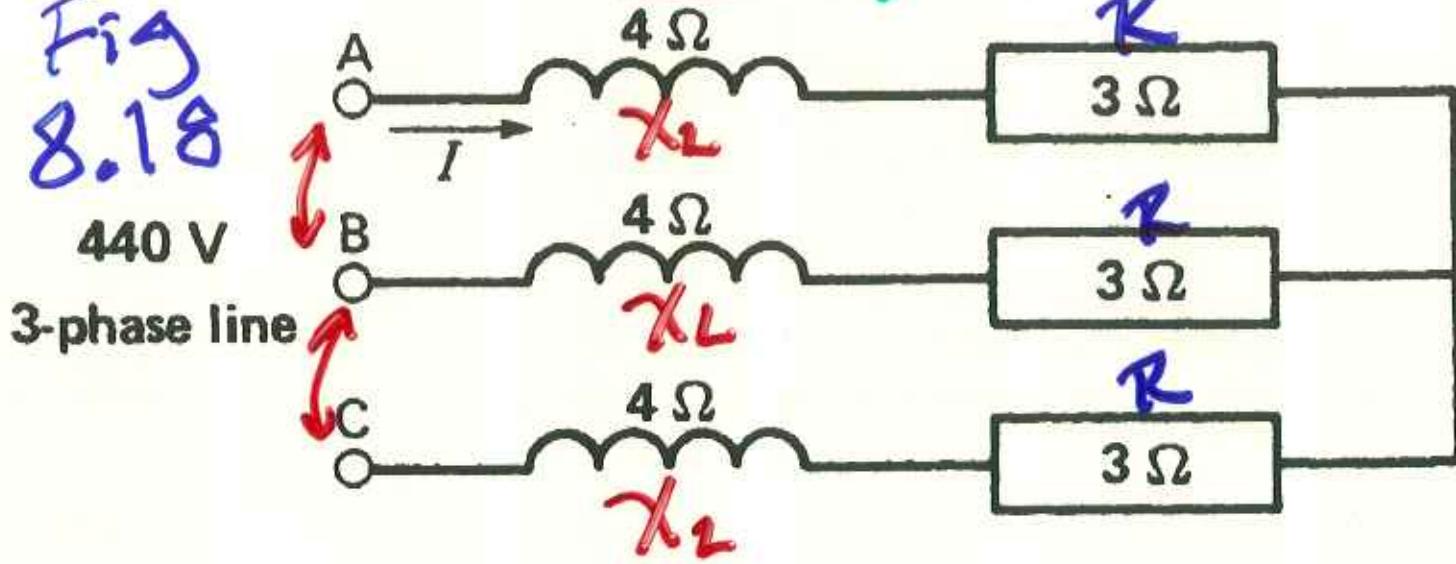

$$\begin{aligned} I &= \\ \frac{254}{151} & \\ \downarrow & \end{aligned}$$

$$\begin{aligned} I &= \\ \frac{508}{508} & \end{aligned}$$

2.4 KV
LL
2400
2400

$S = 600 \text{ kVA}$
 $\text{PF} = .8 \text{ lag}$

$$V_\phi = \frac{V_{ll}}{\sqrt{3}}$$

$$I_{line} = I_{phase}$$

$Y(Z) \rightarrow \text{model}$

8-24

a. $I = \frac{600000}{2400 \times \sqrt{3}} = 144 \text{ A}$

$$Z = \frac{2400}{\sqrt{3} \times 144} = 9.6 \Omega$$

Find $10A^2 \cdot X \cdot R$


b. $P = 600 \times 0.8 = 480 \text{ kW} = 160 \text{ kW per phase}$

$Q = 600 \times 0.6 = 360 \text{ kvar} = 120 \text{ kvar per phase}$

$$I^2 X = 120000 \quad \therefore X = \frac{120000}{144^2} = 5.79 \Omega$$

$$I^2 R = 160000 \quad R = 160000 / 144^2 = 7.72 \Omega$$

$$V_\phi = \frac{2400}{\sqrt{3}}$$

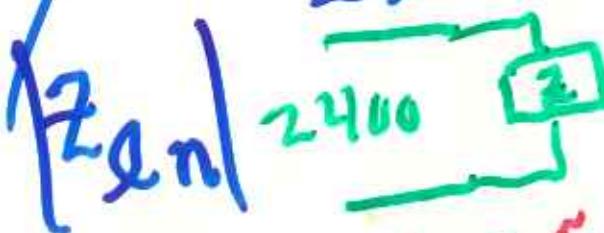


$L^2 \text{ line value } \frac{1}{4}$

Q

3Φ Wiring

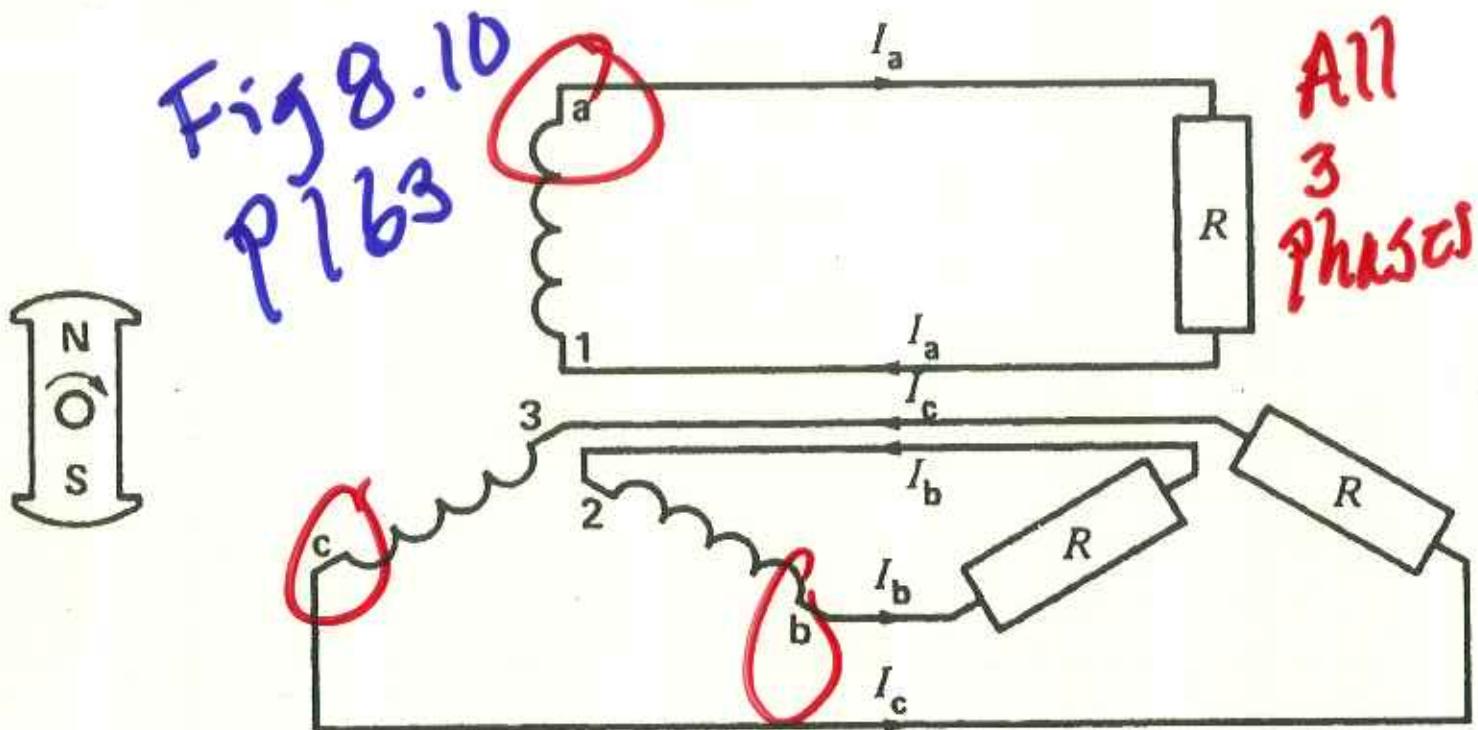If it first appears to have
a 3 resistor load we
need 3 wires




Wires cost A. Can we do a better wiring job???? Use less wire?

$$i_L \quad i_a \quad i_b \quad \sum i = ?$$

10


3W
kills

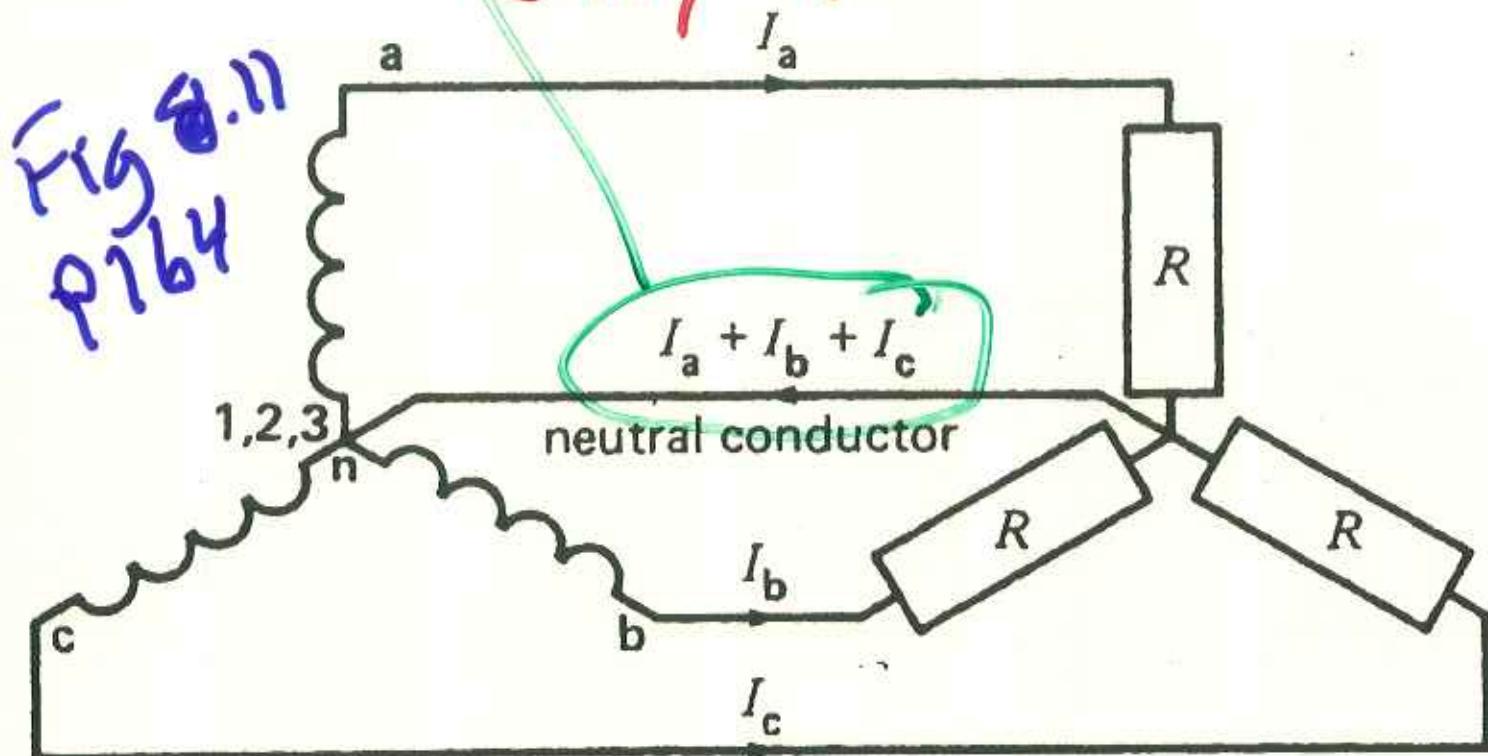Could we even use a smaller area wire to save more \$ B_0
 After all $\sum i = 0$
 Only 4 wires not 6



What about

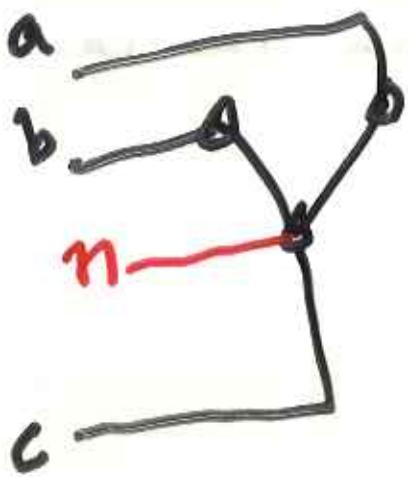
- unbalanced 3 φ i
 - Harmonic Currents
- $i_{3W}(\text{neutral}) = ?$



$$I_n = ?$$

mains 3 ϕ balanced

\Rightarrow What

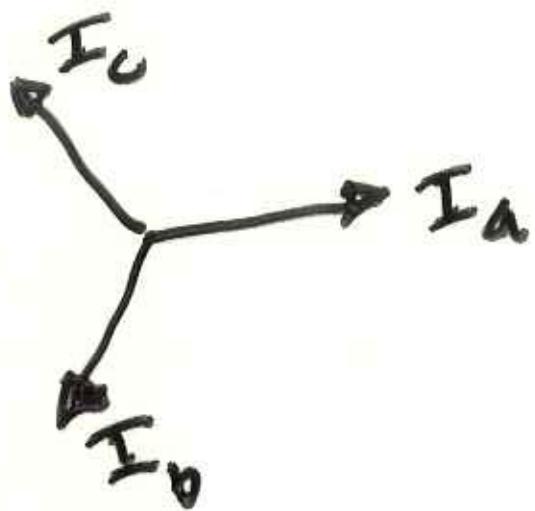


What about harmonics at

$$3\omega \quad I_n(3\omega) = ?$$

$\Sigma i @ \text{node}$ convention
i into node is (+)

@ node a $I_a + I_3 - I_1 = 0$


$$I_a \equiv I_1 - I_3$$

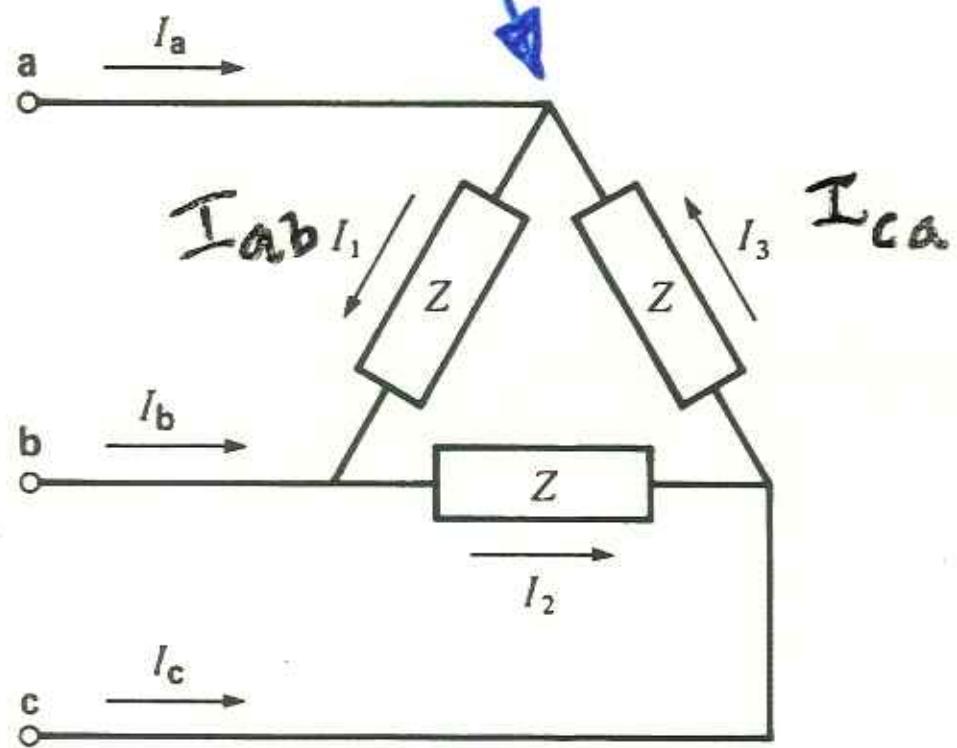

I_1, I_3 are phase current
 I_a is line current

I_a leads I_1

by 30° again!

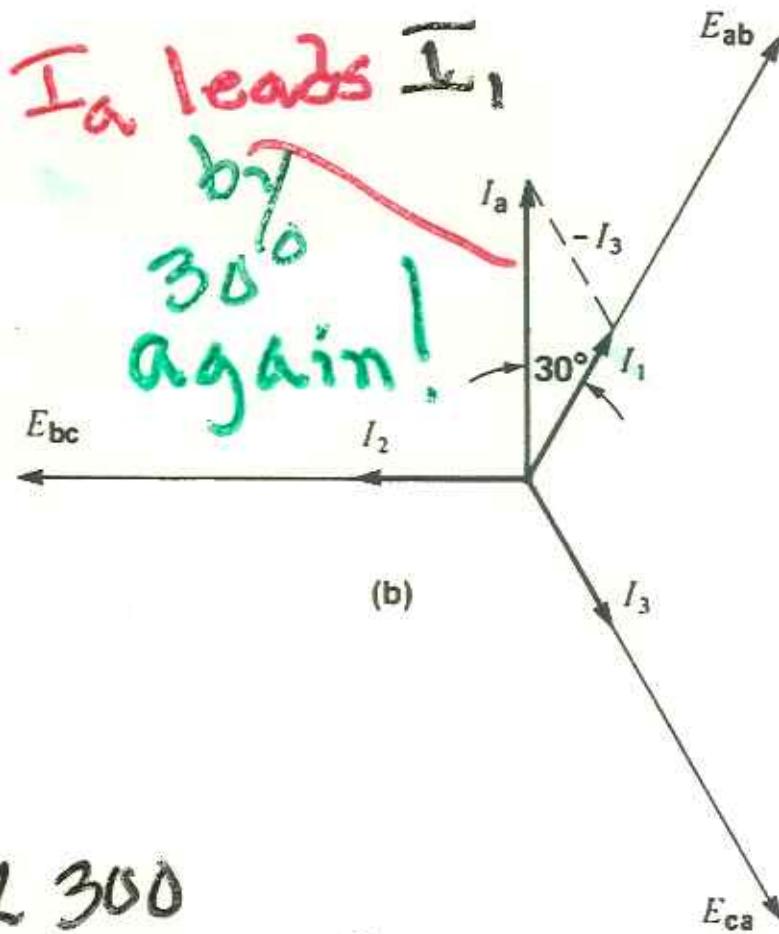

(a) If $I_1 \angle 60^\circ$

Then $I_2 \angle 180^\circ$, $I_3 \angle 300^\circ$

[line current] $= \sqrt{3} |I_\phi|$ Again!

18

$$|I_a| = I_1 - I_3 = \sqrt{3}|I_\phi| \\ = 2|I_\phi|\cos 30^\circ$$

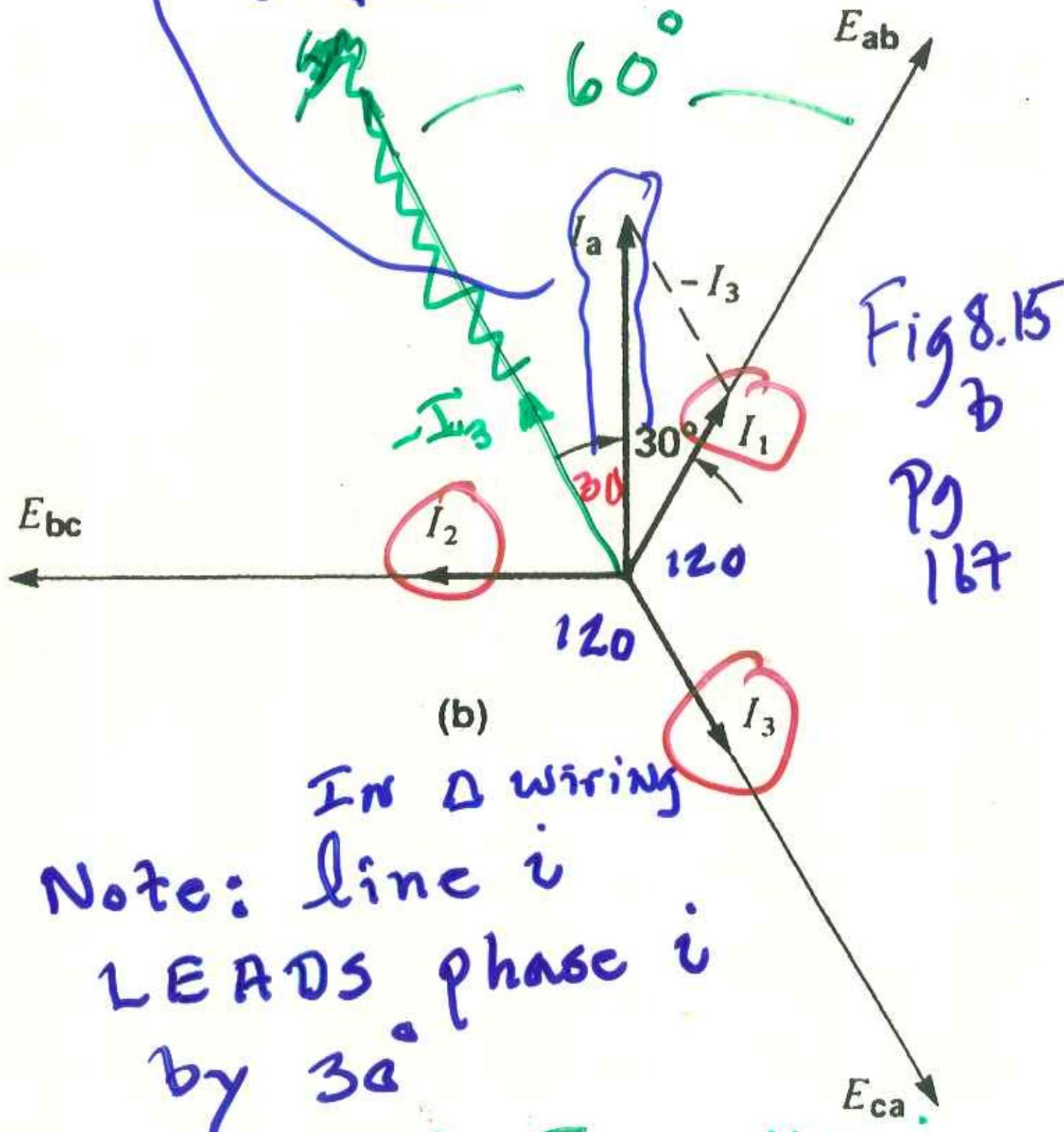


Fig 8.15

Pg
167


(b)

In Δ wiring

Note: line i

LEADS phase i

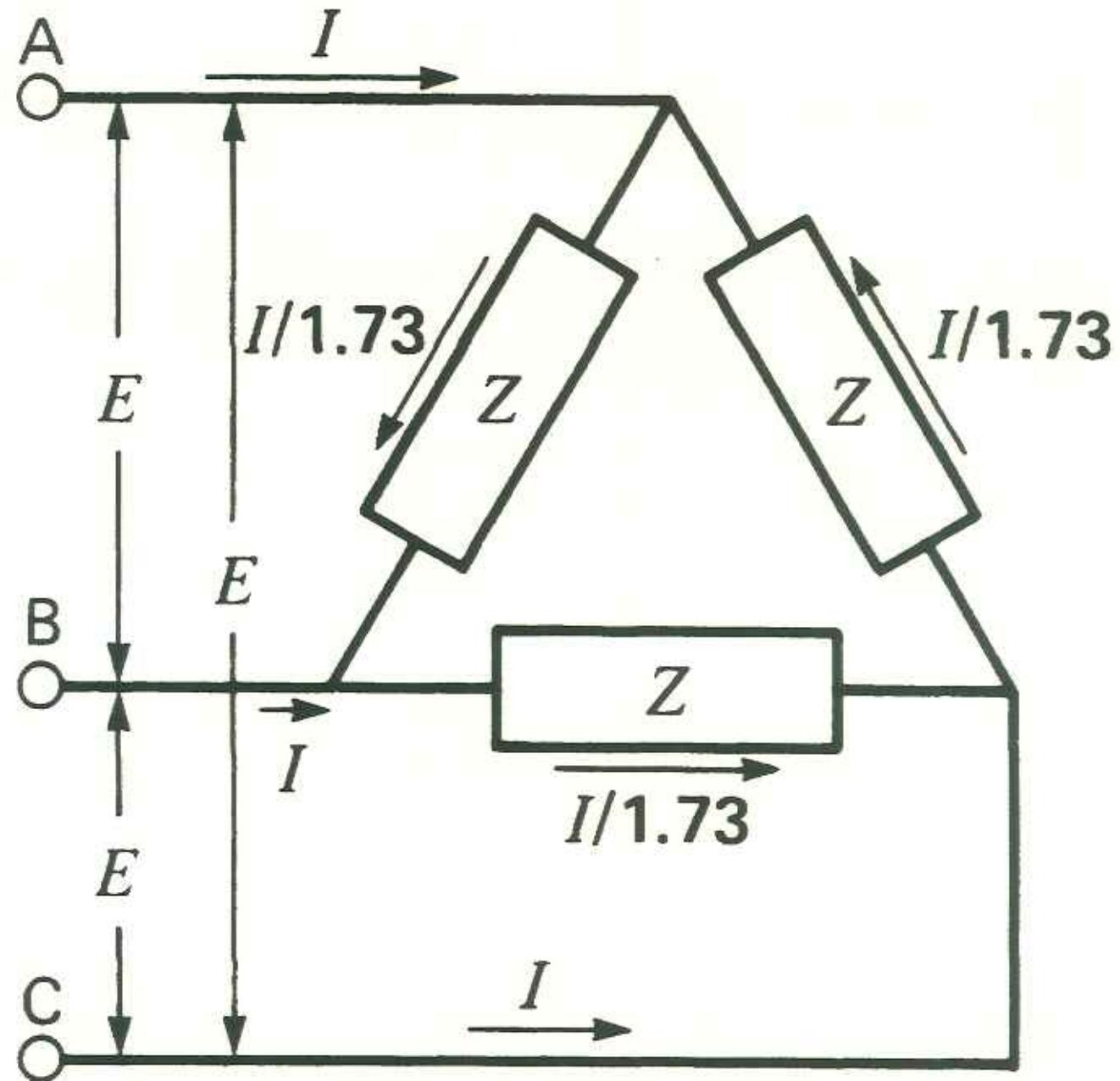by 30° I_a leads I_1 line i
leads
phase i



Σi convention : in is positive





$$I_a + I_{ca} - I_{ab} = 0$$

Impedances connected in delta

$$I_a \equiv I_{ad} - I_{ca}$$

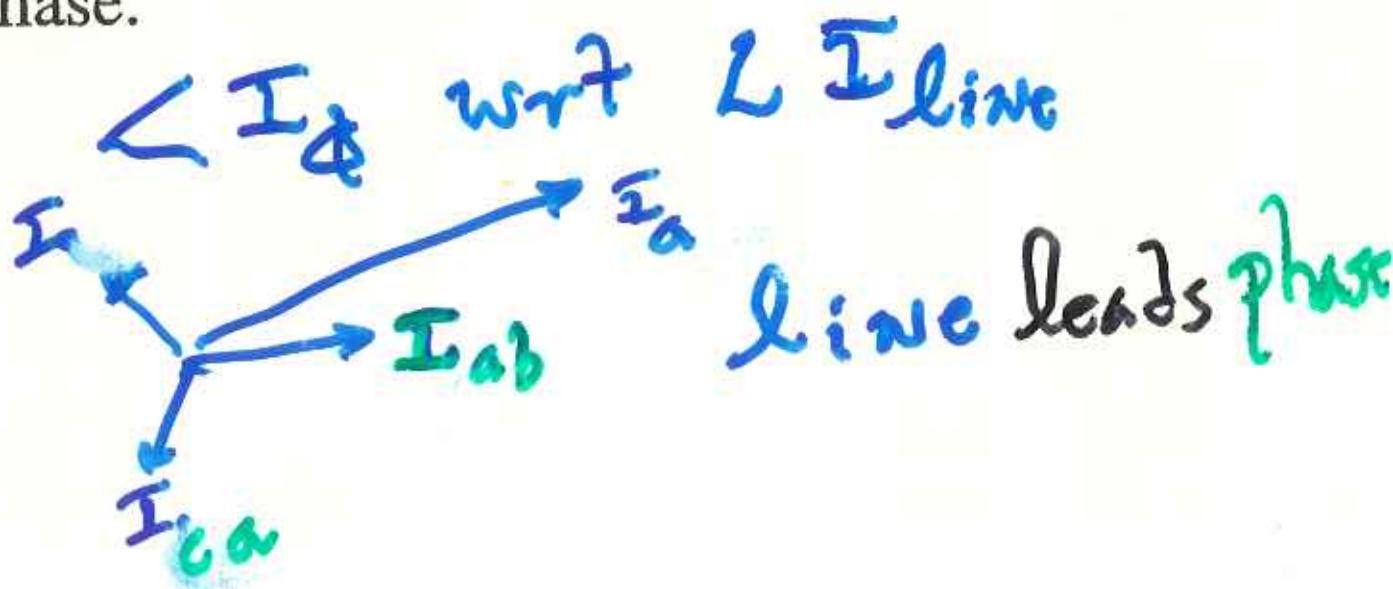- The current in each element is equal to the line current I divided by $\sqrt{3}$.
- The voltage across each element is equal to the line voltage E .
- The voltages across the elements are 120° out of phase.
- The currents in the elements are 120° out of phase.



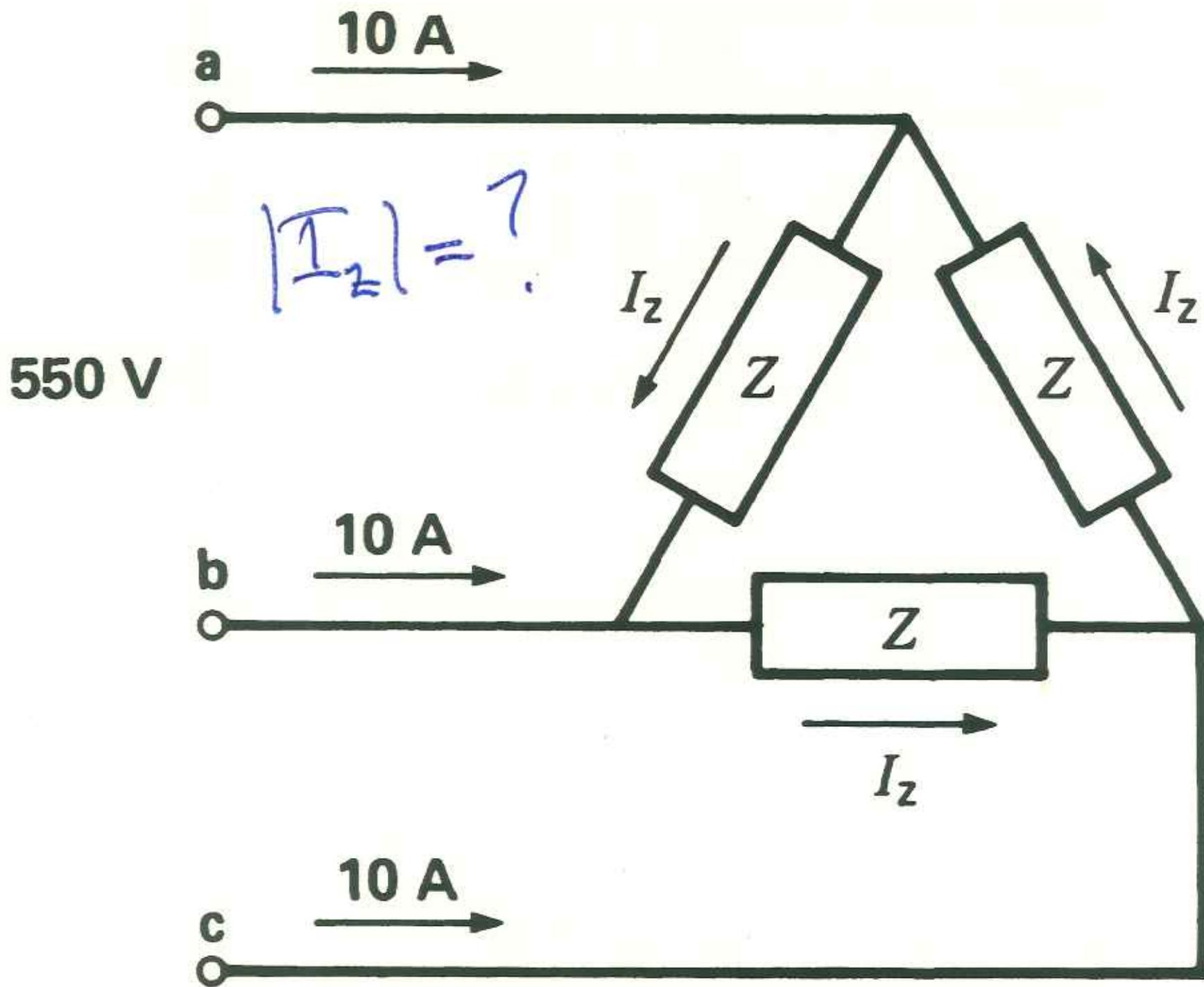


19

Given: V_{line} and I_R for DOL
 $Z = ?$

Fig 8.15C
 Pg 168

$$Z = \frac{V_{line}}{I_R}$$

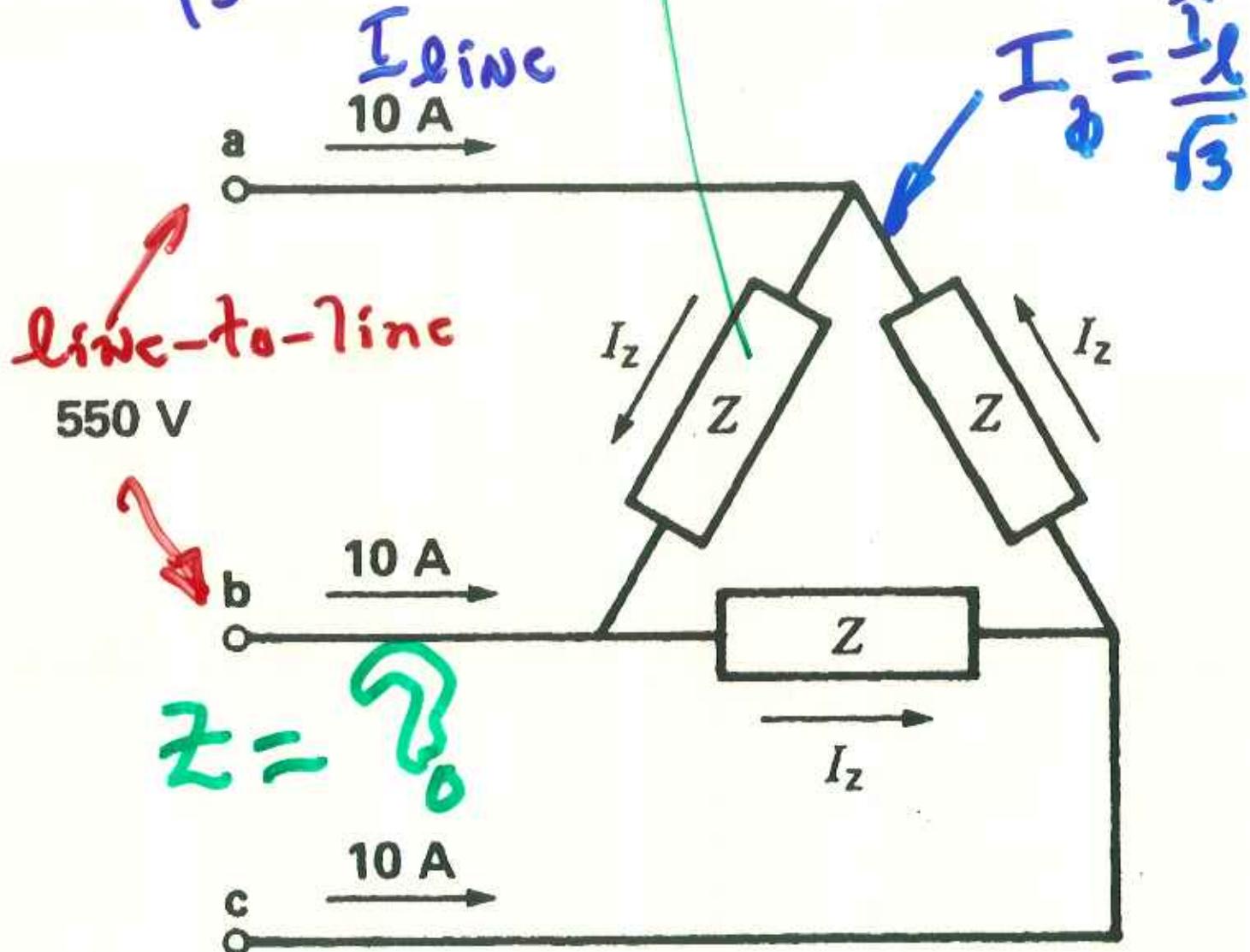

$$Z = \frac{550 \text{ (rms)}}{\frac{10}{\sqrt{3}}} = 95 \Omega$$


$I_R \neq I_{line}$

18

\triangle Connected in Caps
 Value of C for measured Given I line
 I_C (each C) = $\frac{22}{\sqrt{3}} = 12.7$ $\boxed{I_D}$

$$X_C = \frac{550}{12.7} = 43.3 \Omega \quad @ f_{\text{mains}}$$

Fig 8.19
Q 17)

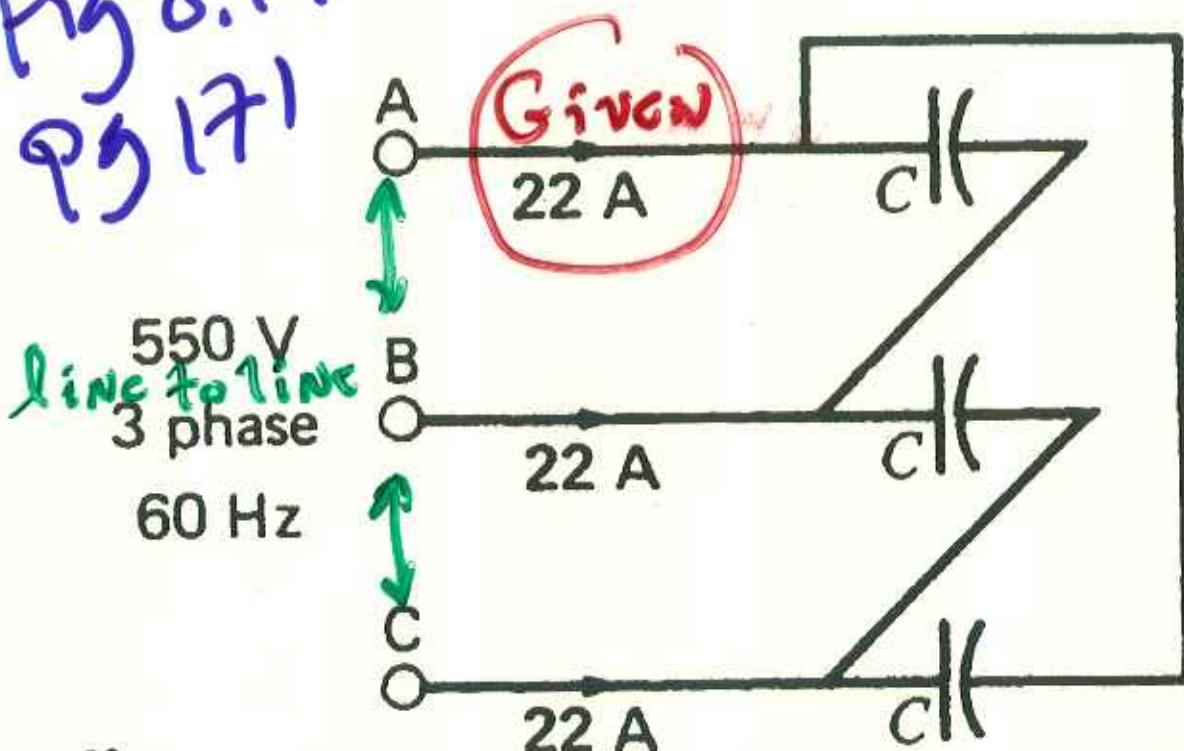



"C" value for $f = 60 \text{ Hz}$ mains

$$C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi(60)(43.3)} \\ = 61.3 \mu F$$

f change from 60 $\rightarrow 50 \text{ Hz}$


$X_C \uparrow$ or \downarrow

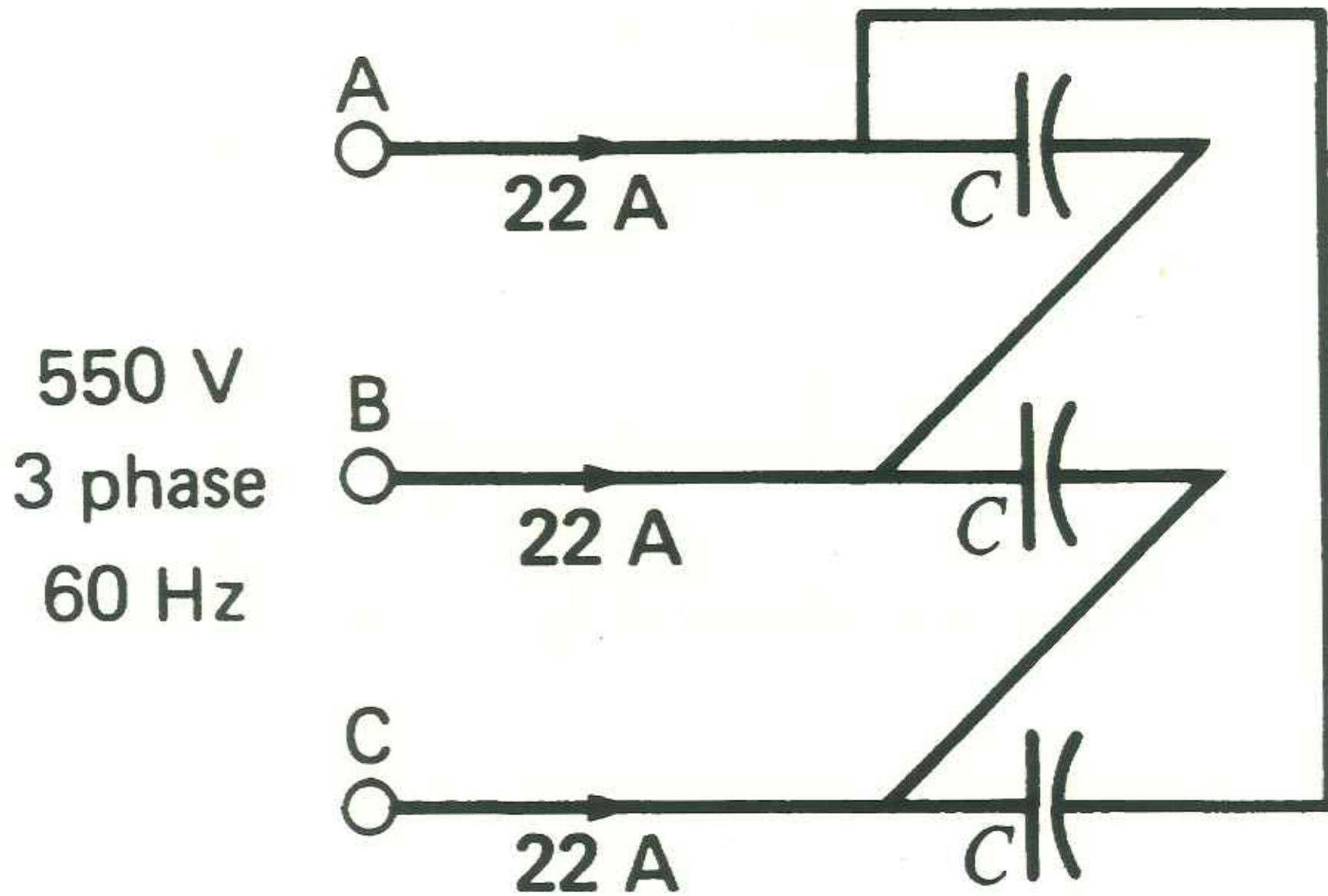

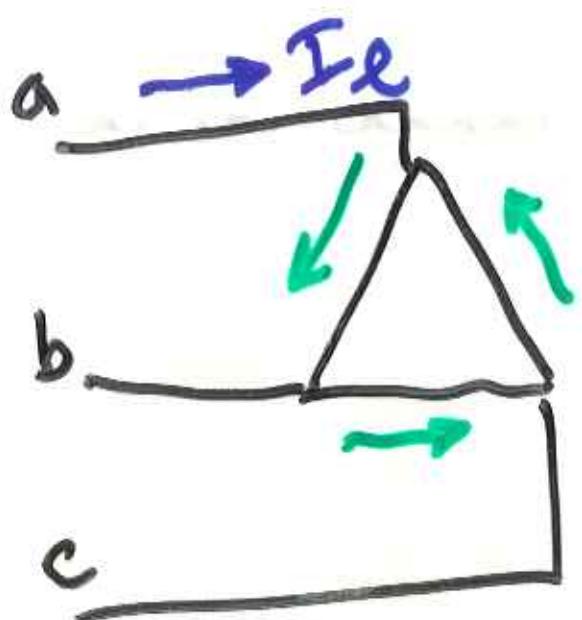

I_Φ has harmonics
say @ 3ω

$$I_a(3\omega) = ?$$

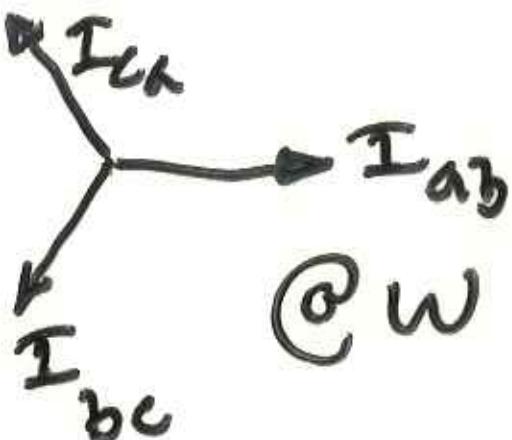


Δ acts as a harmonic




P Δ S Δ



Trf H Coils Primary wired as ?

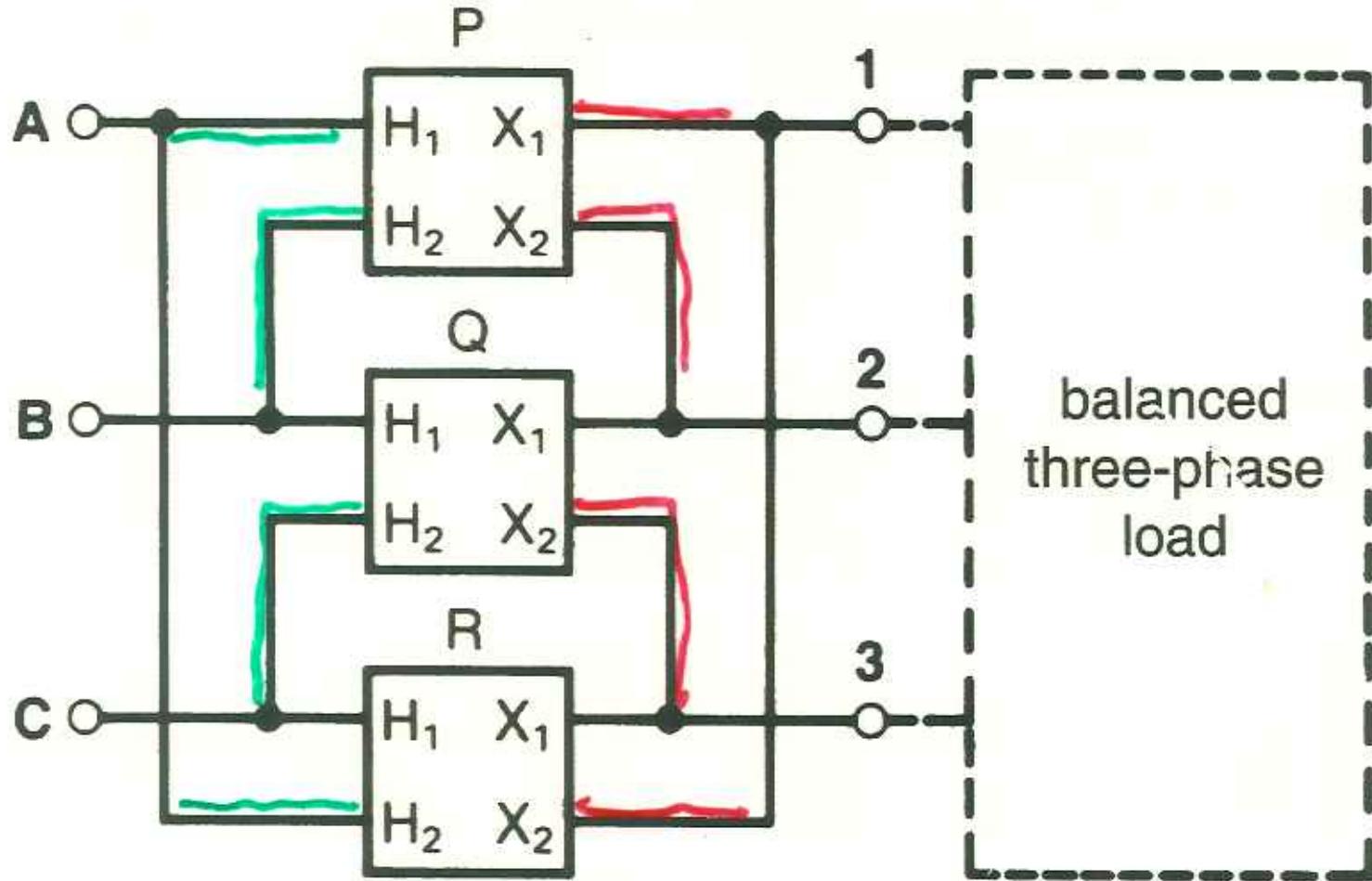


Trf X Coils Secondary wired as ?

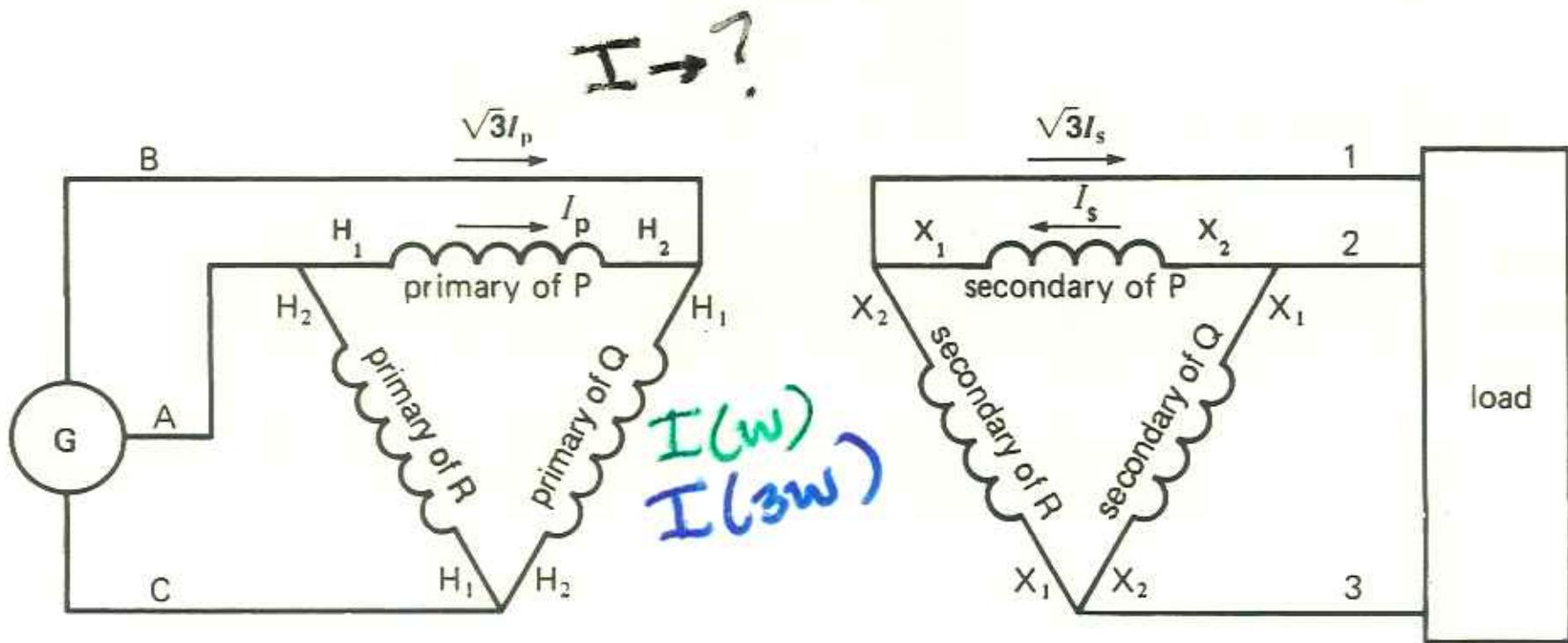

Layout wiring "like phasors"

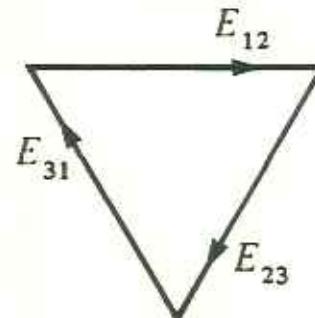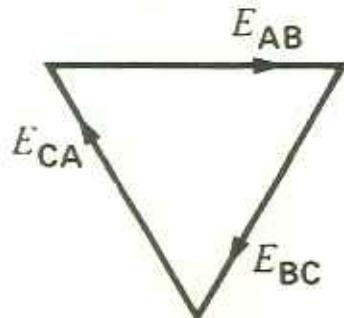


P Δ S Δ Y
Primary wired as ?

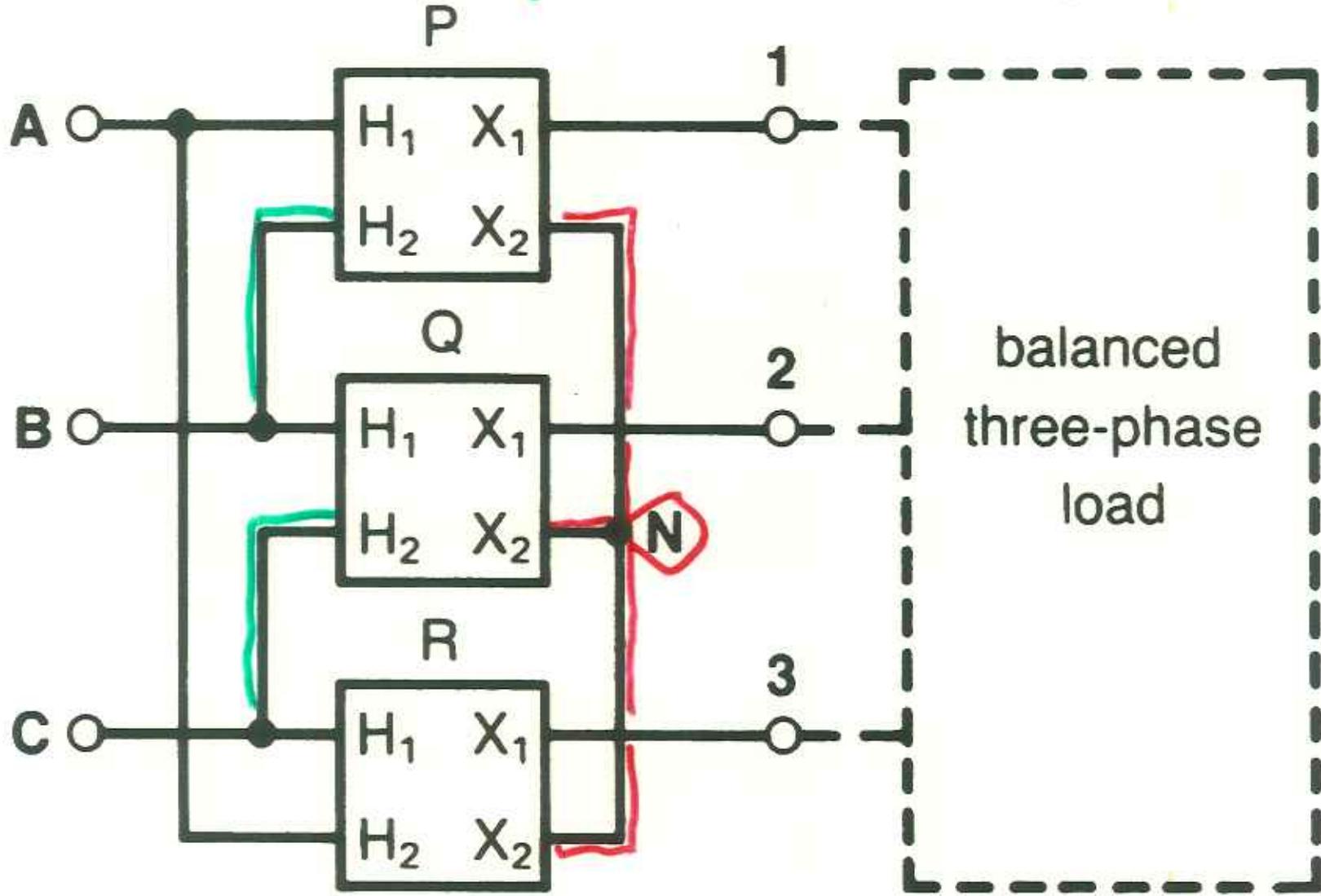


Secondary wired as ?

Primary


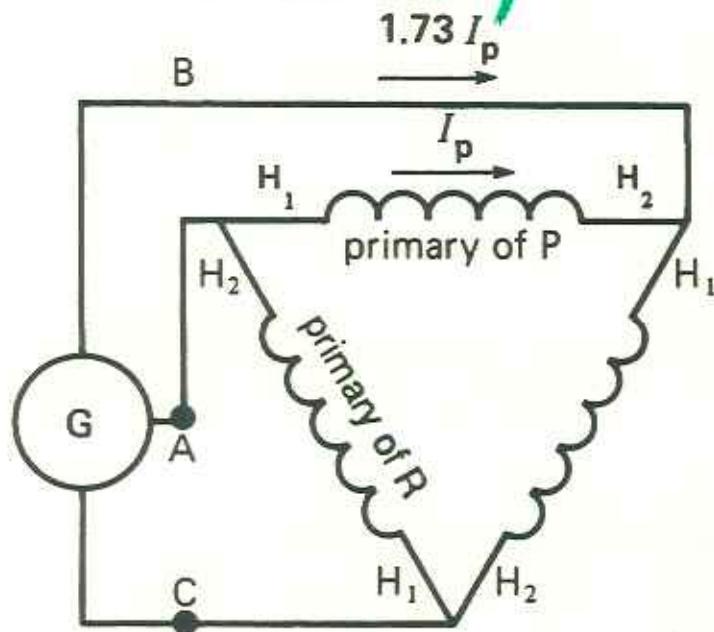


Secondary

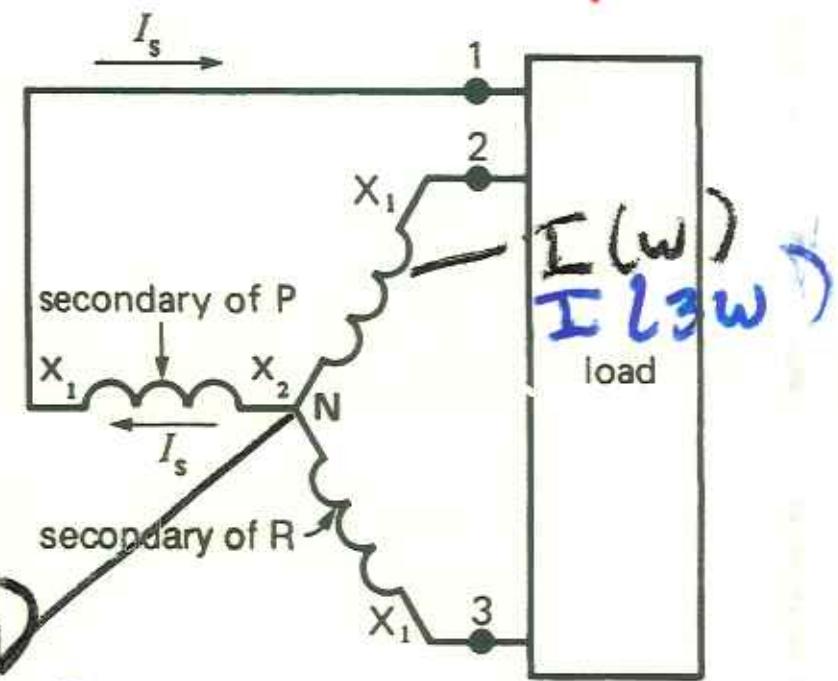



$$I_L(\omega)$$

$$I(3\omega)$$

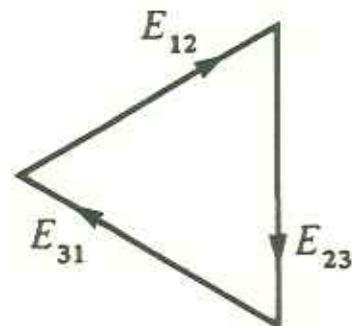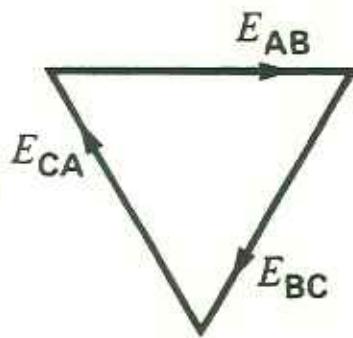

Δ - Y Conversion

$$Z_Y = \frac{Z_\Delta}{3}$$

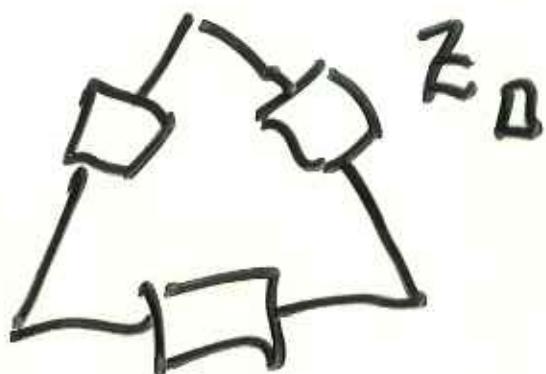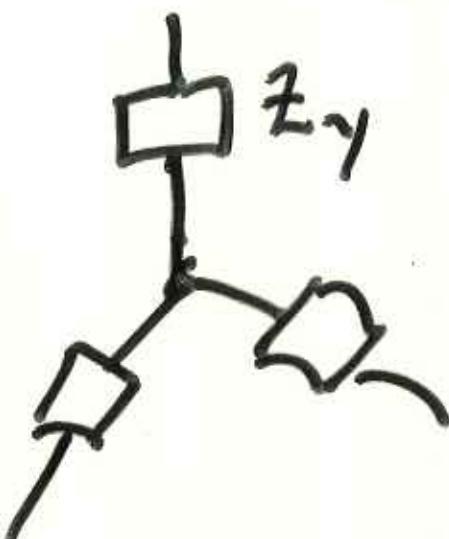



$$P_{3\phi} = 3 P_{1\phi} \quad Q_{3\phi} = 3 Q_{1\phi}$$

$$P(t) = \overline{P} = \omega \bar{T} \xrightarrow{\text{Constant Torque}} \text{Constant}$$

Constant
 3ϕ power
 $P \neq f(t)$

$\bar{T} \neq f(t)$

Each phase pulsates but not $P_{3\phi}$

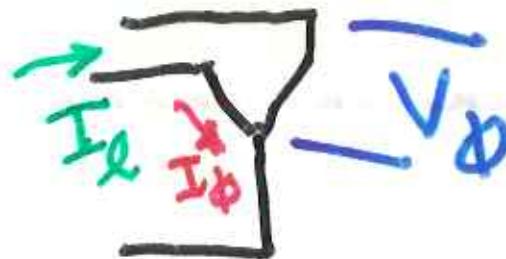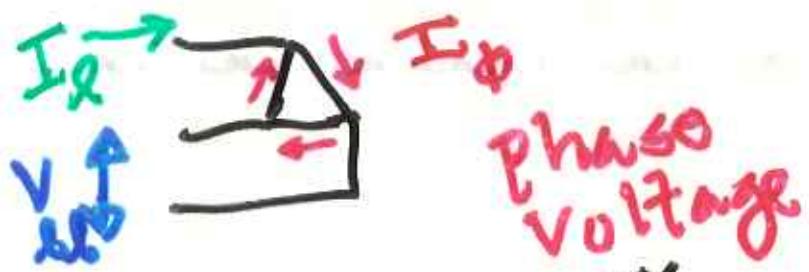

$$V_{ll} = V_\phi \quad \text{vs line voltage} \quad I_\phi = I_l$$

$$P_{3\phi} = 3 P_{1\phi} = \quad P_{3\phi} = 3 P_{1\phi}$$

$$\Rightarrow I = \frac{I_l}{\sqrt{3}} \quad \Rightarrow V_\phi = \frac{V_{ll}}{\sqrt{3}}$$

@ fixed $P_{3\phi}$ Impedance or R_ϕ per phase

$$R_\Delta^\phi = \frac{V_{ll}}{\frac{I_l}{\sqrt{3}}} = \frac{V_{ll}\sqrt{3}}{I_l}$$

$$R_\Delta^\phi = \sqrt{3} \frac{V_{ll}}{I_l} \quad R_y^\phi = \left(\frac{V_{ll}}{I_l} \right) \frac{1}{\sqrt{3}}$$

$$\frac{R_y^\phi}{R_\Delta^\phi} = \frac{1}{3}$$


$$R_\Delta^\phi = 3 R_y^\phi$$

For same power

$$24\Omega (\Delta) = ? \Omega (Y)$$

Via memory

8-14

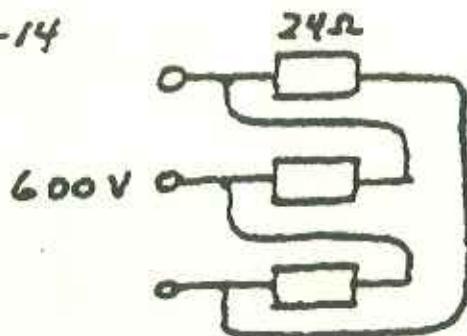


$$I_R = 600/24 = 25A$$

$$\begin{aligned} \text{Power dissipated per resistor} \\ = 600V \times 25A = 15kW \end{aligned}$$



If resistors are connected in Y,
they must each also dissipate 15 kW. The voltage
across each resistor = $600/\sqrt{3} = 346.4V$.
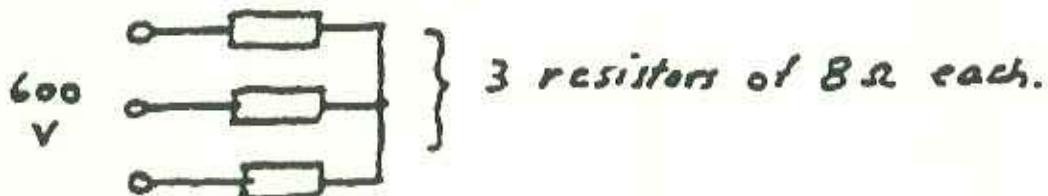
$$\therefore 15000 = \frac{346.4^2}{R} \quad \therefore R = 8\Omega \text{ (see below)}$$



Both loads \rightarrow Desire $S = 100 \text{ kVA}$
 $R_\Delta \text{ vs } R_Y = ?$

21

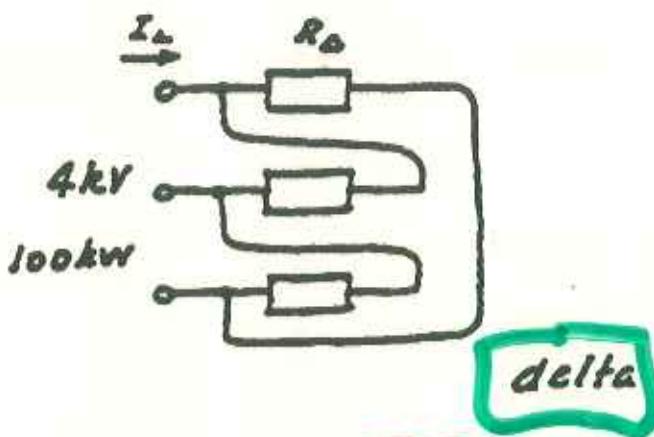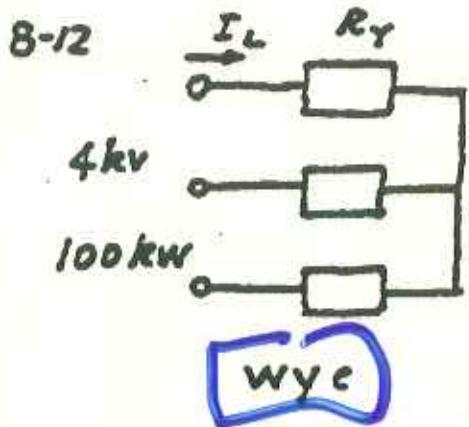


In both cases $I_L = \frac{100 \text{ kVA}}{4000 \sqrt{3}} = 14.43 \text{ A}$

a. $R_Y = \frac{4000}{\sqrt{3} \times 14.43} = 160 \Omega$

b. $R_\Delta = \frac{4000}{(14.43 / \sqrt{3})} = 480 \Omega$

$$\frac{V^2}{R} \quad R_\Delta = 3 R_Y \text{ for same power why?}$$


At a remote substation

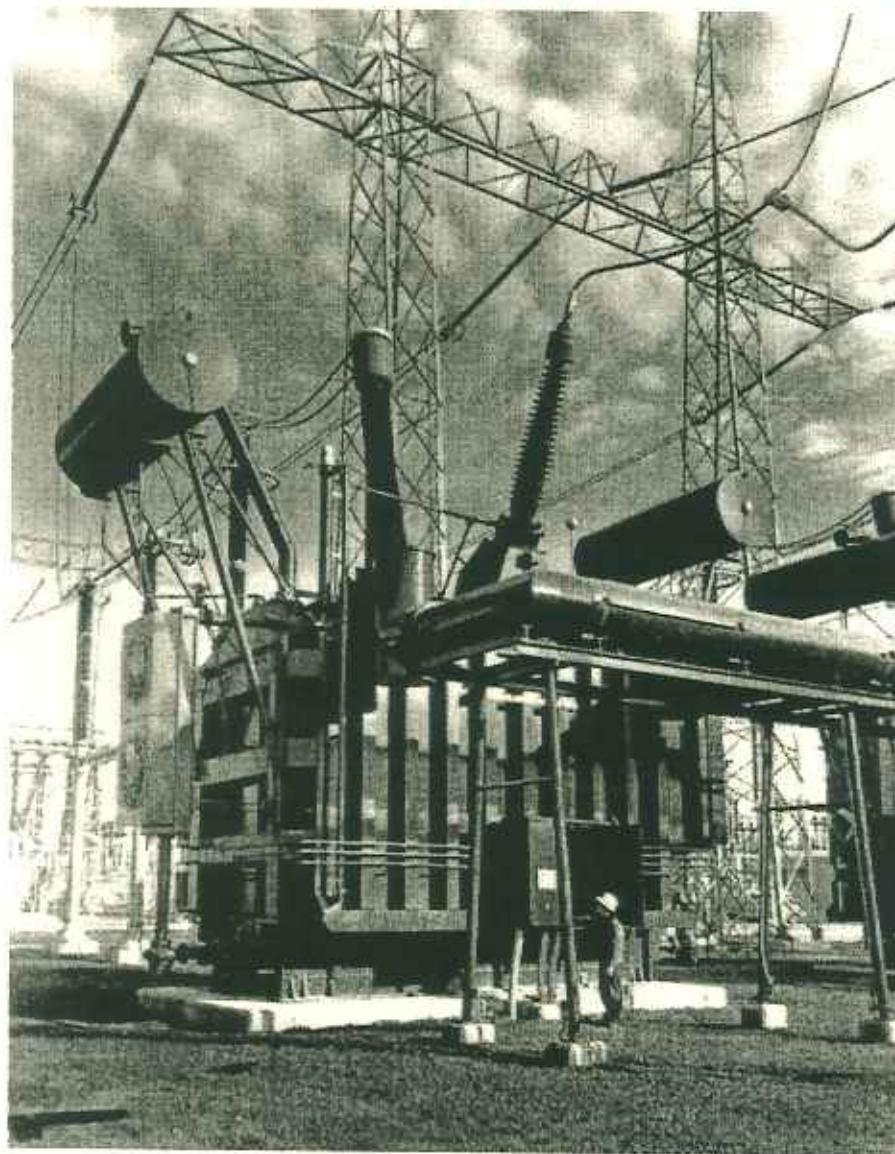

Dot Y
to HV
and
reasons

480Y277V, 3PH, 4C, GN TRANSFORMER

480V, 3PH MOTOR

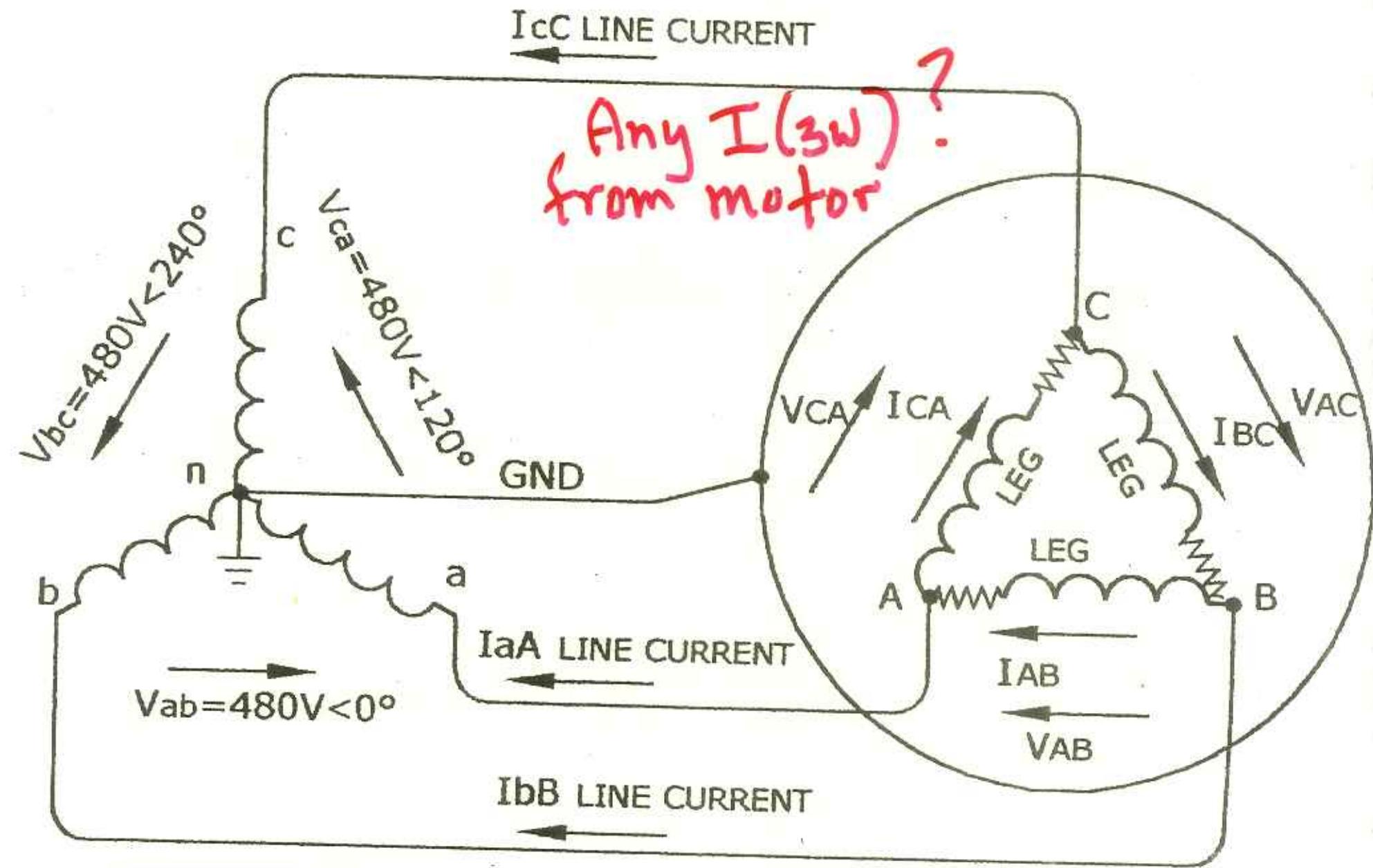

$$450 \text{ kW} \\ 575 \text{ V}_{\text{LL}} (3\Delta) \quad \Rightarrow 1300 \text{ lb steam/hr}$$


What if $V_{\text{LL}} \uparrow$ to 612 V?

~~E-33~~ The quantity of steam is proportional to the thermal power, which in turn varies as the square of the voltage. Thus
 steam produced = $1300 \times \left(\frac{612}{575}\right)^2 = 1359.16 \text{ lb}$

E-34 (a) $P = \frac{P_e}{\eta_{\text{N}}} = \frac{40 \times 746}{0.936} = 31.88 \text{ kW}$

(b) $S = \frac{P}{\cos \phi} = \frac{31.88}{0.83} = 38.41 \text{ kVA}$ Convert $P \rightarrow S$

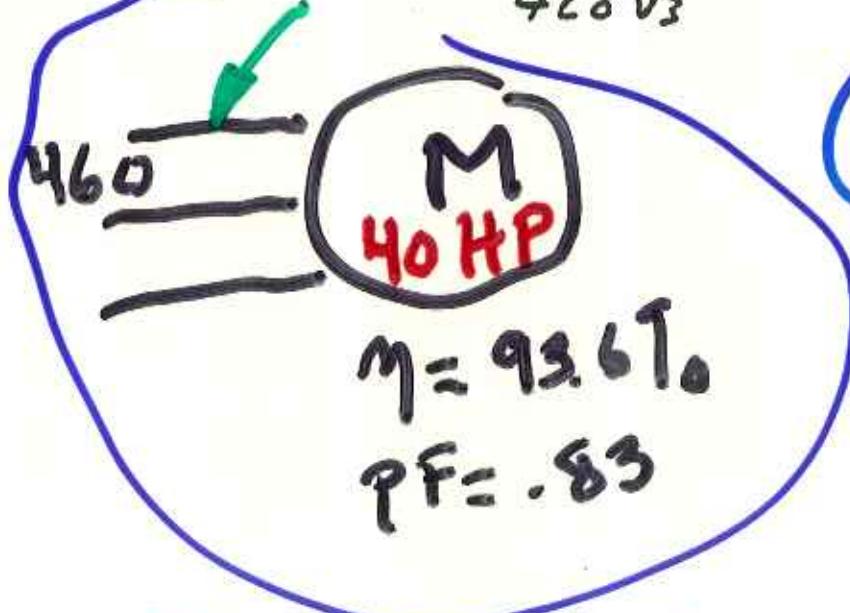
(c) $I = \frac{38.41 \times 1000}{460 \sqrt{3}} = 48.2 \text{ A}$



Choose motor wiring to be either Δ or ∇
 $\sqrt{3} \times V_{\text{LL}}$

FIND
 P_{Drawn}
 S_{Drawn}
 $I_{\text{line full load}}$

Why Δ wiring best on motor

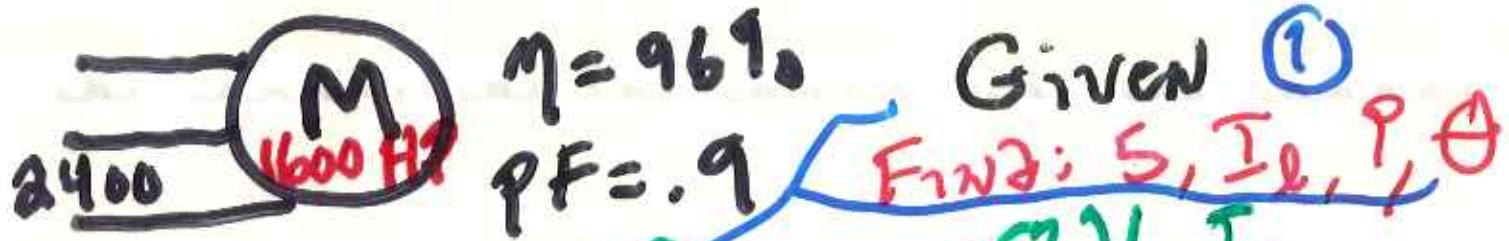

$$S = \frac{P_c}{\rho F} = \sqrt{3} V_{le} I_{le}$$

8-35(a) $S = \frac{1600 \times 746}{0.96 \times 0.90} = 1381 \text{ kVA}$




$$I_L = \frac{1381 \times 1000}{2400 \sqrt{3}} = 332 \text{ A}$$

(b) $P = \frac{1600 \times 746}{0.96} = 1243 \text{ kW}$

$$Q = \sqrt{1381^2 - 1243^2} = 602 \text{ kvar}$$

(c) $\theta = \arccos \frac{1243}{1381} = 25.8^\circ$



$$S \cos \phi = P$$

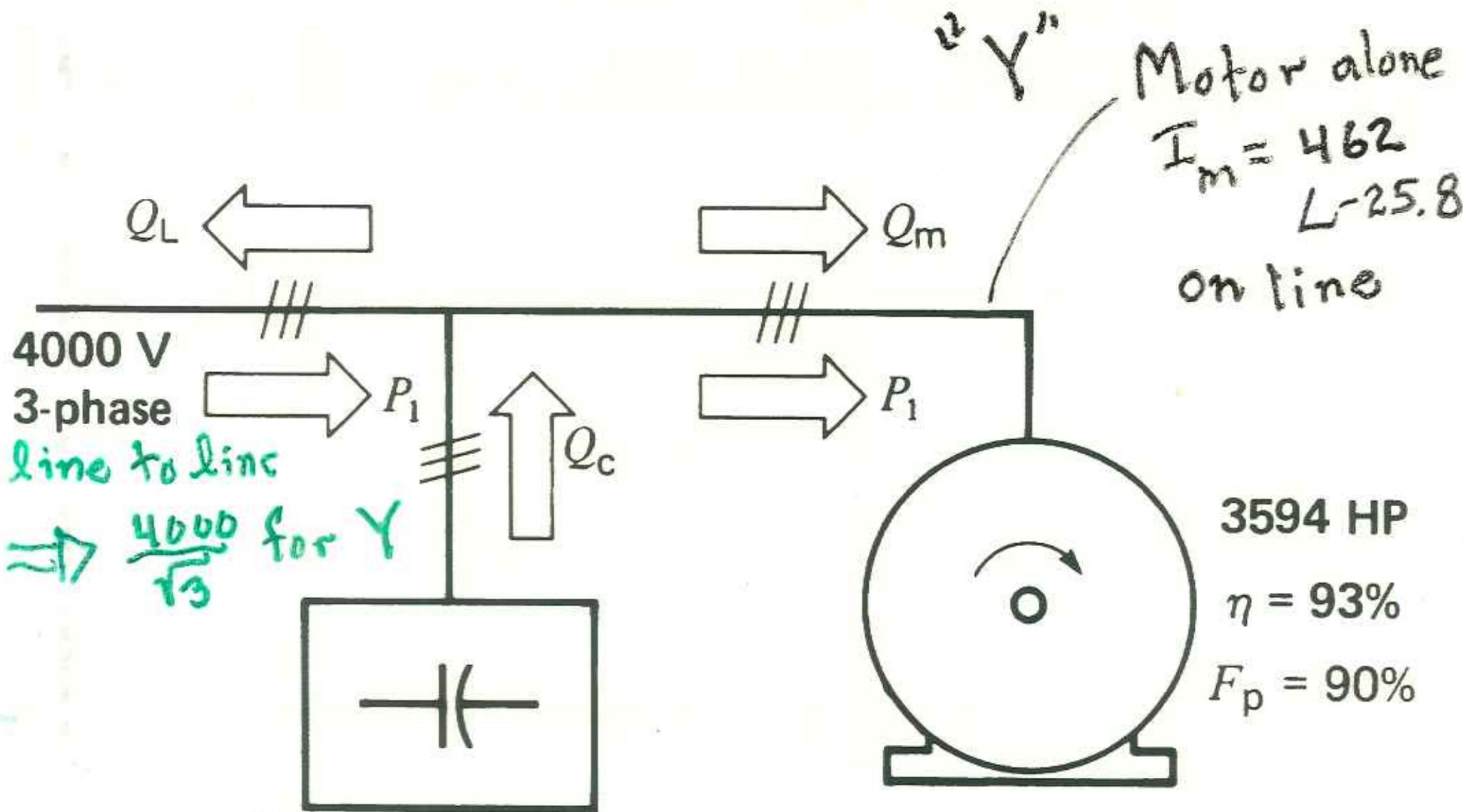


"Y" Capacitor alone
 $I = 260 L90$

What is I_{line} for both in 11


3594 HP
 $\eta = 93\%$
 $F_p = 90\%$

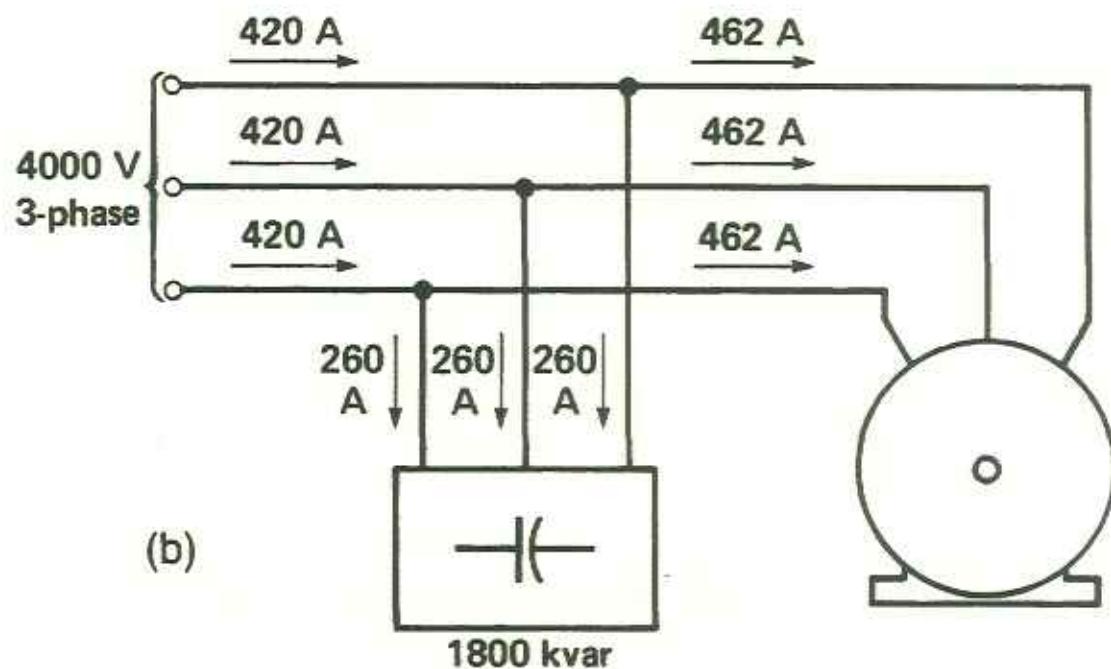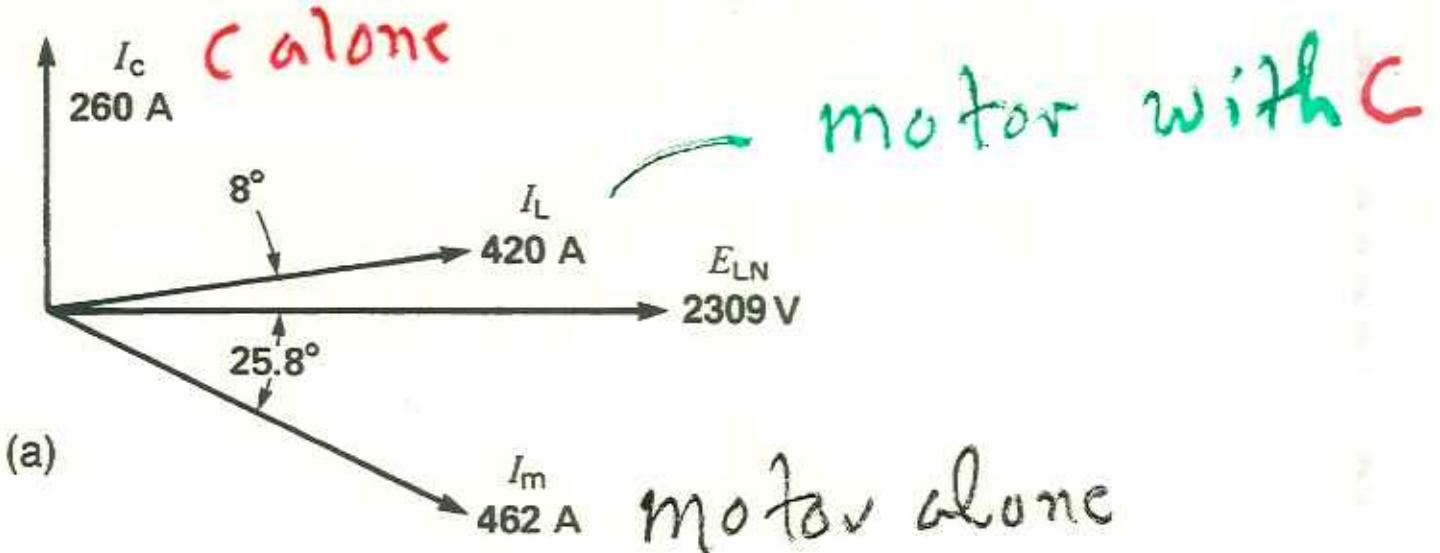

B-31

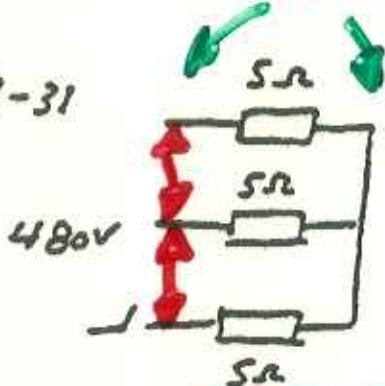

277 industrial voltage

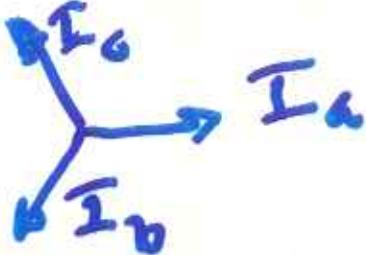


$$E(\text{line-to-neutral}) = 480/\sqrt{3} = 277\text{V}$$

$$I_A = I_B = I_C = 277/5 = 55.4\text{A}$$

If one line is disconnected, the remaining two resistors are in series across the 480V line. The current in each becomes $480\text{V}/10\Omega = 48\text{A}$.



(Tricky lose a Φ
UNbalanced 3 Φ)

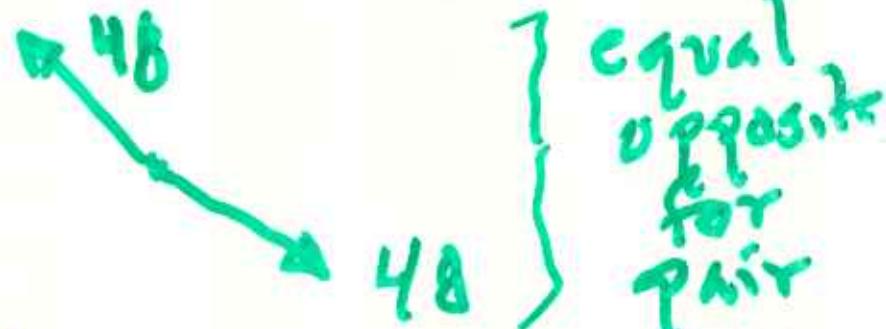



But recall
• R only

upon leg
 $i=0$

2 R $R=0$
third line $\sim R=0$

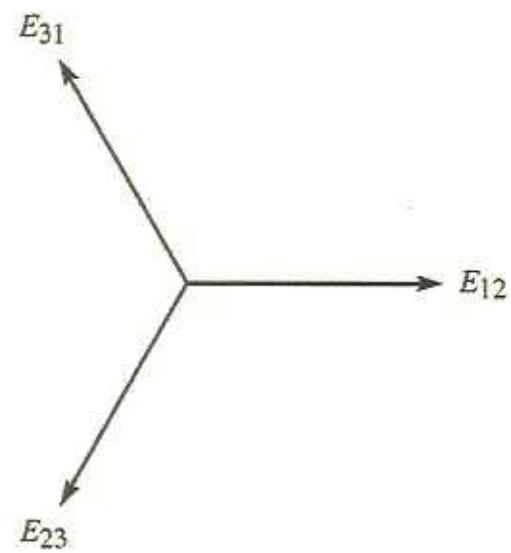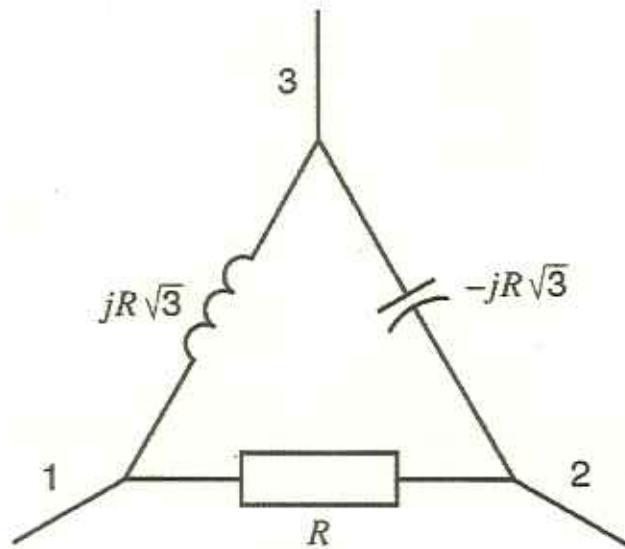


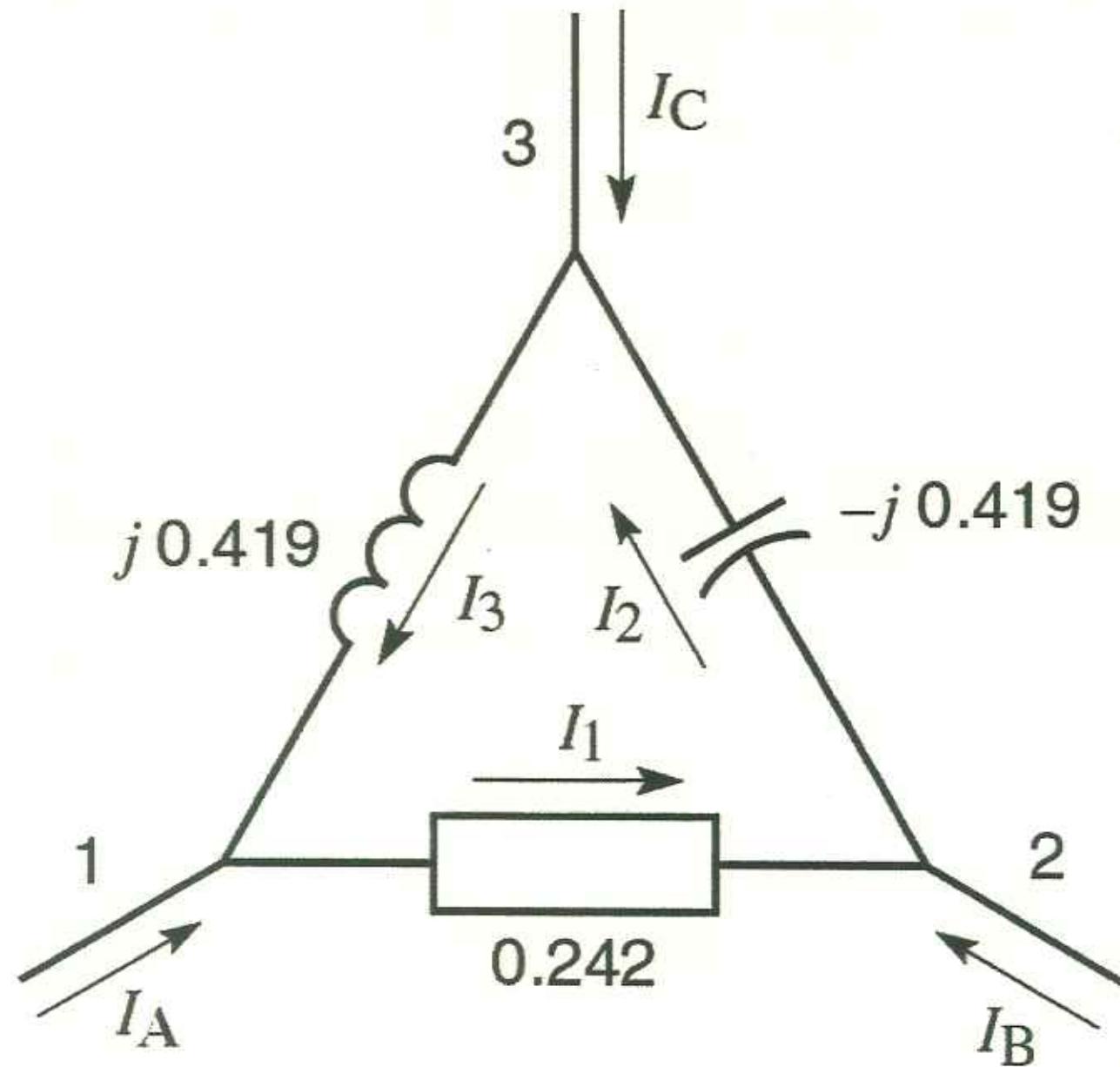

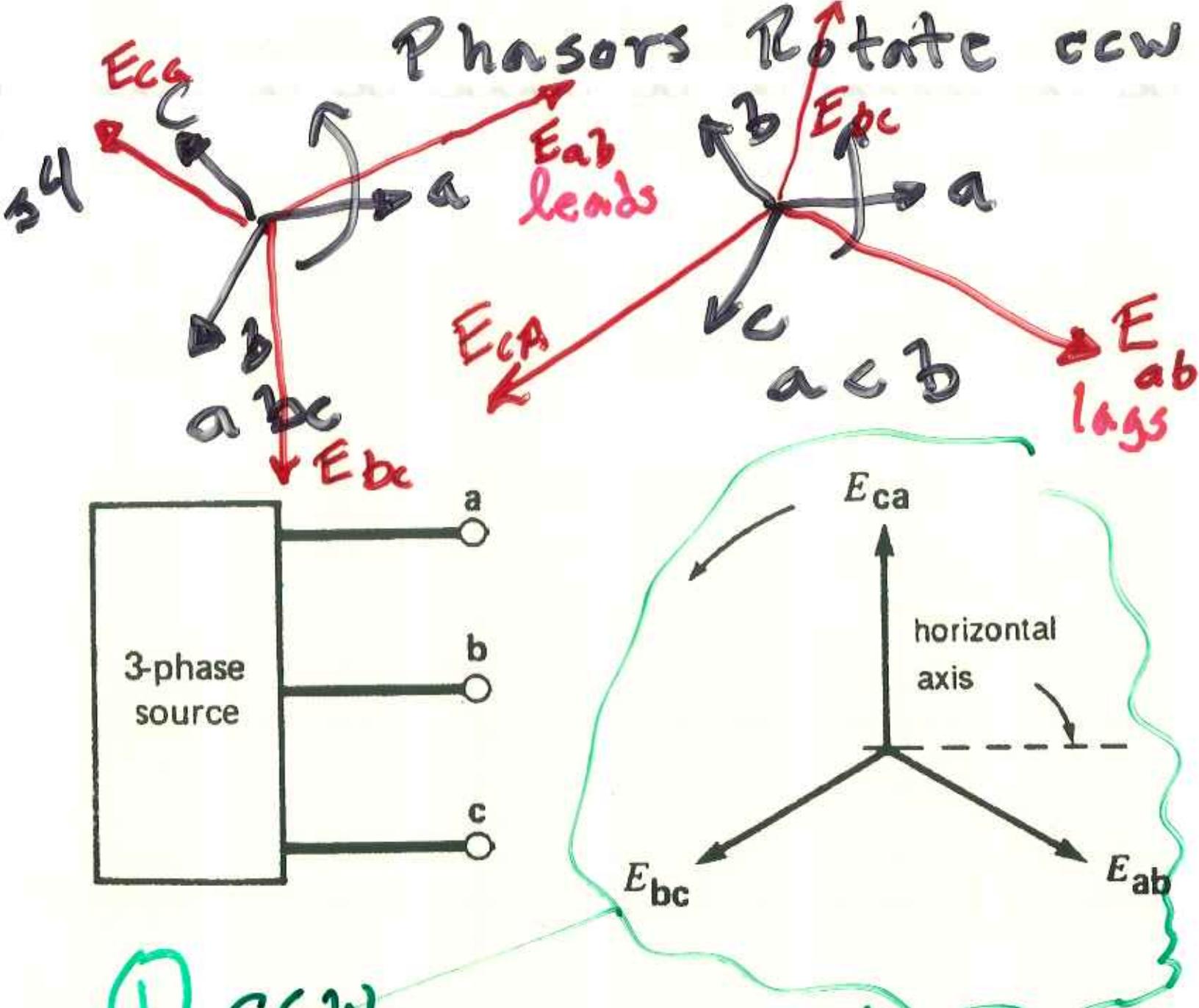

① ccw
Corresponds to what
sequence? } challenge!
cw? }
rotation

35
Below corresponds to
what sequence?

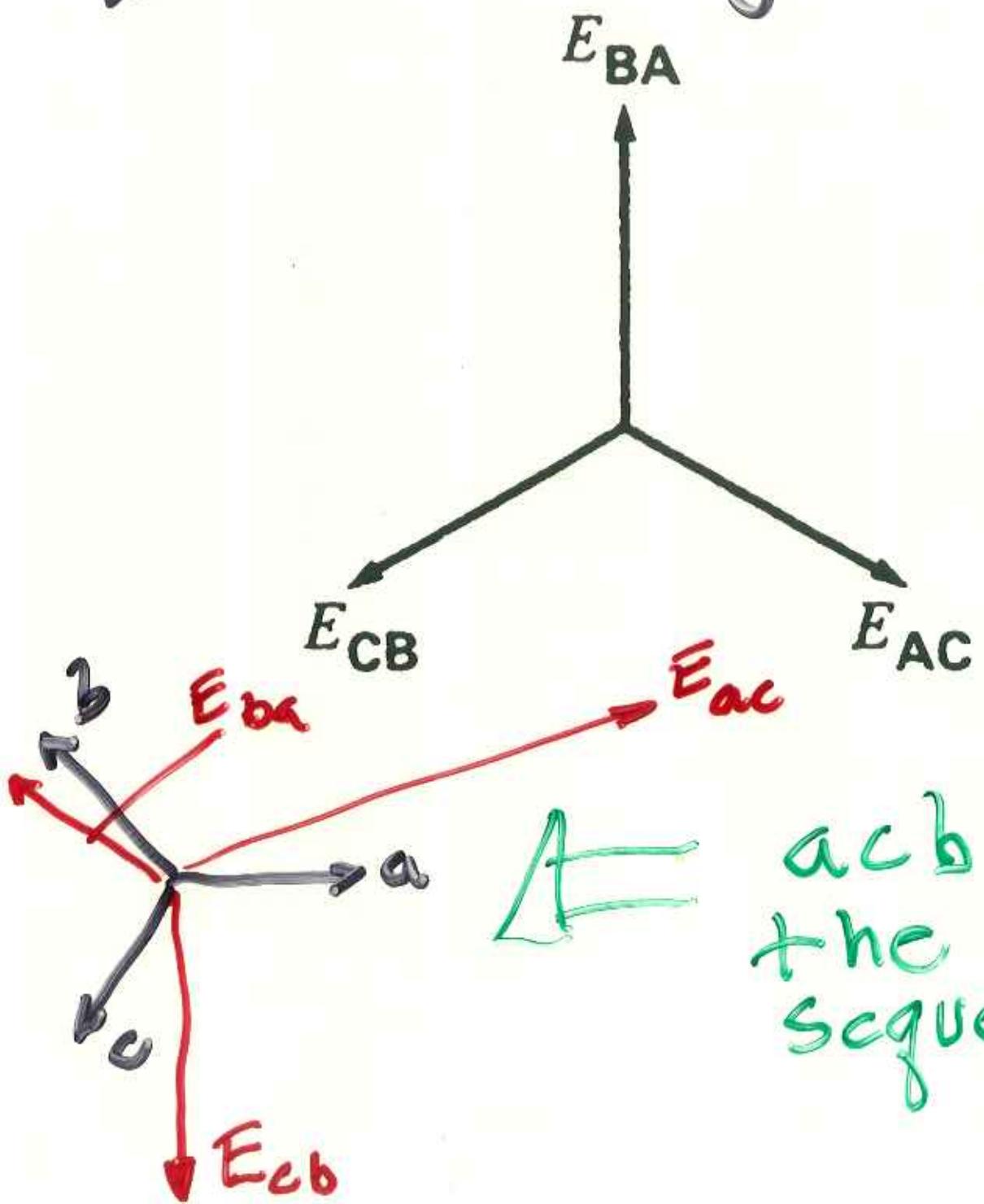


acb is
the
sequence

2 Hot filament bulbs { easy
1 Capacitor { to
{ find

16 Connect all 3 in "WYE"

Fig 8.28
Pg 176

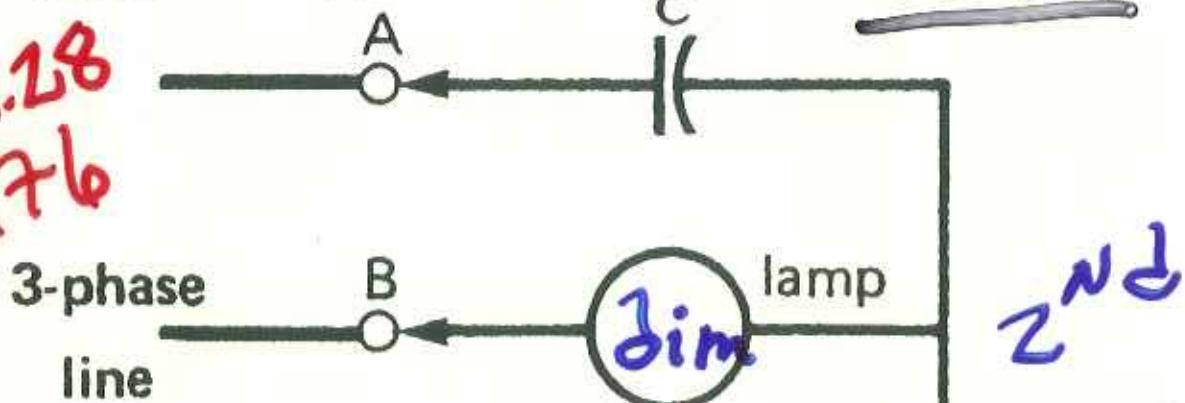

Key
n
Bright first

Leave
neutral
unconnected

Yield
cba

