

## LECTURE 12

Lossy Converters (Static State Losses  
but Neglecting Switching Losses)

### HW #2 Erickson Chapter 3 Problems 6 & 7

A. General Effects Expected:

$V(\text{load}) \downarrow$  as  $I(\text{load}) \uparrow$

B. Switch and Resistive Losses Change  $M(D)$   
Modified DC Voltage Transfer


Functions  $M(D)$  with loss  $\neq M(D)$  for no loss

1. General aspects of the origin of  $M(D)$   
changes in static state loss terms:  
 $R_L, V_d, R_d,$  and  $R_{on}$ 
  - a.  $V_{max} / V_{min}$
  - b.  $V/L$  Slopes
2. General solution for lossy Boost Converter
  - a.  $R_L$  only:  $M(D, R_L), \eta \neq 1$
  - b. Static State Device DC losses:  
 $M(D, V_d, R_{on}, R_D)$
3. Buck Converter
  - a. Problem 3.3 of Erickson
4. General solution for lossy Buck-Boost Converter
  - a.  $M(D, V_d, R_{on}, R_L),$  Problem 3.4 of Erickson
5. Compare for a specific task:
  - a. Buck vs. Buck-Boost Circuits,  
Problem 3.5 of Erickson
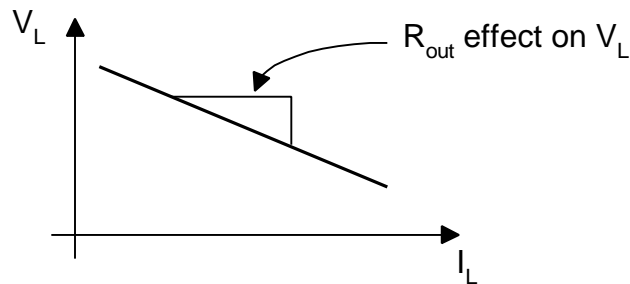
### A. GENERAL EFFECTS EXPECTED ON $M(D)$

Lossy Converters: Consider the static state DC loss only, no dynamic switch loss will be considered here

Generally one expects, due to finite  $R_{out}$ , from any power supply for  $V_L$  to fall as  $I_L$  increases. In converters  $R_{out}$  is much more complex, especially with feedback.



For fixed  $P_{out}$  and  $V_{in}$  for a converter the input current increases proportional to the losses so that  $P_{in} = P_{out} + \text{losses}$ . The losses we will consider will also include device losses but only in the static states due to finite  $R_{on}$  and  $V_{on}$  values.


**B. Effects on voltage DC transfer function  $M(D)$  due to resistive and device voltage drops.** Besides decreasing converter efficiency static state losses will also effect dc transfer functions.  $M(D)$  becomes a function of  $R_L$ ,  $V_{on}$ ,  $R_{on}$ , etc. when losses are included as shown below.

1.  $V_{max}/V_{min}$  changes as seen by any converter inductor will cause  $di/dt$  slope changes.  
 $\Rightarrow \Delta i_L = V/L$  (in units of A/sec) slopes change, affecting  $D$  and  $D'$  themselves just by including resistance and device voltage drops. Hence, the value of  $M(D)$  changes.
2. Including inductor resistance  $R_L$ , device  $R_{on}$ , as well as  $V_{on}$  changes  $M(D)$ , from  $M(D)$  with these effects ignored. Lets consider the inductor


resistance effects.

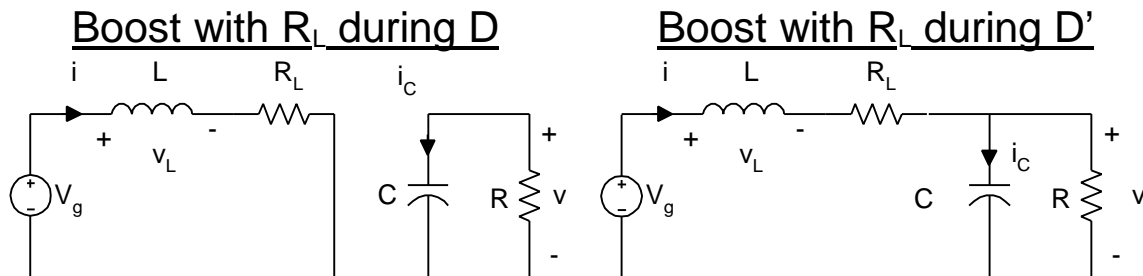- a. Illustrative  $R_L$  (inductor series equivalent resistance) effects in boost topology

**M will change from  $M(D)$  to  $M(D, R_L)$  as shown below.**  
 $R_L$  is finite not only because of simple copper resistive losses. Wound inductors at high frequencies (0.1 - 1 MHz) have additional core and proximity effect losses. To a first approximation:  $R_{ac}/R_{dc} = 0.5 \tilde{D} (\text{wire dia. in cm}) \times f^{1/2} \times 100$   
 Larger diameter wire has more effect than a small diameter  
 Below we carefully distinguish between  $R_L$  with the dominant  $R$  for the load.




1. V-sec balance across  $V_L$

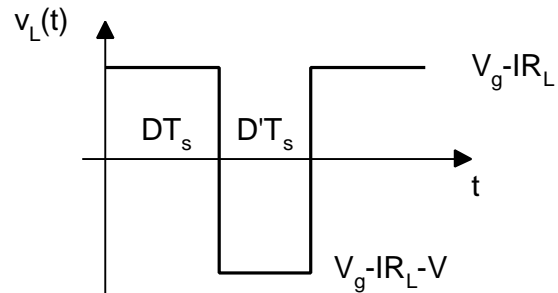

$$D[V_g - IR_L] + D'[V_g - IR_L - V] = 0$$

$$\Rightarrow V_g - IR_L - D'V = 0$$

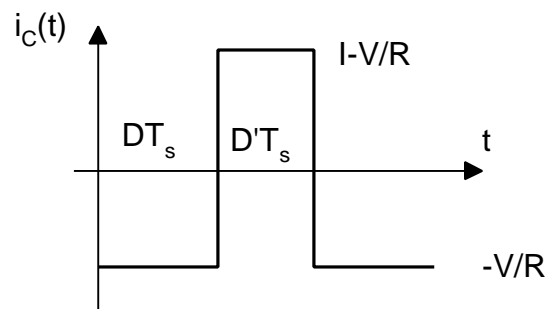2. Current-time balance across the capacitor



$$D[-V/R] + D'[I - V/R] = 0$$

$$\Rightarrow D'I - V/R = 0$$

$$\frac{V_o}{V_g} = \frac{1}{D'} \left[ \begin{array}{l} \text{Usual} \\ \text{Boost} \\ \text{lossless} \\ \text{term} \end{array} \right] \left[ \frac{1}{1 + \frac{R_L}{D'^2 R}} \right]$$

Second term has all effects of including finite  $R_L$ .  
 $\leftarrow R_L > D'^2 R$  big effect  
 Also big effects occur for  $D' \rightarrow 0$  or for  $D \rightarrow 1.0$

Note some extreme converter operating conditions will amplify finite  $R_L$  effects.

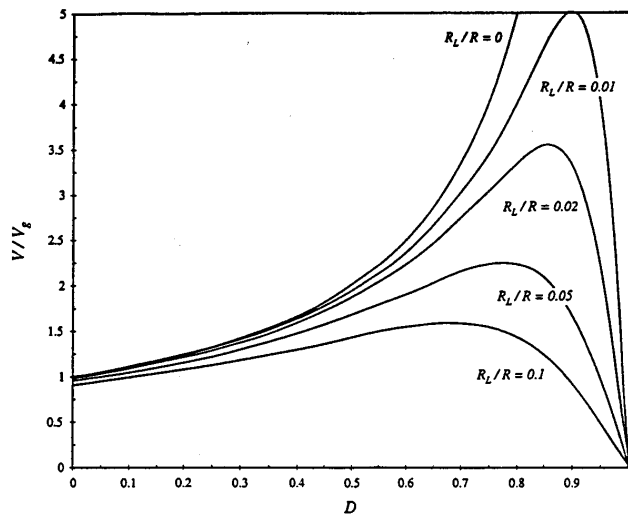


Fig. 3.9. Output voltage vs. duty cycle, boost converter with inductor copper loss.

Note well:

- (1)  $R$  is the load resistor
- (2)  $R_L$  = inductor losses

For  $D \rightarrow 1.0$   
 $R_L/R$  has a big effect on  $M(D)$   
 As  $R_L/R \rightarrow 0$  no effect on  $M(D)$


Note also as  $D \rightarrow 1.0$ ,  $M(D)$  has big “rollover” if  $R_L$  is even 1% of the load resistance. Note also in DC gain at high  $D$  that for  $D \leq 0.2$ ,  $R_L$  effects are minimal.

### Summary

The operating duty cycle,  $D$  value, amplifies equivalent series resistance,  $R_L$ , effects.


$D > 0.5$  and  $R_L/R$  even 1% you see big changes to  $M(D)$ .

$D < 0.5$  you see no effects.

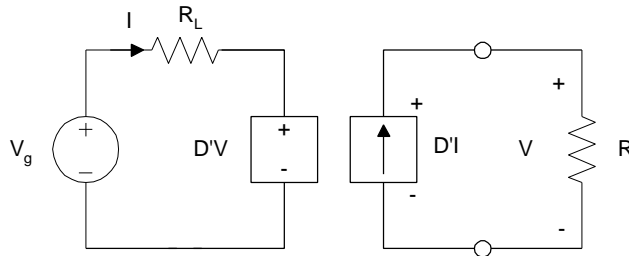


Equivalent Circuit with  
"DC Transformer":  
**Use to get the  
operating  
efficiency**
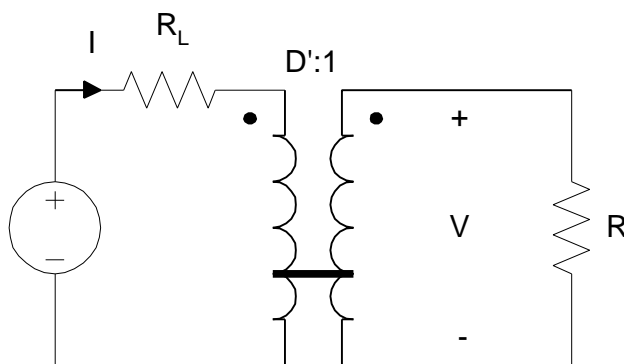
$$\eta = P_{\text{out}} / P_{\text{in}}$$



Equivalent circuit model  
of the boost converter,  
including a  $D':1$  dc  
transformer and the  
inductor winding  
resistance  $R_L$ .

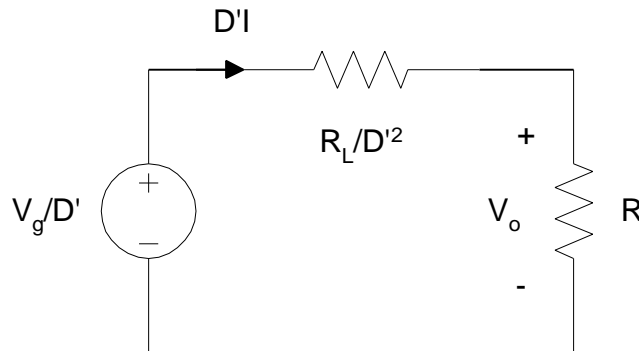Referring to the secondary to get one loop equation.



Clearly want  $R_L \ll D'^2 R$   
Easy if  $D' = 1.0$ ,  $D = 0$   
Hard to achieve if  $D' \rightarrow 0$   
 $D \rightarrow 1.0$

$$V_o = V_g \left[ \begin{array}{c} \text{Ideal} \\ \text{Case} \end{array} \right] \left( 1 + \frac{R_L}{D'^2 R} \right)^{-1}$$

$\uparrow$   
 $1/D'$

$$I(\text{input}) = \frac{V_g}{D'^2} \left[ \frac{\text{Ideal}}{\text{Case}} \right] \left( 1 + \frac{R_L}{D'^2 R} \right)^{-1}$$

$$h = \frac{P_{\text{out}}}{P_{\text{in}}} = \frac{V_o}{V_g} D' = \left( 1 + \frac{R_L}{D'^2 R} \right)^{-1}$$

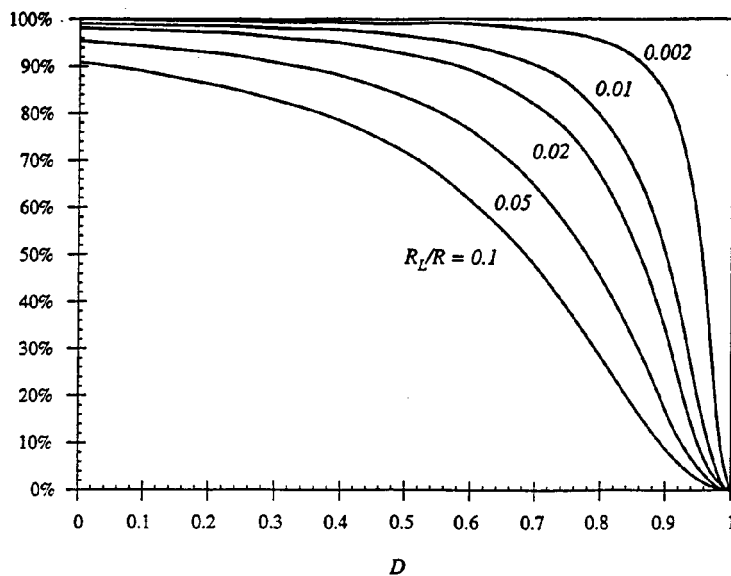



Fig. 3.15. Efficiency vs. duty cycle, boost converter with inductor copper loss.

$\eta(D, R_L/R)$

1) As the on duty cycle  $D \rightarrow 0$  one gets high  $\eta$  but efficiency is little effected by  $R_L$

2)  $D \rightarrow 1$  and  $D' \rightarrow 0$   
 $\eta \rightarrow 0$  still we get much lower  $\eta$  for  $R_L$  not negligible and much greater sensitivity to  $R_L$  changes.

Compare the above to the Lossless Boost:

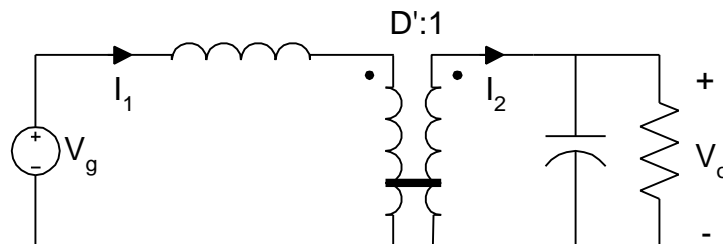

$$I_2 = D' I_1 \quad \eta = D' V_o / V_g = P_o / P_{\text{in}} = 1.0 \text{ (lossless)}$$

$$V_o = V_g / D'$$

Next we include static device losses to the system loss.

b. Static State Device Loss Effects in the Boost Topology.

In our static states of the switching devices we only consider  $R_{on}$  from the transistor but both  $R_D$  and  $V_D$  for the diode when on, because  $V_{on}(TR) \approx 0$ . We expect to obtain  $M(D, R_L, V_{on}, R_D, V_D)$  and  $\eta(D, R_L, R_{on}, R_D, V_D)$ .

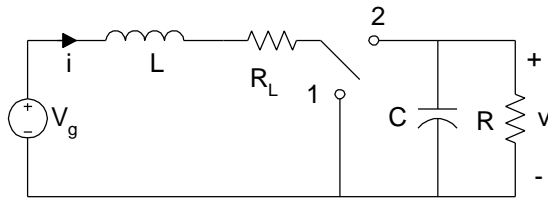


Fig. 3.6. Boost converter circuit, including inductor resistance  $R_L$ .

SW position 1:

SW position 2:

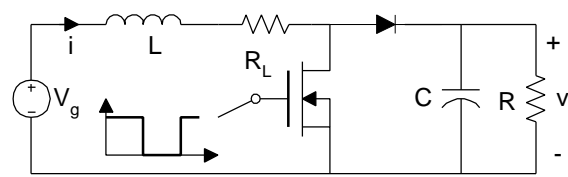



Fig. 3.22. Boost converter example.

Transistor is on case:  $R_{on}(I)$


Diode on case:  $V_D$  and  $R_D$

Effects of  $R_{on}$ ,  $V_D$  and  $R_D$  follow from revised circuits which change values of  $V_L$  and hence circuit  $D$  and  $D'$  periods as well.

Period  $DT_s$  Circuit Connections

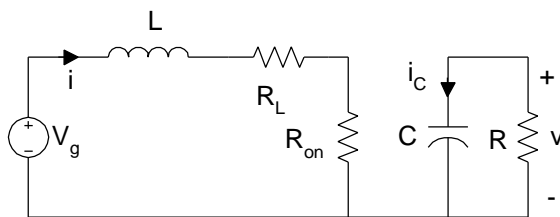


Period  $D'T_s$  Circuit Connections

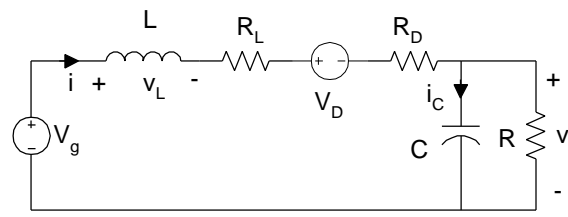

Next, we invoke both volt-sec and current-sec balance on the inductor voltage,  $V_L$ , and capacitor current,  $i_c$ , respectively.

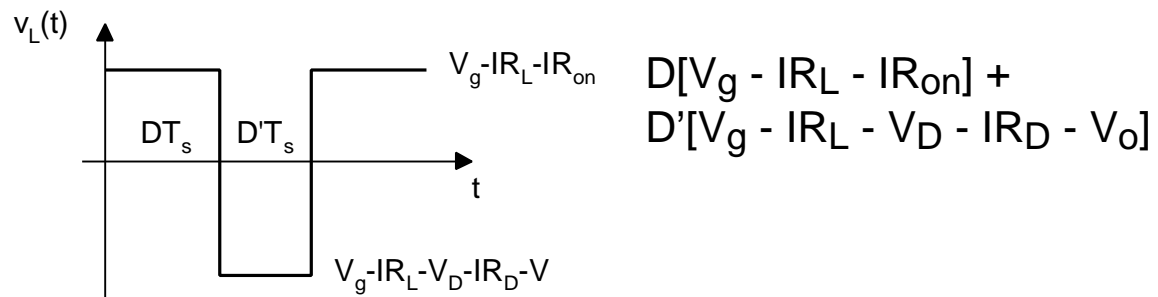
### (1) Volt-sec balance on $V_L$ vs. time




Input Conditions = 0 yields:

$$V_g - IR_L - IDR_{on} - D'V_D - ID'R_D - D'V_o = 0$$

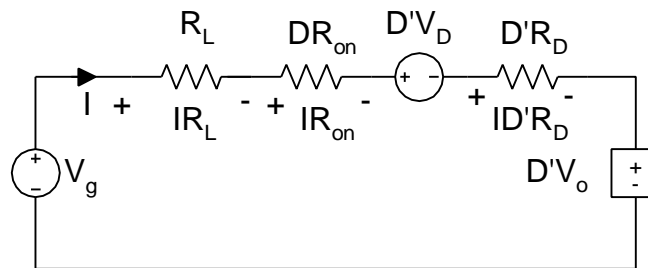
This is the input circuit loop for the above equation:


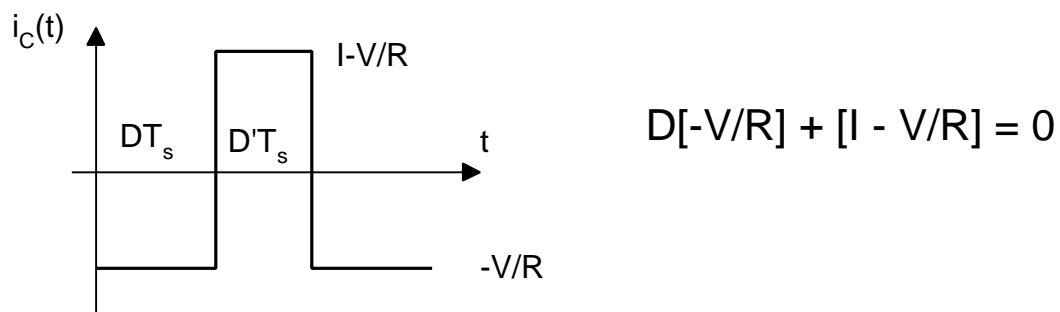
### (2) Current-sec balance on $I_c$ vs. time



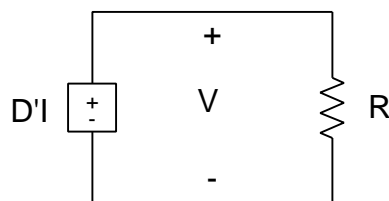Output conditions yield the simple equivalent output circuit result:




$$D'I - V/R = 0$$





- Transistor with  $R_{on}$
- Diode with  $R_D$  and  $V_D$

Lossless Buck:

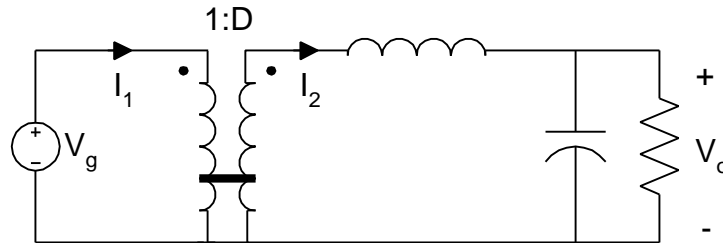


$$V_o = DV_g$$


$$I_1 = I_2/D$$

$$\eta = V_o/(DV_g) = P_o/P_{in}$$

$$= 1.0 \text{ (lossless)}$$

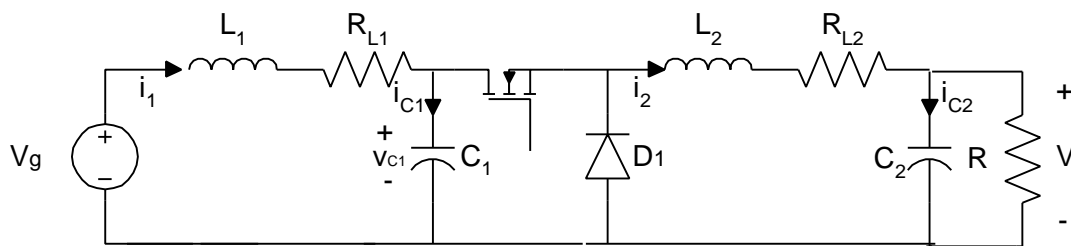

a) Q(on)

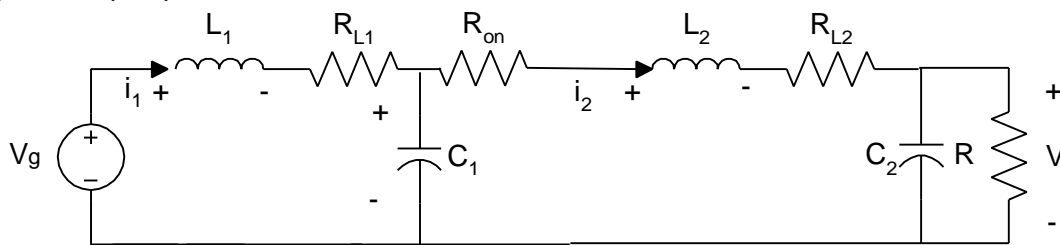


$$V_{L1} = V_g - V_{C1} - I_1 R_{L1}$$

$$V_{L2} = -I_2 R_{on} + V_{C1} - V - I_2 R_{L2}$$

$$I_{C1} = I_1 - I_2$$

$$I_{C2} = I_2 - V/R$$

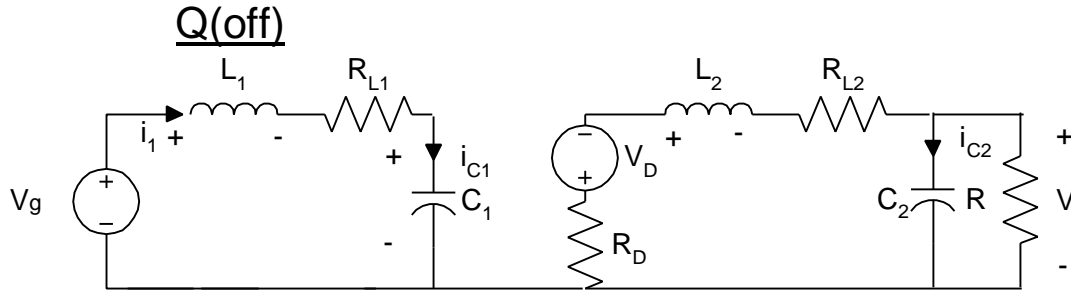Next we will consider the switch case when the transistor is off and the diode is on.



$$V_{L1} = V_g - V_{C1} - I_1 R_{L1}$$

$$V_{L2} = -V_D - I_2 R_D - V - I_2 R_{L2}$$

$$I_{C1} = I_1$$

$$I_{C2} = I_2 - V/R$$

Do Volt-second balance on L's / Charge balance on C's

$$1. L_1: D(V_g - V_{C1} - I_1 R_{L1}) + D'(V_g - V_{C1} - I_1 R_{L1}) = 0$$


$$\therefore V_g = V_{C1} + I_1 R_{L1}$$

$$2. L_2: D(-I_2 R_{on} + V_{C1} - V - I_2 R_{L2}) + D'(-V_D - I_2 R_D - V - I_2 R_{L2}) = 0$$

$$\therefore -D I_2 R_{on} + D V_{C1} - D' V_D - D' I_2 R_D - V - I_2 R_{L2} = 0$$

$$3. C_1: I_1 - D I_2 = 0 \quad \therefore I_1 = D I_2$$
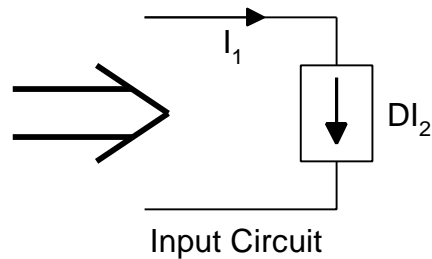
$$4. C_2: I_2 - V/R = 0 \quad \therefore I_2 = V/R$$



$$\text{From 1, 3, and 4} \quad V_{C1} = V_g - I_1 R_{L1} = V_g - D I_2 R_{L1} = V_g - D R_{L1} \frac{V}{R}$$

$$\therefore V_{C1} = V_g - D R_{L1} \frac{V}{R}$$

Output Circuit:

Then:

$$(2) -D R_{on} \frac{V}{R} + D V_g - D^2 R_{L1} \frac{V}{R} - D' V_D - D' R_D \frac{V}{R} - V - R_{L2} \frac{V}{R} = 0$$

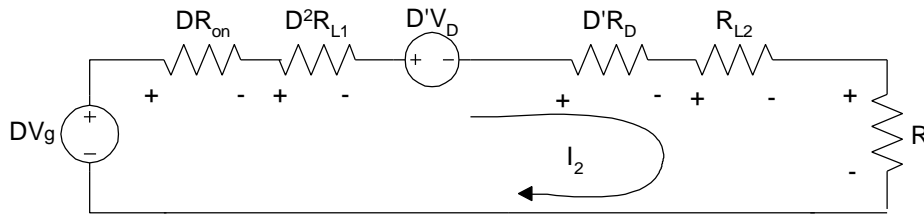


Fig. 1

DC Trf Model:

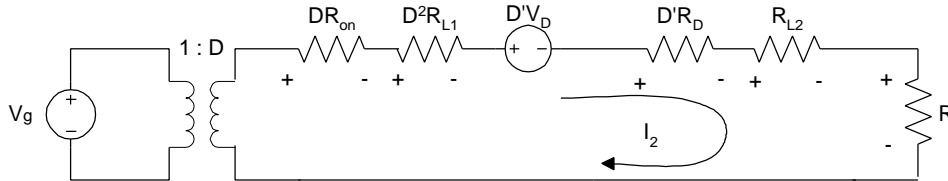


Fig. 2

b) From Fig. 1

$$V = -DR_{on} \frac{V}{R} + DV_g - D^2R_{L1} \frac{V}{R} - D'V_D - D'R_D \frac{V}{R} - R_{L2} \frac{V}{R}$$

c) Using the Voltage Divider:

$$V = \frac{R}{R + DR_{on} + D^2R_{L1} + D'R_D + R_{L2}} (DV_g - D'V_D)$$


Filtered Buck

$$\frac{V}{V_g} = (D - D' \frac{V_D}{V_g}) \frac{R}{R + DR_{on} + D^2R_{L1} + D'R_D + R_{L2}}$$

$$\eta = \frac{V}{DV_g} = (1 - \frac{D'V_D}{DV_g}) \frac{R}{R + DR_{on} + D^2R_{L1} + D'R_D + R_{L2}}$$


Next we solve the general equations for the Buck-Boost

#### 4. Buck-Boost solved in general

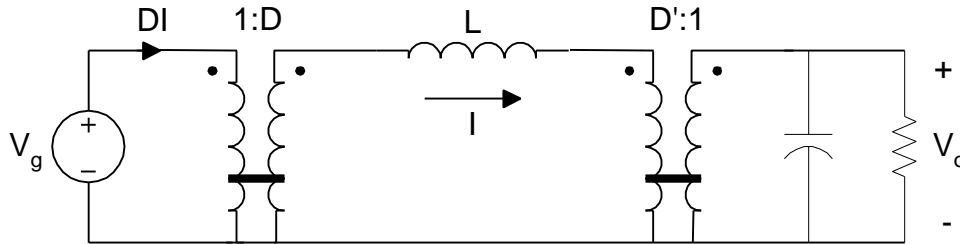

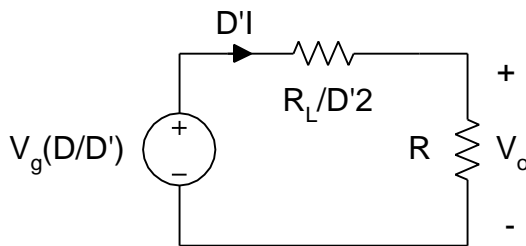(a) Equivalent Series Resistance,  $R_L$ , losses only

- Assume lossless except for  $R_L$
- Reflect all to load side. For DC  $L \rightarrow$  short and  $C \rightarrow$  open.



For DC conditions:


$$V_o = \frac{R}{\frac{R_L}{D'^2} + R} V_g \frac{D}{D'}$$


(b) **Device losses only**

Buck-Boost with device loss ( $R_L \equiv 0$ )


Transistor:  $R_{on}$

Diode:  $V_D$

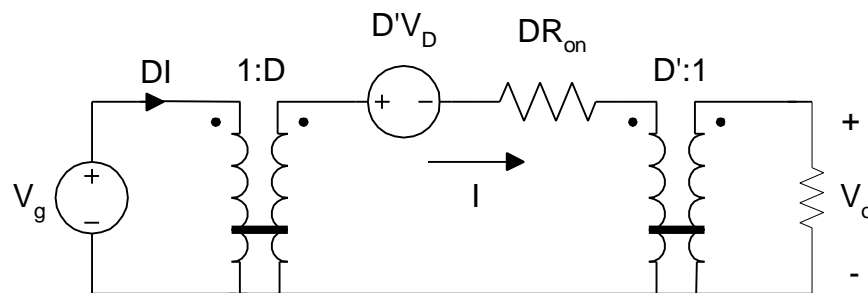

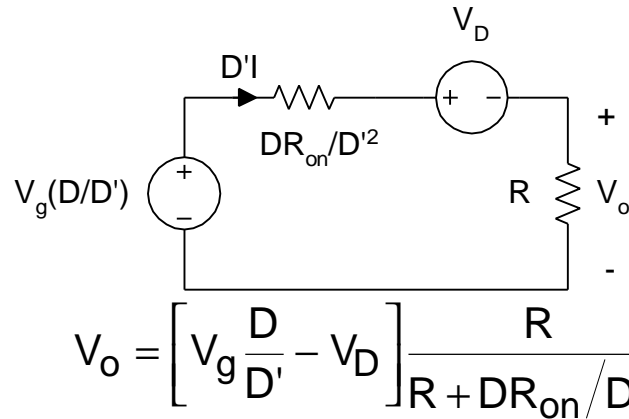

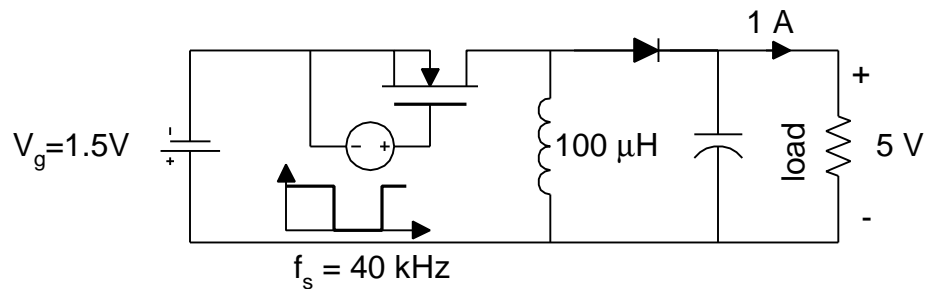(c) Buck-Boost Converter including all static losses. This is problem 3.4 from Erickson



$V_{out}$  required is +5 V and  $V_g = -1.5$  V

Diode:  $V_D = 0.5$  V Schottky

$R_D = 0$  (approx.)

Transistor:  $R_{on} = 35$  m $\Omega$

Ideal Buck-Boost:

$$\frac{V_o}{V_g} = \frac{-D}{1-D} = \frac{-D}{D'}$$

Real Buck-Boost: we will find in the next few pages


$$V_o = \left[ \frac{D}{D'} V_g - V_D \right] \frac{R}{R + \text{other}(R_{on}, R_L)}$$

$\uparrow$                        $\uparrow$   
**Diode**                      **Resistive**  
**Effect**                      **Effect**


Below we work out Erickson problem 3.4 for illustration of how to do the HW for Chapter 3

HW # 2 will be Erickson Chapter 3 Pbms.6 and 7. This will be due next week along with any questions asked in the lectures

3-4 Buck boost

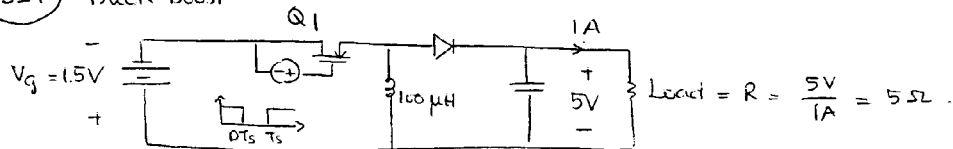


(a) when MOSFET conducts

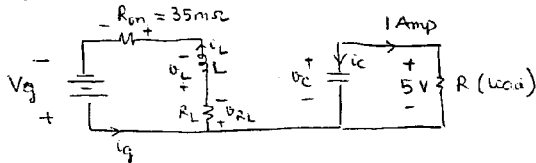

$$\begin{cases} v_L(t) = v_g - v_{RL} - v_{Ron} \approx v_g - I R_L - I R_{on} \\ i_c(t) = -\frac{v}{R} \approx -\frac{V}{R} \end{cases}$$

when diode conducts

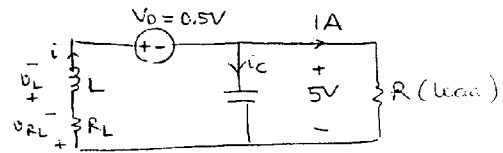


$$\begin{cases} v_L(t) = -v_D - i R_L - v \approx -V_D - I R_L - V \\ i_c(t) = i - \frac{v}{R} \approx I - \frac{V}{R} \end{cases}$$

DC component of inductor voltage is given by

$$\langle v_L \rangle = D (v_g - I R_{on} - I R_L) + D' (-V_D - I R_L - V) = 0$$

$$D v_g - D I R_{on} - D I R_L - D' V_D - D' I R_L - D' V = 0$$

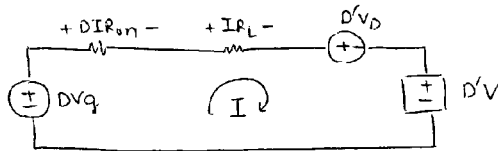
since  $D + D' = 1 \Rightarrow$   $D v_g - D I R_{on} - I R_L - D' V_D - D' V = 0$



and  $\langle i_c \rangle = D (-\frac{V}{R}) + D' (I - \frac{V}{R}) = 0$


$$-D \frac{V}{R} + D' I - D' \frac{V}{R} = 0$$

$$D' I - \frac{V}{R} = 0$$

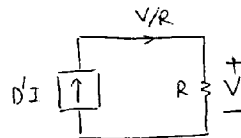


also  $\langle i_g \rangle = I_g = D I$


$$I_g = D I$$

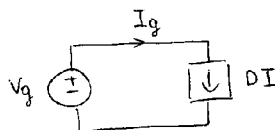


Put 3 ccts together:

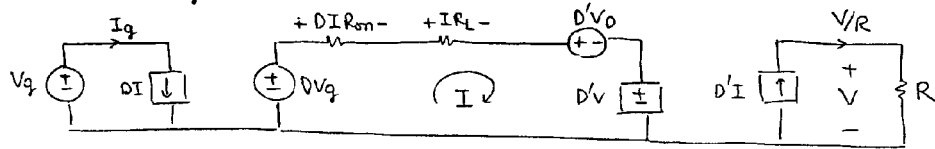

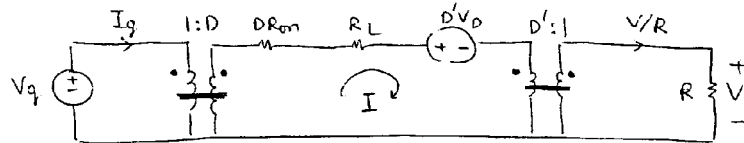The completed dc equivalent ckt model (Buck Boost)



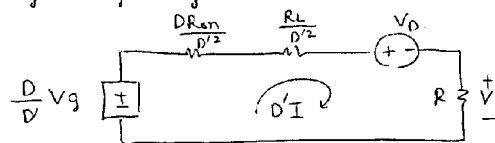(b) Reflecting everything on the middle ckt, we get



$$Vg = 1.5 \text{ Volts}$$

$$V = 5 \text{ Volts}$$

$$R = 5 \Omega$$

$$R_{in} = 35 \text{ m}\Omega$$

$$V = \left( \frac{D}{D'} Vg - V_D \right) \left( \frac{R}{R + \frac{D}{D'^2} R_{in} + \frac{R_L}{D'^2}} \right) \quad \text{using voltage divider}$$

$$\Rightarrow \frac{V}{Vg} = \left( \frac{D}{D'} - \frac{V_D}{Vg} \right) \left( \frac{R D'^2}{R D'^2 + D R_{in} + R_L} \right) = \frac{D}{D'} \left( 1 - \frac{D' V_D}{D Vg} \right) \underbrace{\left( \frac{1}{1 + \frac{D}{D'^2} \frac{R_{in}}{R} + \frac{R_L}{D'^2}} \right)}_{\text{Efficiency } \eta}$$

with  $\frac{D}{D'} \equiv$  dc conversion ratio in the ideal case  
( $R_L = R_{in} = V_D = 0$ )

$$\eta = \frac{P_{out}}{P_{in}} = \frac{D' I V}{D I Vg} = \frac{D'}{D} \cdot \frac{V}{Vg} \quad \Leftrightarrow \quad 0.7 = \frac{1-D}{D} \cdot \frac{5}{1.5}$$

$$\Leftrightarrow \quad \boxed{D = 0.83} \quad \text{and} \quad D' = 1 - 0.83 = \boxed{0.17}$$

$$\text{So } 0.7 = \left( 1 - \frac{0.17}{0.83} \frac{0.5}{1.5} \right) \left( \frac{1}{1 + \frac{0.83}{0.17^2} \cdot \frac{35 \text{m}}{5} + \frac{R_L}{0.17^2 (5)}} \right) \quad \Rightarrow \quad \boxed{R_L \approx 20 \text{ m}\Omega}$$

$$I = \frac{1}{D'} I_2 = \frac{1 \text{ Amp}}{0.17} = \frac{1}{0.17} = 5.88 \text{ Amp}$$



(c) Compute power loss:


$$\begin{cases}
 P_{R_L} = I^2 R_L = (5.88)^2 (20\text{m}) = \boxed{0.69\text{W}} \\
 P_{R_{\text{on}} D} = I^2 R_{\text{on}} D = (5.88)^2 (35\text{m}) (0.83) = \boxed{1\text{W}} \\
 P_{\text{diode}} = V_D I = (0.5) (1) = \boxed{0.5\text{W}}
 \end{cases}$$

$$P_{\text{in}} = 0.69 + 1 + 0.5 + 5 = \boxed{7.19\text{W}}$$


$$P_{\text{out}} = 5 (1)^2 = \boxed{5\text{W}}$$

check :  $\eta = \frac{P_{\text{out}}}{P_{\text{in}}} = \frac{5}{7.19} = 0.69 \approx 0.7 \Rightarrow \text{OK!}$

(d) Plots :

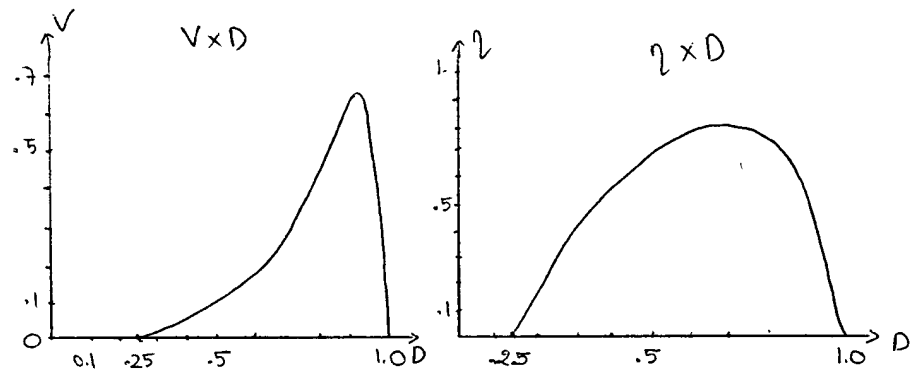

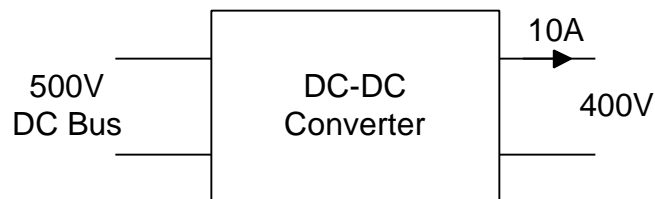(5) Compare Buck vs. Buck-Boost Topology for DC Conditions Only. This is problem 3.5 of Erickson.




Transistor:  $R_{\text{on}} = 0.5 \Omega$        $R_D \rightarrow 0$   
 Diode:  $V_D \rightarrow 0$                       Inductor:  $R_L \rightarrow 0$

Find  $D$  and  $\eta$  for placing different topologies inside the DC-DC converter. Then compare why one topology might be favored over the other for the specified conditions.


**Prob. 3.5**

Only loss is Mosfet with  $R_{on} = 0.5\Omega$

**Buck**

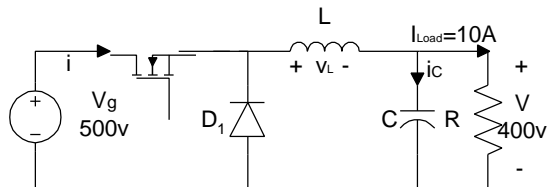


Mosfet on and Diode off.

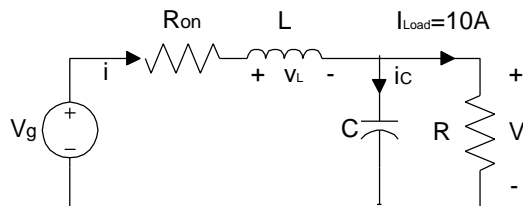

$$v_L(t) = V_g - i R_{on} - V \approx V_g - I R_{on} - V$$

$$i_c(t) = i - 10 \approx I - 10$$

Mosfet off and Diode on.

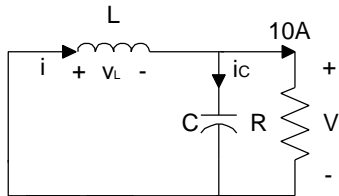

$$v_L(t) = -V$$

$$i_c(t) = i - 10 \approx I - 10$$

Thus averaging we get:


$$\langle v_L \rangle = (V_g - I R_{on} - V)D + (-V)D' = 0$$

$$\langle i_c \rangle = D(I - 10) + D'(I - 10) = 0$$


$$\text{So } \Rightarrow DV_g - D I R_{on} - V = 0$$

$$I - 10 = 0 \Rightarrow I = 10$$

**Buck-Boost**

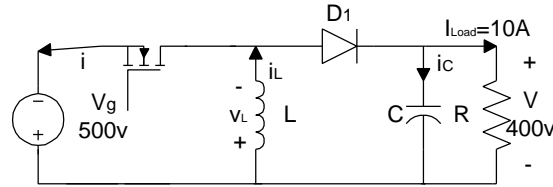


Mosfet on and Diode off.

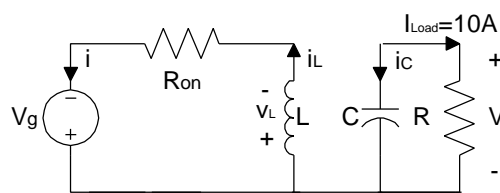

$$v_L(t) = V_g - i R_{on} \approx V_g - I R_{on}$$

$$i_c(t) = -10$$

Mosfet off and Diode on.

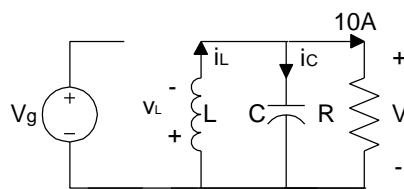

$$v_L(t) = -V$$

$$i_c(t) = i - 10 \approx I - 10$$





Thus averaging we get:

$$\langle v_L \rangle = (V_g - I R_{on})D + (-V)D' = 0$$

$$\langle i_c \rangle = D(-10) + D'(I - 10) = 0$$

$$\text{So } \Rightarrow DV_g - I R_{on} D - V + VD = 0$$

$$I D' - 10 = 0 \Rightarrow I = 10/D'$$

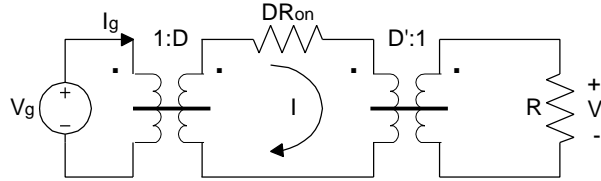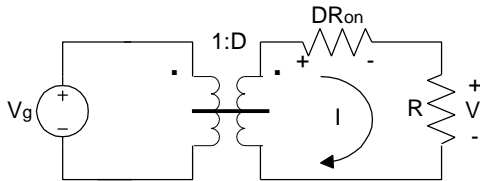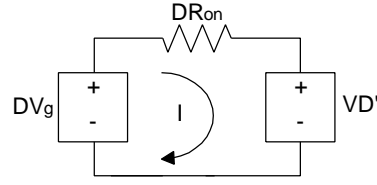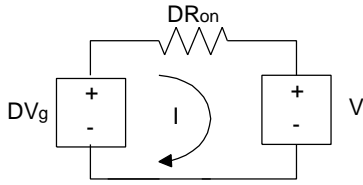

First we need D:

$$DVg - 10R_{on}D - V = 0$$

$$D = V/(Vg - IR_{on})$$

$$D = \underline{0.81}; D' = \underline{0.19}$$

Solving for efficiency:  $I_g = DI$

$$\eta = P_{out}/P_{in} = V I_{load}/VgDI$$

$$= (4000)/[DVg(10)]$$

$$\eta = 0.99 = \mathbf{99\%}$$

$$P_{loss} = P_{in} - P_{out}$$

$$P_{loss} = 4050 - 4000 = \mathbf{50 \text{ Watts}}$$

**The BUCK is better for this application!**

Another way to calculate the Power loss is to use the voltage divider and find  $V_g$  with Respect to  $V$  as shown below:

$$V = \frac{RDVg}{R + DR_{on}}$$

Knowing that:

$V = DVg$  for the lossless Buck:

$$\text{we can see that } \frac{R}{R + DR_{on}} = 1$$

for the lossless Buck case thus:

$$\eta = \frac{R}{R + DR_{on}}$$

$$\eta = 0.99 = \mathbf{99\%}$$

since  $\eta = P_{out}/P_{in}$ :

$$P_{in} = P_{out}/\eta = 4000/.99 = 4040.4 \text{ W}$$

$$P_{loss} = 4040.4 - 4000 = \mathbf{40.4 \text{ W}}$$

**The BUCK is better for this application!**

$$DVg - 10R_{on}D/D' - VD' = 0$$

$$DVg - VgD^2 - 10R_{on}D - V + 2VD - VD^2 = 0$$

$$D^2(-Vg - V) + D(2V + Vg - 10R_{on}) - V = 0$$

Using the quadratic equation for D:

$$D = \underline{0.45}; D' = \underline{0.55}$$

Solving for efficiency:  $I_g = ID$

$$\eta = P_{out}/P_{in} = V I_{load}/VgID$$

$$= (4000)/[VgD(10/D')]$$

$$\eta = 0.978 = \mathbf{97.8\%}$$

$$P_{loss} = P_{in} - P_{out}$$

$$P_{loss} = 4090 - 4000 = \mathbf{90 \text{ Watts}}$$

$$V = \frac{RDVg}{D'(R + \frac{DR_{on}}{D'^2})}$$

$V = DVg/D'$  for the Buck-Boost:

$$\eta = \frac{R}{(R + \frac{DR_{on}}{D'^2})}$$

$$\eta = 0.98 = \mathbf{98\%}$$

$$P_{in} = P_{out}/\eta = 4000/.98 = 4081.63 \text{ W}$$

$$P_{loss} = 4081.63 - 4000 = \mathbf{81.63 \text{ W}}$$