

Lecture 38

Establishing DCM V_{out}/V_{in} Quadratic Relations

A. DCM DC Transfer Functions via Quadratic Relations

1. Overview of the DCM Operation Conditions
2. V_o for the Buck
3. V_o for the Boost
4. V_o for the Buck-Boost
5. Summary
6. $L_{critical}$ for the Three Major Circuits
7. Critical Capacitance: $C_{critical}$

B. Homework Solutions and Hints

1. Problem 5.1
2. Problem 5.9
3. Hints for Problem 5.4
4. Hints for Problem 5.14

Lecture 38


Establishing DCM V_{out}/V_{in} Quadratic Relations

A. DCM DC Transfer Functions via Quadratic Relations

1. Overview


The figure below summarizes DCM operation for all three major converters: buck, boost and buck-boost using transistor and diode switches. Note i_L (inductor) goes to zero each switch period and hence is insured to start from zero at the start of each switch period. We will show i_L (on far left), i_{in} (middle plot), and i_d (far right) for each circuit versus time. Note that V_o in DCM comes only from solving a quadratic equation not from $M(D)$, assuming V_{in} is constant over the switch period. $P_{in} = P_{out}$ is also assumed. We will use linear variations of all currents as a good first approximation.

1. V_o Buck

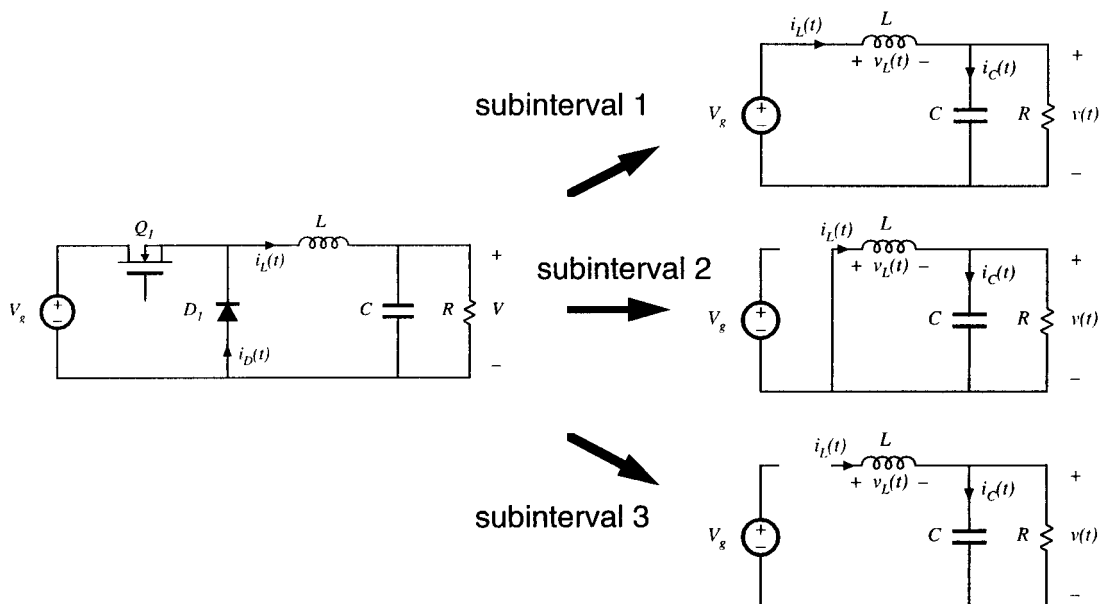

The three circuit topologies for the buck are as above:

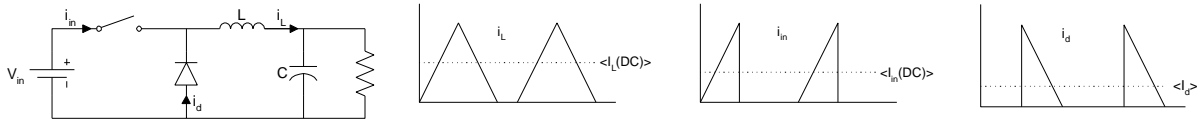The circuit and associated waveforms are shown below in DCM operation.



$$v_L = D_1(V_{in} - V_{out}) + D_2(-V_{out}), (D_1 + D_2)V_{out} = D_1V_{in}$$

$$I_L(\text{DC}) = V_{out}/R = \frac{1}{2}(D_1 + D_2) i_L(\text{max})$$

b. Derivation of DCM DC Transfer Function

Since D_1T_s is set by the control circuit and V_{in} is assumed constant, the peak inductor current is from the far left waveform:

$$i_L(\text{peak}) = D_1T_s \left[\frac{(V_{in} - V_{out})}{L} \right]$$

From i_{in} triangular waveforms in the middle plot we calculate:

$$i_{in}(\text{av}) = \frac{D_1}{2} i_L(\text{peak}) = D_1^2 T_s \left[\frac{(V_{in} - V_{out})}{2L} \right]$$

$$P_{in}(\text{av}) = V_{in}(\text{constant}) i_{in}(\text{av}) = D_1^2 T_s \left[\frac{(V_{in}^2 - V_{in} V_{out})}{2L} \right]$$

For lossless converters we can say the following:

$$P_{in} = P_{out} = V_{out}^2/R$$

Yielding a quadratic equation in V_{out} .

Solving:

$$V_o(\text{DCM Buck}) = \frac{-D_1^2 V_{in} R T_s}{4L} + D_1 V_{in} \sqrt{\frac{RT}{2L} + \frac{R^2 T_s^2 D_1^2}{16L^2}}$$

c. Alternative Derivation

Two equations and two unknowns (V and D_2):

$$V = V_g \frac{D_1}{D_1 + D_2} \quad (\text{from inductor volt-second balance})$$

$$\frac{V}{R} = \frac{D_1 T_s}{2L} (D_1 + D_2) (V_g - V) \quad (\text{from capacitor charge balance})$$


Eliminate D_2 , solve for V :

$$\frac{V}{V_g} = \frac{2}{1 + \sqrt{1 + 4K/D_1^2}}$$

where $K = 2L / RT_s$

valid for $K < K_{crit}$

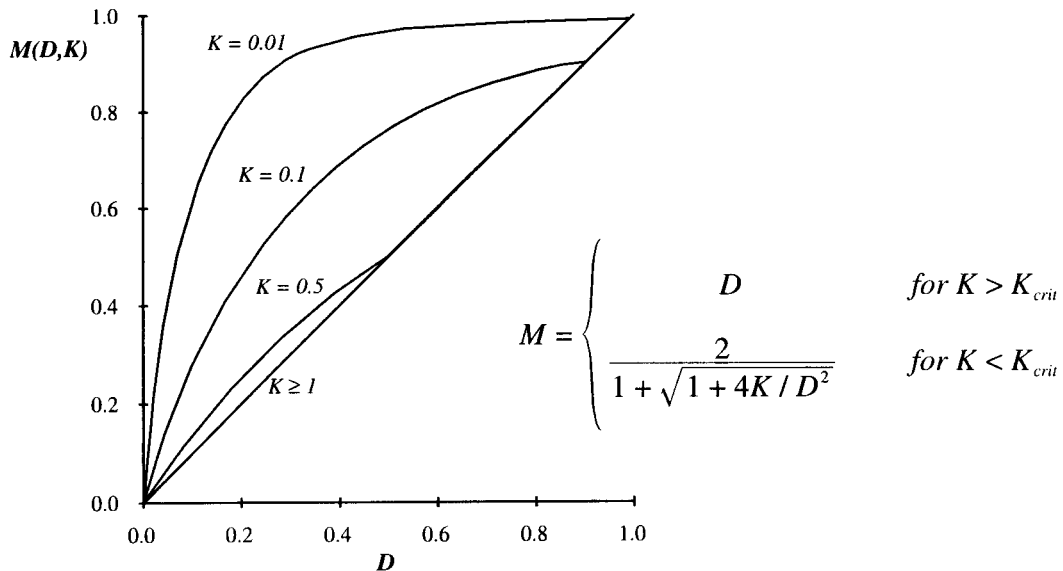We get this from doing out steady-state balance. The resulting plot for the buck DCM transfer function vs. D is:




Again note the trend for the DCM DC transfer function to be bigger for all D values than the CCM transfer function.

3 V_o Boost in DCM Operation

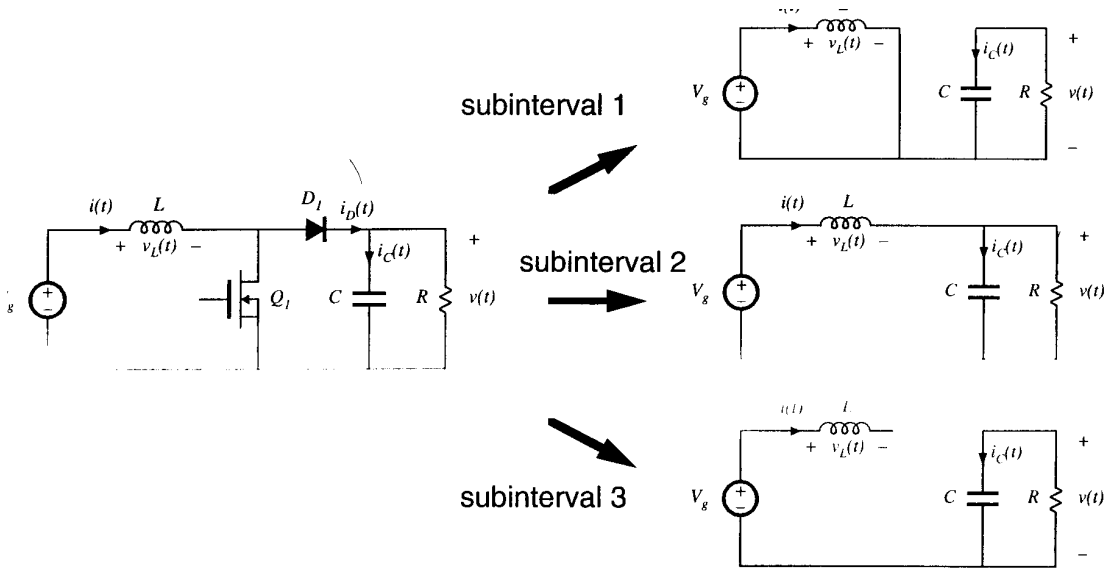
a. General

The three circuit topologies for the DCM boost are shown below:



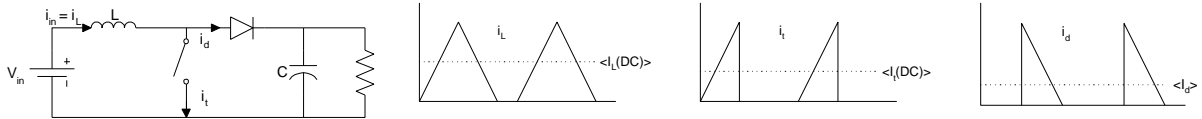b. Derive DCM DC Transfer Function

We also show below the three boost circuit current waveforms i_L (inductor), i_t (switch) and i_D (diode):



$$V_L = D_1(V_{in}) + D_2(V_{in} - V_{out}), (D_1 + D_2)V_{in} = D_2V_{out}$$

$$I_L(DC) = I_{in}(DC) = \frac{1}{2}(D_1 + D_2) i_L(max)$$

Since D_1 is set by the control circuit the and V_{in} is fixed the peak inductor current from the left side plot is:

$$i_L(peak) = \frac{D_1 T_s V_{in}}{L}$$

From the middle I_{in} plot vs. time in the middle we can find:

$$I_{in}(av) = I_L(av) = \frac{D_1 + D_2}{2} i_L(peak)$$

$$I_{in}(av) = \frac{(D_1 + D_2)V_{in} D_1 T_s}{2L}$$

$$P_{in}(av) = V_{in}(fixed) I_{in}(av) = \frac{(D_1 + D_2)V_{in}^2 D_1 T_s}{2L}$$

$P_{in}(av) = P_{out}(av) = V_o^2/R_L$
Both D_2 and V_{out} are unknown.

Yielding a quadratic equation in V_{out} . Fortunately the sawtooth diode current waveform drives the load so that

$$I_{out(av)} = V_{out}/R = \frac{D_2}{2} i_{diode(peak)}$$

Which sets $D_2 = \frac{2V_o L}{RV_{in} D_1 T}$ and we obtain a new quadratic equation for V_o .

Solving:

$$V_o(\text{Boost DCM}) = \frac{V_{in}}{2} + \frac{V_{in}}{2} \sqrt{1 + \frac{2RT_s D_1}{L}}$$

c. Alternative DCM Transfer Function Derivation

Two equations and two unknowns (V and D_2):

$$V = \frac{D_1 + D_2}{D_2} V_g \quad (\text{from inductor volt-second balance})$$

$$\frac{V_g D_1 D_2 T_s}{2L} = \frac{V}{R} \quad (\text{from capacitor charge balance})$$

Eliminate D_2 , solve for V . From volt-sec balance eqn:

$$D_2 = D_1 \frac{V_g}{V - V_g}$$

Substitute into charge balance eqn, rearrange terms:

$$V^2 - VV_g - \frac{V_g^2 D_1^2}{K} = 0$$

This can be solved via the quadratic formula as shown on page 7.

Solving for V_o/V_g (input) we find:

$$V^2 - VV_g - \frac{V_g D_1}{K} = 0$$

Use quadratic formula:

$$\frac{V}{V_g} = \frac{1 \pm \sqrt{1 + 4D_1^2 / K}}{2}$$


Note that one root leads to positive V , while other leads to negative V . Select positive root:

$$\frac{V}{V_g} = M(D_1, K) = \frac{1 + \sqrt{1 + 4D_1^2 / K}}{2}$$

where $K = 2L / RT_s$
 valid for $K < K_{crit}(D)$

Transistor duty cycle $D =$ interval 1 duty cycle D_1

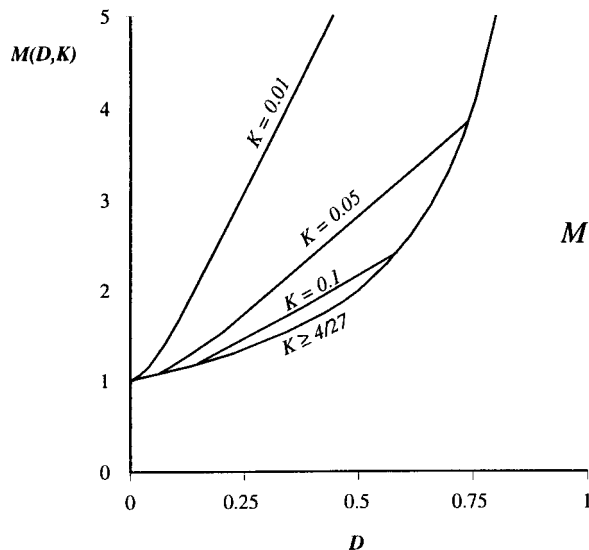This comparative plot again shows the DCM DC transfer



$$M = \begin{cases} \frac{1}{1-D} & \text{for } K > K_{crit} \\ \frac{1 + \sqrt{1 + 4D^2 / K}}{2} & \text{for } K < K_{crit} \end{cases}$$

Approximate M in DCM:


$$M \approx \frac{1}{2} + \frac{D}{\sqrt{K}}$$

function lying above the CCM values for all D .

4. V_o Buck-Boost DCM Operation

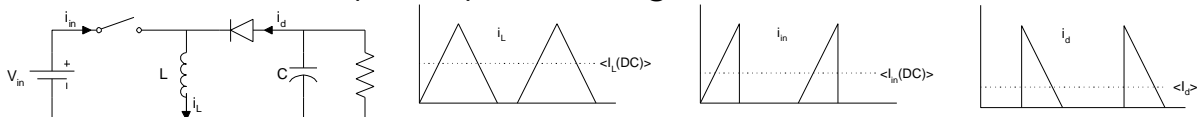a. General

We skip to the current waveforms i_L (inductor) on the right, i_{in} in the middle and i_d (diode) on the right hand side.



$$v_L = D_1(V_{in}) + D_2(V_{out}), \quad D_1 V_{in} = -D_2 V_{out}$$

$$i_L(DC) = i_{in}(DC) + i_{out}(DC)$$

b. Derive the DCM DC Transfer Function
 Since D_1 is known and V_{in} is constant the peak inductor current when the Tr is on is:

$$i_L(\text{peak}) = \frac{D_1 T_s V_{in}}{L}$$

From the sawtooth $i_{in}(t)$ waveform:

$$I_{in}(\text{av}) = \frac{D_1}{2} i_L(\text{peak}) = \frac{V_{in} D_1^2 T_s}{2L}$$

$$P_{in}(\text{av}) = V_{in}(\text{const}) I_{in}(\text{av}) = \frac{V_{in}^2 D_1^2 T_s}{2L} = P_{out} = V_o^2 / R$$

Solving for V_{out} directly:

$$V_o(\text{Buck-Boost DCM}) = -D_1 V_{in} \sqrt{\frac{RT_s}{2L}}$$

c. Alternative derivation

For HW# 2 YOU Derive the buck-boost transfer function using the proper balance equations

DCM operation occurs for small L , $L < L_c$ (critical), i_L goes to zero before the end of the cycle and when the Tr goes on i_L always starts from zero. That is the ratio RT_s/L has to be below a critical level to avoid DCM and remain in CCM operation.


5. A summary would include:

Table 5.2. Summary of CCM-DCM characteristics for the buck, boost, and buck-boost converters

Converter	$K_{crit}(D)$	DCM $M(D,K)$	DCM $D_2(D,K)$	CCM $M(D)$
Buck	$(1 - D)$	$\frac{2}{1 + \sqrt{1 + 4K/D^2}}$	$\frac{K}{D} M(D,K)$	D
Boost	$D(1 - D)^2$	$\frac{1 + \sqrt{1 + 4D^2/K}}{2}$	$\frac{K}{D} M(D,K)$	$\frac{1}{1 - D}$
Buck-boost	$(1 - D)^2$	$-\frac{D}{\sqrt{K}}$	\sqrt{K}	$-\frac{D}{1 - D}$

with $K = 2L / RT_s$. DCM occurs for $K < K_{crit}$.

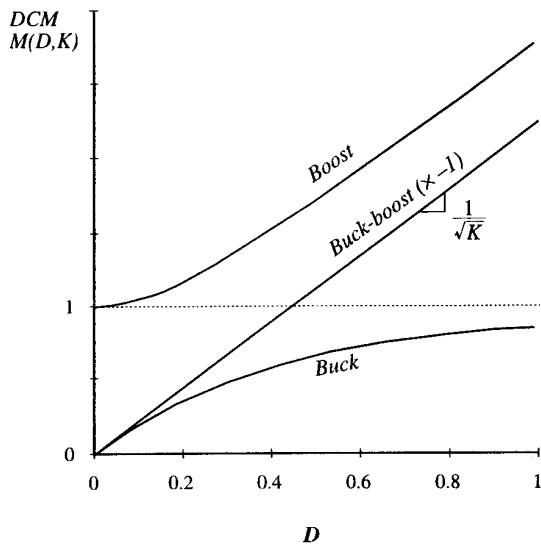This could also be plotted as shown below:



- DCM buck and boost characteristics are asymptotic to $M = 1$ and to the DCM buck-boost characteristic
- DCM buck-boost characteristic is linear
- CCM and DCM characteristics intersect at mode boundary. Actual M follows characteristic having larger magnitude
- DCM boost characteristic is nearly linear

Next we get expressions for L_c (critical) for each converter topology.

6. L_c (critical) for the Three Major Circuits

We expose the DCM / CCM boundary in terms of an L_c (critical). When $L = L_c$ the i_L waveform is always triangular within T_s , so that $D_1 + D_2 = 1$. At this value of L we can also use the DCM expressions for V_o . Setting the two V_o expressions equal sets L_c .


a. Buck critical L

For $V_o = D_1 V_{in}$ (at DCM-CCM boundary)

$$\frac{V_{in}^2 D_1}{R} = \frac{D_1^2 T_s}{2L_c} [V_{in}^2 - D_1 V_{in}^2]$$

$$L_c = \frac{RT_s}{2} (1 - D_1)$$

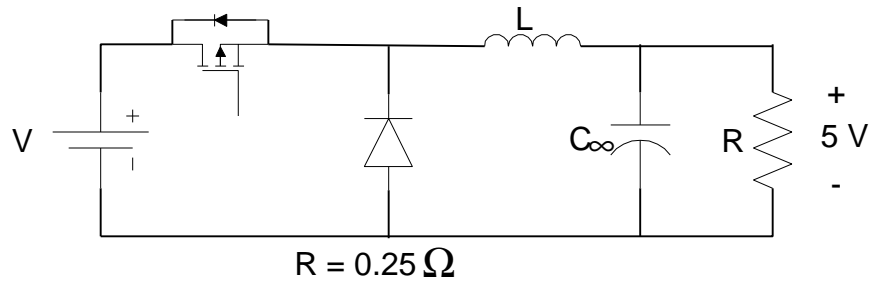The buck circuit below provides 100W at 5V with a 48V input.



What is L_c ? At the DCM-CCM boundary using $V_{out} = D_1 V_{in}$ yields $D_1 = 5/48$ and $D_2 = 43/48$. $P_{av} = 100$ implies $I_{out(av)} = 20A$ and $\Delta i_L(\text{peak}) = 2I_{av} = 40A$.

$$e = L_c di/dt \text{ where } dt = D_1 10\mu s$$

$$43 = L_c * 40 / (5 * 50 / 48) \text{ or } L_c = 1.1 \mu H$$

For $L < L_c$ DCM operation for $L > L_c$ CCM operation.


b. Boost critical L

For $V_o = V_{in} / (1 - D_1)$ (at DCM-CCM boundary)

$$\frac{V_{in}^2}{(1 - D_1)^2} = \frac{V_{in}^2 D_1^2 T_s R}{2L_c} + \frac{V_{in}^2}{1 - D_1}$$

$$L_c = \frac{D_1 R T_s}{2} (1 - D_1)^2$$

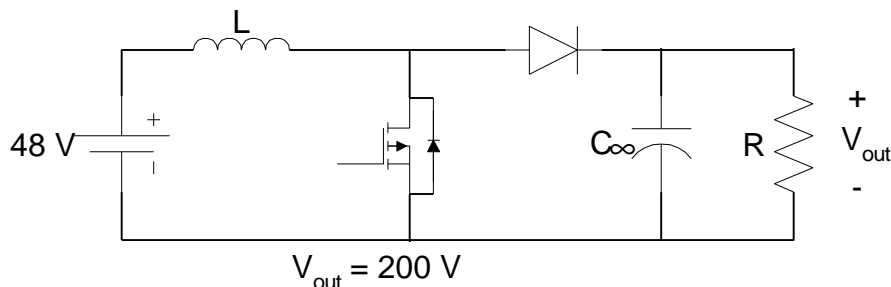In the boost circuit below $V_{in} = 48V$, $V_o = 200V$, $L = 15 \mu H$ and $f_{sw} = 50 \text{ kHz}$ ($T_s = 20 \mu s$)



What is load $P(\text{min})$ so that $L \geq L_c$? At the DCM / CCM boundary using $V_{out} = V_{in} / (1 - D_1)$ yields $D_1 = 0.76$ and $D_2 = 0.24$. When the Tr is on V_L is 48V for a time $dt = 0.76 * 20 \mu s$.

$$V_L = L di/dt$$

The di range during this time is $2I_L(av) = 2I_{in}(av)$

$$2I_L(av) = di > 48 \cdot 0.76 \cdot 20 / 15 \mu s = 48.64$$

The load power must be at least $48 \cdot 48.6 / 2 = 1167 \text{ W}$.

c. Buck-Boost critical L_c


For $V_o = D_1 V_{in} / (1 - D_1)$ (at DCM-CCM boundary)

Likewise from the DCM relations

$$V_{out}^2 = \frac{V_{in}^2 D_1^2 R T_s}{2L_c} = \frac{V_{in}^2 D_1^2}{(1 - D_1)^2}$$

$$L_c = \frac{R T_s}{2} (1 - D_1)^2$$

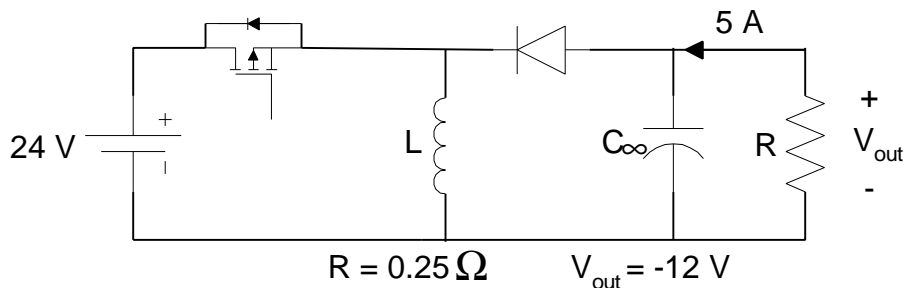The buck-boost circuit below has $V_{in} = 24\text{V}$, $V_o = -12\text{V}$ and provides 60 W on average.



Find L_c vs. f_{sw} . $I_{out}(av) = 60/12 = 5\text{A}$. For $V_{in} = 24\text{V}$ $I_{in}(av) = 25\text{A}$. Now $I_L = I_o + I_D = 7.5\text{A}$ provided we are in CCM and

$L > L_c$. Then i_L is a triangle wave from 0 to 2. $I_{av} = 15\text{A}$ over the time $D_1 T_s$. Again $V_o = V_{in} D_1 / (1 - D_1)$ yields $D_1 = 1/3$.


$$V_L = L di/dt = L \cdot dI_{av} / D_1 T_s$$

$$24 = L_c \cdot 15 / (1/3)(f_{sw})$$

$$L_c = 8 T_s / 15 = 8 / (15) f_{sw} \text{ (}\mu\text{H)}$$

$L_c(1\text{kHz}) = 533 \mu\text{H}$ but $L_c(1\text{MHz}) = 0.5 \mu\text{H}$. Clearly higher f_{sw} is desired to make L_c as small as possible.

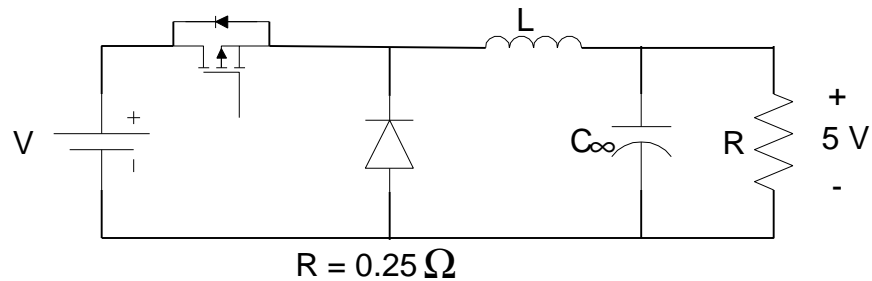
For **HW#2** use the buck converter shown below:



A buck converter is designed for nominal 48 V input and 5 V output. It switches at 100 KHz. In practice the input can be anywhere between 30 V and 60 V. the load power ranges between 10 W and 200 W. What is L_{crit} for this converter? Conversely, what is the maximum inductance that will ensure discontinuous mode under all allowed conditions?

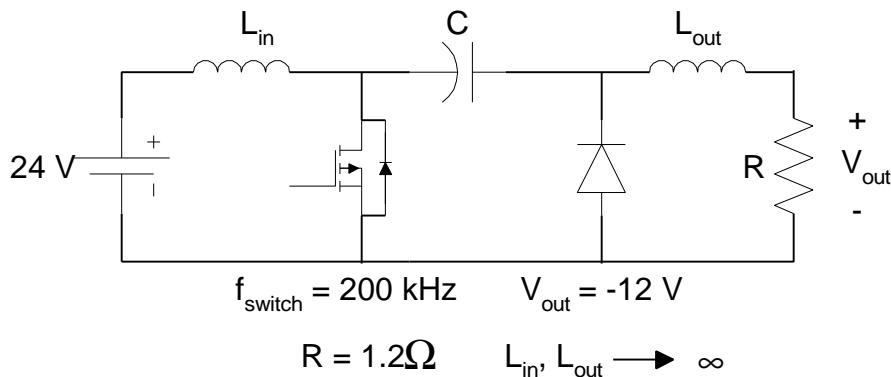5. Critical Capacitance C_c (critical)

$C_{CRITICAL}$ is the capacitance required to keep $V_c > 0$ for all circuit conditions. The Cuk circuit shown below has $V_{in} = 24V$, $V_o = -12$, $f_{sw} = 200$ kHz and provides 120 W.



What is C_c (critical)?

$I_o(av) = 120/12 = 10A$, $R_L = 1.2\Omega$, $D_1 = 1/3$ and $I_{in}(av) = 120/24 = 5A$. At the CCM / DCM boundary the boost portion provides a voltage on average across the capacitor $V_{in}/(1-D_1) = 36V$ which is the sum of the input and output (12+24).

For C_c the V_c will vary from 0 to $2V_c(av) = 72V$ while the transistor is on for

$$D_1 T_s = (1/3)5 \mu s.$$

$$i_c = C_c * dV/dt = [C_c * 2V_c(av)] / [(1/3)*5] = C_c * 72 * (3) / 5$$

$$C_c = 0.23 \mu F$$

At C_c we get $V_o = -12$ for $V_{in} = 24V$. Will this V_o increase / decrease as $C < C_c$? What if $C = C_c/2 = 0.116 \mu F$?

Since we have DCM V_c will ramp down to zero while the Tr is on. When V_c goes negative the diode goes on while the Tr is on. This causes $D_1 + D_2 > 1$. While the diode is on for a time

$\Delta t(1-D_1)T_s = 3.33 \mu s$. The voltage varies from 0 to $2(V_{in} + V_{out})$.

$$I_c = I_{in} = P_{in} / V_{in} = C\Delta V/\Delta t$$

$$1. (P_{in}/V_{in}) = C_c * 2(V_{in} + V_{out})/3.33\mu s$$

$$2. P_{in} = P_{out} = V_o^2/R$$

Combining 1. and 2. we obtain DCM:

$$V_o^2 - 2V_o - 48 = 0$$

$$V_{out} = 8V$$

$$P_{out} = V_o^2/1.6 = 53.33 W$$

$$I_{in} = 2.2A$$


Hence V_o drops for $C < C_c$

C. Homework Solutions and Hints

1. Problem 5.1

Erickson Problem 5.1: Buck-boost is given on pages 14-16

②

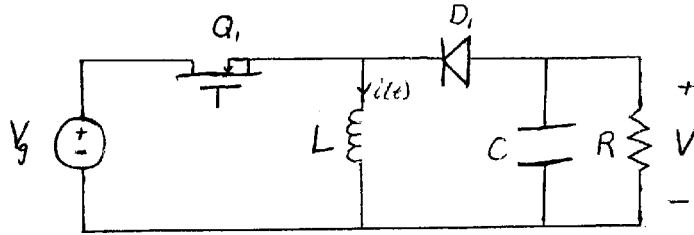

(a) From prob. 2.1:

$$V = \frac{D}{D'} V_g; I = \frac{D V_g}{(D')^2 R}; \Delta i = \frac{D T_s V_g}{2L}$$

Knowing For CCM: $I > \Delta i$
DCM: $I < \Delta i$


We want DCM thus $\underline{I < \Delta i}$ or $\frac{D V_g}{(D')^2 R} < \frac{D T_s V_g}{2L}$ ①

Relating $K < K_{crit}(D)$ we solve for k and $K_{crit}(D)$

From ① simplified $\Rightarrow (D')^2 > \frac{2L}{R T_s}$ or $\frac{2L}{R T_s} < (D')^2$

$K = \frac{2L}{R T_s}$ and $K_{crit} = (D')^2$


(b) Find $\frac{V}{V_g}$ for DCM:

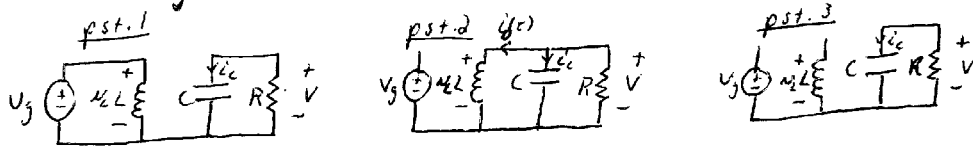

$\langle v_L \rangle = D_1(V_g) + D_2(V) + D_3(0) = 0$ rearranging $\Rightarrow V = \frac{-D_1 V_g}{D_2}$ ①

$\langle i_C \rangle = C \frac{V}{R} = 0$ or $\langle i_D \rangle = -\frac{V}{R}$

No dc current through "C".

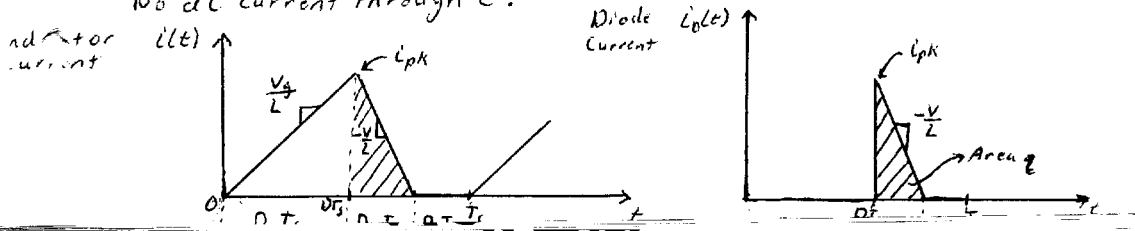

AND: $\langle i_o \rangle = \frac{1}{T_s} \int_0^{T_s} i_o(t) dt = \frac{\text{Area } q}{T_s} = \frac{V_g D_1 D_2 T_s}{2L}$

$i_{pk} = \left(\frac{V_g}{L}\right)(D_1 T_s)$ thus: $\langle i_o \rangle = \frac{(1)V_g D_1 D_2 T_s}{2L} = \frac{V_g D_1 D_2 T_s}{2L}$



relating $\langle i_o \rangle$ from earlier $\Rightarrow \langle i_o \rangle = \frac{V_g D_1 D_2 T_s}{2L} = \frac{-V}{R}$

Knowing from (b) $V = \frac{-D_1}{D_2} V_g$: $\frac{V_g D_1 D_2 T_s}{2L} = \frac{V_g D_1}{D_2 R}$ or $D_2 = \sqrt{\frac{2L}{RT_s}} = \sqrt{K}$

$M = \frac{V}{V_g} = \frac{-D_1}{D_2} = \frac{-D_1}{\sqrt{K}}$

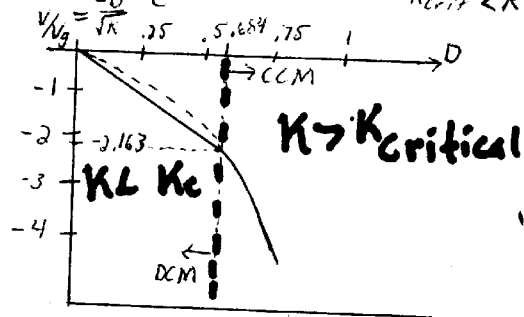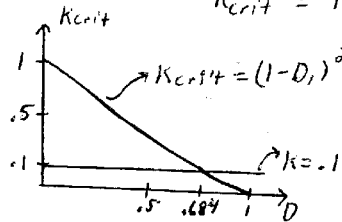(c) $K = 0.1$, plot V/V_g over $0 \leq D \leq 1$



From (b) $(D_2)^2 = K$ or $(1-D_1)^2 = K$; $D_1 \approx .684$ $\begin{cases} D < .684 & \text{DCM } K_{crit} > K \\ D > .684 & \text{CCM } K_{crit} < K \end{cases}$



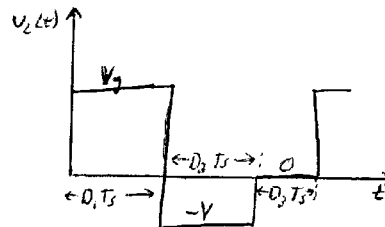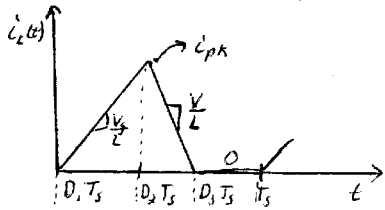(d) $K = 1$, $D_1 = .3$ knowing $D_2 = \sqrt{K} = .316$ and $D_3 = 1 - D_1 - D_2 = .384$

All three time periods known

$i_{pk} = \frac{V_g D_1 T_s}{L} \Rightarrow \frac{V}{V_g} = \frac{-D_1}{\sqrt{K}} \approx .95$




(e) $R \rightarrow \infty$; $K = \frac{2L}{RT_s} \rightarrow 0$ $K < K_{crit}$ DCM. $M = \frac{V}{V_g} = \frac{-D_1}{\sqrt{K}} \rightarrow -\infty$ For $D_1 > 0$

V tends toward $-\infty$. Since V becomes very large it probably exceeds the transistor and Diode ratings. To avoid this a minimum load can be used to prevent $R \rightarrow \infty$ or a control network to reduce D to 0 when V becomes too large.


2. Erickson Problem 5.9

EMI Noise Issues from Converters to Mains: Example of Input Filter PWM dc-dc buck converter


Erickson Problem. 5.9

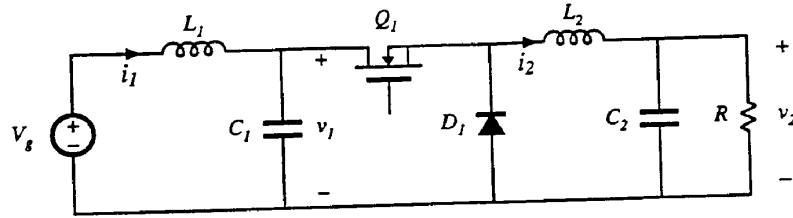

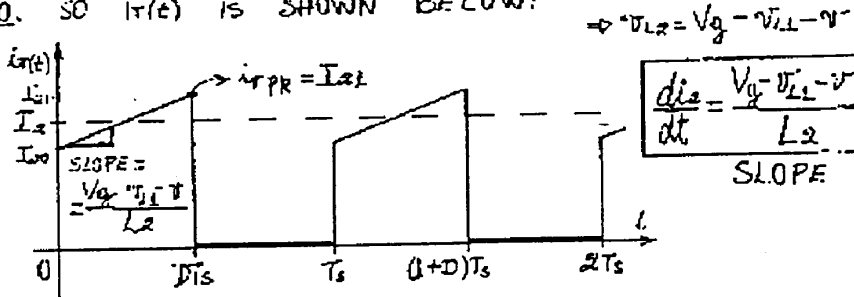a) WHEN THE TRANSISTOR Q_1 IS ON (DI OFF), THE TRANSISTOR CURRENT $i_1(t)$ IS EQUAL TO $i_2(t)$. THIS CURRENT $i_2(t)$ INCREASES LINEARLY AS WELL AS $i_1(t)$. WHEN Q_1 IS OFF (DI ON), THE TRANSISTOR CURRENT IS ZERO. SO $i_1(t)$ IS SHOWN BELOW:



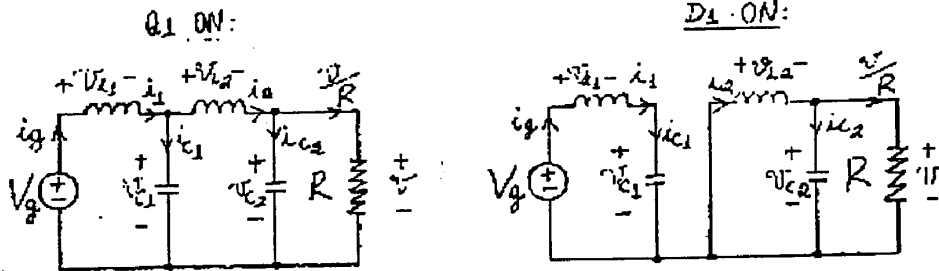b) LET'S MAKE INDUCTOR VOLT-SECOND BALANCE & CAPACITOR CHARGE BALANCE ON THE CIRCUIT OF FIG. 2.32:



$\Rightarrow L_1$ VOLT-SEC BALANCE: (Obs: SRA \Rightarrow SMALL RIPPLE APPROXIMATION)

$$\frac{\Delta I_1}{T_s} = 0 = D(V_g - v_{C1}) + D'(V_g - v_{C1}) = 0 \Rightarrow \boxed{v_{C1} = V_g} \quad (1) \Rightarrow \text{SRA IS NOT USEFUL!}$$

NO SRA!

$\Rightarrow L_2$ VOLT-SEC BALANCE:

$$\frac{\Delta I_2}{T_s} = 0 = D(v_{C1} - v) + D'(-v) = 0 \Rightarrow \boxed{v = D v_{C1}} \quad (2) \text{ USE SRA!}$$

WITH (1) $\Rightarrow \boxed{v = D V_g}$

⇒ C1 CHARGE BALANCE:

$$\frac{Q_{C1}}{T_s} = 0 = D(I_1 - I_2) + D'(I_1) = 0 \Rightarrow \boxed{I_1 = DI_2} \quad \textcircled{3} \text{ USE SRA!}$$

WITH $\textcircled{4}$ & $\textcircled{2} \Rightarrow \boxed{I_1 = D \frac{V}{R}} \neq \boxed{I_1 = D^2 \frac{V_g}{R}}$

⇒ C2 CHARGE BALANCE:

$$\frac{Q_{C2}}{T_s} = 0 = D \left(I_2 - \frac{V}{R} \right) + D' \left(I_2 - \frac{V}{R} \right) = 0 \Rightarrow \boxed{I_2 = \frac{V}{R}} \quad \textcircled{1} \Rightarrow \text{AVOID SRA!}$$


NO SRA!

Summary of V_1 versus time

$$V_1 = V_g, \quad V = DV_g, \quad I_1 = \frac{DV}{R} = \frac{D^2 V_g}{R}, \quad I_2 = \frac{V}{R}$$

$$\Delta v_{C1} = \left(\frac{I_1 - I_2}{C_1} \right) (D' T_s)$$
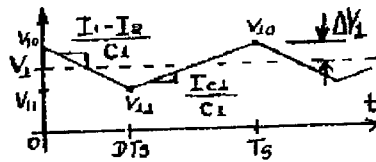
$$\Delta v_{C2} = \frac{V_g D' D' T_s}{2RC_2}$$



Now conditions @ V_1 for DCM as well as ΔI_1 , ΔI_2 and ΔV_2

1) LET'S EVALUATE THE RIPPLE FOR: L_1, L_2, C_1 & C_2 :


⇒ $L_1 \Rightarrow$ NO SRA $\Rightarrow \boxed{\Delta i_{L1} = \frac{\Delta v_{C1} \cdot T_s}{8L_1}} \quad \textcircled{5} \Rightarrow$ DUAL FOR EB. (2-60).

⇒ $L_2 \Rightarrow$ USE SRA $\Rightarrow \Delta v_{C2} = \left(\frac{V_g - V}{L_2} \right) (DT_s) \Rightarrow \boxed{\Delta i_{L2} = \frac{(V_g - V) DT_s}{2L_2}} \quad \textcircled{6}$

⇒ $C_1 \Rightarrow$ USE SRA $\Rightarrow \Delta v_{C1} = \left(\frac{I_1}{C_1} \right) (D' T_s) \Rightarrow \boxed{\Delta v_{C1} = \frac{V D (1-D) T_s}{2C_1}} \quad \textcircled{7}$


⇒ $C_2 \Rightarrow$ NO SRA $\Rightarrow \Delta v_{C2} = \Delta v = \frac{\Delta i_{L2} \cdot T_s}{8C_2} \quad \textcircled{8} \Rightarrow$ FA. (2-60), P. 32.

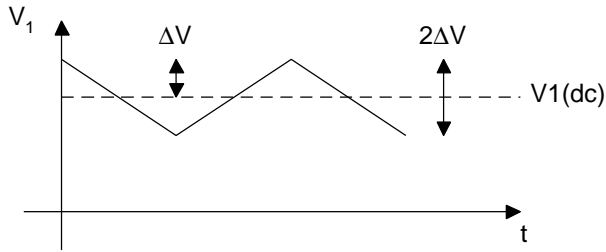Now determine when the DCM occurs by plotting $v_1(t)$ with DC value and ripple



$$V_1(\text{dc}) \quad K = \frac{2RC_1}{T_s}$$

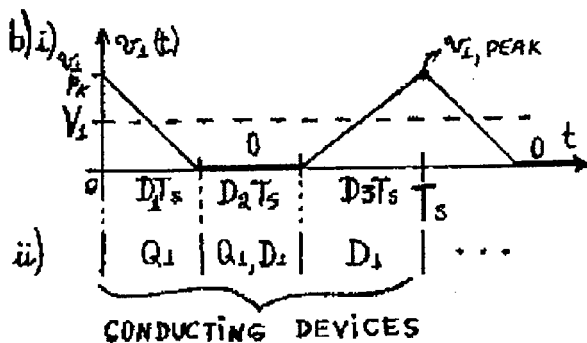Find Q_1 conducts but when V_1 tries or goes negative diode conducts. $K(\text{critical}) = D^2 D'$.



iii) FOR DCM $\Rightarrow \Delta v_L > V_L$, OR: ^{FOR THE CAPACITOR C_L}



$$\frac{D^2 V_g D' T_s}{2RC_1} > V_g \Rightarrow \text{DEFINE } K = \frac{2RC_1}{T_s} \Rightarrow$$

$$\Rightarrow K < D^2 D' \quad \text{OR} \quad K < K_{\text{CRIT}} \Rightarrow \underline{K_{\text{CRIT}} = D^2 D'}$$

3. Hints for Erickson Problem 5.4
 Watkins Johnson Converter in CCM
 (See Erickson's Chapter 6 page 137 for the #6 topology and timing)

$D T_s$
 Q_1, Q_2 on
 D_2, D_2 off

$D' T_s$
 Q_1, Q_2 off
 D_1, D_2 on

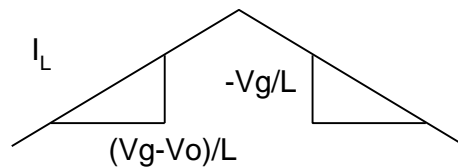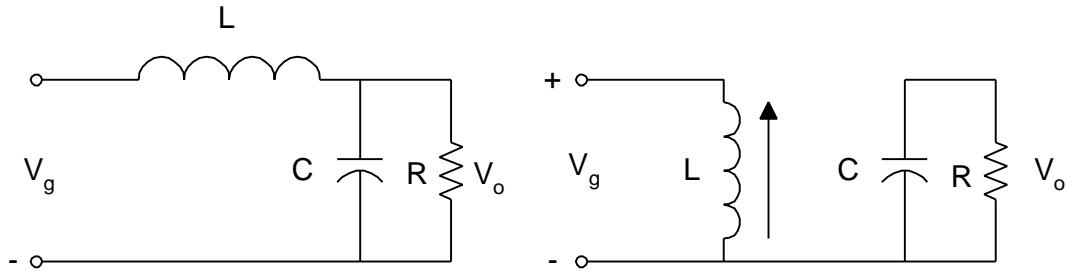


Note: Be careful when dividing by a negative number. If you divide by a negative number you must change the sign of the operator $\Rightarrow -5a < b$ or $a > -b/5$ but not $a < -b/5$, Try $a=1$ and $b=1$

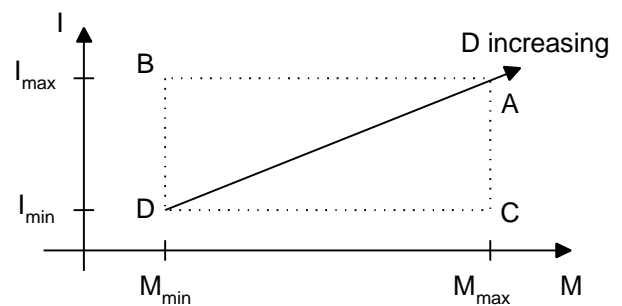4. Hints for Erickson Problem 5.14

DCM Boost

Draw a plot to find "worst case" DCM operation or nearly CCM. $D_3 = 0.1$ is minimum



Fill in the box for all cases of I vs. M .

Four Boundary Points

A. $V_g(\min)$, Maximum D values, M_{\max} , I_{\max} , k_{\max} , P_{\max}

I_{\max} & Max D \Rightarrow worst case
 $D_3 = 0.1$ is lowest \equiv Point A

B. $V_g(\max), M_{\min}, I_{\max}, k_{\max}, P_{\max}$
 Intermediate D values

C. $V_g(\min),$ Intermediate D, $M_{\max}, I_{\min}, k_{\min}, P_{\min}$

D. $V_g(\max), M_{\min}, I_{\min}, k_{\min}, P_{\min}, D_{\min}$

A is choice for boundary of CCM \leftrightarrow DCM
 and $D_3 = 0.1$ at A as per statement in problem $D_3(\min) = 0$.

From here use steady state DCM Boost equations

$$D_1 = f(k, M) = \sqrt{k(m-1)M}$$

$$D_2 = f(D_1, k) = ?? \quad \{\text{Lots of algebra}\}$$

Use D_1 above and: $k = \frac{2L}{RT_s}$

D_2 should be: $\sqrt{\frac{2LI}{V_g T_s (M-1)}}$

Show all work!

Set $D_3 = 0.1 = 1 - D_1 = D_2$

$$D_3 = 1 - M \left[\frac{2LI}{T_s V_g (M-1)} \right]^{1/2}$$

$$D_1 \text{ at point A} \equiv \sqrt{k_{\max}(M_{\max} - 1)M_{\max}}$$

\downarrow \downarrow
 Use equations on a spreadsheet

$$D_1 = \sqrt{\frac{2LI(M-1)}{T_s V_g}} \quad \text{and specs}$$

Gives L around 5μH

Output capacitor-

1. Use i_D vs. time to get Q
 $2\Delta v_c \approx Q/C \rightarrow$ Estimate C for $\Delta v = 2v$ or $\pm 1V$
2. Use $i_{\text{peak}} - I$ vs. time to get Q
 $2\Delta v_c = Q/C \rightarrow$ Estimate C for $\pm 1 V$ ripple.

The following is a list of equations used to derive the spreadsheet values. Where a, b, c, and d refer to points A, B, C, and D respectively.

$$T_s = \frac{1}{f_s} \quad I_{\min} = \frac{P_{\min}}{V} \quad I_{\max} = \frac{P_{\max}}{V} \quad R_{\min} = \frac{V}{I_{\max}} \quad R_{\max} = \frac{V}{I_{\min}}$$

$$M_{\max} = \frac{V}{V_{g\min}} \quad M_{\min} = \frac{V}{V_{g\max}} \quad L = \left(\frac{1 - D_3}{M_{\max}} \right)^2 \cdot T_s \cdot V_{g\min} \cdot \frac{M_{\max} - 1}{2 \cdot I_{\max}}$$

$$D_a = \sqrt{2 \cdot L \cdot I_{\max} \cdot \frac{M_{\max} - 1}{T_s \cdot V_{g\min}}} \quad D_b = \sqrt{2 \cdot L \cdot I_{\max} \cdot \frac{M_{\min} - 1}{T_s \cdot V_{g\max}}}$$

$$D_c = \sqrt{2 \cdot L \cdot I_{\min} \cdot \frac{M_{\max} - 1}{T_s \cdot V_{g\min}}} \quad D_d = \sqrt{2 \cdot L \cdot I_{\min} \cdot \frac{M_{\min} - 1}{T_s \cdot V_{g\max}}}$$

$$K_a = \frac{2 \cdot L \cdot I_{\max}}{T_s \cdot M_{\max} \cdot V_{g\min}} \quad K_b = \frac{2 \cdot L \cdot I_{\max}}{T_s \cdot M_{\min} \cdot V_{g\max}} \quad K_c = \frac{2 \cdot L \cdot I_{\min}}{T_s \cdot M_{\max} \cdot V_{g\min}} \quad K_d = \frac{2 \cdot L \cdot I_{\min}}{T_s \cdot M_{\min} \cdot V_{g\max}}$$

$$K_{rita} := D_a \cdot (1 - D_a)^2 \quad K_{ritb} := D_b \cdot (1 - D_b)^2 \quad K_{rite} := D_c \cdot (1 - D_c)^2 \quad K_{ritd} := D_d \cdot (1 - D_d)^2$$

$$ipka = \frac{V_{g\min} \cdot D_a \cdot T_s}{L} \quad ipkb = \frac{V_{g\max} \cdot D_b \cdot T_s}{L} \quad ipkc = \frac{V_{g\min} \cdot D_c \cdot T_s}{L} \quad ipkd = \frac{V_{g\max} \cdot D_d \cdot T_s}{L}$$

$$D_{2a} = \sqrt{\frac{2 \cdot L \cdot I_{\max}}{V_{g\min} \cdot T_s \cdot (M_{\max} - 1)}} \quad D_{2b} = \sqrt{\frac{2 \cdot L \cdot I_{\max}}{V_{g\max} \cdot T_s \cdot (M_{\min} - 1)}}$$

$$D_{2c} = \sqrt{\frac{2 \cdot L \cdot I_{\min}}{V_{g\min} \cdot T_s \cdot (M_{\max} - 1)}} \quad D_{2d} = \sqrt{\frac{2 \cdot L \cdot I_{\min}}{V_{g\max} \cdot T_s \cdot (M_{\min} - 1)}}$$

$$D_{3a} := 1 - D_a - D_{2a} \quad D_{3b} := 1 - D_b - D_{2b} \quad D_{3c} := 1 - D_c - D_{2c} \quad D_{3d} := 1 - D_d - D_{2d}$$

$$C := \frac{(ipka - I_{\max})^2 \cdot D_{2a} \cdot T_s}{4 \cdot ipka \cdot 1}$$