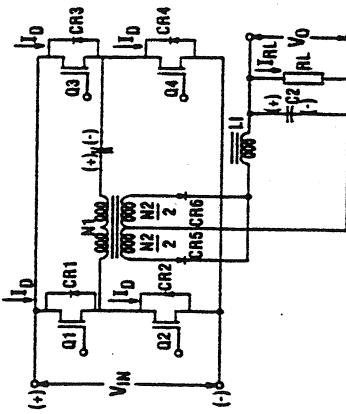


TYPE OF CONVERTER


CIRCUIT CONFIGURATION

DIODE VOLTAGES (VRM)

$$V_{RM} \begin{cases} V_{CR5} = 2V_{IN} \left(\frac{N_2}{N_1} \right) V_{CR1} = V_{IN} \\ V_{CR6} = 2V_{IN} \left(\frac{N_2}{N_1} \right) V_{CR2} = V_{IN} \end{cases}$$



VOLTAGE AND CURRENT WAVEFORMS

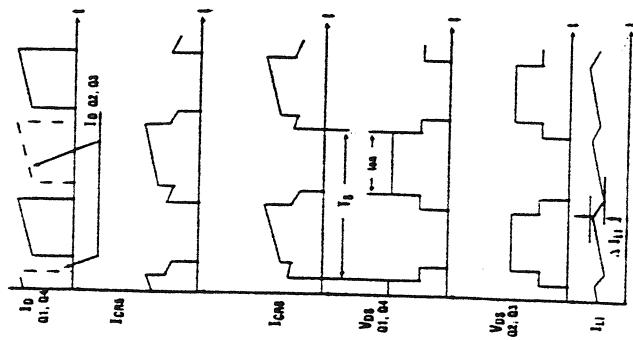

IDEAL TRANSFER FUNCTION

$$\frac{V_O}{V_{IN}} = 2 \frac{N_2}{N_1} \left(\frac{t_{on}}{T_S} \right) = 2 \frac{N_2}{N_1} (D)$$

PEAK DRAIN CURRENT

$$I_{DMAX} = \frac{N_2}{N_1} \left(I_{RL} + \frac{\Delta I_L}{2} \right) + \hat{I}_{MAG}$$

(\hat{I}_{MAG} = peak magnetizing current.)

PEAK DRAIN VOLTAGE

$$V_{DS} = V_{IN}$$

AVERAGE DIODE CURRENTS

$$I_{CR5} = I_{RL}$$

$$I_{CR6} = I_{RL}$$

ADVANTAGES

Good transformer utilization, transistors rated at V_{IN} , isolation, multiple outputs. ID is reduced as a ratio of N_2/N_1 . Zero voltage switching possible. Low output ripple.

DISADVANTAGES

High parts count. C1 has high ripple current. Requires high side switch drive. Cross conduction of Q1 and Q2 or Q3 and Q4 possible. High input current ripple.

TYPICAL APPLICATIONS

High power, high input voltage.


APPLICABLE HARRIS PRODUCTS

HIP4080/81, HIP2500, HV400


TYPE OF CONVERTER

CIRCUIT CONFIGURATION

Half Bridge

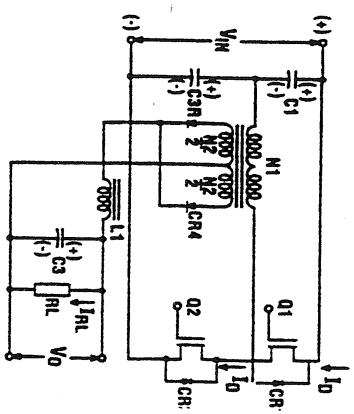

VOLTAGE AND CURRENT WAVEFORMS

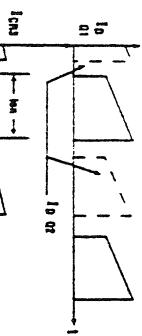

$$V_{RM} \left\{ \begin{array}{l} V_{CR3} = V_{IN} \left(\frac{N_2}{N_1} \right) \\ V_{CR4} = V_{IN} \left(\frac{N_2}{N_1} \right) \end{array} \right.$$

IDEAL TRANSFER FUNCTION

$$\frac{V_o}{V_{IN}} = \frac{N_2}{N_1} \left(\frac{t_{on}}{T_s} \right) = \frac{N_2}{N_1} (D)$$

$$\text{IDEAL TRANSFER FUNCTION}$$

$$I_{DMAX} = \frac{N_2}{N_1} \left(I_{RL} + \frac{\Delta I_L}{2} \right) + \hat{I}_M$$

(\hat{I}_{MAG} = Peak magnetizing current.)

PEAK DRAIN VOLTAGE

$$V_{DS} = V_{IN}$$

AVERAGE DIODE CURRENTS

$$ICR3 = \frac{I_{RL}}{2}$$

ADVANTAGES

DISADVANTAGES

Good transformer utilization. Transistors rated at V_{IN} . Isolation, multiple outputs, ID reduced as a ratio of N_2/N_1 . High power output. Zero voltage switching possible, near $D = 1$. Low output ripple.

Poor transient response, high parts count, C_1 and C_2 have high ripple current. Requires high side switch drive. Cross conduction of Q1 and Q2 possible. High input current ripple.

TYPICAL APPLICATIONS

High input voltage, moderate-to-high power.


APPLICABLE HARRIS PRODUCTS

HIP2500, HIP5500, HV400

TYPE OF CONVERTER


DIODE VOLTAGES (VRM)

$$V_{CR1,PK} = V_{CR2,PK} = V_{IN}$$

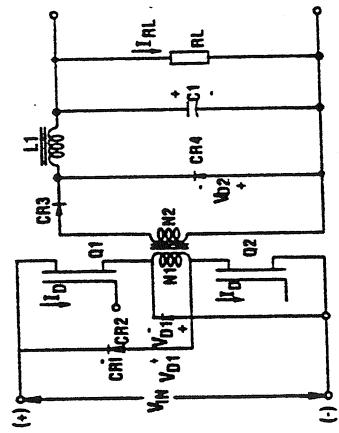

CIRCUIT CONFIGURATION

VOLTAGE AND CURRENT WAVEFORMS

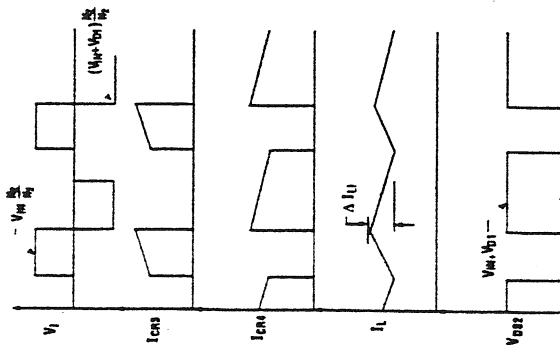

IDEAL TRANSFER FUNCTION

$$\frac{V_0}{V_{IN}} = \frac{N_2}{N_1} \left(\frac{t_{on}}{T_S} \right) = \frac{N_2}{N_1} (D)$$

PEAK DRAIN CURRENT

$$I_{MAX} = \frac{N_2}{N_1} \left(I_{RL} + \frac{\Delta I_L}{2} \right) + \hat{I}_{MAG}$$

(\hat{I}_{MAG} = peak magnetizing current.)

PEAK DRAIN VOLTAGE

$$(Q_1 \text{ or } Q_2) \quad V_{DS} = V_{IN} + V_{D1}$$

AVERAGE DIODE CURRENTS

$$I_{CR3,AVE} = I_{RL,D}$$

$$I_{CR4,AVE} = I_{RL}(1-D)$$

ADVANTAGES

Drain currents reduced by turns ratio. Lossless snubber recovers energy. Drain voltage 1/2 that of conventional forward converter. Low output ripple.

DISADVANTAGES

Poor transformer utilization, high parts count, high-side switch drive required. Transformer reset limits duty ratio. High input current ripple.

TYPICAL APPLICATIONS

High input voltage, moderate power. Supports multiple outputs.


APPLICABLE HARRIS PRODUCTS

HIP2500, HV400


TYPE OF CONVERTER

Push-Pull

CIRCUIT CONFIGURATION

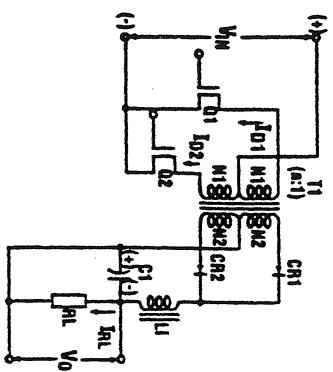

VOLTAGE AND CURRENT WAVEFORMS

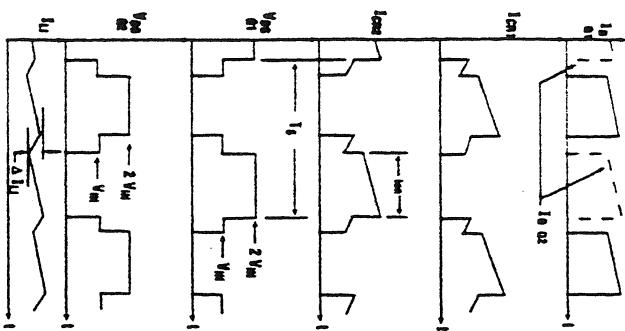

IDEAL TRANSFER FUNCTION

$$\frac{V_0}{V_{IN}} = 2 \frac{N_2}{N_1} \left(\frac{t_{on}}{T_S} \right) = 2 \frac{N_2}{N_1} (D)$$

PEAK DRAIN CURRENT FUNCTION

$$I_{DMAX} = \frac{N_2}{N_1} \left(I_{RL} + \frac{\Delta I_{L1}}{2} \right) + \hat{I}_{MAG}$$

(\hat{I}_{MAG} = peak magnetizing current.)

$$V_{DS} = 2 V_{IN}$$

PEAK DRAIN VOLTAGE

AVERAGE DIODE CURRENTS

$$I_{CR1} = \frac{I_{RL}}{2}$$

$$I_{CR2} = \frac{I_{RL}}{2}$$

ADVANTAGES

Good transformer utilization. Drain current reduced as a function of N_2/N_1 . Good at low values of V_{IN} . Low output ripple.

DISADVANTAGES

Cross conduction of Q1 and Q2 possible, high parts count. Transformer design critical. High voltage required for Q1 and Q2. High input current ripple.

DIODE VOLTAGES (VRM)

$$VRM \left\{ \begin{array}{l} V_{CR1} = 2V_{IN} \left(\frac{N_2}{N_1} \right) \\ V_{CR2} = 2V_{IN} \left(\frac{N_2}{N_1} \right) \end{array} \right.$$

TYPICAL APPLICATIONS


Low input voltage.

APPLICABLE PRODUCTS

HIP5062, HIP5061

DIODE VOLTAGES (VRM)

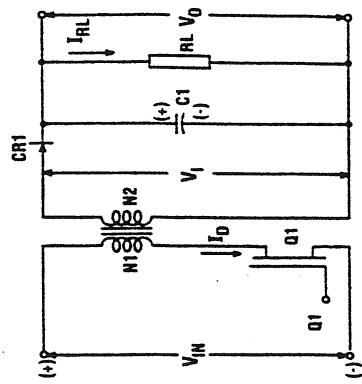
$$V_{RM} = V_{IN} \left(\frac{N_2}{N_1} \right)$$



TYPE OF CONVERTER

CIRCUIT CONFIGURATION

VOLTAGE AND CURRENT WAVEFORMS

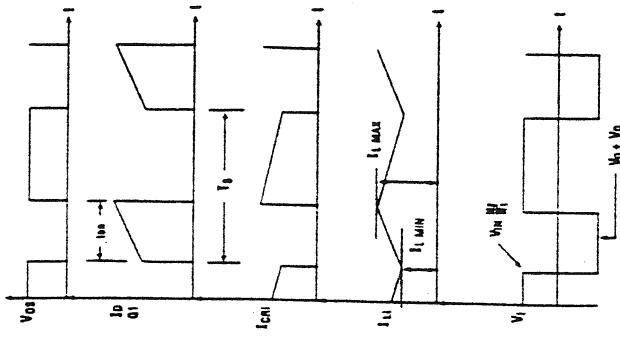

$$\frac{V_O}{V_{IN}} = \frac{N_2}{N_1} \left(\frac{t_{on}}{T_S - t_{on}} \right) = \frac{N_2}{N_1} \left(\frac{D}{1-D} \right)$$

IDEAL TRANSFER FUNCTION

PEAK DRAIN CURRENT

$$I_{DMAX} = I_{RL} \left(\frac{N_2}{N_1} \right) \left(\frac{1}{1-D} \right) + \frac{\Delta I_L}{2}$$

PEAK DRAIN VOLTAGE

$$V_{DS} = V_{IN} + \left(\frac{N_1}{N_2} \right) (V_{OUT} + V_{D})$$

AVERAGE DIODE CURRENTS

$$I_{CR1} = I_{RL}$$

Drain current reduced by turns ratio of transformer
Low parts count. Isolation. Has no secondary
output inductors.

ADVANTAGES

DISADVANTAGES

Poor transformer utilization. Transformer size
energy. High output ripple. CR1 needs fast recovery.

TYPICAL APPLICATIONS

Low output power. Supports multiple outputs

APPLICABLE HARRIS PRODUCTS

HIP5061, ICL7667, HV400


TYPE OF CONVERTER

CIRCUIT CONFIGURATION

Forward


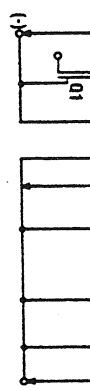
$$\left. \begin{array}{l} V_{CR1} = V_{IN} \left(1 + \frac{N_3}{N_1} \right) \\ V_{CR2} = V_{IN} \left(\frac{N_2}{N_3} \right) \\ V_{CR3} = V_{IN} \left(\frac{N_2}{N_1} \right) \end{array} \right\}$$



VOLTAGE AND CURRENT WAVEFORMS

IDEAL TRANSFER FUNCTION

$$\frac{V_o}{V_{IN}} = \frac{N_2}{N_1} \left(\frac{t_{on}}{T_S} \right) = \frac{N_2}{N_1} = (D)$$

$$I_{DMAX} = \frac{N_2}{N_1} \left(I_{RL} + \frac{\Delta I_L}{2} \right) + \hat{I}_{MAG}$$

(\hat{I}_{MAG} = peak magnetizing current.)

PEAK DRAIN VOLTAGE


$$V_{DS} = V_{IN} \left(1 + \frac{N_1}{N_3} \right)$$

AVERAGE DIODE CURRENTS

$$I_{CR1} = \frac{\hat{I}_{MAG}}{2} (D)$$

$$I_{CR2} = I_{RL} (D)$$

$$I_{CR3} = I_{RL} (1-D)$$

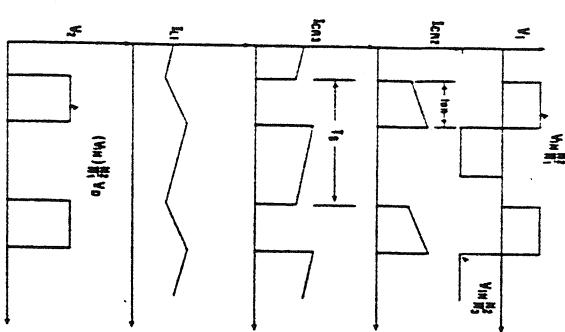

ADVANTAGES

Drain current reduced by ratio of N_2/N_1 . Low output ripple.

DISADVANTAGES

Poor transformer utilization. Poor transient response. Transformer design is critical. Transformer reset limits duty ratio. High voltage required for Q1. High input current ripple.

TYPICAL APPLICATIONS

Low-to-moderate output power. Supports multiple outputs.

APPLICABLE SEMICONDUCTORS


HIP5061, ICL7667, HV400

TYPE OF CONVERTER

CUK (Step Up/Down)


DIODE VOLTAGES (VRM)

$$V_{RM} = V_0 + V_{IN}$$

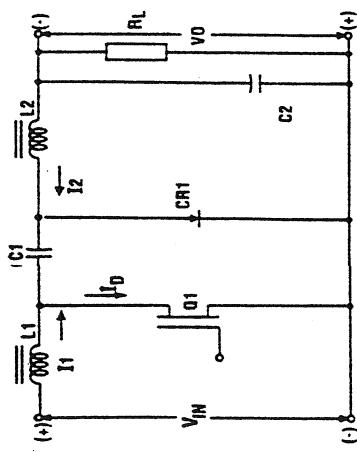

CIRCUIT CONFIGURATION

VOLTAGE AND CURRENT WAVEFORMS

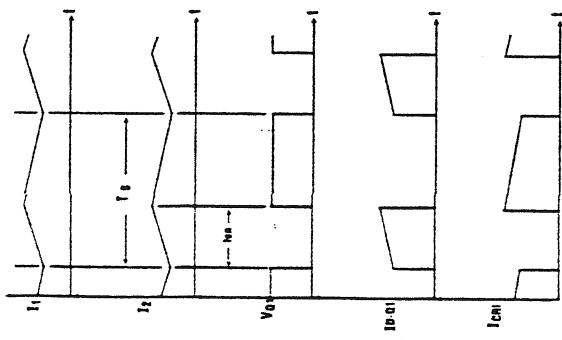

IDEAL TRANSFER FUNCTION

$$\frac{V_0}{V_{IN}} = -\left(\frac{t_{on}}{T_S - t_{on}}\right) = -\left(\frac{D}{1-D}\right)$$

PEAK DRAIN CURRENT

$$I_{MAX} = I_1 + I_2 = I_1 \left(\frac{1}{D}\right)$$

PEAK DRAIN VOLTAGE

$$V_{DS} = 2 V_{IN}$$

AVERAGE DIODE CURRENTS

$$I_{CR1} = I_1 + I_2$$

$$I_1 + I_2 = I_1 \left(\frac{1}{D}\right)$$

ADVANTAGES

Simple, low ripple input and output current, capacitive isolation protects against switch failure.

DISADVANTAGES

High drain current, C1 has high ripple current requirement (low ESR), High voltage required for Q1. Voltage inversion.

TYPICAL APPLICATIONS

Low noise, inverse output voltages.

APPLICABLE HARRIS PRODUCTS

HIP5060, HIP5061, HIP5062, HIP5063


TYPE OF CONVERTER

SEPIC (Step Down/Up)


DIODE VOLTAGES (VRM)

$$V_{RM} = V_0 + V_{IN}$$

CIRCUIT CONFIGURATION

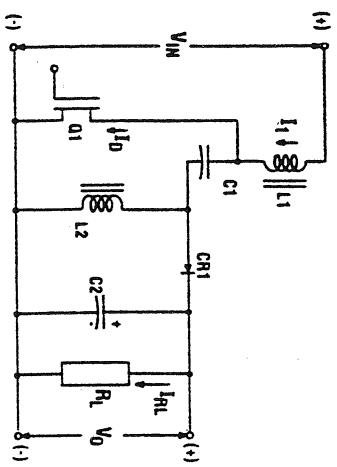

VOLTAGE AND CURRENT WAVEFORMS

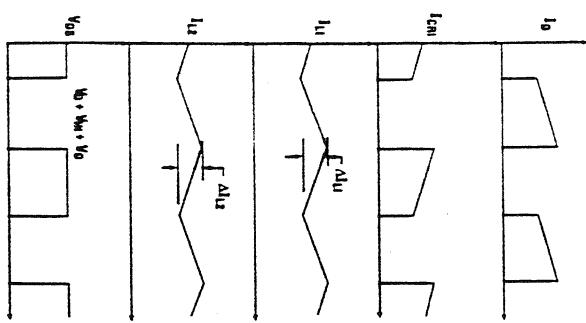

IDEAL TRANSFER FUNCTION

$$\frac{V_0}{V_I} = \frac{D}{1-D}$$

$$IDMAX = I_1 + I_{RL} + \frac{\Delta I_{L1} + \Delta I_{L2}}{2}$$

PEAK DRAIN CURRENT

$$V_{DS} = V_0 + V_{IN} + V_D$$

AVERAGE DIODE CURRENTS

$$ICR1 = I_{RL}$$

ADVANTAGES

No isolation between input and output. Switch has high peak and rms currents which limit output power. C1 and C2 have high ripple current requirements (low ESR), continuous current mode makes loop stabilization difficult, potential instabilities with circuit-mode control. High output ripple.

DISADVANTAGES

No isolation between input and output. Switch has high peak and rms currents which limit output power. C1 and C2 have high ripple current requirements (low ESR), continuous current mode makes loop stabilization difficult, potential instabilities with circuit-mode control. High output ripple.

Power-factor correction. High reliability. Wide input voltage range.

TYPICAL APPLICATIONS

APPLICABLE HARRIS PRODUCTS


TYPE OF CONVERTER

Buck - Boost (Step Down/Up)

DIODE VOLTAGES (VRM)

$$V_{RM} = V_0 + V_{IN}$$

CIRCUIT CONFIGURATION

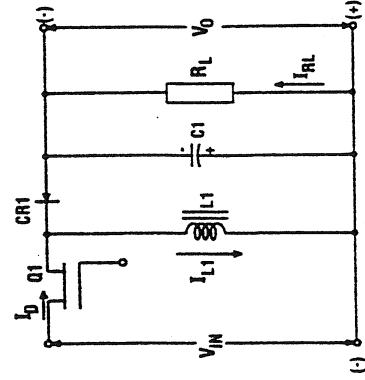

IDEAL TRANSFER FUNCTION

$$\frac{V_0}{V_{IN}} = -\left(\frac{t_{on}}{T_S \cdot t_{on}}\right) = -\left(\frac{D}{1-D}\right)$$

PEAK DRAIN CURRENT

$$I_{DMAX} = I_{RL} \left(\frac{1}{1-D}\right) + \frac{\Delta I_{L1}}{2}$$

PEAK DRAIN VOLTAGE

$$V_{DS} = V_{IN} + V_0 + V_D$$

AVERAGE DIODE CURRENTS

$$I_{CR1} = I_{RL}$$

ADVANTAGES

Voltage inversion without using a transformer,
simple, high frequency operation.

DISADVANTAGES


No isolation between input and output. Only one
output is possible. Regulator loop hard to stabilize.
High-side switch required. High output ripple.
High input ripple current.

TYPICAL APPLICATIONS

Inverse output voltages.

APPLICABLE HARRIS PRODUCTS

VOLTAGE AND CURRENT WAVEFORMS

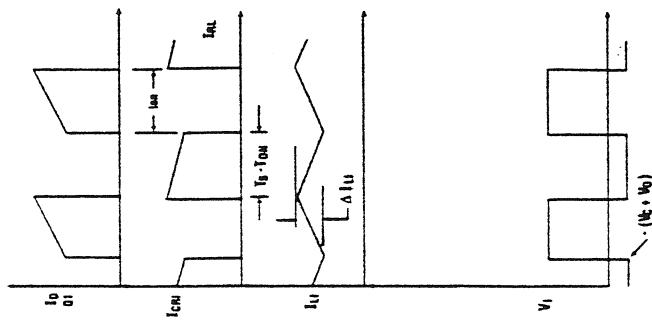


TYPE OF CONVERTER

Boost (Step Up)

DIODE VOLTAGES (VRM) *

$$V_{RM} = V_0$$

CIRCUIT CONFIGURATION

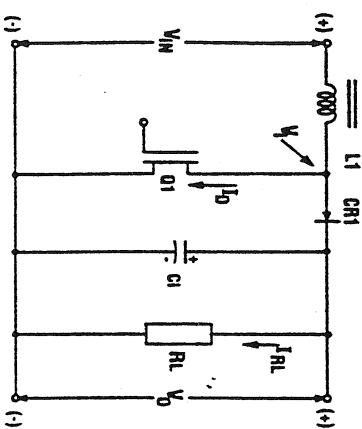

VOLTAGE AND CURRENT WAVEFORMS

$$\frac{V_0}{V_{IN}} = \frac{T_S}{T_S - t_{on}} = \frac{1}{(1-D)}$$

IDEAL TRANSFER FUNCTION

$$I_{DMAX} = I_{RL} \left(\frac{1}{1-D} \right) + \frac{\Delta I_{L1}}{2}$$

PEAK DRAIN CURRENT

$$V_{DS} = V_0 + V_D$$

AVERAGE DIODE CURRENTS

$$I_{CR1} = I_{RL}$$

ADVANTAGES

High efficiency, simple, no transformer. Low input ripple current.

DISADVANTAGES


No isolation between input and output. High peak collector current. Only one output is possible. Regulator loop hard to stabilize. High output ripple. Unable to control short-circuit current.

TYPICAL APPLICATIONS

Power-factor correction. Battery up-converters.

APPLICABLE HARRIS PRODUCTS

HIP5061, ICL7667, HV400

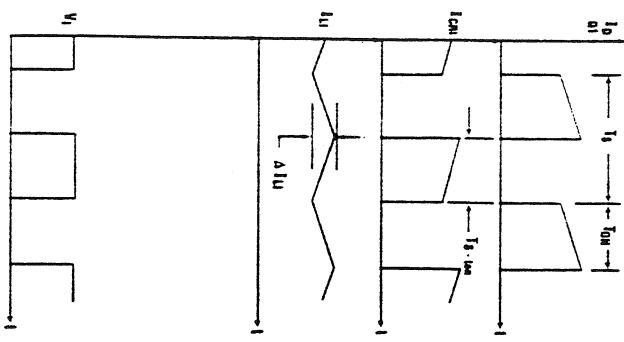


TYPE OF CONVERTER

Buck (Step Down)

DIODE VOLTAGES (VRM)

$$V_{DM} = V_{IN}$$

CIRCUIT CONFIGURATION

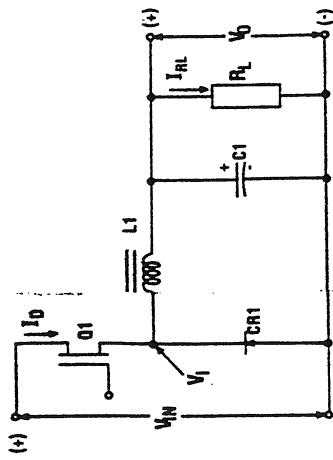

IDEAL TRANSFER FUNCTION

$$\frac{V_O}{V_{IN}} = \frac{t_{ON}}{T_S} = D$$

PEAK DRAIN CURRENT

$$I_{DMAX} = I_{RL} + \frac{\Delta I_L}{2}$$

AVERAGE DIODE CURRENTS

$$V_{DQ} = V_{IN} + V_D$$

$$I_{CR1} = I_{RL} (1-D)$$

ADVANTAGES


High efficiency, simple, no transformer, low switch stress. Small output filter, low ripple.

DISADVANTAGES

No isolation between input and output. Potential over-voltage if Q1 shorts. Only one output possible. High-side switch drive required. High input ripple current.

TYPICAL APPLICATIONS

Small size, imbedded systems.

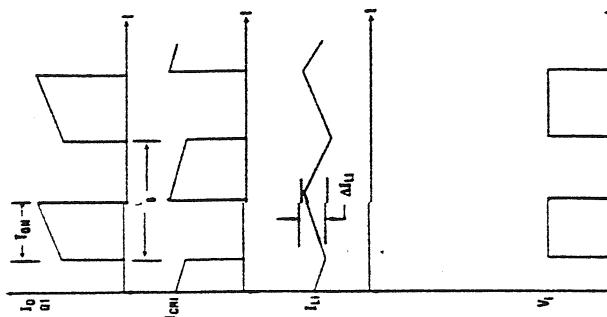

VOLTAGE AND CURRENT WAVEFORMS

APPLICABLE HARRIS PRODUCTS

HIP5600 w/P-IGBT For off line CKTs.

