
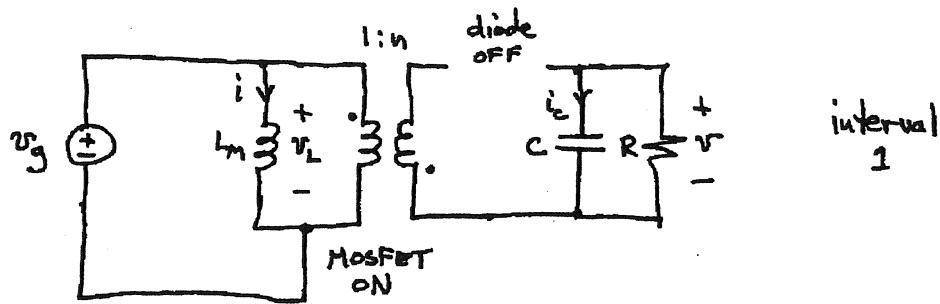


Problem 6.2


a)

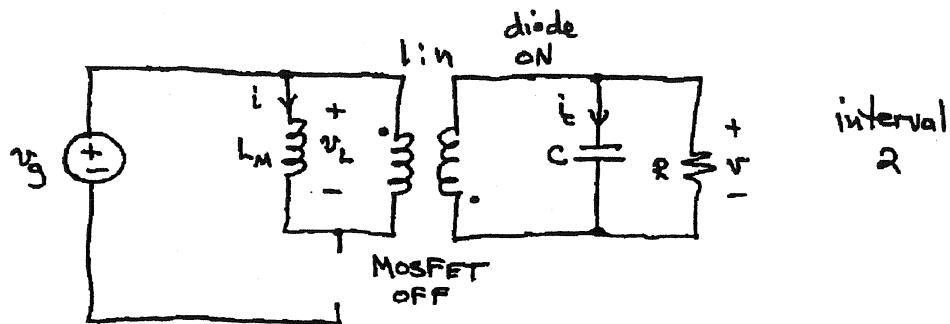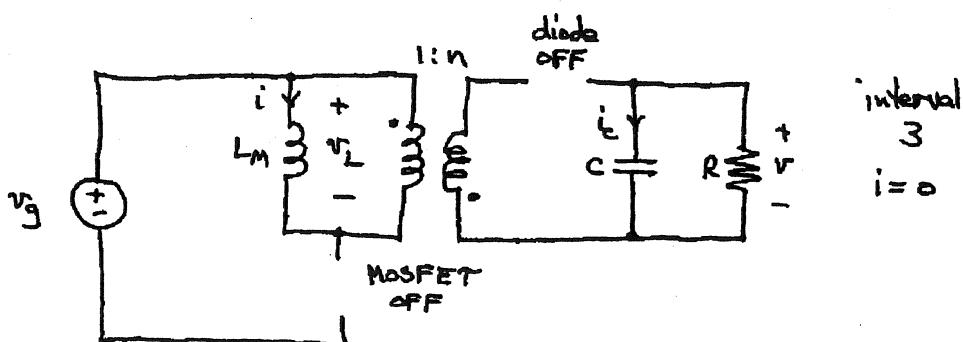

interval 1



interval 2

interval 3  
 $i = 0$ 

- b) From the text, the steady-state solution of this converter in CCM is

$$V = n \frac{D}{1-D} V_g \quad I = \frac{nV}{(1-D)R}$$

C J C  
H F J U

The inductor current ripple (in the magnetizing current, referred to primary side) is


$$\Delta i = \frac{V_g D T_s}{2 L_M}$$

The converter operates in DCM when  $\Delta i > I$ , or

$$\frac{V_g D T_s}{2 L_M} > \frac{n V}{(1-D) R} \quad \text{with } V = V_g n \frac{D}{(1-D)}$$

$$\Rightarrow (1-D)^2 > \frac{2 L_M n^2}{R T_s}$$

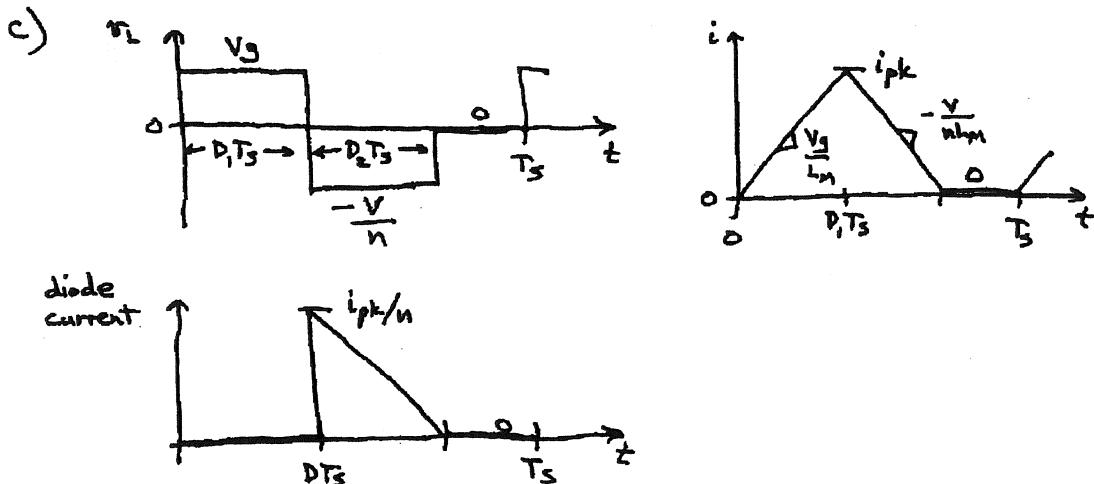which resembles the result for the buck-boost listed in Chapter 5. The factor of  $n^2$  occurs because  $L_M$  is referred to the primary, but  $R$  is connected to the secondary side.




Inductor volt-second balance:  $D_1 V_g - D_2 \frac{V}{n} = 0$

Capacitor charge balance:  $\frac{1}{2} D_2 \frac{i_{pk}}{n} = \frac{V}{R}$

with  $i_{pk} = \frac{V_g D_1 T_s}{L_M}$


Solve:  $V = V_g n \frac{D_1}{\sqrt{K}}$  where  $K = \frac{2 n^2 L_M}{R T_s}$

and  $D_2 = \sqrt{K}$

 

Tutorial  
Solution to Problem 6.1

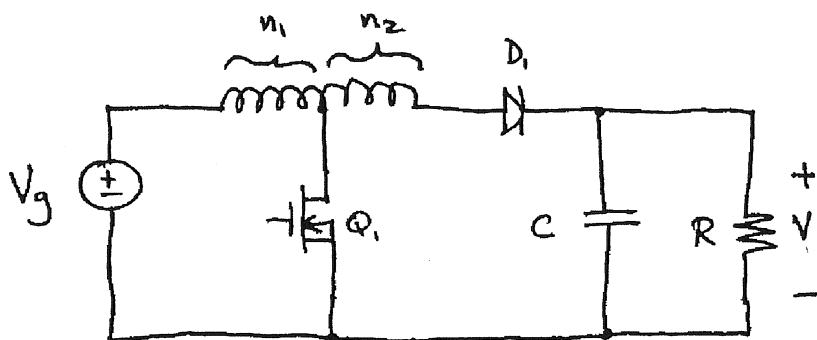
Analysis of tapped-inductor boost converter




Inductance of entire  $(n_1+n_2)$  turn inductor is  $L$

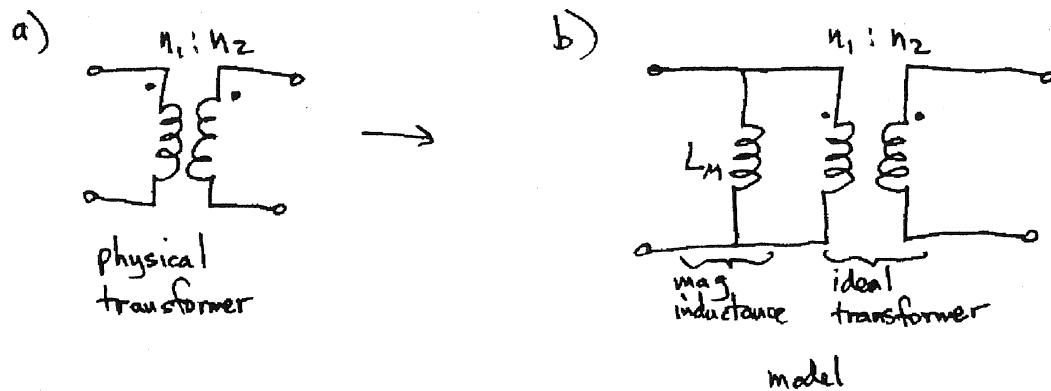- a) Sketch an equivalent circuit model for the tapped inductor, which includes an ideal transformer and a magnetizing inductance.


The equivalent circuit model of Fig. 6.17:



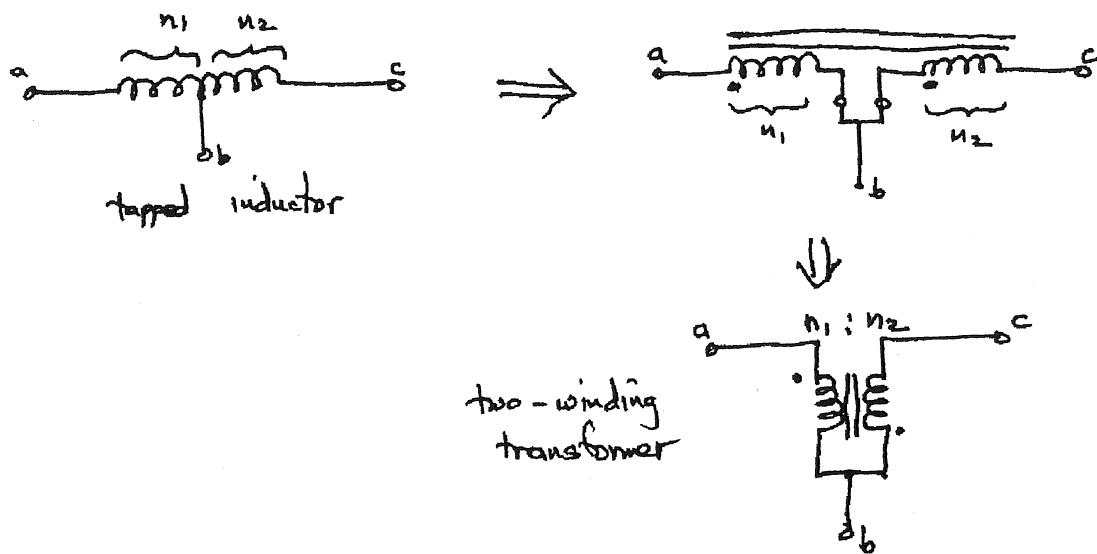The tapped inductor can be viewed as a two-winding transformer:



use two-winding transformer model:

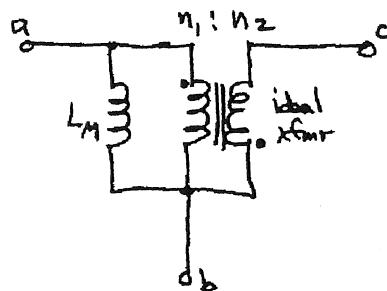


what is the value of  $L_M$ ?

We are given that the inductance of the entire  $(n_1+n_2)$  turn winding is  $L$ . So we should choose the value of  $L_M$  such that the inductance between terminals a and c, with terminal b open, is  $L$ .

Measurement of inductance between terminals a and c:

inject ac voltage  $v$ , measure current  $i$ . Impedance

$$is \ Z(s) = sL = \frac{v(s)}{i(s)}$$

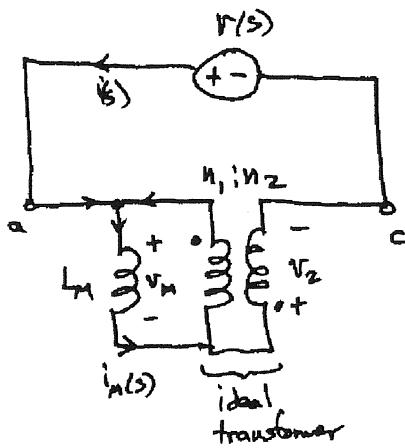

• Current in  $n_2$  winding is  $i(s)$ , going into dot

$\Rightarrow$  current in  $n_1$  winding is  $\frac{n_2}{n_1} i(s)$ , coming out of dot

$\Rightarrow$  node equation for magnetizing current  $i_M(s)$ :

$$i_M(s) = i(s) + \frac{n_2}{n_1} i(s) = \frac{n_1+n_2}{n_1} i(s)$$

$\Rightarrow$  voltage across inductor is

$$v_m(s) = sL_M i_M(s) = sL_M \frac{n_1+n_2}{n_1} i(s)$$

$\Rightarrow$  voltage across  $n_2$  winding is  $v_2 = \frac{n_2}{n_1} v_m(s) = \frac{n_2(n_1+n_2)}{n_1^2} sL_M i(s)$   
(positive at dot)

$\Rightarrow$  voltage  $v(s)$  is

$$\begin{aligned} v(s) &= v_m(s) + v_2(s) = sL_M i(s) \left( \frac{n_1+n_2}{n_1} + \frac{n_2(n_1+n_2)}{n_1^2} \right) \\ &= s \left( \frac{n_1+n_2}{n_1} \right)^2 L_M i(s) \end{aligned}$$


So the inductance between terminals a and c is

$$L = \left( \frac{n_1 + n_2}{n_1} \right)^2 L_M$$

$$\Rightarrow L_M = \left( \frac{n_1}{n_1 + n_2} \right)^2 L$$



---

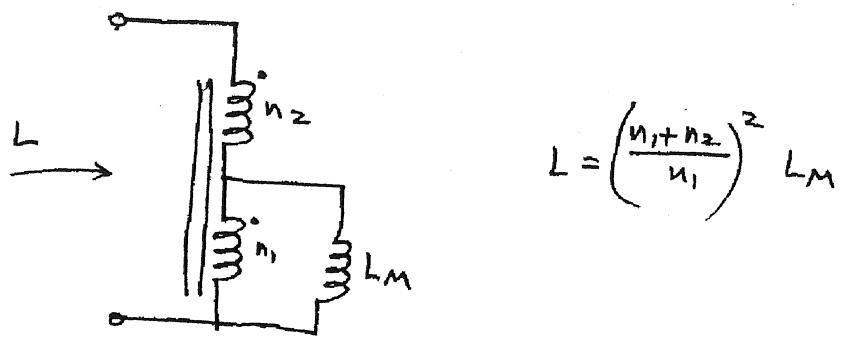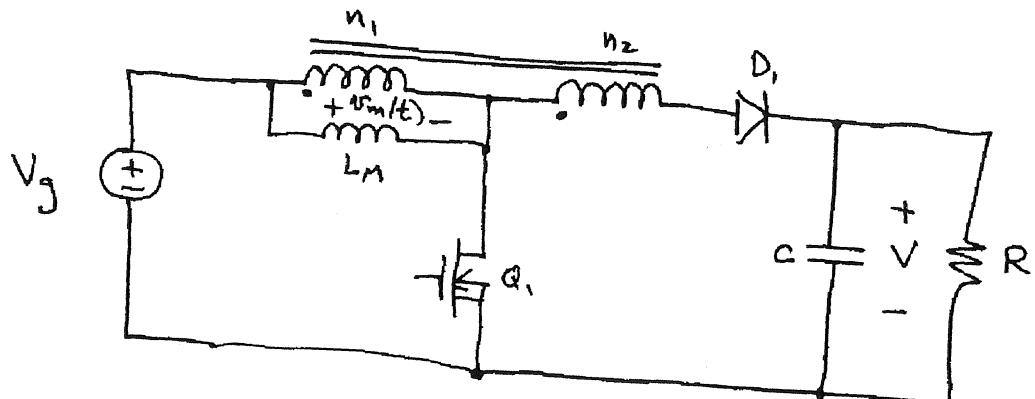an easier way: reflect  $L_M$  through auto transformer




---


So the converter circuit becomes



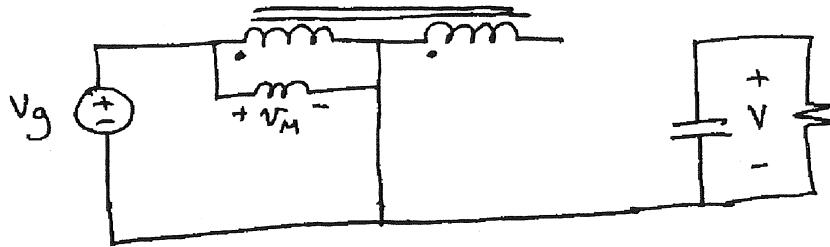b) Determine an analytical expression for  $M(D) = \frac{V}{V_g}$  in CCM, no losses.


Apply volt-second balance to LM

$D T_S < L < T_S$     Q<sub>1</sub> on, D<sub>1</sub> off




$$V_m = V_g$$

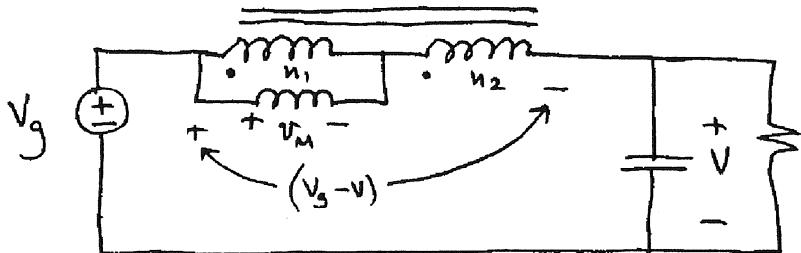$D T_S < L < T_S$     Q<sub>1</sub> off, D<sub>1</sub> on



$$V_m = \frac{n_1}{n_1+n_2} (V_g - V)$$

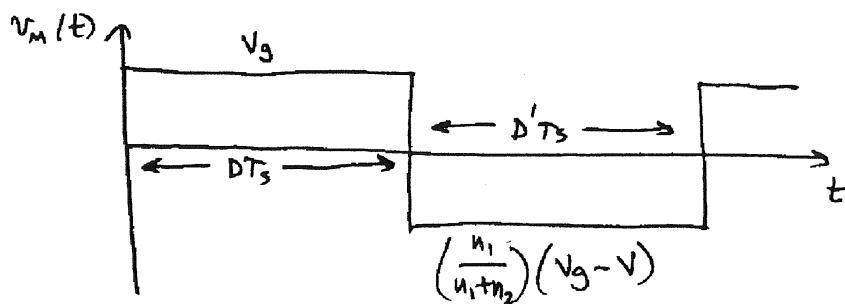

$$\langle V_m \rangle = 0 = D V_g + D' \left( \frac{n_1}{n_1+n_2} \right) (V_g - V)$$

Solve for  $V$ :


$$V D' \left( \frac{n_1}{n_1+n_2} \right) = DV_g + D' V_g \frac{n_1}{n_1+n_2}$$

$$\Rightarrow \frac{V}{V_g} = \frac{D + D' \left( \frac{n_1}{n_1+n_2} \right)}{D' \left( \frac{n_1}{n_1+n_2} \right)} = \frac{1}{D'} \cdot \left[ D \frac{n_1+n_2}{n_1} + D' \right]$$

$$M(D) = \left( \frac{1}{D'} \right) \left( 1 + \frac{n_2}{n_1} D \right)$$

which differs from the conventional untapped ( $n_2=0$ ) boost  $M(D)$  by a factor of  $\left(1 + \frac{n_2}{n_1} D\right)$ .

c)

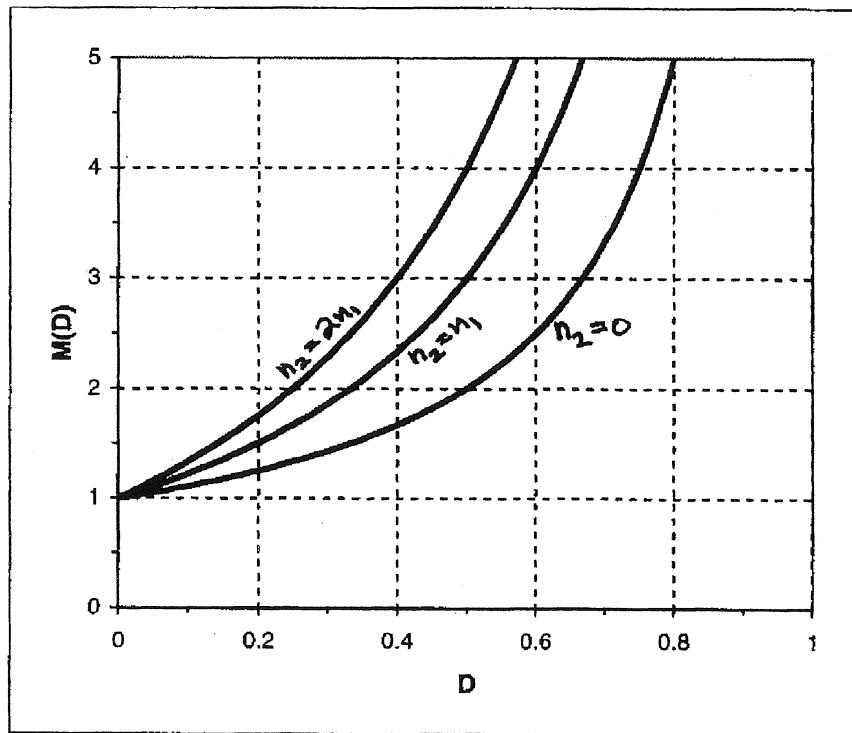

Tapped case  
yields increased  
output voltage