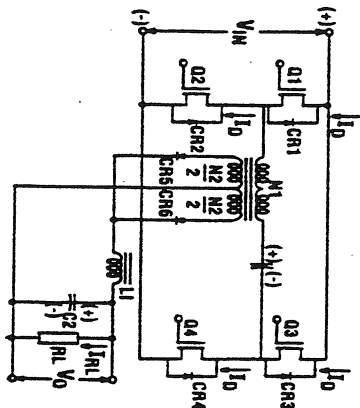


TYPE OF CONVERTER

Full Bridge


CIRCUIT CONFIGURATION



DIODE VOLTAGES (VRM)

$$VRM \begin{cases} V_{CR5} = 2V_{IN} \left(\frac{N_2}{N_1} \right) & V_{CR1} = V_{IN} \\ V_{CR6} = 2V_{IN} \left(\frac{N_2}{N_1} \right) & V_{CR2} = V_{IN} \end{cases}$$

VOLTAGE AND CURRENT WAVEFORMS

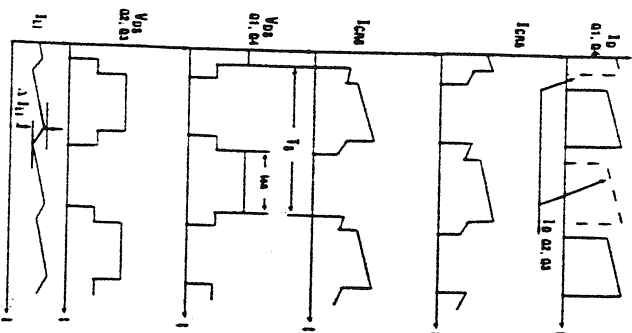

IDEAL TRANSFER FUNCTION

$$\frac{V_0}{V_{IN}} = 2 \frac{N_2}{N_1} \left(\frac{t_{on}}{T_S} \right) = 2 \frac{N_2}{N_1} (D)$$

PEAK DRAIN CURRENT

$$I_{DMAX} = \frac{N_2}{N_1} \left(I_{RL} + \frac{\Delta I_L}{2} \right) + \hat{I}_{MAG}$$

(\hat{I}_{MAG} = Peak magnetizing current.)

PEAK DRAIN VOLTAGE

$$V_{DS} = V_{IN}$$

AVERAGE DIODE CURRENTS

$$I_{CR5} = I_{RL}$$

$$I_{CR6} = I_{RL}$$

ADVANTAGES

Good transformer utilization, transistors rated at V_{IN} , isolation, multiple outputs. I_D is reduced as a ratio of N_2/N_1 . Zero voltage switching possible. Low output ripple.

DISADVANTAGES

High parts count. C1 has high ripple current. Requires high side switch drive. Cross conduction of Q1 and Q2 or Q3 and Q4 possible. High input current ripple.

TYPICAL APPLICATIONS

High power, high input voltage


APPLICABLE HARRIS PRODUCTS

HIP4080/81, HIP2500 HV400

TYPE OF CONVERTER

CIRCUIT CONFIGURATION

Half Bridge

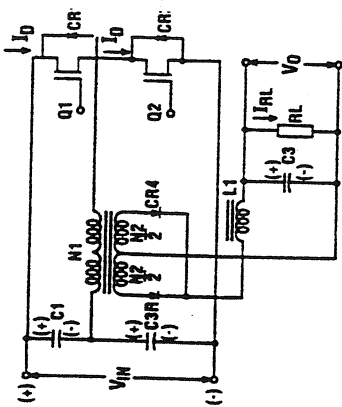

IDEAL TRANSFER FUNCTION

$$\frac{V_O}{V_{IN}} = \frac{N_2}{N_1} \left(\frac{t_{ON}}{T_S} \right) = \frac{N_2}{N_1} (D)$$

PEAK DRAIN CURRENT

$$I_{DMAX} = \frac{N_2}{N_1} \left(I_{RL} + \frac{\Delta I_L}{2} \right) + \hat{I}_M$$

(\hat{I}_M = Peak magnetizing current.)

PEAK DRAIN VOLTAGE

$$V_{DS} = V_{IN}$$

AVERAGE DIODE CURRENTS

$$I_{CR3} = \frac{I_{RL}}{2}$$


$$I_{CR4} = \frac{I_{RL}}{2}$$

DIODE VOLTAGES (V_{RM})

$$V_{CR3} = V_{IN} \left(\frac{N_2}{N_1} \right)$$

$$V_{CR4} = V_{IN} \left(\frac{N_2}{N_1} \right)$$

VOLTAGE AND CURRENT WAVEFORMS

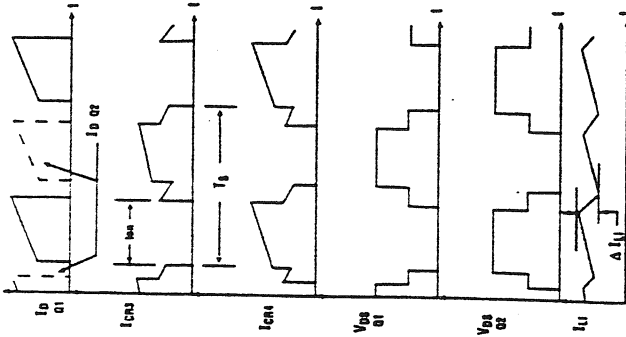

ADVANTAGES

Good transformer utilization. Transistors rated at V_{IN} , isolation, multiple outputs. I_D reduced as a ratio of N_2/N_1 . High power output. Zero voltage switching possible, near $D = 1$. Low output ripple.

DISADVANTAGES

Poor transient response, high parts count, C1 and C2 have high ripple current. Requires high side switch drive. Cross conduction of Q1 and Q2 possible. High input current ripple.

TYPICAL APPLICATIONS

High input voltage, moderate-to-high power.


APPLICABLE HARRIS PRODUCTS

HIP2500, HIP5500, HV400

TYPE OF CONVERTER

Two-Switch Forward

CIRCUIT CONFIGURATION

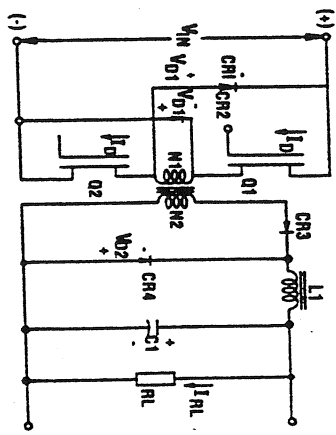


DIODE VOLTAGES (VRM)

$V_{CR1,PK} = V_{CR2,PK} = V_{IN}$

$V_{CR3} = V_{CR4} = \left(\frac{N_2}{N_1}\right) V_{IN}$

VOLTAGE AND CURRENT WAVEFORMS

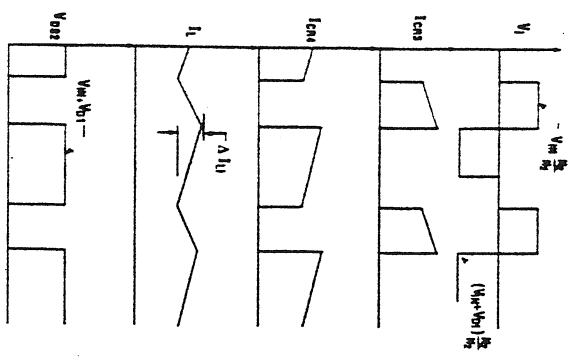

IDEAL TRANSFER FUNCTION

$$\frac{V_O}{V_{IN}} = \frac{N_2}{N_1} \left(\frac{t_{on}}{T_S} \right) = \frac{N_2}{N_1} (D)$$

PEAK DRAIN CURRENT

$$I_{DMAX} = \frac{N_2}{N_1} \left(I_{RL} + \frac{\Delta I_L}{2} \right) + \hat{I}_{MAG}$$

(\hat{I}_{MAG} = Peak magnetizing current.)

PEAK DRAIN VOLTAGE

$$V_{DS} = V_{IN} + V_{D1}$$

(Q_1 or Q_2)

AVERAGE DIODE CURRENTS

$$I_{CR1,AVE} = I_{CR2,AVE} = \frac{\hat{I}_{MAG}}{2} D$$

$$I_{CR3,AVE} = I_{RL} D$$

$$I_{CR4,AVE} = I_{RL} (1-D)$$

ADVANTAGES

Drain currents reduced by turns ratio. Lossless snubber recovers energy. Drain voltage 1/2 that of conventional forward converter. Low output ripple.

DISADVANTAGES

Poor transformer utilization, high parts count, high-side switch drive required. Transformer reset limits duty ratio. High input current ripple.

TYPICAL APPLICATIONS

High input voltage, moderate power. Supports multiple outputs.


APPLICABLE HARRIS PRODUCTS

HIP2500, HV400

TYPE OF CONVERTER

CIRCUIT CONFIGURATION

Push-Pull

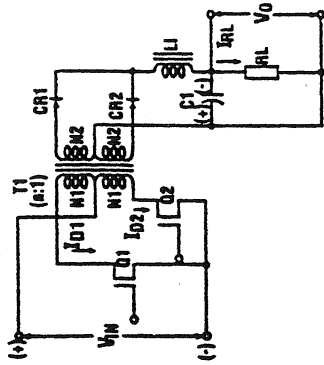

IDEAL TRANSFER FUNCTION

$$\frac{V_O}{V_{IN}} = 2 \frac{N_2}{N_1} \left(\frac{t_{on}}{T_S} \right) = 2 \frac{N_2}{N_1} (D)$$

PEAK DRAIN CURRENT

$$I_{D_{MAX}} = \frac{N_2}{N_1} \left(I_{RL} + \frac{\Delta I_L}{2} \right) + \hat{I}_{MAG}$$

(\hat{I}_{MAG} = Peak magnetizing current.)

PEAK DRAIN VOLTAGE

$$V_{DS} = 2 V_{IN}$$

AVERAGE DIODE CURRENTS

$$I_{CR1} = \frac{I_{RL}}{2}$$


$$I_{CR2} = \frac{I_{RL}}{2}$$

DIODE VOLTAGES (VRM)

$$V_{CR1} = 2V_{IN} \left(\frac{N_2}{N_1} \right)$$

$$V_{CR2} = 2V_{IN} \left(\frac{N_2}{N_1} \right)$$

VOLTAGE AND CURRENT WAVEFORMS

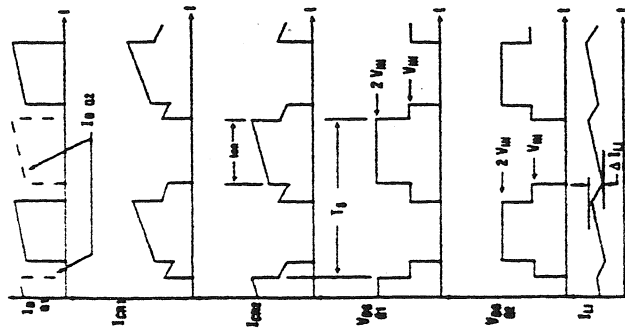

ADVANTAGES

Good transformer utilization. Drain current reduced as a function of N_2/N_1 . Good at low values of V_{IN} . Low output ripple.

DISADVANTAGES

Cross conduction of Q1 and Q2 possible, high parts count. Transformer design critical. High voltage required for Q1 and Q2. High input current ripple.

TYPICAL APPLICATIONS

Low Input voltage.


APPLICABLE HARRIS PRODUCTS

HIP5062, HIP5061

TYPE OF CONVERTER

Flyback


CIRCUIT CONFIGURATION

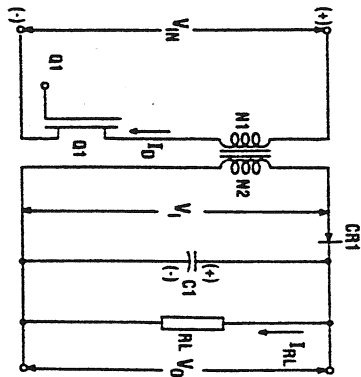

DIODE VOLTAGES (VRM)

$$V_{RM} = V_{IN} \left(\frac{N_2}{N_1} \right)$$

VOLTAGE AND CURRENT WAVEFORMS

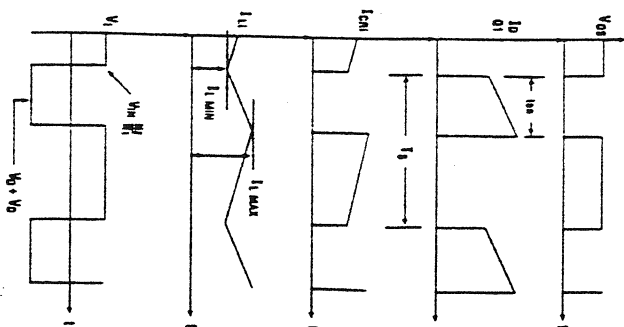

IDEAL TRANSFER FUNCTION

$$\frac{V_0}{V_{IN}} = \frac{N_2}{N_1} \left(\frac{t_{on}}{T_S - t_{on}} \right) = \frac{N_2}{N_1} \left(\frac{D}{1-D} \right)$$

PEAK DRAIN CURRENT

$$I_{D_{MAX}} = I_{RL} \left(\frac{N_2}{N_1} \right) \left(\frac{1}{1-D} \right) + \frac{\Delta I_L}{2}$$

PEAK DRAIN VOLTAGE

$$V_{DS} = V_{IN} + \left(\frac{N_1}{N_2} \right) (V_{OUT} + V_D)$$

AVERAGE DIODE CURRENTS

$$I_{CR1} = I_{RL}$$

DISADVANTAGES

Poor transformer utilization. Transformer size energy. High output ripple. CR1 needs fast recovery.

ADVANTAGES

Drain current reduced by turns ratio of transformer. Low parts count. Isolation. Has no secondary put inductors.

TYPICAL APPLICATIONS

Low output power. Supports multiple outputs


APPLICABLE HARRIS PRODUCTS

HIP5061, ICL7667, HV400

TYPE OF CONVERTER

CIRCUIT CONFIGURATION

Forward

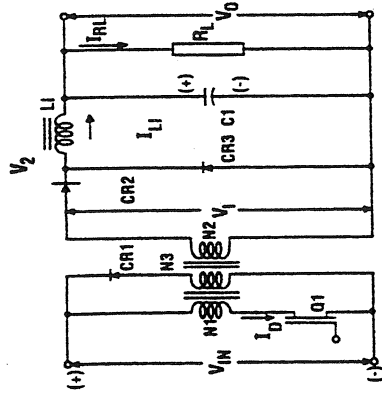

IDEAL TRANSFER FUNCTION

$$\frac{V_O}{V_{IN}} = \frac{N_2}{N_1} \left(\frac{t_{ON}}{T_S} \right) = \frac{N_2}{N_1} (D)$$

PEAK DRAIN CURRENT

$$I_{DMAX} = \frac{N_2}{N_1} \left(I_{RL} + \frac{\Delta I_L}{2} \right) + \hat{I}_{MAG}$$

(\hat{I}_{MAG} = Peak magnetizing current.)

PEAK DRAIN VOLTAGE

$$V_{DS} = V_{IN} \left(1 + \frac{N_1}{N_3} \right)$$

AVERAGE DIODE CURRENTS

$$I_{CR1} = \frac{\hat{I}_{MAG}}{2} (D)$$


$$I_{CR2} = I_{RL} (D)$$

$$I_{CR3} = I_{RL} (1-D)$$

DIODE VOLTAGES (V_{RM})

$$V_{RM} \begin{cases} V_{CR1} = V_{IN} \left(1 + \frac{N_3}{N_1} \right) \\ V_{CR2} = V_{IN} \left(\frac{N_2}{N_3} \right) \\ V_{CR3} = V_{IN} \left(\frac{N_2}{N_1} \right) \end{cases}$$

VOLTAGE AND CURRENT WAVEFORMS

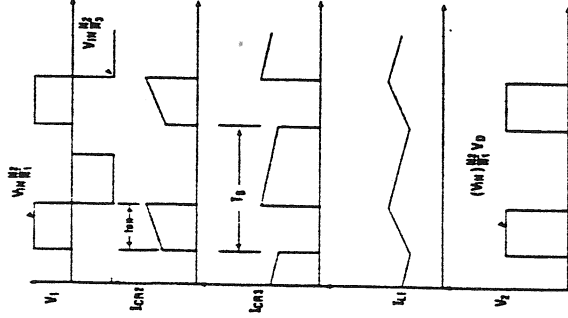

ADVANTAGES

Drain current reduced by ratio of N_2/N_1 . Low output ripple.

DISADVANTAGES

Poor transformer utilization. Poor transient response. Transformer design is critical. Transformer reset limits duty ratio. High voltage required for Q1. High input current ripple.

TYPICAL APPLICATIONS

Low-to-moderate output power. Supports multiple outputs.

APPLICABLE HARRIS PRODUCTS

HIP5061, ICL7667, HV400


TYPE OF CONVERTER

CUK (Step Up/Down)


DIODE VOLTAGES (VRM)

$V_{RM} \approx V_O + V_{IN}$

CIRCUIT CONFIGURATION

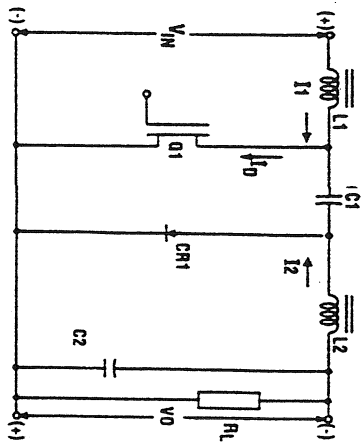

VOLTAGE AND CURRENT WAVEFORMS

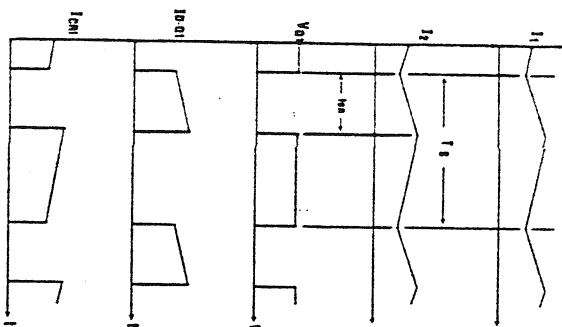

IDEAL TRANSFER FUNCTION

$\frac{V_O}{V_{IN}} = - \left(\frac{t_{on}}{T_s - t_{on}} \right) = - \left(\frac{D}{1-D} \right)$

PEAK DRAIN CURRENT

$I_{D_{MAX}} = I_1 + I_2 = I_1 \left(\frac{1}{D} \right)$

PEAK DRAIN VOLTAGE

$V_{DS} = 2 V_{IN}$

AVERAGE DIODE CURRENTS

$I_{CR1} = I_1 + I_2$

$I_1 + I_2 = I_1 \left(\frac{1}{D} \right)$

ADVANTAGES

Simple, low ripple input and output current, capacitive isolation protects against switch failure.

DISADVANTAGES

High drain current. C-1 has high ripple current requirement (low ESR). High voltage required for Q1. Voltage inversion.

TYPICAL APPLICATIONS

Low noise, inverse output voltages.


APPLICABLE HARRIS PRODUCTS

HIP5060, HIP5061, HIP5062, HIP5063

TYPE OF CONVERTER

CIRCUIT CONFIGURATION

SEPIC (Step Down/Up)

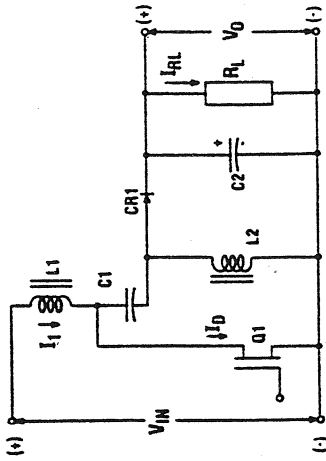

IDEAL TRANSFER FUNCTION

$$\frac{V_O}{V_I} = \frac{D}{1-D}$$

PEAK DRAIN CURRENT

$$I_{DMAX} = I_1 + I_{RL} + \frac{\Delta I_{L1} + \Delta I_{L2}}{2}$$

PEAK DRAIN VOLTAGE

$$V_{DS} = V_O + V_{IN} + V_D$$


AVERAGE DIODE CURRENTS

$$I_{CR1} = I_{RL}$$

DIODE VOLTAGES (V_{RM})

$$V_{RM} = V_O + V_{IN}$$

VOLTAGE AND CURRENT WAVEFORMS

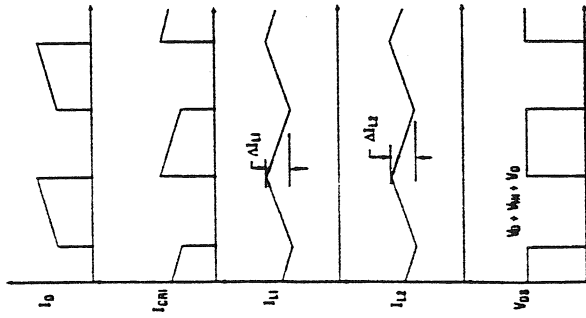

ADVANTAGES

Low ripple input current, step-up or step-down with no inversion, no transformer. Capacitive isolation protects against switch failure (unlike Buck).

DISADVANTAGES

No isolation between input and output. Switch has high peak and rms currents which limit output power. C1 and C2 have high ripple current requirements (low ESR), continuous current mode makes loop stabilization difficult, potential instabilities with circuit-mode control. High output ripple.

TYPICAL APPLICATIONS

Power-factor correction. High reliability. Wide input voltage range.

APPLICABLE HARRIS PRODUCTS

HIP5060, HIP5061, HIP5062, HIP5063


TYPE OF CONVERTER

Buck - Boost (Step Down/Up)


DIODE VOLTAGES (V_{RM})

$V_{RM} = V_0 + V_{IN}$

CIRCUIT CONFIGURATION

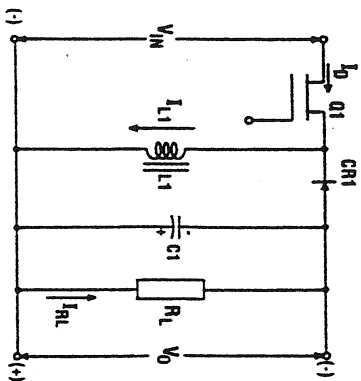

VOLTAGE AND CURRENT WAVEFORMS

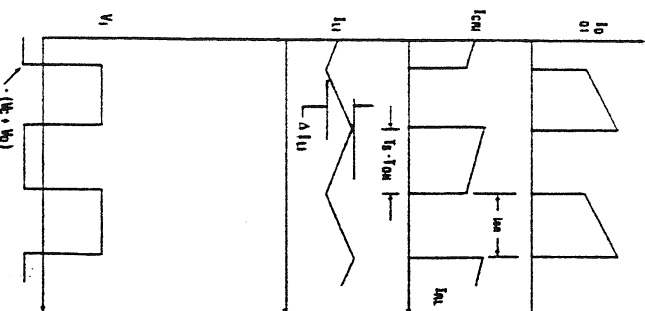

IDEAL TRANSFER FUNCTION

$\frac{V_0}{V_{IN}} = - \left(\frac{t_{on}}{T_S - t_{on}} \right) = - \left(\frac{D}{1-D} \right)$

PEAK DRAIN CURRENT

$I_{DMAX} = I_{RL} \left(\frac{1}{1-D} \right) + \frac{\Delta I_{L1}}{2}$

PEAK DRAIN VOLTAGE

$V_{DS} = V_{IN} + V_0 + V_D$

AVERAGE DIODE CURRENTS

$I_{CR1} = I_{RL}$

ADVANTAGES

Voltage inversion without using a transformer, simple, high frequency operation.

DISADVANTAGES

No isolation between input and output. Only one output is possible. Regulator loop hard to stabilize. High-side switch drive required. High output ripple. High input ripple current.

TYPICAL APPLICATIONS


Inverse output voltages.

APPLICABLE HARRIS PRODUCTS

TYPE OF CONVERTER

CIRCUIT CONFIGURATION

Boost (Step Up)

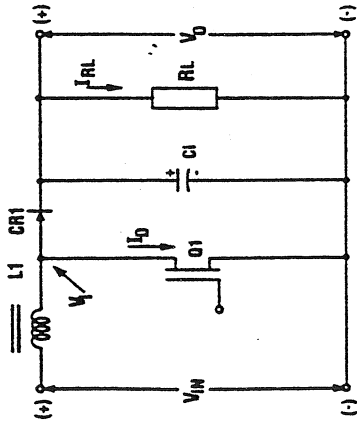

IDEAL TRANSFER FUNCTION

$$\frac{V_O}{V_{IN}} = \frac{T_S}{T_S - t_{on}} = \frac{1}{1-D}$$

PEAK DRAIN CURRENT

$$I_{DMAX} = I_{RL} \left(\frac{1}{1-D} \right) + \frac{\Delta I_L}{2}$$

PEAK DRAIN VOLTAGE

$$V_{DS} = V_O + V_D$$


AVERAGE DIODE CURRENTS

$$I_{CR1} = I_{RL}$$

DIODE VOLTAGES (V_{RM})

$$V_{RM} = V_O$$

VOLTAGE AND CURRENT WAVEFORMS

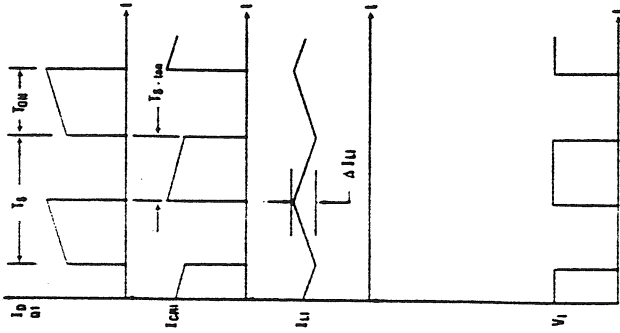

ADVANTAGES

High efficiency, simple, no transformer. Low input ripple current.

DISADVANTAGES

No isolation between input and output. High peak collector current. Only one output is possible. Regulator loop hard to stabilize. High output ripple. Unable to control short-circuit current.

TYPICAL APPLICATIONS

Power-factor correction. Battery up-converters.

APPLICABLE HARRIS PRODUCTS

HIP5061, ICL7667, HV400


TYPE OF CONVERTER

Buck (Step Down)


DIODE VOLTAGES (VRM)

$V_{RM} = V_{IN}$

CIRCUIT CONFIGURATION

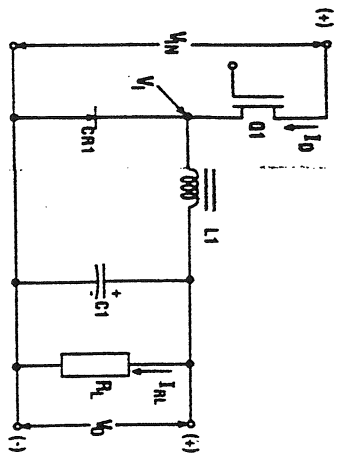

VOLTAGE AND CURRENT WAVEFORMS

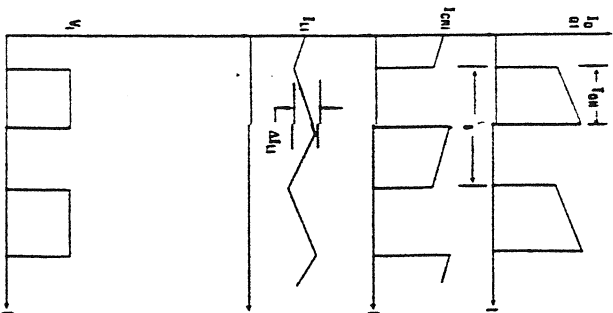

IDEAL TRANSFER FUNCTION

$\frac{V_O}{V_{IN}} = \frac{t_{on}}{T_S} = D$

PEAK DRAIN CURRENT

$I_{DMAX} = I_{RL} + \frac{\Delta I_L}{2}$

PEAK DRAIN VOLTAGE

$V_{Dd} = V_{IN} + V_D$

AVERAGE DIODE CURRENTS

$I_{CR1} = I_{RL} (1-D)$

DIODE VOLTAGES (VRM)

$V_{RM} = V_{IN}$

ADVANTAGES

High efficiency, simple, no transformer, low switch stress. Small output filter, low ripple.

DISADVANTAGES

No isolation between input and output. Potential over-voltage if Q1 shorts. Only one output possible. High-side switch drive required. High input ripple current.

TYPICAL APPLICATIONS

Small size, inbedded systems.

APPLICABLE HARRIS PRODUCTS

HPP5600 w/P-IGBT For off line CKTS.

