

Copy CWB

L13


DIODE VOLTAGES (VRM)

$$V_{RM} = V_{IN} \left(\frac{N_2}{N_1} \right)$$

5

TYPE OF CONVERTER

CIRCUIT CONFIGURATION

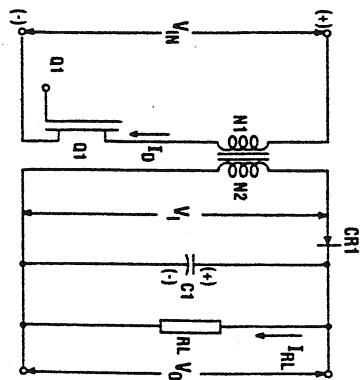

VOLTAGE AND CURRENT WAVEFORMS

IDEAL TRANSFER FUNCTION

$$\frac{V_o}{V_{IN}} = \frac{N_2}{N_1} \left(\frac{t_{on}}{T_S - t_{on}} \right) = \frac{N_2}{N_1} \left(\frac{D}{1-D} \right)$$

IDEAL TRANSFER FUNCTION

$$IDMAX = I_{RL} \left(\frac{N_2}{N_1} \right) \left(\frac{1}{1-D} \right) + \frac{\Delta I_L}{2}$$

PEAK DRAIN CURRENT

$$V_{DS} = V_{IN} + \left(\frac{N_1}{N_2} \right) (V_{OUT} + V_D)$$


AVERAGE DIODE CURRENTS

$$ICR1 = I_{RL}$$

ADVANTAGES

DISADVANTAGES

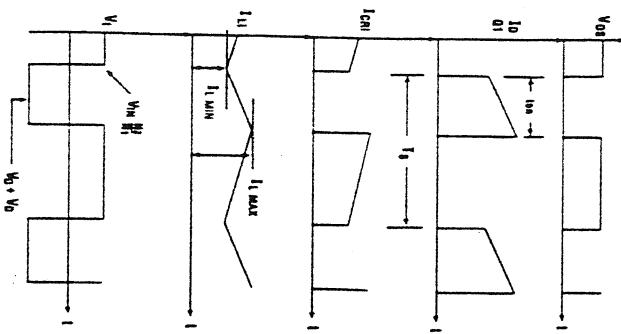Poor transformer utilization. Transformer size energy. High output ripple. CR1 needs fast recovery.



TYPICAL APPLICATIONS

Low output power. Supports multiple outputs


APPLICABLE HARRIS PRODUCTS

HIP5061, ICL7667, HV400

TYPE OF CONVERTER

Forward

CIRCUIT CONFIGURATION

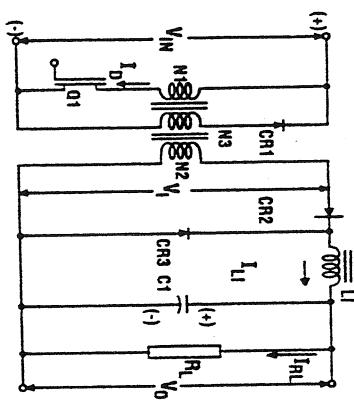


DIODE VOLTAGES (VRM)

$$V_{CR1} = V_{IN} \left(1 + \frac{N_3}{N_1} \right)$$

$$V_{CR2} = V_{IN} \left(\frac{N_2}{N_3} \right)$$

$$V_{CR3} = V_{IN} \left(\frac{N_2}{N_1} \right)$$

VOLTAGE AND CURRENT WAVEFORMS

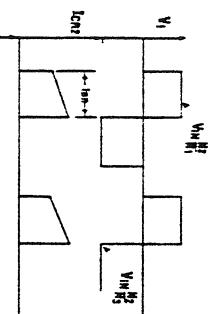

IDEAL TRANSFER FUNCTION

$$\frac{V_o}{V_{IN}} = \frac{N_2}{N_1} \left(\frac{t_{on}}{T_S} \right) = \frac{N_2}{N_1} = (D)$$

$$\text{PEAK DRINK CURRENT} \quad I_{D\text{MAX}} = \frac{N_2}{N_1} \left(I_{RL} + \frac{\Delta I_L}{2} \right) + \hat{I}_{\text{MAG}}$$

(\hat{I}_{MAG} = Peak magnetizing current.)


$$\text{PEAK BRAIN VOLTAGE} \quad V_{DS} = V_{IN} \left(1 + \frac{N_1}{N_3} \right)$$

ADVANTAGES

$$\text{AVERAGE DIODE CURRENTS} \quad I_{CR1} = \frac{\hat{I}_{\text{MAG}}}{2} (D)$$

$$I_{CR2} = I_{RL} (D)$$

$$I_{CR3} = I_{RL} (1-D)$$

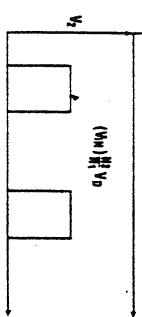

Drain current reduced by ratio of N_2/N_1 . Low output ripple.

DISADVANTAGES

Poor transformer utilization. Poor transient response. Transformer design is critical. Transformer reset limits duty ratio. High voltage required for Q1. High input current ripple.

TYPICAL APPLICATIONS

Low-to-moderate output power. Supports multiple outputs.


APPLICABLE SEMICONDUCTORS

HP5061, ICL7667, HV400


TWO-Switch Forward

DIODE VOLTAGES (VRM)
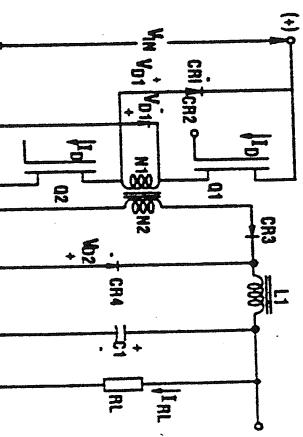
$$V_{CR1,PK} = V_{CR2,PK} = V_{IN} \left(\frac{N_2}{N_1} \right)$$



VOLTAGE AND CURRENT WAVEFORMS

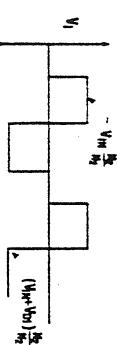

IDEAL TRANSFER FUNCTION

$$\frac{V_O}{V_{IN}} = \frac{N_2}{N_1} \left(\frac{t_{on}}{T_S} \right) = \frac{N_2}{N_1} (D)$$

PEAK DRAIN CURRENT

$$I_{DMAX} = \frac{N_2}{N_1} \left(I_{RL} + \frac{\Delta I_L}{2} \right) + \hat{I}_{MAG}$$

(\hat{I}_{MAG} = peak magnetizing current.)

PEAK DRAIN VOLTAGE

$$(Q_1 \text{ or } Q_2) \quad V_{DS} = V_{IN} + V_{B1}$$

AVERAGE DIODE CURRENTS

- $I_{CR1,AVE} = I_{CR2,AVE} = \frac{\hat{I}_{MAG}}{2} D$
- $I_{CR3,AVE} = I_{RL} D$
- $I_{CR4,AVE} = I_{RL}(1-D)$

ADVANTAGES

DISADVANTAGES

Poor transformer utilization, high parts count, high-side switch drive required. Transformer reset limits duty ratio. High input current ripple.

TYPICAL APPLICATIONS

High input voltage, moderate power. Supports multiple outputs.

APPLICABLE HARRIS PRODUCTS

HIP2500, HV400




TYPE OF CONVERTER

Push-Pull

DIODE VOLTAGES (VRM)

CIRCUIT CONFIGURATION

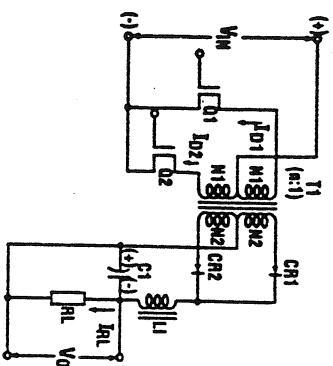

IDEAL TRANSFER FUNCTION

$$\frac{V_0}{V_{IN}} = 2 \frac{N_2}{N_1} \left(\frac{t_{on}}{T_S} \right) = 2 \frac{N_2}{N_1} (D)$$


$$I_{DMAX} = \frac{N_2}{N_1} \left(I_{RL} + \frac{\Delta I_L}{2} \right) + \hat{I}_{MAG}$$

(\hat{I}_{MAG} = peak magnetizing current.)

PEAK DRAIN VOLTAGE

$$V_{DS} = 2 V_{IN}$$

VOLTAGE AND CURRENT WAVEFORMS

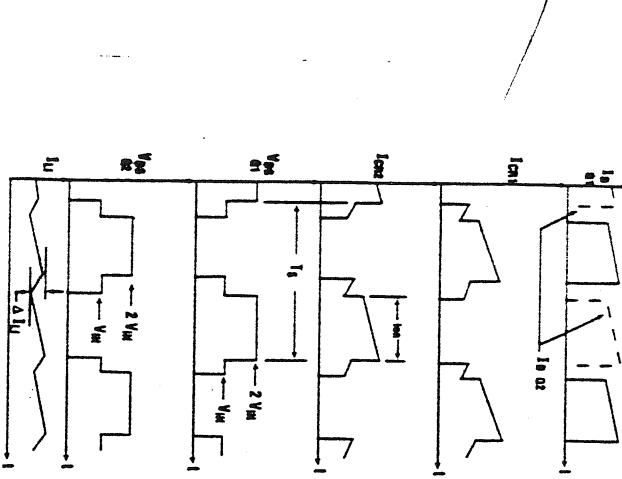

AVERAGE DIODE CURRENTS

$$I_{CR1} = \frac{I_{RL}}{2}$$

ADVANTAGES

Good transformer utilization. Drain current reduced as a function of N_2/N_1 . Good at low values of V_{IN} . Low output ripple.

DISADVANTAGES

Cross conduction of Q1 and Q2 possible, high parts count. Transformer design critical. High voltage required for Q1 and Q2. High input current ripple.

TYPICAL APPLICATIONS

Low input voltage.

APPLICABLE HARRIS PRODUCTS


HIP5062, HIP5061

Half Bridge


DIODE VOLTAGES (VRM)

TYPE OF CONVERTER

CIRCUIT CONFIGURATION

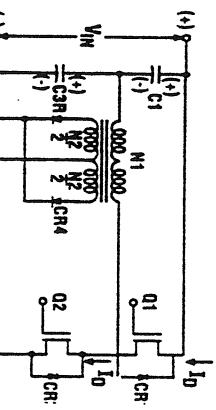

VOLTAGE AND CURRENT WAVEFORMS

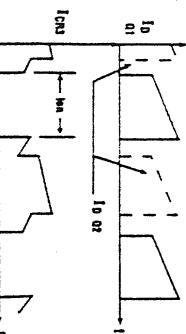

IDEAL TRANSFER FUNCTION

$$\frac{V_O}{V_{IN}} = \frac{N_2}{N_1} \left(\frac{t_{on}}{T_S} \right) = \frac{N_2}{N_1} (D)$$

PEAK DRAIN CURRENT

$$I_{DMAX} = \frac{N_2}{N_1} \left(I_{RL} + \frac{\Delta I_L}{2} \right) + \hat{I}_M$$

(\hat{I}_M = peak magnetizing current.)

PEAK DRAIN VOLTAGE

$$V_{DS} = V_{IN}$$

ADVANTAGES

AVERAGE DRAIN CURRENTS

$$ICR3 = \frac{I_{RL}}{2}$$

$$ICR4 = \frac{I_{RL}}{2}$$

DISADVANTAGES

Good transformer utilization. Transistors rated at V_{IN} isolation, multiple outputs, ID reduced as a ratio of N_2/N_1 . High power output. Zero voltage switching possible, near D = 1. Low output ripple.

Poor transient response, high parts count, C1 and C2 have high ripple current. Requires high side switch drive. Cross conduction of Q1 and Q2 possible. High input current ripple.

TYPICAL APPLICATIONS


HIP2500, HIP5500, HV400

$$V_{RM} \left\{ \begin{array}{l} V_{CR3} = V_{IN} \left(\frac{N_2}{N_1} \right) \\ V_{CR4} = V_{IN} \left(\frac{N_2}{N_1} \right) \end{array} \right.$$

TYPE OF CONVERTER

Full Bridge


CIRCUIT CONFIGURATION

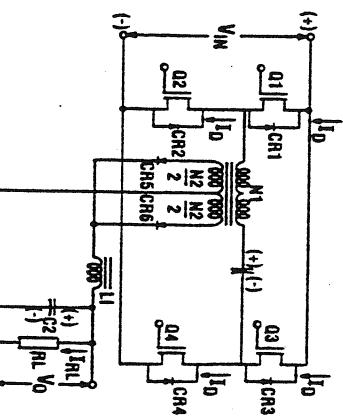

DIODE VOLTAGES (VRM)

$$V_{RM} \left\{ \begin{array}{l} V_{CR5} = 2V_{IN} \left(\frac{N_2}{N_1} \right) \\ V_{CR6} = 2V_{IN} \left(\frac{N_2}{N_1} \right) \\ V_{CR1} = V_{IN} \\ V_{CR2} = V_{IN} \end{array} \right.$$

VOLTAGE AND CURRENT WAVEFORMS

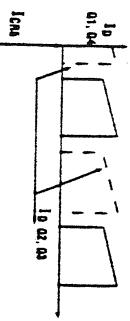

IDEAL TRANSFER FUNCTION

$$\frac{V_O}{V_{IN}} = 2 \frac{N_2}{N_1} \left(\frac{t_{on}}{T_S} \right) = 2 \frac{N_2}{N_1} (D)$$

PEAK DRAIN CURRENT

$$I_{DMAX} = \frac{N_2}{N_1} \left(I_{RL} + \frac{\Delta I_{L1}}{2} \right) + \hat{I}_{MAG}$$

(\hat{I}_{MAG} = Peak magnetizing current.)

PEAK DRAIN VOLTAGE

$$V_{DS} = V_{IN}$$


ADVANTAGES

AVERAGE DIODE CURRENTS

$$I_{CR5} = I_{RL}$$

DISADVANTAGES

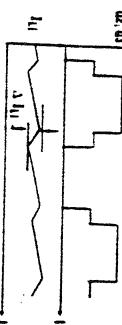Good transformer utilization, transistors rated at V_{IN} isolation, multiple outputs, ID is reduced as a ratio of N_2/N_1 . Zero voltage switching possible. Low output ripple.



TYPICAL APPLICATIONS

High power, high input voltage.

APPLICABLE HARRIS PRODUCTS

HIP4080/81, HIP2500 HV400