

ECE 562


Week 11 Lecture 1


Fall 2008

Week 11 Lecture 1

Summary

Slides	Topic
3-6	Progress in microelectronics
7-11	Resonant converters
12-21	RLC impedance
22-29	Impedance in resonant converters
30-33	DC-DC resonant converters
34-40	Solving for resonant converter
41-45	Fluorescent lamp circuits

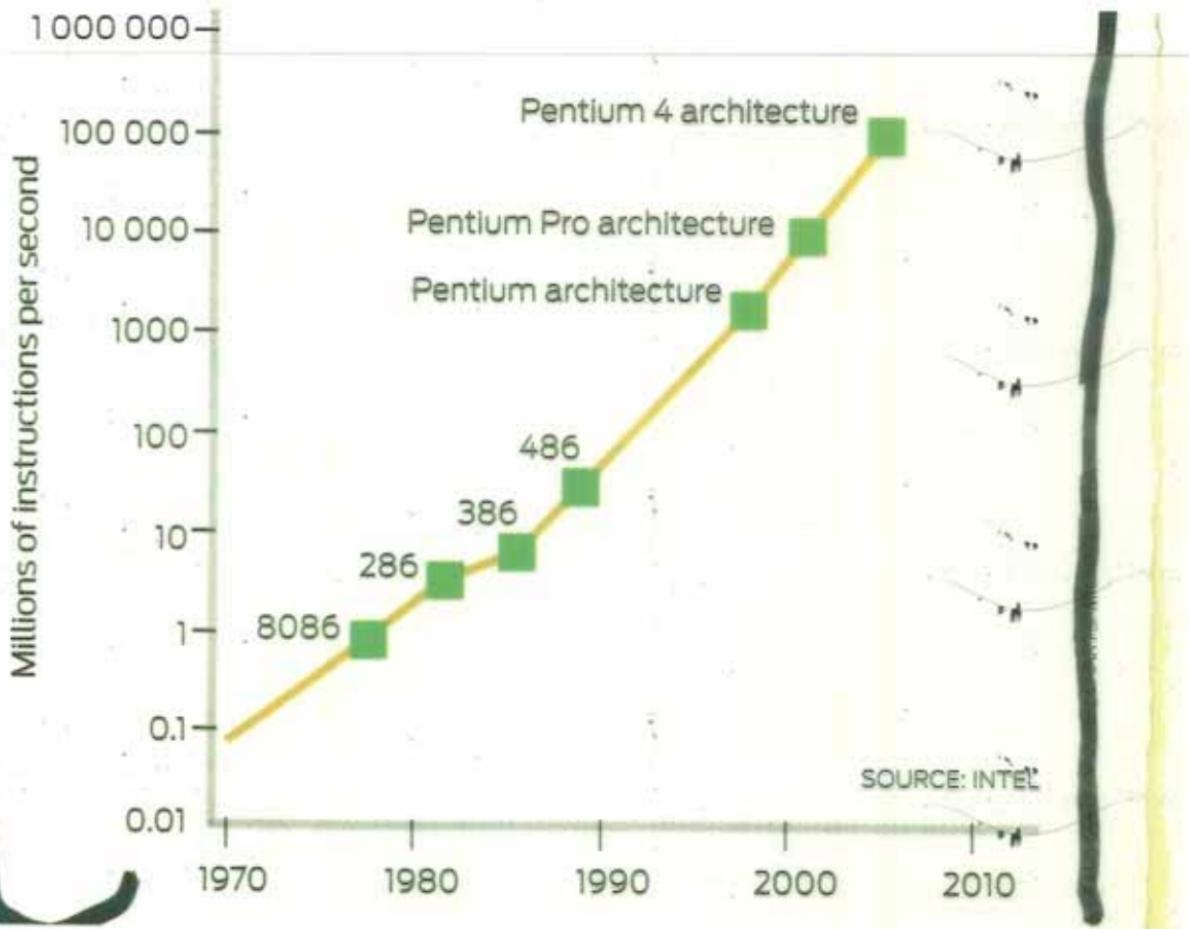

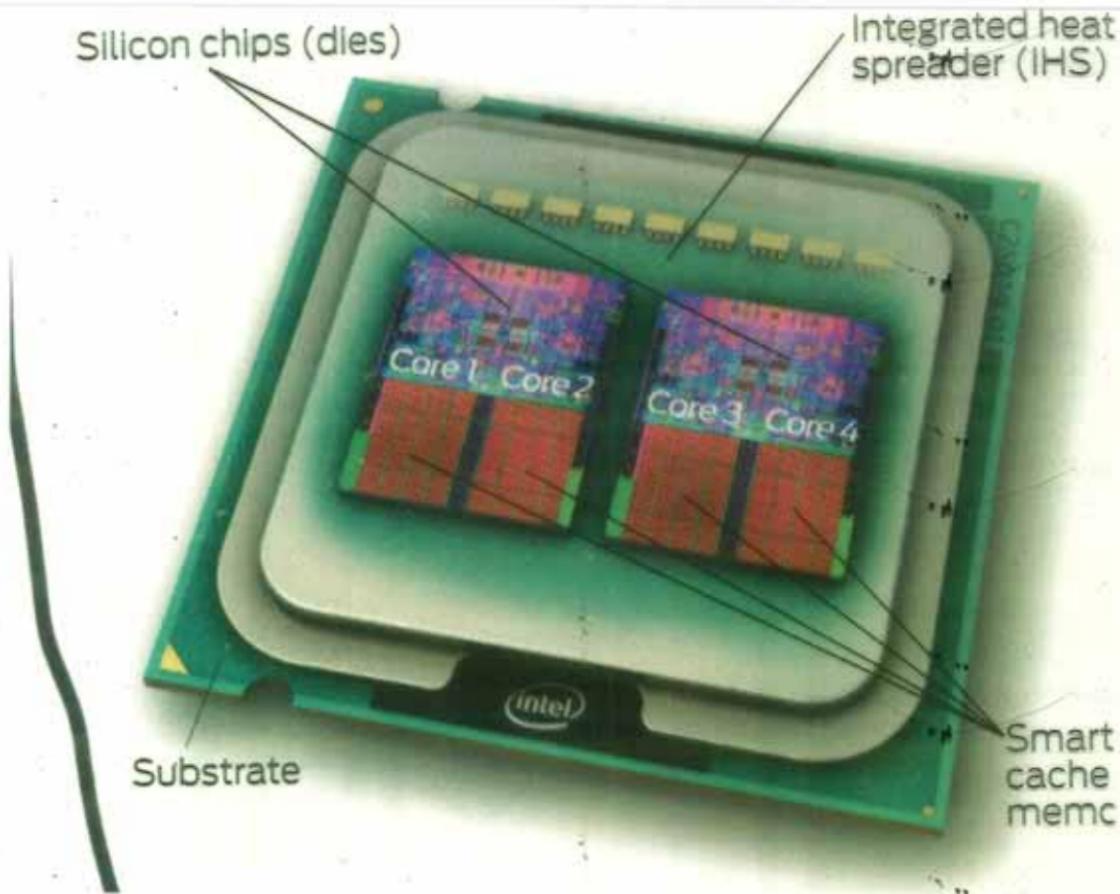

Parallel Paths

Chips with multiple processors to speed computing chores

Supplier/chip	Processors	Typical use
Sun Microsystems/UltraSparc T1	8	Managing Web applications
IBM, Sony, Toshiba/Cell	9	PlayStation 3 game console
Cavium Networks/Octeon	16	Data storage networks
Azul Systems/Vega	48	Accelerating Java software
Intel/Teraflops chip	80	Research
Rapport/KC256	256	Image processing
PicoChip/PC102	302	Wireless communications

Sources: the companies

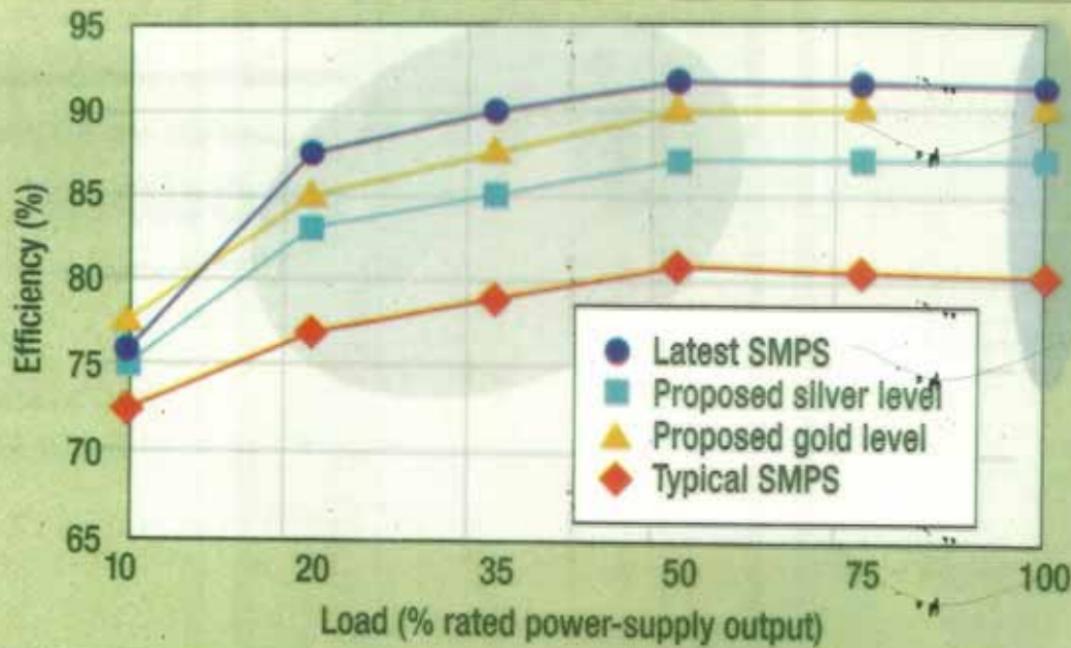


Fig. 1. In some computing and telecom applications, power supplies are now expected to meet targets for efficiency in the 10% to 50% load range, while still achieving high efficiency at full load.^[1]

Why Resonant Converters?

PWM Converters are limited in efficiency as few \uparrow MHz


$$P_{\text{loss}} = [\text{DC + fixed}] + f_{\text{sw}} \frac{E_{\text{sw}}}{\text{sw}}$$

Can be trended to zero if:

- ① Employ ④ ZVS zero voltage switching
- ② ⑤ (ZCS) zero current switching
- ③ ① requires changing from D-Waves, B-Waves, trapezoid-waves

to

Sinusoids

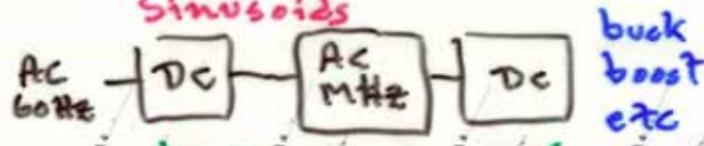

> 96% efficient


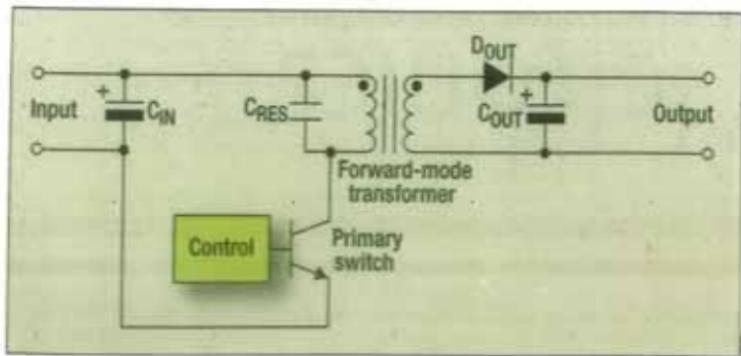


Fig. 1. Key components of the RDFC resonant topology include a bipolar junction transistor as the primary switch and resonant capacitor (C_{RES}), which resonates with the transformer magnetizing inductance to achieve fully resonant switching.

Subtle fix to PWM
use (resonant) switching

ECE 564

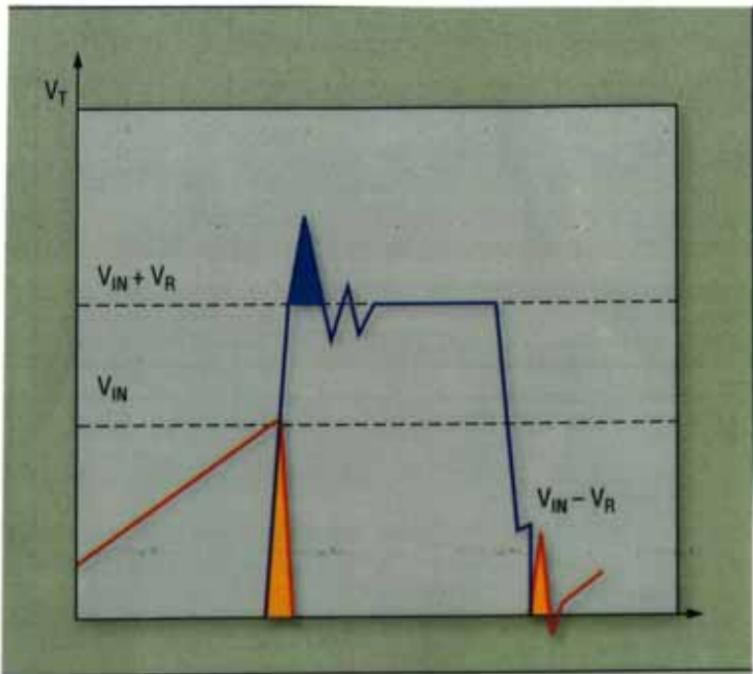

p.2. In a valley switching or quasi-resonant topology, the power transistor is turned on after leakage-inductance demagnetization, when circuit resonance causes a dip in the voltage across the transistor.

the meter's power requirements by up to 10 times, pushing consumption of the meter's electronics as high as 20 W.

As mentioned previously, electric-energy metering

	frequency	wavelength
60 Hz		5000 km (3107 mi)
3 kHz		100,000 m
30 kHz		10,000 m
300 kHz		1000 m
3 MHz		100 m
30 MHz		10 m
300 MHz		1 m
3 GHz		10 cm
30 GHz		1 cm
300 GHz		0.1 cm

PWM

resonant


The electrical dimensions of a device or circuit are determined by comparing physical dimensions to wavelength. A device with length l has electrical dimensions (in wavelengths)

$$d_e = \frac{l}{\lambda}$$



Pepper . . . And Salt

THE WALL STREET JOURNAL

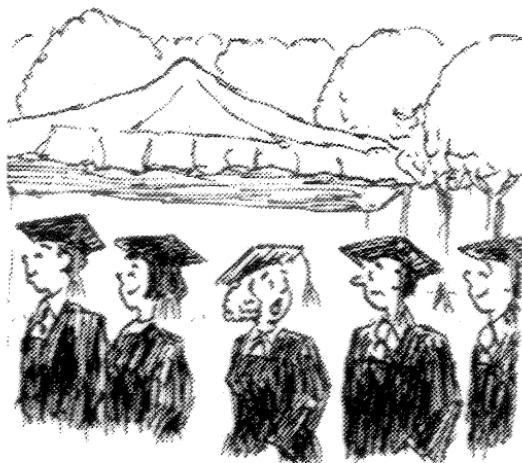

*"Another hour and
we'll be unemployed."*

Graphical Guide: $Z(f)$

Semilog scale vs f

$\log Z$ vs f (linear)

$$\begin{array}{ccc} \text{base or} & 10\Omega & \rightarrow 20 \text{db} \\ \text{per unit} & 1\Omega & \xrightarrow{\uparrow \times 10} 0 \text{db} \\ \text{employed} & \frac{1}{10} & \xrightarrow{\downarrow \div 10} -20 \text{db} \end{array}$$





$20 \log \frac{Z}{1} \Rightarrow Z=1 \text{ is } 0 \text{ db}$
could be $Z=50$ is 0 db

Recall also the



$$\pm 3 \text{db} \left\{ \begin{array}{l} -3 \text{db} \rightarrow \frac{1}{\sqrt{2}} \text{ of base} \\ +3 \text{db} \rightarrow \sqrt{2} \text{ of base} \end{array} \right.$$

$$\pm 6 \text{db} \left\{ \begin{array}{l} -6 \text{db} \rightarrow \frac{1}{2} \text{ of base} \\ +6 \text{db} \rightarrow 2 \text{ of base} \end{array} \right.$$

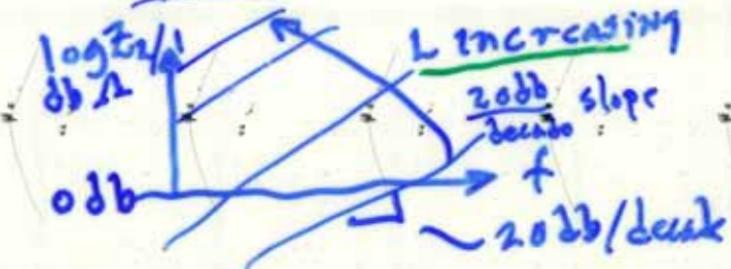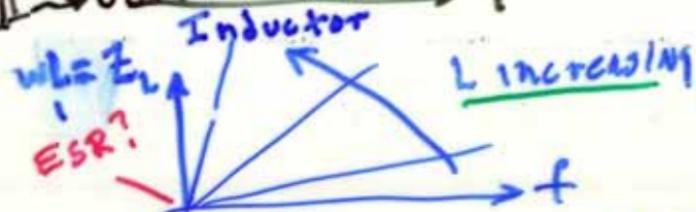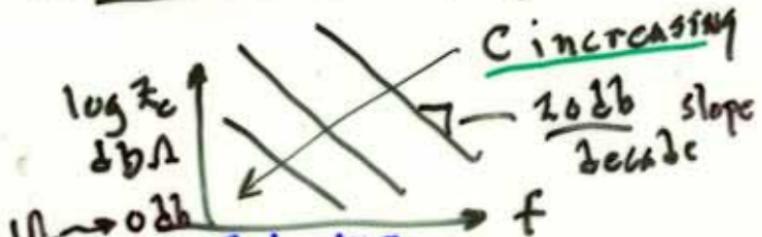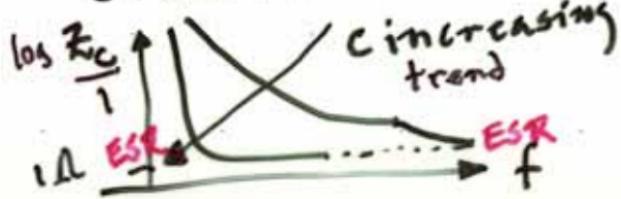Ultra Basics: $\log Z_C = \frac{1}{\omega C}$



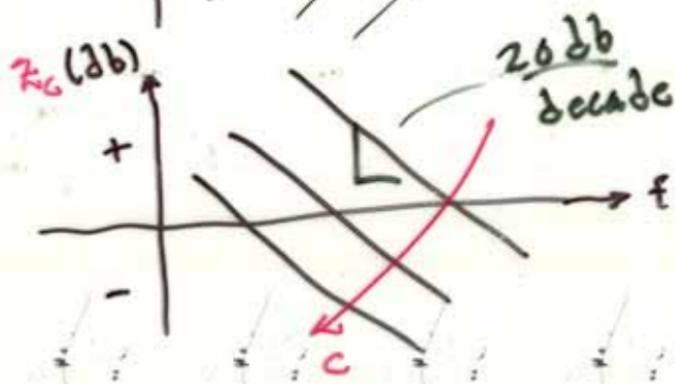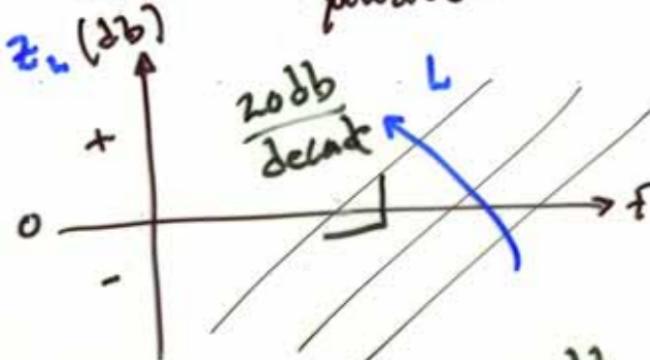
Base impedance could be
50 Ω in rf
circuits




R-C and R-L Circuits

$$\frac{Z_R}{\text{base}} \quad \frac{Z_C}{\text{base}} \quad \frac{Z_L}{\text{base}}$$

odd when $|Z| = \text{base}$

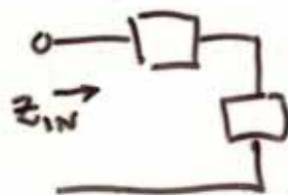

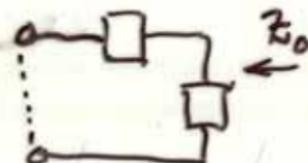
Series case
always take
the largest
at any f



Parallel Case
always take
the smallest
at any f

$$Z_R = Z_C \rightarrow R = \frac{1}{\omega C} \rightarrow \omega = \frac{1}{RC}$$

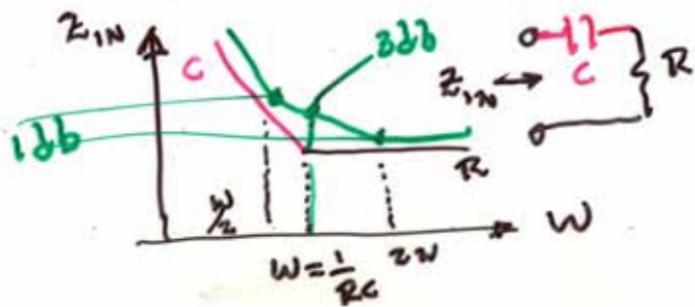
$$Z_R = Z_L \rightarrow R = \omega L \rightarrow \omega = \frac{R}{L}$$




3 db point @ w break

1 db points @ $\frac{w}{2}$

For the circuit $\frac{m}{L}$

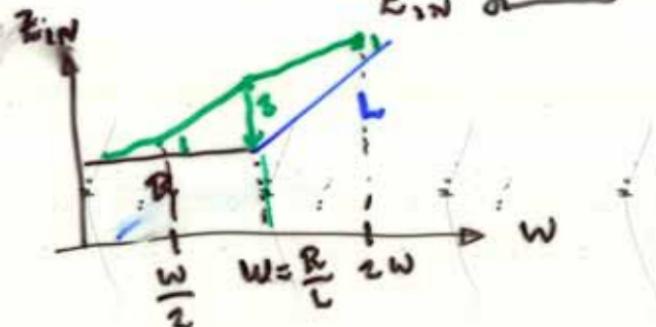


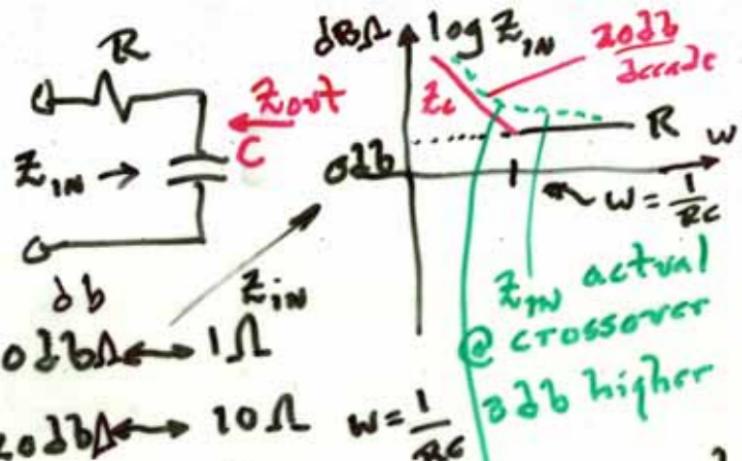


$f = \frac{1}{2\pi RC}$ from asymptotes
 Series elements take the largest.
 Recall from asymptotes

$$f = \left\{ \begin{array}{l} 2f_{\text{cross}} \\ \frac{1}{2}f_{\text{cross}} \end{array} \right\} \text{from asymptotes}$$

$$Z_{out} = R \parallel C$$

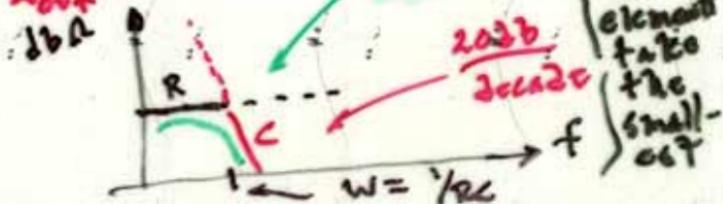

Key Benchmark

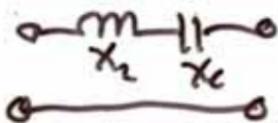

Resonance occurs when

$$X_L = X_C$$

$$f_R = \frac{1}{2\pi\sqrt{LC}}$$

Characteristic Impedance: Z_0

$$Z_0 = X_L(f_R) = X_C(f_R)$$

$$Z_0 = \sqrt{\frac{L}{C}}$$




Always take in series the largest term

#1 $R > Z_C$

$$f < f_R < f_{RL}$$

$$\frac{1}{RC} \quad \frac{1}{RL}$$

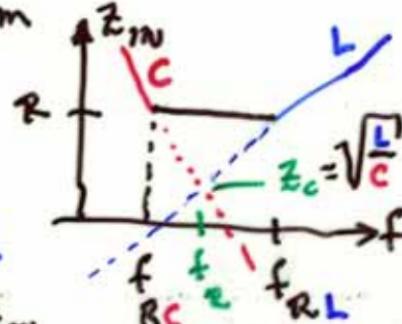


#2 $R < Z_L$

$$f < f_R < f_{RC}$$

$$\frac{1}{RL} \quad \frac{1}{RC}$$

$$Q = \frac{Z_C}{R}$$

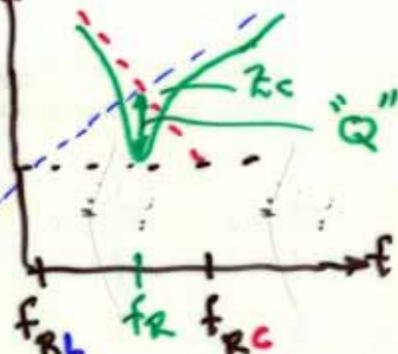

Q'ing Up of a circuit

depends on:


1) Circuit Topology

2) $|Z_C|$ vs R

3) $Q \sim \frac{Z_C}{R}$ Series
L-R-C

$Q \sim \frac{R}{Z_C}$ Parallel
R-L-C

Insight

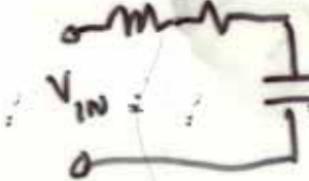

$$I_{IN} = \frac{V_{IN}}{Z_{IN}}$$

V_{out} minimum @ f_R
 $V_o = I_{IN} Z_C$
 V_{out} maximum @ f_R

Chapter 19 Resonant Conversion

Introduction

crawling but insightful
for "general trends"

19.1 Sinusoidal analysis of resonant converters

19.2 Examples

Series resonant converter

Parallel resonant converter

$V_{out}(f)$, V_{IN} , L, C
range of V_{out} , i_{tank}

19.3 Exact characteristics of the series and parallel resonant converters

19.4 Soft switching

Zero current switching

Zero voltage switching

The zero voltage transition converter

19.5 Load-dependent properties of resonant converters

Surprise $R_L \rightarrow \infty$ $i_{sw} \uparrow$
for Naric

Chapter 19

Resonant Conversion

Introduction

19.1 Sinusoidal analysis of resonant converters

19.2 Examples

Series resonant converter

Parallel resonant converter

19.3 Exact characteristics of the series and parallel resonant converters

19.4 Soft switching


Zero current switching

Zero voltage switching

The zero voltage transition converter

19.5 Load-dependent properties of resonant converters



Resonant circuit displays $Q(R)$


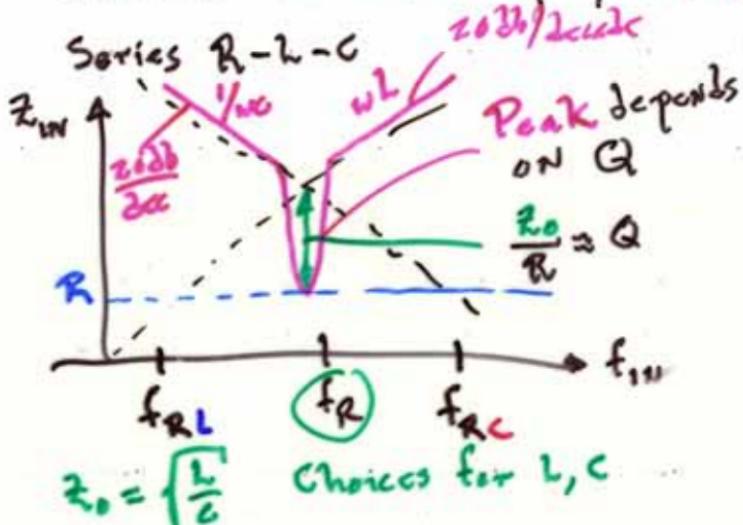


R is series resistance

$$R = R_L + \underbrace{R_L(\text{ESR}) + R_C(\text{ESR})}_{\text{limits } Q_{\max}}$$

$$Z_0(f_R) = R$$

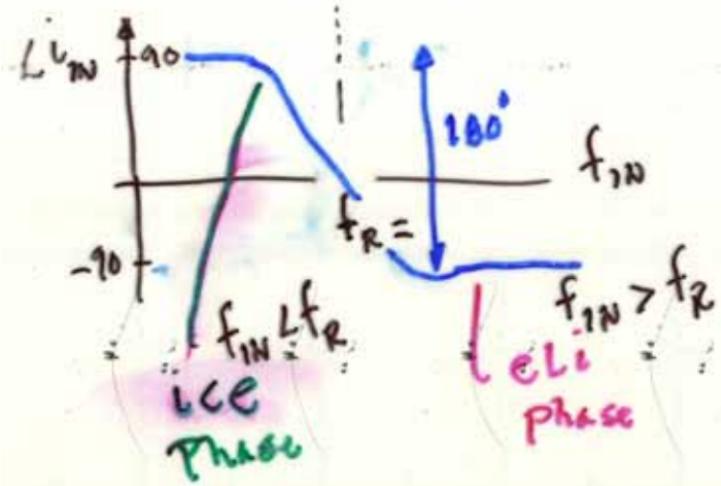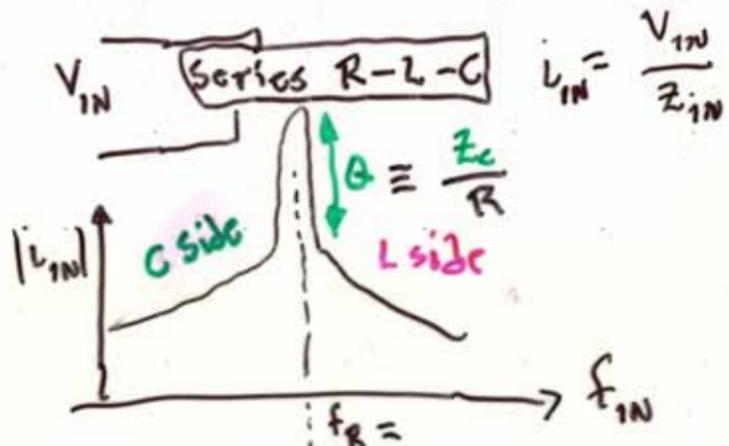

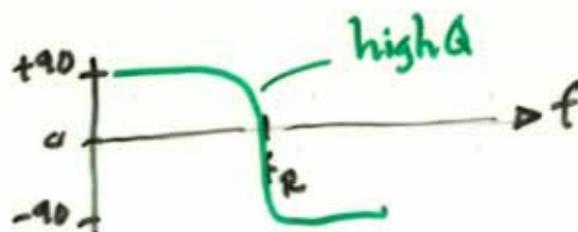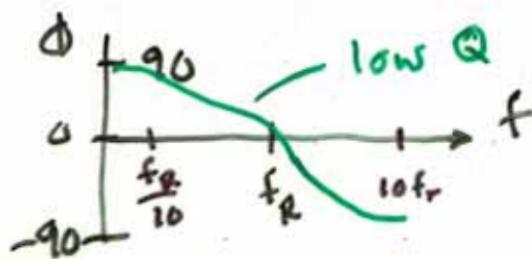


Slope of phase $= \frac{-180^\circ Q}{\text{decade}}$

$$Q = \frac{1}{2} \quad \frac{180^\circ \text{ change}}{\text{two decades}}$$

$$\therefore Q = 1 \quad \therefore \frac{180^\circ \text{ change}}{\text{decade}}$$

$$Q = 5 \quad \frac{180^\circ \text{ change}}{\text{octave}}$$

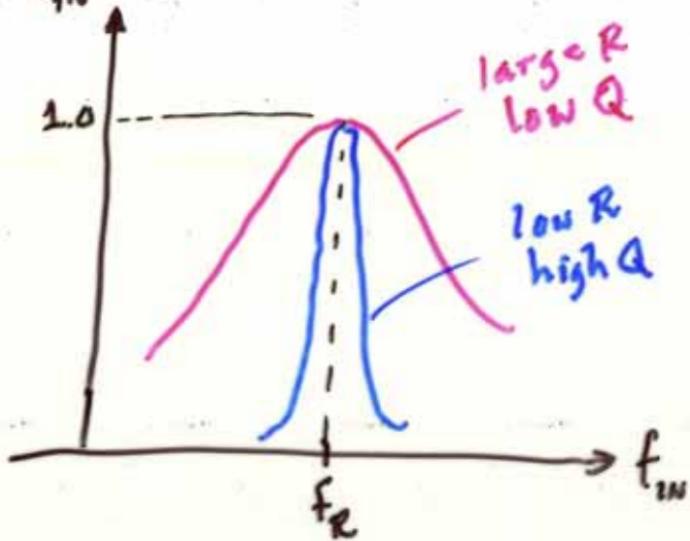$\frac{V_o}{V_{in}}$ (linear scale) take V_{out} across R



$f_{in} \neq f_R$ Buck Circuit

In resonant converters:

$\frac{V_o(t)}{V_{in}(t)}$ set by f choice
VCO for feedback!



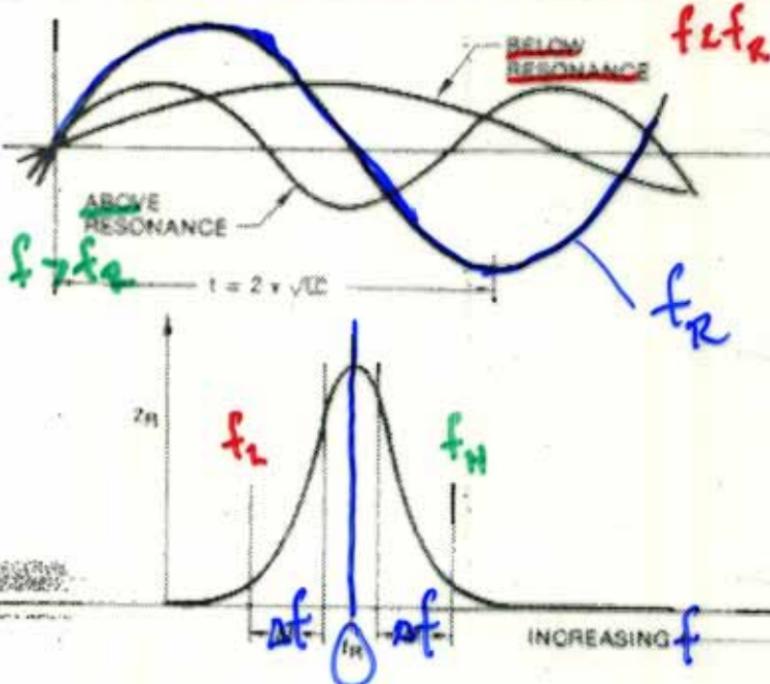
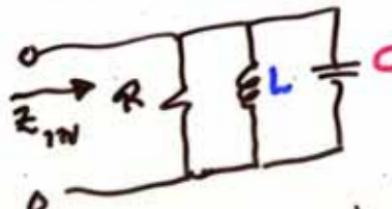


Fig. 11 - Variable Frequency Continuous Resonance

Parallel Resonant Circuit

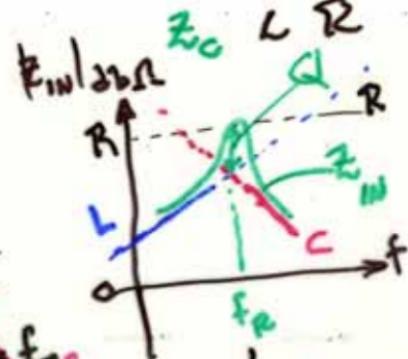

Two cases:
R w.r.t. Z_C


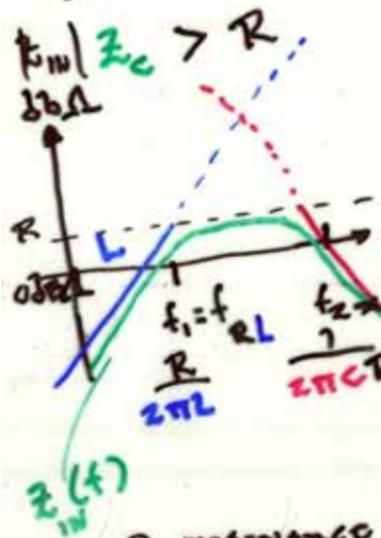


$$Q = \frac{R}{Z_C}$$

$$\text{@ resonance } Z_C \parallel Z_L = \frac{Z_0 Z_L}{Z_0 - Z_L} \rightarrow \infty$$

$$\Rightarrow Z_{IN} = R \parallel \infty = R$$

$V_{out} = V_{IN}$ for all f BUT

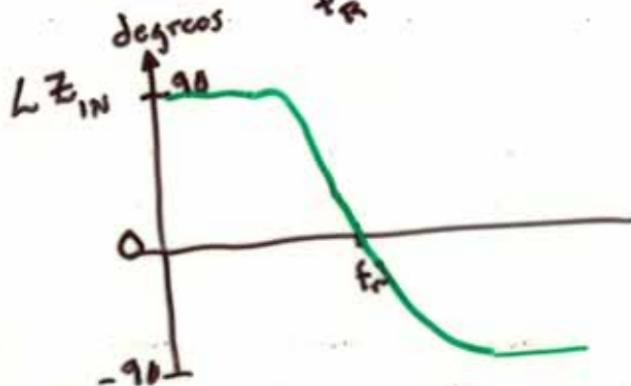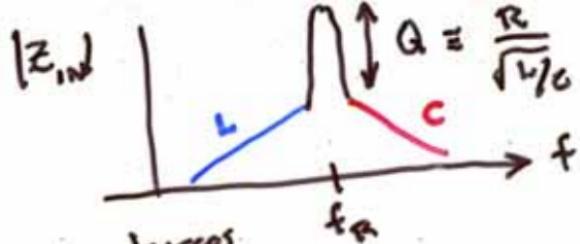


$\gamma_{Z_{IN}} = V_{IN} / Z_{IN}$

L

C

f_R

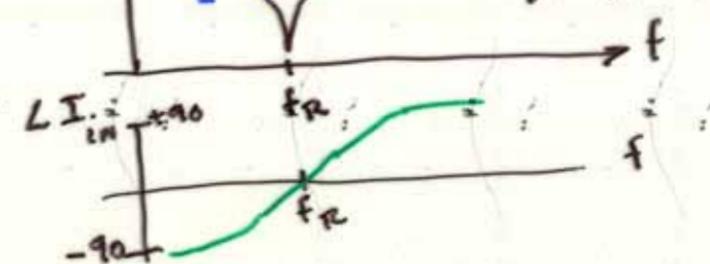
low I_{IN} @ f_R
high I_{IN} $f \neq f_R$



DC → DC

Derivation of a resonant dc-dc converter

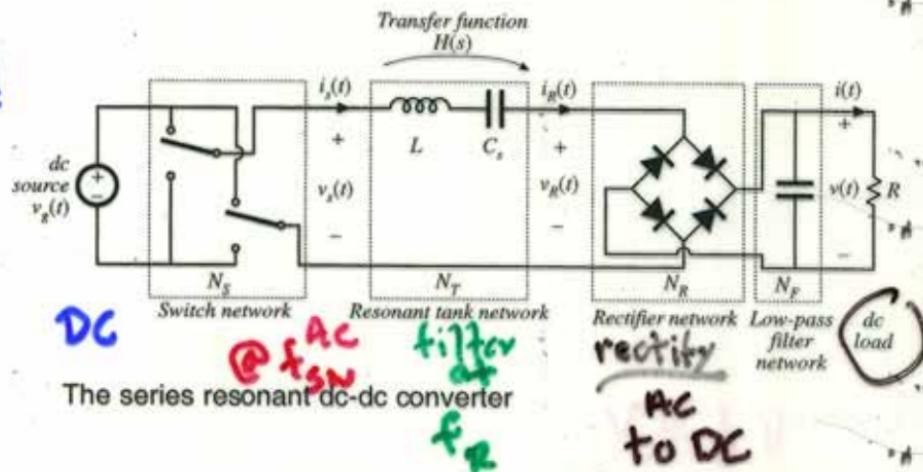
Rectify and filter the output of a dc-high-frequency-ac inverter



Solve diode loss for low Vout


A series resonant link inverter

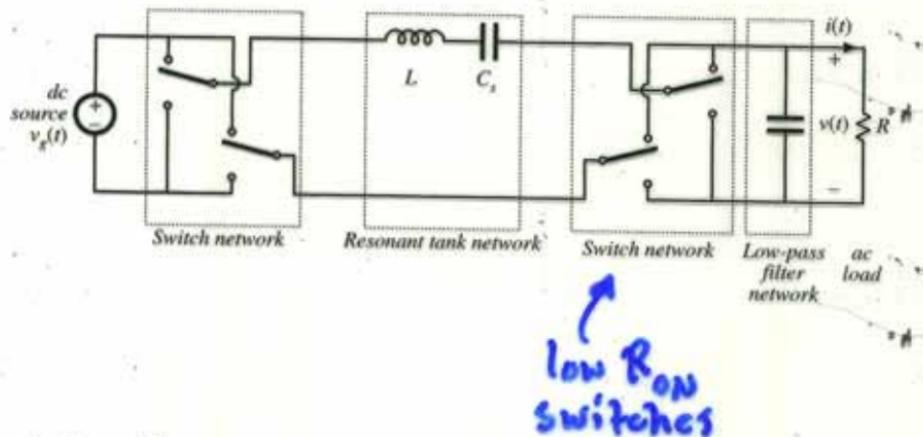Same as dc-dc series resonant converter, except output rectifiers are,
replaced with four-quadrant switches:




19.2 Examples

19.2.1 Series resonant converter

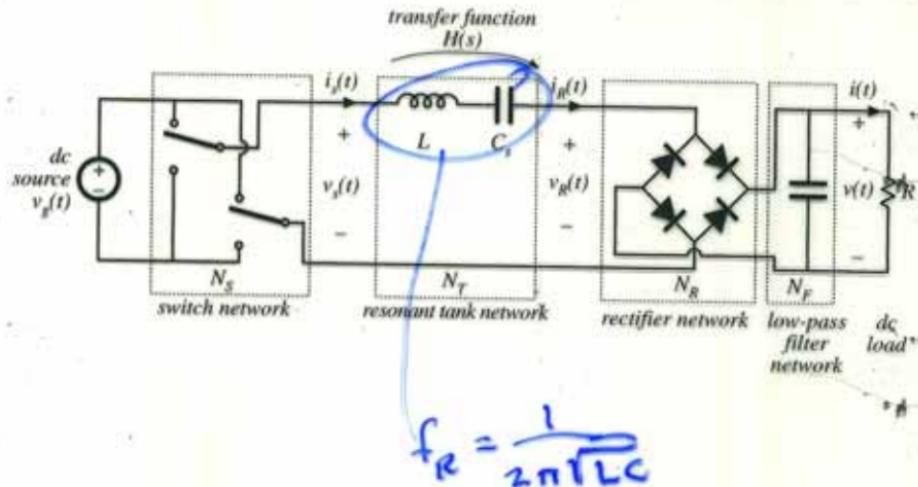

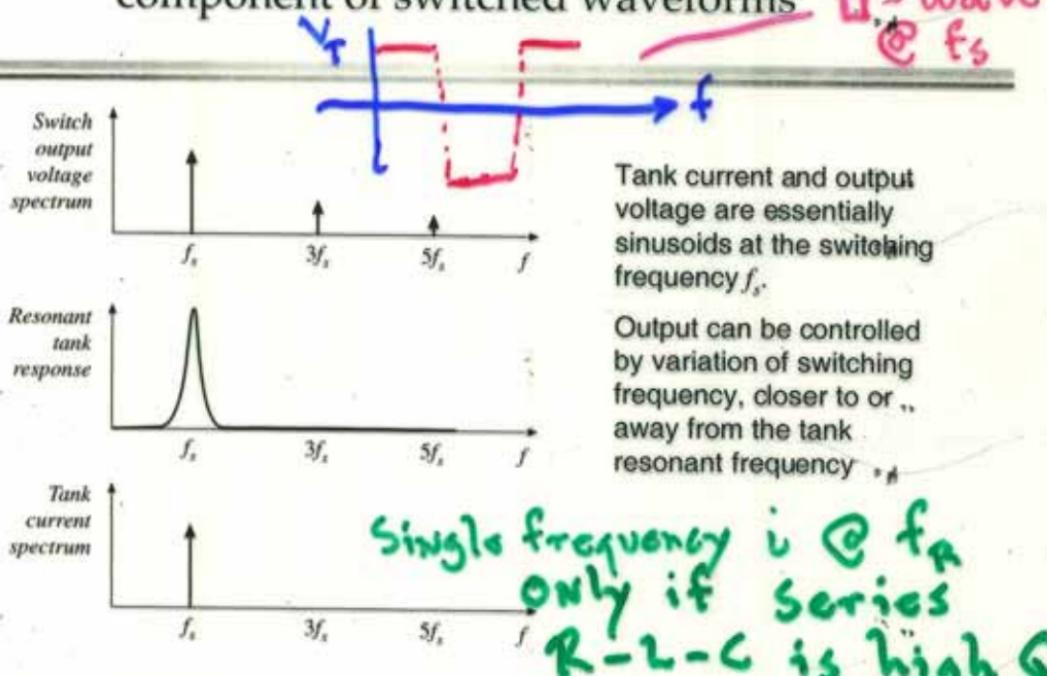Tank network responds only to fundamental component of switched waveforms




Power Electronics 3

1/5

564 Lecture 3 $Z(s)$

Up:


Page 1

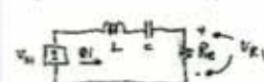

$$R(s) = \frac{V_{R1}(s)}{V_{S1}(s)}$$

Put $\frac{V}{V}$
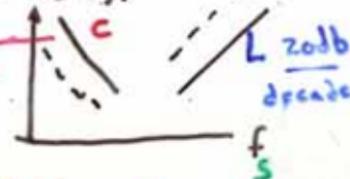
$$R(s) = \frac{R_o}{Z(s)} \quad Z(s) = sL + \frac{1}{sC} + R_o$$




$$|Z_c| = \frac{1}{\omega C}$$

$$|Z_L| = \omega L$$

$$Z_c = Z_L @$$

$$\omega_R = \frac{1}{\sqrt{LC}}$$

Page 2

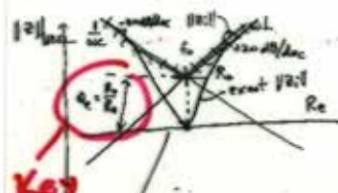

$$|Z_c| = |Z_L| @ \omega_R$$

$$= Z_0 = \sqrt{\frac{L}{C}}$$

Page 3


Case: $R_o < Z_0$

$$Z_i(\omega_R) = ?$$

$$R_0 = \sqrt{L/C}$$

Construction of Z_i

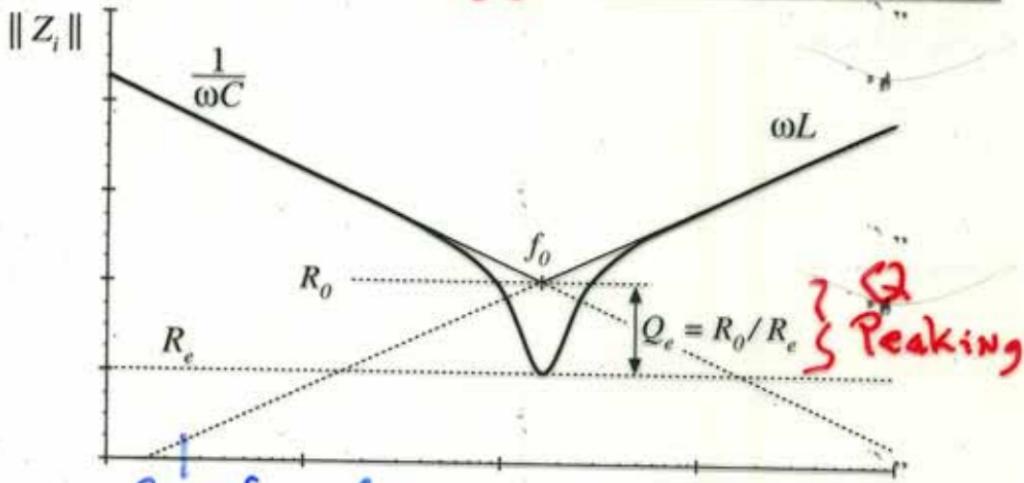Series RLC: $Z_i = sL + \frac{1}{sC} + R_e$



$$f_{SW} = \frac{f_0}{\sqrt{3}}, \frac{f_0}{5}$$

resonance


both missing
In case of π -wave V_{IN} will appear

$$\begin{aligned}
 & \text{at } f_0: \quad \omega_0 = 2\pi f_0 \\
 & R_L = \frac{1}{j\omega_0 C} = \omega_0 L \quad \Rightarrow \omega_0^2 = \frac{1}{LC} \\
 & \quad \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \\
 & \text{From Eq 2.11:} \\
 & \text{at } \omega = \omega_0 \\
 & Z_i(j\omega) = j\omega L + \frac{1}{j\omega C} + R_L = jL + \frac{R_L}{j\omega} + R_L \\
 & \quad = R_L
 \end{aligned}$$


Z_C cancels Z_L

Page 4

$$\frac{V_R}{V_{IN}} = \frac{R_L}{Z_i} = M = \frac{V_{out}}{V_{sig}}$$

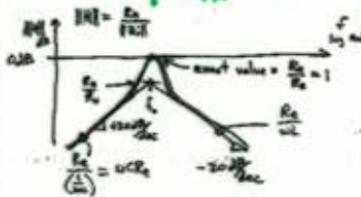

Page 5

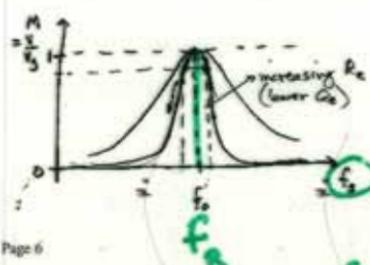

$$Q = \frac{Z_0}{R} = \frac{\sqrt{\frac{L}{C}}}{R}$$


$$Q = \frac{j\omega_0}{R} \sqrt{\frac{L}{C}} = \frac{1}{\omega_0 C R} = \frac{1}{w_R C R}$$

Page 6

$$\text{Define } \frac{f_S}{f_R} = F$$

$$H_{ab} = [R_{eb} - R_i]_{ab}$$

Construction of $H = \frac{R_e}{Z_i}$

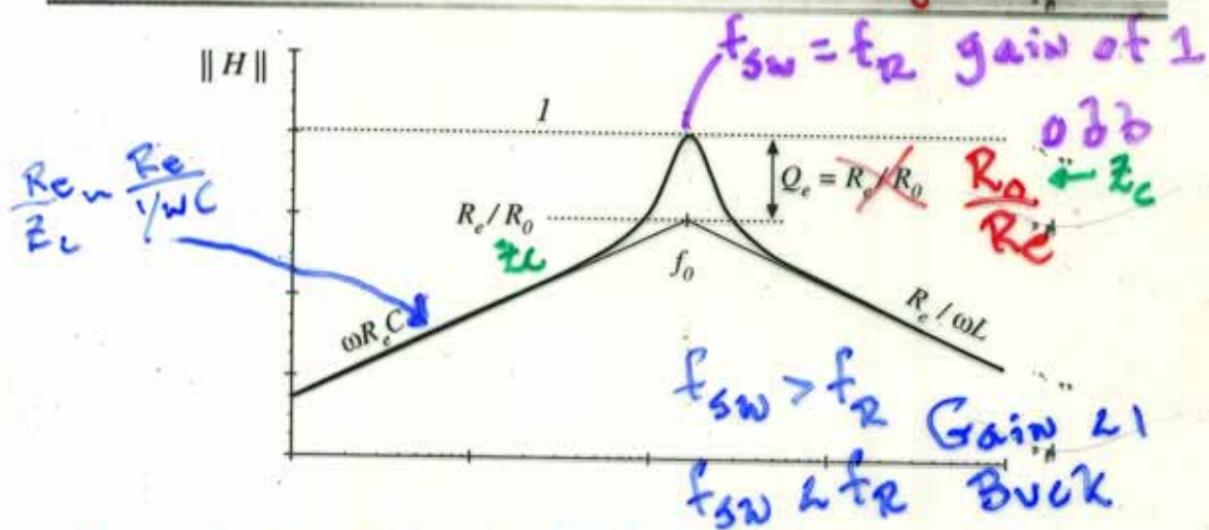

$R_{load} \rightarrow \infty$ Gives DCM which is not predicted by simple sine analysis

Fundamentals of Power Electronics 27 Chapter 19: Resonant Conversion

$R_{load} \rightarrow \infty \Rightarrow \text{low } Q \text{ assumption violated}$
need harmonics for validity

Equation of M vs F

$$M = \frac{V}{V_s} \quad F = \frac{f_s \omega}{f_o \omega} = \frac{\omega_s}{\omega_o}$$

$$M = |H(j\omega_s)| \quad \omega_s = 2\pi f_s$$

$$H(j\omega_s) = \frac{R_o}{j\omega_s L + \frac{1}{j\omega_s C} + R_o}$$

$$= \frac{V_o}{V_{\text{signal}}}$$

3/5

Page 7

$$= \frac{j\omega_s C R_o}{(j\omega_s L)(j\omega_s C) + 1 + j\omega_s C R_o}$$

$$= \frac{j\omega_s C R_o}{1 + j\omega_s C R_o - \underbrace{\omega_s^2 L C}_{\frac{Q_o}{\omega_o^2} = F}}$$

$$= j \frac{F}{Q_o}$$

$$\frac{V_o}{V_s} = f(F, Q)$$

$$W_o = W_R \sqrt{L/C}$$

Page 8

$$Q_o = \frac{R_o}{R_e} = \frac{1}{\omega_s C R_e}$$

$$\Rightarrow C = \frac{1}{\omega_s R_e Q_o}$$

$$\therefore j\omega_s C R_e = \frac{j\omega_s R_e}{\omega_s R_e Q_o} = j \frac{\omega_s}{\omega_o} \frac{1}{Q_o}$$

$$R_o = \sqrt{L/C} \quad \left. \begin{array}{l} Q = W_R R \\ W_o = \frac{1}{\sqrt{L/C}} \end{array} \right\} = \frac{1}{W_R C R}$$

Page 9

$$\begin{aligned}
 H(j\omega_s) &= \frac{j\frac{F}{Q}}{1 - F^2 + j\frac{F}{Q_0}} \\
 M = \|H(j\omega_s)\| &= \frac{\left\| j\frac{F}{Q_0} \right\|}{\left\| 1 - F^2 + j\frac{F}{Q_0} \right\|} \\
 &= \frac{\left(\frac{F}{Q_0} \right)^2}{\sqrt{(1 - F^2)^2 + \left(\frac{F}{Q_0} \right)^2}}
 \end{aligned}
 \quad \left. \right\} \frac{V_{out}}{V_{in}} \quad 4/5$$

Page 10


$$M = \frac{1}{\sqrt{1 + \frac{Q_0^2}{F^2} (1 - F^2)^2}}$$

$$M = \frac{1}{\sqrt{1 + Q_0^2 \left(\frac{1}{F} - F\right)^2}}$$

Page 11



Model: series resonant converter

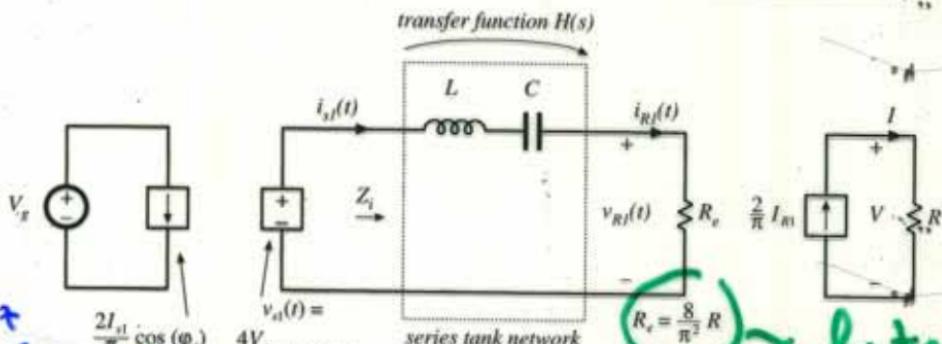

$$H(s) = \frac{R_e}{Z_i(s)} = \frac{R_e}{\frac{R_e}{s} + s_C + \frac{1}{sL}}$$

$$= \frac{\left(\frac{s}{Q_e \omega_0}\right)}{1 + \left(\frac{s}{Q_e \omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$

std.
form

$$\omega_0 = \frac{1}{\sqrt{LC}} = 2\pi f_0$$

$$R_0 = \sqrt{\frac{L}{C}}$$




$$Q_e = \frac{R_0}{R_e}$$

Series L/C
only


$$M = |H(j\omega_0)| = \frac{1}{\sqrt{1 + Q_e^2 \left(\frac{f_0}{F} - F\right)^2}}$$


$R \uparrow Q \uparrow$
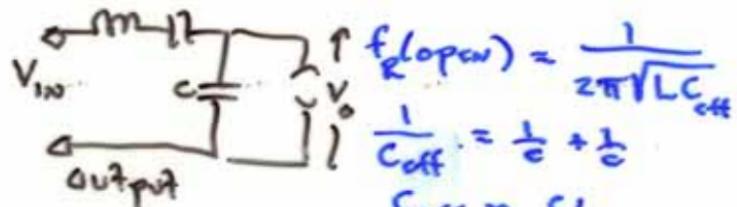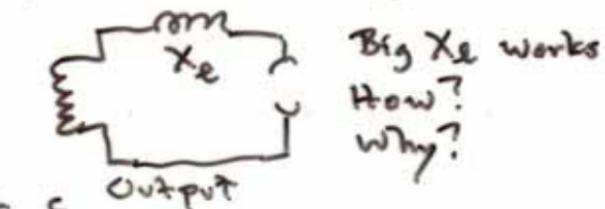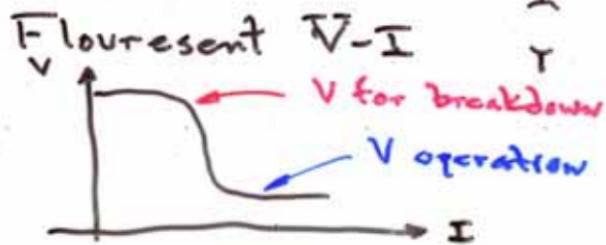
$$Q_e = \underline{\omega_e L} / R_e = \frac{1}{\omega_0 e R_e}$$



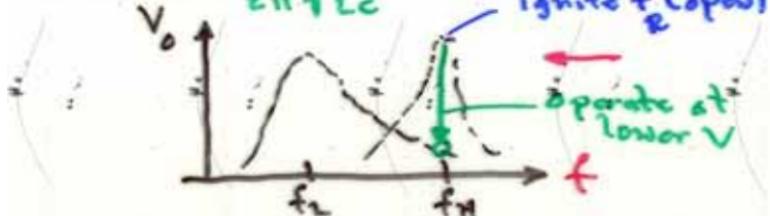$f(\text{short}) = \frac{1}{2\pi\sqrt{LC}}$



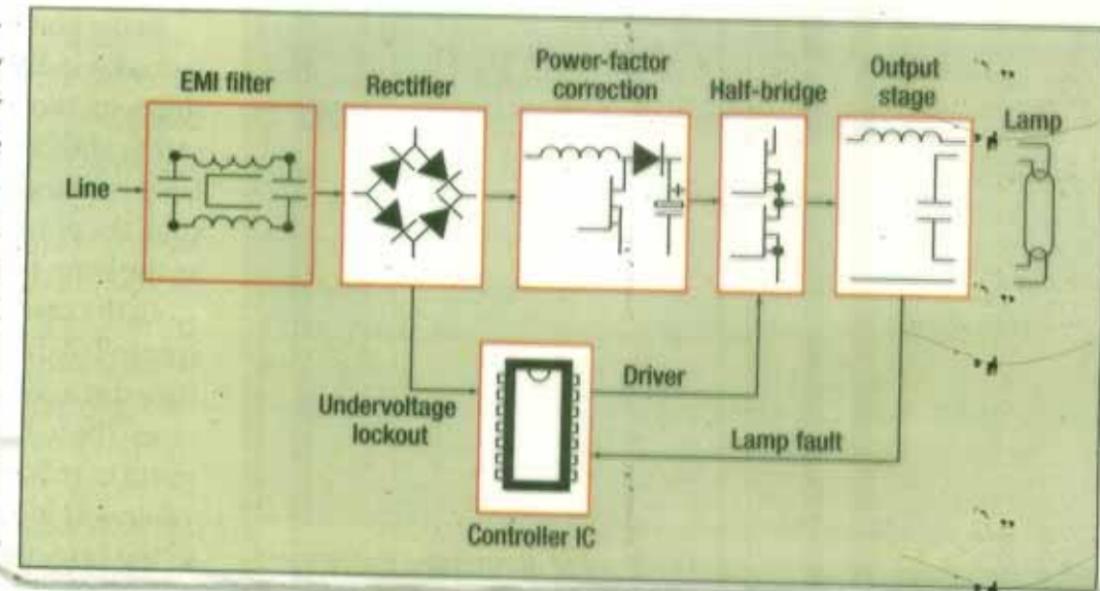

y
y
e
-
l
i
n
s
g


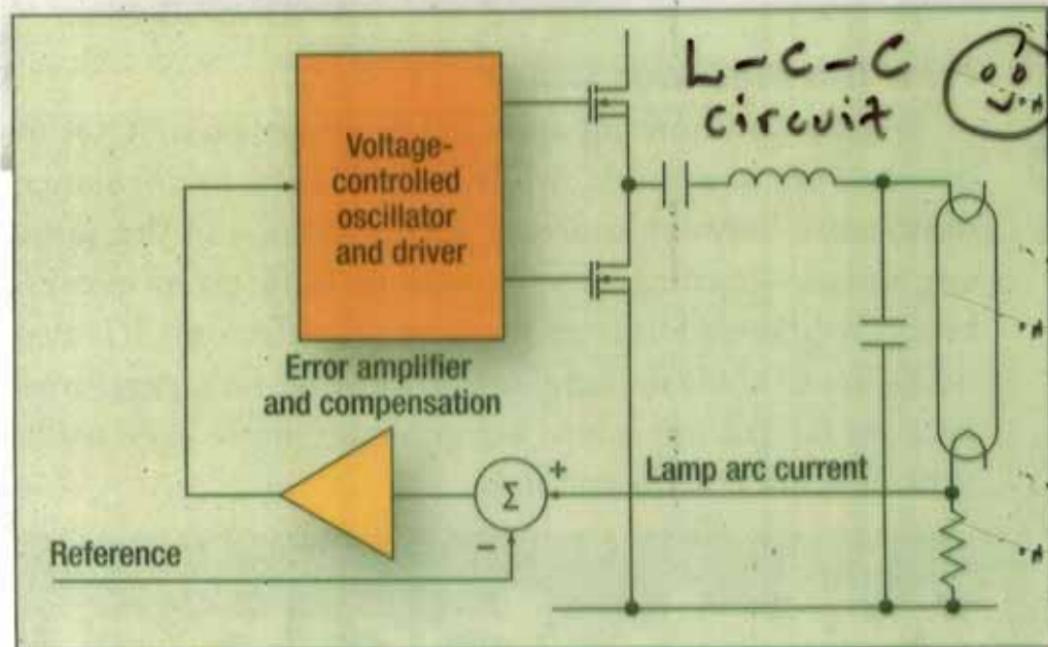


Fig. 3. The analog arc-current control method of dimming a fluorescent lamp's ballast using frequency modulation is generally simpler than the digital approach.

Fig. 1. Dimming fluorescent-lamp ballasts is commonly done by controlling the lamp power by modulating the frequency of the switched dc bus. Results shown here are for single-lamp voltage-mode heating, 90-Vac to 265-Vac input, 500-Vdc output, TC-T 32 W lamp, $L = 4.30 \text{ mH}$ and $C = 3.3 \text{ nF}$.

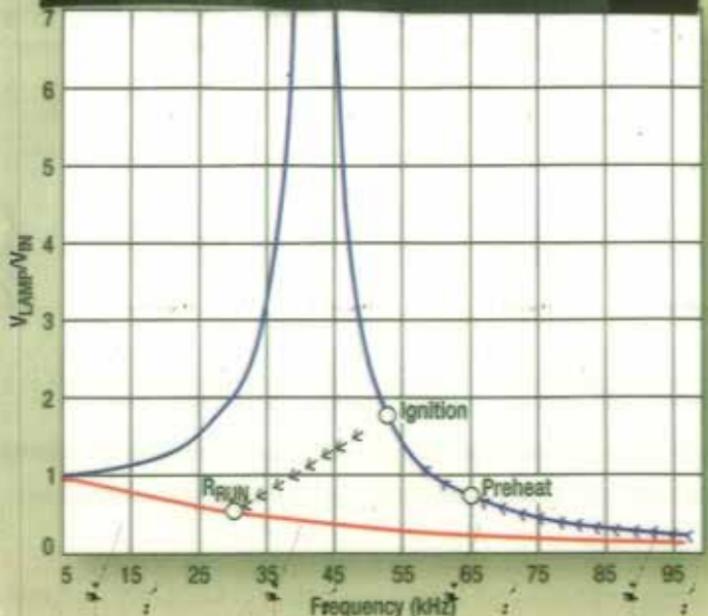

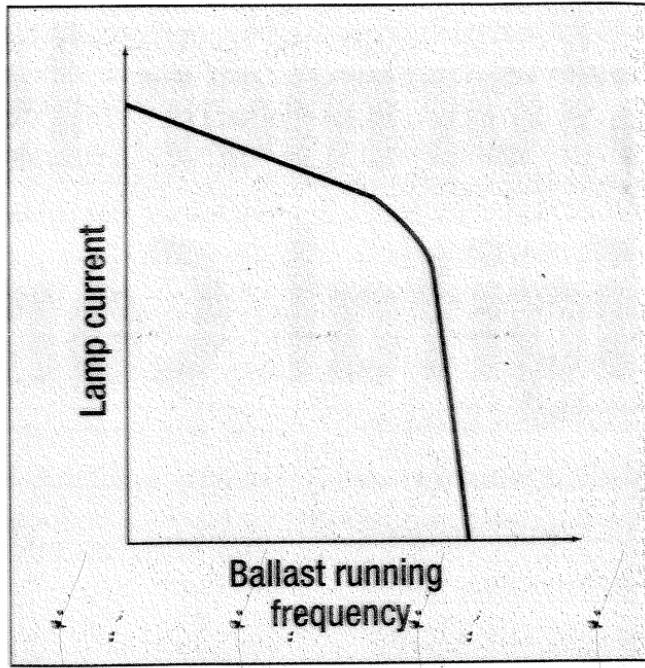


Fig. 7. The increasing frequency of a fluorescent lamp's ballast sharply