

ECE 562

Week 11 Lecture 2

Fall 2008

Week 11 Lecture 2 Summary

Slides	Topic
3-9	RLC circuits and resonance
10-13	Resonant converter principles
14-17	Trends in power electronics
18-336	Switching efficiency
37-44	Zero current and zero voltage switching
45-63	Problem 19.1
64-73	Analysis of resonant converters
74-86	Conversion ratio and filter networks

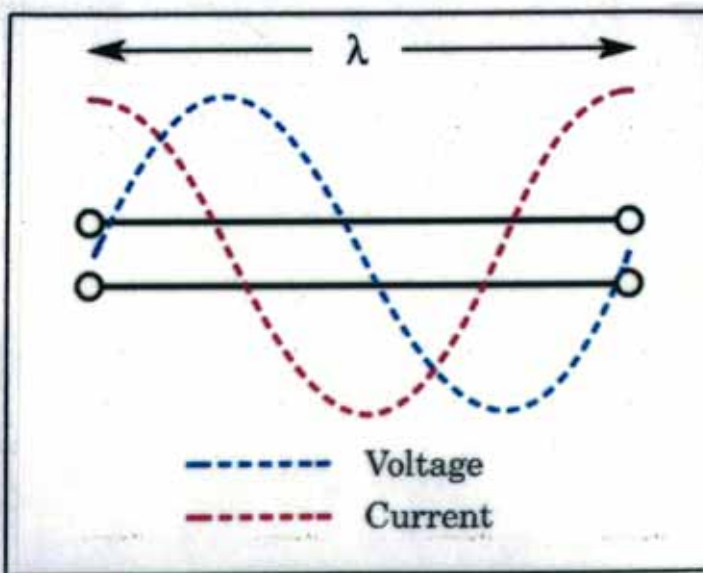


Figure 4 · Voltage and current on a one-wavelength long transmission line.




5 to 20 kHz	<ul style="list-style-type: none"> -AUDIBLE NOISE -SLOW BIPOLAR SWITCHES -LARGE L's AND C's
20 to 100 kHz	<ul style="list-style-type: none"> -ABOVE AUDIBLE RANGE -FAST BIPOLAR TRANSISTOR -MAGNETICS BECOME IMPORTANT -SMALL SIZES
100 to 500 kHz	<ul style="list-style-type: none"> -POWER MOSFET SWITCHES -LOSSES IN L's AND C's -DIODE RECOVERY TIME -RFI AND EMI -PACKAGING PROBLEMS

Fig. 2 - Power Supply Switching Frequencies


Series RLC: 

$$f_{RC} = \frac{1}{2\pi RC}$$


Z_C series with R

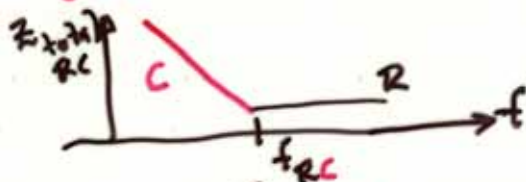


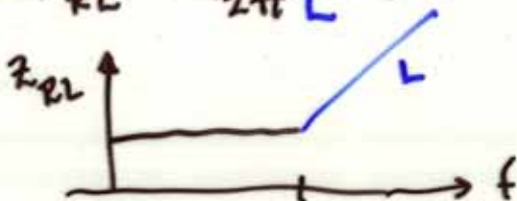
$f_{RL} = \frac{R}{2\pi L}$ Z_L series with R



Finally
R-L-C

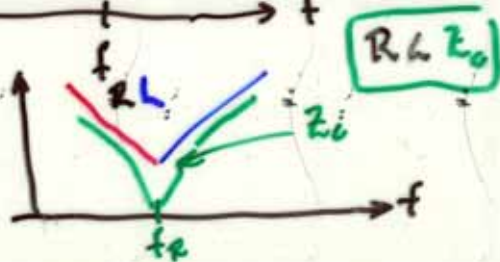

Series RLC

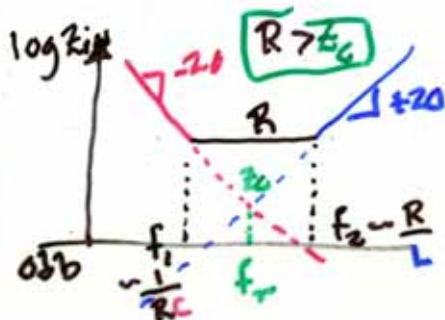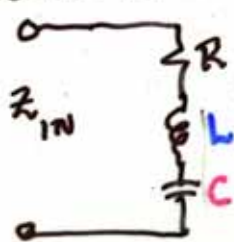

$$f_1 = \frac{1}{2\pi RC}$$

$$f_2 = \frac{R}{2\pi L}$$

$$f_R = ? \quad \left| \frac{1}{\omega C} \right| = |\omega L| @ \omega_R$$


$$\omega_R = \frac{1}{\sqrt{LC}}$$

$$f_R = \frac{1}{2\pi \sqrt{LC}}$$

$$Z_C = Z_L @ \omega_R = \sqrt{\frac{L}{C}} \equiv Z_C$$

Above case for $R > Z_C$

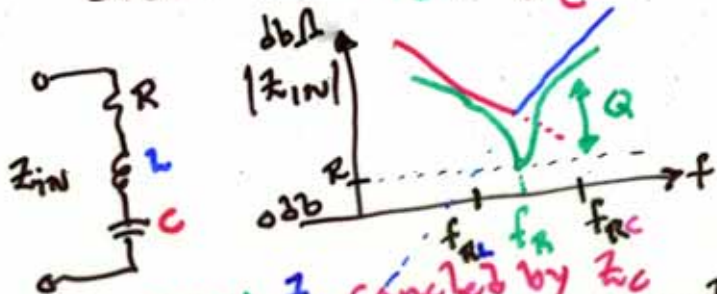Case: $R \ll Z_c \equiv \sqrt{\frac{L}{C}}$




Resonance: Z_L canceled by Z_C


$$Q = \text{Deviation from asymptote @ } f_r$$

$$= \frac{Z_c}{R}$$

$$Q(\omega) = Z_c(\omega) - R(\omega)$$

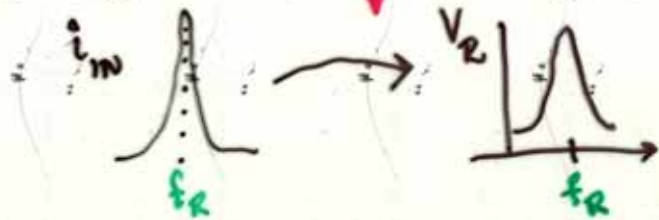If Z_{in} "Q's" down \downarrow then $i_m(t)$?



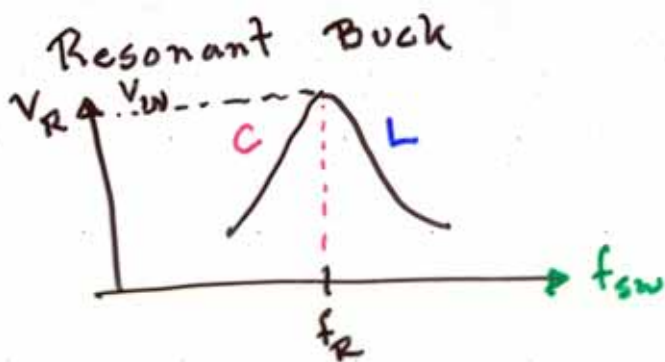

$$f_{sw} = f_R \quad V_R = V_{IN}$$

$$f_{sw} \neq f_R \quad V_R < V_{IN}$$

$f < f_R$: **Capacitive** Buck

BVS for FET

$f > f_R$: **Inductive**

ZCS for FET

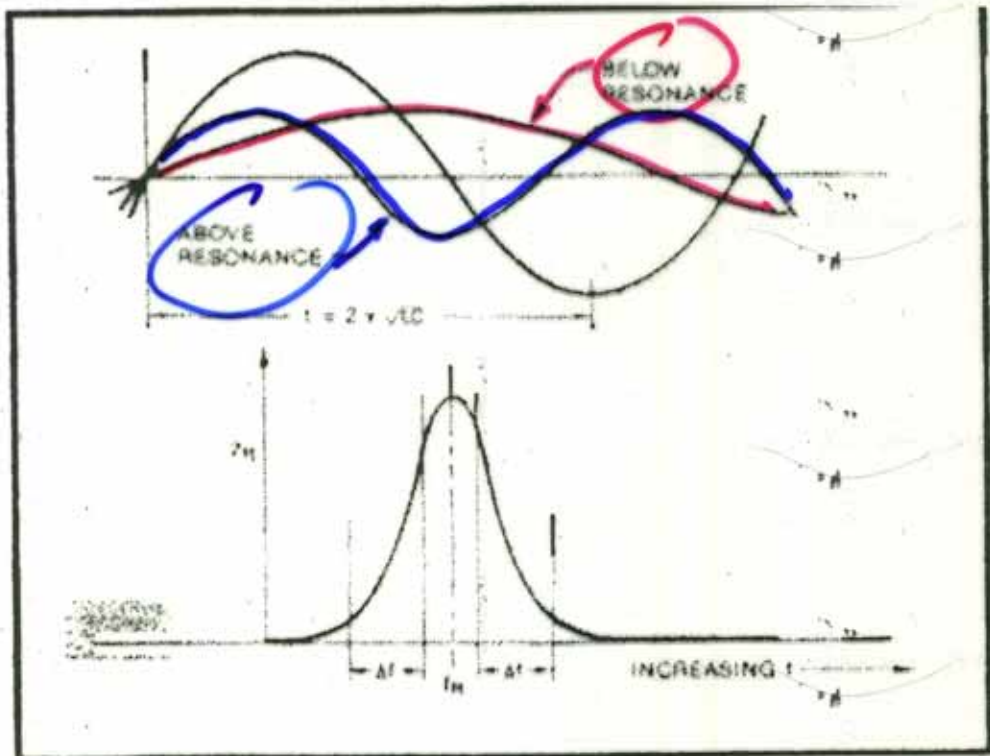


Fig. 11 - Variable Frequency Continuous Resonance

Introduction to Resonant Conversion

Resonant power converters contain resonant L-C networks whose voltage and current waveforms vary sinusoidally during one or more subintervals of each switching period. These sinusoidal variations are large in magnitude, and the small ripple approximation does not apply.

? No small ripple approx.

Some types of resonant converters:


- Dc-to-high-frequency-ac inverters AE $\frac{1}{2}, 2, 13, 60, 160 \text{ MHz}$
- Resonant dc-dc converters AE Pinnacle, Pinnacle Plus
- Resonant inverters or rectifiers producing line-frequency ac

cycloconverters $f \approx 60 \text{ Hz}$




} 461

A basic class of resonant inverters

Basic circuit

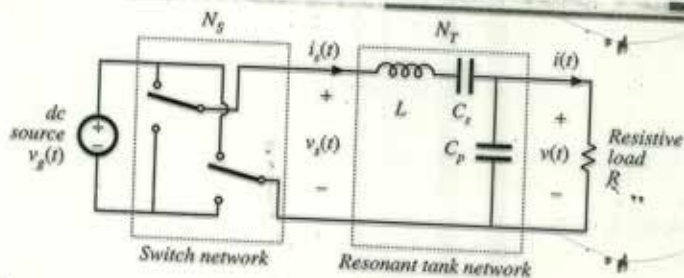

Several resonant tank networks

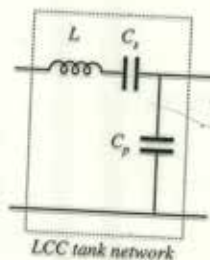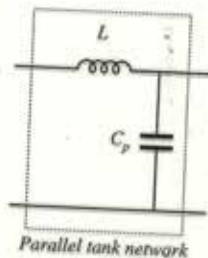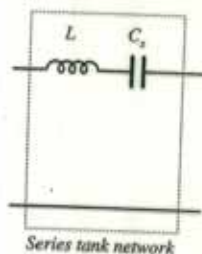

1. SERIES OR PARALLEL LOADED?
2. FIXED OR VARIABLE FREQUENCY?
3. CONTINUOUS / DISCONTINUOUS RESONANCE?
4. ZERO CURRENT OR VOLTAGE SWITCHING?
5. HALF OR FULL CYCLE CONDUCTION?

Fig. 8 - Classifying Resonant Converters

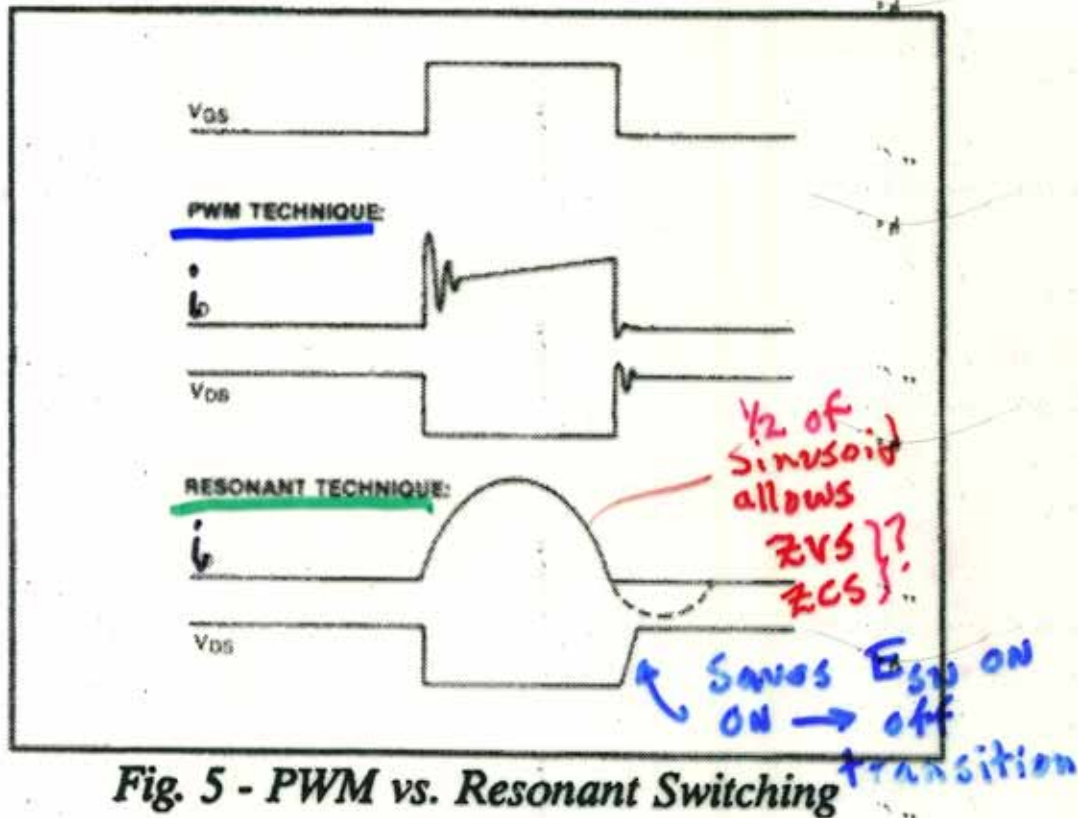


Fig. 5 - PWM vs. Resonant Switching

Trends in the power electronics field

- Improved packaging of semiconductors, to reduce size of control circuitry and power switches. Use of application-specific ICs (ASICs)
- **Increased switching frequencies**, to reduce size of magnetics
- System integration, leading to distributed power supplies having high density

Much R&D effort has been devoted to **high-density power supplies**, including resonant converters and **soft switching** techniques

Introduction to Resonant Conversion

Resonant power converters contain resonant L-C networks whose voltage and current waveforms vary sinusoidally during one or more subintervals of each switching period. These sinusoidal variations are large in magnitude, and the small ripple approximation does not apply.

Some types of resonant converters:


- Dc-to-high-frequency-ac inverters $DC - \begin{matrix} IF \\ RF \end{matrix}$
- Resonant dc-dc converters $- DC - DC$
- Resonant inverters or rectifiers producing line-frequency ac

$DC \rightarrow 60\text{ Hz}$

An electronic ballast

Rapid start
Instant start

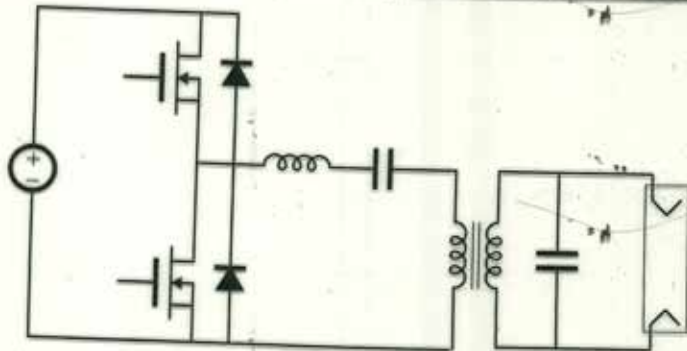- Must produce controllable high-frequency (50 kHz) ac to drive gas discharge lamp
- DC input is typically produced by a low-harmonic rectifier
- Similar to resonant dc-dc converter, but output-side rectifier is omitted



Half-bridge, driving LCC tank circuit and gas discharge lamp


High efficiency is essential

$$\eta = \frac{P_{out}}{P_{in}}$$

High efficiency leads to
low power loss within
converter

Small size and reliable
operation is then
feasible

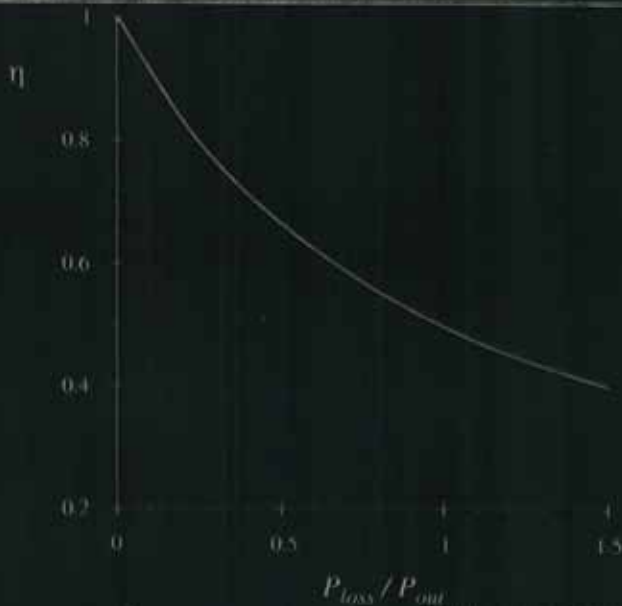Efficiency is a good
measure of converter
performance



Switching loss

(Section 4.3 of Power Electronics 1 text)

- Energy is lost during the semiconductor switching transitions, via several mechanisms:
 - Transistor switching times
 - Diode stored charge
 - Energy stored in device capacitances and parasitic inductances
- Semiconductor devices are *charge controlled*
- Time required to insert or remove the controlling charge determines switching times

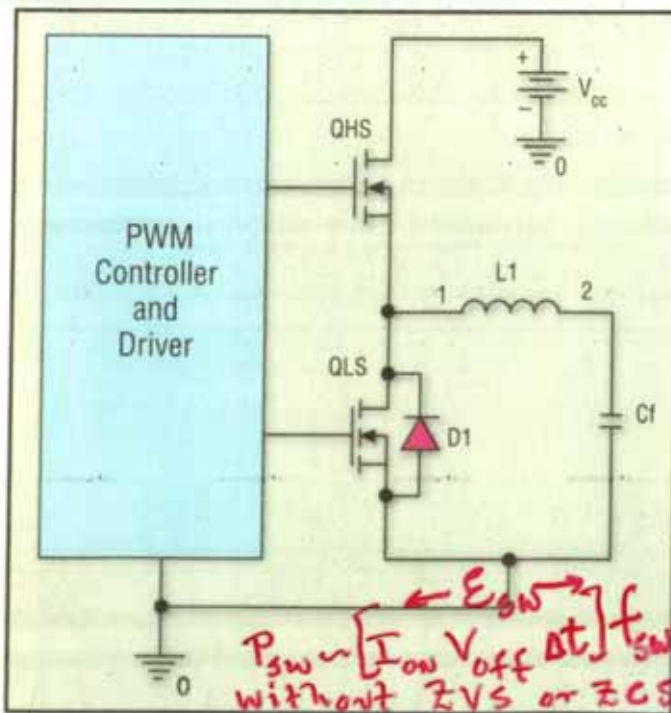


Fig. 1, The classical synchronous buck converter uses two switching MOSFETs: the high-side (control) device, QHS, and the low-side synchronous rectifier, QLS.

4.3.4. Efficiency vs. switching frequency

Add up all of the energies lost during the switching transitions of one switching period:

$$W_{tot} = W_{on} + W_{off} + W_D + W_C + W_L + \dots$$

Average switching power loss is

$$P_{sw} = W_{tot} f_{sw}$$

Total converter loss can be expressed as

$$P_{loss} = P_{cond} + P_{fixed} + \underbrace{W_{tot} f_{sw}}_{\text{Key}}$$

where

P_{fixed} = fixed losses (independent of load and f_{sw})


P_{cond} = conduction losses

$$\left[\epsilon(\text{off to on}) + \epsilon(\text{on to off}) \right]$$

$$W_T \frac{1}{f_{sw}}$$

Efficiency vs. switching frequency
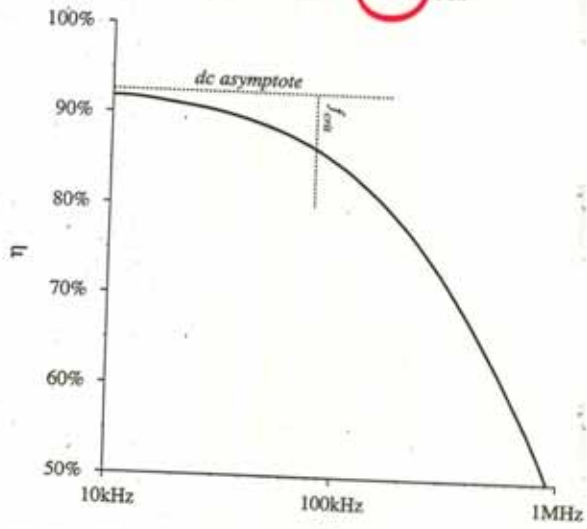
$$P_{loss} = P_{cond} + P_{fixed} + W_{tot} f_{sw}$$



Switching losses are equal to the other converter losses at the critical frequency

$$f_{crit} = \frac{P_{cond} + P_{fixed}}{W_{tot}}$$

This can be taken as a rough upper limit on the switching frequency of a practical converter. For $f_{sw} > f_{crit}$, the efficiency decreases rapidly with frequency.

Unless $W_{total} \rightarrow 0$

Resonant conversion: disadvantages

Can optimize performance at one operating point, but not with wide range of input voltage and load power variations

Significant currents may circulate through the tank elements, even when the load is disconnected, leading to poor efficiency at light load

Quasi-sinusoidal waveforms exhibit higher peak values than equivalent rectangular waveforms

} 33% ↑
Fourier
Analysis

These considerations lead to increased conduction losses, which can offset the reduction in switching loss

Resonant converters are usually controlled by variation of switching frequency. In some schemes, the range of switching frequencies can be very large

} Need
V-f
chips

Complexity of analysis

Introduction to Resonant Conversion

Resonant power converters contain resonant L-C networks whose voltage and current waveforms vary sinusoidally during one or more subintervals of each switching period. These sinusoidal variations are large in magnitude, and the small ripple approximation does not apply.

Some types of resonant converters:

- Dc-to-high-frequency-ac inverters
- Resonant dc-dc converters
- Resonant inverters or rectifiers producing line-frequency ac


$\frac{1}{2} \rightarrow 162 \text{ MHz}$

Pinnacle

360 kW


Derivation of a resonant dc-dc converter

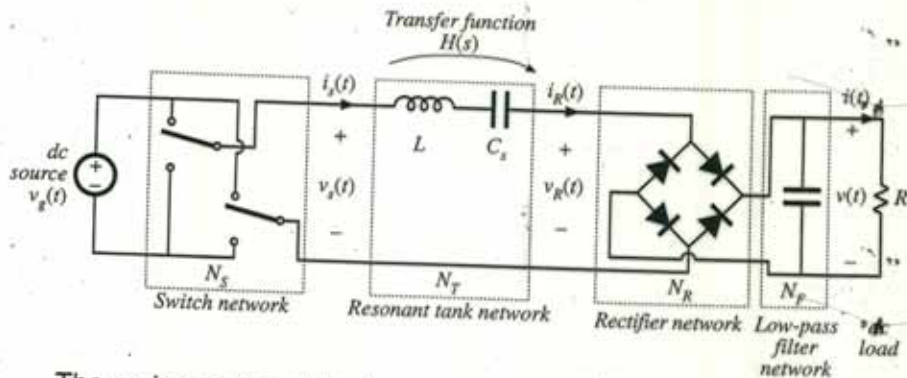Rectify and filter the output of a dc-high-frequency-ac inverter



The series resonant dc-dc converter

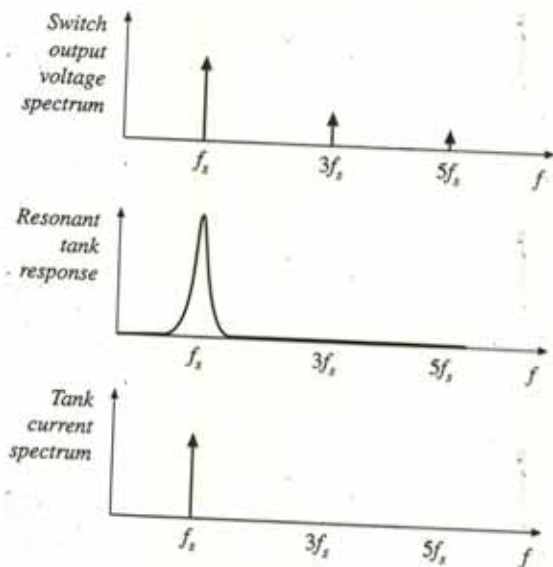
Tank network responds only to fundamental component of switched waveforms



Tank current and output voltage are essentially sinusoids at the switching frequency f_s .

Output can be controlled by variation of switching frequency, closer to or away from the tank resonant frequency

Control Loop for Resonant Converter

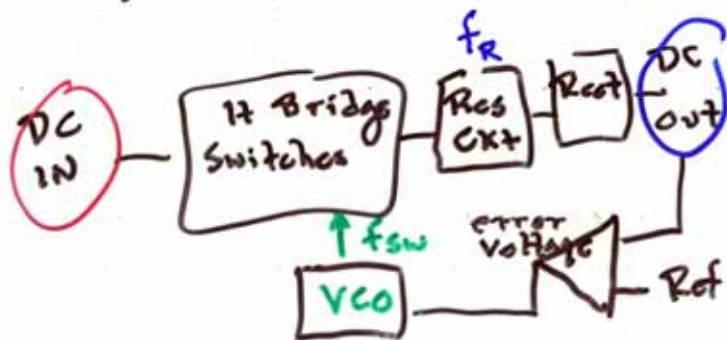

f_{sw} varied until

error voltage $\rightarrow 0$



Three-Phase Resonant Converter PPU 10KW Breadboard




Magnetics development


for sinusoids is unique

Two magnetic designs are being developed. The candidate with the best combination of efficiency and specific mass will be chosen.

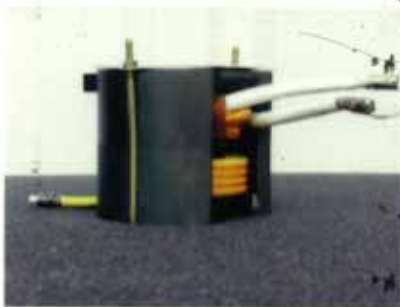Critical attention is needed for larger magnetic structures due to eddy current losses in the ferrite. The larger structures have an increased volts per turn which causes loss factors not prevalent in lower power magnetic structures.



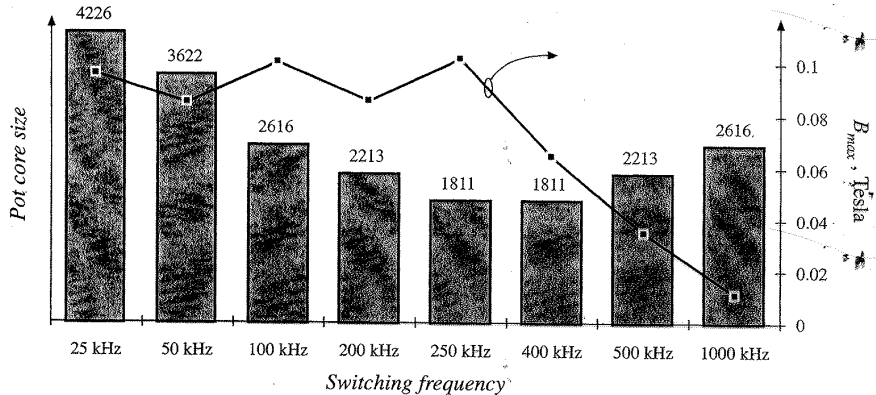Effect of switching frequency on transformer size for this P-material Cuk converter example



- As switching frequency is increased from 25 kHz to 250 kHz, core size is dramatically reduced
- As switching frequency is increased from 400 kHz to 1 MHz, core size increases

SW loss ~ $\left[\frac{1}{2} V_{off} I_{on} \Delta t \right]$
in Joules energy to switch

Switching loss

(Section 4.3 of Power Electronics 1 text)

- Energy is lost during the semiconductor switching transitions, via several mechanisms:
 - Transistor switching times
 - Diode stored charge
 - Energy stored in device capacitances and parasitic inductances
- Semiconductor devices are *charge controlled*
- Time required to insert or remove the controlling charge determines switching times

$$P_{loss} = E_{sw} f_{sw}$$

4.3.4. Efficiency vs. switching frequency

Add up all of the energies lost during the switching transitions of one switching period:

$$W_{tot} = W_{on} + W_{off} + W_D + W_C + W_L + \dots$$

What is missing?

Average switching power loss is

$$P_{sw} = W_{tot} f_{sw}$$

Total converter loss can be expressed as

$$P_{loss} = P_{cond} + P_{fixed} + W_{tot} f_{sw}$$

where

P_{fixed} = fixed losses (independent of load and f_{sw})


P_{cond} = conduction losses

Efficiency vs. switching frequency

GSC student 2ays
 $f_{sw} = 25 \text{ kHz}$

Now: ? .. 2.5 MHz
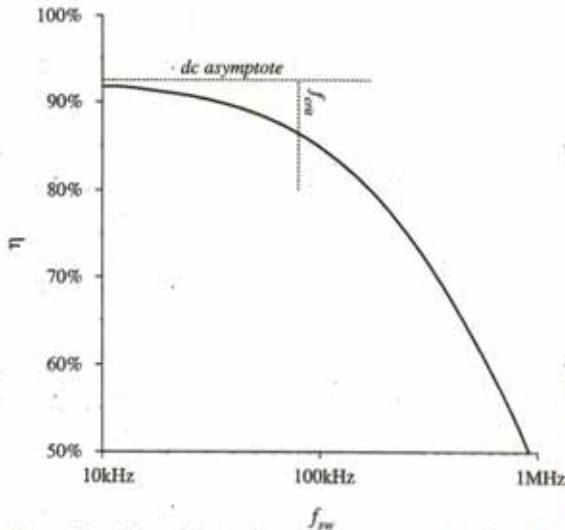
$$P_{loss} = P_{cond} + P_{fixed} + W_{tot} f_{sw}$$



Switching losses are equal to the other converter losses at the critical frequency

$$f_{crit} = \frac{P_{cond} + P_{fixed}}{W_{tot}}$$

This can be taken as a rough upper limit on the switching frequency of a practical converter. For $f_{sw} > f_{crit}$, the efficiency decreases rapidly with frequency.

2 VS


$f_{sw} \uparrow$ requires \downarrow CS

Chapter 4: Switch realization

oo $[I_{on} V_{off} \Delta t] = E_{sw} \downarrow$

Applications of resonant and soft-switching converters


- **Electronic ballasts** for gas-discharge lamps
 - Produce high-frequency ac
- High-frequency high-density **dc-dc converters**
 - Reduce switching loss and improve efficiency
- High-voltage and other specialized converters
 - Transformer nonidealities lead to **ringing waveforms**
- Converters using **IGBTs**
 - **Mitigate switching loss caused by current tailing**
- Converters using piezoelectric transformers
 - Converter is designed to excite one mode of piezo
- Low-harmonic rectifiers
 - Mitigate switching loss caused by diode stored charge

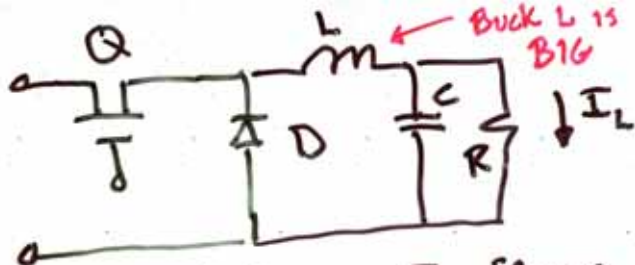

- ① if Q off D ON, I_L flows through D
- ② I_D will continue to flow due to Q_{rr} for Δt_{rr} after Q ON
- ③ When Q goes from off to ON large E_{off} occurs since

V_{DS} large as current increases I_{on}

force i_Q to be zero as

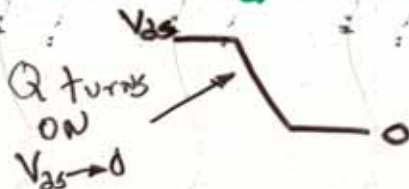

} ZCT switching

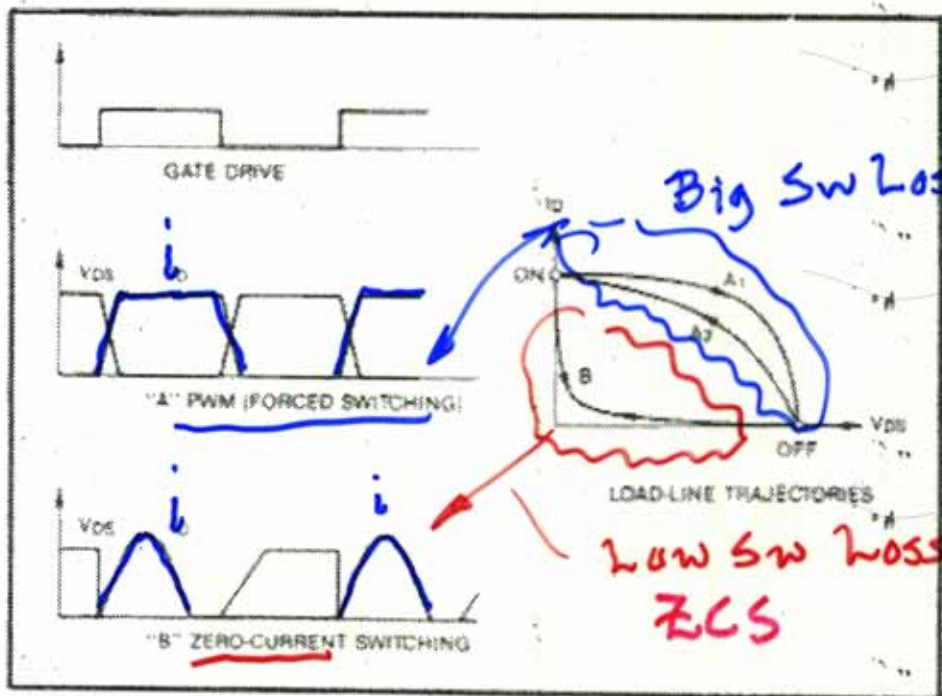


Fig. 6 - Switching Stress and Switching Loss

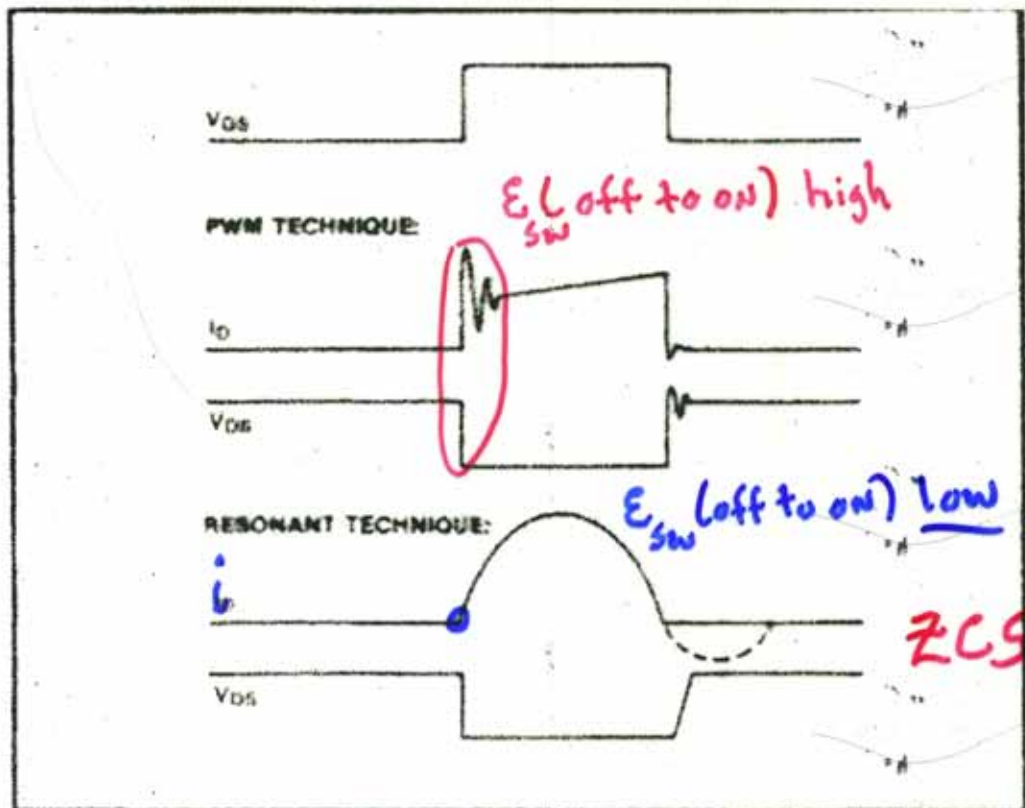


Fig. 5 - PWM vs. Resonant Switching

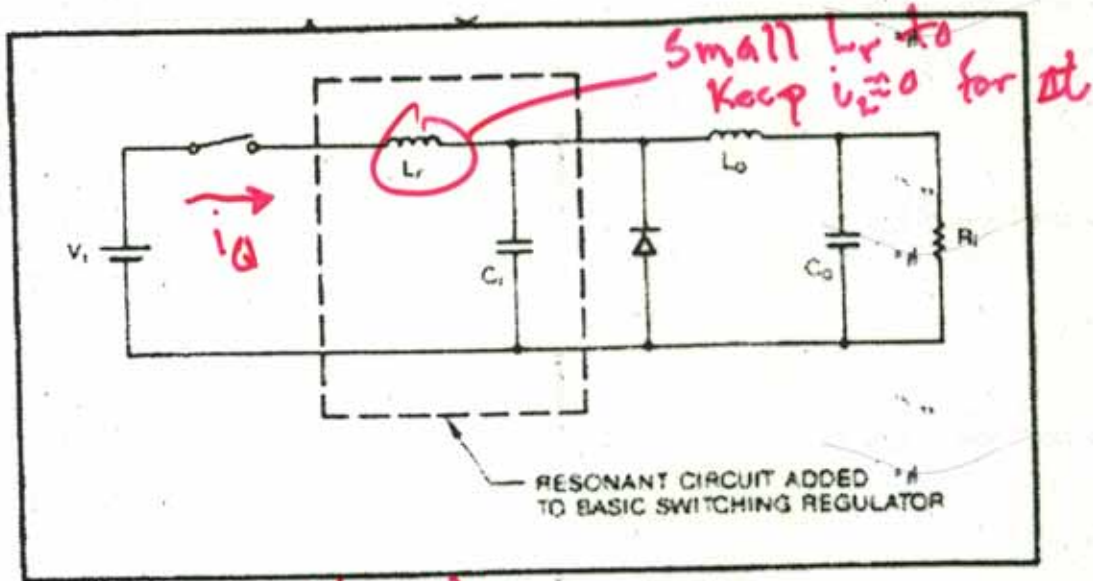

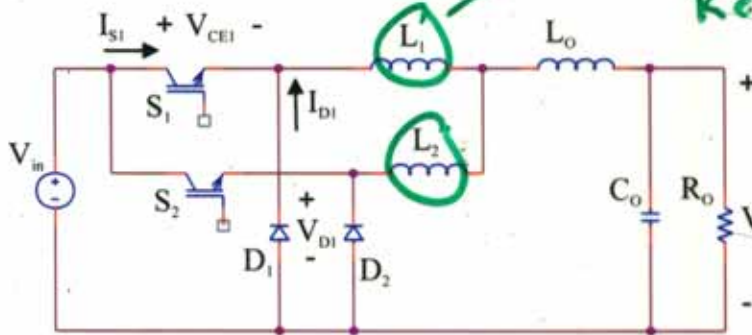


Fig. 3 - (Basic) Resonant Converter
(Buck)

L_r, C_r allow reduction of Sw loss
force $\approx C \cdot T$

How? L_r keeps $i_D \approx 0$ while V_{DS} 

Interleaved ZCT Buck



- Two small inductors (L_1, L_2) added to achieve zero-current-transition turn on of the switches S_1 and S_2
- Out-of-phase operation of S_1 and S_2 , as in two-phase converters
- Significant reduction of losses associated with diode reverse recovery
- Simple operation, no resonant circuit

ZCT Only for turn-on

Comparison of Losses

Powerex: CM150DU-24NFH		Hard switched	New circuit
Turn-on loss	(mJ)	4.0	0.4
Turn off loss	(mJ)	3.8	3.8
Conduction loss (one sw. period)	(mJ)	6.1	6.1
Loss per switch (32 kHz)	(W)	444.2	164.5
Diode recovery loss	(mJ)	12.0	2.0
Diode conduction loss (one sw. per.)	(mJ)	3.5	3.5
Diode loss (32 kHz)	(W)	496.6	88.3
Aux switch, eq (10)* in [2]	(mJ)		
Total loss (32 kHz)	(W)	940.8	505.6

*m=0.6, To=3 μ s, k=2, Vc=10 V

10x
NO
advantage

6x

2x
better
overall



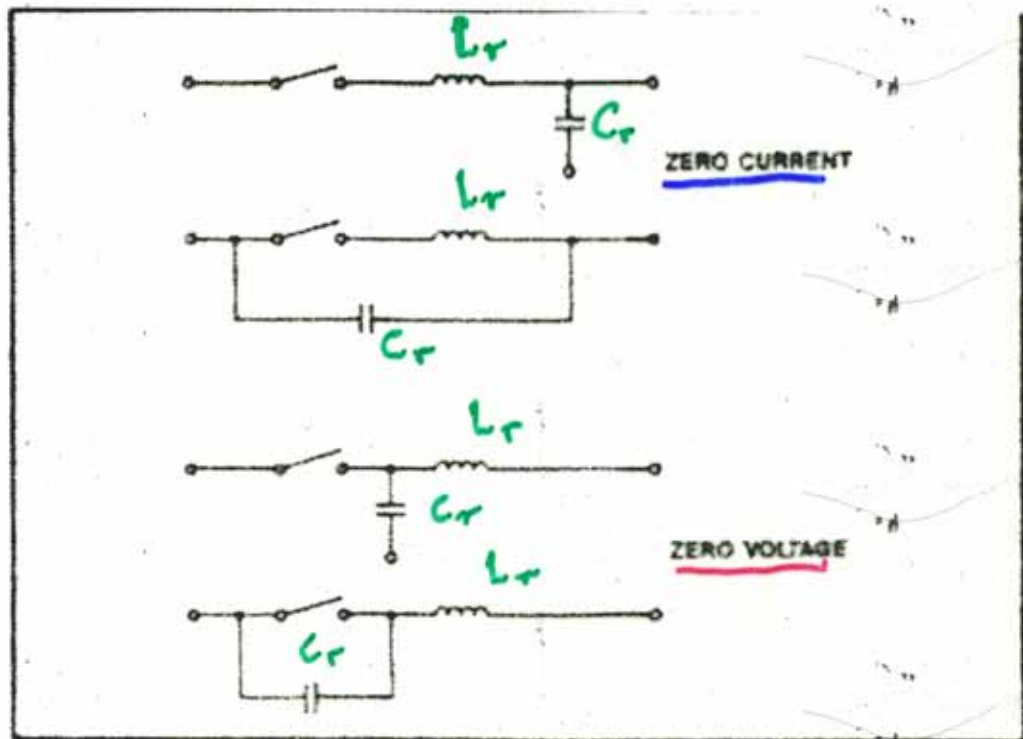


Fig. 7 - Resonant Switches

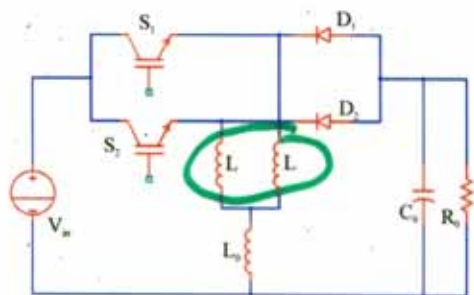
Examples of Other Interleaved ZCT Converters



Buck-boost

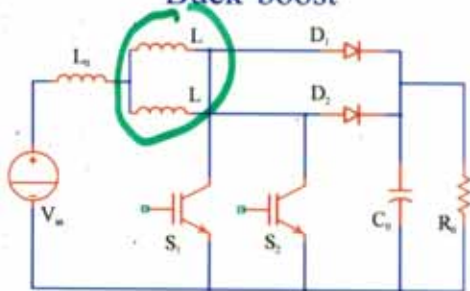


Boost

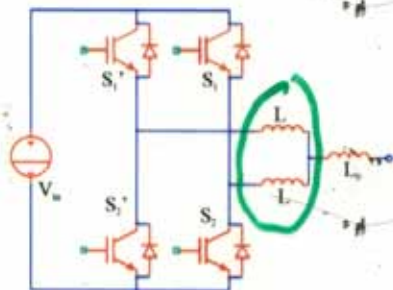


One leg of an
interleaved ZCT bridge
or three-phase inverter

BASIC Concept ZVS

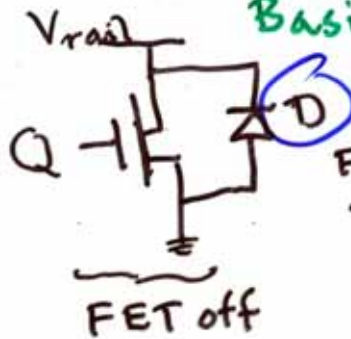

To go from FET off to FET ON

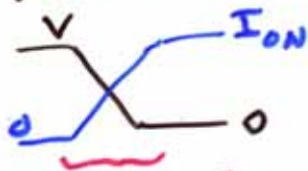


$$[VI_{ON}dt]$$

$E_{off \text{ to } ON}$

$$P_{off \text{ ON}} = f_{sw} [E_{off \text{ ON}}]$$

if \textcircled{D} is placed on ahead of \overline{Q} by a leading i

$V_g = 0$ during

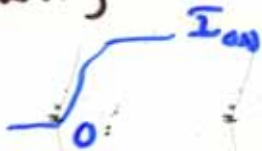

$$E_{off \text{ ON}} \rightarrow 0$$

Soft switching: Zero-voltage and zero-current switching




H bridge: Approx
V is ?
i is ?

Soft switching can mitigate some of the mechanisms of switching loss and possibly reduce the generation of EMI

Semiconductor devices are switched on or off at the zero crossing of their voltage or current waveforms

if tank Q is high L is sine

Angle i is α to $Z(\tan \phi)$ IN

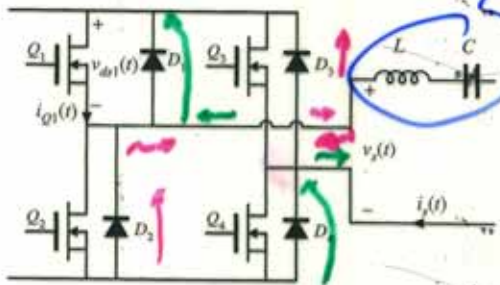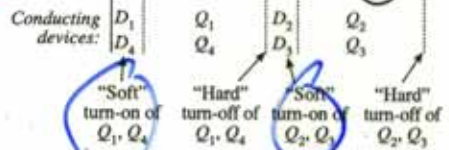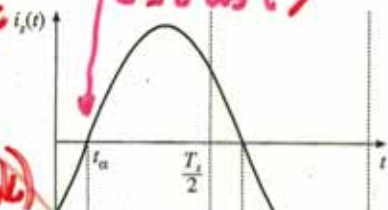

Conduction sequence: $D_1-Q_1-D_2-Q_2$

Q_1 is turned on during D_1 conduction interval, without loss

leading i forces $V_a = 0$ (via diode) prior to Q ON

E_{off} ON

i_s is \oplus as shown \Rightarrow diodes 2 and 3 are ON
Forces V_{a2} and $V_{a3} = 0$ even if gate
 drives keep Q_2 and Q_3 off



\Rightarrow as i_{a2} and i_{a3} increase $i_a \neq V_a \neq 0 \Rightarrow E_{sw} = 0$
 Soft switching: \uparrow make zero

Zero-voltage and zero-current switching

Below ZVT turn-on of Q_2 & Q_3

Soft switching can mitigate some of the mechanisms of switching loss and possibly reduce the generation of EMI

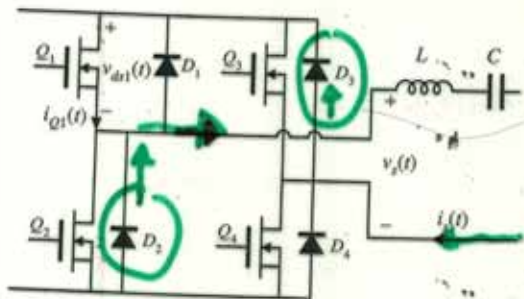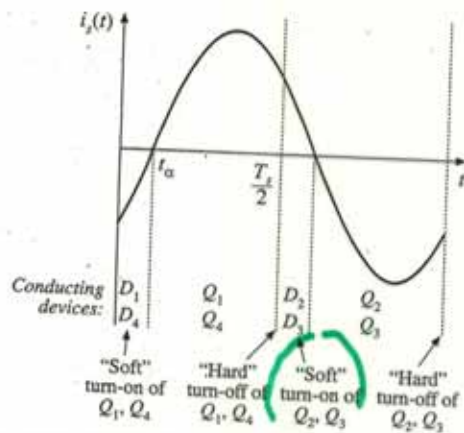Semiconductor devices are switched on or off at the zero crossing of their voltage or current waveforms



Conduction sequence: $D_1 - Q_1 - D_2 - Q_2$
 Q_1 is turned on during D_1 conduction interval, without loss

i_s is $\ominus \Rightarrow$ Diodes 1 and 4 on

Forces V_{Q_1} & $V_{Q_4} = 0$
 even if Q_1 and Q_4 are off
 $i_a + v_a \frac{dt}{dt} = E_{sw} = 0$

\Rightarrow as i_a , $d i_a / dt$ increase



Soft switching:

Zero-voltage and zero-current switching

i_s is $\oplus \Rightarrow$ Diodes 2 and 3 on etc

Soft switching can mitigate some of the mechanisms of switching loss and possibly reduce the generation of EMI

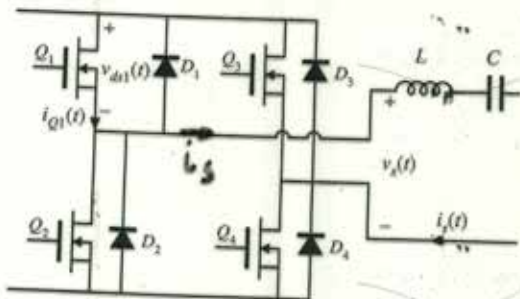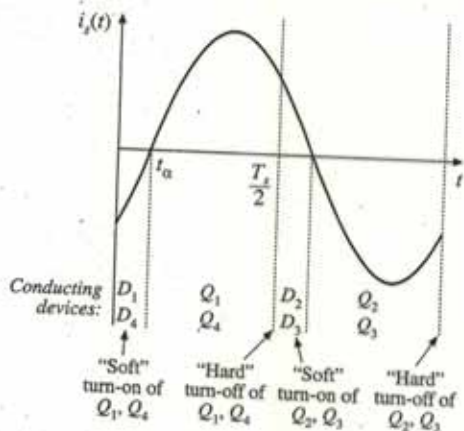Semiconductor devices are switched on or off at the zero crossing of their voltage or current waveforms



Conduction sequence: $D_1 - Q_1 - D_2 - Q_2$

Q_1 is turned on during D_1 conduction interval, without loss

Pbm 19.1 HW Sct #C

f_{sw} only

$V_g - I_g$ model

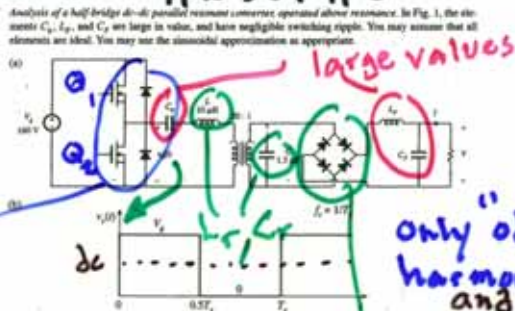


Fig. 1 Half-bridge parallel resonant converter of Problem 1. (a) schematic, (b) switch voltage waveform.

(a) Construct an equivalent circuit for this converter, similar to Fig. 19.22, which models the fundamental components of the tank waveforms and the dc components of the converter input current and output voltage. Clearly label the values and/or give expressions for all elements in your model, as appropriate.

At rated (maximum) load, this converter produces $I = 20$ A at $V = 3.3$ V.

(b) What is the converter switching frequency f_s at rated load?

(c) What is the magnitude of the peak transistor current at rated load?

At minimum load, the converter produces $I = 2$ A at $V = 3.3$ V.

(d) What is the converter switching frequency f_s at minimum load?

(e) What is the magnitude of the peak transistor current at minimum load? Compare with your answer from part (c)—what happens to the conduction loss and efficiency at minimum load?

only "odd" harmonics and dc level

easy to model $V_g - I_g$

V_{out} fixed @ 3.3V
 $2 \leq I_{out} \leq 20$ A

as V_g or I_g vary requires f to change to keep $V_o = 3.3V$

$$V_{out} = \underbrace{\begin{bmatrix} \frac{V_{s1}}{V_g} \end{bmatrix}}_{\text{Input Switch}} \underbrace{\begin{bmatrix} \frac{V_{R1}}{V_{s1}} \end{bmatrix}}_{\text{Resonant Circuit}} \underbrace{\begin{bmatrix} \frac{V_{out}}{V_{R1}} \end{bmatrix}}_{\text{Rectifier}}$$


$\sim \frac{2}{\pi}$ $H(\omega)$ $\sim \frac{2}{\pi}$

$\frac{4}{\pi^2}$ for $\frac{1}{2}$ bridge


$\frac{8}{\pi^2}$ for full bridge

$$H(\omega) \sim \left(\frac{V_{in}}{Z_{in}} \right) \underbrace{\left[\frac{1}{\omega C} \parallel R \right]}_{\text{load}}$$

i

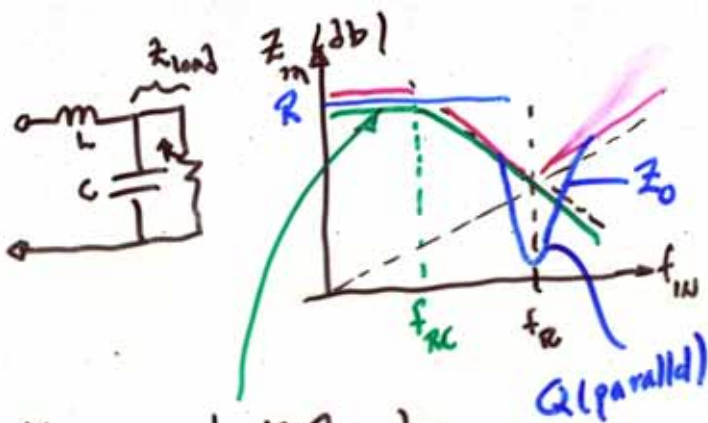

$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{\omega C} \parallel R \} Z_{load}}{\omega L + \frac{1}{\omega C} \parallel R \} Z_{in}}$$

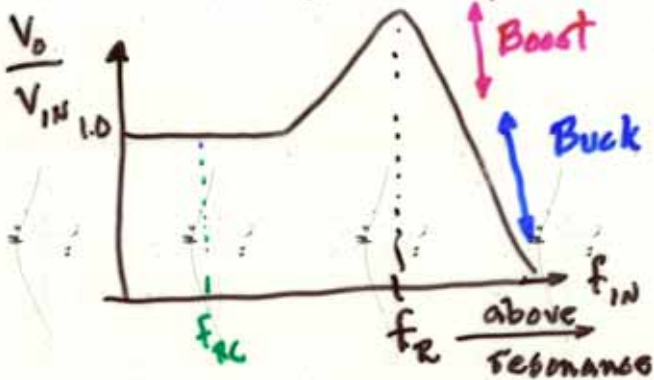

Pbm 1A.1



Half-bridge dc-dc parallel resonant converter

a) Equivalent circuit model



① Input Model

high Q $\frac{2V_o}{\pi} \sin \omega_s t$

Switch network model:

Model the dc component of $i_g(t)$, and the fundamental component of $v_s(t)$.

$\omega_s = 2\pi / T_{sw}$

$i_g(t)$ contains a dc component (that is removed by C_s), and odd harmonics. Fourier series of $v_s(t)$:

$v_s(t) = \frac{1}{2} V_g + \sum_{n=1,3,5,\dots} \frac{2}{n} \frac{V_g}{\pi} \sin(n\omega_s t)$ with $\omega_s = \frac{2\pi}{T_s}$

The fundamental component is

$v_{s1}(t) = \frac{2V_g}{\pi} \sin(\omega_s t)$


full bridge $\frac{4}{\pi} \frac{V_g}{\pi}$

In response to this applied voltage, the fundamental component of the tank input current is


$i_{s1}(t) = I_{s1} \sin(\omega_s t - \phi_s)$

The input current on the dc side of the switch network is given by
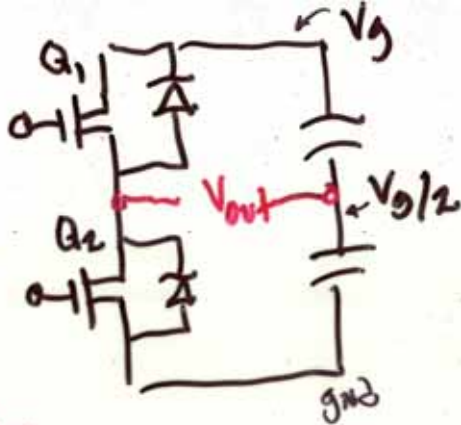
$$i_g(t) = \begin{cases} i_{s1}(t) & \text{when } Q_1/D_1 \text{ conduct } (0 < t < \frac{1}{2}T_s) \\ 0 & \text{when } Q_2/D_2 \text{ conduct } (\frac{1}{2}T_s < t < T_s) \end{cases}$$



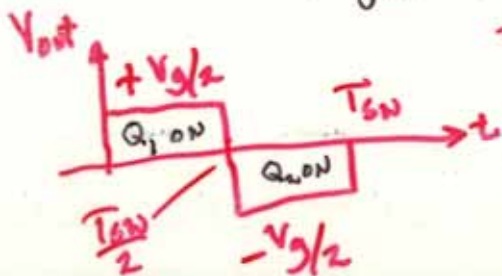with C
 $\frac{1}{2}$ bridge
 of
 Pbm 19.1
 V_{out} is
 \pm wrt 0




by symmetry
 only
 odd
 harmonics

look @

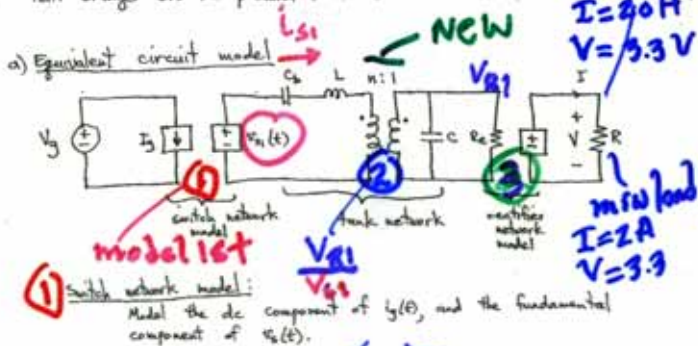1. Input circuit model
2. Rectifier model
3. Tank model

$$f_{sw} > f_r$$

Half-bridge dc-dc parallel resonant converter



$v_n(t)$ contains a dc component (that is removed by C_0), and add harmonics. Fourier series of $v_n(t)$:

why?

$$v_n(t) = \frac{1}{2} V_g + \sum_{n=1,3,5,\dots} \frac{2}{n} V_g \sin(n\omega_s t) \quad \text{with } \omega_s = \frac{\pi}{T_s}$$

The fundamental component is

$$v_n(t) = \frac{2}{\pi} V_g \sin(\omega_s t)$$

$$|V_n| = \frac{2}{\pi} V_g \quad \text{VS full bridge } \frac{4}{\pi}$$

In response to this applied voltage, the fundamental component of the tank input current is

key

$$i_n(t) = I_{n1} \sin(\omega_s t - \phi_s)$$

$$f > f_r \quad i \text{ lags}$$

The input current on the dc side of the switch network is given by

$$i_g(t) = \begin{cases} i_n(t) & \text{when } Q_1/D_1 \text{ conduct } (0 < t < \frac{1}{2}T_s) \\ 0 & \text{when } Q_2/D_2 \text{ conduct } (\frac{1}{2}T_s < t < T_s) \end{cases}$$


For $f_{op} > f_{LC}$

The dc component of $i_g(t)$ is therefore **Average over T_s**

$$I_g = \frac{1}{T_s} \int_0^{T_s} i_g(t) dt = \frac{1}{T_s} \int_0^{\frac{1}{2}T_s} I_{s1} \sin(\omega_s t - \phi_s) dt$$

$$= \frac{I_{s1}}{\pi} \cos(\phi_s)$$

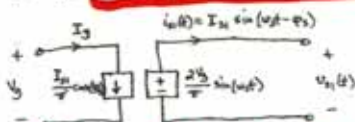So the half-bridge switch network model is **DC \leftrightarrow AC**
Input model




$$\left. \begin{array}{l} V_{B1} \\ V_g \end{array} \right\} = \frac{2}{\pi}$$

Do next easiest model F.B.R.

③

Rectifier network model

Model the fundamental component of $i_p(t)$, and the dc component of $|V_o(t)|$. The waveforms and resulting model are identical to those derived in the textbook for the parallel resonant converter:

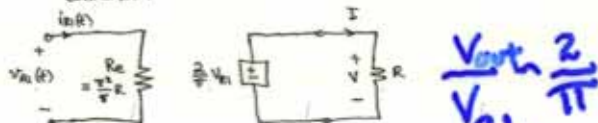

$$\frac{V_{out}}{V_{B1}} = \frac{2}{\pi}$$

with $\frac{V_o(t)}{V_{B1}} = \frac{2}{\pi} \sin(\omega_s t - \phi_o)$
 $i_p(t) = \frac{I_g}{2} \sin(\omega_s t - \phi_e)$

$$R_e = \frac{\pi^2}{8} \left[\frac{V_{out}}{I_{out}} \right]$$

Next resonant network $H(\omega)$


③

The dc component of $i_g(t)$ is therefore

$$I_g = \frac{1}{T_s} \int_0^{T_s} i_g(t) dt = \frac{1}{T_s} \int_0^{\frac{1}{2}T_s} I_{s1} \sin(\omega_s t - \phi_s) dt$$


$$= \frac{I_{s1}}{\pi} \cos(\phi_s)$$

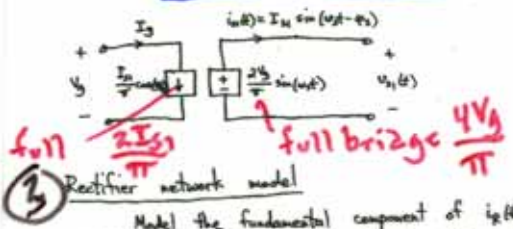So the half-bridge switch network model is




③ Rectifier network model

Model the fundamental component of $i_g(t)$, and the dc component of $|v_{r2}(t)|$. The waveforms and resulting model are identical to those derived in the textbook for the parallel resonant converter:

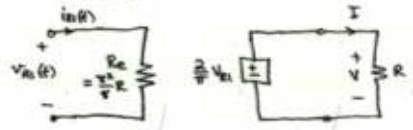


with $v_{r2}(t) = V_{r2} \sin(\omega_s t - \phi_{r2})$

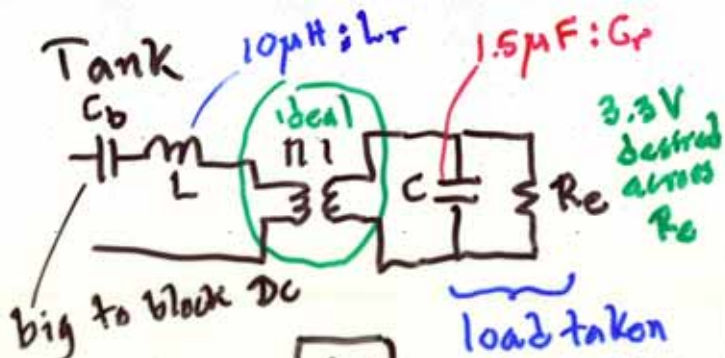$i_{R2}(t) = \frac{I_{r2}}{\pi} \sin(\omega_s t - \phi_{r2})$



For $R_e > \sqrt{L/C}$


expect

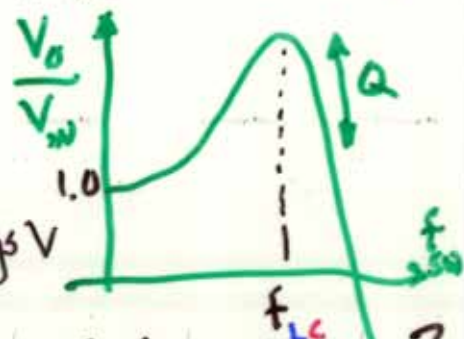

$f_{op} > f_{LC}$
 $\Rightarrow i_{tank} \text{ lags } V$

Any effects of transformer?


- (a) ON F
- (b) ON Q

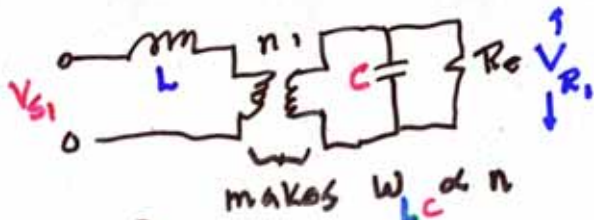


$$Q_e = \frac{R_e}{Z_0} = \frac{R_e}{\sqrt{\frac{L/n^2}{C}}} = \frac{n R_e}{\sqrt{L/C}}$$

$Q = f(n)$

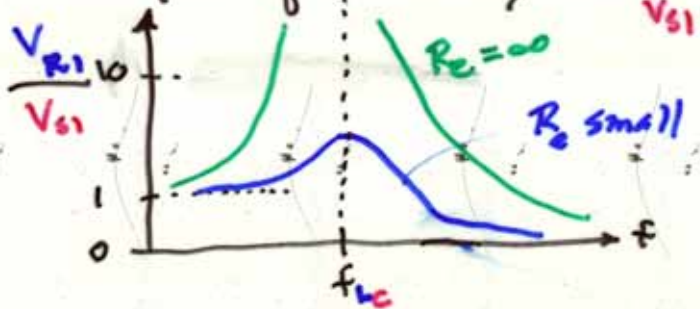Expect qualitatively two $\frac{V_{r1}}{V_{s1}}$



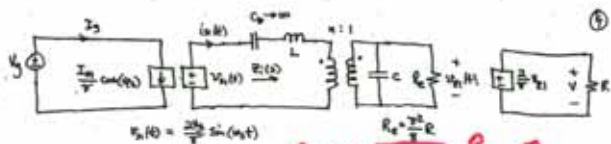

full $R_e = \frac{8}{\pi^2} R$

Solution of model for dc conversion ratio $M = \frac{V_o}{V_s}$:

$$V = \left(\frac{V_{s1}}{V_s} \right) \left(\frac{V_{o1}}{V_{s1}} \right) \left(\frac{V_o}{V_{o1}} \right) = \frac{4}{\pi^2} \|H(j\omega)\|$$

③ resonant network; Move L and V_{s1} to secondary!
 where the transfer function H(s) is

$$H(s) = \frac{1}{n} \frac{R \parallel \frac{1}{sC}}{\frac{sL}{n} + R \parallel \frac{1}{sC}} = \frac{1}{n} \frac{1}{1 + \frac{sL}{nR} + \frac{s^2 LC}{n^2}}$$

$$= \frac{1}{n} \frac{1}{1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

with $\omega_0 = \frac{1}{\sqrt{LC}}$
 $Q = R \sqrt{\frac{C}{L}}$

$V_{s1} \rightarrow \frac{V_{s1}}{n}$
 $L \rightarrow \frac{L}{n^2}$

$$\|H(j\omega)\| = \frac{1}{n} \frac{1}{\sqrt{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2 + \left(\frac{\omega}{Q\omega_0}\right)^2}} = \frac{1}{n} \frac{1}{\sqrt{\left(1 - F^2\right)^2 + \left(\frac{F}{Q}\right)^2}}$$

$$\text{So } M = \frac{4}{\pi^2} \frac{1}{\sqrt{\left(1 - F^2\right)^2 + \left(\frac{F}{Q}\right)^2}}$$

This equation is used to plot V vs. f_s :
 on the next page, at maximum load and
 at minimum load.

2A 20A

Analytically $\frac{V_{R1}}{V_{S1}} =$

$$\frac{R_e \parallel \frac{1}{sC}}{\frac{sL}{n^2} + R_e \parallel \frac{1}{sC}} = \frac{Z_{load}}{Z_{in}}$$

$$\frac{R_e / sC}{R_e + \frac{1}{sC}} = \frac{R_e}{R_e s + 1} = R_e \parallel \frac{1}{sC}$$

$$\frac{R_e}{(R_e s + 1) \frac{sL}{n^2} + R_e} \left. \begin{array}{l} \text{from} \\ Z_{load} = \frac{1}{R_e s + 1} \end{array} \right\} \frac{Z_{load}}{Z_{in}} = \frac{1}{R_e s + 1}$$

$$\left[\frac{s^2 LC}{n^2} + \frac{sL}{R_e n^2} + 1 \right]^{-1} \frac{1}{n} = \frac{V_{R1}}{V_{S1}}$$

$$\frac{1}{n} \frac{1}{\frac{s^2}{\omega_R^2} + \frac{s}{Q\omega_R} + 1} = \frac{V_{R1}}{V_{S1}} \cdot \frac{1}{n}$$

from V_{S1}

Quantitative

⑤

Chosen values

Element values


L	10 μ H
C	1.5 μ F
n	20
V ₁	160 V
V	3.3 V

Operating points

at I =	20 A	2 A
R =	0.165 Ω	1.65 Ω
R _e =	0.204 Ω	2.036 Ω
f ₀ =	821.873 Hz	821.873 Hz
Q _s =	1.58	15.77
f	1.031,696 Hz	1.156,025 Hz

for $V_0 = 3.3$

$$R_e \approx \frac{I^2 R}{8}$$

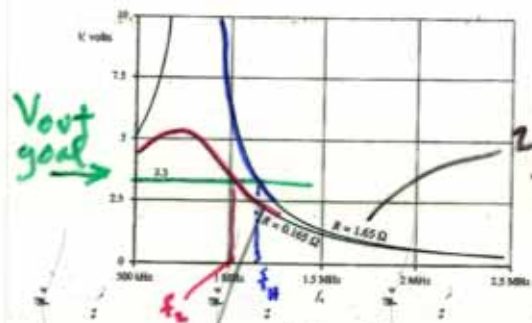

2A load
 $R \uparrow$
 $Q \uparrow = 16$

20A load
 $R \downarrow$
 $Q \downarrow = 1.6$

b) Finding f_3 at a given load current

⑥

We know that

$$M = \frac{4}{\omega^2 M} \frac{1}{\sqrt{(1-F^2)^2 + \left(\frac{F}{Q_c}\right)^2}}$$

We want to solve for F:

$$\left(\frac{4}{\omega^2 M}\right)^2 = (1-F^2)^2 + \left(\frac{F}{Q_c}\right)^2 = 1 - 2F^2 + \frac{F^4}{Q_c^2} + F^2$$

So

$$F^4 + F^2\left(\frac{1}{Q_c^2} - 2\right) + 1 - \left(\frac{4}{\omega^2 M}\right)^2 = 0$$

Quadratic formula:

$$F^2 = \frac{-\left(\frac{1}{Q_c^2} - 2\right) \pm \sqrt{\left(\frac{1}{Q_c^2} - 2\right)^2 - 4 + 4\left(\frac{4}{\omega^2 M}\right)^2}}{2}$$

Simplify:

$$F = \sqrt{1 - \frac{1 - \sqrt{1 - Q_c^2 + 4 + Q_c^2 / \omega^2 M^2}}{2 Q_c^2}}$$

- ① At rated load, $Q_c = 1.58$ } f_L $R_c = 0.204$
 and: $f_s = F \cdot f_n = 1.03 \text{ MHz}$
- ② At minimum load, $Q_c = 15.8$ and $f_s = 1.156 \text{ MHz}$ } f_H $R_c = 2.04$
 (answers to parts b and d)

1. Analysis of a half-bridge parallel resonant converter operated above resonance. In Fig. 1, the elements C_1 , L_m , and C_2 are large in value, and have negligible switching ripple. You may assume that all elements are ideal. You may use the sinusoidal approximation as appropriate.

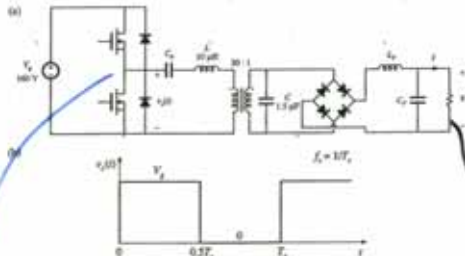


Fig. 1 Half-bridge parallel resonant converter of Problem 1. (a) schematic, (b) switch voltage waveforms.

(a) Construct an equivalent circuit for this converter, similar to Fig. 19.22, which models the fundamental components of the load waveforms and the dc components of the converter input current and output voltage. Clearly label the values and/or give expressions for all elements in your model, as appropriate.

At rated (maximum) load, this converter produces $I = 20 \text{ A}$ at $V = 3.3 \text{ V}$.

- (b) What is the converter switching frequency f_s at rated load?
- (c) What is the magnitude of the peak transistor current at rated load?

At minimum load, the converter produces $I = 2 \text{ A}$ at $V = 3.3 \text{ V}$.

- (d) What is the converter switching frequency f_s at minimum load?
- (e) What is the magnitude of the peak transistor current at minimum load? Compare with your answer from part (c)—what happens to the conduction loss and efficiency at minimum load?

Question
 Is a largest for $R_L \rightarrow \infty$?

When $f_{op} = f_{LC}$


Largest $i_{IN} = i_a$ when

$$R_L = \infty$$


$$\text{OR}$$

$$R_L = 0$$

for $f_{op} = f_{LC}$

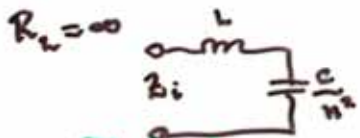

Series Resonance

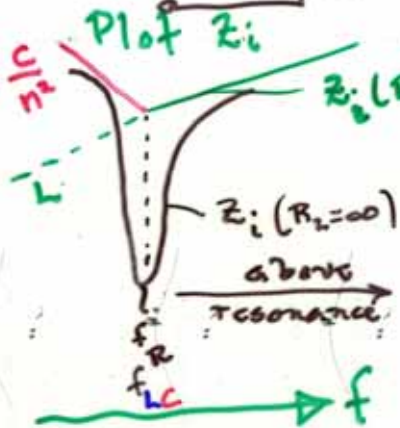


$i_{IN} = i_a$
largest
for
 $R_L = \infty$
@ $f_{op} = f_{LC}$

(7)

Peak transistor current

$$I_{s1} = \frac{V_{s1}}{\|Z\|} \quad \text{where } Z(s) \text{ is the tank network input impedance and with } V_{s1} = 2V_g/r$$

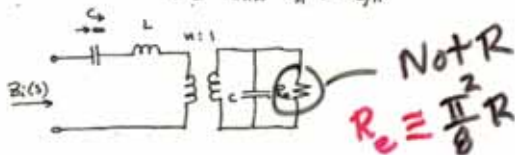

$$Z(s) = sL + n^2 \left(\frac{1}{sC} \parallel R_e \right)$$

$$= n^2 R_e \frac{(1 + s \frac{L}{n^2 R_e} + s^2 \frac{L^2 C}{n^2})}{(1 + s R_e C)}$$



At maximum load:

$$R_e = 0.204 \Omega$$

$$f_0 = 1.03 \text{ MHz}$$

$$Q_e = 1.58$$

$$\|Z\|_{f_0} = 36.1 \Omega$$

$$\text{Peak transistor current } I_{s1} = \frac{2(160)}{36.1} = 2.82 \text{ A}$$


Peak transistor current

occurs

R_L small or large. ⁽⁷⁾

$$I_{s1} = \frac{V_{s1}}{\|Z_1\|}$$

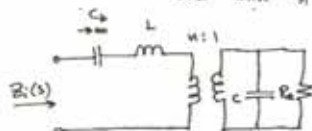
where $Z_1(s)$ is the tank network input impedance and with $V_{s1} = 210/\text{sr}$



$n = 20$
 $L = 10 \mu\text{H}$
 $C = 1.5 \mu\text{F}$

$$Z_1(s) = sL + n^2 \left(\frac{1}{sC} \parallel R_e \right)$$
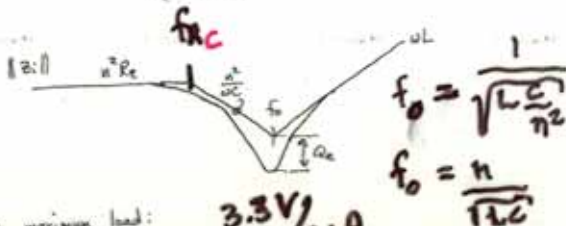
$$= n^2 R_e \frac{(1 + s \frac{L}{n^2 R_e} + s^2 \frac{LC}{n^2})}{(1 + s R_e C)}$$



At maximum load:

$$R_e = 0.204 \Omega$$

$$f_s = 1.03 \text{ MHz}$$

$$Q_e = 1.58$$

$$\|R_e\|_{f=f_s} = 36.1 \Omega$$

Peak transistor current

$$\frac{3.3\text{V}}{20\text{A}} \times \frac{\pi}{8} R_L(\text{min})$$

$$I_{s1} = \frac{2(160)}{36.1} = 2.82 \text{ A}$$

At minimum load:

⑧

$$R_e = 2.036 \Omega$$

$$f_s = 1.156 \text{ MHz}$$

$$Q_e = 15.8$$

$$\|Z\|_{f=f_s} = 36.0 \Omega$$

$$I_{s1} = \frac{36(160)}{36.0} = 2.83 \text{ A}$$


The peak transistor current is essentially independent of load current. Hence, the conduction loss is also independent of load current. This would lead to near efficiency at light load.



DC \rightarrow \square -wave \rightarrow Sine wave $\xrightarrow{\text{Rectifier}}$ DC

19.1 Sinusoidal analysis of resonant converters

A resonant dc-dc converter:

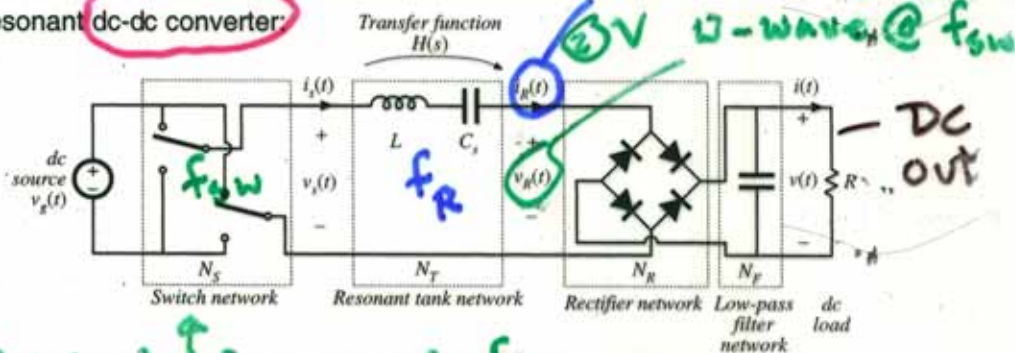

By control you set f_{sw}

If tank responds primarily to fundamental component of switch network output voltage waveform, then harmonics can be neglected.

Let us model all ac waveforms by their fundamental components.

$\frac{f_{sw}}{f_R}$ determines $|i_p|$


Suprise: V_R and V_S both \square -waves

AE Family


Standard DC/LF/MF Topologies (3-10kW)

- Offline pulse width modulated full-bridge
 - MDX (DC)
 - MDXII (DC)
- Offline phase-modulated full-bridge for greater dynamic range
 - PE (LF)
 - PDX (MF)
- Promising results in the HF range (3-30MHz)

Success to 160 MHz DC

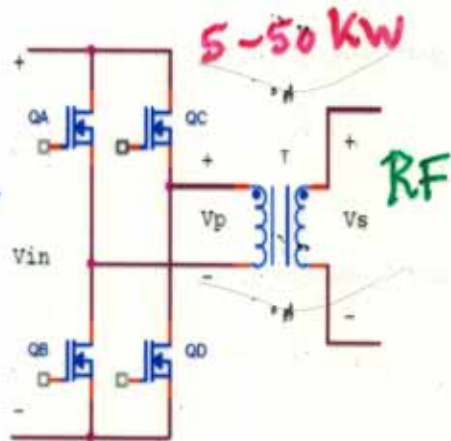

The sinusoidal approximation

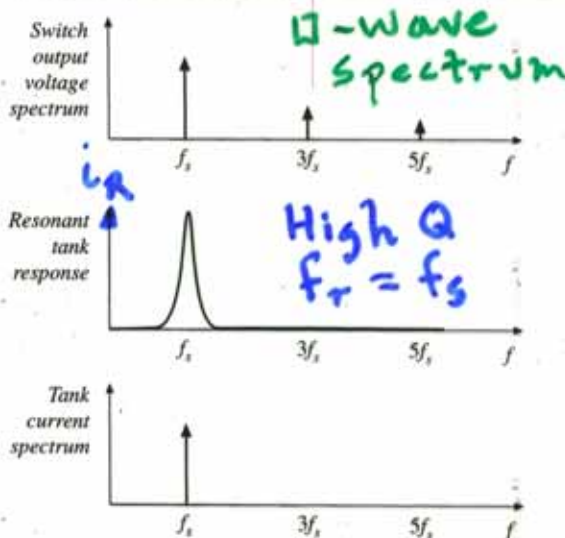

Tank current and output voltage are essentially sinusoids at the switching frequency f_s .



Neglect harmonics of switch output voltage waveform, and model only the fundamental component.

Remaining ac waveforms can be found via phasor analysis.

DC \rightarrow \square -wave \rightarrow fundamental component

19.1.1 Controlled switch network model

peak $1.3 V_g$

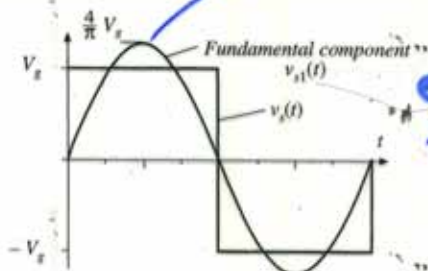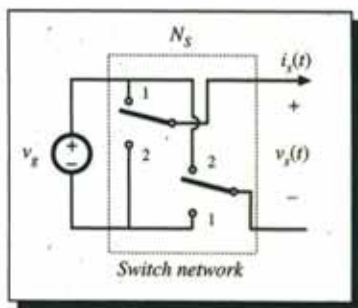

equal time $\pm V_g$

If the switch network produces a square wave, then its output voltage has the following Fourier series:


$$v_s(t) = \frac{4V_g}{\pi} \sum_{n=1,3,5,\dots} \frac{1}{n} \sin(n\omega_s t)$$

The fundamental component is

$$v_{s1}(t) = \frac{4V_g}{\pi} \sin(\omega_s t) = V_{s1} \sin(\omega_s t)$$

So model switch network output port with voltage source of value $v_{s1}(t)$


Model of switch network input port

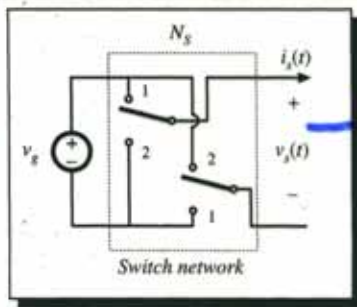

Assume that switch network output current is

$$i_s(t) = I_{s1} \sin(\omega_s t - \phi_s)$$

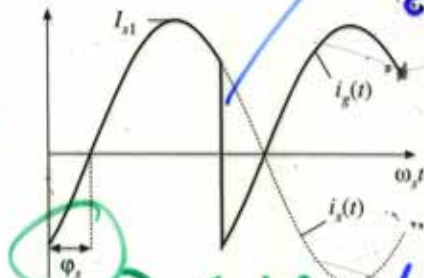It is desired to model the dc component (average value) of the switch network input current.



i_s is abruptly switched by control gate drive

set by $L Z_{in}$ @ f_{sw}

$$\begin{aligned} \langle i_s(t) \rangle_{T_s} &= \frac{2}{T_s} \int_0^{T_s/2} i_s(\tau) d\tau \\ &= \frac{2}{T_s} \int_0^{T_s/2} I_{s1} \sin(\omega_s \tau - \phi_s) d\tau \\ &= \frac{2}{\pi} I_{s1} \cos(\phi_s) \end{aligned}$$

$$\phi_s = f(f_{sw}/f_r)$$

For narrow of

①


f_{r2c}

\approx

f_{sw}

② High Q

Switch network: equivalent circuit

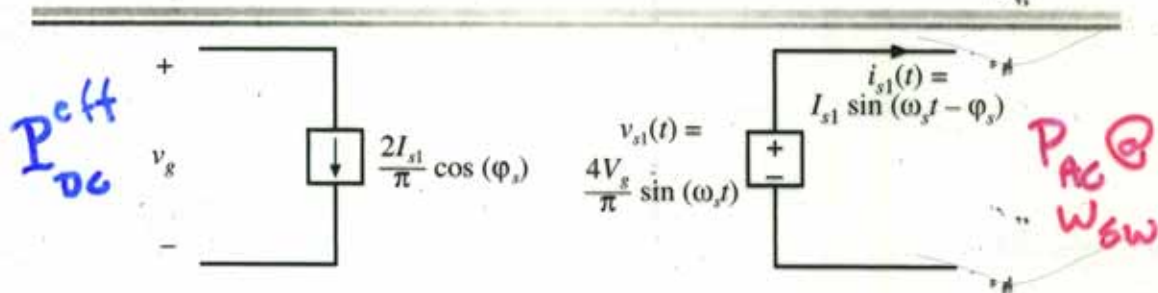



- Switch network converts dc to ac
- Dc components of input port waveforms are modeled
- Fundamental ac components of output port waveforms are modeled
- Model is power conservative: predicted average input and output powers are equal

If lossless switches and lossless L C

$$P_{DC}^{eff} = P_{AC}$$

ϕ_s set by switch phasings and $L Z_{in}$
 Switch network: equivalent circuit

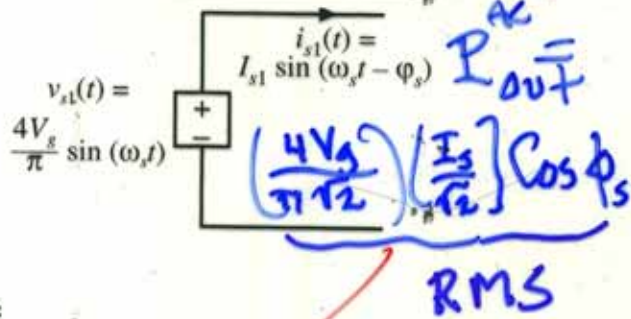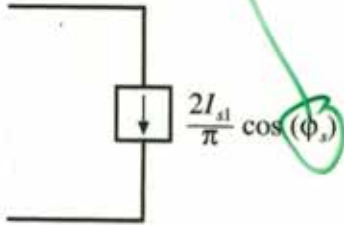$P_{in} = P_{DC}$
 $= V_g I_{eff}$
 CONSTANT DC power




- Switch network converts dc to ac
- Dc components of input port waveforms are modeled
- Fundamental ac components of output port waveforms are modeled
- Model is power conservative: predicted average input and output powers are equal

$P_{in}^{DC} = P_{out}^{DC}$ ON AVERAGE ONLY

High Q

19.1.3 Resonant tank network

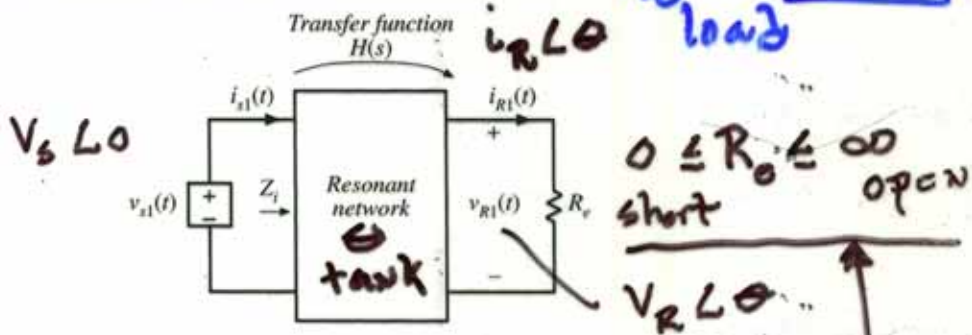

Model of ac waveforms is now reduced to a linear circuit. Tank network is excited by effective sinusoidal voltage (switch network output port), and is load by effective resistive load (rectifier input port).

Can solve for transfer function via conventional linear circuit analysis.

Sw stress each! extrem!

Solution of tank network waveforms

Transfer function:

$$\frac{v_{R1}(s)}{v_{s1}(s)} = H(s)$$

Ratio of peak values of input and output voltages:


$$\frac{V_{R1}}{V_{s1}} = |H(s)|_{s=j\omega_s}$$

Solution for tank output current:

$$i_{R1}(s) = \frac{v_{R1}(s)}{R_e} = \frac{H(s)}{R_e} v_{s1}(s)$$


which has peak magnitude

$$I_{R1} = \frac{|H(s)|_{s=j\omega_s}}{R_e} V_{s1}$$

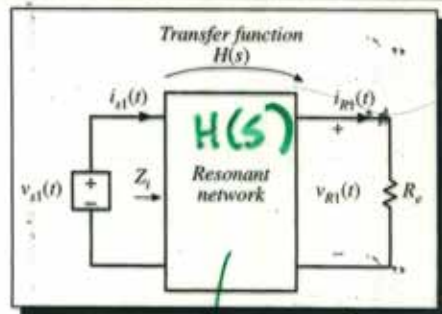

- ① series RLC
- ② parallel RLC
- ③ L-C-C
- ④ C-L-L

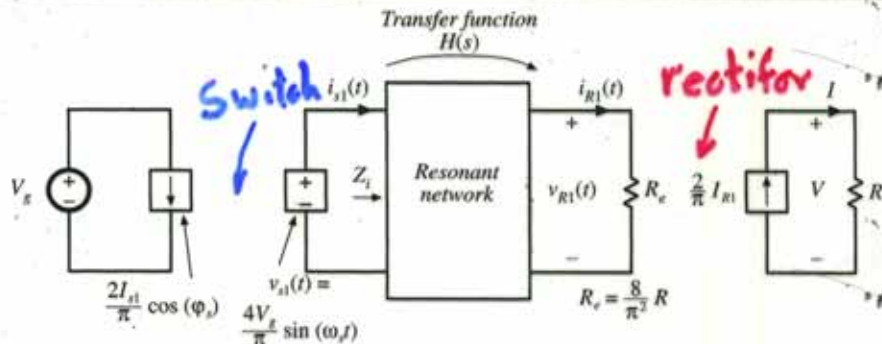19.1.4 Solution of converter voltage conversion ratio $M = V/V_g$



$$M = \frac{V}{V_g} = \underbrace{\left(\frac{R}{I}\right)}_{\left(\frac{V}{I}\right)} \underbrace{\left(\frac{2}{\pi}\right)}_{\left(\frac{I}{I_{R1}}\right)} \underbrace{\left(\frac{1}{R_e}\right)}_{\left(\frac{I_{R1}}{V_{R1}}\right)} \underbrace{\left(|H(s)|_{s=j\omega_s}\right)}_{\left(\frac{V_{R1}}{V_{s1}}\right)} \underbrace{\left(\frac{4}{\pi}\right)}_{\left(\frac{V_{s1}}{V_g}\right)}$$


Eliminate R_e :

$$\frac{V}{V_g} = |H(s)|_{s=j\omega_s}$$

Conversion ratio M

$$\frac{V}{V_g} = \|H(s)\|_{s=j\omega_s}$$

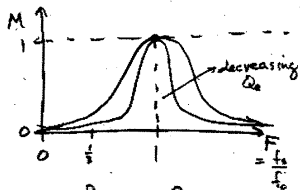
So we have shown that the conversion ratio of a resonant converter, having switch and rectifier networks as in previous slides, is equal to the magnitude of the tank network transfer function. This transfer function is evaluated with the tank loaded by the effective rectifier input resistance R_e .



$$V_R / V_G \approx 5/3$$

$$Q_e = \frac{\omega_0 R_e}{\omega_0} = \frac{R_e}{\left(\frac{\omega_0}{\omega_0} R\right)}$$

What about $\frac{V_C}{V_G}(f)$?

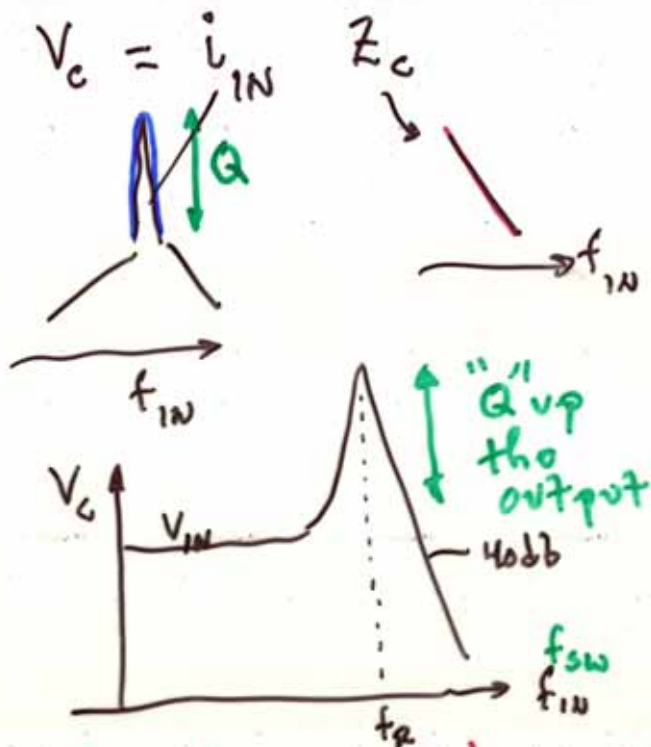


Anticipates parallel resonance
 $f_{sw} > f_r$ boost or buck

Sinusoidal
from tank

rectified i_R

Rectifier dc output port model

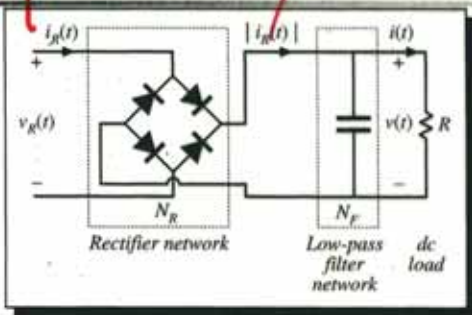


Output capacitor charge balance: dc load current is equal to average rectified tank output current

$$\langle |i_R(t)| \rangle_{T_S} = I$$

Hence

$$I = \frac{2}{T_S} \int_0^{T_S/2} I_{R1} |\sin(\omega t - \phi_R)| dt$$

$$= \frac{2}{\pi} I_{R1}$$

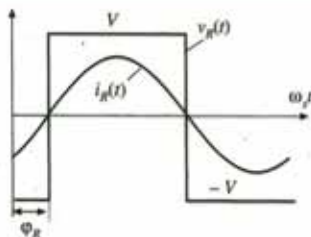



$$|I_R| = \frac{\pi}{2} I_{DC}$$

Rectifier ON $V_{R1} = |V_0^{ac}|$

i
filtered @ f_R

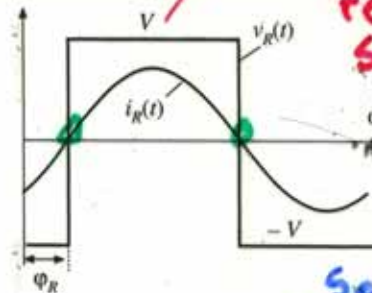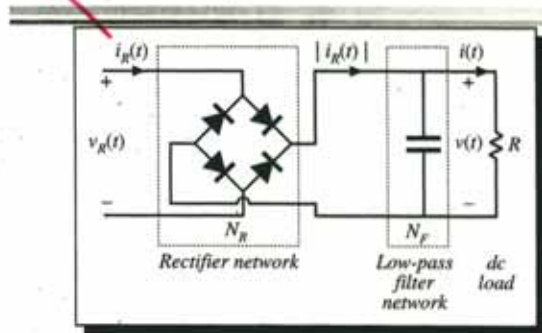19.1.2 Modeling the rectifier and capacitive filter networks

surprise!
 V_R is \square -wave
for as the
rectifier
sees
 $\pm V_{out}$



Set by
tank @
 f_{ω}/f_R

Assume large output filter capacitor, having small ripple.

$v_R(t)$ is a square wave, having zero crossings in phase with tank output current $i_R(t)$.

If $i_R(t)$ is a sinusoid:

$$i_R(t) = I_{R1} \sin(\omega t - \varphi_R)$$

Then $v_R(t)$ has the following Fourier series:

$$v_R(t) = \frac{4V}{\pi} \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{n} \sin(n\omega t - \varphi_n)$$


High Q

Sinusoidal approximation: rectifier


Again, since tank responds only to fundamental components of applied waveforms, harmonics in $v_R(t)$ can be neglected. $v_R(t)$ becomes

$$v_{R1}(t) = \frac{4V}{\pi} \sin(\omega_s t - \phi_R) = V_{R1} \sin(\omega_s t - \phi_R)$$

Actual waveforms

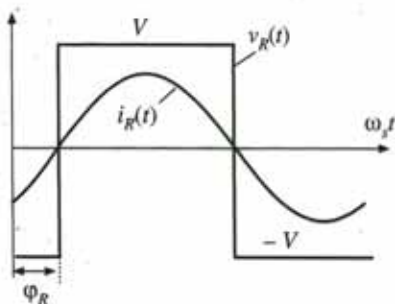

with harmonics ignored

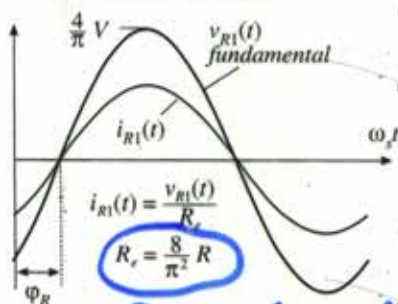

R_{eff} of rectifier

Equivalent circuit of rectifier

$$\frac{\pi}{2} I_{dc} = I_{(avg)}$$

fund: $\frac{4V_{out}}{\pi}$

Rectifier input port:

Fundamental components of current and voltage are sinusoids that are in phase


Hence rectifier presents a resistive load to tank network

Effective resistance R_e is


$$R_e = \frac{v_{R1}(t)}{i_R(t)} = \frac{8}{\pi^2} \frac{V}{I}$$

With a resistive load R , this becomes

$$R_e = \frac{8}{\pi^2} R = 0.8106R$$

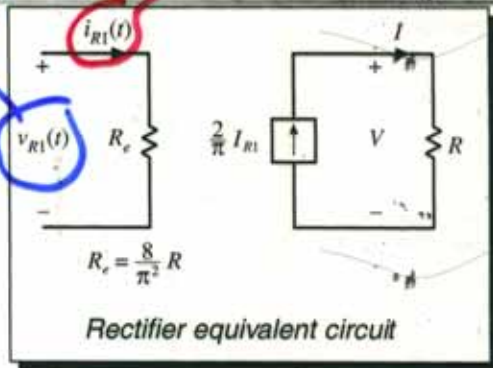

All together

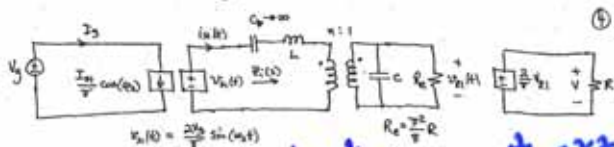

Last resonant ckt.

Solution of model for dc conversion ratio $M = \frac{V_o}{V_s}$:

$$V = \left(\frac{V_{s1}}{V_s} \right) \left(\frac{V_{R1}}{V_{s1}} \right) \left(\frac{V_o}{V_{R1}} \right) = \left(\frac{4}{\pi^2} \right) \|H(j\omega)\|$$

VS text
full-bridge

$\frac{8}{\pi^2}$ Eq 19.27

②

TANK

where the transfer function $H(s)$ is

trsf

$$H(s) = \frac{1}{n} \frac{R_e \parallel \frac{1}{sC}}{\frac{sL}{n} + R_e \parallel \frac{1}{sC}} = \frac{1}{n} \frac{1}{1 + \frac{sL}{nR_e} + \frac{s^2 LC}{n}}$$

$\frac{1}{s}$ divider

new

$Q = f(n)$
 $\omega_0 = f(n)$

with $\omega_0 = \frac{1}{\sqrt{LC}}$
 $Q_e = nR_e \sqrt{\frac{C}{L}}$

$$\|H(j\omega)\| = \frac{1}{n} \frac{1}{\sqrt{(1 - (\frac{\omega}{\omega_0})^2)^2 + (\frac{\omega}{Q\omega_0})^2}} = \frac{1}{n} \frac{1}{\sqrt{(1 - F^2)^2 + (\frac{F}{Q_0})^2}}$$

$$\text{So } M = \frac{4}{\pi^2} \frac{1}{\sqrt{(1 - F^2)^2 + (\frac{F}{Q_0})^2}}$$

This equation is used to plot V vs. f_s on the next page, at maximum load and at minimum load.

Vary R_L by factor 10
 ∞Q_L by factor 10

(5)

Element values

L	10 μ H
C	1.5 μ F
n	20
V_s	160 V
V	3.3 V

R_{load} range 10x

Operating points


at $I =$	20 A	2 A
$R =$	0.165 Ω	1.65 Ω
$R_L =$	0.204 Ω	2.036 Ω
$f_0 =$	821.873 Hz	821.873 Hz
$Q_s =$	1.58	15.77
$f_s =$	1.031,696 Hz	1.156,025 Hz

Max — min

Big Q

min load

\Rightarrow large R

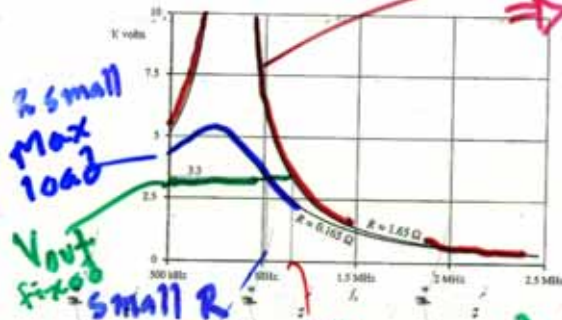

2 small
Max
load

Vout
fixed

small R

max
load

1.03
MHz = f_{op}

min
load

1.15
MHz = f_{op}

f_{op}

f

Vout fixed

\Rightarrow $1.03 \leq f \leq 1.15$

At minimum load:

$$R_e = 2.036 \Omega$$

$$f_s = 1.152 \text{ MHz}$$

$$Q_0 = 15.8$$

$$\|Z\|_{f_s} = 36.0 \Omega$$

$$I_{s1} = \frac{2(140)}{36.0} = 2.83 \text{ A}$$

$$R_{\text{load}} (\text{min}) = \frac{3.3}{2A} \quad (8)$$
$$R_e = \frac{\pi^2}{8} \left(\frac{3.3}{2.0} \right)$$

The peak transistor current is essentially independent of load current. Hence, the conduction loss is also independent of load current. This would lead to poor efficiency at light load.

(9)
Surprise?

$\eta \downarrow$ for large R_L



b) Finding f_s at a given load current

(6)

We know that

$$M = \frac{4}{\pi V^2} \frac{1}{\sqrt{(1-F^2)^2 + \left(\frac{F}{Q_c}\right)^2}}$$

We want to solve for F:

$$\left(\frac{4}{\pi V^2 M}\right)^2 = (1-F^2)^2 + \left(\frac{F}{Q_c}\right)^2 = 1 - 2F^2 + \frac{F^4}{Q_c^2} + F^4$$

So

$$F^4 + F^2\left(\frac{1}{Q_c^2} - 2\right) + 1 - \left(\frac{4}{\pi V^2 M}\right)^2 = 0$$

Quadratic formula:

$$F^2 = \frac{-\left(\frac{1}{Q_c^2} - 2\right) \pm \sqrt{\left(\frac{1}{Q_c^2} - 2\right)^2 - 4 + 4\left(\frac{4}{\pi V^2 M}\right)^2}}{2}$$

Simplify:

$$F = \sqrt{1 - \frac{1 - \sqrt{1 - 4Q_c^2 + 64Q_c^2/\pi^2 V^2 M^2}}{2Q_c^2}}$$

At rated load, $Q_c = 155$

and $f_s = \omega \cdot F \cdot f_0 = 1.03 \text{ MHz}$

At minimum load, $Q_c = 15.8$ and $f_s = 1.156 \text{ MHz}$

(answers to parts b and d)

large R

Max load \Rightarrow small R