

B. BOOST TOPOLOGY:

Inductor is attached to crude dc (rectified mains):
again note that L is preventing kvI violations during switching
as well as storing energy.



- V_{out} NEVER REACHES ZERO. $v_{out}(\text{minimum}) = v_{dc}$
and can exceed v_{dc} *why*
- V_{out} IS UNIPOLAR but can achieve $v_o > v_i$
- $V_o/V_i = 1 / (1-D)$. non-linear dependence on d
will be shown in later lectures
- Note that the input and the output are NOT

electrically isolated from each other as we have a common terminal to both the input and the output. How to easily fix this?? Finally, we consider one special case for the duty cycle- $D=1/2$

Consider the switch duty cycle of $1/2$ and consider the power in the inductor for each switch position.

$$p_{in}(av) = v_{dc}i/2 \text{ while } p_{out}(av) = (v_{out} - v_{dc})i/2 = p(\text{inductor})$$

if no losses occur in switching, wires or in reactive elements:



$$p_{in} = p_{out} \text{ which implies } v_o = 2v_{dc}$$

On the next page we give a qualitative summary of the boost topology for the conditions of the bipolar transistor switch on and off. Note the very different current paths for the two circuit conditions. Of special note is the inductive kick from the series inductor which makes the switch voltage exceed V_{in} when the transistor is switched off. **Why does this occur??**

The boost converter

Suprising?
Role of L:

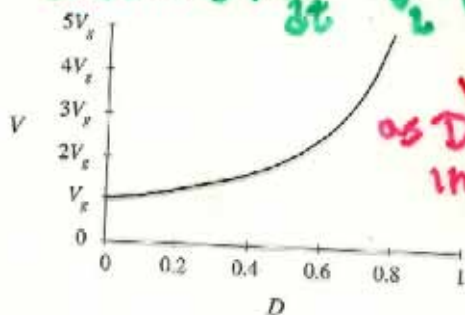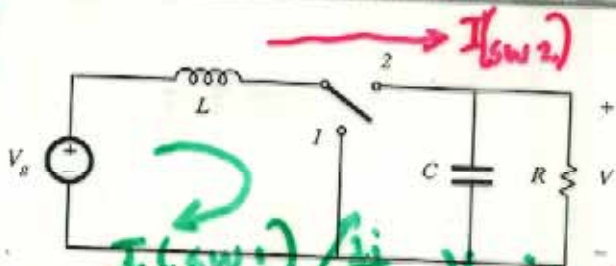$\downarrow \frac{di}{dt}$ V_L is $- \rightarrow +$ Boost



Why $V_o > V_g$?
as D increases
intuitively

Why a boost

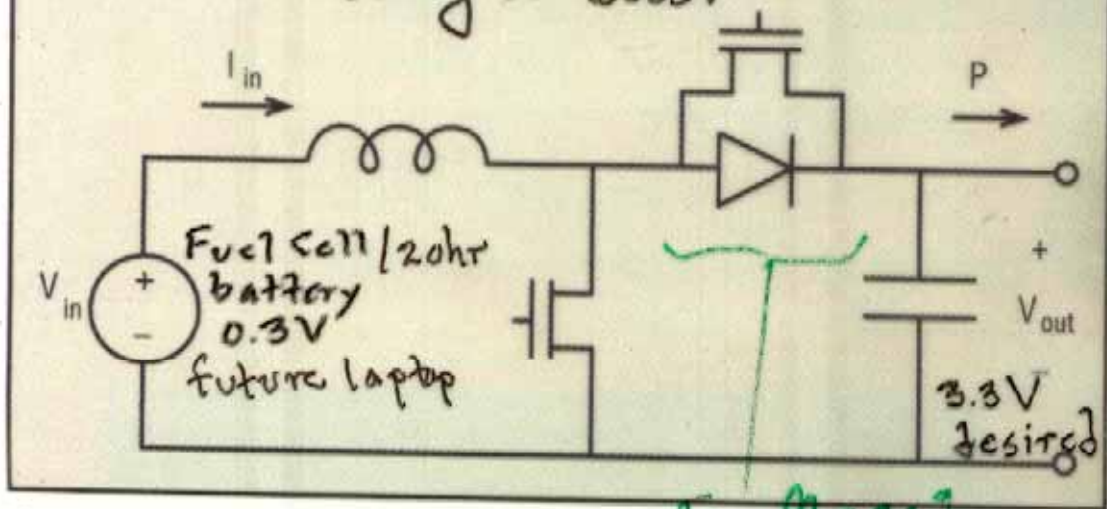


Fig. 1. Synchronous boost converter.


For $\eta = 90\%$
 $R_{ON} = 4m\Omega$

(during analog operation of a fuel cell)

1" long 50mil 2oz Cu PCB trace

Camera flash voltage $\gg V_{battery}$

$V_{IN} = 1.8 - 5.5V$ (DC)

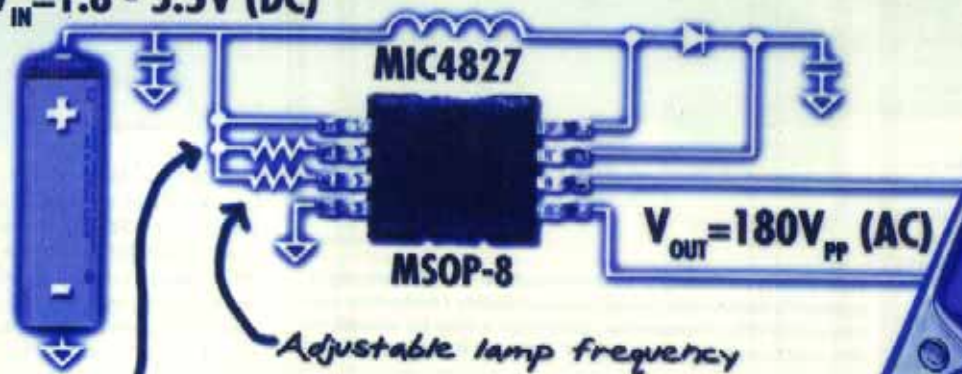

Adjustable boost converter frequency

The Good Stuff

- ◆ 1.8V to 5.5V DC input
- ◆ 160V_{pp} AC output (MIC4826)
- ◆ 180V_{pp} AC output (MIC4827)
- ◆ Independently adjustable boost converter frequency
- ◆ Independently adjustable EL lamp frequency
- ◆ <0.1μA shutdown current
- ◆ Small MSOP-8 package

V_{IN}
 V_{out} for lamp

Subinterval 1: switch in position 1

Inductor voltage and capacitor current


$$v_L = V_s$$

$$i_C = -v / R$$

Small ripple approximation:

$$v_L = V_s$$

$$i_C = -V / R$$

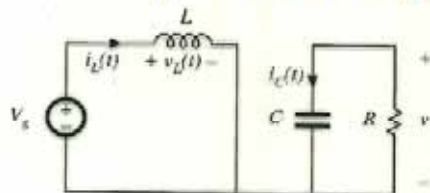

Subinterval 2: switch in position 2

di/dt is \ominus

Inductor voltage and capacitor current

$$v_L = V_g - v$$


$$i_C = i_L - v/R$$

Small ripple approximation:

$$v_L = V_g - V$$

$$i_C = I - V/R$$

↑
do inductor
current


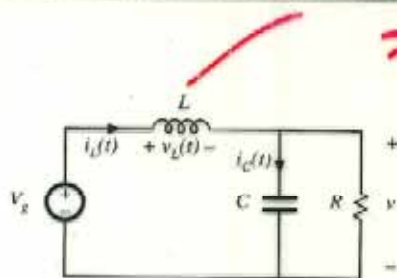


⇒
 V_L is
- → +
Boost

$$V_0 = \frac{V_g}{D'} = \frac{V_g}{1-D}$$

$$D = \frac{1}{2} \quad V_0 = ?$$

The boost converter

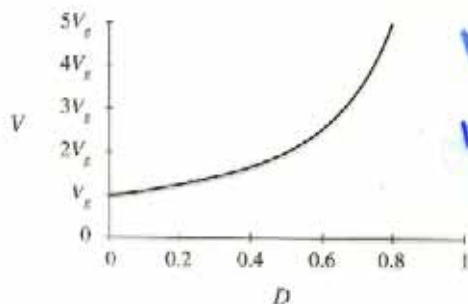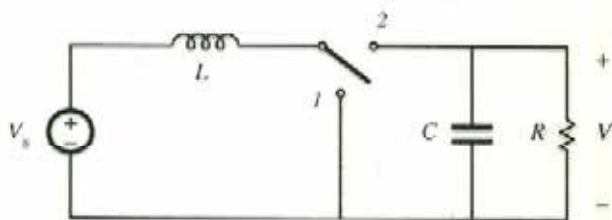

Why $V_o^{DC} > V_{in}^{DC}$
intuitively as
 $D \uparrow$

Pg 22


2.3

Switch Realization


Boost converter example

implies $V_{out} > V_{in}$

Boost converter
with ideal switch

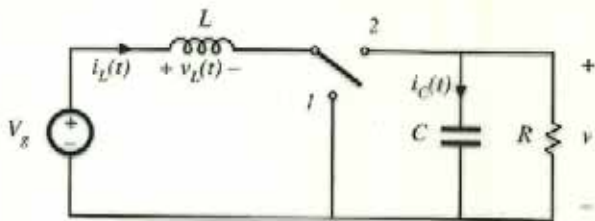

Realization using
power MOSFET
and diode

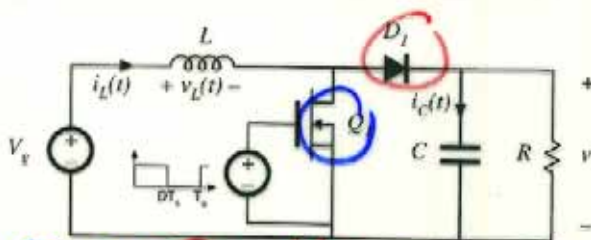


Q_1 ON D_1 off why?


Fig
2.13
Pg
22

Use solid state switches

Non-synchronous Boost

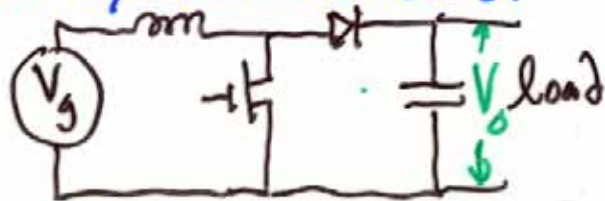

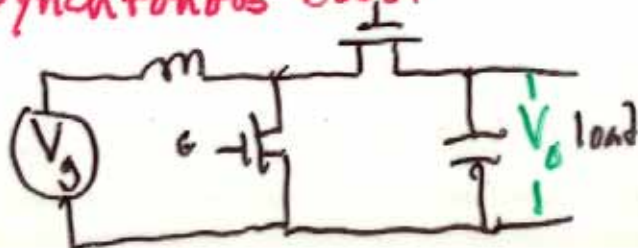$V_0 \gg V_g$ diode ok but...
Synchronous Boost



Eliminates diode loss
due to:
 Q_{rr} , V_D^{ON} Details
Ch3

Determination of inductor current ripple

I of FET

Δi
spec
easy

Fig 2.78
p 26

I of diode

Inductor current slope during subinterval 1:


$$\frac{di_L(t)}{dt} = \frac{v_L(t)}{L} = \frac{V_g}{L}$$

up $\frac{di}{dt}$

Inductor current slope during subinterval 2:

$$\frac{di_L(t)}{dt} = \frac{v_L(t)}{L} = \frac{V_g - V}{L}$$

down $\frac{di}{dt}$

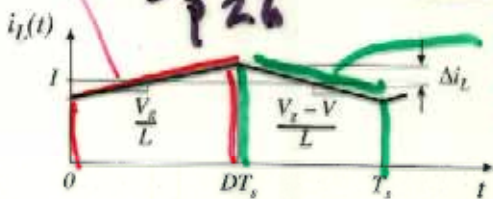

Change in inductor current during subinterval 1 is (slope) (length of subinterval):

$$2\Delta i_L = \frac{V_g}{L} DT_s$$

Solve for peak ripple:

$$\Delta i_L = \frac{V_g}{2L} DT_s$$

- Choose L such that desired ripple magnitude is obtained

Δi spec from
 $e = L \frac{di}{dt}$

$L \sim D$

L sets Δi

Determination of capacitor voltage ripple

ΔV
spec
easy

Fig 2.19
p 26


$$I/C = \frac{\Delta V}{\Delta t}$$

Capacitor voltage slope during subinterval 1:

$$\frac{dv_c(t)}{dt} = \frac{i_c(t)}{C} = \frac{-V}{RC}$$

Capacitor voltage slope during subinterval 2:
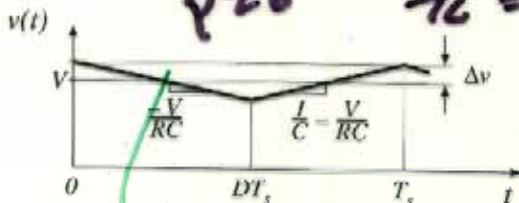
$$\frac{dv_c(t)}{dt} = \frac{i_c(t)}{C} = \frac{I}{C} - \frac{V}{RC}$$



Small ripple

Change in capacitor voltage during subinterval 1 is (slope) (length of subinterval):

$$-2\Delta v = \frac{-V}{RC} DT_s$$

Solve for peak ripple:

$$\Delta v = \frac{V}{2RC} DT_s$$


C ~ D

- Choose C such that desired voltage ripple magnitude is obtained
- In practice, capacitor equivalent series resistance (esr) leads to increased voltage ripple

$\Delta i_c R_{ESR}$ *

C sets ΔV

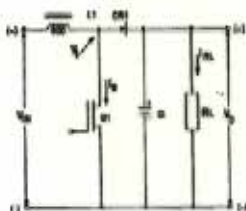

TYPE OF CONVERTER**CIRCUIT CONFIGURATION****IDEAL TRANSFER FUNCTION****PEAK DRAIN CURRENT****PEAK DRAIN VOLTAGE****AVERAGE DIODE CURRENTS****Boost (Step Up)**

$$\frac{V_0}{V_{IN}} = \frac{T_S}{T_S - t_{on}} = \frac{1}{(1-D)}$$

$$I_{D_{MAX}} = I_{RL} \left(\frac{1}{(1-D)} \right) + \frac{\Delta I_L}{2}$$

$$V_{DS} = V_0 + V_D \quad \text{--- diode}$$

$$I_{CR1} = I_{RL}$$

VOLTAGES (VRM)

$$V_{RM} = V_0$$

VOLTAGE AND CURRENT WAVEFORMS

$i_L = i + i_q$
is small ripple

#2 of 11
Not small ripple

ADVANTAGES

High efficiency, simple, no transformer. Low input ripple current.

DISADVANTAGES

No isolation between input and output. High peak collector current. Only one output is possible. Regulator loop hard to stabilize. High output ripple. Unable to control short-circuit current.

TYPICAL APPLICATIONS


Power-factor correction. Battery up-converters.

APPLICABLE HARRIS PRODUCTS

HIP5061, ICL7667, HU400




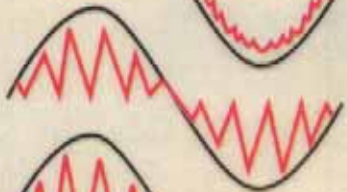Typical input voltage and current:
continuous conduction mode



Typical input voltage and current:
critical conduction mode

Lab try small signal

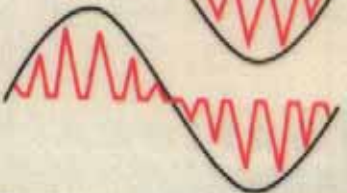

Typical input voltage and current:
discontinuous conduction mode

Ch5

Fig. 1. Comparison of conduction modes for a boost converter.

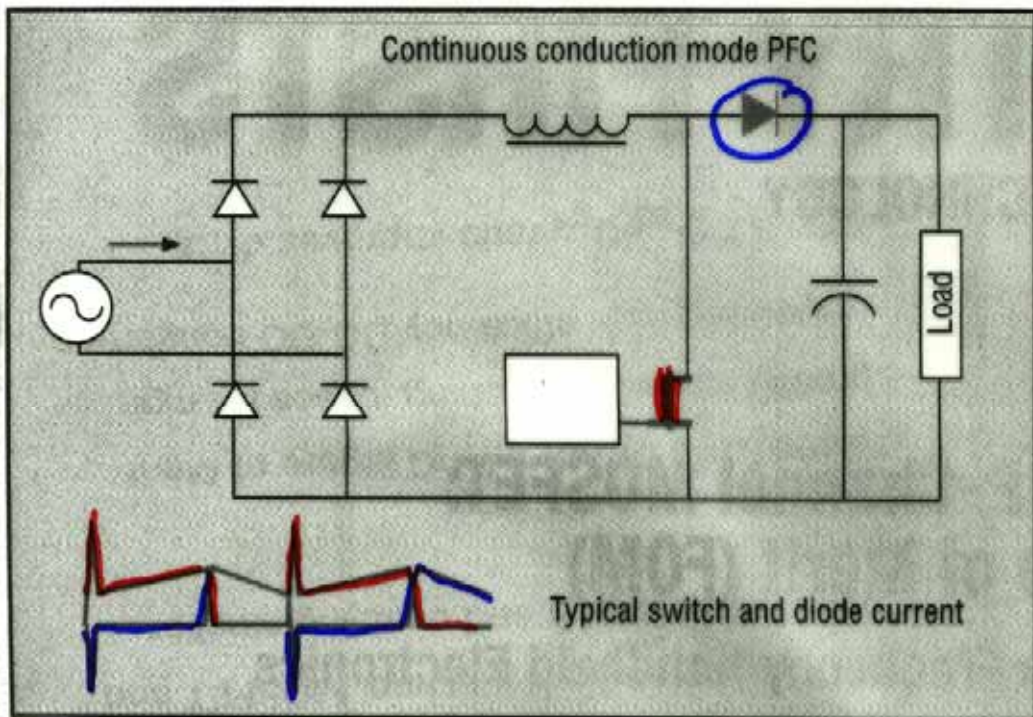



Fig.2. Typical MOSFET and diode current waveforms.

high-
advan-
at hi

It's A

Th
of re
pacit
form
able
curre

Es
ply c
are a
desig

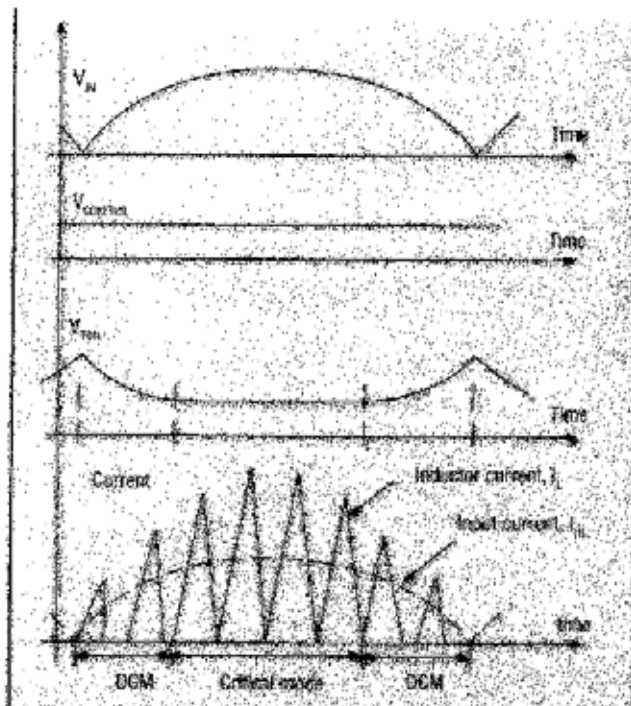

The timing diagram of the PFC stage reveals key voltage and current parameters as the controller transitions between discontinuous conduction mode and critical conduction modes.


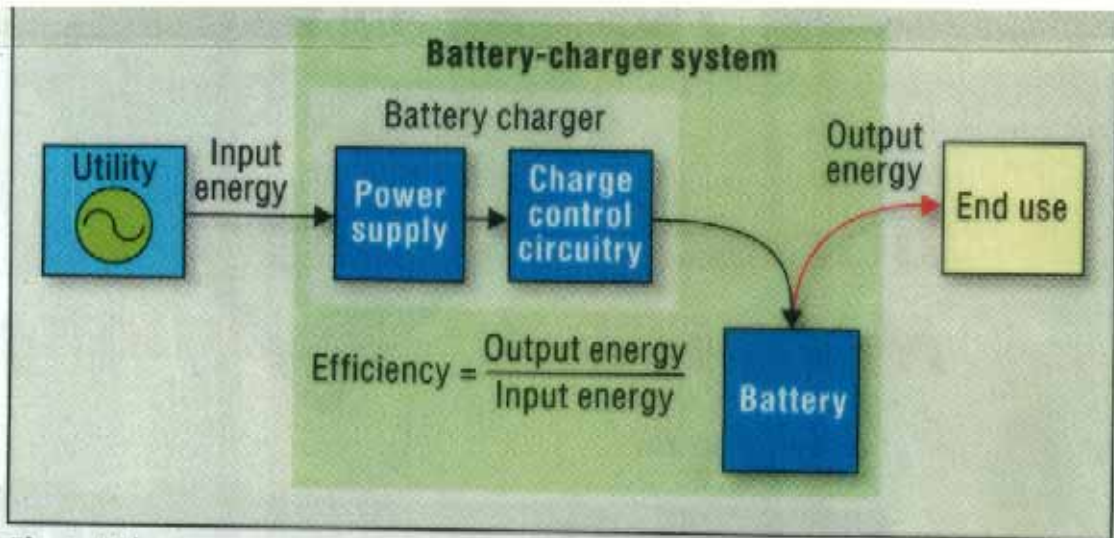


Fig. 1. When measuring battery-charger efficiency, the ac-dc power supply, the charge control circuitry, and the battery should all be counted as parts of the battery-charger system.

TYPE OF CONVERTER

CIRCUIT CONFIGURATION

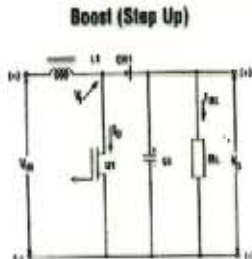

IDEAL TRANSFER FUNCTION

$$\frac{V_0}{V_{IN}} = \frac{T_S}{T_S - t_{on}} = \frac{1}{1-D}$$

PEAK DRAIN CURRENT

$$I_{DMAX} = I_{RL} \left(\frac{1}{1-D} \right) + \frac{\Delta I_{L1}}{2}$$

PEAK DRAIN VOLTAGE

$$V_{DS} = V_0 + V_D$$


AVERAGE DIODE CURRENTS

$$I_{CR1} = I_{RL}$$

DIODE VOLTAGES (VRM)

$$V_{RM} = V_0$$

VOLTAGE AND CURRENT WAVEFORMS

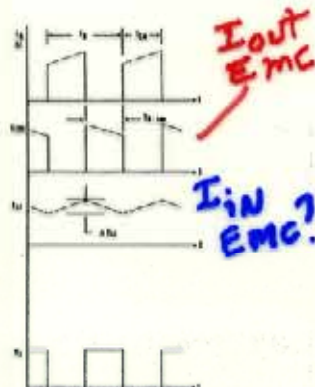

ADVANTAGES

High efficiency, simple, no transformer. Low input ripple current.

DISADVANTAGES


No isolation between input and output. High peak collector current. Only one output is possible. Regulator loop hard to stabilize. High output ripple. Unable to control short-circuit current.

TYPICAL APPLICATIONS

Power-factor correction. Battery up-converters.

APPLICABLE HARRIS PRODUCTS

HP9061, ICL7667, 1W400

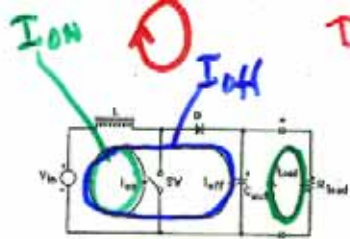


A basic flyback-mode converter (boost converter) circuit

DCM
Ch 5
Spice Lab
 $i_L \rightarrow 0$

V_{off}
Spec on
FET


look ahead
Ch 5
 $i_L = 0$

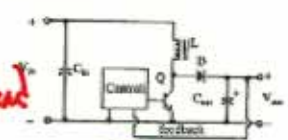

$$I_{off} = \frac{5.5 \cdot P_{out}}{V_{max}} = 1.5 A$$

$$V_{off} = V_{in} = V_{DS}$$

$$P_{off} = 0.15 W$$

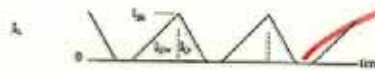


The boost regulator topology

? $i_L = 0$
 \Rightarrow

For now realize that the boost circuit while delivering an output voltage above $V(in)$ does have to ask the solid state switch to handle a **peak current 6 times the nominal average current** when the switch is on. When the switch is off the solid state switch must withstand across itself a voltage up to the full output value.



Another unemployed
English major.

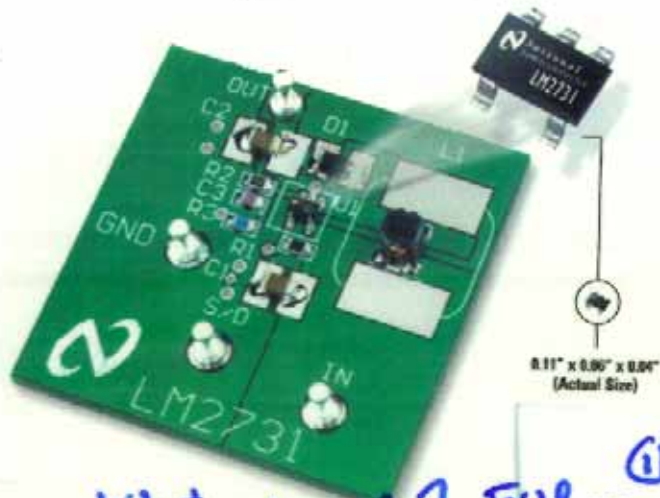


What circuit? Either ① ?
② ?



National Semi Boost

Talk #1

LM2731 Typical Application

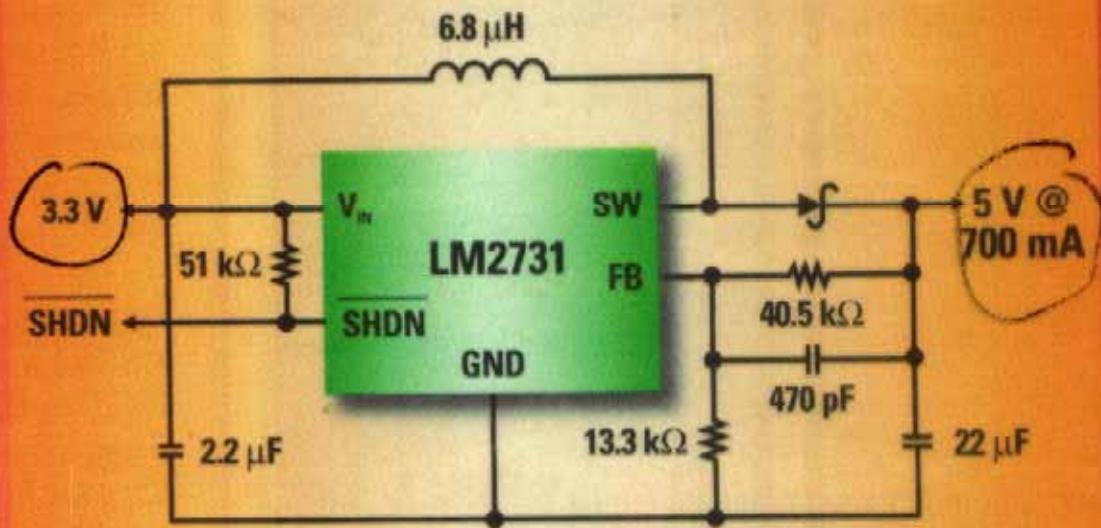

LM2731/33: SOT-23 Switchers


Establish New Standards In Power Density, Efficiency, And Performance

- 1.6 MHz-(X), 0.6 MHz-(Y)
Switching Frequency Options
- Up to 90% Conversion Efficiency
- Low $r_{DS(ON)}$ DMOS Power Switch
- 1A, 40 V Switch (LM2733)
- 1.8A, 22 V Switch (LM2731)
- Wide Input Voltage Range (2.7 V to 14 V)
- Low Shutdown Current ($<1 \mu A$)
- Current-Mode Control for Superior Performance Over Wide Input Voltage Range

*Diode
why*

Ideal for Use in USB/xDSL Modems,
Digital Cameras, and Cellular Handsets
(esp. White-LED Backlights and Flash)

TPS6110x

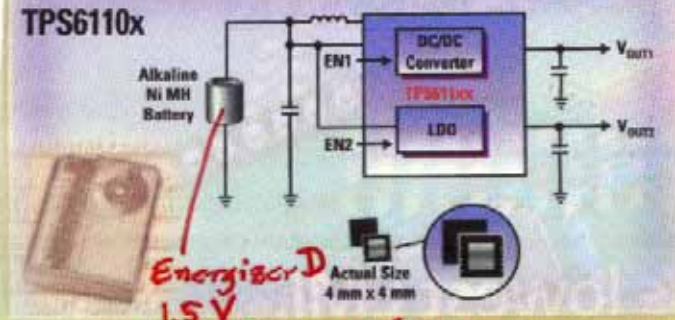

Energizer D
1.5V

and sinking vs time

► 95% efficient dual output boost converter with integrated LDO for 1-cell/2-cell alkaline/NiMH applications


Applications

- All 1-cell or 2-cell alkaline/NiMH battery-operated products like:
 - Digital still camera
 - Internet audio player
 - PDA
 - Portable meter

Features

- Synchronous 95% efficient boost with 200-mA output current from 0.9-V supply
- Input: 0.8 V to 3.3 V output: up to 5.5 V
- 120-mA LDO for second output voltage
- 4x4 mm² QFN/MLP package
- 65- μ A quiescent current
- Pricing starts at \$1.75 in quantities of 1,000

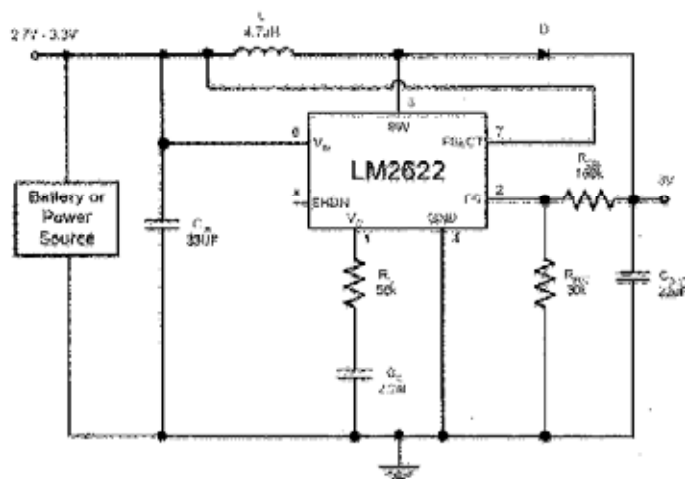High-Frequency Boost: Integrated Regulator



Boost @ 1.3MHz – tiny external components

National Semiconductor

▼ Features


- High Efficiency: Up to 95%
- 4-Phase, 8MHz Operation
- 5A Rated Switch Current
- Ultralow Output Ripple
- Output Disconnect and Inrush Current Limiting
- Only 12 μ A Quiescent Current
- 5mm x 5mm QFN Package
- Footprint < 3cm², \leq 2mm Profile



Fig. 2. Photograph of sample boost converter.


efficiency is greater than 85%. For an
some load efficiency is only 67%. Do

Typical Application

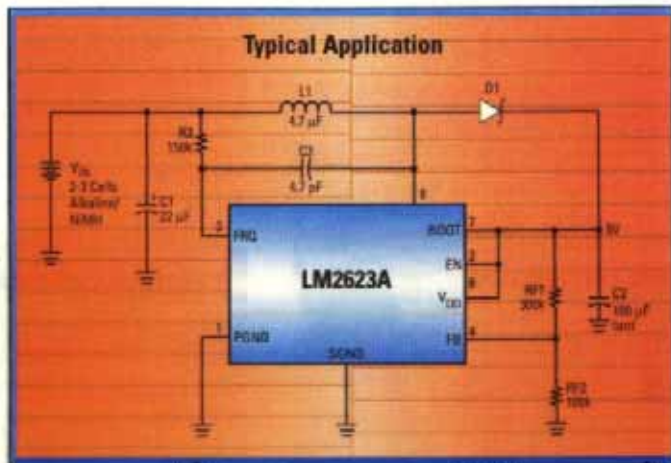

Chapter 3 Efficiency/Losses

Efficiency vs. V_{in} @ $V_{out} = 5V$

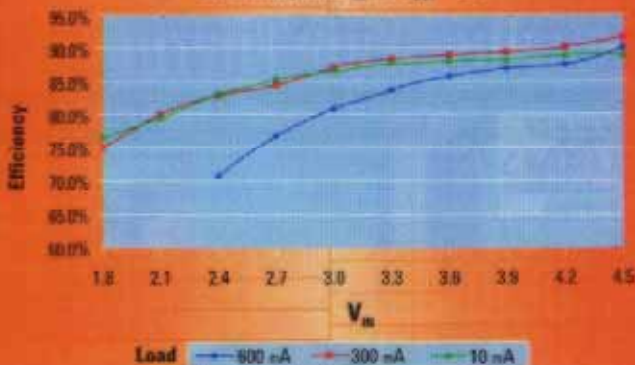

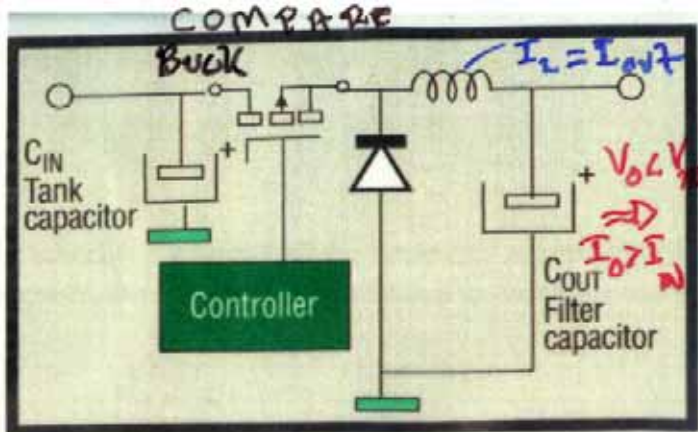


Fig. 1. Basic schematic for a buck converter.



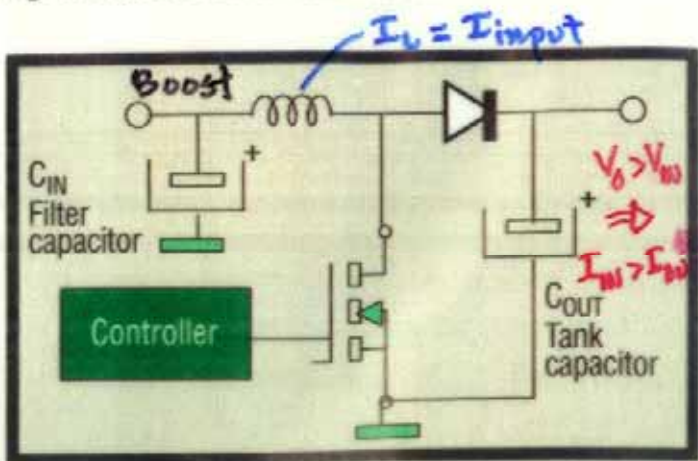


Fig. 2. Basic schematic for a boost converter.

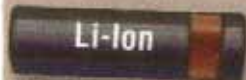


Li-Ion

or

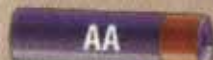


AA

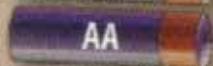

AA

or

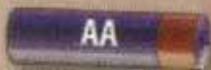

AA



LTC3400

95% Efficient ThinSOT
Synchronous Boost
 $V_{out} = 5V @ 300mA$



LTC3440

96% Efficient MSOP
Buck/Boost
 $V_{out} = 3.3V @ 600mA$


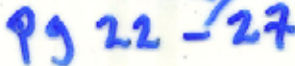


LTC3405


96% Efficient ThinSOT
Synchronous Buck
 $V_{out} = 1.8V @ 300mA$

Chapter 2

Principles of Steady-State Converter Analysis

- 2.1. Introduction
- 2.2. Inductor volt-second balance, capacitor charge balance, and the small ripple approximation
- 2.3. Boost converter example  Today
- 2.4. Cuk converter example 
- 2.5. Estimating the ripple in converters containing two-pole low-pass filters
- 2.6. Summary of key points


SIMPLE SWITCH MODE CONVERTERS

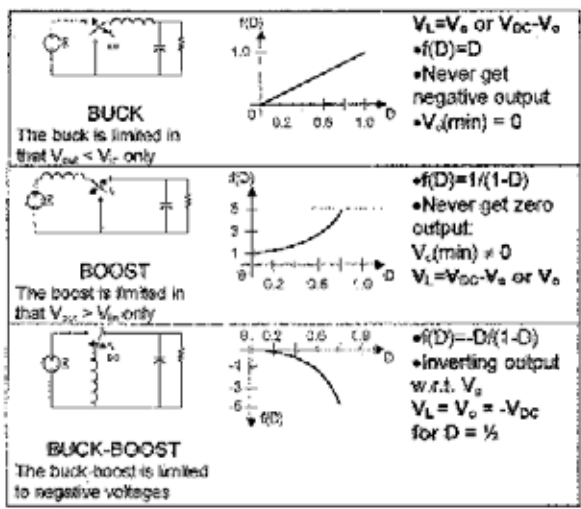

4. UNSYMMETRIC i_L AND v_C WAVEFORMS OF EQUAL INTEGRATED AREA IN THE ABOVE THREE CONVERTERS

for Single Cell Li-Ion USB Applications

Total Power Solutions

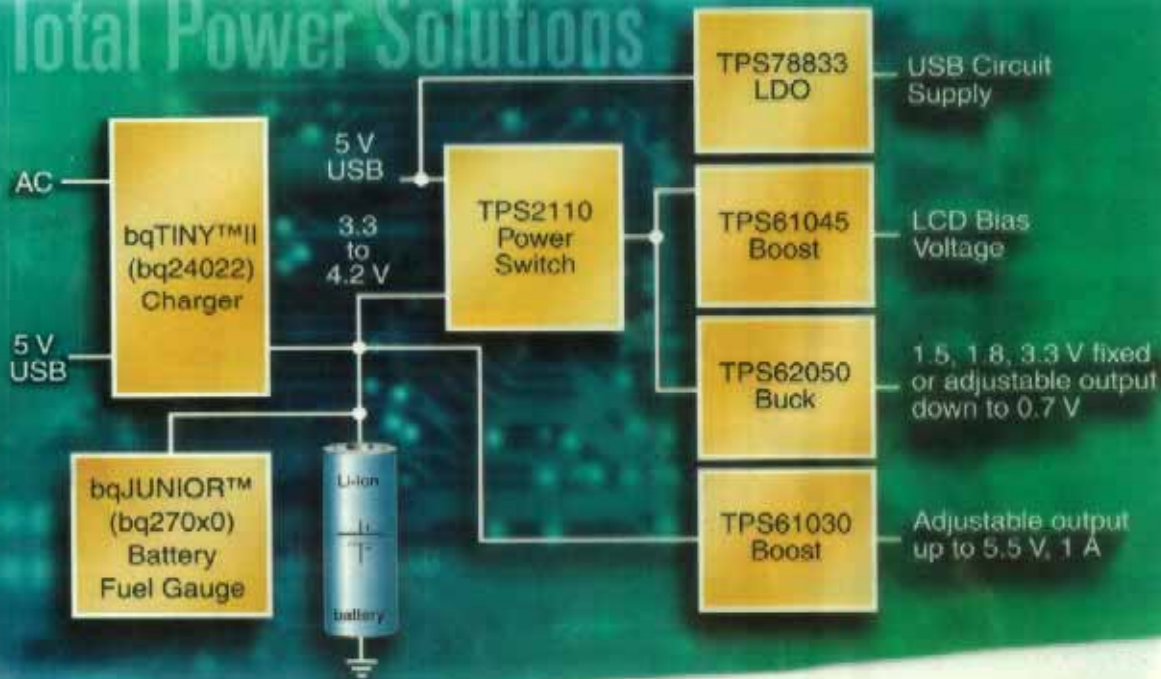

2.6 Summary of Key Points

1. The dc component of a converter waveform is given by its average value, or the integral over one switching period, divided by the switching period. Solution of a dc-dc converter to find its dc, or steady state, voltages and currents therefore involves averaging the waveforms.
2. The linear ripple approximation greatly simplifies the analysis. In a well-designed converter, the switching ripples in the inductor currents and capacitor voltages are small compared to the respective dc components, and can be neglected.
3. The principle of inductor volt-second balance allows determination of the dc voltage components in any switching converter. In steady-state, the average voltage applied to an inductor must be zero.

$$\left. \begin{array}{l} V_0 \text{ (buck)} \\ = ? \\ V_{in} \end{array} \right\}$$

Δi_L
 Δv_C
DC

$$I_{DC} = \text{constant}$$



Summary of Chapter 2

4. The principle of capacitor charge balance allows determination of the dc components of the inductor currents in a switching converter. In steady-state, the average current applied to a capacitor must be zero.
5. By knowledge of the slopes of the inductor current and capacitor voltage waveforms, the ac switching ripple magnitudes may be computed. Inductance and capacitance values can then be chosen to obtain desired ripple magnitudes.
6. In converters containing multiple-pole filters, continuous (nonpulsating) voltages and currents are applied to one or more of the inductors or capacitors. Computation of the ac switching ripple in these elements can be done using capacitor charge and/or inductor flux-linkage arguments, without use of the small-ripple approximation.
7. Converters capable of increasing (boost), decreasing (buck), and inverting the voltage polarity (buck-boost and Cuk) have been described. Converter circuits are explored more fully in a later chapter.

$V_c \approx$
Constant

} Double
Pole
Case

Entry Level Engineer Expectations

	Proficiency
✓ Switching power supply <u>technology</u>	4
✓ Analog circuit design and <u>analysis</u> techniques	3
✓ Understanding of magnetics	3
✓ Simulation skills SPICE	3
• Basic understanding	
✓ <u>Communication skills</u>	5
• Written  Word	
• Oral  Powerpoint	
✓ <u>Teamwork experience and skills</u>	5

Group Project
Oral Talks
Written Papers

Experienced Engineer Expectations

	Proficiency
✓ Power supply design experience	5
✓ Analog circuit design and analysis	5
✓ Magnetic component design and implementation	5
✓ Analog simulation	5
✓ Digital design	4
✓ Digital simulation	3
✓ <u>Verbal communication</u>	5
✓ <u>Written communication</u>	5
✓ <u>Teamwork experience and skills</u>	5

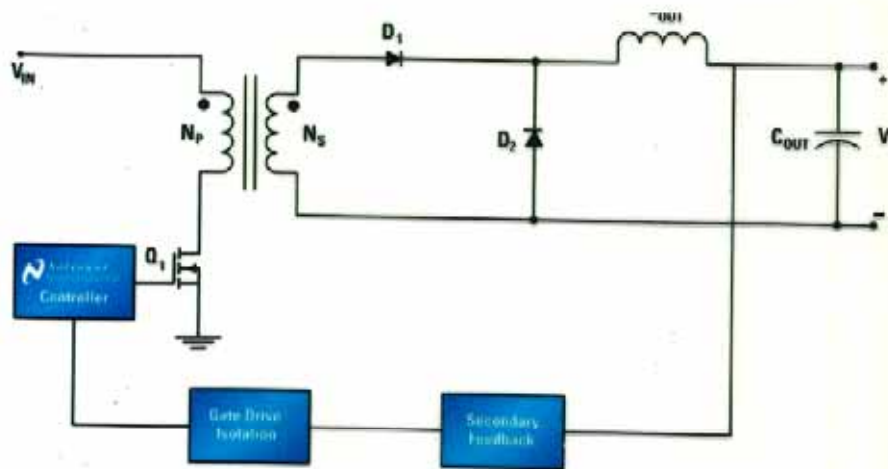


Figure 2. Isolated power converter with output synchronous rectification

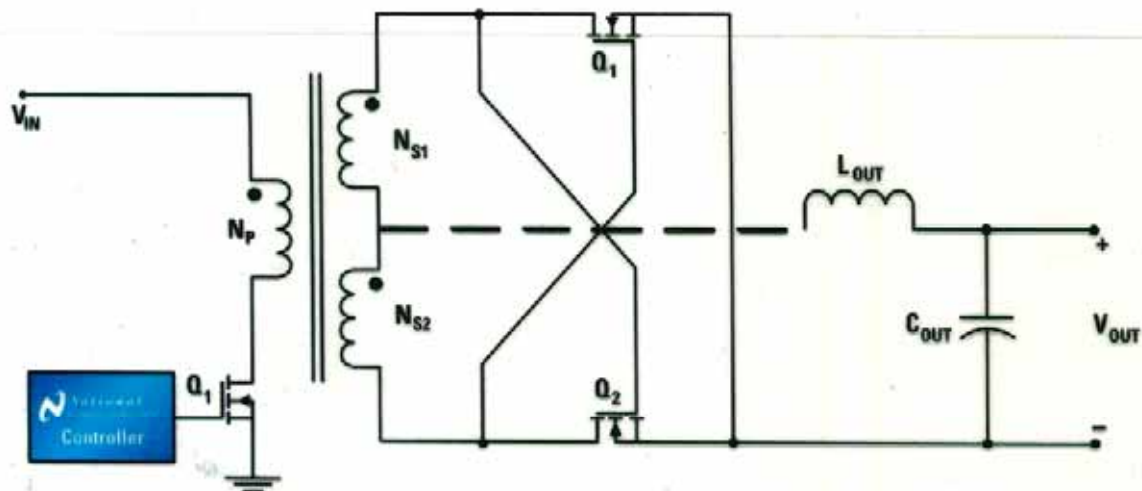


Figure 3. Self-driven synchronous rectification output stage


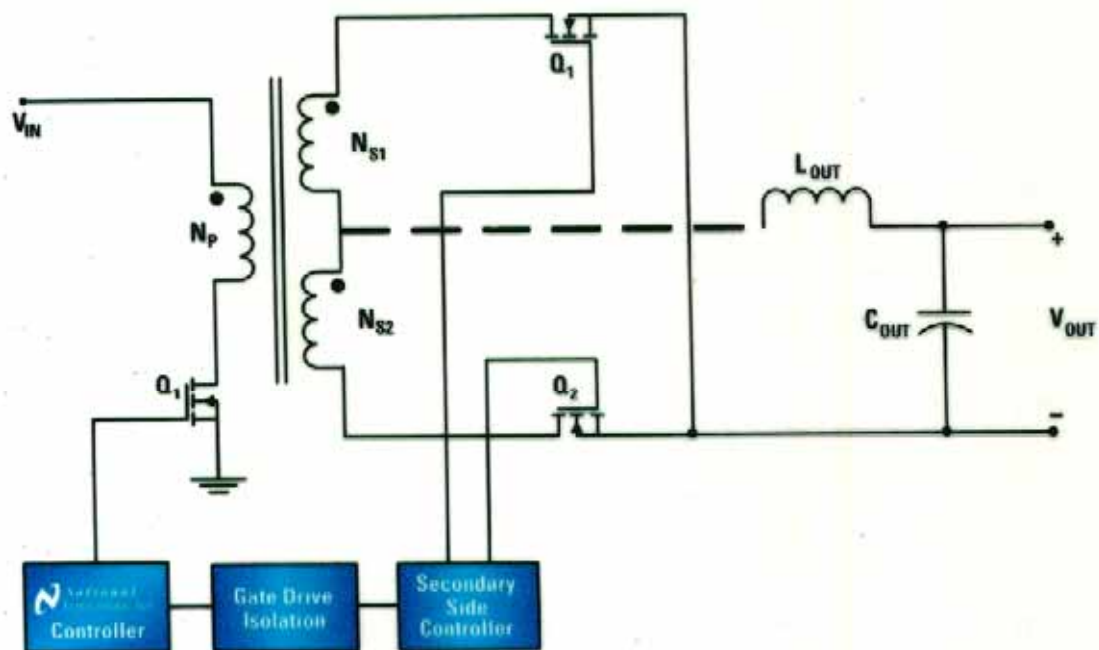


Figure 4. Control-driven synchronous rectification output stage

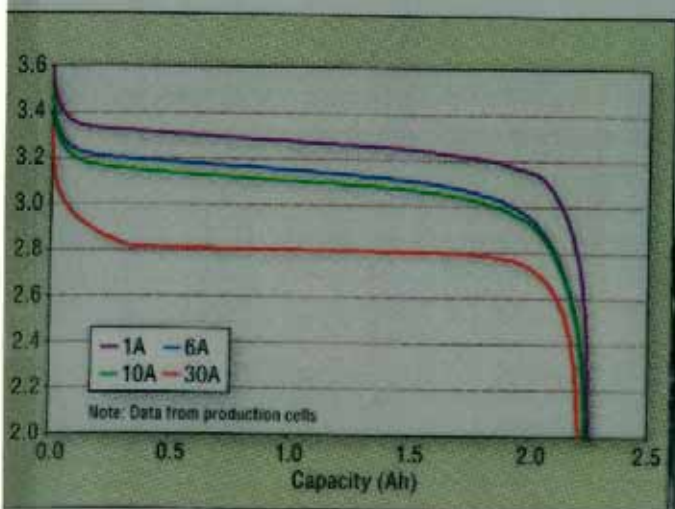


Based on a lithium-iron-phosphate cathode, a Li-ion cell from supports high-drain rates, but has a lower operating voltage cells using more conventional cathode materials.

LM2731/33: SOT-23 Switchers Establish New Standards In Power Density, Efficiency, And Performance

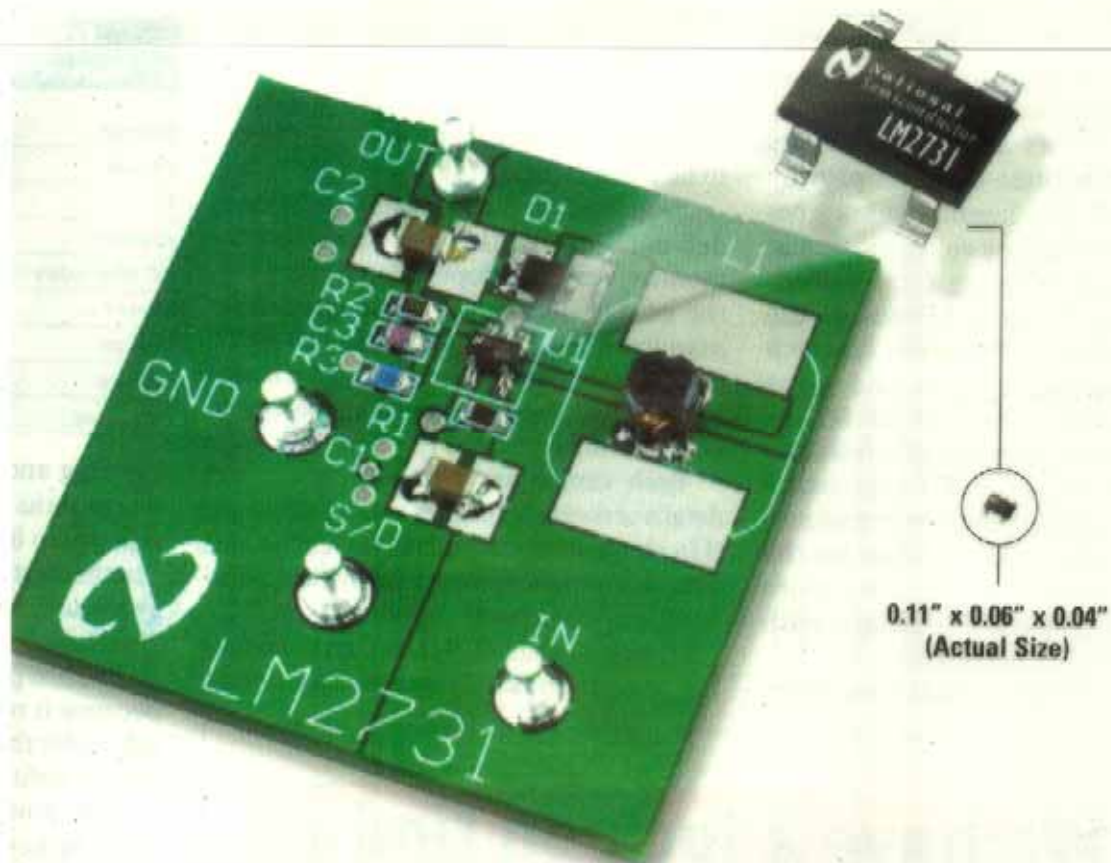- 1.6 MHz-(X), 0.6 MHz-(Y)
Switching Frequency Options
- Up to 90% Conversion Efficiency
- Low t_{prop} DMOS Power Switch
- 1A, 40 V Switch (LM2733)
- 1.8A, 22 V Switch (LM2731)
- Wide Input Voltage Range (2.7 V to 14 V)
- Low Shutdown Current (<1 μA)
- Current-Mode Control for Superior Performance
Over Wide Input Voltage Range





0.11" x 0.06" x 0.04"
(Actual Size)

2.6 Summary of Key Points

1. The dc component of a converter waveform is given by its average value, or the integral over one switching period, divided by the switching period. Solution of a dc-dc converter to find its dc, or steady-state, voltages and currents therefore involves averaging the waveforms.
2. The linear ripple approximation greatly simplifies the analysis. In a well-designed converter, the switching ripples in the inductor currents and capacitor voltages are small compared to the respective dc components, and can be neglected.
3. The principle of inductor volt-second balance allows determination of the dc voltage components in any switching converter. In steady-state, the average voltage applied to an inductor must be zero.

Boost converter analysis

$I_{DC} + \Delta i_L(t)$

original
converter



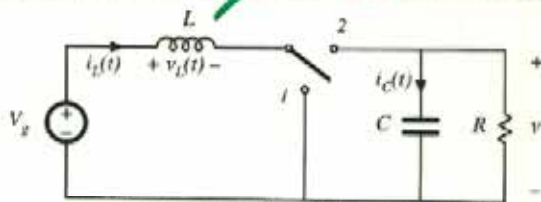


Fig 2.14
pg 23

switch in position 1

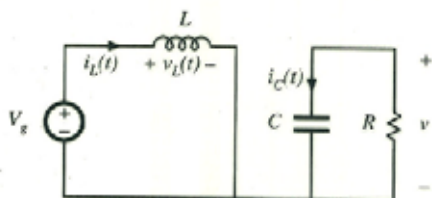

switch in position 2

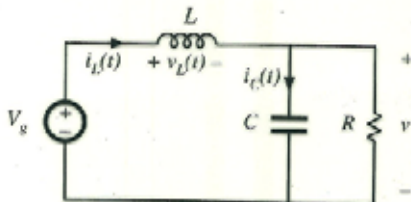

Inductor volt-second balance

Net volt-seconds applied to inductor over one switching period:

$$\int_0^{T_s} v_L(t) dt = (V_g) DT_s + (V_g - V) D'T_s$$

Equate to zero and collect terms:


$$V_g (D + D') - V D' = 0$$

Solve for V:

$$V = \frac{V_g}{D}$$

The voltage conversion ratio is therefore

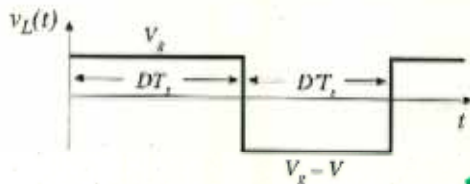
$$M(D) = \frac{V}{V_g} = \frac{1}{D} = \frac{1}{1-D}$$



sets $\frac{V_o}{V_{in}}$

OK? $D \rightarrow 1$ $V_{out} = ?$

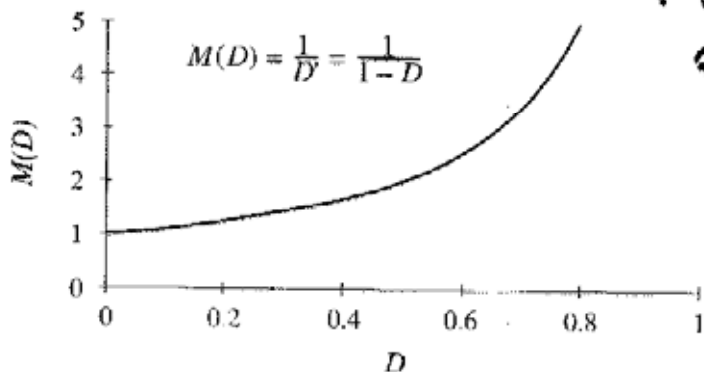Conversion ratio $M(D)$ of the boost converter



Determination of inductor current dc component

Sets $I_L(DC)$

Capacitor charge balance:

$$\int_0^{T_s} i_c(t) dt = \left(-\frac{V}{R}\right) DT_s + \left(I - \frac{V}{R}\right) D'T_s$$

Collect terms and equate to zero:

$$-\frac{V}{R}(D + D') + I D' = 0$$

Solve for I :

$$I = \frac{V}{D'R}$$

Eliminate V to express in terms of V_s :

$$I = \frac{V_s}{D'^2 R}$$

effective dc value


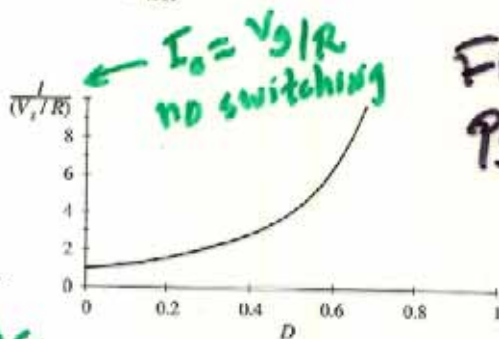
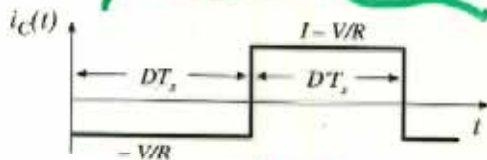


Fig 2.17
Pg 25


Capacitor current and voltage, buck example

Must not neglect inductor current ripple!

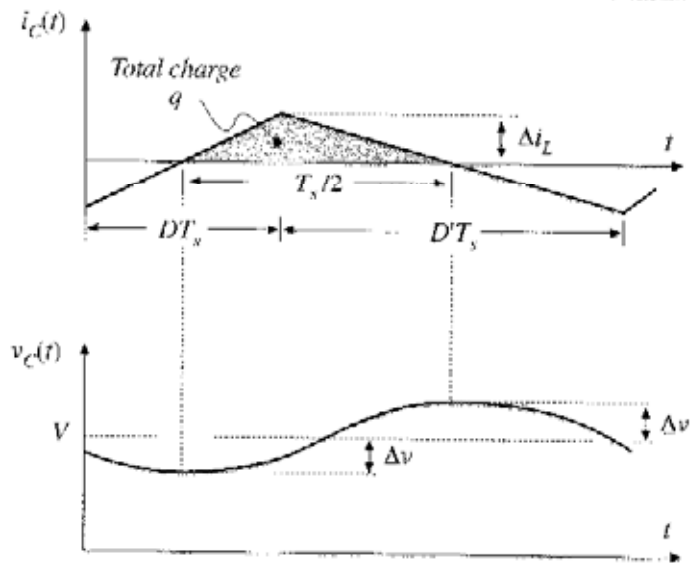If the capacitor voltage ripple is small, then essentially all of the ac component of inductor current flows through the capacitor.



Estimating capacitor voltage ripple Δv

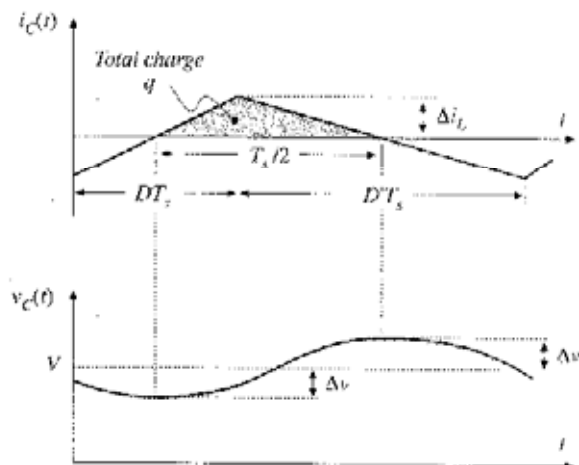


Current $i_C(t)$ is positive for half of the switching period. This positive current causes the capacitor voltage $v_C(t)$ to increase between its minimum and maximum extrema. During this time, the total charge q is deposited on the capacitor plates, where

$$q = C (2\Delta v)$$

$$\begin{aligned} (\text{change in charge}) &= \\ C (\text{change in voltage}) \end{aligned}$$

Estimating capacitor voltage ripple Δv

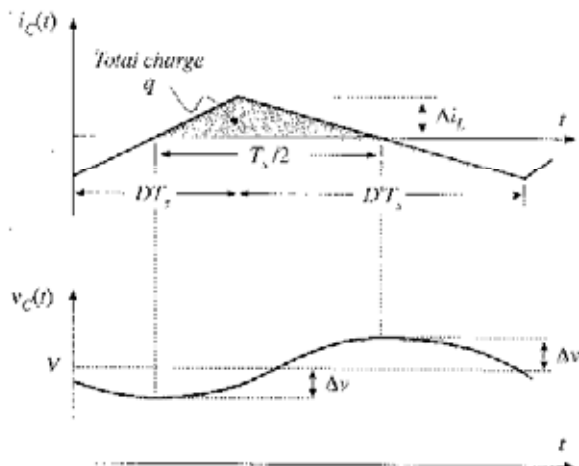

The total charge q is the area of the triangle, as shown:

$$q = \frac{1}{2} \Delta i_L \frac{T_s}{2}$$



Eliminate q and solve for Δv :

$$\Delta v = \frac{\Delta i_L T_s}{8 C}$$

Note: in practice, capacitor equivalent series resistance (esr) further increases Δv .

Inductor current ripple in two-pole filters

Example:
problem 2.9

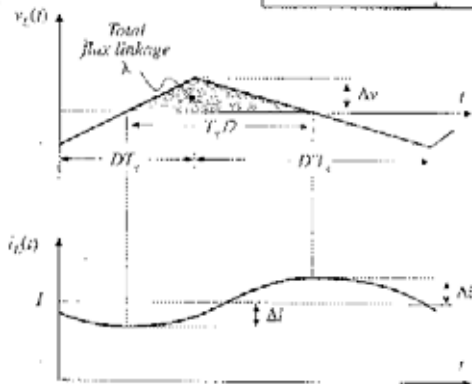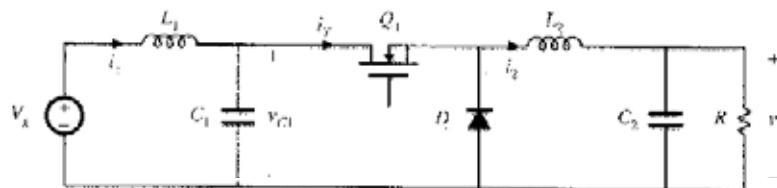

can use similar arguments, with
 $\lambda = L (2\Delta i)$

λ = inductor flux linkages
= inductor volt-seconds

2.6 Summary of Key Points

1. The dc component of a converter waveform is given by its average value, or the integral over one switching period, divided by the switching period. Solution of a dc-dc converter to find its dc, or steady-state, voltages and currents therefore involves averaging the waveforms.
2. The linear ripple approximation greatly simplifies the analysis. In a well-designed converter, the switching ripples in the inductor currents and capacitor voltages are small compared to the respective dc components, and can be neglected.
3. The principle of inductor volt-second balance allows determination of the dc voltage components in any switching converter. In steady-state, the average voltage applied to an inductor must be zero.

Summary of Chapter 2

4. The principle of capacitor charge balance allows determination of the dc components of the inductor currents in a switching converter. In steady-state, the average current applied to a capacitor must be zero.
5. By knowledge of the slopes of the inductor current and capacitor voltage waveforms, the ac switching ripple magnitudes may be computed. Inductance and capacitance values can then be chosen to obtain desired ripple magnitudes.
6. In converters containing multiple-pole filters, continuous (nonpulsating) voltages and currents are applied to one or more of the inductors or capacitors. Computation of the ac switching ripple in these elements can be done using capacitor charge and/or inductor flux-linkage arguments, without use of the small-ripple approximation.
7. Converters capable of increasing (boost), decreasing (buck), and inverting the voltage polarity (buck-boost and Cuk) have been described. Converter circuits are explored more fully in a later chapter.

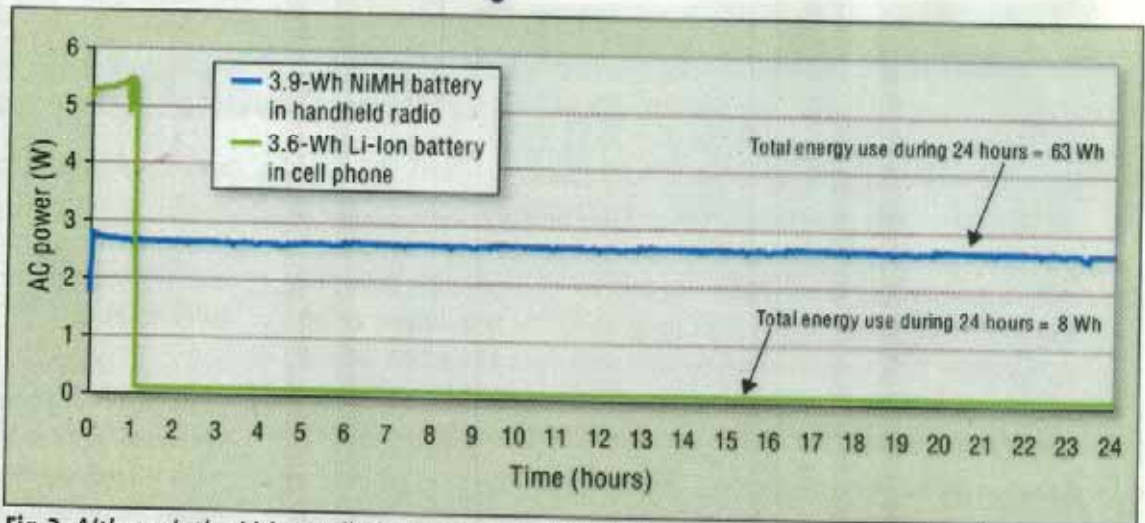


Fig. 2. Although the Li-ion cell phone charger initially draws more ac power than the NiMH-powered radio when charging, the Li-ion charger completes the charging process more rapidly, so its total energy consumption is less than the NiMH charger.