

Single
Phase
Buck

Q_1 ON

L_1 stores

Q_1 off

Q_2 ON

L_1 serves
load

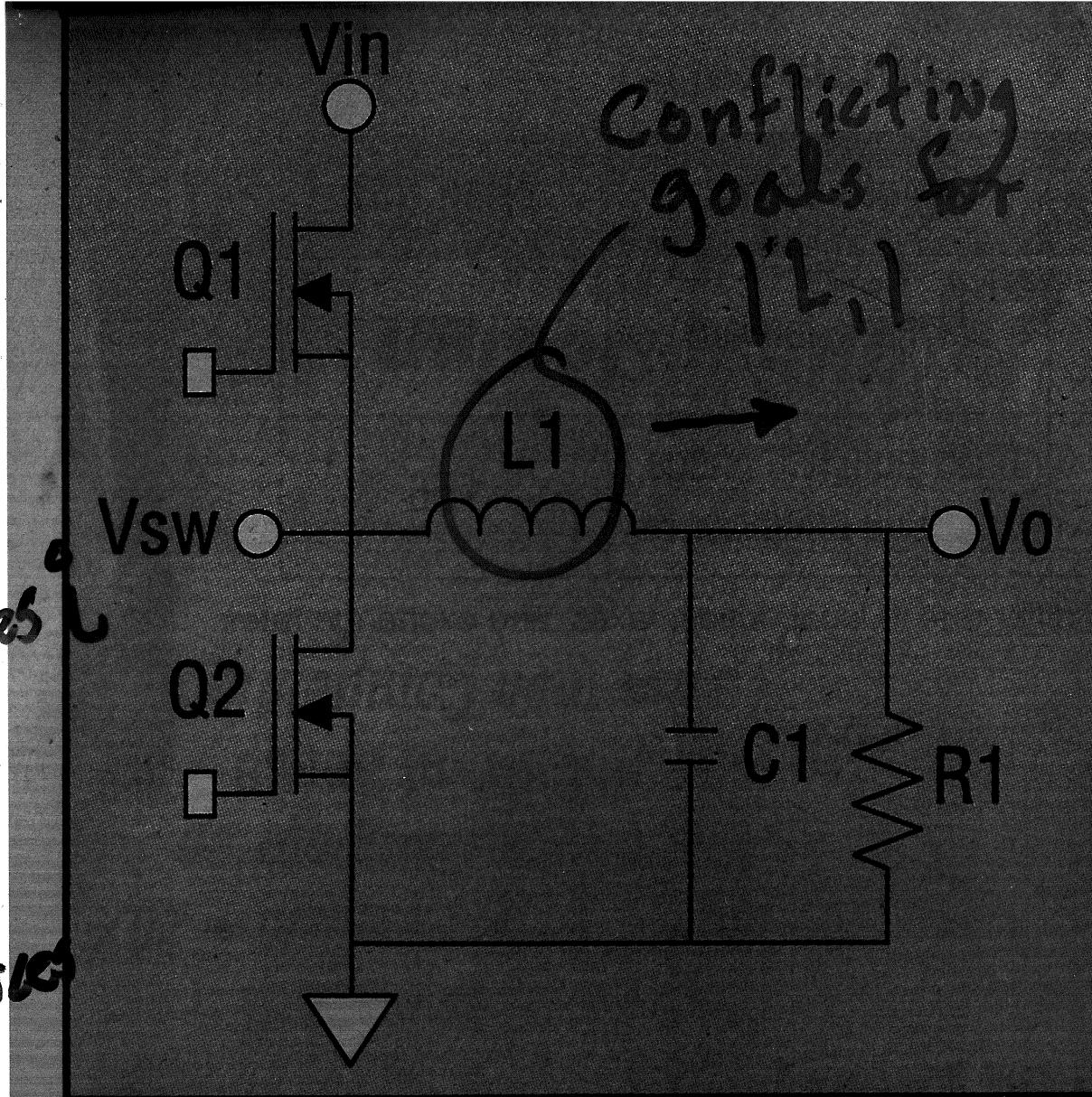


Fig. 1. Simplified schematic of a typical synchronous buck converter. The inductor current always flows through either Q_1 or Q_2 . During the on-time, Q_1 is ON, and inductor current increases. During the off-time, Q_2 is ON, and the inductor current decreases. At the on/off transition times, the inductor current has to quickly switch from one FET to the other one.

High L for low ripple
Low L for fast di/dt


1Φ Buck

I_{out}: 50A notebook }
 100A desktop }
 150A server } $I^2 R$ losses
 high for one path

Conflict / Compromise on single
 "L" is necessary

Big "L"
 for small
 Δi_L

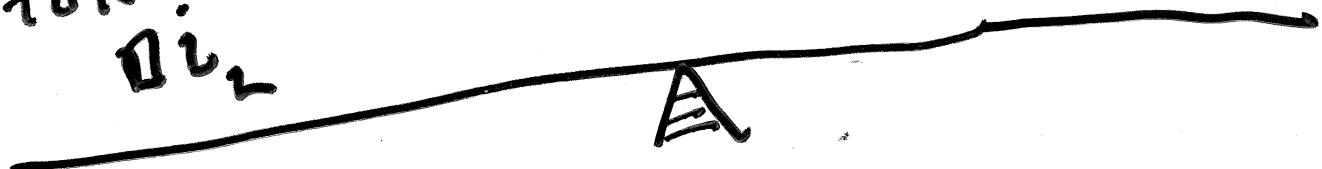small "L"
 for fast di_L
 $\frac{dt}{dt}$



Solution: "X" separate current paths each with own

$\sum_{x=1}^n i_x = i_{out}$ and Δi_x
 $\Delta \phi_x$ shift phases to reduce $|\Delta i_L|$

Phase shift $\Delta \phi_x$ to minimize $|\Delta i_{out}|$

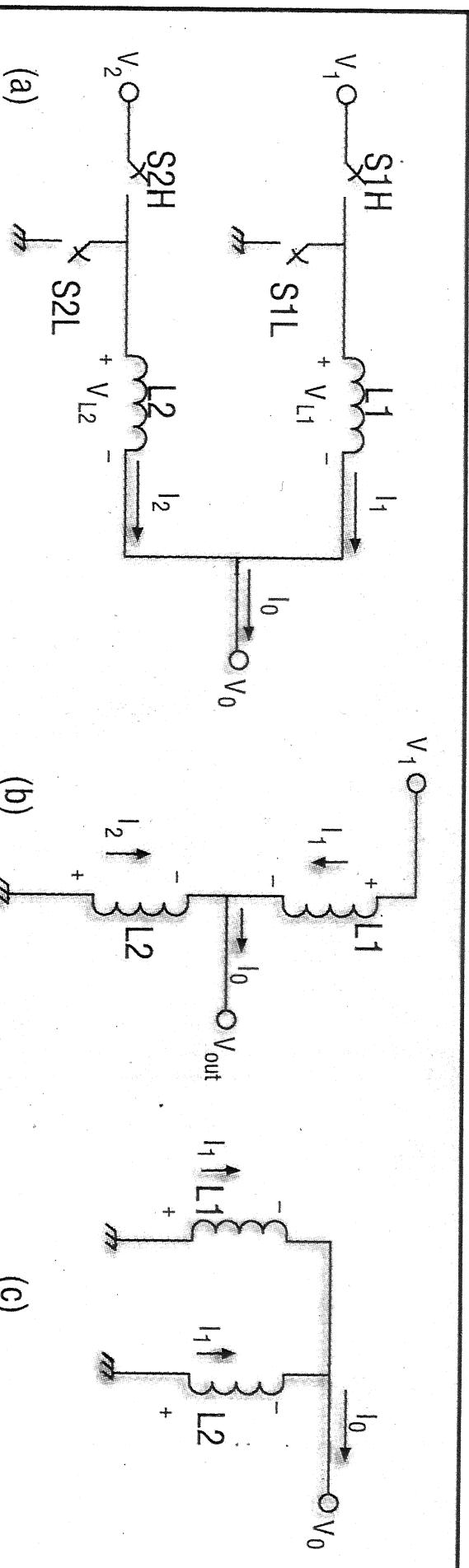



Fig. 2. A simplified schematic of a multiphase uncoupled buck regulator (a) illustrates the two basic switching actions. In state one (b), S_{1H} and S_{2L} are closed while S_{1L} and S_{2H} are open. The input then sources energy to L_1 and the output, and L_2 sources energy to the output. In state two (c), S_{1L} and S_{2H} are closed, and S_{1H} and S_{2L} are open. Thus, both inductors source energy to the output. These operations are reversed for states three and four (not shown).

**I^2R loss @ 150 A sever too high
for one path use several parallel paths**

Multiphase Output:

$$|T_m| \downarrow$$

Yet $|T_o|$
same

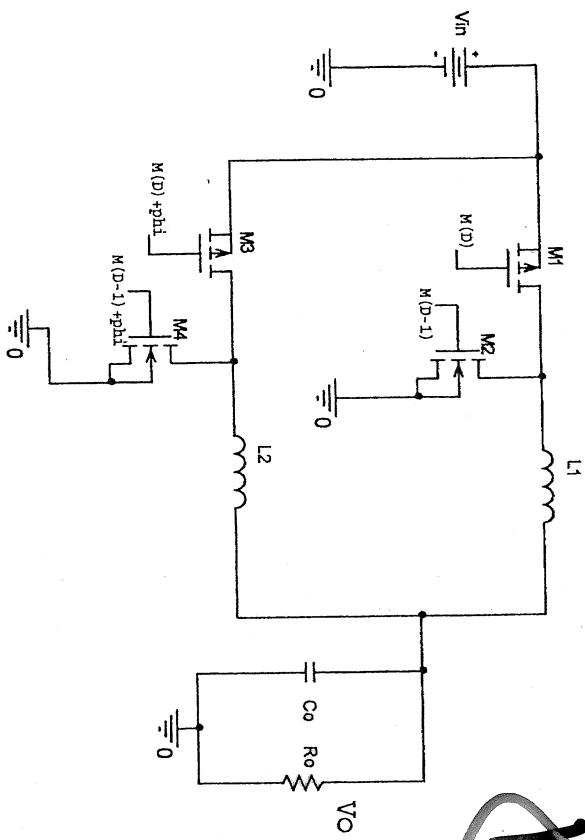

$$(I_{\text{in}}^n)$$

loss due to

$$I_{\text{in}}^n$$

& as N

$I_{\text{in}}^n R_{\text{in}}$ loss
down as N^2

- Reduces output ripple due to cancellation of inductor ripple currents
- Relaxes maximum current rating requirements of switches, inductors and caps
- Reduces stress and I^2R loss on input source by reducing amplitude of input current pulses

① State 1: 2Φ $V_{in} \xrightarrow{m} V_o \rightarrow$

$$dt = DT_{sw}$$

$$\frac{di_1}{dt} = \frac{V_{in}}{L_1} (1-D) DT_{sw}$$

$$\frac{di_2}{dt} = \frac{V_{in}}{L_2} (D) DT_{sw}$$

$$= \frac{m}{L_2} V_o \rightarrow$$

$$L_1 = L_2 = L$$

$$i_1 = i_2 \quad di_{out} = di_1 + di_2$$

$$di_{out} = \frac{V_{in}}{2} (1-2D) DT_{sw}$$

② State 2: 2Φ

$$t = DT_{sw} \rightarrow \frac{T_{sw}}{2}$$

ripple is at $2 f_{sw}$

$$di_{out} = -\frac{V_{in}}{2} (1-2D) DT_{sw}$$

Recall $di_{out}(1\Phi)$: $\frac{V_{in}}{2} (2-D) D T_{sw}$

$$\frac{\Delta i_{out}(2\Phi)}{\Delta i_{out}(1\Phi)} = \frac{1-2D}{1-D}$$

lower Δi_{out} for all D


OR

L reduced for same Δi_{out}
but faster di_o / dt

Δv_{out} (multiphase) can be zero for some D

Frequency and Phases

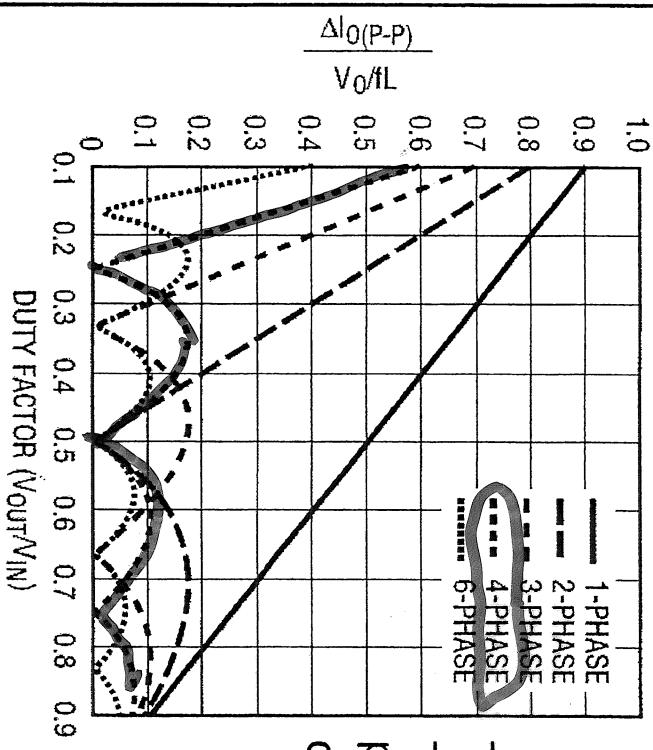For $V_{in} = 5V$, $V_{out} = 1.8V$, $D \approx .35$



- Optimal number of phases 3 or 6
- Though 4 or even 2 phases also provides good output ripple cancellation versus a single phase


$$\Delta v_{out} = 0$$

$$D =$$

0.25
0.50
0.75

Ultrafast Transient Response

2% ΔV_{OUT} with a 5A Step

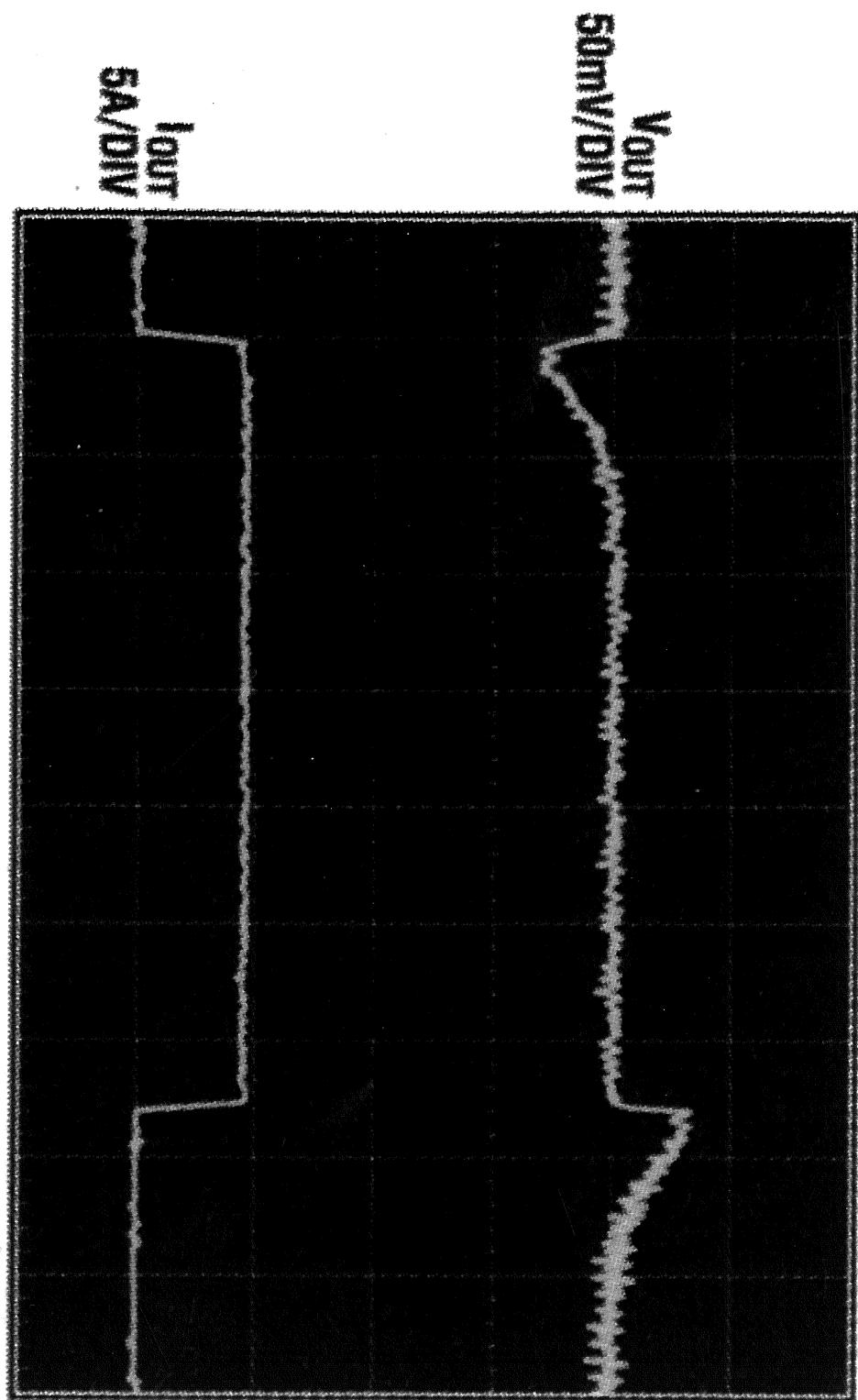

$V_{\text{IN}} = 12\text{V}$, $V_{\text{OUT}} = 1.5\text{V}$, 0A to 5A Load Step
($C_{\text{OUT}} = 3 \times 22\mu\text{F}$ CERAMICS, $470\mu\text{F}$ POS CAP)