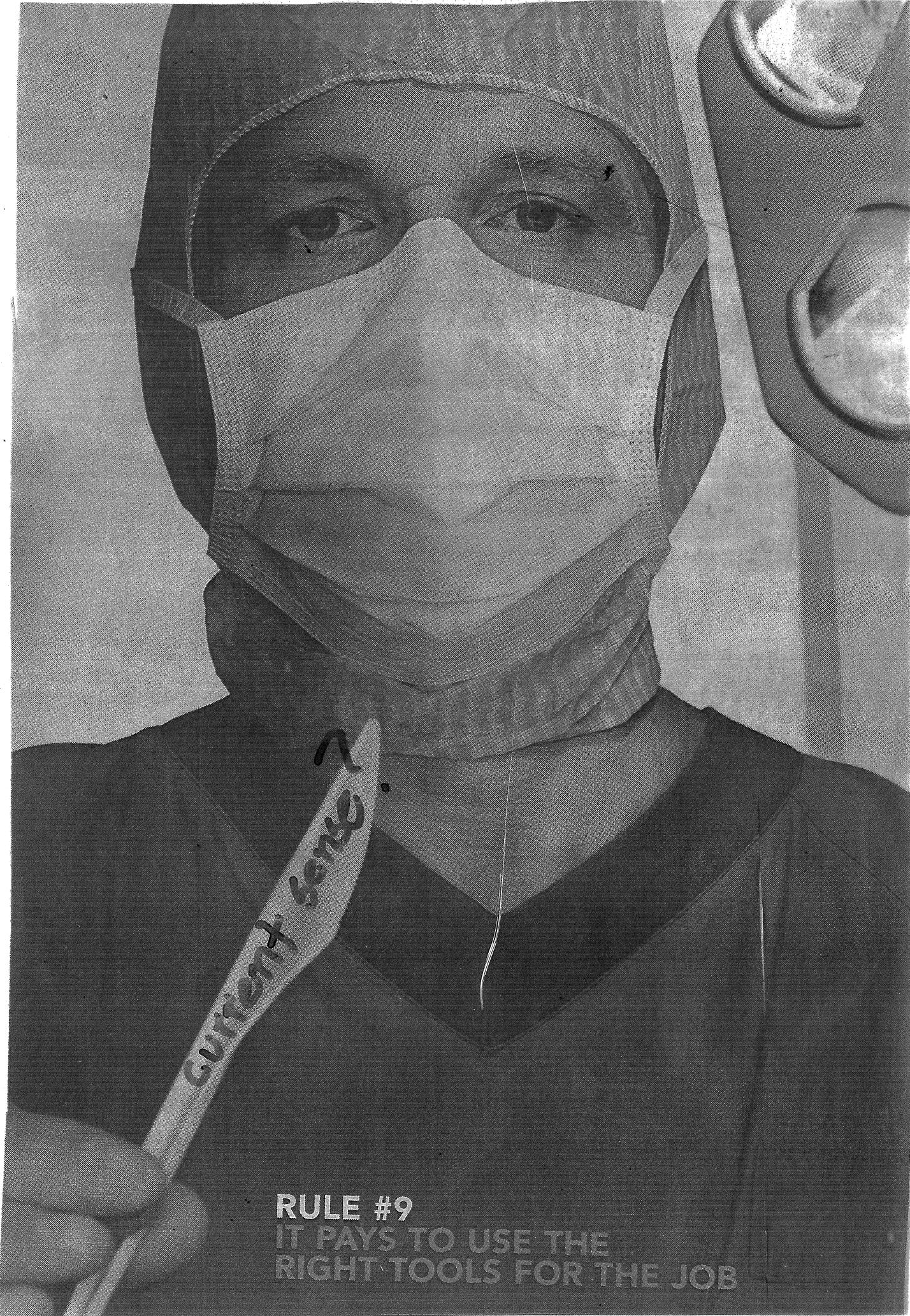


## **Applications:**

- Low-voltage, high-density distributed power systems
- Point-of-load regulation for high-performance DSPs, FPGAs, ASICs and microprocessors
- Broadband, networking and optical communications infrastructure
- Portable computing/notebook PCs

## **Features:**


- 3-V to 6-V input
- 30-mΩ, 12-A peak MOSFET switches for high efficiency at 6-A continuous output
- 0.9-V to 3.3-V adjustable output voltage range with 1.0% initial accuracy; fixed versions available
- Wide PWM frequency — fixed 350 kHz, 550 kHz or adjustable 280 kHz to 700 kHz
- Load protected by peak current limit and thermal shutdown
- Complete set of design tools: EVM, software tool and datasheets
- TPS5461x starts at \$4.99 per device in quantities of 1,000



**RULE #9**  
**IT PAYS TO USE THE**  
**RIGHT TOOLS FOR THE JOB**
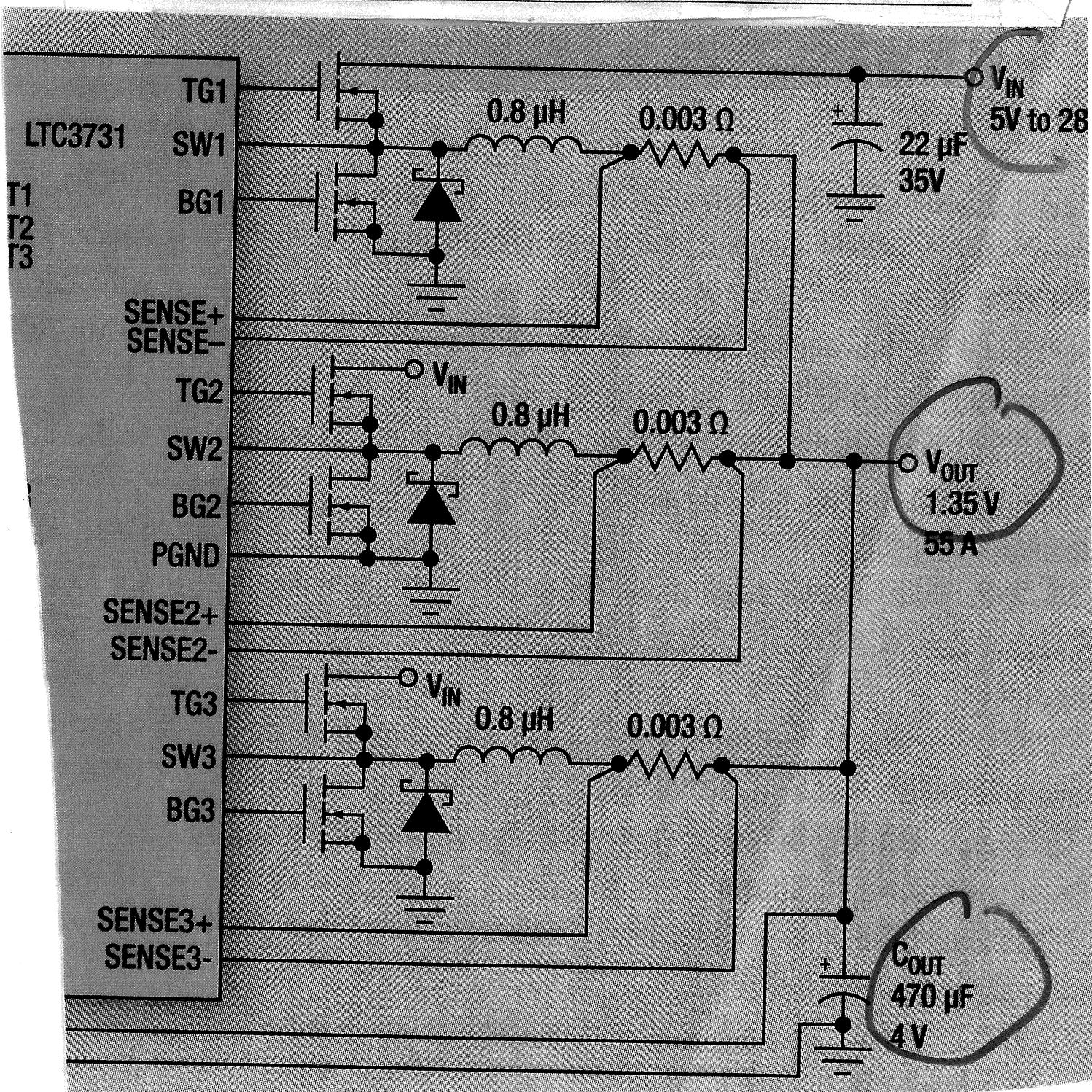
# Fig. 1. Linear Technology's LTC3731 is a PolyPhase synchronous step-down

switching regulator controller that drives all N-channel external power MOSFETs in a phase-lockable fixed frequency architecture.



One vendor's chip

① latest  $f \uparrow * 5$

## The Good Stuff

- ◆ ② Up to 2.5MHz switching frequency
- ◆ >4MHz sync capability
- ◆ Minimum pulse width <25ns
- ◆ Fast current limit: <35ns
- ◆ Built-in 180V start-up circuitry
- ◆ <1mA quiescent current
- ◆ Built-in MOSFET driver:  $3\Omega$  sink,  $7\Omega$  source
- ◆ Programmable undervoltage lockout
- ◆ Programmable soft start
- ◆ Resistor programmable current sense threshold
- ◆ Primary power limit for fault conditions
- ◆ Low current <5 $\mu$ A shutdown mode
- ◆ 50% duty cycle limit with MIC9130
- ◆ 75% duty cycle limit with MIC9131
- ◆ 16-pin SOIC and QSOP packages

③ \$15 / chip

$$1 \leq K_{on} \leq 100 \text{ m}^{-1}$$

$$V_{FET(on)} = I R_{on}$$

if too high use  $V_{CE}$  (bipolar)  $\approx 0.1V$


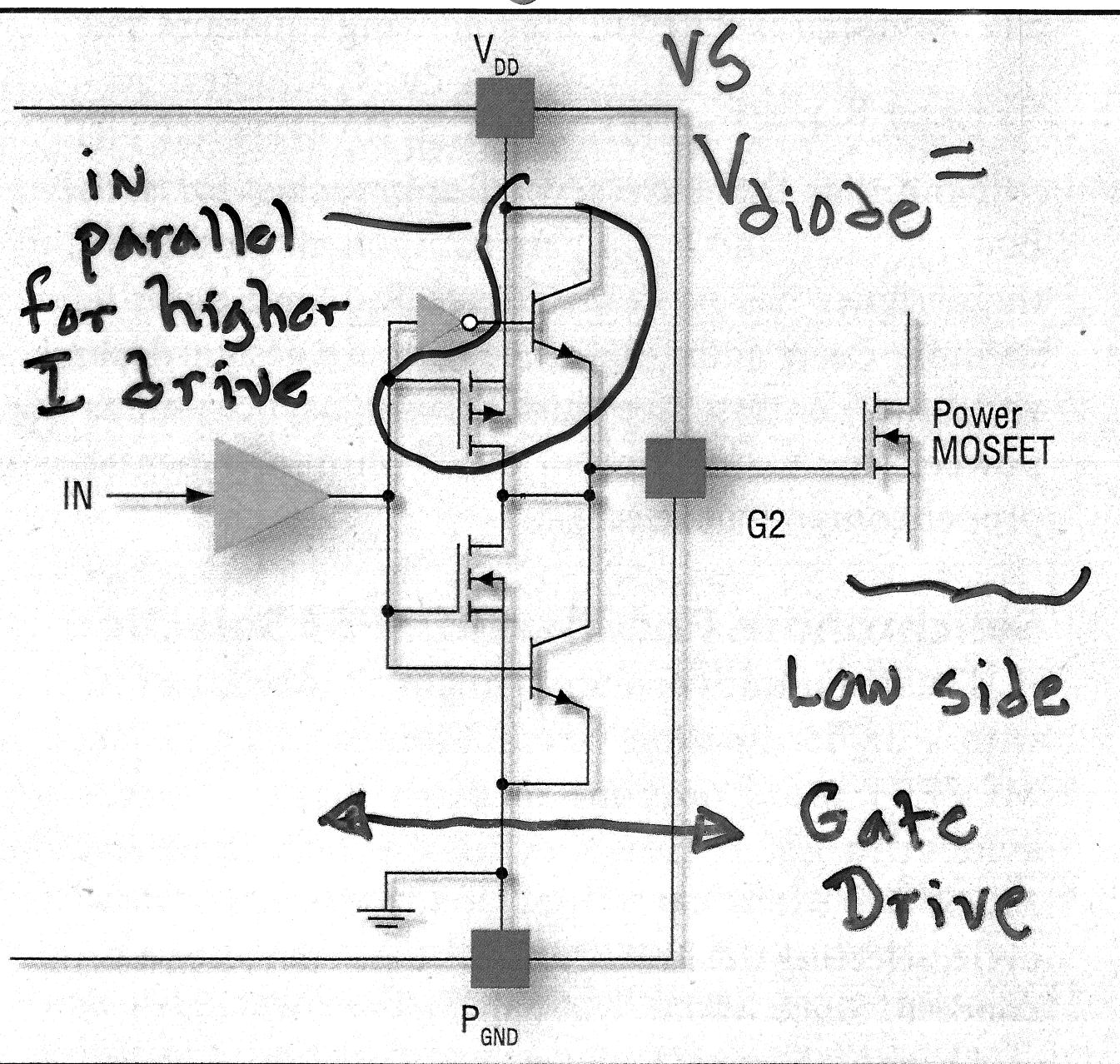


Fig. 3. The TrueDrive gate-drive architecture (low-side only) from Texas Instruments places bipolar and MOS transistors in parallel to deliver the rated drive current while lowering the pull-down impedance for better dv/dt immunity.

Replace diode with M<sub>2</sub>  
to reduce switch losses

## Synchronous Rectification

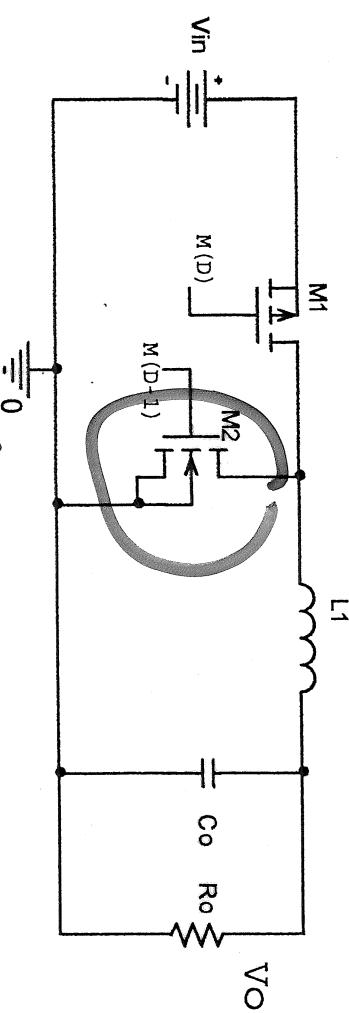

Goal:

$$P_{M2\_ON} = R_{M2\_ON} \left\{ I_{out} * (1 - D) \right\}^2 < P_{diode\_conduction} = V_{diode} * I_{out} * (1 - D)$$


-There are other switching losses in M<sub>2</sub>

-Additional Circuitry Needed in Controller (\$\$)

$V_{ON}$  diode  
say 1/2 V

$V_{ON}$  FET  
50 mV  
⇒ 10 times  
lower

# Synchronous buck

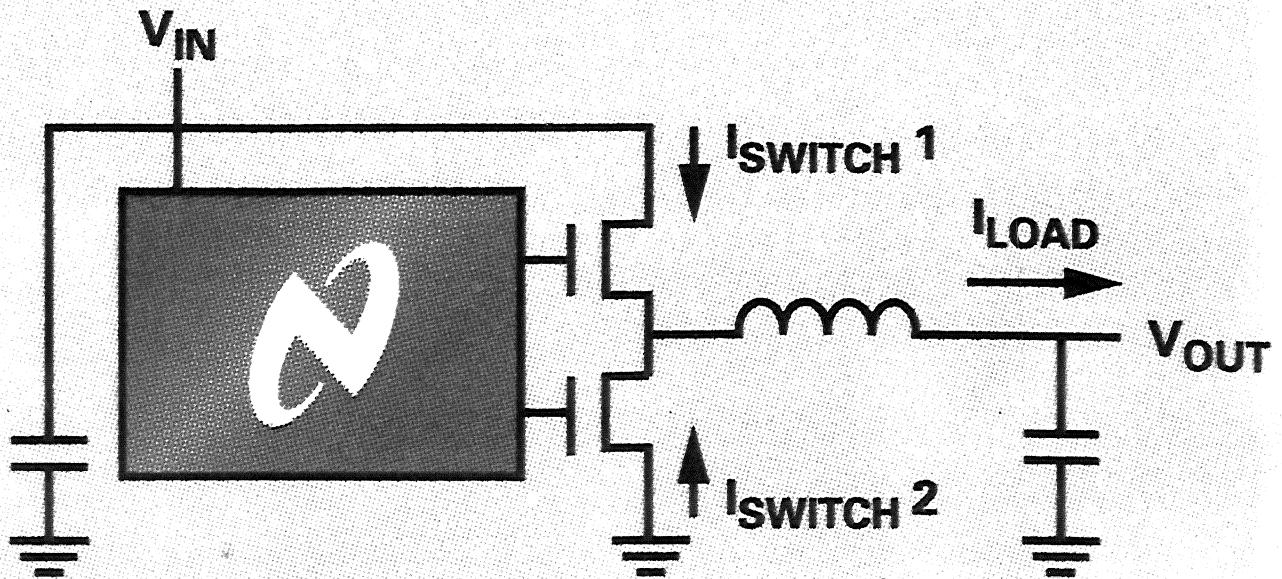

**Function:** Step-down ( $V_{OUT} < V_{IN}$ )

**When to use:** When high efficiency is required with high-output current ( $> 5A$ ) or low duty cycles ( $V_{IN} > 5 \times V_{OUT}$  and/or  $I_{OUT} < 0.5A$ )

**Characteristics:** A second switch replaces the diode in the basic buck topology, reducing losses in the conditions mentioned above

**Devices to use:** Any “synchronous rectification” buck integrated regulator or controller

## Figure 2: Step-down configurations

Cost of FET Drives ?

VS  
“Smart” diode

# Synchronous Rectification in High-Performance Power Converter Design

— By Robert Selders, Jr., Applications Engineer

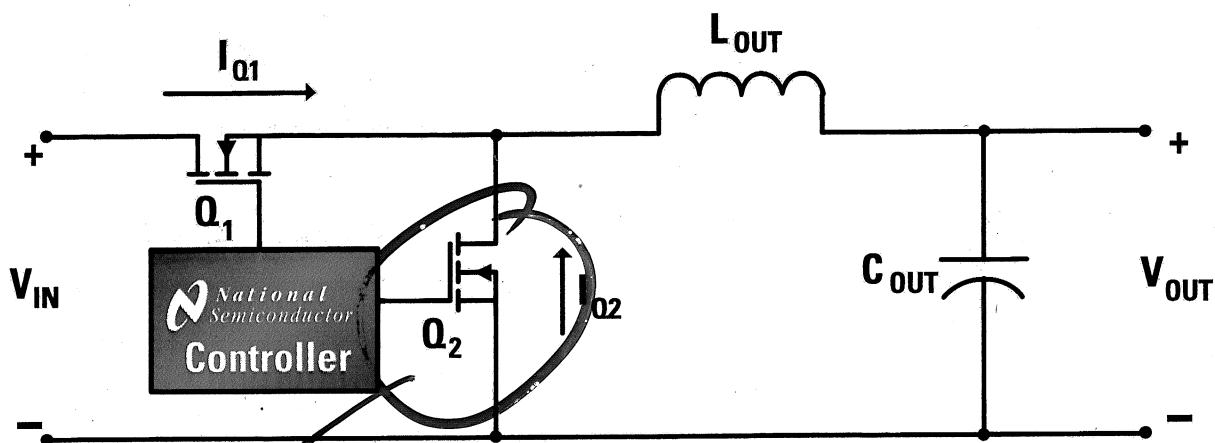
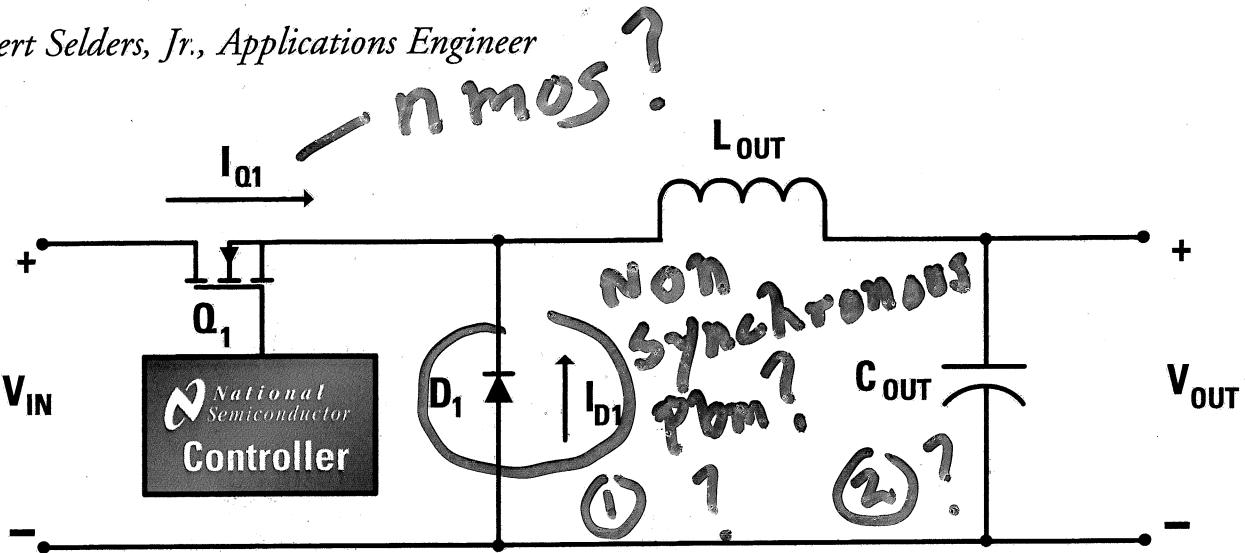


Figure 1. (a) Non-synchronous and (b) Synchronous Buck Converters

replace (IV) power diodes

- ① avoid shoot through from  $Q_{1\text{off}}$
- ② Always CCM (no need  $C_L$ )
- ③  $V_{ON} = I * R_{ON}$  (parallel FETs)
- ④ Need  $100A$  in  $\Delta \rightarrow 0.1V$