

ECE 562

Week 5 Lecture 2

Fall 2008

Week 5 Lecture 2

Summary

- Section notes
 - Slides 3-9 – Power consumption in switches
 - Slides 10-14 – Current losses
 - Slides 15-21 – Managing heat
 - Slides 22-34 – Problem 3.8 homework
 - Slides 35-39 – Problem 3.9 homework
 - Slides 40-43 – Problem 3.9 homework
 - Slides 44-51 – Buck converters

active switch(es) ? * smaller than 60 Hz Trf

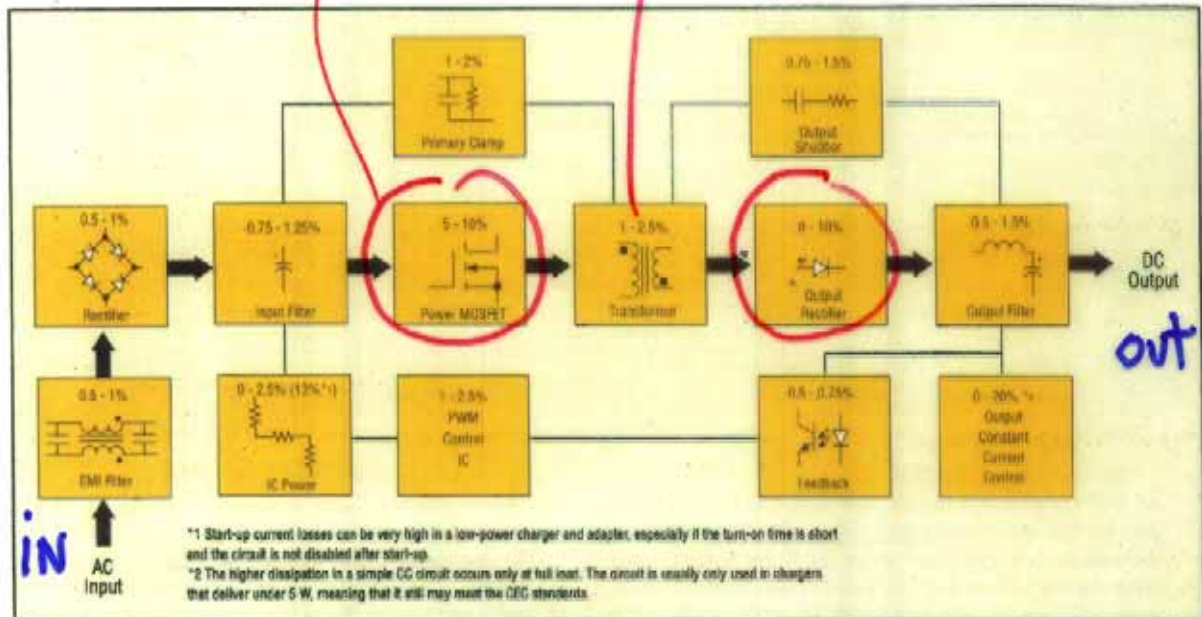


Fig.2. Block diagram of the power-consuming circuits within a SMPS.




Li-Ion

or




AA

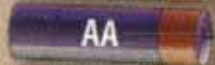

AA

or

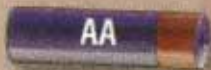

AA



LTC3400

95% Efficient ThinSOT
Synchronous Boost
 $V_{OUT} = 5V @ 300mA$



LTC3440


96% Efficient MSOP
Buck/Boost
 $V_{OUT} = 3.3V @ 600mA$



LTC3405

96% Efficient ThinSOT
Synchronous Buck
 $V_{OUT} = 1.8V @ 300mA$

SIMPLE SWITCH MODE CONVERTERS

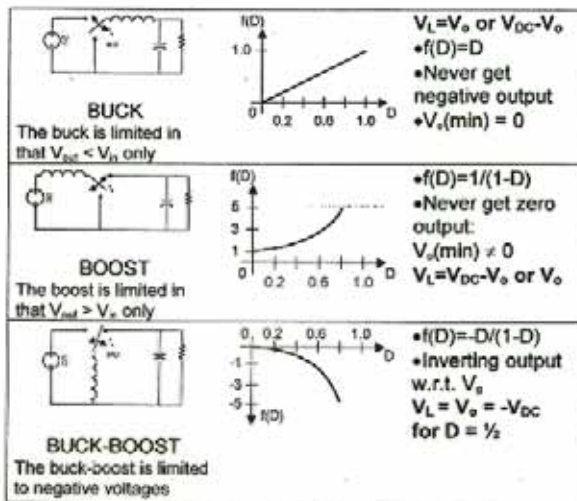

4. UNSYMMETRIC i_L AND v_C WAVEFORMS OF EQUAL INTEGRATED AREA IN THE ABOVE THREE CONVERTERS


ideal no losses
no heat

INDUSTRY
FIRST!




SAME OUTLINE
AS STANDARD SO-8

$R_{th(j-c)}$: 3°C/W

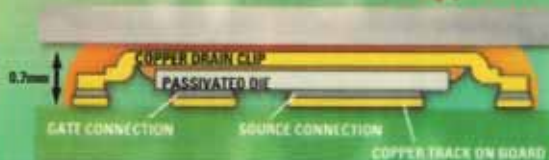

$R_{th(j-die)}$: 1°C/W

2-Phase Buck Converter, 2 MOSFETs per Phase, 1U V_{RM}
with 425 LFM Airflow, 12V_{IN}, 1.7V_{OUT}, 2MHz

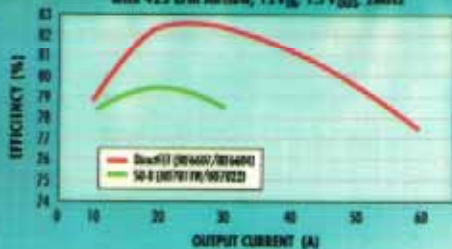


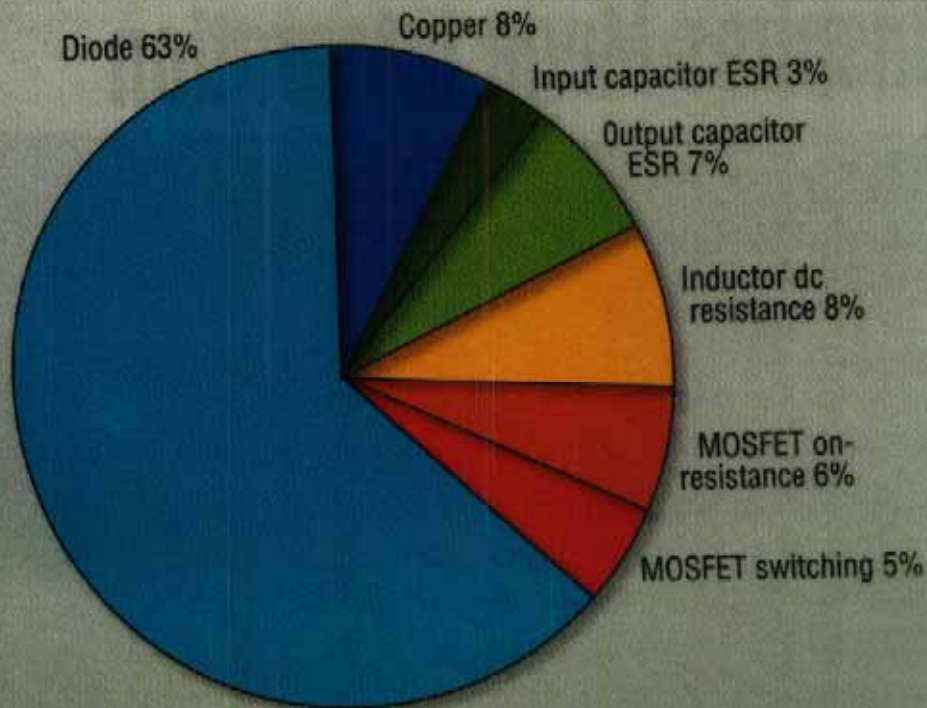


Fig. 6. Power loss caused by the freewheeling diode should be eliminated to increase the converter's efficiency.

Diode is biggest source losses


- hot spot to cool
- max fsw limit

- ignores magneto core loss

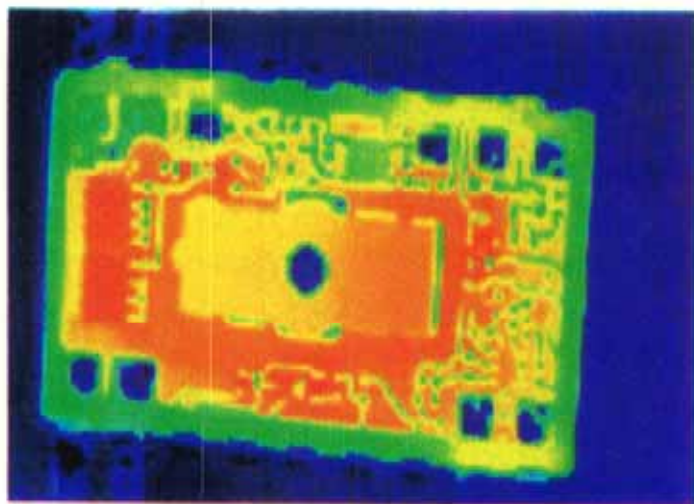

I.R.
Camera!

Fig. 4. Thermal photograph of a dc-dc converter with uniform heat distribution.

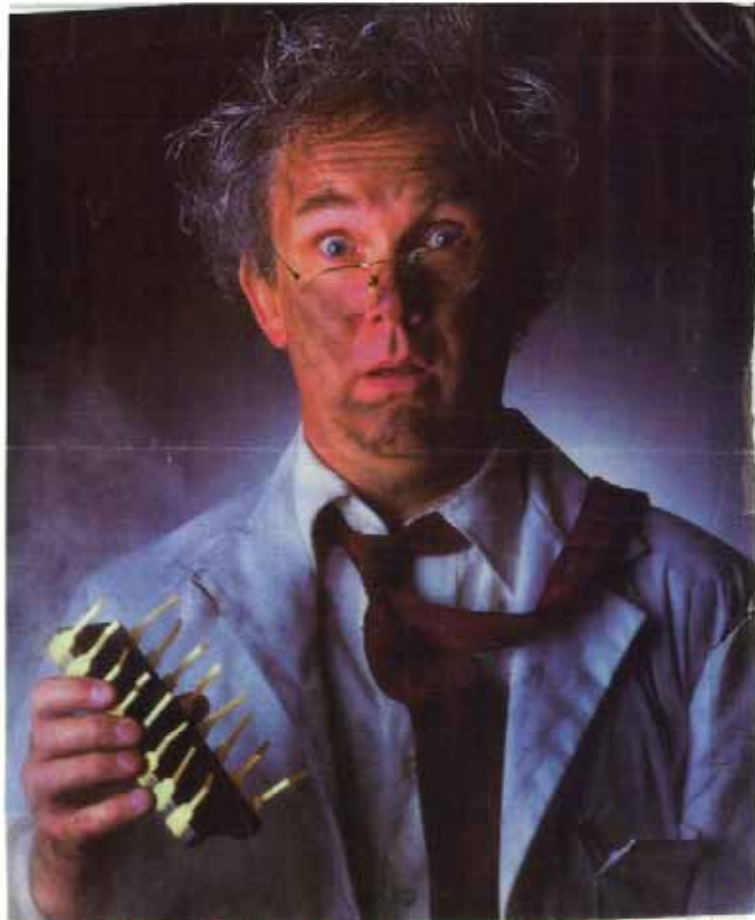

Chris/Ch4 Address SW 1065


Simple $I_{RMS}^2 R$ heating

- $I_{rms}^2 R_{on}$ (FET)


↑ not so simple
See $i(t)$ various shapes
Calculate I_{RMS} from
say $I(\text{peak})$



Diodes/Transistors

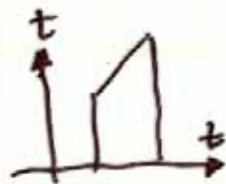

R_L in inductor

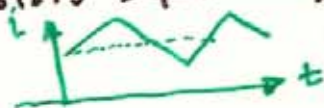


RMS Sine $\rightarrow V_{PK}/\sqrt{2}$
 \square -WAVE RMS $\rightarrow \sqrt{D} V_{PK}$

M(D) lossless itself will change only when we include lossy L and C inside the converter itself. See section III below.


C. RMS Values for Converter Waveforms
 1. Square and Ramp Waveforms

Waveforms

Typical Transistor Waveform

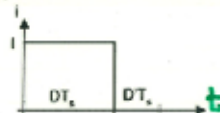

Typical Diode Waveform

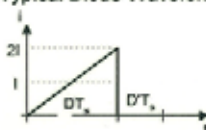

$$I_{rms} = \sqrt{\frac{1}{T_s} \int_0^{T_s} i_s^2 dt}$$

$$I_{rms} = I\sqrt{D}$$

$$I_{rms} = 115I\sqrt{D}$$

Erickson
Appendix 1

easiest case

The two above are among the simplest cases. Recall that in the big three circuits we have even more complex AC waveforms as those shown below from Lecture 4. We repeat only one BOOST circuit waveforms from lecture 4 below but the point is made that each waveform has a unique RMS value that I_{rms} is a function of the duty cycle D.


On the next pages we also review the converter topologies as well as the current flows in each switch position so that the full waveform is developed. It is left to the student to match waveforms to RMS calculations using Appendix 1 of Erickson.

Accuracy of the averaged equivalent circuit in prediction of losses *Losses only DC?*

- Model uses average currents and voltages
- To correctly predict power loss in a resistor, use rms values
- Result is the same, provided ripple is small

Table 3.1

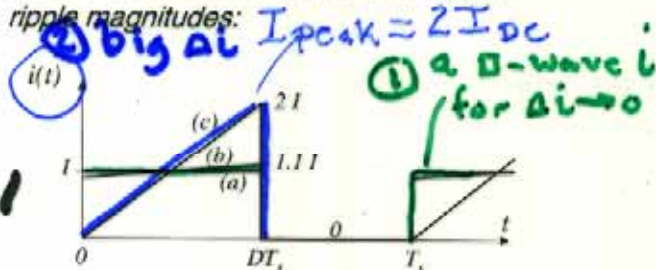MOSFET current waveforms, for various ripple magnitudes:



Inductor current ripple	MOSFET rms current	Average power loss in R_{on}
<u>(a) $\Delta i = 0$</u>	<u>$I\sqrt{D}$</u>	<u>$D^2 R_{on}$</u>
(b) $\Delta i = 0.1 I$	$(1.00167) I\sqrt{D}$	$(1.0033) D^2 R_{on}$ ← Usual
<u>(c) $\Delta i = I$</u>	<u>$(1.155) I\sqrt{D}$</u>	<u>$(1.3333) D^2 R_{on}$</u>

Losses - Two Types


DC losses in electronics

$$I_{DC}^2 R$$

$$I_{DC}(ON) V_{ON}(bipolar)$$

$$I_{DC}^2(ON) R_{DS}(FET)$$

AC losses in electronics

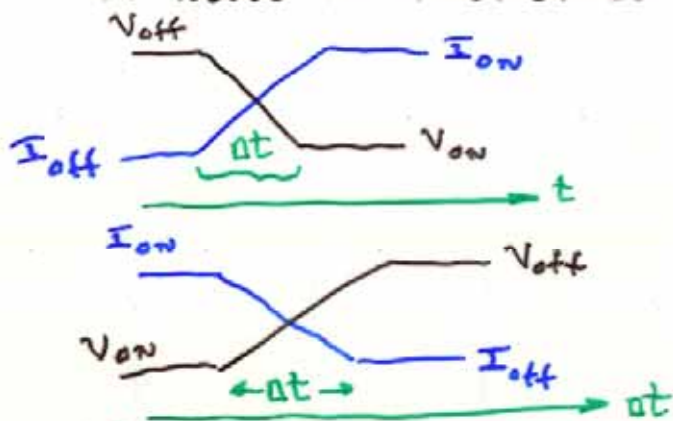

Other two device losses

AC Range
265
75

CCM for I_L

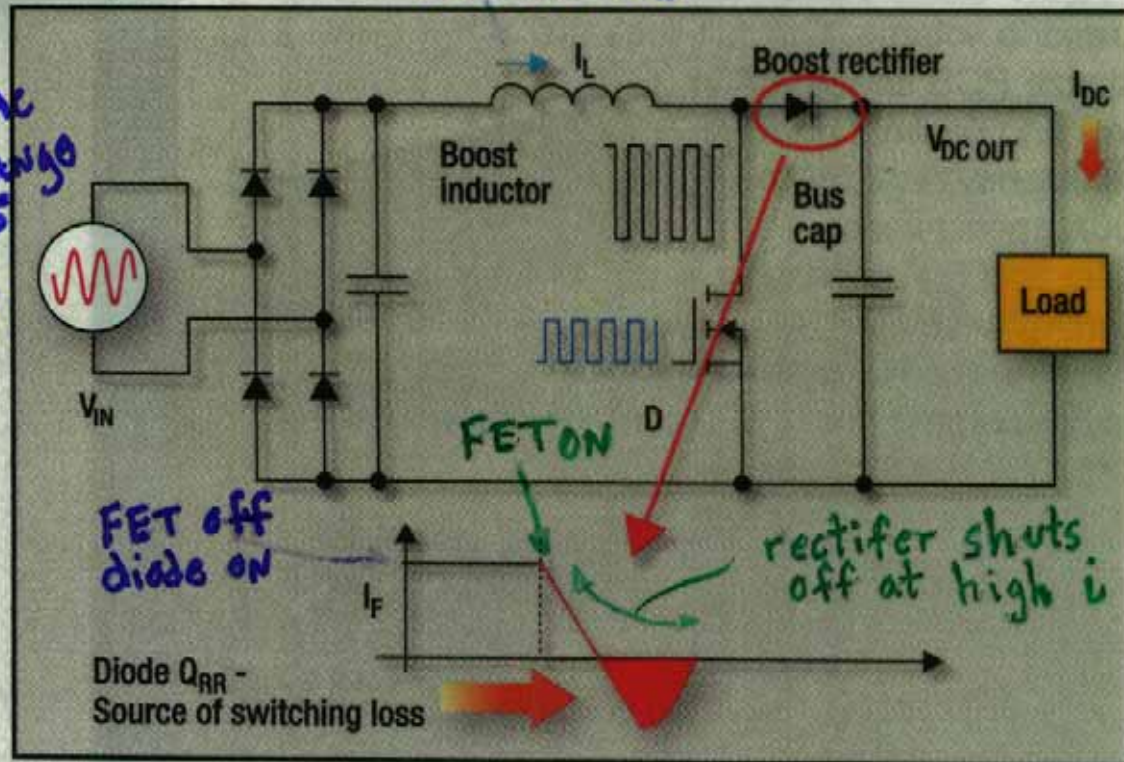


Fig. 1. In the basic single-phase boost PFC converter, the boost rectifier's Q_{rr} produces significant switching losses.

HW 3.8

You choose
Heatsinks
Board level
for power semiconductors

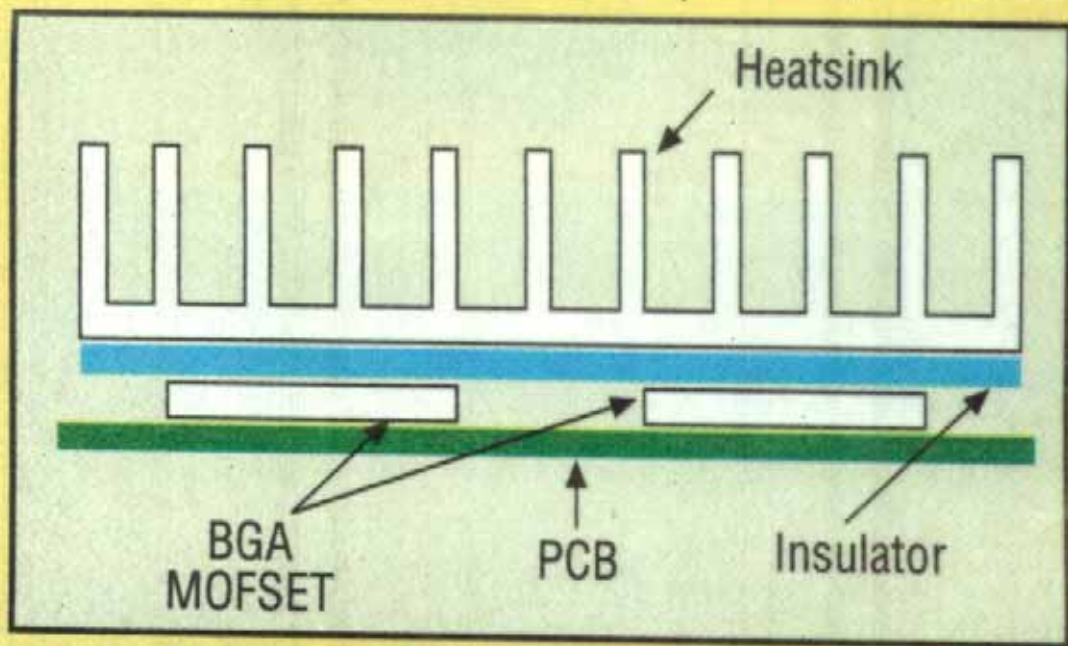


Fig. 1. BGA heatsinking arrangement.

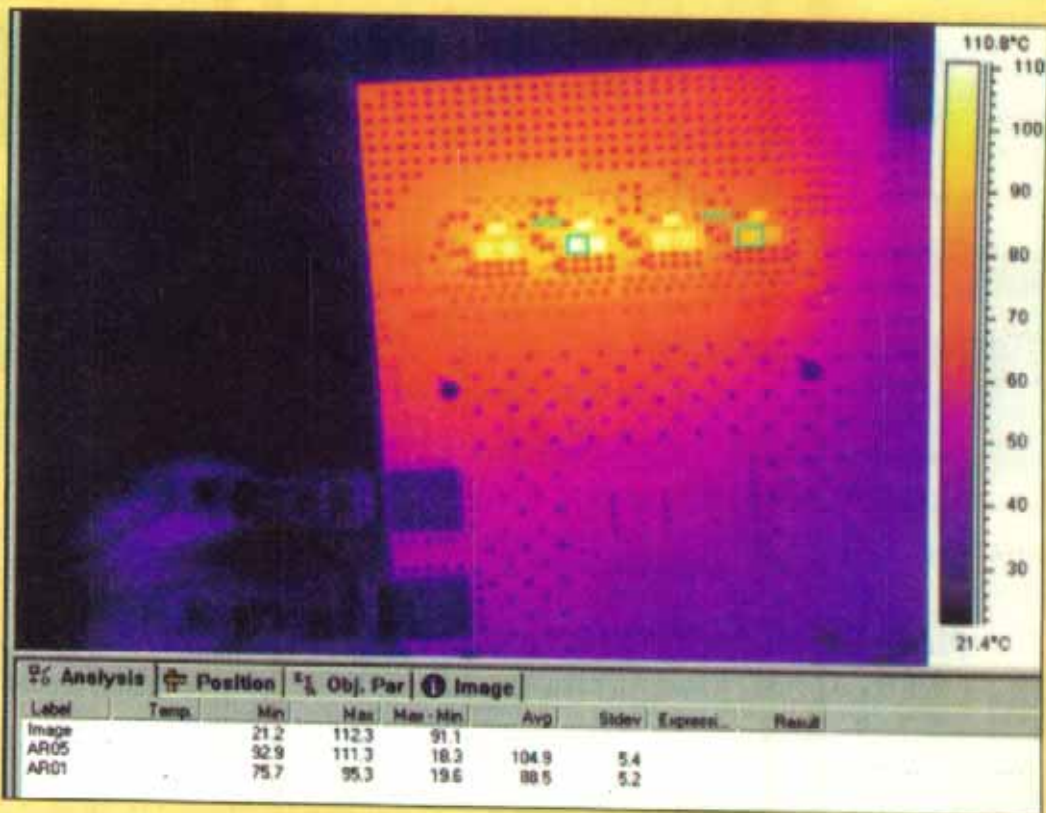


Fig. 4. IR image of the notebook board running at output current of 90 A.

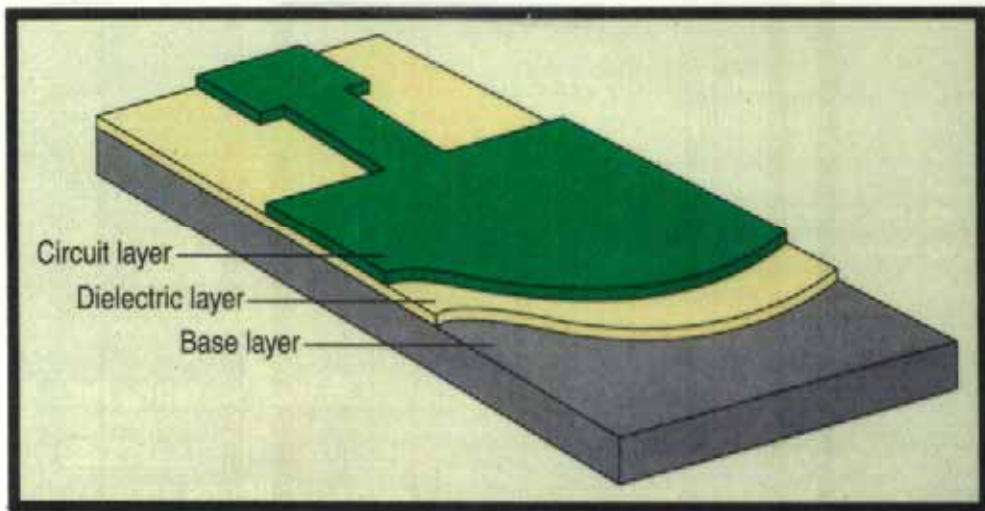


Fig. 1. Insulated metal substrate construction.

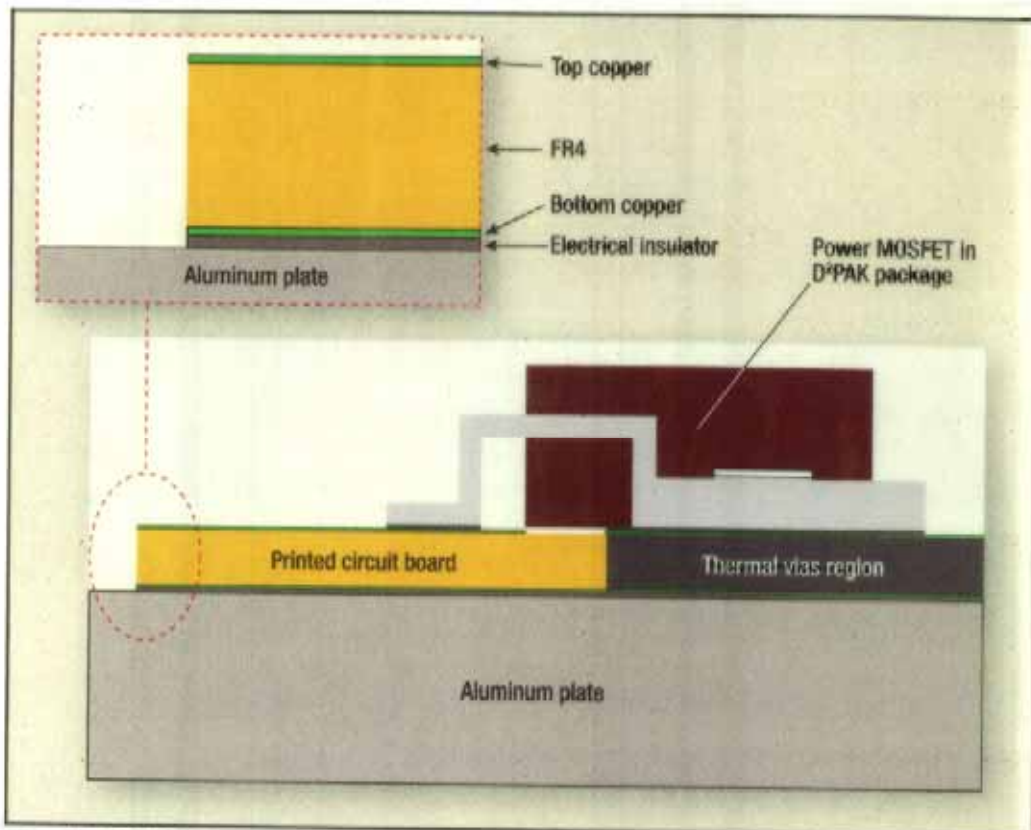


Fig. 1. A D²PAK MOSFET mounted on a pc board employing bottom-side cooling transfers heat to the aluminum plate heatsink through the thermal vias region.

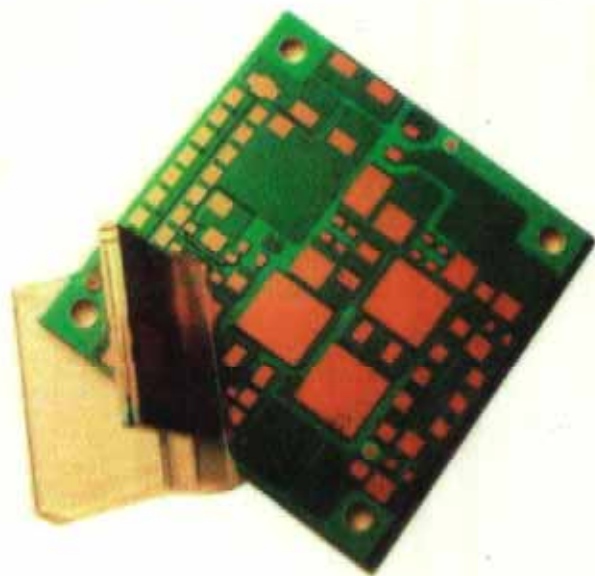


Fig. 2. The copper core board spreads heat, eliminating hot spots and reducing thermal resistance for higher reliability. The copper core adds a 10°C edge to converter performance.

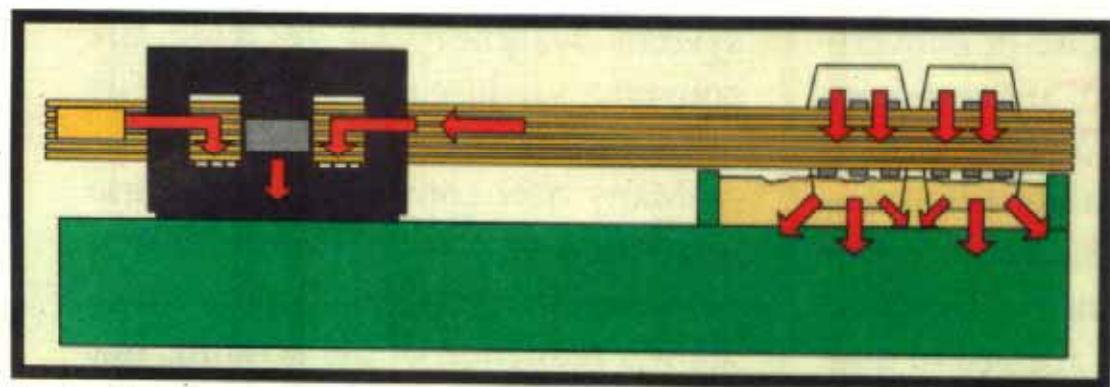


Fig. 3a. *The Cast Carrier is shown in green, with direct contact to a ferrite core, and an encapsulant bath for semiconductors.*

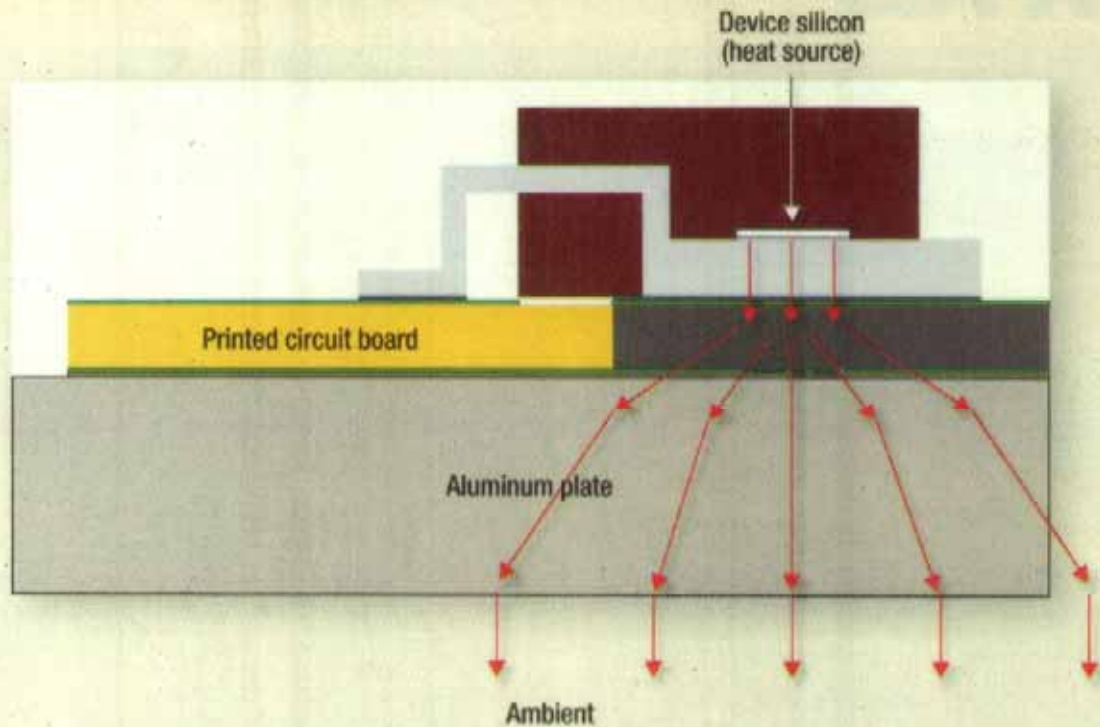



Fig. 2. The primary heat path from device silicon to ambient for a D²PAK MOSFET in a bottom-side cooling scheme diverts the majority of heat directly to ambient via the pc board and heatsink.

L3 Copy


Problem 3.8

Note paragraph about problem 3.8

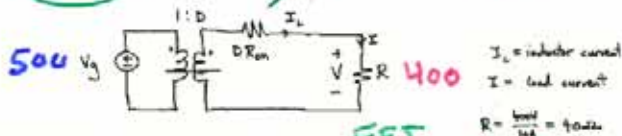(a) Buck converter model FET $R_{DS(on)}$



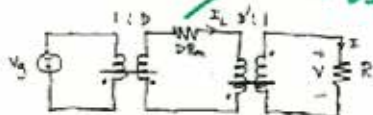Buck-boost converter model FET $R_{DS(on)}$



(b) Buck converter analysis

$$V = D V_g \frac{R}{R + R_{DS(on)}} = \frac{D V_g}{1 + D \frac{R_{DS(on)}}{R}}$$

$$\eta = \frac{1}{1 + D \frac{R_{DS(on)}}{R}}$$

Solve for D:

$$V + D V \frac{R_{DS(on)}}{R} = D V_g$$


$$\Rightarrow D \left(V_g - V \frac{R_{DS(on)}}{R} \right) = V$$

$$D = \frac{V}{V_g - V \frac{R_{DS(on)}}{R}} = \frac{400}{500 - 400 \frac{0.5}{40}} = 0.808$$


No loss
0.8

Construct equivalent circuit

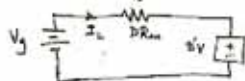
inductor - loop equation $\langle I_L \rangle = 0 = V_S - DR_L I_L - V$



capacitor - node equation

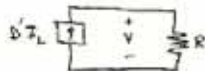

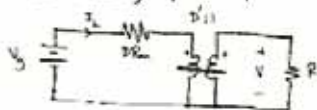Combine circuits, replace dependent sources with $D:1$ transformer



Solution:

$$V = \frac{1}{D} V_S \frac{1}{1 + \frac{D}{\omega^2} \frac{R}{R}}$$

$$I_L = \frac{V}{DR}$$

$$\eta = \frac{1}{1 + \frac{D}{\omega^2} \frac{R}{R}}$$

$$P_{in} = I_L^2 DR$$

For the values $V_S = 300$, $V = 100$, $R = 10$, $R_{in} = 0.5$

find D and η (and also I_L and P_{in})

the quadratic equation for D (arises from $\frac{V}{V_S} = \frac{1}{1 + \frac{D}{\omega^2} \frac{R}{R}}$)
 $\Rightarrow D = 0.2593$ (note $D \rightarrow 0.25$ for $R_{in} \rightarrow 0$)

You!
 "Pick the
 R - web
 10 A
 Rating
 ON
 R?

1990 EJ

$$\eta = \frac{1}{1 + (0.001) \frac{0.5}{40}} = 0.990$$

$$\text{loss} = (100)(10) \left(\frac{1}{0.990} - 1 \right) = 40.4 \text{ W}$$

Market conduction loss

Find
a
Heat
Sink

Back-boost converter analysis

500 → 400

$$V = \frac{D}{D'} V_3 \frac{R}{R + \frac{D R_m}{D'}} = \frac{D}{D'} \frac{1}{1 + \frac{D R_m}{D' R}} V_3$$

$$\eta = \frac{1}{1 + \frac{D R_m}{D' R}}$$

since $D < D'$:

$$D' V + \frac{D}{D'} \frac{R_m}{R} V = D V_3$$


$$(1 - 2D + D^2) V + D \frac{R_m}{R} V = (D - D^2) V_3$$

$$D^2 (V + V_3) + D \left(\frac{R_m}{R} V - 2V - V_3 \right) + V = 0$$

$$D = \frac{-\left(\frac{R_m}{R} V - 2V - V_3\right) \pm \sqrt{\left(\frac{R_m}{R} V - 2V - V_3\right)^2 - 4V(V + V_3)}}{2(V + V_3)}$$

Two roots:

- | | $\frac{D}{D'}$ | η |
|---|----------------|--------|
| ① | 0.9999 | 0.999 |
| ② | 0.4109 | 0.982 |

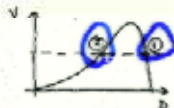

We would always choose to operate at root ② because of higher efficiency.

MOSFET conduction loss at $D = 0.4487$ is

$$P_{\text{loss}} = P_{\text{out}} \left(\frac{1}{\eta} - 1 \right) = (400)(10) \left(\frac{1}{0.982} - 1 \right)$$
$$= 73.9 \text{ W}$$

Find a heatsink

This is nearly twice as large as in the buck converter.

⇒ The buck-boost approach would require a heatsink that is nearly twice as large.

⇒ Buck is better approach.


L3 Copy

Problem 3.8

Note paragraph above problem 3.8

(a)

Buck converter model

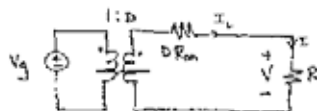


I_L = inductor current

I = load current

$$R = \frac{90\text{mV}}{10\text{A}} = 9\text{m}\Omega$$

Buck-boost converter model

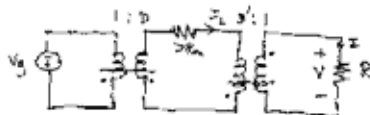

(b)

Buck converter analysis

(c)

$$V = D V_g \frac{R}{R + D R_{on}} = \frac{D V_g}{1 + D \frac{R_{on}}{R}}$$

$$D = \frac{1}{1 + \frac{R_{on}}{R}}$$

also from D:

$$V + D V \frac{R_{on}}{R} = D V_g$$

$$\Rightarrow D \left(V_g - V \frac{R_{on}}{R} \right) = V$$

$$D = \frac{V}{V_g - V \frac{R_{on}}{R}} = \frac{90\text{mV}}{570\text{mV} - 570\text{mV} \frac{0.5}{90}} = 0.808$$

— 1990 EJ

$$\eta = \frac{1}{1 + (0.101) \frac{0.5}{10}} = 0.990$$

$$\text{loss} = (100)(10) \left(\frac{1}{0.990} - 1 \right) \quad (\text{from Eq. (1.2)})$$

$$= 40.4 \text{ W} \quad \text{Nucleon conduction loss}$$

Buck-boost converter analysis

$$V = \frac{D}{D'} V_3 \frac{R}{R + \frac{D R_m}{(D')^2}} = \frac{D}{D'} \frac{1}{1 + \frac{D R_m}{R (D')^2}} V_3$$

$$\eta = \frac{1}{1 + \frac{D R_m}{R (D')^2}}$$

Set $L = 2$:

$$D'V + \frac{D}{D'} \frac{R_m}{R} V = D V_3$$

$$(1 - 2D + D^2)V + 2 \frac{R_m}{R} V = (D - D^2)V_3$$


$$D^2(V + V_3) + D \left(\frac{R_m}{R} V - 2V - V_3 \right) + V = 0$$

$$D = \frac{- \left(\frac{R_m}{R} V - 2V - V_3 \right) \pm \sqrt{\left(\frac{R_m}{R} V - 2V - V_3 \right)^2 + 4D(V + V_3)}}{2(V + V_3)}$$

Two notes:

	$\frac{D}{1.1111}$	$\frac{V}{0.008}$
①	0.8889	0.992

	$\frac{D}{1.1111}$	$\frac{V}{0.008}$
②	0.8889	0.992

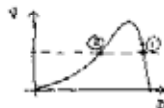

We could also choose to operate at point ② because of higher efficiency.

MOSFET conduction loss at $D = 0.9489$ is

$$P_{\text{loss}} = P_{\text{av}} \left(\frac{1}{\eta} - 1 \right) = (400)(10) \left(\frac{1}{0.972} - 1 \right) \\ = 73.9 \text{ W}$$

This is nearly twice as large as in the buck converter.

⇒ The buck-boost approach would require a MOSFET that is nearly twice as large.

⇒ Buck is better approach.

500 → 400 How to


Choices - - -

Problem 3.8

Note paragraph above problem 3.8


(a)

Buck converter model

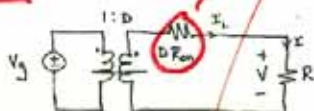

Pbm 2.1 handout

Boost converter model

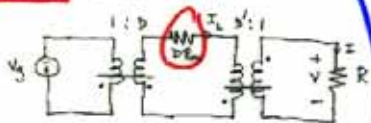

(b)
(c)

Buck converter analysis

$$V = D V_g \frac{R}{R + D r_L} = \frac{D V_g}{1 + D \frac{r_L}{R}}$$

$$\eta = \frac{1}{1 + D \frac{r_L}{R}}$$

Solve for D:

$$V + D V \frac{r_L}{R} = D V_g$$

$$\Rightarrow D (V_g - V \frac{r_L}{R}) = V$$

$$D = \frac{V}{V_g - V \frac{r_L}{R}} = \frac{400}{500 - 400 \frac{0.5}{40}} = 0.808$$

FET $r_{on} \rightarrow 0.1 \Omega$
EVEN 10 mA

I_L = inductor current

I = load current

$$R = \frac{400}{10} = 40 \Omega$$

Both can provide $V_{out} = 400$

Which is better? and why? as an engineer

D to achieve 500 → 400

$$\eta = \frac{1}{1 + (0.507) \frac{0.5}{0.01}} = 0.970$$

$$\text{loss} = (100)(10) \left(\frac{1}{0.970} - 1 \right) \quad \text{from Eq. (1.2)}$$

$$= 40.4 \text{ W} \quad \text{As a set conduction loss}$$

**Choose QP Heat sink required?
Fan?**

Block-most converter analysis

$$V = \frac{D}{D'} V_3 \frac{R}{R + \frac{D R_m}{D'^2}} = \frac{D}{D'} \frac{1}{1 + \frac{D R_m}{D'^2 R}} V_3$$

$$\eta = \frac{1}{1 + \frac{D R_m}{D'^2 R}}$$

solve Eq. 2:

$$D'V + \frac{D}{D'} \frac{R_m}{R} V = D V_3$$


$$(1 - 2D + D^2)V + D \frac{R_m}{R} V = (D - D^2)V_3$$

$$D^2(V + V_3) + D \left(\frac{R_m}{R} V - 2V - V_3 \right) + V = 0$$

$$D = \frac{- \left(\frac{R_m}{R} V - 2V - V_3 \right) \pm \sqrt{\left(\frac{R_m}{R} V - 2V - V_3 \right)^2 - 4V(V + V_3)}}{2(V + V_3)}$$

Two roots:

$\frac{D}{D'}$	η
① 0.9997	0.998
② 0.9909	0.982

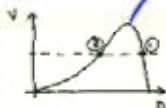

$V_{out} (DC)$

Same V_{out}

We would always choose to operate at ref ② because of higher efficiency

But for f.b. stability?

MOSFET conduction loss at $D = 0.9987$ is

$$P_{\text{loss}} = P_{\text{out}} \left(\frac{1}{D} - 1 \right) = (400)(10) \left(\frac{1}{0.9987} - 1 \right)$$

$$= 73.9 \text{ W}$$

Choose G, D

Heat sink?

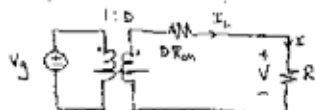
- This is nearly twice as large as in the buck converter.
- ⇒ The buck-boost approach would require a heatsink that is nearly twice as large.
- ⇒ Buck is better approach.

Problem 3.8

Note paragraph about problem 3.8


(a)

Buck converter model

 $I_L = \text{inductor current}$ $I = \text{load current}$

$$R = \frac{50\Omega}{10} = 5\Omega$$

Buck-boost converter model

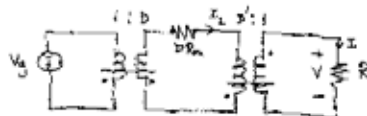

(b)

Buck converter analysis

(c)

$$V = D V_g \frac{R}{R + D R_L} = \frac{D V_g}{1 + D \frac{R_L}{R}}$$

$$D = \frac{V}{V_g - V \frac{R_L}{R}}$$

Solve for D:

$$V + D V \frac{R_L}{R} = D V_g$$

$$\Rightarrow D \left(V_g - V \frac{R_L}{R} \right) = V$$

$$D = \frac{V}{V_g - V \frac{R_L}{R}} = \frac{40}{50 - 40 \frac{5}{10}} = 0.889$$

$$\eta = \frac{1}{1 + (0.009) \frac{0.5}{40}} = 0.990$$

$$\text{loss} = (400)(10) \left(\frac{1}{0.990} - 1 \right) \quad \text{from Eq. (1,2)}$$

$$= 40,400 \quad \text{Market conduction loss}$$

Back-most converter analysis

$$V = \frac{D}{D'} V_3 \approx \frac{R}{R + \frac{D^2 R_m}{D'^2}} = \frac{R}{D'} \frac{1}{1 + \frac{D^2 R_m}{D'^2 R}} V_3$$

$$\eta = \frac{1}{1 + \frac{D^2 R_m}{D'^2 R}}$$

Sub. Eq. (1)

$$D'V + \frac{D}{D'} \frac{R_m}{R} V = D'V_3$$


$$\left(1 - 2D + D^2\right)V + 2\frac{D}{D'}V = (D - D^2)V_3$$

$$D^2(V + V_3) + D\left(\frac{R_m}{R}V - 2V - V_3\right) + V = 0$$

$$D = \frac{-\left(\frac{R_m}{R}V - 2V - V_3\right) \pm \sqrt{\left(\frac{R_m}{R}V - 2V - V_3\right)^2 - 4V(V + V_3)}}{2(V + V_3)}$$

Two roots:

- | | | |
|---|-------|-------|
| | D | Z |
| ① | 0.999 | 0.001 |
| ② | 0.999 | 0.002 |

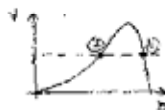

We could always choose to operate at root ② because of higher efficiency.

MOSFET conduction loss at $D = 0.9999$ is

$$P_{\text{loss}} = P_{\text{out}} \left(\frac{1}{D} - 1 \right) = (400)(10) \left(\frac{1}{0.9999} - 1 \right) \\ = 73.9 \text{ W}$$

This is nearly twice as large as in the buck converter.

⇒ The buck-boost approach will require a heatsink that is nearly twice as large.

⇒ Buck is better approach.


Tutorial
Solution to Problem 3.7

Note paragraph
above Problem 3.1

Choices
...


Interface a 300V battery to a 400V, 10A load.
Investigate boost and buck-boost converters: which has better efficiency?
MOSFET has 0.5Ω on-resistance. All other losses can be ignored.

Boost converter

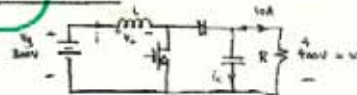

$$R = \frac{400\text{V}}{10\text{A}} = 40\Omega$$


transistor on diode off

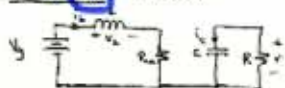

$$v_L(t) = V_3 - i_L(t)R_{on} \approx V_3 - I_L R_{on}$$

$$i_L(t) = -V(t)/R \approx -\frac{V}{R}$$

transistor off diode on

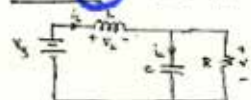

$$v_L(t) = V_3 - V(t) = V_3 - V$$

$$i_L(t) = i_L(t) - \frac{V(t)}{R} \approx I_L - \frac{V}{R}$$

Off-state balance

$$\Delta v_L(t) = 0 = D(V_3 - I_L R_{on}) + D'(V_3 - V) = V_3 - D R_{on} I_L - D'V$$

Charge balance

$$\Delta i_L(t) = 0 = D\left(-\frac{V}{R}\right) + D'\left(I_L - \frac{V}{R}\right) = D'I_L - \frac{V}{R}$$


Then $\eta = 0.9993$

$I_L = 13.7A$


$P_{loss} = 22.7W$

99.93% Pick a Heat sink

Buck-boost converter

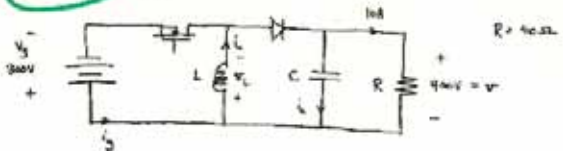

transistor on, output is kind of off

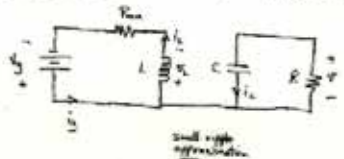

Using the converter input current i_{MOS} is positive, so not write equations for i_{MOS} during this subinterval. Also, average is 0, so do not proceed.

$$v_L(t) = V_g - i_L R_m = V_g - I_L R_m$$

$$i_L(t) = -V/R \approx -V/R$$

$$i_M(t) = i_L(t) \approx I_L$$

transistor off $DT_2 < t < T_2$ diode on



$$V_d(t) = -V(t) \approx -V$$

$$i_d(t) = i_c(t) = V(t)/R \approx I_L - V/R$$

$$i_b(t) = 0$$

volt-second balance

$$\langle V_d(t) \rangle = 0 = D(I_2 - I_L R) + D'(-V)$$

charge balance


$$\langle i_d(t) \rangle = 0 = D(-I_L/R) + D'(I_L - V/R)$$

average input current

$$\langle I_2 \rangle = I_2 = D(I_L) + D'(0)$$

Construct equivalent circuit

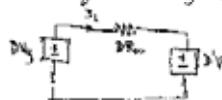inductor loop equation: $D I_2 - I_L D R_{eq} - D' V = \langle V_{L,2} \rangle = 0$




Capacitor node equation: $D'I_L - \frac{V}{R} = \langle i_C \rangle = 0$




Input current (node) equation: $I_g = DI_L$



Draw circuit models together:

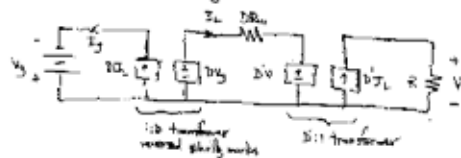

Model including ideal dc transformers:

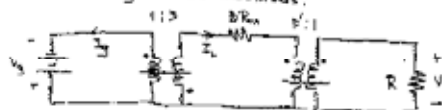

Solution of model:

$$V = \frac{D}{D'} V_g \frac{R}{R + \frac{D}{(D')^2} R_{on}} \Rightarrow \frac{V}{V_g} = \frac{D}{D'} \frac{1}{1 + \frac{D}{(D')^2} \frac{R_{on}}{R}}$$

$$\eta = \frac{1}{1 + \frac{D}{(D')^2} \frac{R_{on}}{R}}$$

$$I_L = \frac{V}{D'R}$$

$$P_{loss} = I_L^2 D'R_{on}$$

Note that, with the exception of the extra factor of D in the $\frac{V}{V_g}$ equation, all of the above equations are identical to the respective best converter equations on page 2.

Because of the extra factor of D, the best converter must operate at a larger duty cycle. This leads to increased inductor current, increased transistor conduction time, and increased power loss.

Solution

$$D = 0.5813$$

$$\eta = 0.7602 \quad 76.02\%$$

$$I_L = 23.89 \text{ A}$$

$$P_{loss} = 165.8 \text{ W}$$


— more than 7 times larger than best
heatsink must be 7 times larger
best is much better than best-best
in this application

Pick a
heatsink!


End of problem

Prob 3.4

Buck Converter

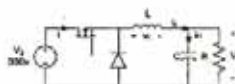
Known: $V_g = 325 + 20\%$ $V = 240$ VDC $10A \leq I \leq 1A$ MOSFET loss: $R_{on} = 0.8\Omega$ Diode loss: $V_{Diode} = 0.7V$ $R_{Diode} = 0.2\Omega$

Position 1: Mosfet on and Diode off

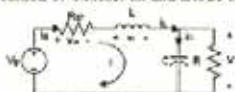

$$v_1(t) = V_g - I R_{on} - V; \quad i_1(t) = I - V/R; \quad i_2(t) = I$$

Position 2: Mosfet off and Diode on

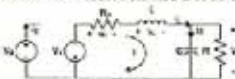

$$v_1(t) = -V_D - I R_D - V; \quad i_1(t) = I - V/R; \quad i_2(t) = 0$$

- Pick:
- ① Heat Sinks
 - ② FET
 - ③ Diode

(a) For the equivalent circuit all we need is to set the average inductor voltage equal to zero and model the equation.


$$\langle v_L \rangle = D(V_g - I R_{on} - V) + D'(-V_D - I R_D - V) = 0$$

$$\text{Thus } \Rightarrow D V_g - D I R_{on} - D' V_D - D' I R_D - V = 0$$

Now we need to get the Primary for the DC transformer model.


$$\text{The DC component of } \langle i_L \rangle = \frac{1}{T_s} \int_0^{T_s} i_L(t) dt = I.$$

Now we can model the circuit.

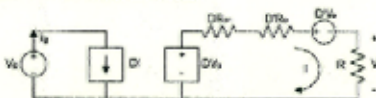

Solution to Problem 3.10

Pick number with
required output voltage

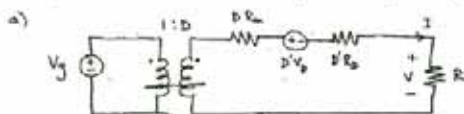

$$V = (D'V_g - D'V_o) \frac{R}{R + DR_m + D'R_o}$$

$$\frac{V}{V_g} = D \frac{(1 - \frac{D'V_o}{D'V_g})}{(1 + D \frac{R_m}{R} + D' \frac{R_o}{R})}$$

$$\gamma = \frac{(1 - \frac{D'V_o}{D'V_g})}{(1 + D \frac{R_m}{R} + D' \frac{R_o}{R})}$$

b) solve for D:

$$V \left(1 + D \frac{R_m}{R} + D' \frac{R_o}{R} \right) = D'V_g - (1-D)V_o$$


$$D \left[V \frac{R_m}{R} - V \frac{R_o}{R} - V_o - V_o \right] = -V_o - V - V \frac{R_m}{R}$$

$$D = \frac{V_o + V \left(1 + \frac{R_m}{R} \right)}{V_g + V_o + V \left(\frac{R_m - R_o}{R} \right)}$$

Results tabulated on next page

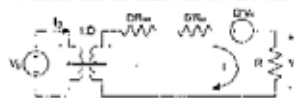c) We expect the worst-case γ to occur at min V_g and max I .
Results given on next page.

We notice that the turns ratio is 1:D. The final transformer model is:



Note: The transformer model is completed when you have the input voltage V_g alone as the input and the output voltage V alone as the output. If you have $V_g D$ or V_g times some other function then you must create a DC transformer to get V_g alone as the input. The same holds for the output voltage V .

$$\begin{aligned} \text{(a)} \quad DV_g - DI R_{eq} - I^2 V_D - D^2 I R_D - V &= 0 \Rightarrow \text{Solve for } D \\ DV_g - DI R_{eq} - V_D + DV_D - IR_D - DI R_D - V &= 0 \\ D(V_g - I R_{eq} + V_D + IR_D) = V + V_D + IR_D \\ D = (V + V_D + IR_D) / (V_g - I R_{eq} + IR_D + V_D) \end{aligned}$$

Thus: we find D_{max} when $V_g = 260$ volts and $I = 10$ A. $D_{max} = 0.955$

we find D_{min} when $V_g = 396$ volts and $I = 1$ A. $D_{min} = 0.62$

$$0.62 \leq D \leq 0.955$$

(c) Power(out) = $V I \Rightarrow 2400$ watts and 240 watts at $I = 10$ A and 1 A

Power(in) = $D V_g I \Rightarrow 2478$ watts and 242 watts at $D = 0.955$ and 0.62

$P_{in(max)} = 2478 - 2400 = 78$ watts, which is at $V_g = 260$ V and $I = 10$ A

$\eta = P_{out}/P_{in} = 2400/2478 * 100\% = 96.85\%$

Buck converter with variable input voltage and load current

	nominal		H	L	H	L
V_{in}	240	240	390	240	390	240
I	10	10	10	10	10	10
V_D	240	240	240	240	240	240
R_{on}	0.7	0.7	0.7	0.7	0.7	0.7
R_{os}	0.8	0.8	0.8	0.8	0.8	0.8
R_D	0.2	0.2	0.2	0.2	0.2	0.2

D	0.7592	0.6306	0.9529	0.8175	0.9262
Output	0.7285	0.6154	0.9231	0.6154	0.9231

efficiency	97.27%	97.04%	96.87%	99.05%	99.85%
Power loss	67.28 W	60.55 W	77.51 W	0.84 W	0.81 W

D varies between
0.6175 and
0.9529

Minimum output power is
0.81 W

which occurs at min V_{in} and max I
Power loss at this point is
77.51 W

High I


low I

← 99 50

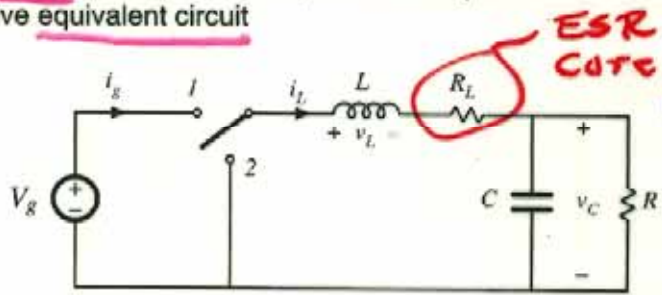3.4. How to obtain the input port of the model

Real Buck Model

Buck converter example — use procedure of previous section to derive equivalent circuit



ESR
Core loss

E.C. loss as f^N .
Hysteresis as f^N ?

Average inductor voltage and capacitor current:

$$\langle v_L \rangle = 0 = DV_g - I_L R_L - V_C$$

$$\langle i_C \rangle = 0 = I_L - V_C / R$$


Together same ckt loop
is it input or output?

Construct equivalent circuit as usual

$$\langle v_L \rangle = 0 = DV_s - I_L R_L - V_C$$

$$\langle i_C \rangle = 0 = I_L - V_C / R$$

Fig 3.17
p 50

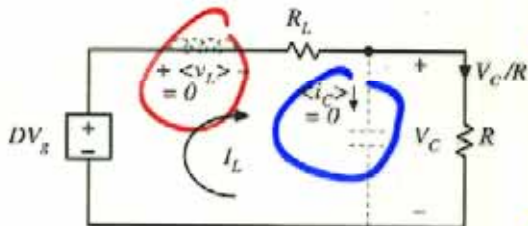

Output part only

What happened to the transformer?

- Need another equation


Whats an equation for Trf?

Modeling the converter input port

Input current waveform $i_g(t)$:

← Good choice for input port

Fig 3.18
P 51

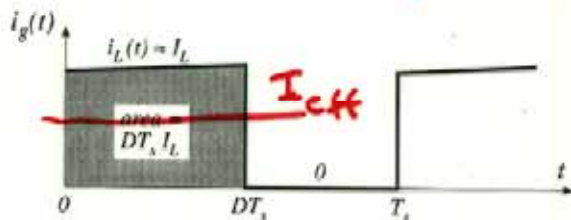

Dc component (average value) of $i_g(t)$ is

$$I_g = \frac{1}{T_s} \int_0^{T_s} i_g(t) dt = DI_L = I_{eff}$$

Input port equivalent circuit

$$I_g = \frac{1}{T_s} \int_0^{T_s} i_g(t) dt = DI_L$$

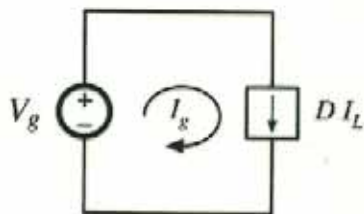


Fig 3.19
pg 51

Complete equivalent circuit, buck converter

Now combine both and simplify

Input and output port equivalent circuits, drawn together:


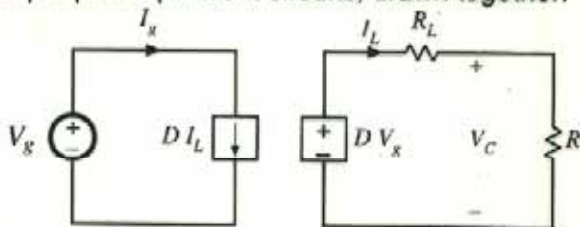


Fig 3.20
Fig 3.21
Pg 51

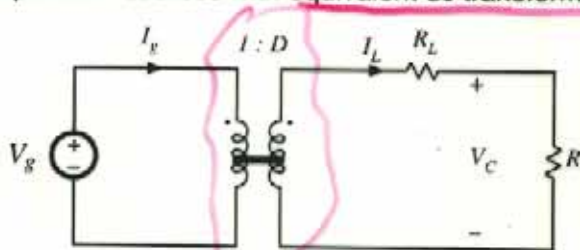Replace dependent sources with equivalent dc transformer:




Move all to input port. How?

Talk #1



Paper #1 Astec

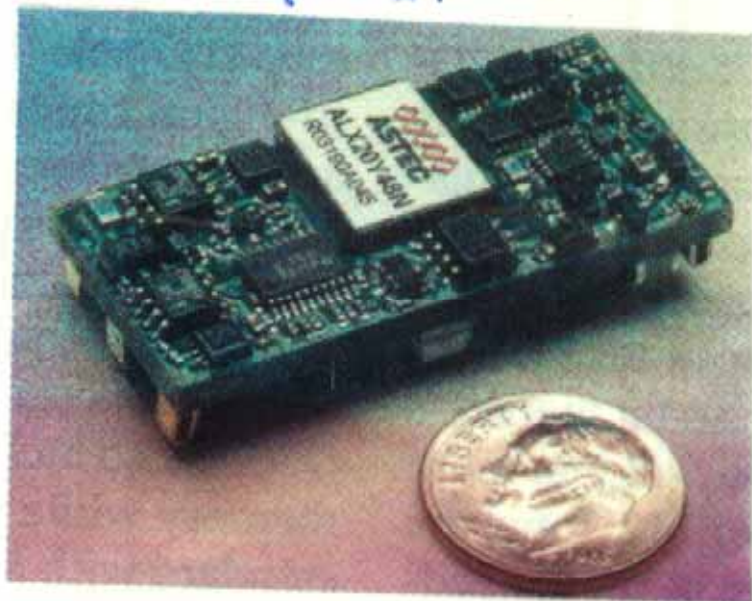

ALX series provides up to 20 A and 50 W for datacom and wireless apps.

Bulk Power (AC/DC) Cost

