

ECE 562


Week 7 Lecture 2

Fall 2008


## Week 7 Lecture 2 Summary

- Section notes
  - Slides 3-6 – In-class talk criteria
  - Slides 7-25 – Insulated Gate Bipolar Transistors (IGBTs)
  - Slides 26-28 – IGBT applications
  - Slide 29-44 IGBT switch characteristics
  - Slides 45-46 – Homework problem 4.7
  - Slides 47-52 – Switching efficiencies
  - Slides 53-57 – Varistors

Paper      Powerpoint

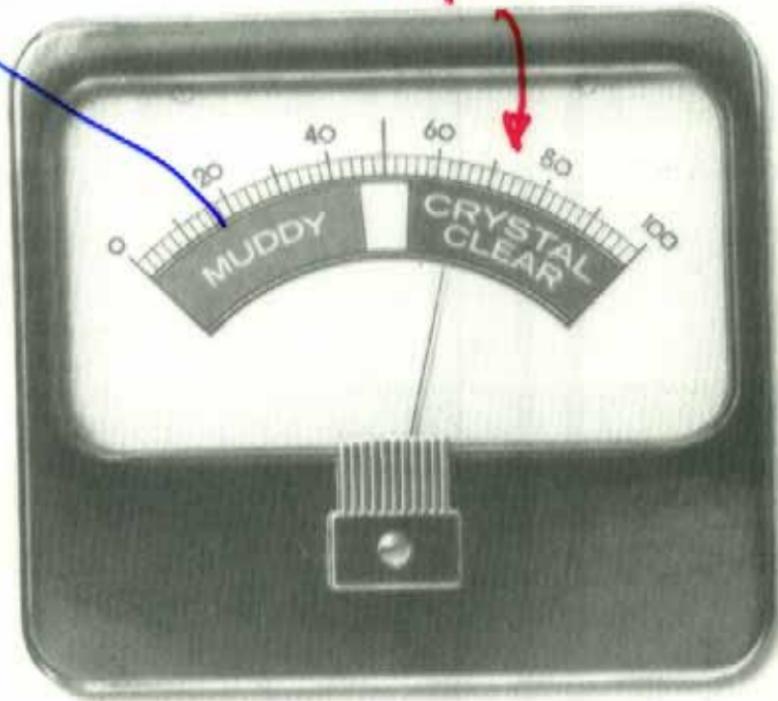


CLARITY

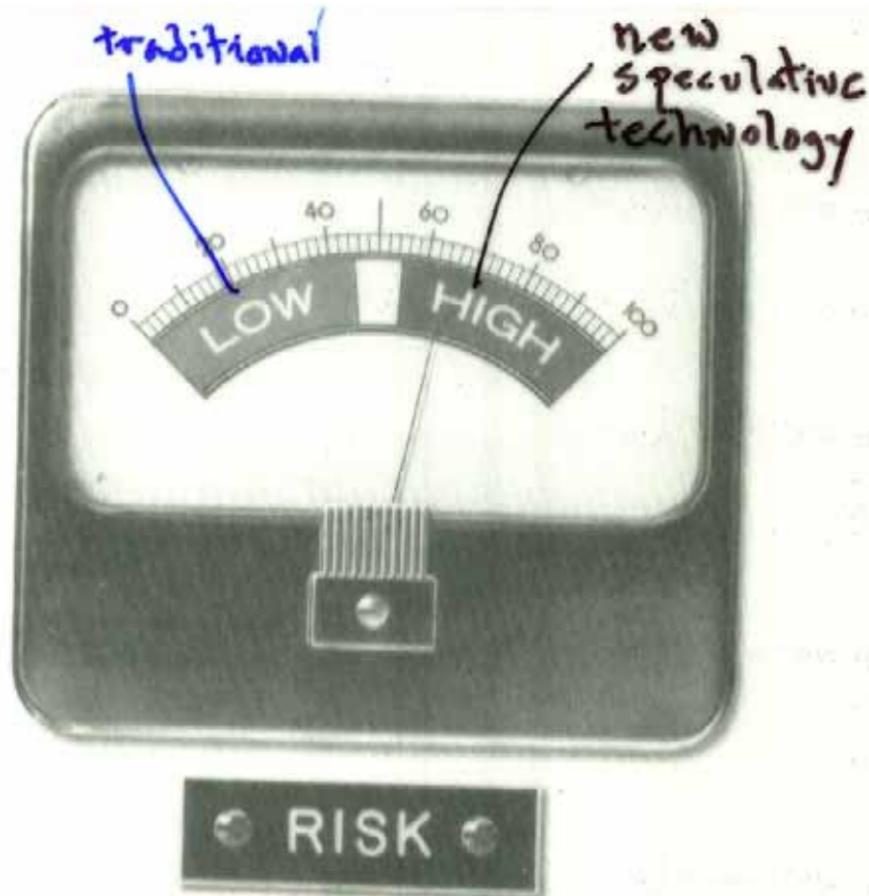


Know it  
when you  
encounter  
it

truth  
tested

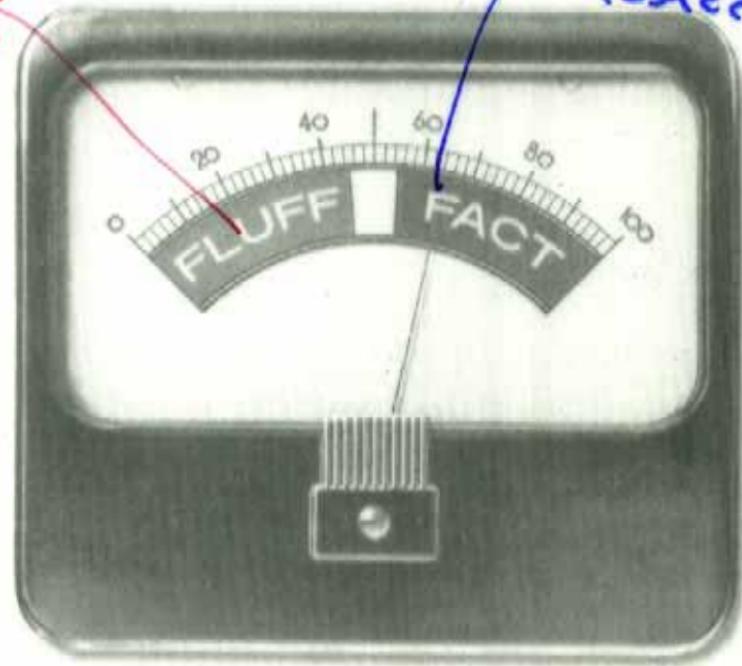

• HONESTY •

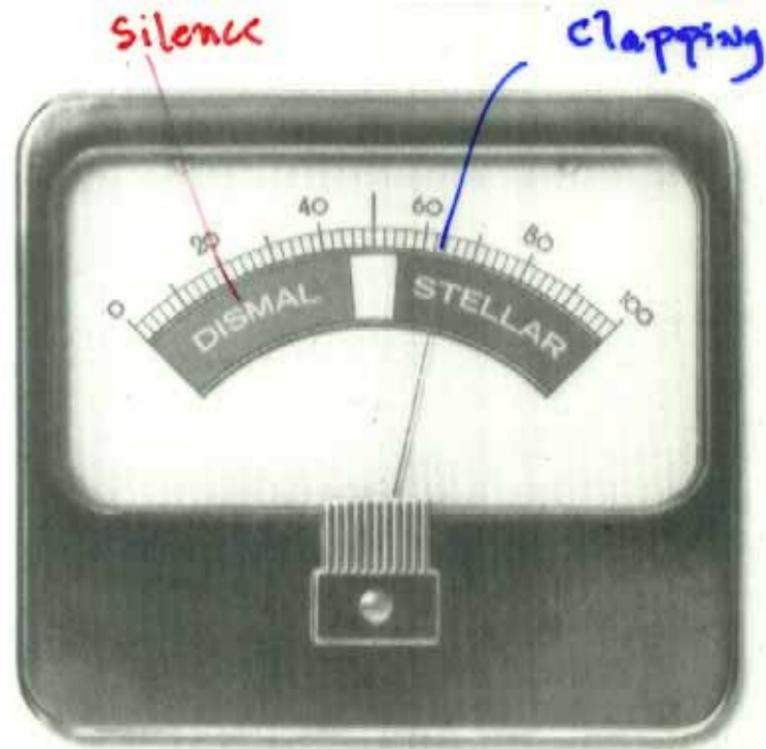

● PERFORMANCE ●

## Summary of chapter 4

1. How an SPST ideal switch can be realized using semiconductor devices depends on the polarity of the voltage which the devices must block in the off-state, and on the polarity of the current which the devices must conduct in the on-state. OK?
2. Single-quadrant SPST switches can be realized using a single transistor or a single diode, depending on the relative polarities of the off-state voltage and on-state current. OK?
3. Two-quadrant SPST switches can be realized using a transistor and diode, connected in series (bidirectional-voltage) or in anti-parallel (bidirectional-current). Several four-quadrant schemes are also listed here. OK?
4. A "synchronous rectifier" is a MOSFET connected to conduct reverse current, with gate drive control as necessary. This device can be used where a diode would otherwise be required. If a MOSFET with sufficiently low  $R_{on}$  is used, reduced conduction loss is obtained. OK?

FET:  $I_{ON} R_{DS} \leq 0.7V$       BJT  $\frac{I_{ON}}{I_0} \frac{V_{CE}}{0.2}$

$I_{DS} = 20A$        $I_{CQ} = 10mA$        $P = 4mW$        $P = 14W$

**International Rectifier introduces Economical, High Power, 150kHz IGBTs for High Frequency SMPS Applications**

EL SEGUNDO, Calif., February 2003 - International Rectifier (IRI) (NYSE: IRF), today introduces new WARP2™ 600V 50A, 55A and 60A non-punch through (NPT) IGBTs with improved turn-off characteristics for high current, high frequency switch-mode power supply (SMPS) circuits in telecom and server systems. The new WARP2 NPT IGBTs offer performance and efficiency with a better price-to-performance value than power MOSFETs. The WARP2 IGBTs are co-packaged with HEXFRED® diodes, which enable better performance compared to the integral body diodes in power MOSFETs. The new devices are available in the TO-247 and TO-220 packages.




Part Number	Package	V <sub>DS(on)</sub>	I <sub>C (25°C)</sub>	V <sub>G (on)</sub> (typ)	Collector Diode	T <sub>case</sub> (C)
IRGP5005P1	TO-247	600	50A	2.0V @ 25A	15A	180°C
IRGP5505P1	TO-247	600	55A	1.95V @ 25A	15A	160°C
IRGP6005P1	TO-247	600	60A	2.05V @ 15A	8A	180°C
IRGP6005P1	TO-220	600	55A	2.05V @ 15A	4A	180°C

Early IGBT  
Similar I, V to FET Big  
Qg  
Lower ON loss

**Availability and Pricing**

The new high frequency NPT IGBTs are available immediately. Pricing begins at \$1.05 each for the IRGP5005P1 in 10,000-unit quantities.
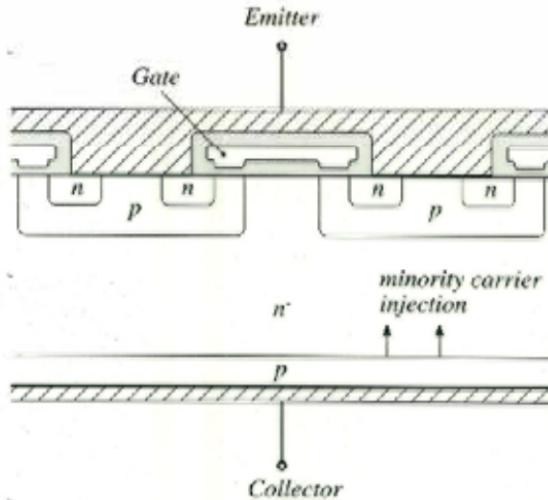
#### 4.2.4. The Insulated Gate Bipolar Transistor (IGBT)





- A four-layer device
- Similar in construction to MOSFET, except extra p region
- On-state: minority carriers are injected into n+ region, leading to conductivity modulation
- compared with MOSFET: slower switching times, lower on-resistance, useful at higher voltages (up to 1700V)


8kV latest IGBT  
for power grid


Chapter 4: Switch realization

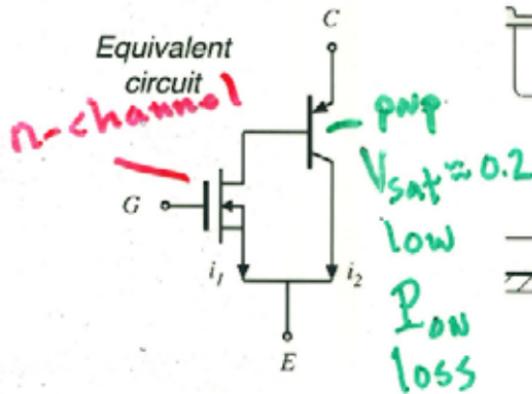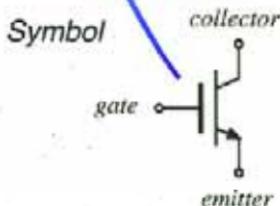$Q_G$  to switch  $50-200nC$   
 $P = C V_{th} f_{SW}$  The IGBT



Location of equivalent devices

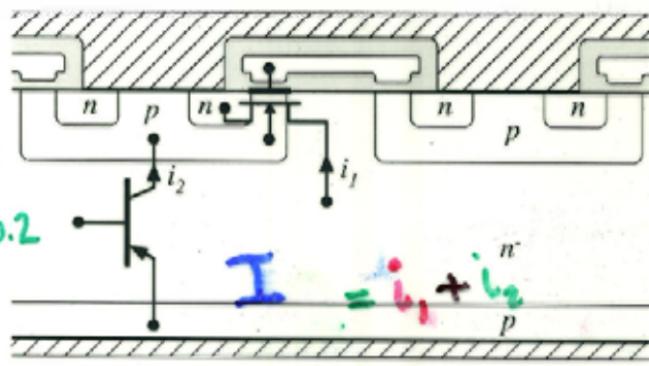

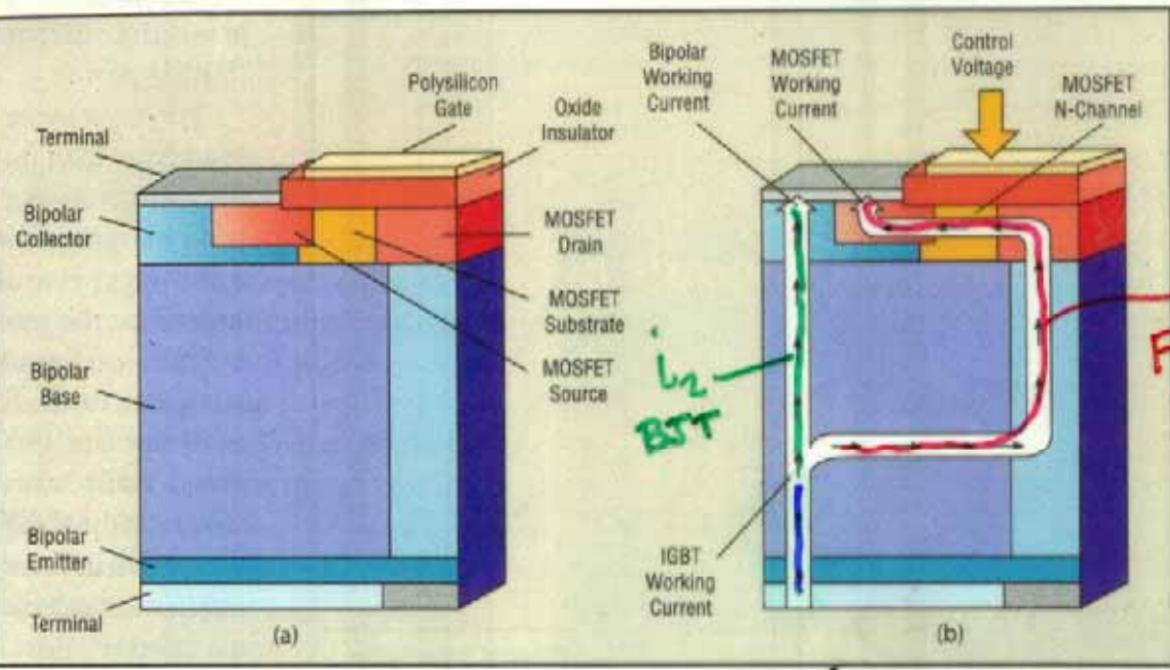

**Fig. 2.** IGBT builds on bipolar and MOSFET design. An IGBT employs both bipolar and MOSFET building blocks (a); consequently, IGBT current, shown in IGBT ON state (b), comprises both bipolar and MOSFET currents.

$$I^T = I(BJT) + I(MOSFET)$$

IGBTs Preferred	MOSFETs Preferred	IGBT Applications	MOSFET Applications
<u>High duty cycle</u> <i>low fsw</i>	Low duty cycle	Motor control	Switched-mode power supplies
Frequencies of <u>20 kHz or less</u>	Applications of <u>200 kHz or more</u>	Uninterruptible power supplies	Battery charging
Small line or load variation	Wide line or load variation	Welding	
High-voltage applications of <u>1000 V or more</u>	Low-voltage applications of <u>200 V or less</u>	Low power lighting	<i>White goods applications</i>
Output power of <u>5 kW or more</u>	Power outputs of <u>500 W or less</u>		
Junction temperatures of <u>100°C or more</u>			

Table. IGBTs versus MOSFETs.

High Duty Cycle on  $\Rightarrow$   $P_{on}$  matters



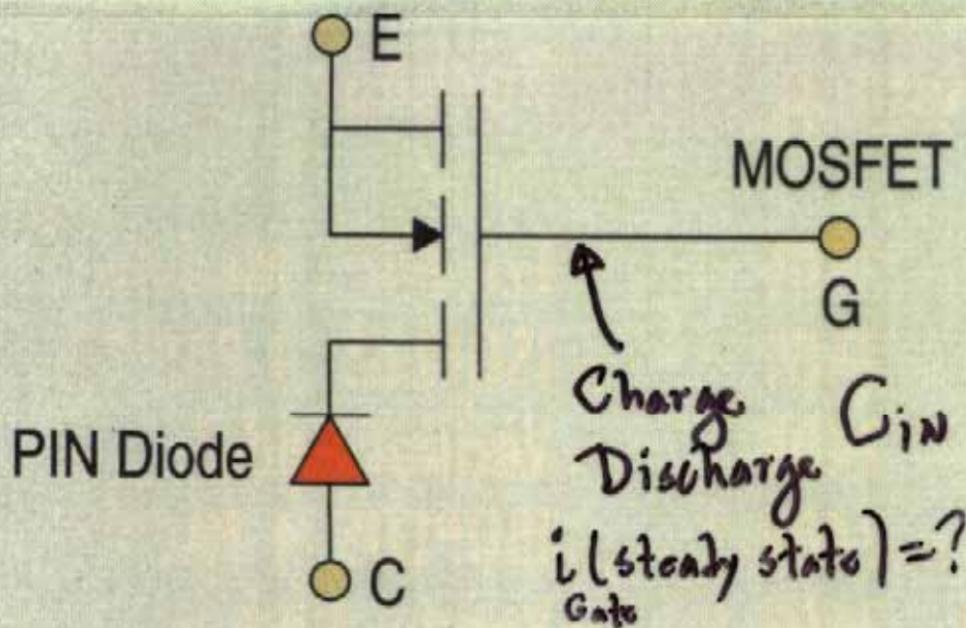


Fig. 1. On-State Model of IGBT.

Apples

Oranges

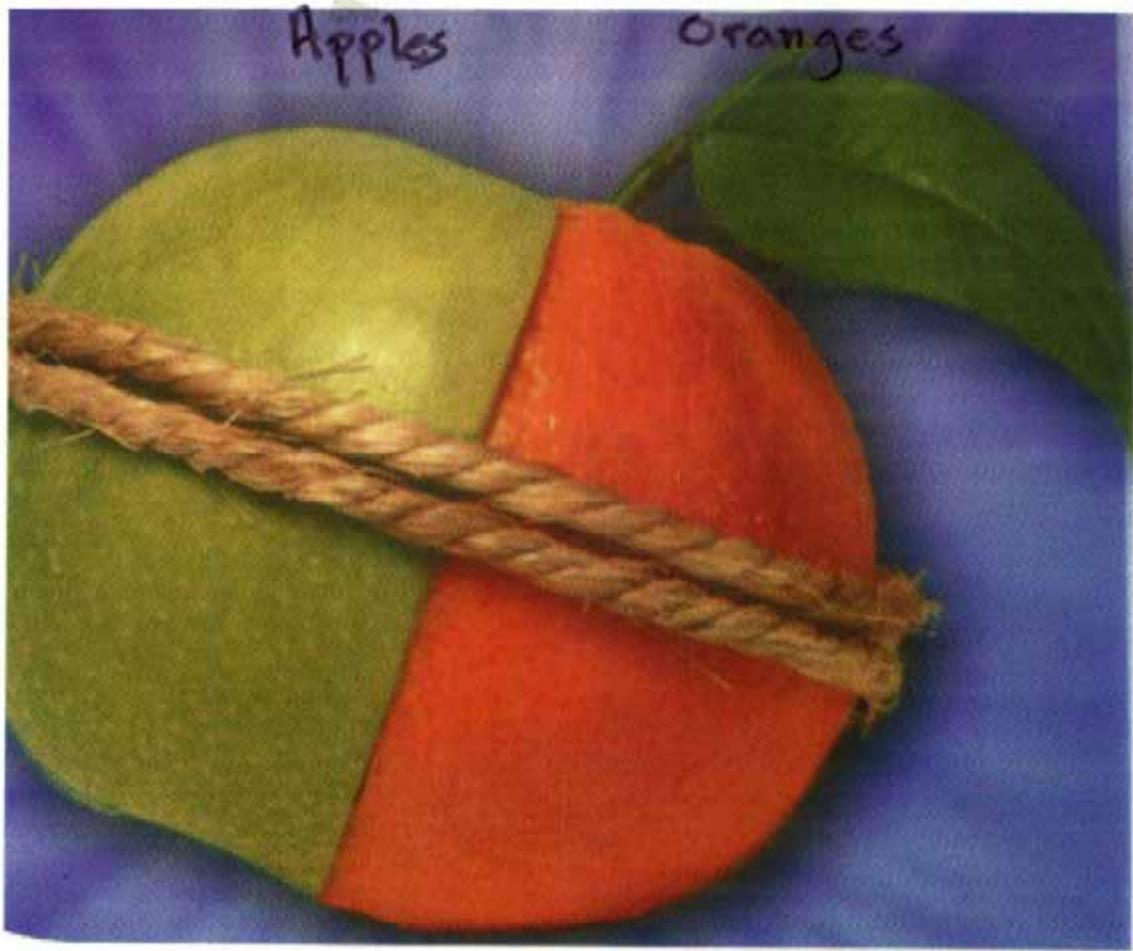

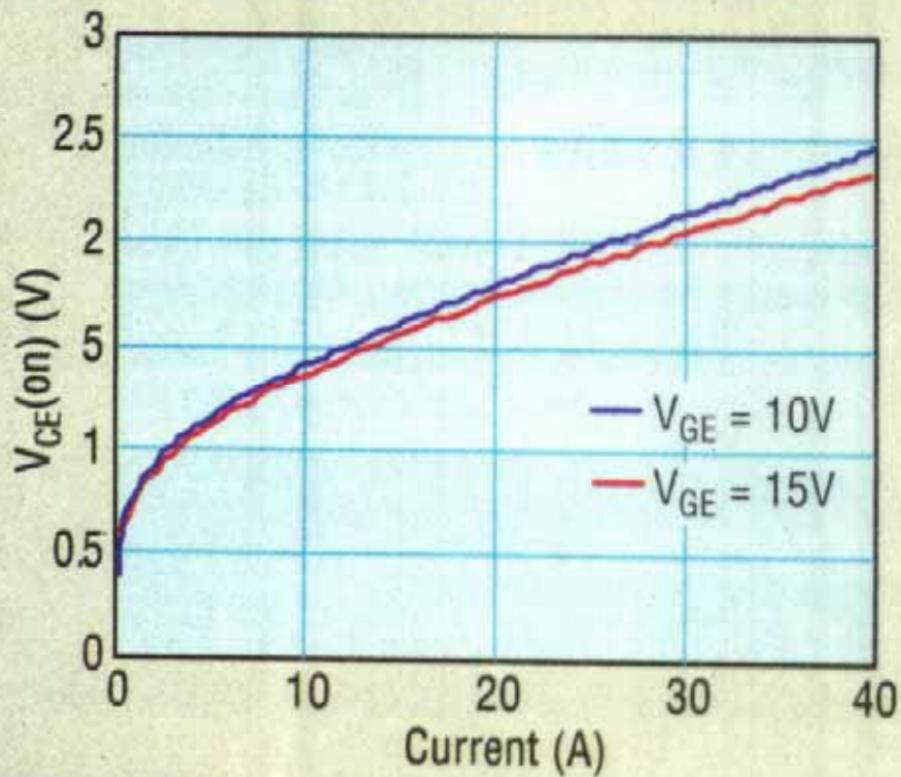

Output  
V<sub>across</sub>  
I<sub>through</sub>

Fig. 4. APT30GP60B on-state voltage vs. current

Input  $V_g - Q_g$

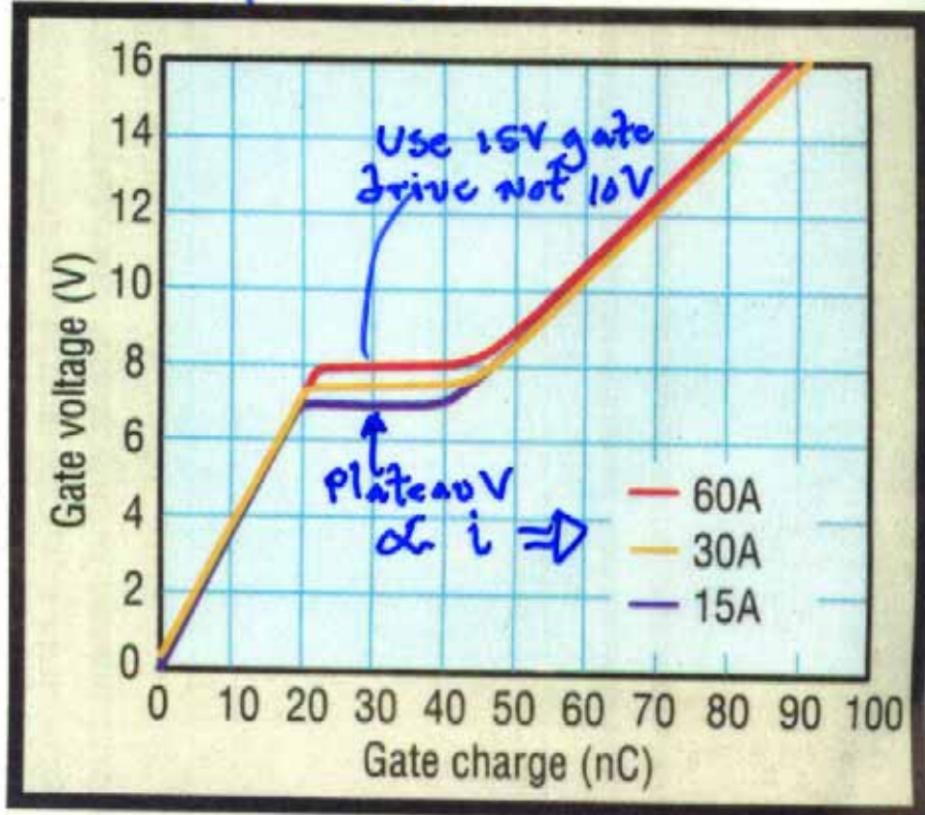


Fig. 5. Gate charge for APT30GP60B at 15A, 30A

# Best Feature 12V Power Tech Snapshot


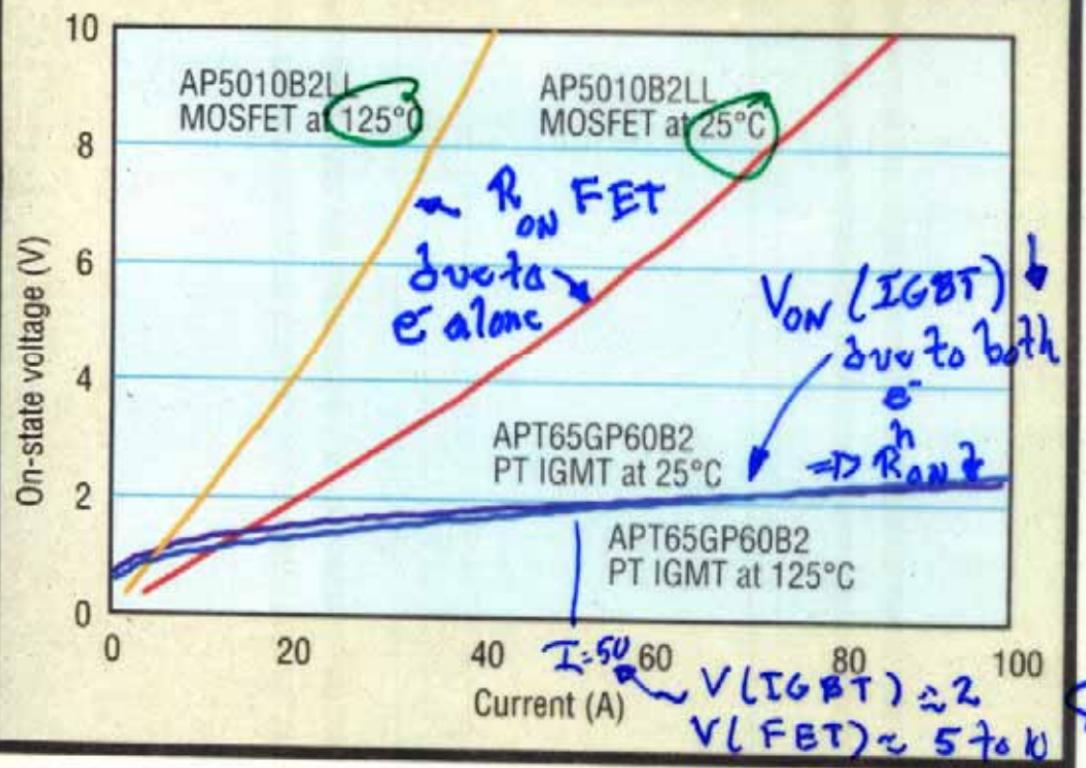


Fig. 1. On-state voltage vs. current for same size power MOSFET and IGBT, 15V gate bias.

Fig 4.34 Pg 86
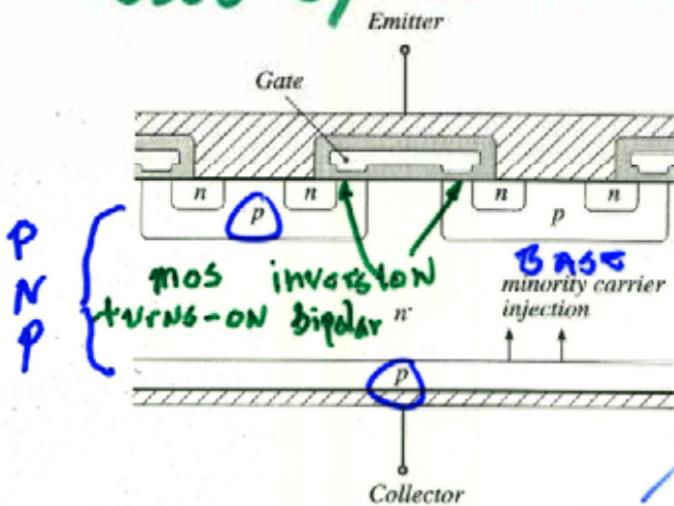
#### 4.2.4. The Insulated Gate Bipolar Transistor (IGBT)

NEW Kid in town wide use  
Used by "Motor Heads"  $\Rightarrow$  lower cost Lowf HighI





- A four-layer device
- Similar in construction to MOSFET, except extra p region
- On-state: minority carriers are injected into n<sup>-</sup> region, leading to conductivity modulation
- compared with MOSFET:  
 slower switching times,  
lower on-resistance, useful  
at higher voltages (up to 1700V)

f up to 100KHz  
 typically 30 KHz  
 B600 V


Figs 4.38  
4.39 Pg 207

### The IGBT

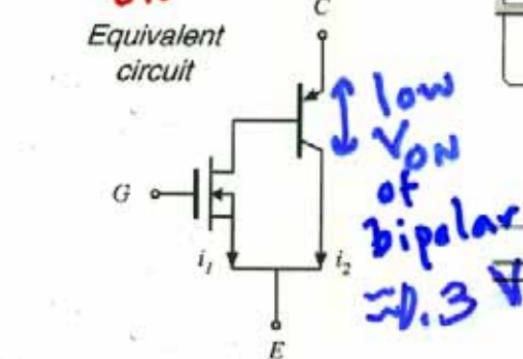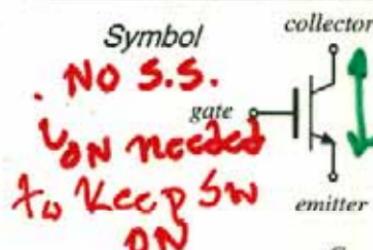

early IGBT 1700V - 2600V }  
Now in place is 8000V IGBT  
for "Power" system DVC

Location of equivalent devices

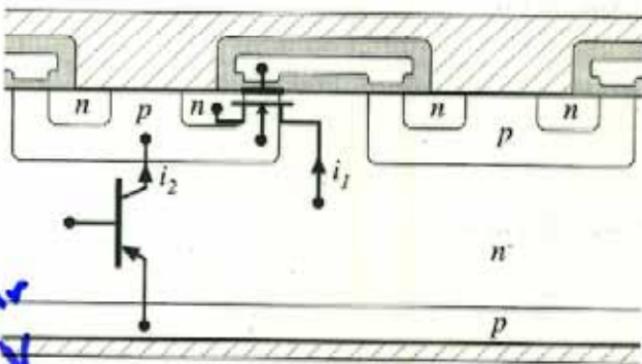

# High-Voltage High-Power IGBTs $\rightarrow I_{on}$

Connection	$I_c$ $V_{CES}$	400A	600A	1200A	1800A
Single	3300V	MBN400C33A*	MBN600C33A*	MBN1200D33A*	
	2500V			MBN1200D25B*	
	2000V	MBN400C20	MBN600C20		
	1700V				MBN1800D17A*

$\uparrow$   
 $V_{off\ (max)}$

$I_{on\ Volt} \approx M.W$   
 switching  
 for  
 several  
 $\mu s$



1Vg not for wires

APT75GP120J

1200V

## POWER MOS 7™ IGBT



The POWER MOS 7™ IGBT is a new generation of high voltage power IGBTs. Using Punch Through Technology this IGBT is ideal for many high frequency, high voltage switching applications and has been optimized for high frequency switchmode power supplies.

- Low Conduction Loss
- Low Gate Charge
- Ultrafast Tail Current shutdown
- 50 kHz operation @ 800V, 20A
- 20 kHz operation @ 800V, 44A
- RBSOA rated

↑ derated  
f ↑ derated

## MAXIMUM RATINGS

All Ratings:  $T_c = 25^\circ\text{C}$  unless otherwise specified.

Symbol / Parameter	AP75GP120J	Unit
$V_{CE}$ Collector-Emitter Voltage	1200	
$V_{GE}$ Gate-Emitter Voltage	±30	Volt
$V_{GSW}$ Gate-Emitter Voltage Threshold	4.0	
$I_C$ Continuous Collector Current @ $T_c = 25^\circ\text{C}$	120	
$I_{C2}$ Continuous Collector Current @ $T_c = 175^\circ\text{C}$	57	Amps
$I_{CR}$ Pulsed Collector Current @ $T_c = 25^\circ\text{C}$	300	
RBSOA Reverse Bias Safe Operating Area @ $T_j = 150^\circ\text{C}$	200A @ 800V	
$P_D$ Total Power Dissipation	643	Watts
$T_J-T_{J2}$ Operating and Storage Junction Temperature Range	-65 to 150	°C
$T_L$ Min. Lead Temp. for Soldering (0.03" Iron, Dew Point: 100°C)	300	


## STATIC ELECTRICAL CHARACTERISTICS

Symbol / Characteristic / Test Conditions	MIN	TYP	MAX	UNIT
$V_{GDS(0)}$ Collector-Emitter Breakdown Voltage ( $V_{CE} = 2V$ , $I_C = 1000\mu\text{A}$ )	1200			
$V_{GS(0.1)}$ Gate Threshold Voltage ( $V_{CE} = V_{GS} - I_C = 2.5\text{V}$ , $T_j = 25^\circ\text{C}$ )	3	4.5	6	Volt
$V_{GS(0.5)}$ Collector-Emitter On Voltage ( $V_{CE} = 10V$ , $I_C = 75A$ , $T_j = 25^\circ\text{C}$ )	2.3	3.8		
$V_{GS(1.0)}$ Collector-Emitter On Voltage ( $V_{CE} = 10V$ , $I_C = 75A$ , $T_j = 125^\circ\text{C}$ )	3.0			
$I_{CBO}$ Collector-Cutoff Current ( $V_{CE} = 1200V$ , $V_{GS} = 0V$ , $T_j = 25^\circ\text{C}$ )		1000		µA
$I_{CBO}$ Collector-Cutoff Current ( $V_{CE} = 1200V$ , $V_{GS} = 0V$ , $T_j = 125^\circ\text{C}$ )		5000		µA
$I_{GSS}$ Gate-Emitter Leakage Current ( $V_{GS} = ±20V$ )		±100		nA

CAUTION: These Devices are Sensitive to Electrostatic Discharge. Proper Handling Procedures Should Be Followed.

**Table 1. Measured IGBT Parameters.**

Test Equipment	DTS_2012T IGBT TESTER
IGBT	BSM75GB120DN2(SIEMENS)
Breakdown voltage ( $V_B$ )(V)	1237
Threshold voltage ( $V_{TH}$ )(V)	5. 517
Oxide thickness ( $t_{OX}$ )(nm)	85
On_state voltage (V)	3. 165( $I_A = 75A, V_g = 12 V$ )
Turn on loss (mj)	16. 16
Turn off loss (mj)	7. 58
A (cm <sup>2</sup> )	1. 198 × 1. 198

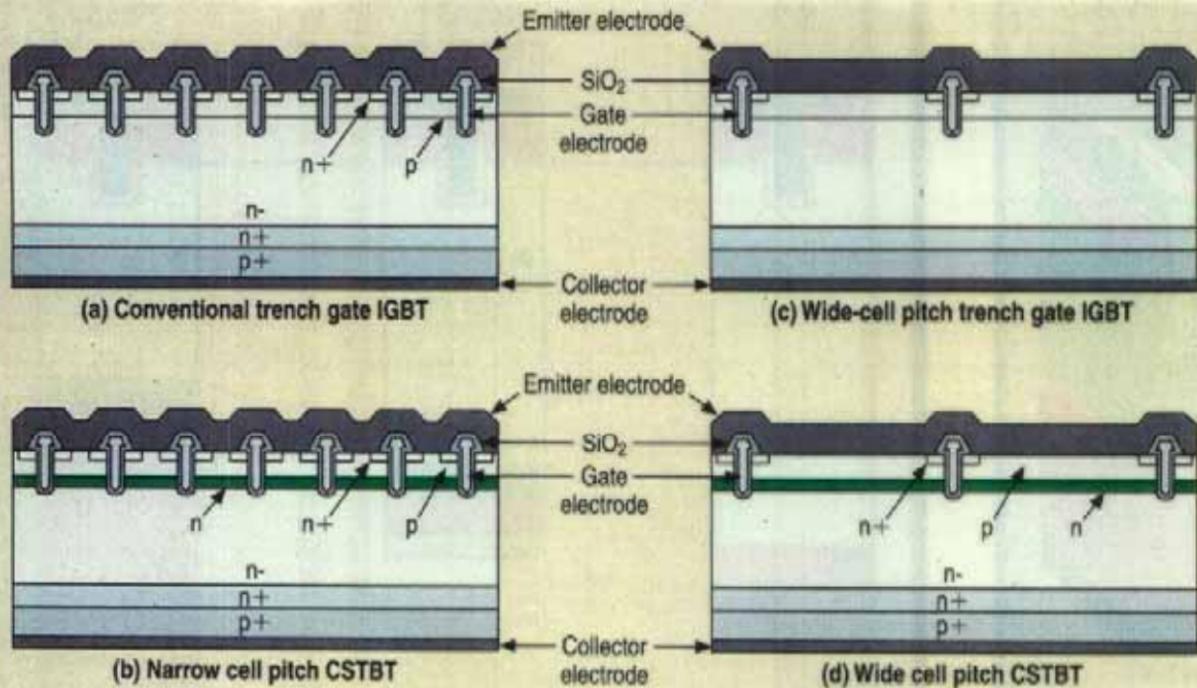

**Fig. 5. IGBT chip structure comparison: a. Conventional trench gate IGBT; b. Narrow cell pitch CSTBT; c. Wide cell pitch trench gate IGBT; d. Wide cell pitch CSTBT.**

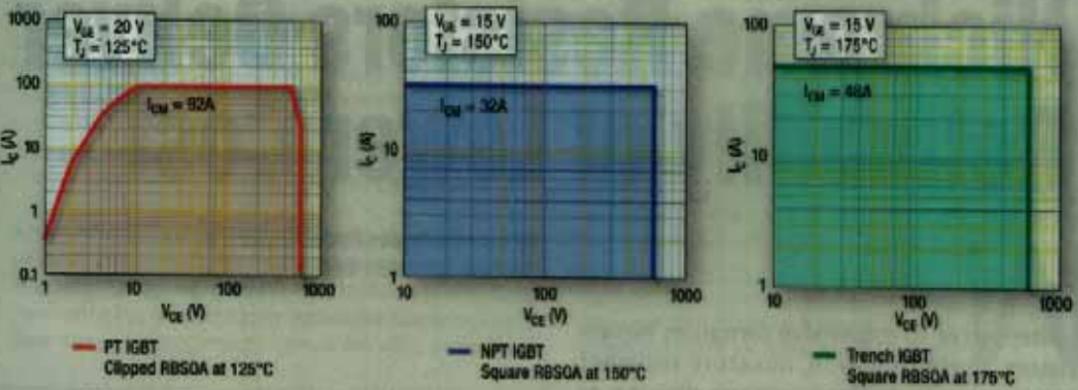


Fig. 7. The wide square-shaped RBSOA characteristic illustrates the robustness of the DS trench IGBT.

## Conclusions: IGBT

- Becoming the device of choice in 500-1700V applications, at power levels of 1-1000kW
- Positive temperature coefficient at high current —easy to parallel and construct modules
- Forward voltage drop: diode in series with on-resistance, 2-4V typical
- Easy to drive —similar to MOSFET
- Slower than MOSFET, but faster than Darlington, GTO, SCR
- Typical switching frequencies: 3-30kHz
- IGBT technology is rapidly advancing —next generation: 2500V


! 6000 !

— ? 10kV  
? 12kV  
o power system


*Joe*
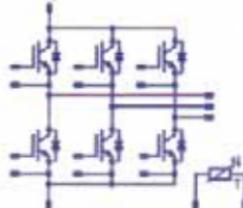
# High Power Sixpacks for Motor Drives

flowPACK 2 3<sup>rd</sup> gen  
up to 150A at 1200V



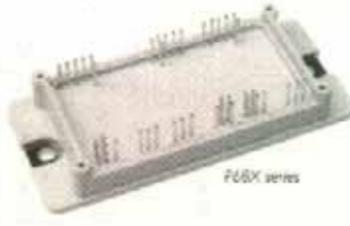- IGBT4 technology for low saturation losses and improved EMC behavior
- Low inductance layout and compact design
- High power flow 2 housing



## Characteristics of several commercial devices

Part number	Rated max voltage	Rated avg current	$V_F$ (typical)	$t_f$ (typical)
<i>Single-chip devices</i>				
HGTG32N60E2	600V	32A	2.4V	0.62μs
HGTG30N120D2	1200V	30A	3.2A	0.58μs
<i>Multiple-chip power modules</i>				
CM400HA-12E	600V	400A	2.7V	0.3μs
CM300HA-24E	1200V	300A	2.7V	0.3μs

9588

## Characteristics of several commercial devices

Part number	Rated max voltage	Rated avg current	$V_f$ (typical)	$t_f$ (typical)
<i>Single-chip devices</i>				
HGTG32N60E2	600V	32A	2.4V	0.62μs
HGTG30N120D2	1200V	30A	3.2A	0.58μs
<i>Multiple-chip power modules</i>				
CM400HA-12E	600V	400A	2.7V	0.3μs
CM300HA-24E	1200V	300A	2.7V	0.3μs

New 6000V


Non  
Higher  
than bipolar

300ns

## Summary of chapter 4

only at for parasitics

- $f \leq 3 \text{ MHz}$
- $I_{SW}$
- $V_{ON} \downarrow$
- $V_{OF} \downarrow$
- Best of both except At**
5. Majority carrier devices, including the MOSFET and Schottky diode, exhibit very fast switching times, controlled essentially by the charging of the device capacitances. However, the forward voltage drops of these devices increases quickly with increasing breakdown voltage.
  6. Minority carrier devices, including the BJT, IGBT, and thyristor family, can exhibit high breakdown voltages with relatively low forward voltage drop. However, the switching times of these devices are longer, and are controlled by the times needed to insert or remove stored minority charge.
  7. Energy is lost during switching transitions, due to a variety of mechanisms. The resulting average power loss, or switching loss, is equal to this energy loss multiplied by the switching frequency. Switching loss imposes an upper limit on the switching frequencies of practical converters.

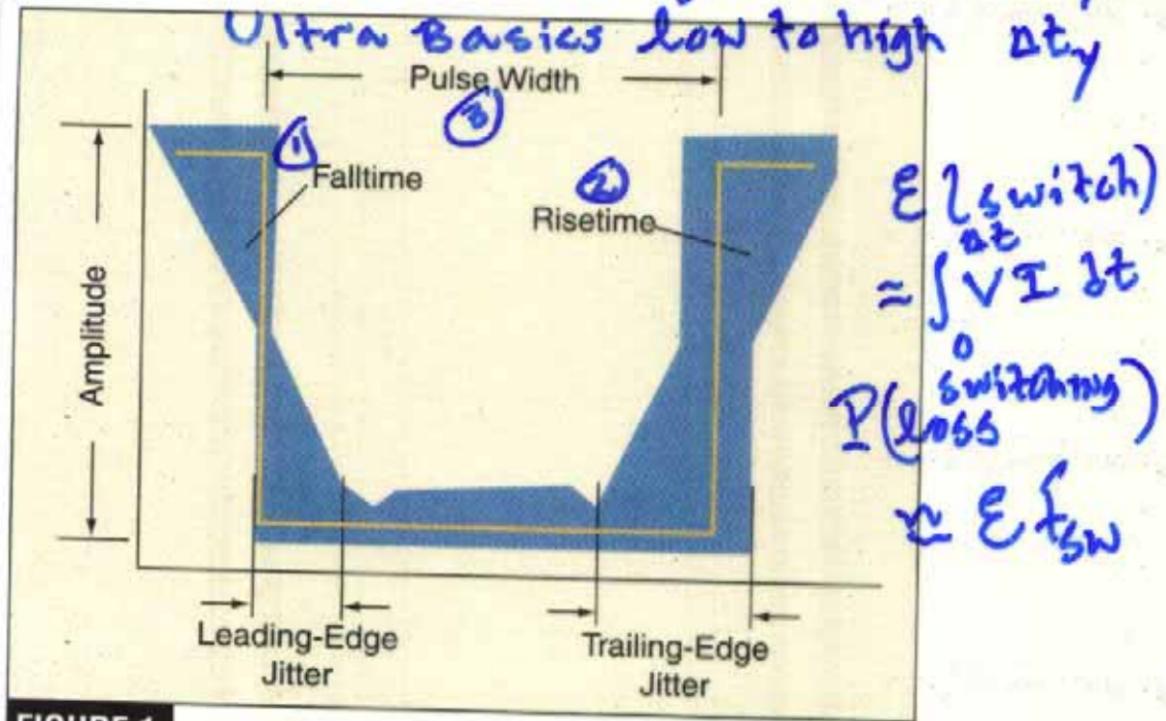

**FIGURE 1** Masks define the amplitude, risetime, falltime, and jitter for pulses in telecom networks.



① ON to off transition "L" load

$$P_{\text{loss}} = \frac{1}{2} V_{\text{off}} I_{\text{ON}}$$

$$W_{\text{loss}} = P_{\text{loss}} * \Delta t$$

Blithley assumes  $I_L$  hangs till  $V_{DS} \rightarrow \text{MAX}$

Fig 3b: Ideal Voltage and Current Waveforms with Inductive Loading

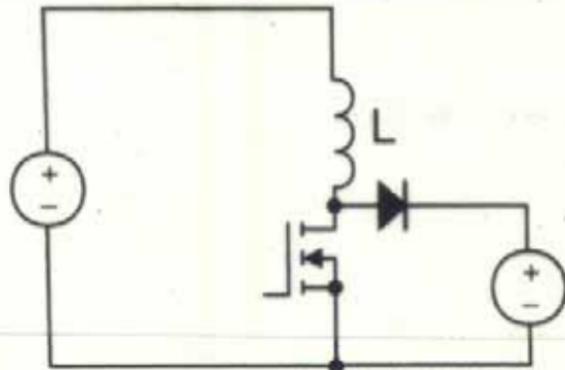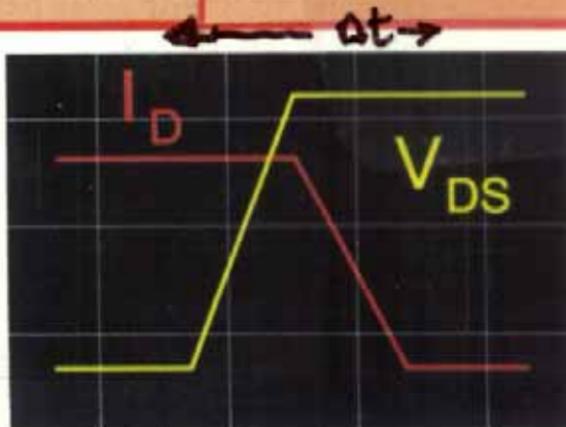



② ON to off Transition R load

$$[t \ V_{off} I_{ON}] = P_{loss}$$

$$P_{loss} * \Delta t = W_{loss}$$

Fig 3a: **Ideal** Voltage and Current Waveforms with Resistive Loading


} other

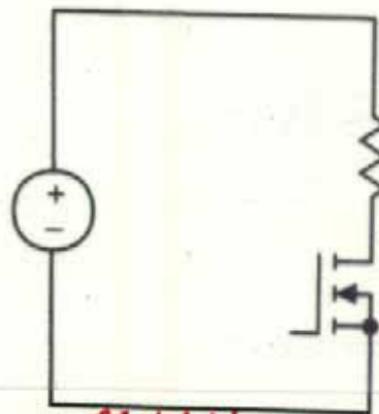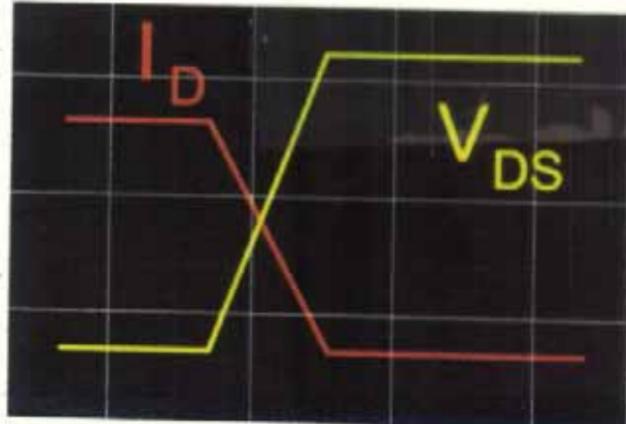

$P_{off}$  due to slow  $i(t)$  decay

160V In, 400V<sub>OUT</sub>, 23A, Duty = 60%  
150 kHz
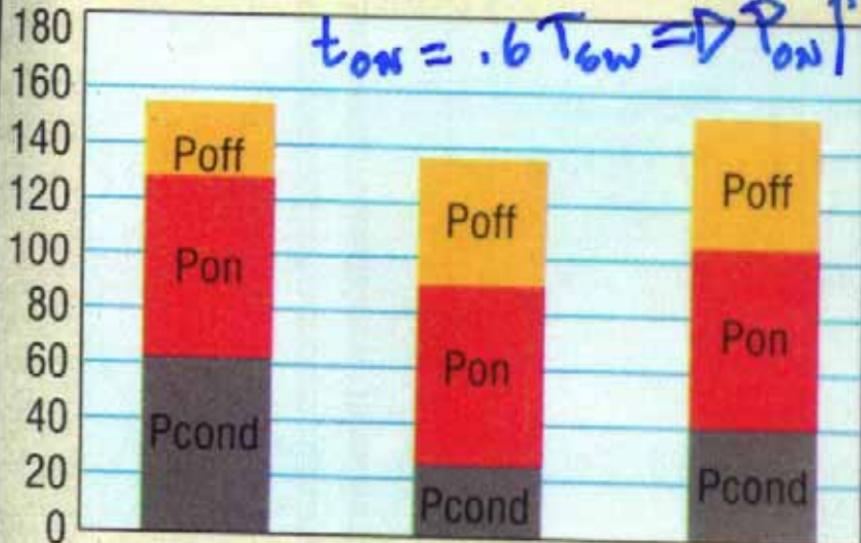
$$t_{on} = .6 T_{sw} \Rightarrow P_{on} \uparrow$$



Total Loss


1. DC losses  
conduction loss
2. Switch Losses

$$P_T = P_{DC} + f_{SW} E_{SW}^T$$

$$E_{SW}^T = E_{SW}^{(on-off)} + E_{SW}^{(off-on)}$$

Fig. 8. Total switch losses, 23A, 60% duty.

At (on-off) (vs)  $V_{CE}$

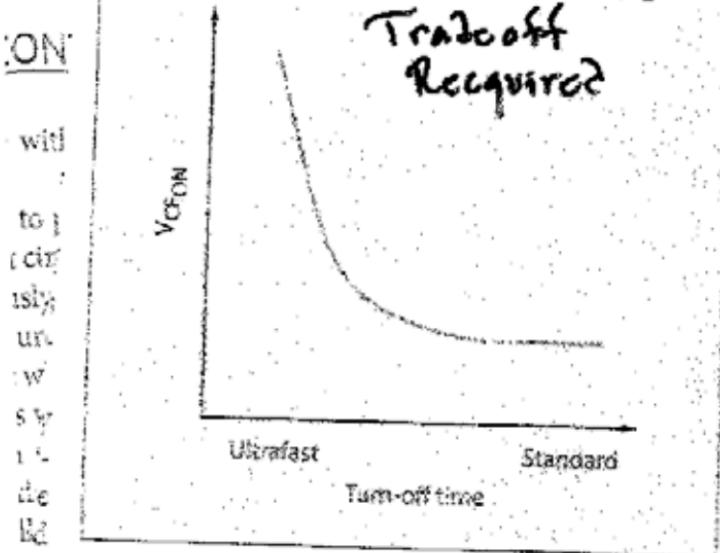

**Fig. 1.** Turn-off time for an IGBT is a function of its collector-emitter voltage ( $V_{CE}$ ). Ultrafast IGBTs have shorter turn-off times than standard-speed IGBTs.

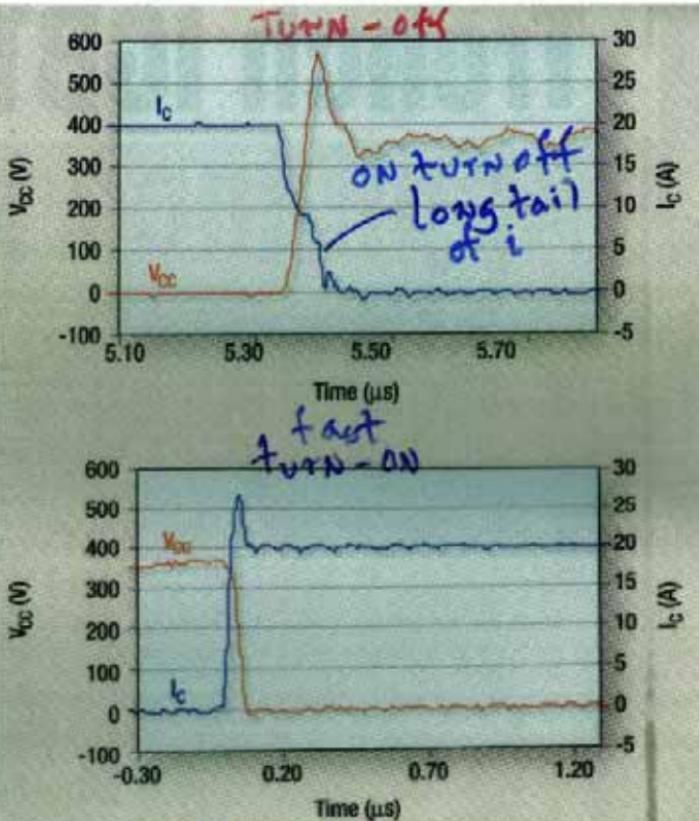


Fig. 3. Typical turn-on (top) and turn-off (bottom) switching waveforms for DS trench IGBT show the smooth turn-off and reduced current tail for these devices ( $V_{CC} = 400$  V;  $I_c = 18$  A;  $L = 200$   $\mu$ H;  $R_g = 22$  W;  $T_{CASE} = 25^\circ\text{C}$ ).


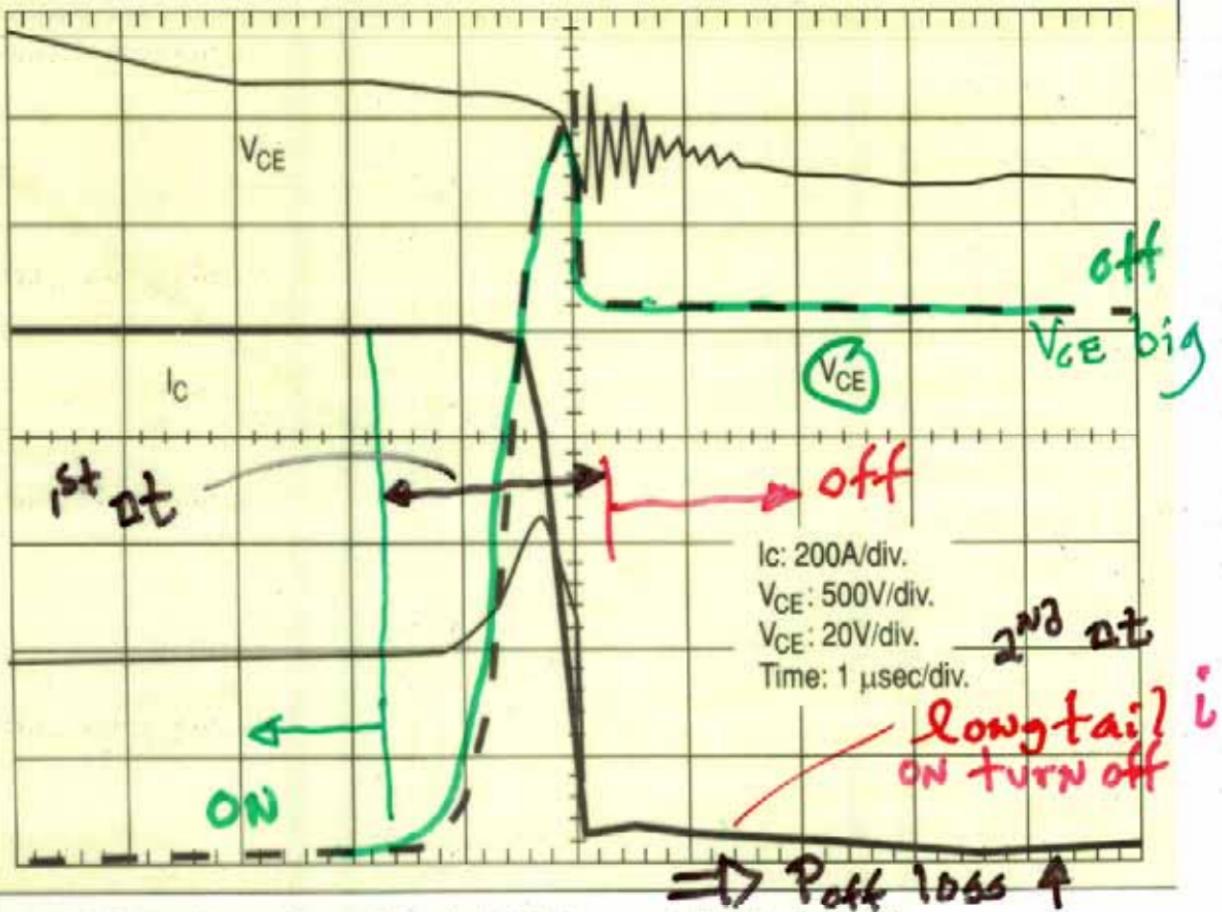



Figure 11. Turn-off waveforms of trench IGBT. Document Toshiba from [13]

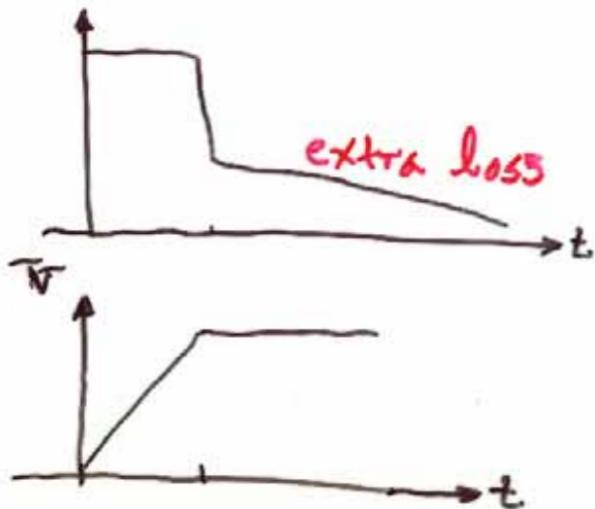Long lived  $i(t)$   
IGBT  
current tail




# Worst Feature Pbm 4.7

~~The IGBT has a tail - a long one~~

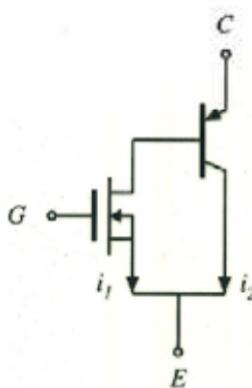

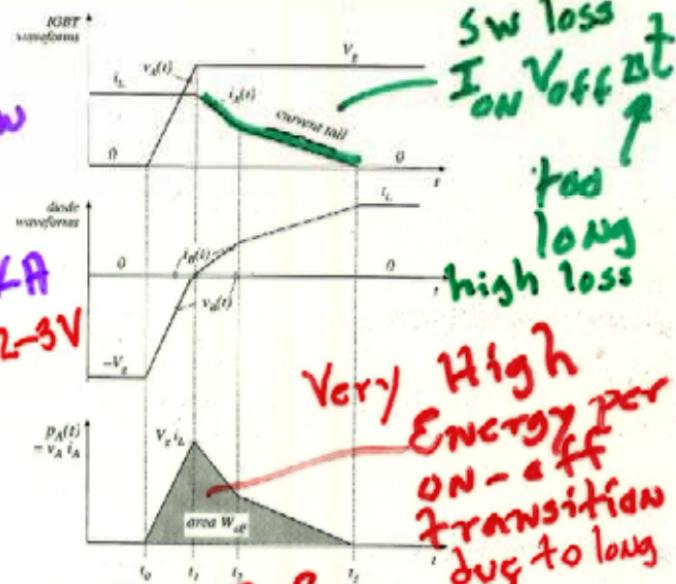WOW  
I<sub>ON</sub>  
of  
1-2 kA  
V<sub>ON</sub>: 2-3V



$$P_{off} = E_{off} f_{sw}$$

Chapter 4: Switch realization

SW loss  
I<sub>ON</sub> V<sub>OFF</sub> BT  
too long  
high loss

Very High Energy per  
on-off transition  
due to long Toff

# Use Modern Sampling Scope

Gating Cursors

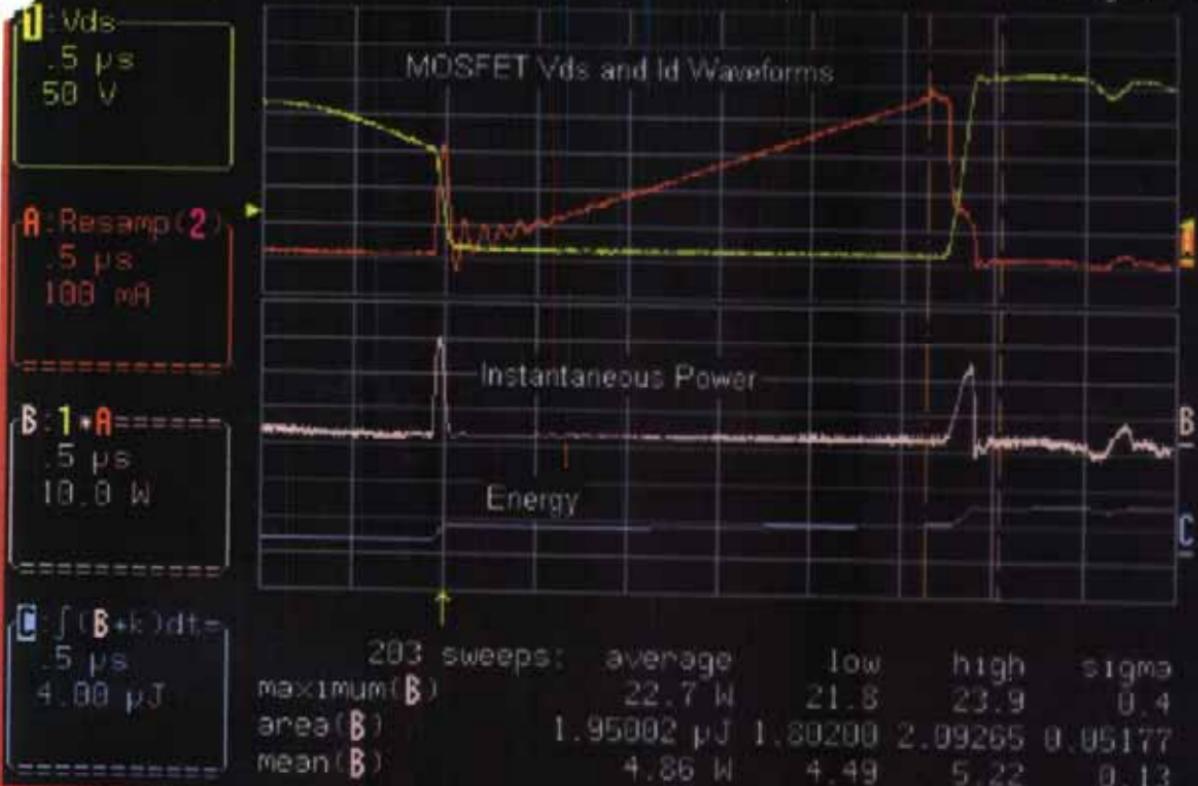


Fig. 4b: Turn-Off Loss Calculations

## Conclusions: IGBT


---

6kV

- Becoming the device of choice in 500 to ~~1700~~V+ applications, at power levels of 1-1000kW
- Positive temperature coefficient at high current — easy to parallel and construct modules
- Forward voltage drop: diode in series with on-resistance. 2-4V typical
- Easy to drive — similar to MOSFET
- Slower than MOSFET, but faster than Darlington, GTO, SCR
- Typical switching frequencies: 3-30kHz
- IGBT technology is rapidly advancing:
  - 3300 V devices: HVIGBTs
  - 150 kHz switching frequencies in 600 V devices

# Real Switch Waveforms

Tek Run: 240MS/s Sample Trig?

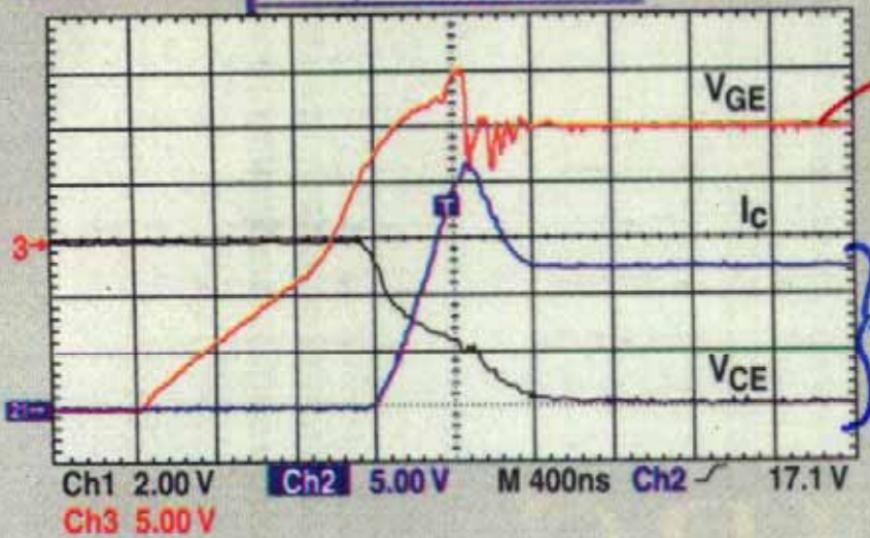

① Drive voltage also has transients and losses not in Erickson

② Output SW losses

Fig. 4(a). FS450R12KE3 characteristics:  
Turn-on.

# Gold Doping reduce $I_{d(t)}$ tail

Tek Run: 250MS/s Sample Trig?


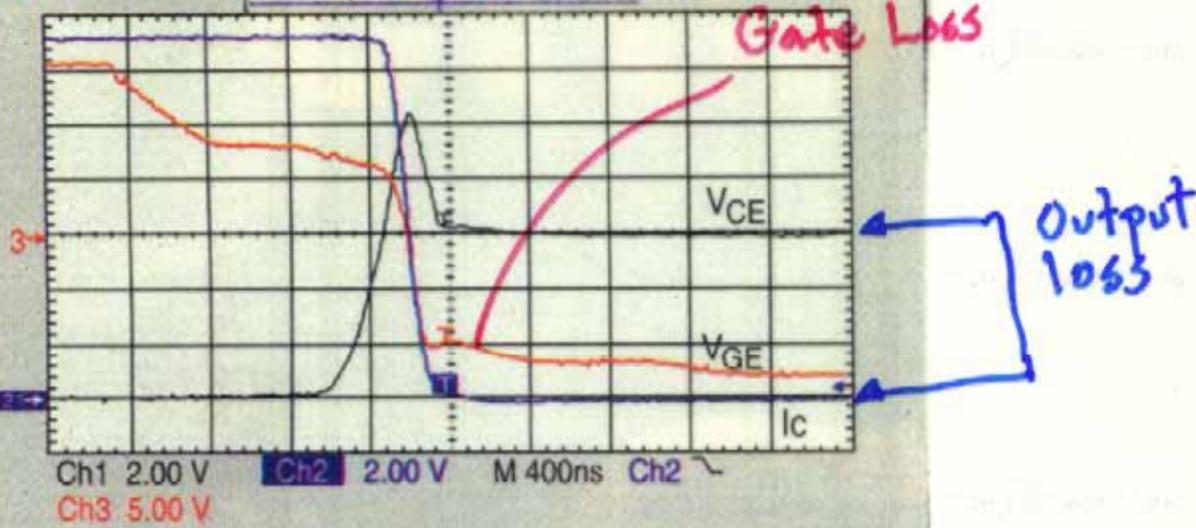


Fig. 4(b). FS450R12KE3 characteristics:  
Turn-off.

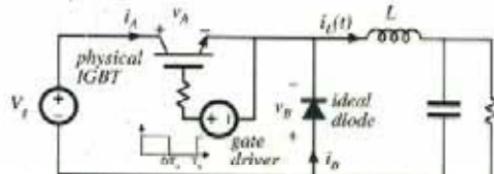
## Switching loss due to current-tailing in IGBT



Example: buck converter with IGBT



$f_{sw}$  each SW cycle  
transistor turn-off transition

$$P_{sw} = \frac{1}{T} \int_{\text{switching transitions}} p_A(t) dt = (W_{on} + W_{off}) f_s$$

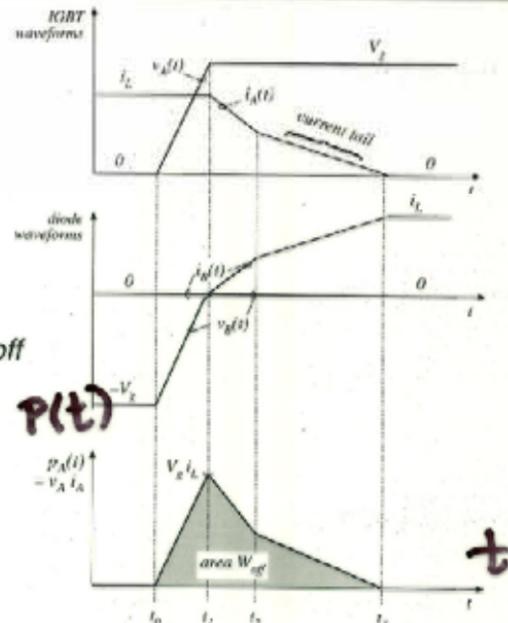

Plan 4.7
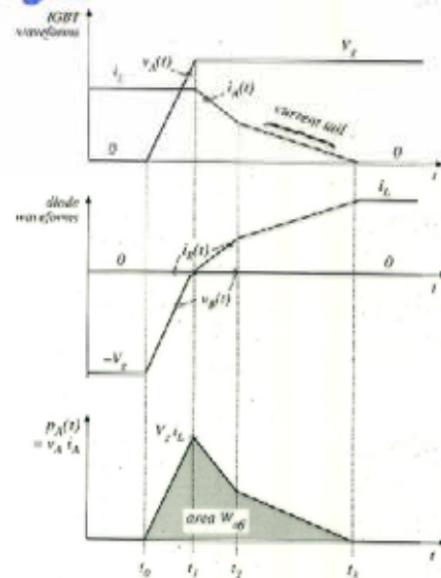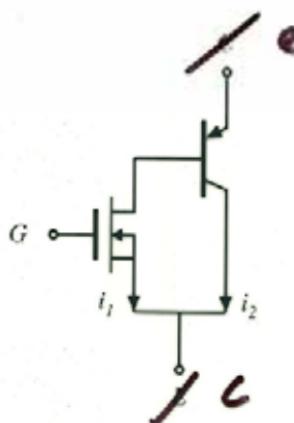
## Current tailing in IGBTs Causes $E_{sw}$ (off-on)




*Modern scope* →  $E_{\text{total}}$   
for transition

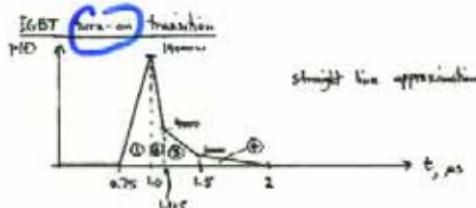Problem 4.7

$$\text{Multiply } V_{CE}(t) I_C(t) = p(t)$$

Estimate energy under  $p(t)$  waveform by graphical integration



time axis: ① - ④:

$$\textcircled{1} \quad \frac{1}{2} (4000)(0.25 \cdot 10^{-6}) = 1.25 \text{ mJ}$$

$$\textcircled{2} \quad \frac{1}{2} (4000+4000)(0.5 \cdot 10^{-6}) = 1.125 \text{ mJ}$$

$$\textcircled{3} \quad \frac{1}{2} (4000+1000)(0.875 \cdot 10^{-6}) = 0.9375 \text{ mJ}$$

$$\textcircled{4} \quad \frac{1}{2} (1000)(0.5 \cdot 10^{-6}) = 0.25 \text{ mJ}$$

$$\text{total } 4.1 \text{ mJ} = E_{\text{on}}$$




each cycle  
at  $t_{\text{DN}}$

$$\frac{\text{Total } E_{\text{on}} + E_{\text{off}}}{E_{\text{DN}}} = 3.1 \text{ mJ}$$

(any estimate near this value is OK)

# Digital DC losses Buck are f(D)

Buck converter model: conduction loss

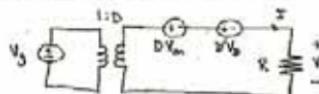

$$V_b = 400 \text{ V}$$

$$V = 200 \text{ V}$$

$$I = 10 \text{ A}$$

$$R = 2 \Omega$$

$$V_m = 2.5 \text{ V}$$

$$V_d = 1.5 \text{ V}$$

$$V = DV_g - DV_m - D'V_d$$

$$\Rightarrow V + V_d = D(V_g - V_m + V_d)$$

$$\Rightarrow D = \frac{V + V_d}{V_g - V_m + V_d} = 0.505$$

Element

	<u>power loss</u>
IGBT	$IDV_m = 12.6 \text{ W}$
diode	$ID'V_d = 7.4 \text{ W}$
total	$\frac{20 \text{ W}}{20 \text{ W}} = P_{loss}$

} DC loss both switches

c) Converter efficiency =  $\frac{P_{out}}{P_{in}}$  with  $P_{out} = (200 \text{ V})(10 \text{ A}) = 2000 \text{ W}$


$$P_{in} = P_{out} + P_{loss} = P_{out} + P_{load} + E_{sw}f_{sw}$$

$$\Rightarrow \eta = \frac{P_{out}}{P_{out} + P_{load} + E_{sw}f_{sw}} = \frac{2000}{2000 + 20 + (2 \cdot 10^3) f_{sw}}$$

Plot on next page

$$\text{From Eq. (123): } f_{crit} = \frac{200}{6.1 \cdot 3} = 2.5 \text{ kHz}$$

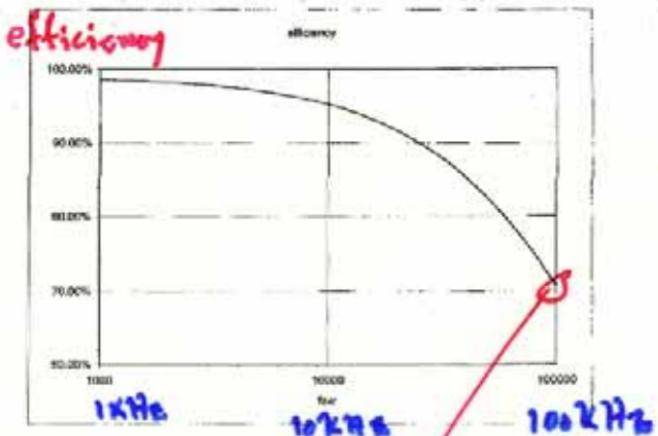Problem 4.7, part (a)  
Efficiency vs. switching frequency




30% heat loss

280V In, 400V<sub>OUT</sub>, 13A, Duty = 30%  
150 kHz

$P_{off} \uparrow$   
due to  
slow iL  
turn off

$P_{on}$   
 $I_{on} V_{CE}$

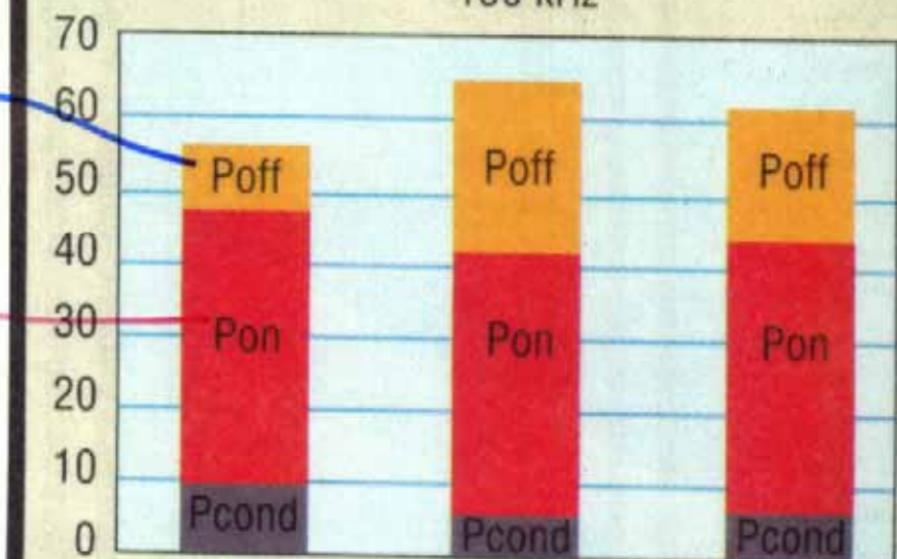


APT5010B2LL APT30GP60B Super-junction

Fig. 7. Total switch losses, 13A, 30% duty.

# $R_{DS(on)}$ Origins in Si Technology

$R_{DS(on)} \sim$   
 $D_S$   
 $10 - 100 \text{ m}\Omega$

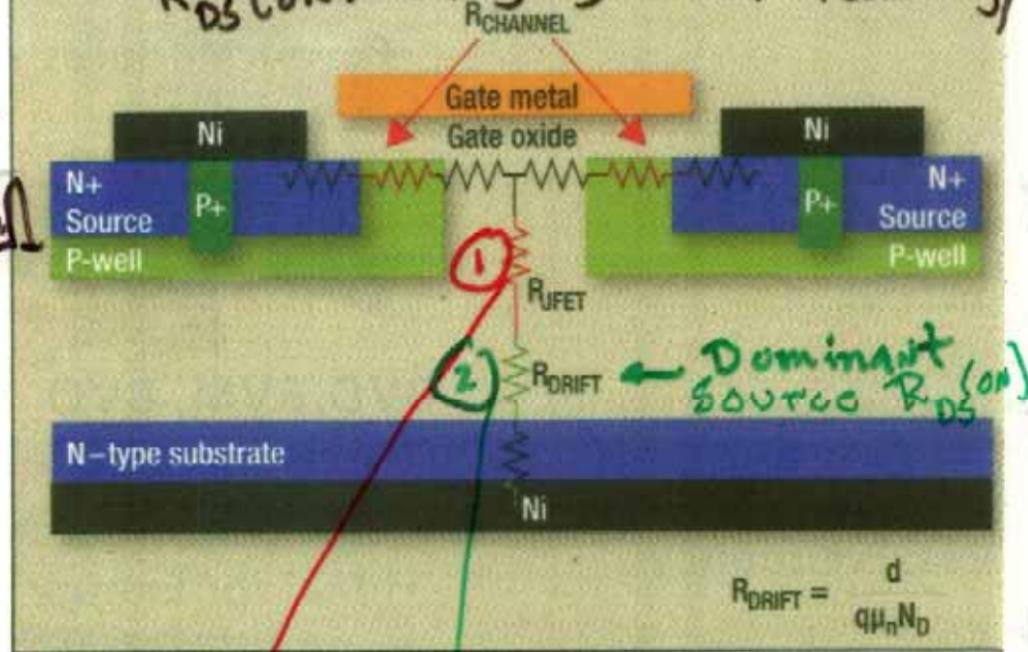

**Fig. 1.** Cross-section of DMOSFET power transistor shows resistive components: the channel resistance, the inherent JFET resistance and the drift resistance that combine to produce a relatively high on-resistance.

*SiC*  
 $R_{on}(I)$   
 $\approx \frac{1}{10} R_{on}$   
for Si

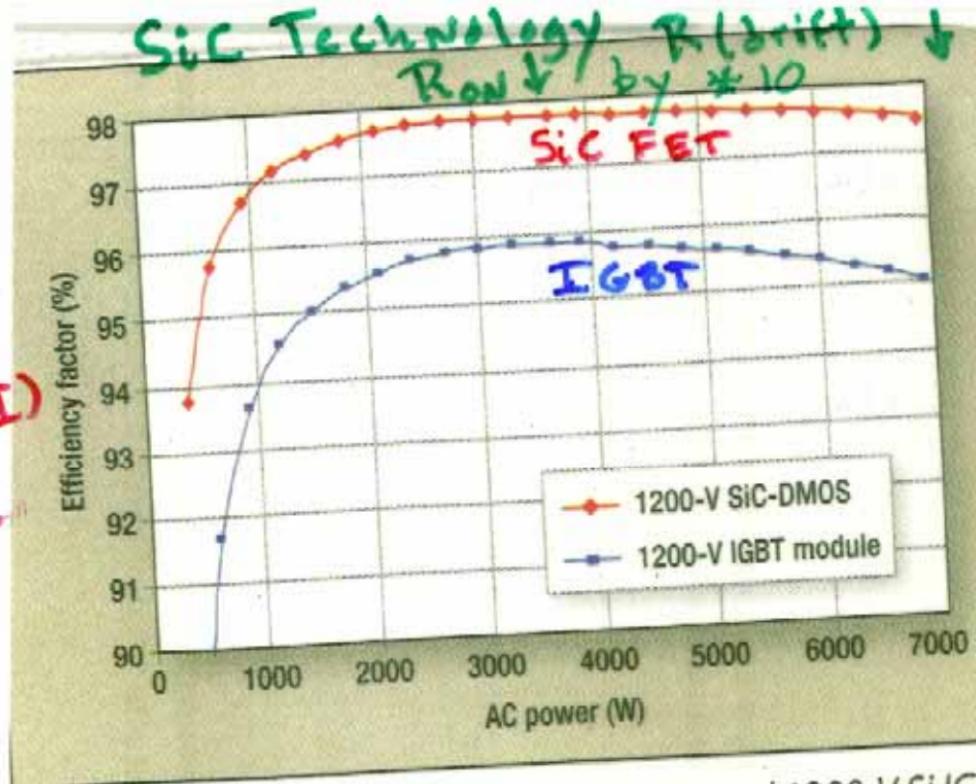



Fig. 2. Comparison of 1200-V SiC DMOSFET and 1200-V Si IGBT efficiencies in a three-phase inverter shows that at the same voltage rating, the higher-efficiency SiC DMOSFETs provide a ... than their Si IGBT counterparts.<sup>[3]</sup>

	E IGBT, 1200-V Infineon BSM 15GD 120 DN2 $I_D$ (max.) = 15 A at 80°C	SiC DMOSFET, 1200-V CREE engineering sample $I_D$ (max.) = 10 A at 25°C to 150°C
$V_{DS}$	600 V	800 V
Load	Inductive	Inductive ( $L_L = 500 \mu H$ )
$V_{GE}$	15 V	0 V/15 V
$R_G$	82 Ω	10 Ω
$E_{ON}$ at $I_D = 10$ A	1.6 mJ	0.8 mJ
$E_{OFF}$ at $I_D = 10$ A	1.0 mJ	0.34 mJ


Wow  
\* 8

Table 1 Switching loss comparison [2]

SiC at (tail) turn-off  $\approx \frac{1}{2}$  Si at (tail)

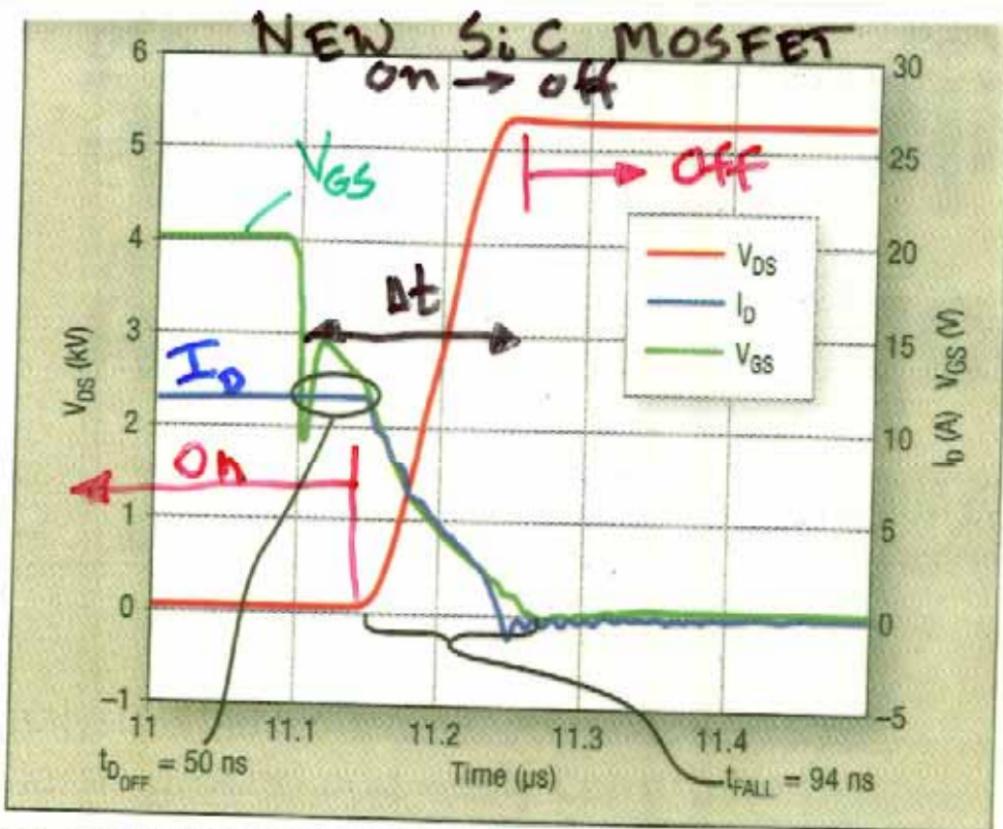

**Fig. 6.** A 10-kV SiC MOSFET running at 20 kHz and dissipating 600 W exhibited about 1.5-μs drain current turn-off transient.<sup>[6]</sup>

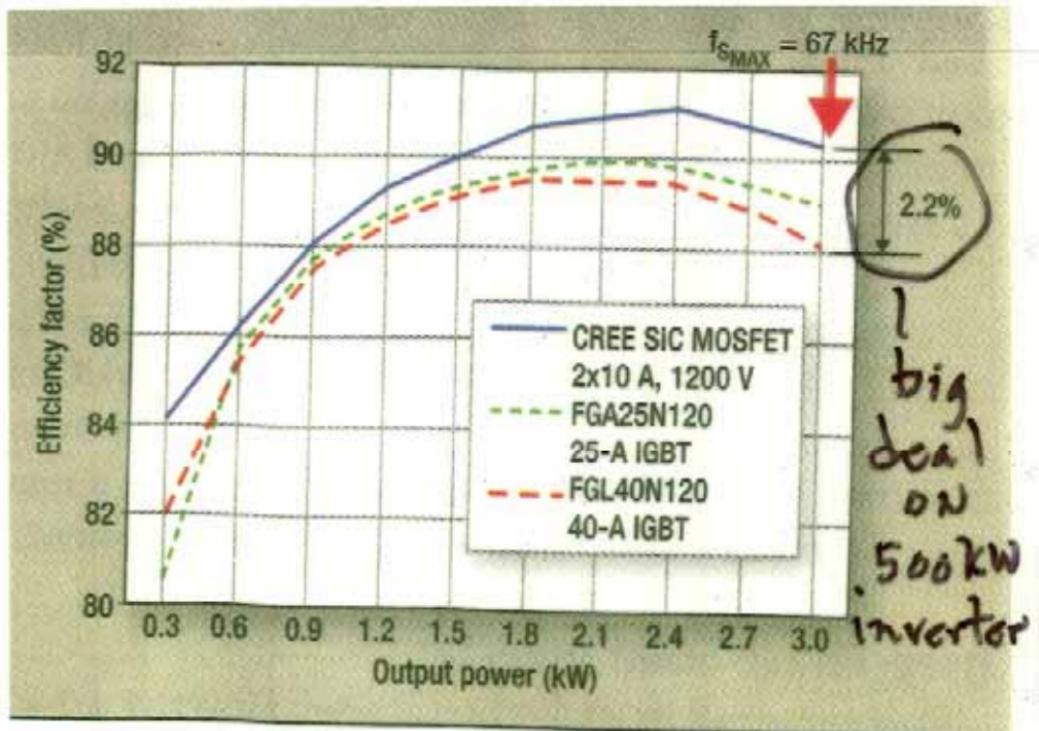

1.4. Efficiency profile comparison at 67 kHz shows a higher efficiency at 3-kW output and throughout the entire id curve, as well as a case-temperature reduction with the MOSFETs relative to the IGBTs [5]



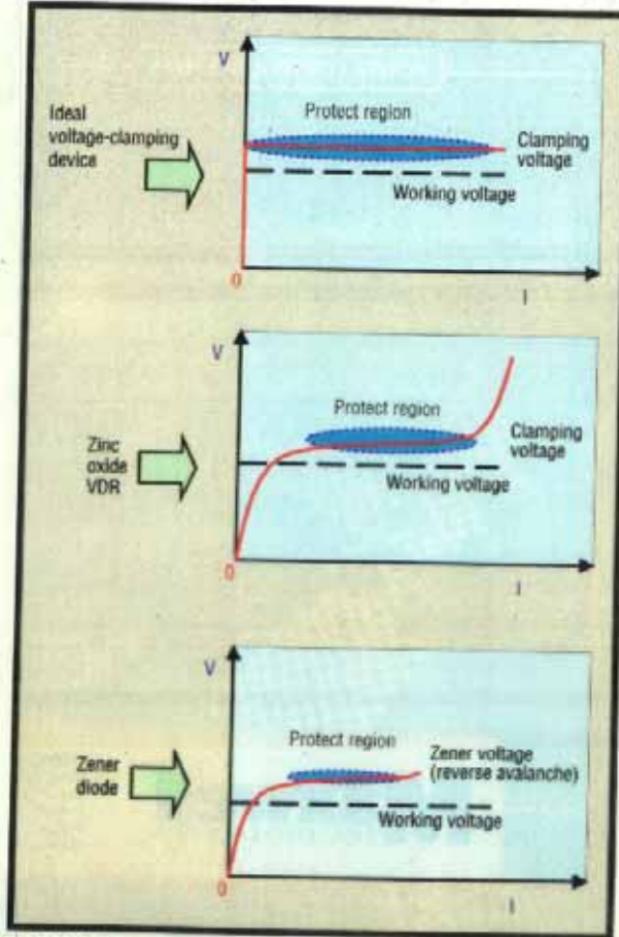



Fig. 1.  $V$ - $I$  behavior of a varistor.

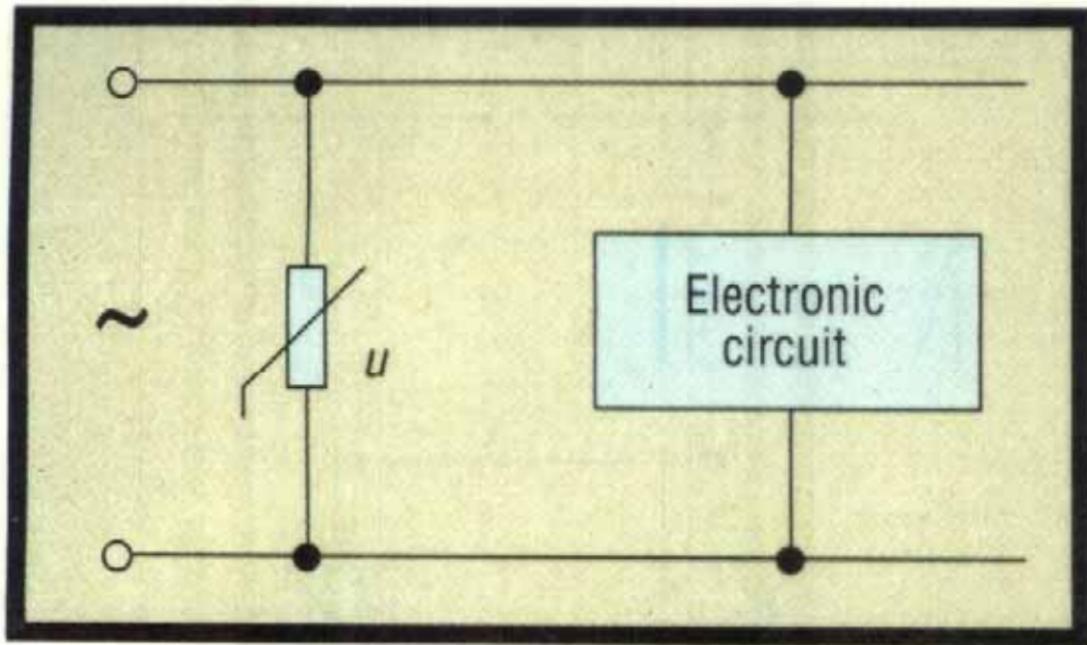

**Fig. 4.** Suppression directly across mains.

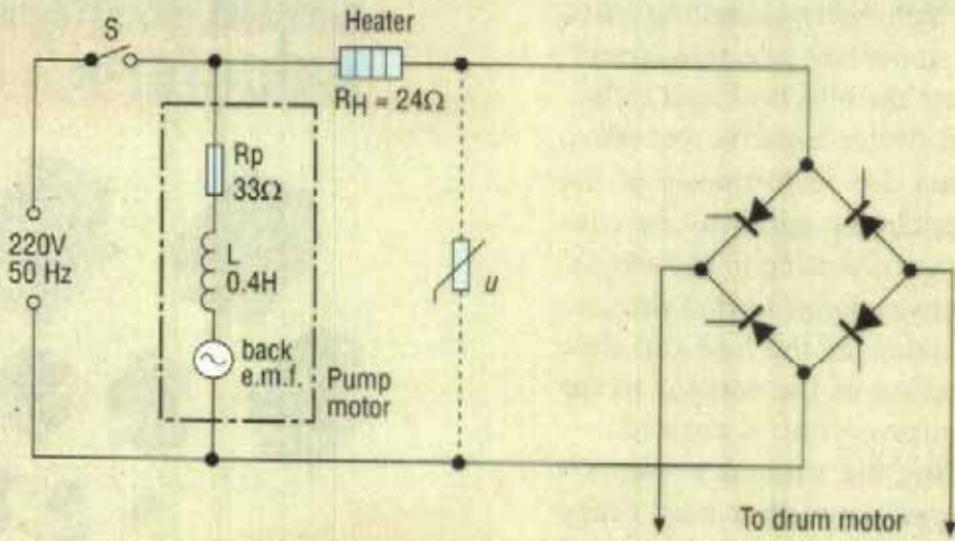

**Fig. 5.** Protection of a thyristor bridge in a washing machine.

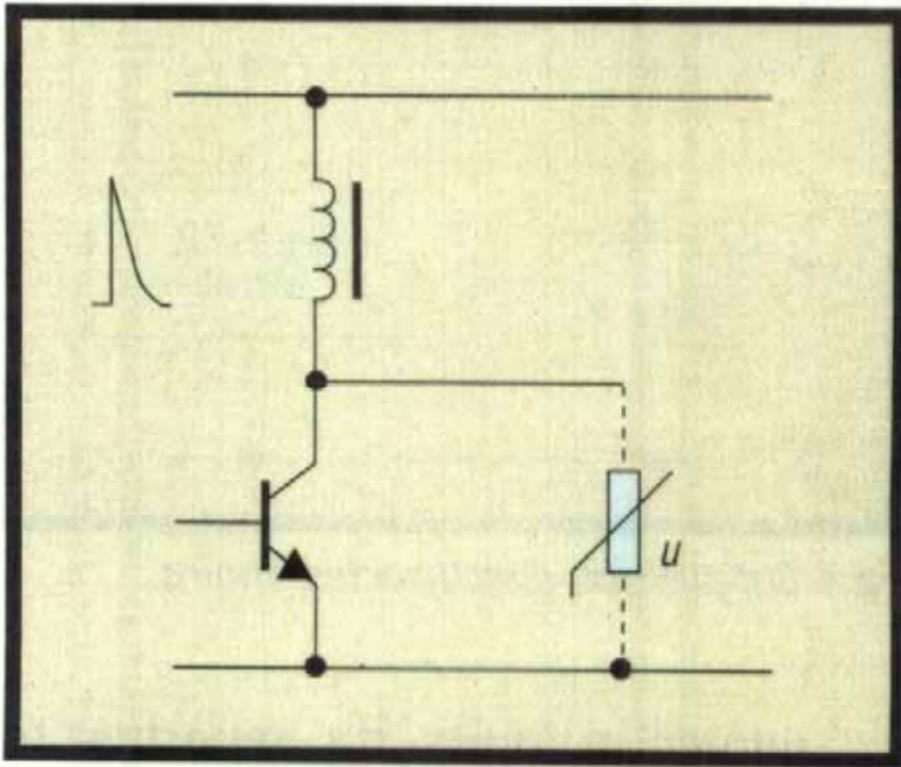

**Fig. 6.** Varistors used to suppress internally generated spikes in a TV application.